
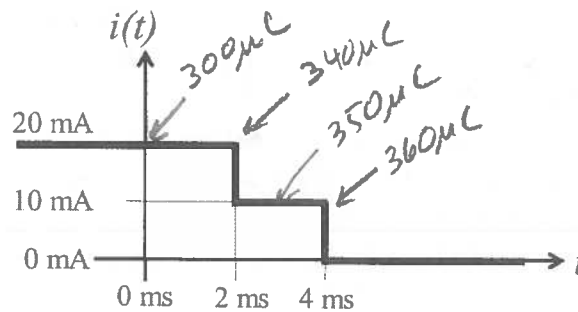


LAST NAME _____ MCGILL ID# _____

FIRST NAME _____ SIGNATURE _____

- Only Faculty standard calculator accepted
- No cellphone allowed
- Show all your work
- Clearly indicate your final answer with the SI unit and multiplier
- You have 45 minutes to complete this quiz

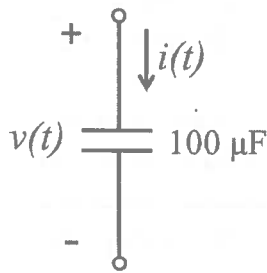Question 1: Consider the $100\ \mu\text{F}$ capacitor ($C = 100\ \mu\text{F}$) shown below along with the diagram illustrating the current $i(t)$ flowing through the capacitor. A constant current of $20\ \text{mA}$ flows through the capacitor up to time $t = 2\ \text{ms}$. At that time $t = 2\ \text{ms}$, the current drops to $10\ \text{mA}$ until time $t = 4\ \text{ms}$. For $t > 4\ \text{ms}$, the current is $0\ \text{A}$. The capacitor is initially charged at $t = 0\ \text{ms}$ and has a voltage of $3\ \text{V}$ across it. Answer the following questions.



- At what time t will the capacitor have a charge separation of $350\ \mu\text{C}$ ($q = 350\ \mu\text{C}$)? [2 pt]
- What is the instantaneous power at $t = 1\ \text{ms}$? [2 pt]
- What is the energy stored as electric potential energy $U(t)$ in the capacitor at time $t = 5\ \text{ms}$? [2 pt]

$$a) \quad v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau \quad \text{and} \quad q = Cv \quad \text{and} \quad i = \frac{dq}{dt}$$

$$\text{at } t = 0\ \text{ms} \quad q(0) = 100\ \mu\text{F} \cdot 3\ \text{V} = 300\ \mu\text{C}$$

$$\text{at } t = 2\ \text{ms} \quad v(2\ \text{ms}) = 3\ \text{V} + \frac{1}{100\ \mu\text{F}} \int_0^{2\ \text{ms}} 20\ \text{mA} dt = 3\ \text{V} + \frac{20\ \text{mA} \cdot 2\ \text{ms}}{100\ \mu\text{F}} = 3.4\ \text{V}$$

$$q(2\ \text{ms}) = 100\ \mu\text{F} \cdot 3.4\ \text{V} = 340\ \mu\text{C}$$

$$\text{at } t = 4\ \text{ms} \quad v(4\ \text{ms}) = 3.4\ \text{V} + \frac{1}{100\ \mu\text{F}} \int_{2\ \text{ms}}^{4\ \text{ms}} 10\ \text{mA} dt = 3.4\ \text{V} + \frac{10\ \text{mA} \cdot 2\ \text{ms}}{100\ \mu\text{F}} = 3.6\ \text{V}$$

$$q(4\ \text{ms}) = 360\ \mu\text{C}$$

$$t - 2\ \text{ms}: \frac{q - Cv(2\ \text{ms})}{i} = \frac{350\ \mu\text{C} - 340\ \mu\text{C}}{10\ \text{mA}} = 1\ \text{ms}$$

$$\boxed{t = 3\ \text{ms}}$$


$$b) \quad p(t) = i(t) \cdot v(t) \quad v(1\ \text{ms}) = 3\ \text{V} + \frac{1}{100\ \mu\text{F}} \int_0^{1\ \text{ms}} 20\ \text{mA} d\tau = 3\ \text{V} + \frac{20\ \text{mA} \cdot 1\ \text{ms}}{100\ \mu\text{F}} = 3.2\ \text{V}$$

$$p(1\ \text{ms}) = 20\ \text{mA} \cdot 3.2\ \text{V} = \boxed{64\ \text{mW}}$$

$$c) \quad \text{for } t > 4\ \text{ms}, i(t) = 0 \quad v(5\ \text{ms}) = 3.6\ \text{V} + 0 \rightarrow U(5\ \text{ms}) = \frac{1}{2} 100\ \mu\text{F} (3.6\ \text{V})^2$$

$$\boxed{U = 648\ \mu\text{J}}$$

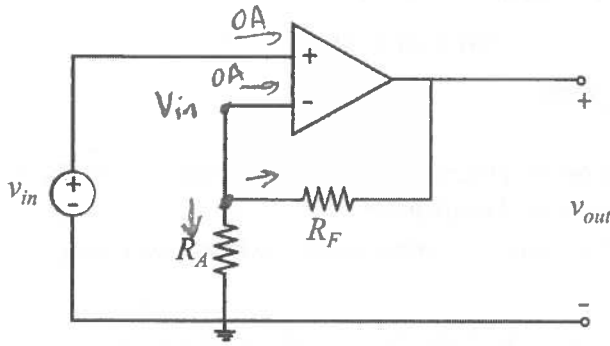Question 2: The circuit shown below is a common operational amplifier (op-amp) circuit. Answer the following questions.



a) $\frac{V_{in}}{R_A} + \frac{V_{in} - V_{out}}{R_F} = 0$ (KCL at inv. node)

$$V_{out} = V_{in} \left(1 + \frac{R_F}{R_A} \right)$$

$$\boxed{\frac{V_{out}}{V_{in}} = 1 + \frac{R_F}{R_A}}$$

- Using the ideal op-amp model, derive the expression for the voltage gain v_{out}/v_{in} as a function of the two resistors R_A and R_F . [1 pt]
- The op-amp circuit above is configured as a non-inverting amplifier. Using the ideal op-amp model, the voltage gain is $v_{out}/v_{in} = 1 + R_F/R_A$ as you found in part a). Choose resistance values for resistors R_A and R_F to design the op-amp circuit such that the voltage gain is $+8 \text{ V/V}$ and the total power absorbed by the two resistors is $500 \mu\text{W}$ when $v_{out} = 2 \text{ V}$. [2 pt]
- Using the practical op-amp circuit model simplified by setting the input resistance to infinity ($R_i \rightarrow \infty$) and the output resistance to zero ($R_o = 0 \Omega$), what is the output voltage value v_{out} if $R_A \rightarrow \infty$, $R_F \rightarrow 0 \Omega$, $v_{in} = 5 \text{ V}$, and the open-loop gain A is 15 V/V ? [2 pt]
- In the circuit described in part c), what is the output voltage value v_{out} using the ideal op-amp model? [1 pt]

b) $\frac{V_{out}}{V_{in}} = 1 + \frac{R_F}{R_A} = +8 \text{ V/V} \rightarrow \frac{R_F}{R_A} = 7 \therefore R_F = 7R_A$ & $V_{in} = \frac{1}{8} V_{out} = \frac{1}{8} \cdot 2 \text{ V} = 0.25 \text{ V}$


$$P_{R_A} = V_{in} \cdot \frac{V_{in}}{R_A} = \frac{V_{in}^2}{R_A} \quad P_{R_F} = (V_{in} - V_{out}) \cdot \frac{(V_{in} - V_{out})}{R_F} = \frac{(V_{in} - V_{out})^2}{R_F}$$

$$P_{tot} = P_{R_A} + P_{R_F} = \frac{(0.25 \text{ V})^2}{R_A} + \frac{(0.25 - 2 \text{ V})^2}{7R_A} = 500 \times 10^{-6}$$

$$\frac{0.4375 + 3.0625}{7R_A} = 500 \times 10^{-6}$$

$$\boxed{R_A = 1 \text{ k}\Omega}$$

$$\boxed{R_F = 7 \text{ k}\Omega}$$

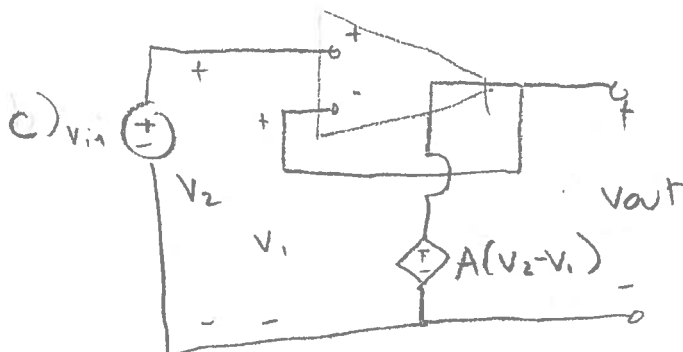

$$V_{out} = A(V_2 - V_1)$$

$$V_2 = V_{in} \quad V_1 = V_{out}$$

$$V_{out} = A(V_{in} - V_{out}) \rightarrow V_{out} = \frac{A}{A+1} V_{in}$$

$$V_{out} = \frac{15 \text{ V/V} \cdot 5 \text{ V}}{15 \text{ V/V} + 1} = \boxed{4.6875 \text{ V}}$$

d) $V_{out} = V_{in}$ $\boxed{V_{out} = 5 \text{ V}}$