

## 4. Circuit Theorems

- Source Transformations
- Linearity and the Principle of Superposition
- Thévenin's Theorem
- Norton's Theorem
- Maximum Power Transfer Theorem

# Motivation

- Circuit theorems can greatly simplify circuit analysis and provide insight into the operation of circuits
- For example: What are the consequences of a circuit being composed of linear circuit elements?

# Today's Outline

## **4. Circuit Theorems**

- Practical Sources
- Source Transformations

# Practical Sources



It is commonly observed in practical sources that:

- power is dissipated when a load is attached to the source (for example, a battery warms up when discharged)
- the voltage from a practical voltage source decreases as current is drawn from the source (as from an audio amplifier)
- the current from a practical current source decreases as voltage develops across the terminals of the source (as from a solar cell)

While the origin and nature of these effects can be very complex, the Thévenin and Norton equivalent circuits are very useful models for practical sources.

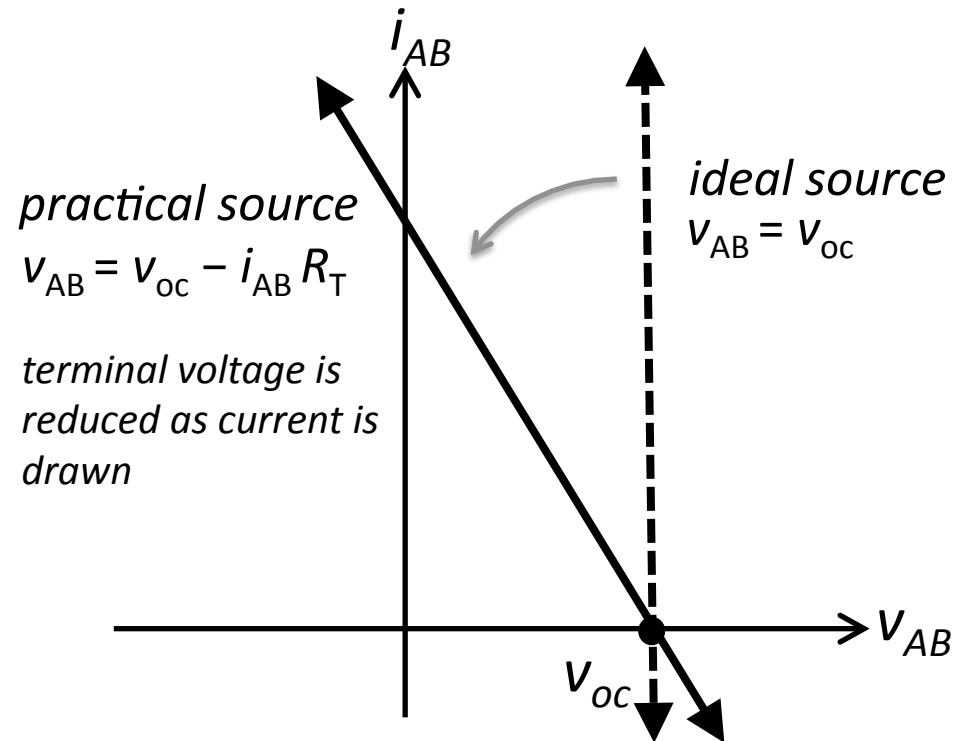
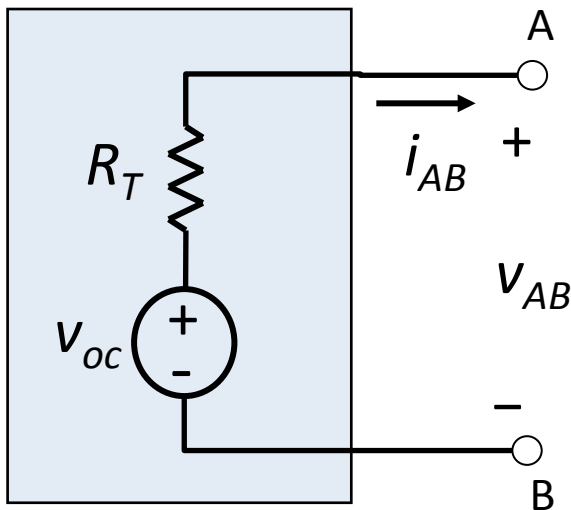
# Practical Voltage Source

A practical voltage source can often be modeled as a **Thévenin circuit**: a voltage source  $v_{oc}$  called the “**open circuit voltage**” in series with a resistance  $R_T$ , called the “**Thévenin resistance**.” An ideal voltage source is recovered as  $R_T \rightarrow 0\Omega$  (short).



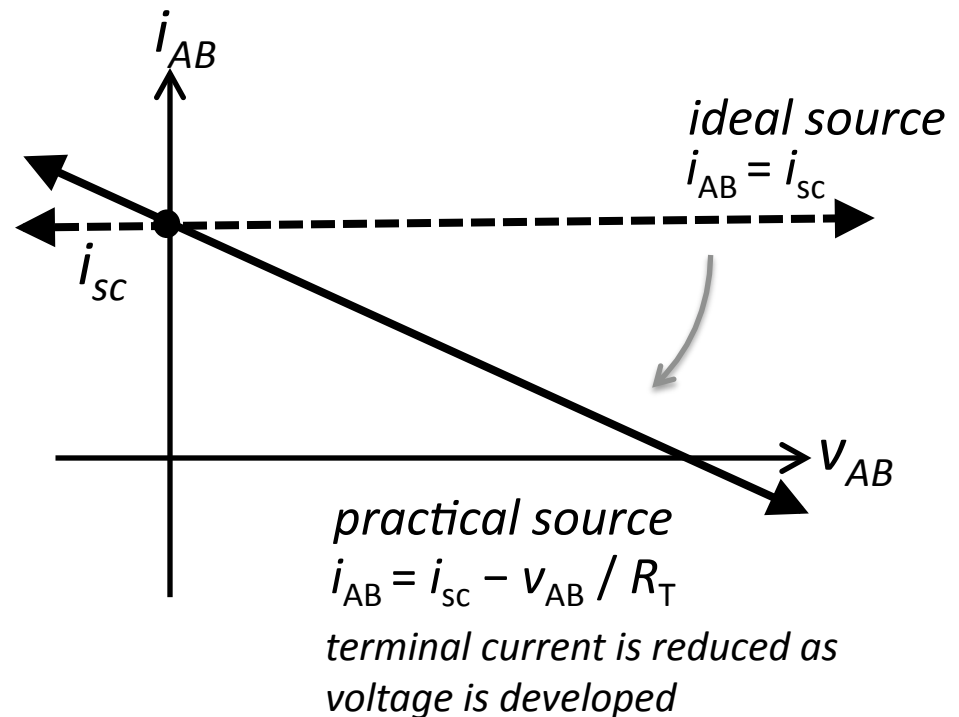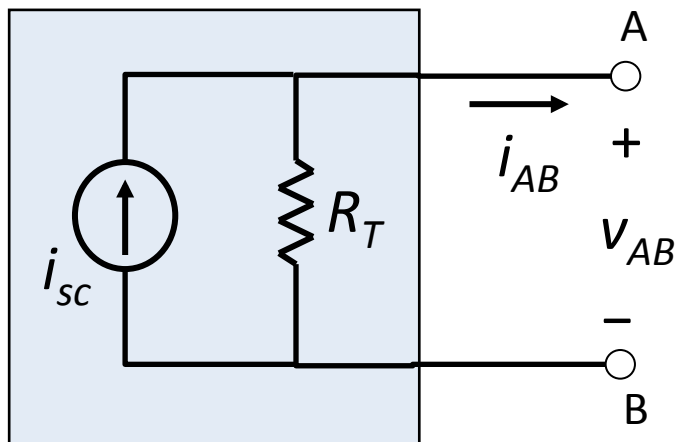
# Practical Current Source

A practical current source can often be modeled as a **Norton circuit**: an independent current source  $i_{sc}$  called the “**short circuit current**” in parallel with a resistance  $R_T$  also called the “**Thévenin resistance**.” An ideal current source is recovered as  $R_T \rightarrow \infty$  (open).


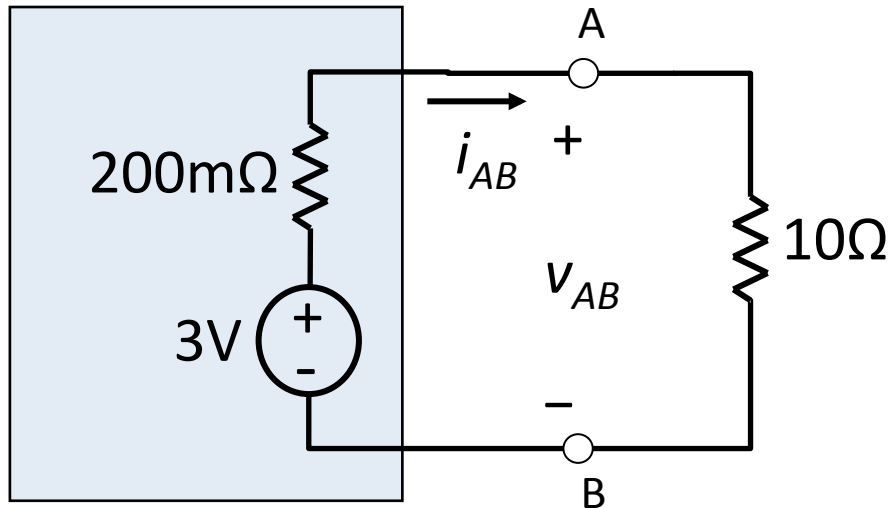
# Example 1


A portable battery is characterized by an open circuit voltage of 3V. The internal (Thévenin) resistance is known to be  $200\text{m}\Omega$ . If a resistive load with  $10\Omega$  equivalent resistance is attached to the battery, what voltage is applied to the load?



Strategy:

- apply the voltage divider equation

# Example 1

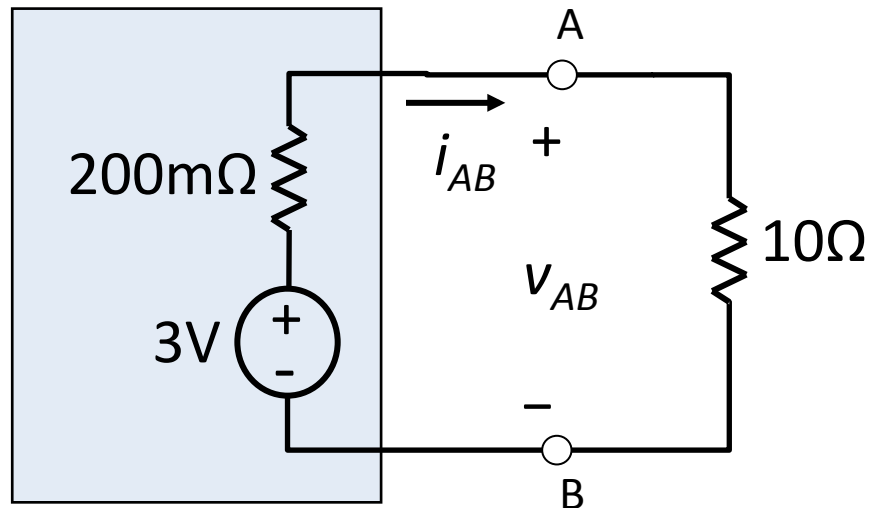

Voltage divider:

$$\frac{V_{AB}}{3V} = \frac{10\Omega}{10\Omega + 0.2\Omega}$$

$$V_{AB} = 0.980 \cdot 3V$$


$$= 2.94V$$

this is a 2% drop in voltage


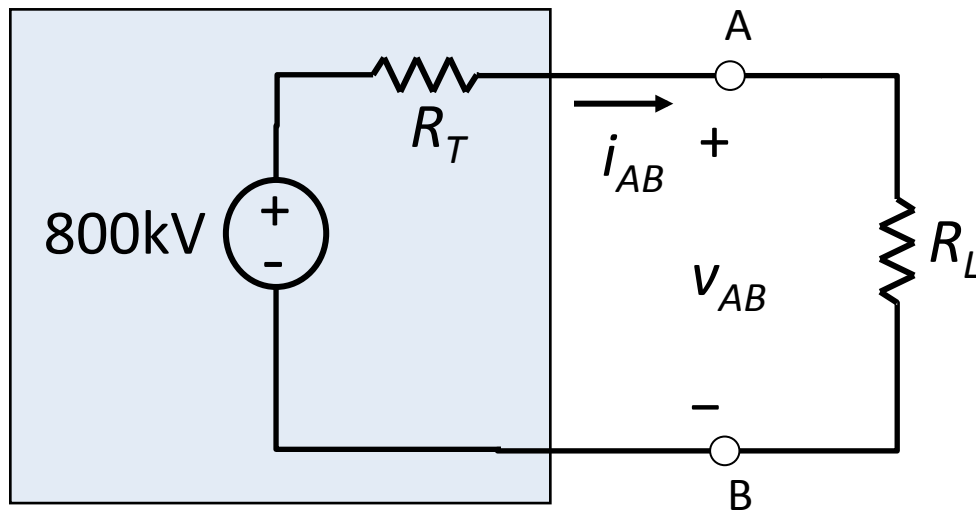
## Example 2


An HVDC (high-voltage direct-current) power supply line is driven by an 800kV source with  $2\Omega$  internal resistance. Of the total 5GW produced by the HVDC source, 10% of the power is lost in internal resistance, including a 3000km transmission line to the load. What is the resistance of the load, the resistance of the transmission lines, and the voltage at the load?



Strategy:

- use power and voltage to find resistance

## Example 2

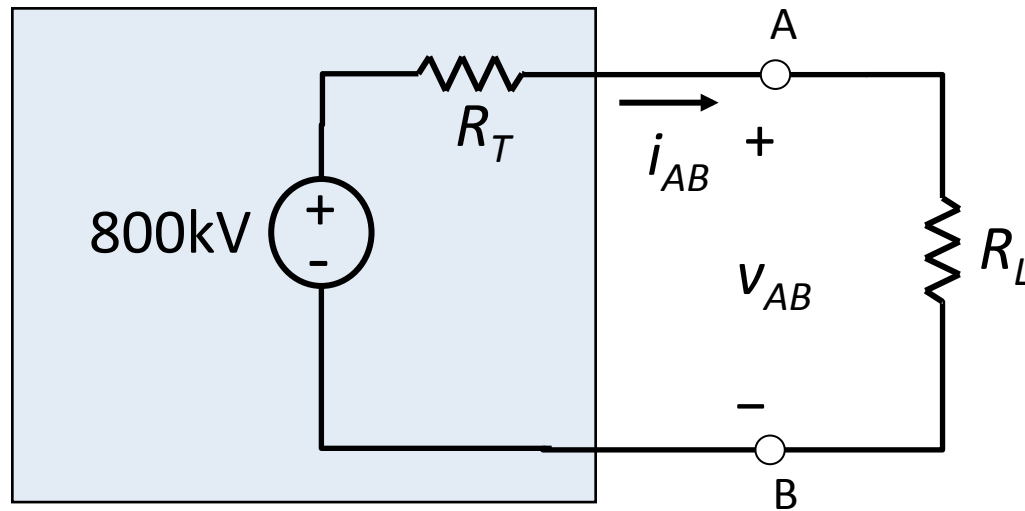

$$P_{del} = i_{AB} \cdot 800\text{kV}$$

$$i_{AB} = \frac{5\text{GW}}{800\text{kV}} = 6.25\text{kA}$$

$$P_{load} = i_{AB}^2 \cdot R_L$$

$$R_L = \frac{0.9 \times 5\text{GW}}{(6.25\text{kA})^2}$$


$$= 115.2\Omega$$

$$P_{internal} = i_{AB}^2 \cdot R_T$$

$$R_T = \frac{0.1 \times 5\text{GW}}{(6.25\text{kA})^2}$$

$$= 12.8\Omega$$

## Example 2

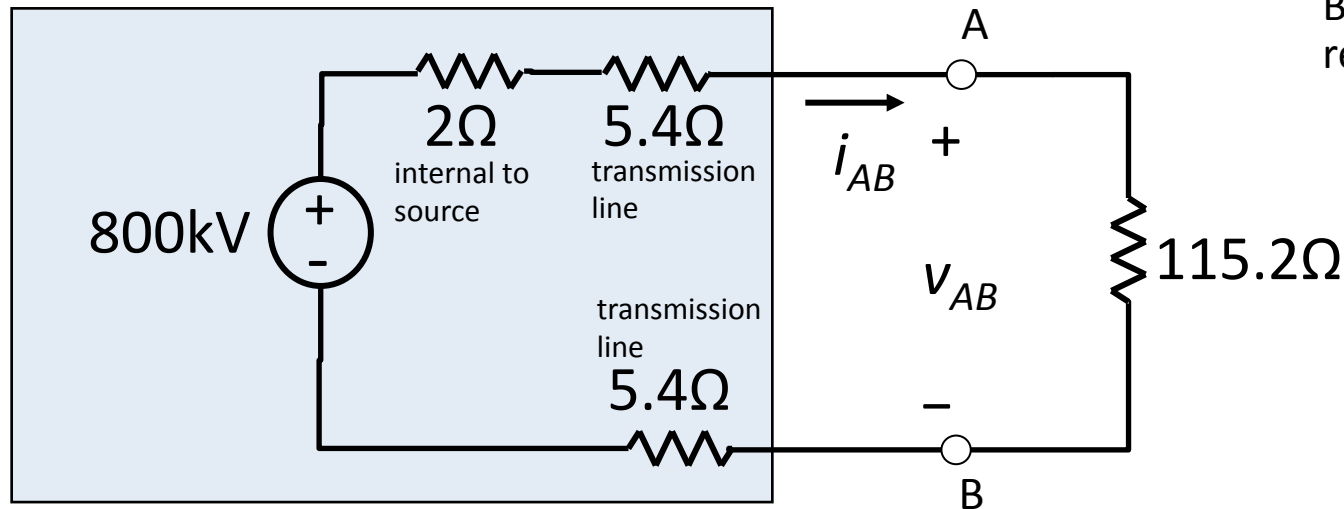

Breakdown of internal resistance contributions:

$$\begin{aligned}
 R_T &= R_{\text{source}} + 2R_{\text{line}} \\
 &= 2\Omega + 2R_{\text{line}} \\
 R_{\text{line}} &= \frac{12.8 - 2\Omega}{2} \\
 &= 5.4\Omega
 \end{aligned}$$

Voltage divider:





$$\begin{aligned}
 \frac{V_{AB}}{800\text{kV}} &= \frac{115.2\Omega}{12.8\Omega + 115.2\Omega} \\
 V_{AB} &= 0.900 \cdot 800\text{kV} \\
 &= 720\text{kV}
 \end{aligned}$$

this is a 10% drop in voltage

# Source Transformation

**Source Transformation:** A Thévenin circuit and a Norton circuit are equivalent when their  $i_{AB}$ - $v_{AB}$  diagrams are identical:


$$v_{oc} = i_{sc} R_T$$

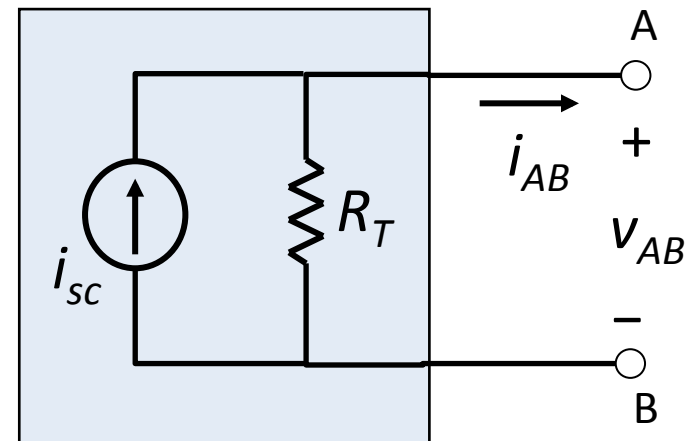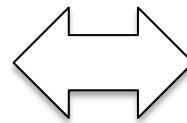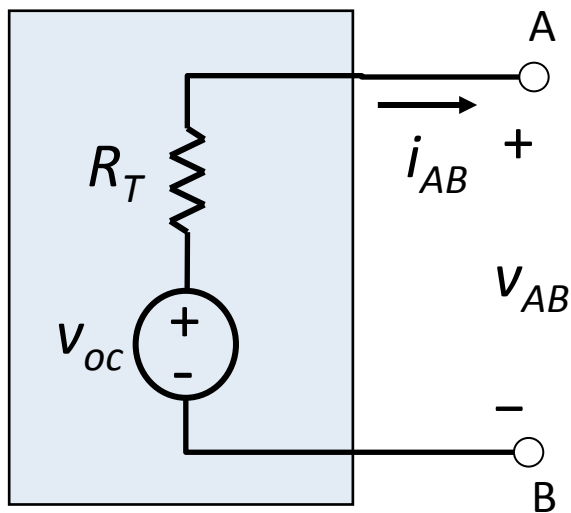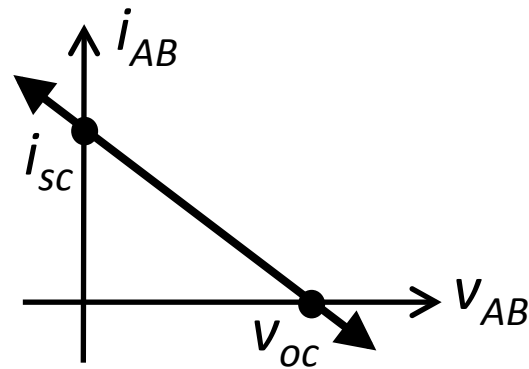

# Source Transformation

**Proof:** Show that the terminal equations relating  $v_{AB}$  and  $i_{AB}$  are identical for appropriately chosen component values. In other words, the  $i_{AB}$ - $v_{AB}$  diagrams are identical.

First analyze the Thévenin circuit:

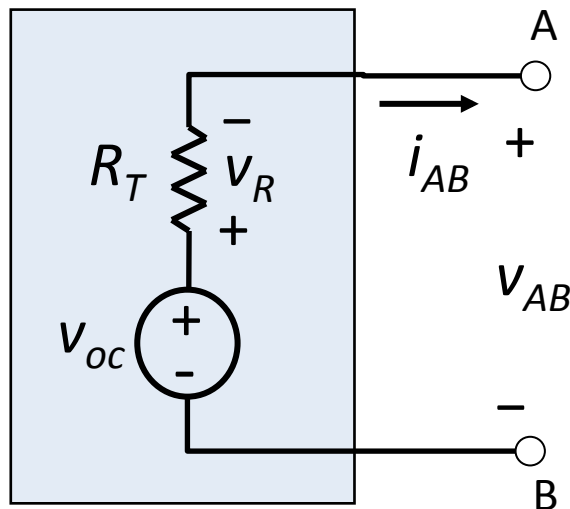

$$\text{KVL: } 0 = -v_{oc} + v_R + v_{AB}$$


$$\text{Ohm: } v_R = i_{AB} R_T$$

Combining the above:

$$v_{AB} = v_{oc} - i_{AB} R_T$$

# Source Transformation

Next analyze the Norton circuit:

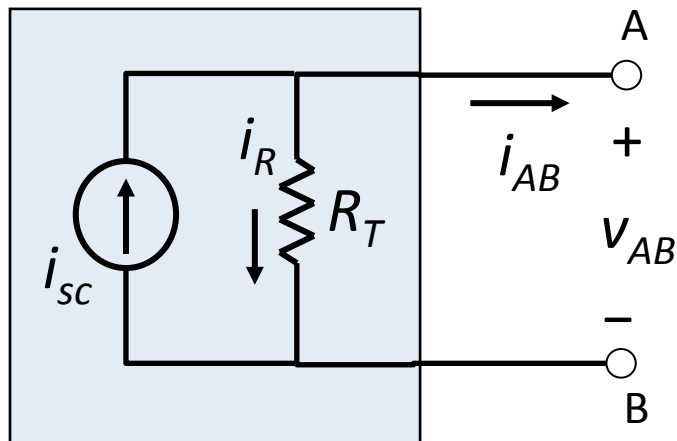

$$\text{KCL: } 0 = -i_{sc} + i_R + i_{AB}$$

$$\text{Ohm: } i_R = v_{AB} / R_T$$


Combining the above:

$$i_{AB} = i_{sc} - v_{AB} / R_T$$

Comparing the two circuit terminal laws:

$$v_{AB} = v_{oc} - i_{AB} R_T$$

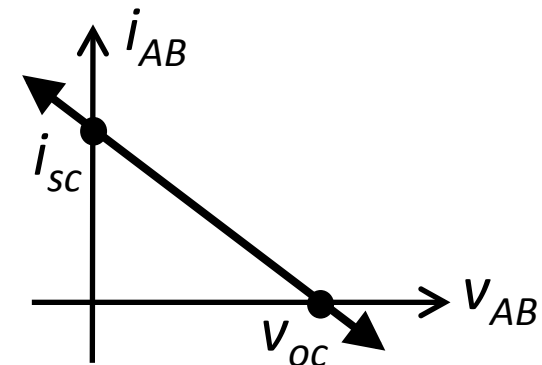
$$i_{AB} = i_{sc} - v_{AB} / R_T \quad \rightarrow \quad v_{AB} = i_{sc} R_T - i_{AB} R_T$$



The two circuits are thus equivalent when  $v_{oc} = i_{sc} R_T$ .
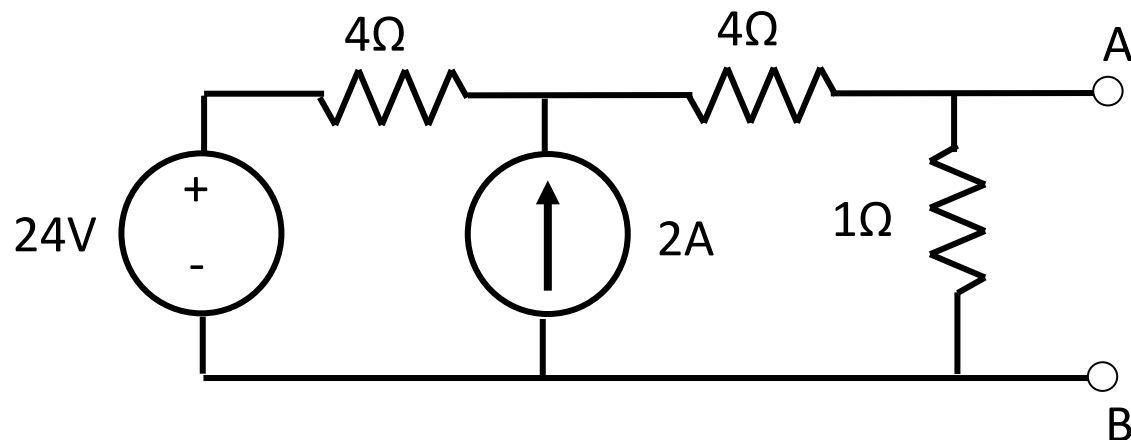
# Example


Reduce the following circuit to a single Norton equivalent circuit with respect to the terminals A and B.



Strategy:


- use transformations between Thévenin and Norton equivalent circuits, working from left to right

## Example

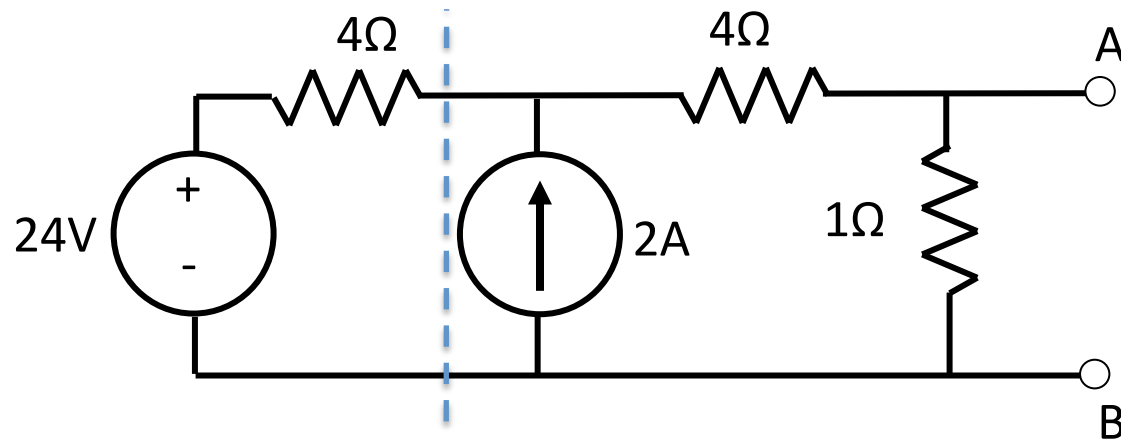


Transform Thévenin circuit on the left into a Norton circuit.
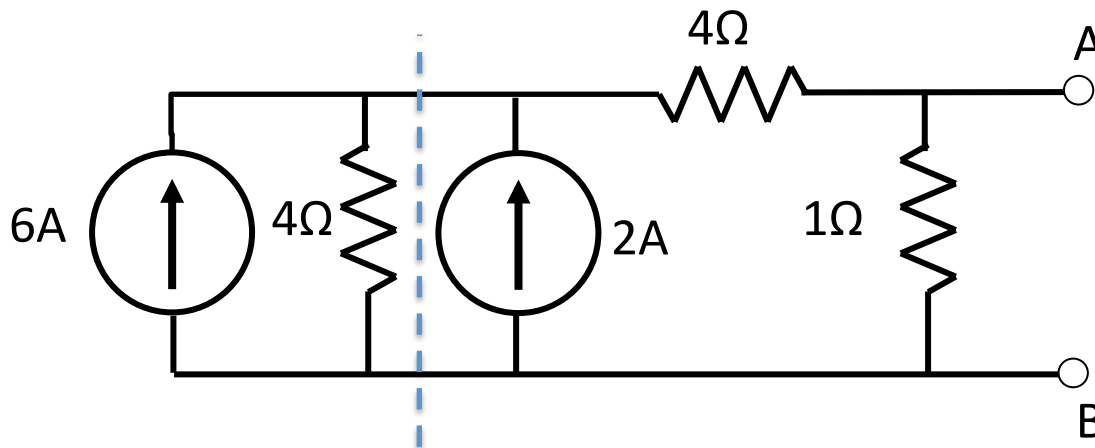
$$\begin{aligned} i_{sc} &= v_{oc} / R_T \\ &= 24V / 4\Omega \\ &= 6A \end{aligned}$$






## Example

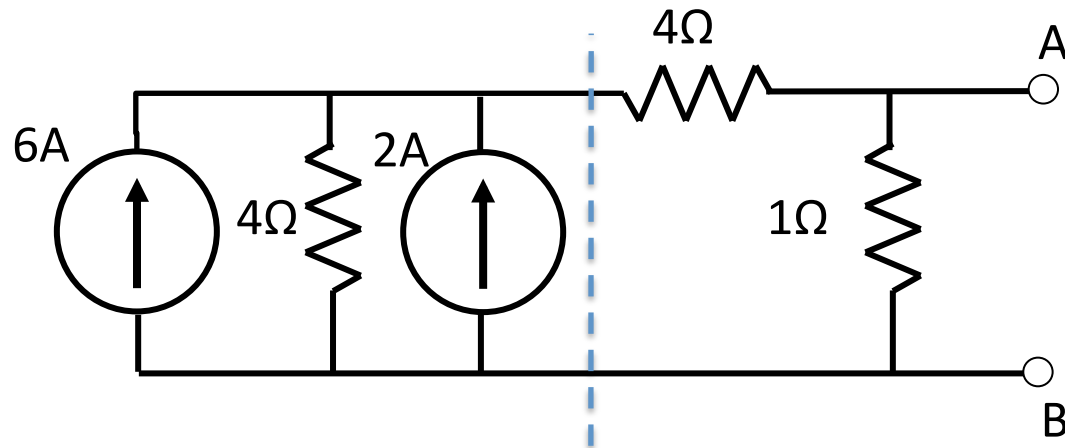


Transform circuit on the left into a Norton circuit.

$$i_{sc} = 2A + 6A = 8A$$

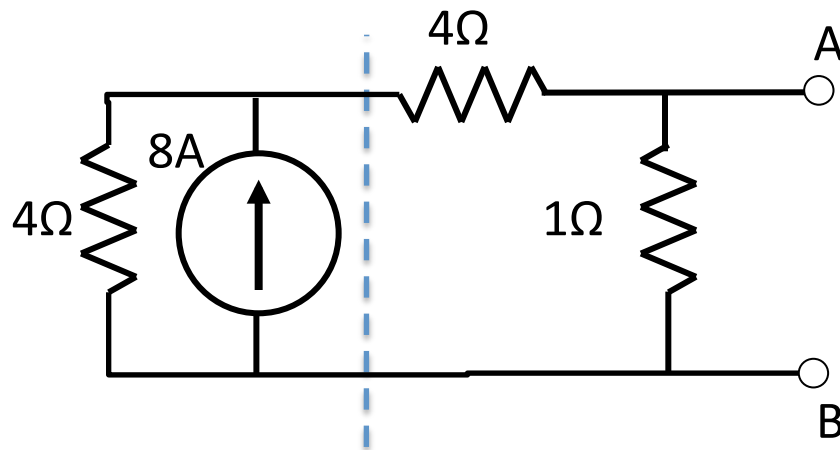


## Example

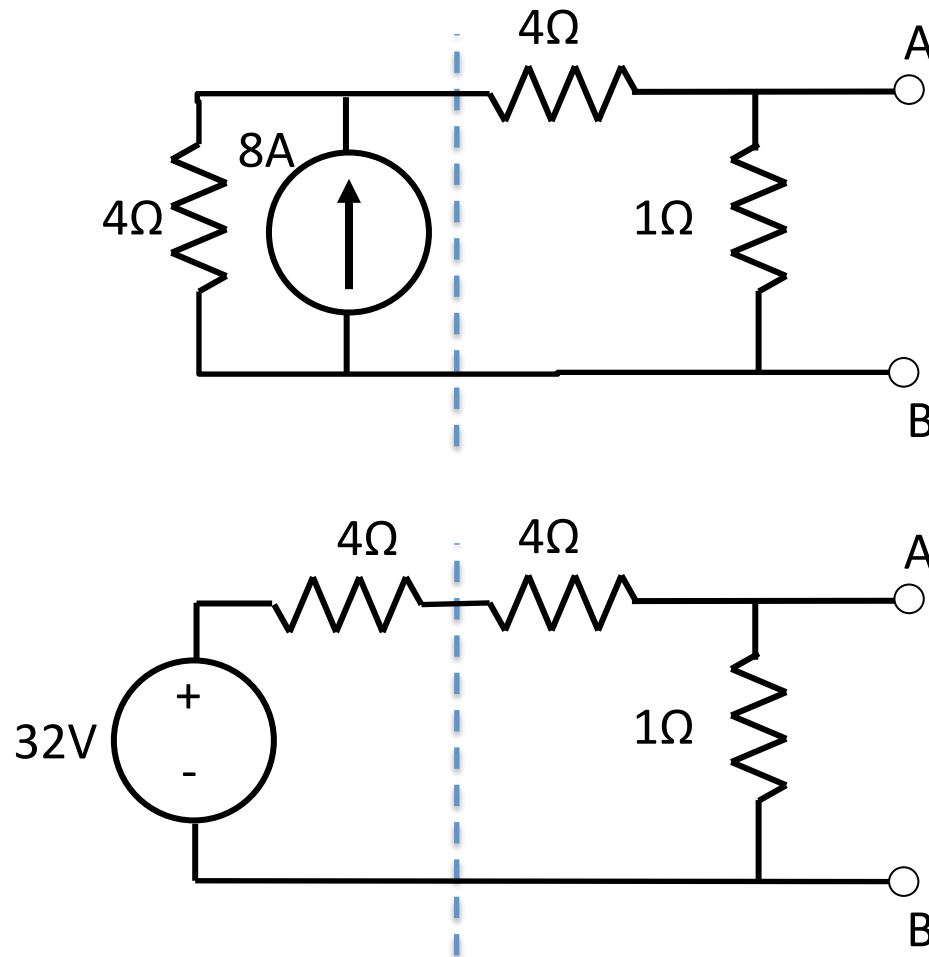


Transform circuit on the left into a Thévenin circuit.

$$\begin{aligned}
 v_{oc} &= i_{sc} R_T \\
 &= 8A \cdot 4\Omega \\
 &= 32V
 \end{aligned}$$

## Example

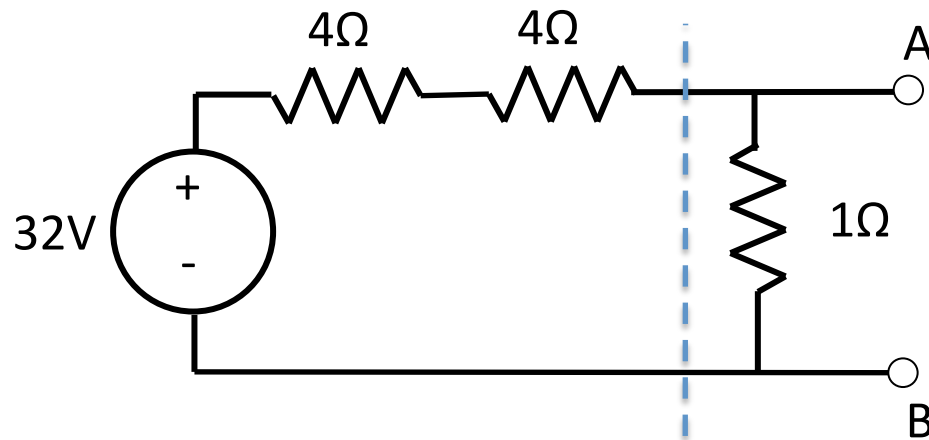

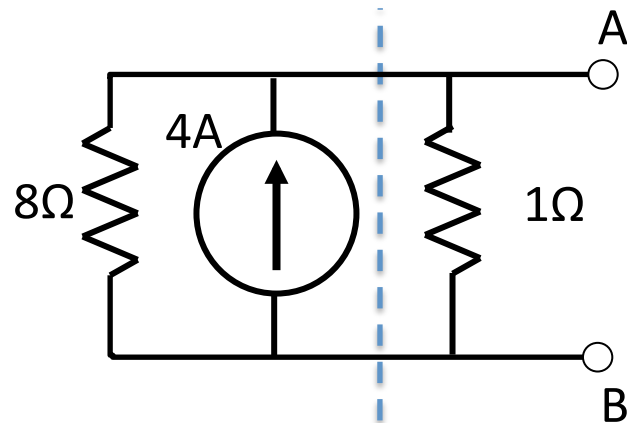
Use series equivalent resistance and transform circuit on the left into a Norton circuit.




$$R_T = 4\Omega + 4\Omega = 8\Omega$$

$$\begin{aligned} i_{sc} &= v_{oc} / R_T \\ &= 32V / 8\Omega \\ &= 4A \end{aligned}$$

## Example

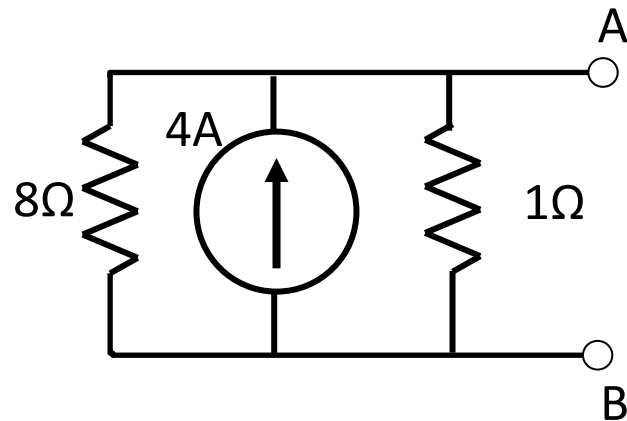

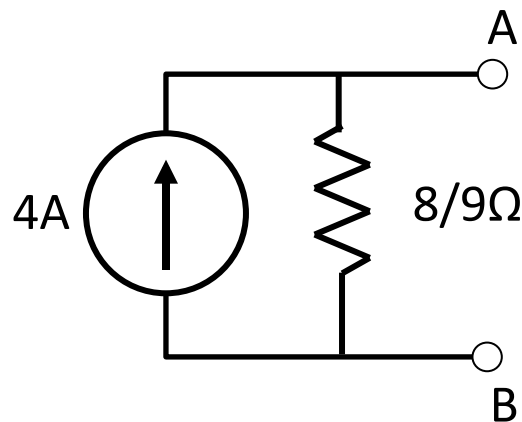Use parallel equivalent resistance to create a Norton circuit.



$$R_T = 8\Omega \parallel 1\Omega$$

$$= \frac{8\Omega \cdot 1\Omega}{8\Omega + 1\Omega} = \frac{8}{9}\Omega$$