

Today's Outline

4. Analysis Methods

- Linearity
- Principle of Superposition

Linearity

Linearity: A function $f(x)$ is **linear** in the argument x if and only if:

$$f(ax + by) = af(x) + bf(y)$$

- To evaluate $f(ax + by)$, we can evaluate $f(x)$ and $f(y)$, and then sum appropriately.
- In some cases, it may be easier to evaluate $f(x)$ and $f(y)$ instead of $f(ax + by)$, for example:

$$f(x) = 2x$$

$$\begin{aligned} f(179) &= f(170) + f(9) \quad [\text{for evaluation without pen or paper}] \\ &= 340 + 18 = 358 \end{aligned}$$

Linearity (more general)

Linearity: An operator $F[x(t)]$ is **linear** in the function $x(t)$ if and only if:

$$F[a x(t) + b y(t)] = a F[x(t)] + b F[y(t)]$$

- To evaluate $F[a x(t) + b y(t)]$, we can evaluate $F[x(t)]$ and $F[y(t)]$, and then sum the appropriately.
- In some cases, it may be easier to evaluate $F[x(t)]$ and $F[y(t)]$ instead of $F[x(t) + y(t)]$, for example:

$$F[x(t)] = \frac{d}{dt} [x(t)]$$

$$\begin{aligned} F[C + D \exp(-kt)] &= F[C] + F[D \exp(-kt)] \\ &= 0 - Dk \exp(-kt) \end{aligned}$$

Linear Circuits


Linear Circuit Element: An element where terminal voltage and current are related to each other by a linear function (or operator). Examples include ideal resistors, dependent sources and ideal op-amps.

Linear Circuit: A circuit composed of independent sources and linear circuit elements.


Any voltage or current variable in a linear circuit can always be described by a linear function (or operator) of other voltage and current variables.

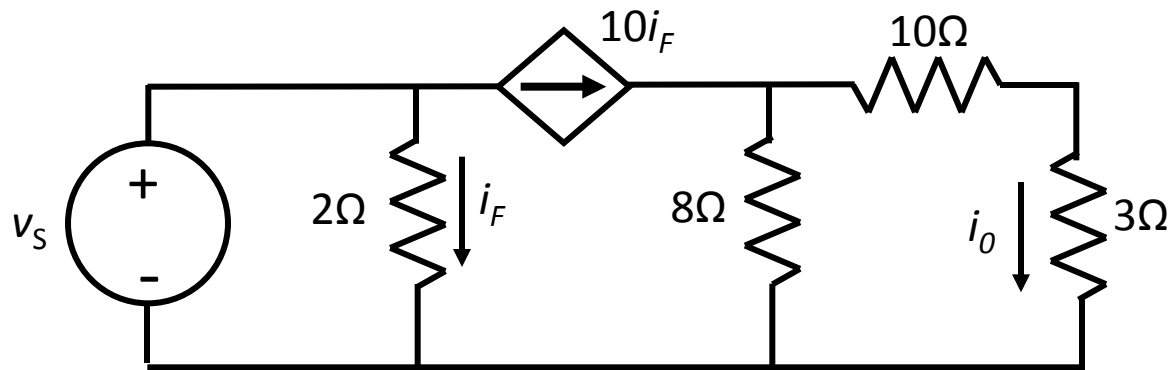Example of Linearity

Verify that the current i_o is a linear function of the voltage source v_s . Is the power dissipated in the 3Ω resistor a linear function of v_s ?



Example of Linearity

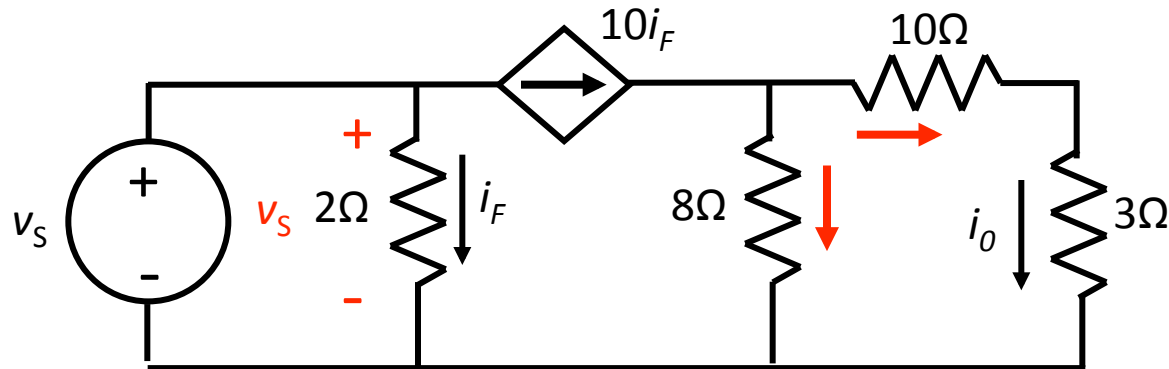

Ohm's Law: $v_s = 2\Omega i_F$

Current Divider:
$$i_o = 10i_F \frac{8\Omega}{8\Omega + (10\Omega + 3\Omega)} = 10 \left(\frac{v_s}{2\Omega} \right) \frac{8\Omega}{21\Omega} = \frac{40}{21} \Omega^{-1} v_s = f(v_s)$$

Power Absorbed:
$$P_{abs} = i_o^2 3\Omega = \left(\frac{40}{21} \Omega^{-1} v_s \right)^2 3\Omega = \frac{1600}{147} \Omega^{-1} v_s^2 = g(v_s)$$

Example of Linearity

Linearity of $i_o = f(v_s)$: $f(ax + by) = \frac{40}{21} \Omega^{-1} (ax + by)$

$$f(x) = \frac{40}{21} \Omega^{-1} x, \quad f(y) = \frac{40}{21} \Omega^{-1} y$$

$$af(x) + bf(y) = a \frac{40}{21} \Omega^{-1} x + b \frac{40}{21} \Omega^{-1} y = f(ax + by)$$

Thus, i_o is a linear function of v_s .


Linearity of $P_{abs} = g(v_s)$: $g(ax + by) = \frac{1600}{147} \Omega^{-1} (ax + by)^2 = \frac{1600}{147} \Omega^{-1} (a^2 x^2 + b^2 y^2 + 2axby)$

$$g(x) = \frac{1600}{147} \Omega^{-1} x^2, \quad g(y) = \frac{1600}{147} \Omega^{-1} y^2$$

$$ag(x) + bg(y) = a \frac{1600}{147} \Omega^{-1} x^2 + b \frac{1600}{147} \Omega^{-1} y^2 \neq g(ax + by)$$

Thus, P_{abs} is not a linear function v_s .

Example of Linearity

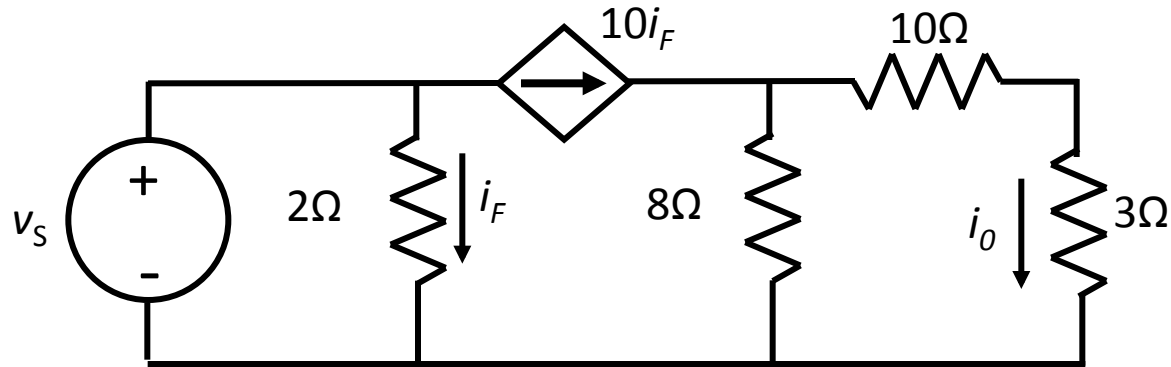

In this linear circuit example, the algebraic circuit variable i_o is a linear function of the voltage source value v_S .

The power dissipated in the 3Ω resistor is not a linear function of the voltage source value v_S .

Voltage and current variables are linear functions of other voltage and current variables, ***but this is not generally true for power.***

Principle of Superposition

Principle of Superposition: Any current or voltage in a **linear circuit** that contains *multiple independent sources* can be calculated as the *algebraic sum* of all the individual contributions due to each independent source acting alone

- Superposition allows a complicated analysis to be performed as a series of simpler analyses
- Superposition will sometimes *but not always* lead to a simpler analysis

Equations of a Linear Circuit

Kirchoff's Current Law: $0 = \sum_m i_m(t) \rightarrow 0 = i_1 + i_2 + i_3 + \dots$

Kirchoff's Voltage Law: $0 = \sum_m v_m(t) \rightarrow 0 = v_1 + v_2 + v_3 + \dots$

Ohm's Law: $0 = v_x - i_x R_x$

Dependent Sources:

$$\begin{aligned} 0 &= v_x - \alpha v_y & 0 &= i_x - \beta i_y \\ 0 &= v_x - r i_y & 0 &= i_x - g v_y \end{aligned}$$

Independent Sources: $V_0 = v_x \quad I_0 = i_x$

We see that every equation is linear. The independent source equations have a different form than the other equations.

Equations of a Linear Circuit

If all the independent sources are “turned off”, meaning each $V_o \rightarrow 0$ and $I_o \rightarrow 0$, the linear system of equations takes the **homogenous** form:

$$\begin{bmatrix} 0 \\ \vdots \\ 0 \end{bmatrix} = \begin{bmatrix} A_{11} & \cdots & A_{1n} \\ \vdots & \ddots & \vdots \\ A_{n1} & \cdots & A_{nn} \end{bmatrix} \begin{bmatrix} x_1 \\ \vdots \\ x_n \end{bmatrix} \quad x_m = v_m \text{ or } i_m$$

$$\mathbf{0} = \mathbf{A} \cdot \mathbf{x}$$

$$\mathbf{x}_0 = \mathbf{A}^{-1} \cdot \mathbf{0} = \mathbf{0} \quad \text{if } \det(\mathbf{A}) \neq 0$$

In other words, all voltages (or currents) are zero.

Equations of a Linear Circuit

If only one independent source is turned on (call it source #1), the linear system of equations takes the *inhomogeneous* form:

$$\begin{bmatrix} b_1 \\ 0 \\ \vdots \\ 0 \end{bmatrix} = \begin{bmatrix} A_{11} & \cdots & A_{1n} \\ \vdots & \ddots & \vdots \\ A_{n1} & & A_{nn} \end{bmatrix} \begin{bmatrix} x_1 \\ \vdots \\ x_n \end{bmatrix} \quad x_m = v_m \text{ or } i_m$$

$$\mathbf{b}_1 = \mathbf{A} \cdot \mathbf{x}$$

$$\mathbf{x}_1 = \mathbf{A}^{-1} \cdot \mathbf{b}_1 \quad \text{if } \det(\mathbf{A}) \neq 0$$

In other words \mathbf{x}_1 is the circuit voltage (or current) with independent source #1 turned on and all others turned off.

Equations of a Linear Circuit

If a different independent source is turned on (calling it #2, and leaving all other independent sources off), the linear system of equations gives:

$$\begin{bmatrix} \vdots \\ 0 \\ b_2 \\ 0 \\ \vdots \end{bmatrix} = \begin{bmatrix} A_{11} & \cdots & A_{1n} \\ \vdots & \ddots & \\ A_{n1} & & A_{nn} \end{bmatrix} \begin{bmatrix} x_1 \\ \vdots \\ x_n \end{bmatrix} \quad x_m = v_m \text{ or } i_m$$

$$\mathbf{b}_2 = \mathbf{A} \cdot \mathbf{x}$$

$$\mathbf{x}_2 = \mathbf{A}^{-1} \cdot \mathbf{b}_2 \quad \text{if } \det(\mathbf{A}) \neq 0$$

In other words \mathbf{x}_2 is the circuit voltage (or current) with independent source #2 turned on and all others turned off.

Equations of a Linear Circuit

If *all* independent sources are turned on, linear algebra gives us:

$$\begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ 0 \\ \vdots \end{bmatrix} = \begin{bmatrix} A_{11} & \cdots & A_{1n} \\ \vdots & \ddots & \\ A_{n1} & & A_{nn} \end{bmatrix} \begin{bmatrix} x_1 \\ \vdots \\ x_n \end{bmatrix}$$

$$\mathbf{b} = \mathbf{A} \cdot \mathbf{x}$$

$$\begin{aligned} \mathbf{x} &= \mathbf{A}^{-1} \cdot \mathbf{b} \quad \text{if } \det(\mathbf{A}) \neq 0 \\ &= \mathbf{A}^{-1} \cdot (\mathbf{b}_1 + \mathbf{b}_2 + \mathbf{b}_3 + \dots) \\ &= \mathbf{A}^{-1} \cdot \mathbf{b}_1 + \mathbf{A}^{-1} \cdot \mathbf{b}_2 + \mathbf{A}^{-1} \cdot \mathbf{b}_3 + \dots \\ &= \mathbf{x}_1 + \mathbf{x}_2 + \mathbf{x}_3 + \dots \end{aligned}$$

In other words, the total response \mathbf{x} is the algebraic sum of responses $\mathbf{x}_1, \mathbf{x}_2, \dots$ to each independent source.

Principle of Superposition


1. Keep one ***independent*** source “on” and “turn-off” all other ***independent*** sources.
2. Calculate the current or voltage variable(s) of interest.
3. Repeat steps 1 and 2 for each remaining ***independent*** source.
4. Add algebraically the individual contributions for the total response.

Note: Retain all ***dependent*** sources, unchanged, through each step of the analysis.


“Turning Off” Sources

When turning off independent sources, we make the following replacements.

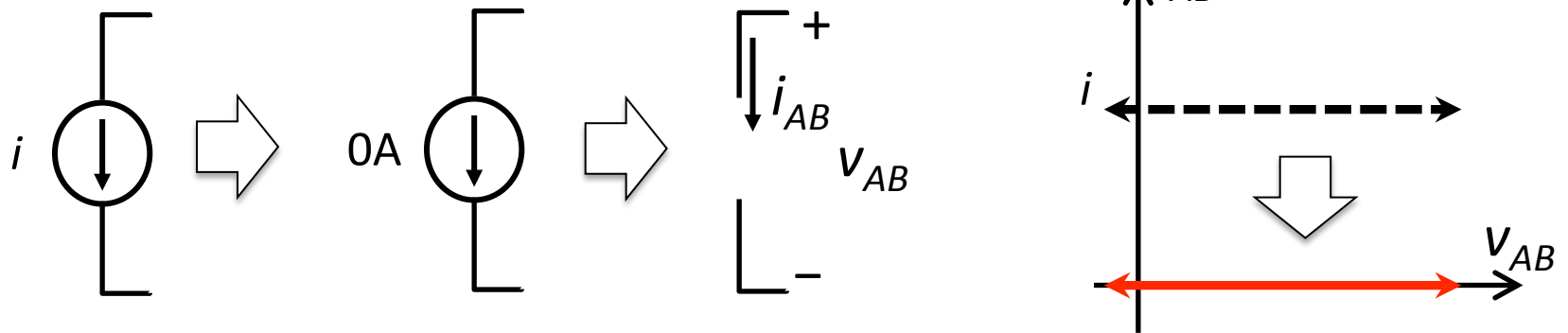Current sources set to 0A = **open circuit**




Voltage sources set to 0V = **short circuit**

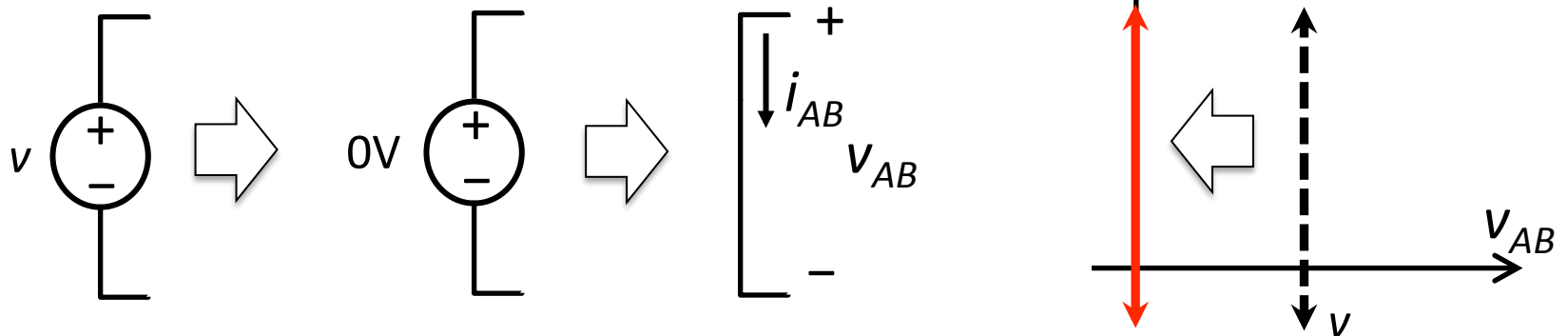

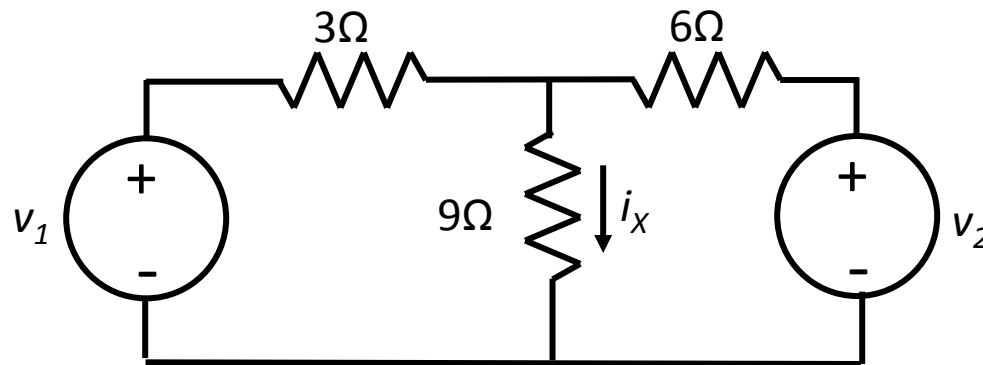Example 1



Find the current i_x and the power dissipated in the 9Ω resistor, as functions of v_1 and v_2 .



Strategy:

- apply superposition, ie. solve for i_x with $v_2=0$, then solve for i_x with $v_1=0$, add the solutions for i_x
- use the solution for i_x to find the power absorbed in the 9Ω resistor

Example 1

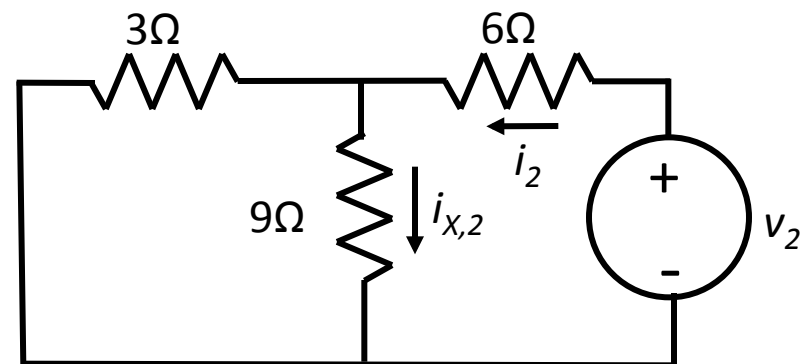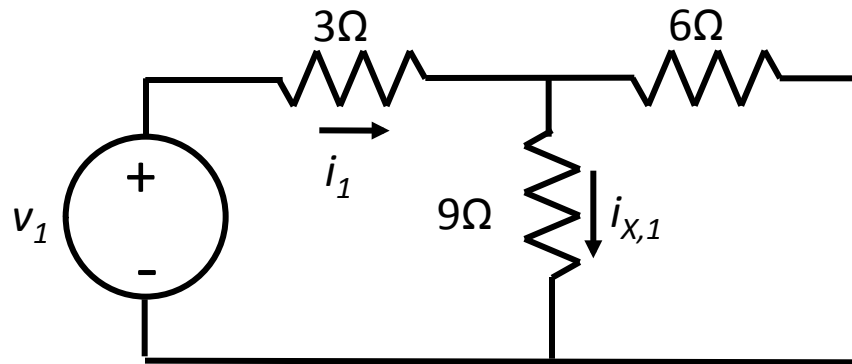

$$i_1 = \frac{v_1}{3\Omega + 6\Omega \parallel 9\Omega} = \frac{5}{33} \Omega^{-1} v_1$$

$$i_{x,1} = i_1 \frac{6\Omega}{6\Omega + 9\Omega} = \frac{2}{5} \frac{5}{33} \Omega^{-1} v_1 = \frac{2}{33} \Omega^{-1} v_1$$

$$i_2 = \frac{v_2}{6\Omega + 3\Omega \parallel 9\Omega} = \frac{4}{33} \Omega^{-1} v_2$$


$$i_{x,2} = i_2 \frac{3\Omega}{3\Omega + 9\Omega} = \frac{1}{4} \frac{4}{33} \Omega^{-1} v_2 = \frac{1}{33} \Omega^{-1} v_2$$

Thus: $i_x = i_{x,1} + i_{x,2} = \frac{2}{33} \Omega^{-1} v_1 + \frac{1}{33} \Omega^{-1} v_2$

$$P_{abs} = i_x^2 9\Omega = \frac{(2v_1 + v_2)^2}{121\Omega}$$

Example 2



Find the voltage v_0 .

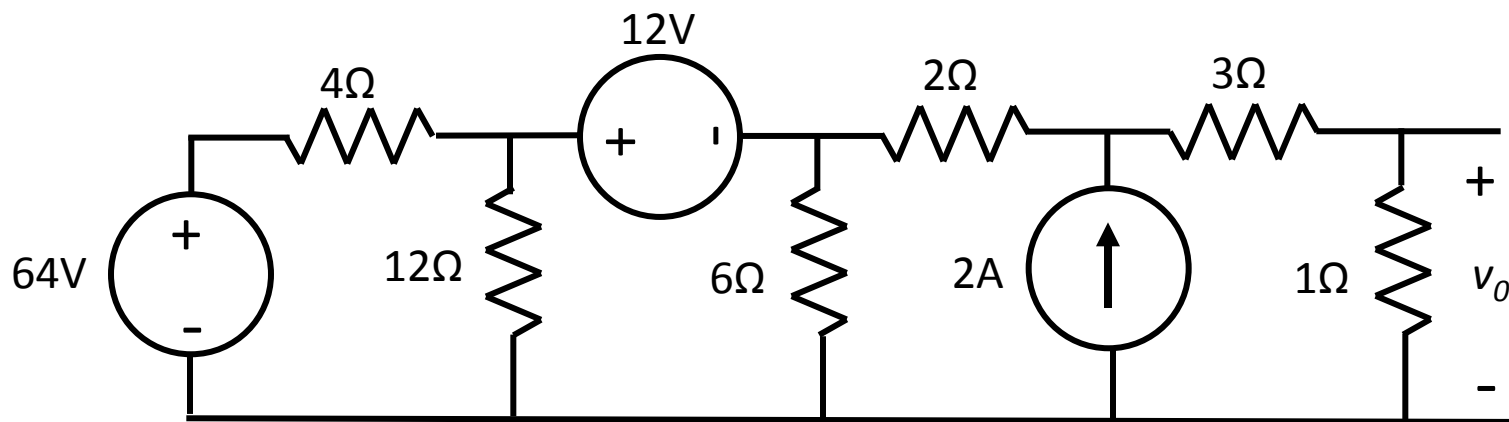

Strategy:

- apply superposition to solve for v_0 , ie. add the contributions to v_0 arising from each source

Example 2

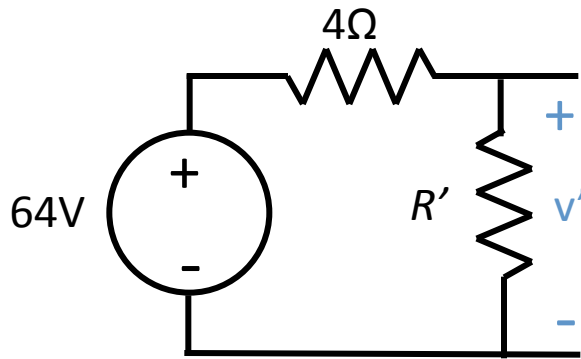
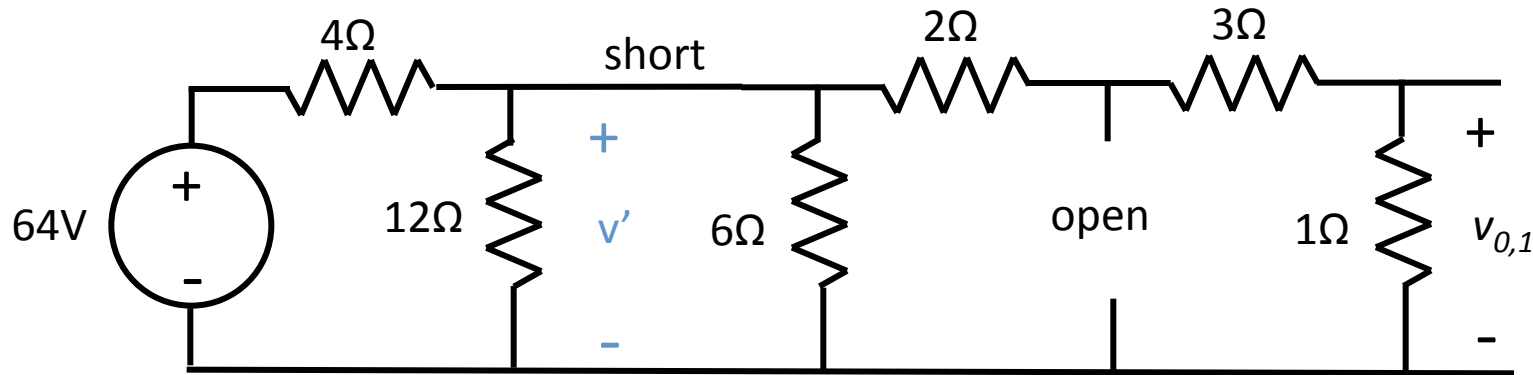


$$\begin{aligned}
 R' &= 12\Omega \parallel 6\Omega \parallel (2\Omega + 3\Omega + 1\Omega) \\
 &= 12\Omega \parallel 6\Omega \parallel 6\Omega \\
 &= 12\Omega \parallel 3\Omega \\
 &= 12/5\Omega
 \end{aligned}$$

voltage divider:
$$v' = 64V \frac{R'}{R' + 4\Omega} = 64V \frac{12/5\Omega}{12/5\Omega + 4\Omega} = 24V$$

voltage divider:
$$v_{0,1} = v' \frac{1\Omega}{1\Omega + 2\Omega + 3\Omega} = 4V$$



Example 2

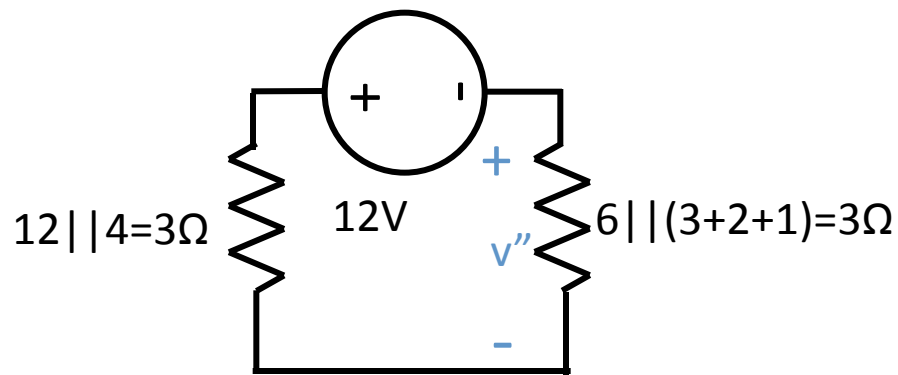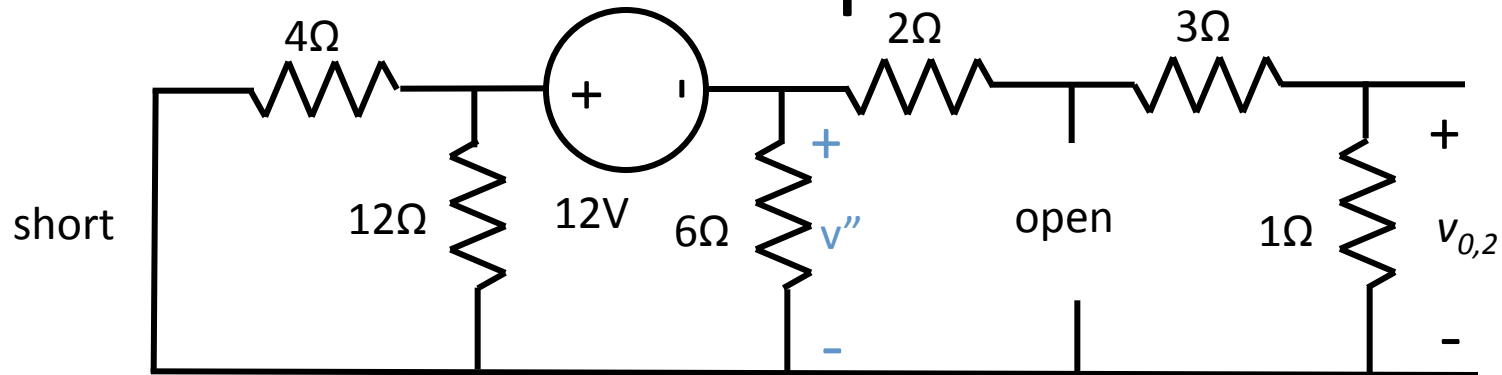

voltage divider:
$$v'' = -12V \frac{3\Omega}{3\Omega + 3\Omega} = -6V$$

voltage divider:
$$v_{0,2} = v'' \frac{1\Omega}{1\Omega + 2\Omega + 3\Omega} = -1V$$

Example 2

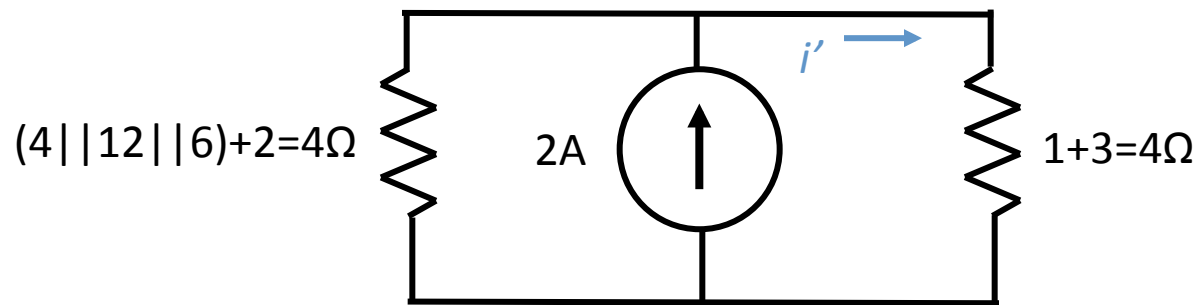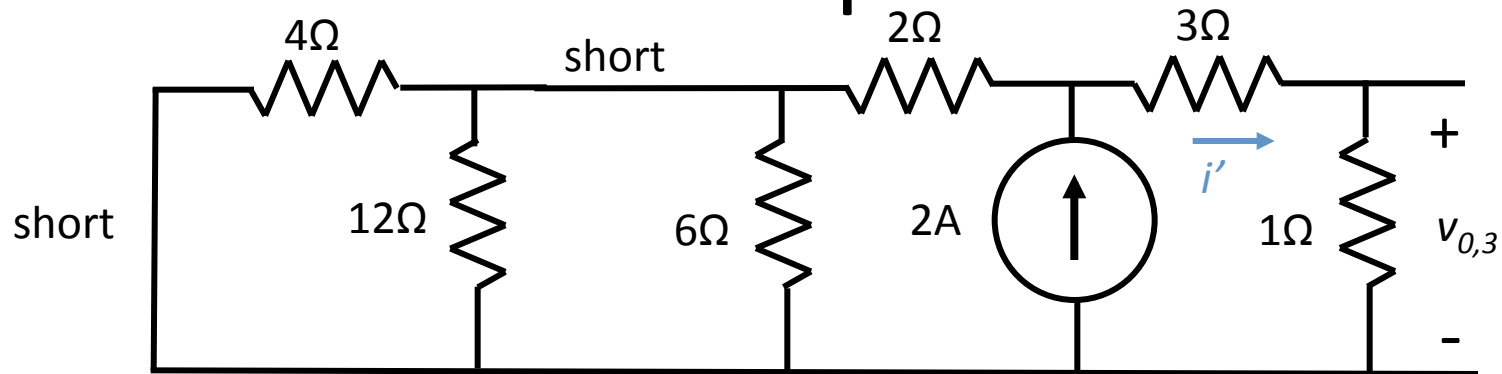

current divider:
$$i' = 2A \frac{4\Omega}{4\Omega + 4\Omega} = 1A$$

Ohm's Law:
$$v_{0,3} = i' 1\Omega = 1V$$

Example 2

Summing up the contributions from each source:


$$\begin{aligned}V_O &= V_{O,1} + V_{O,2} + V_{O,3} \\&= 4V + (-1V) + 1V \\&= 4V\end{aligned}$$

The problem was reduced to a series of calculations using equivalent resistance, voltage dividers and current dividers.


Source transformations could also be used to solve this problem.

Superposition Example 3

Find the voltage v_o .

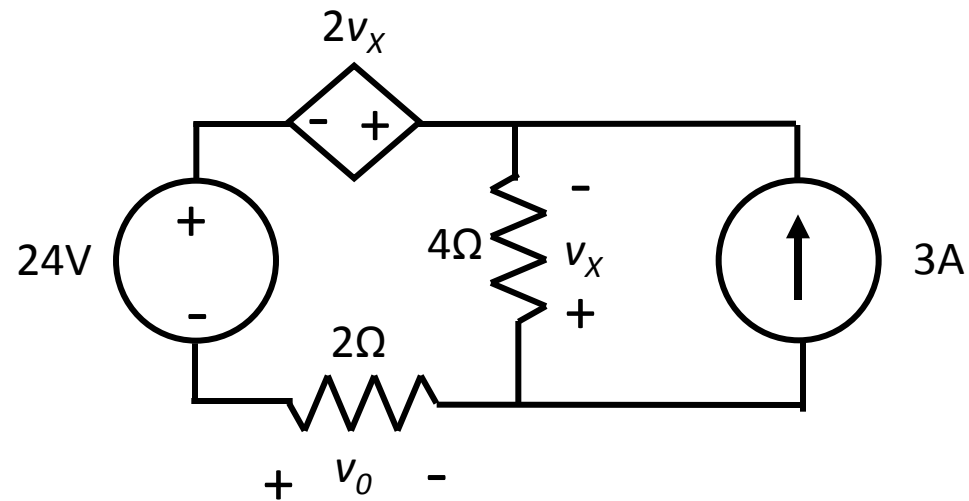

Superposition Example 3

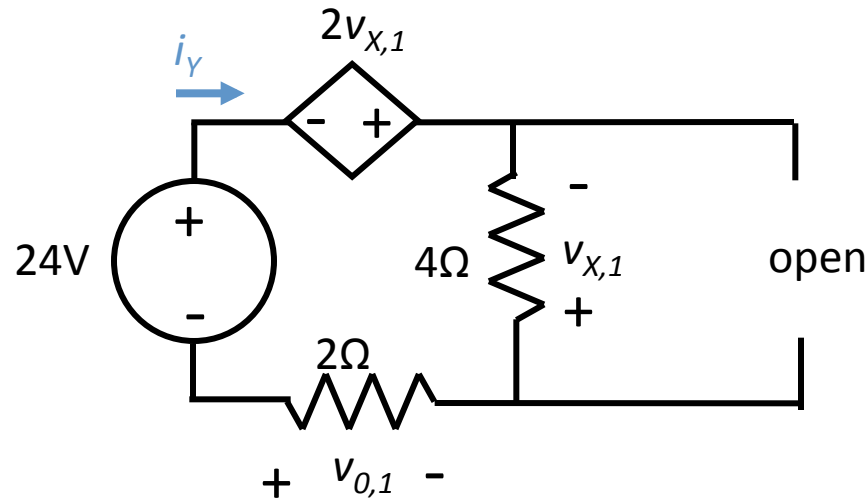


$$\text{KVL: } -24\text{V} - 2v_{x,1} - v_{x,1} - v_{0,1} = 0$$

$$\text{KCL+Ohm's Law: } i_Y = -v_{x,1}/4\Omega = -v_{0,1}/2\Omega \rightarrow v_{x,1} = 2v_{0,1}$$

$$\text{Substitution: } -24\text{V} - 4v_{0,1} - 2v_{0,1} - v_{0,1} = 0$$

$$v_{0,1} = -24/7 \text{ V}$$

Superposition Example 3

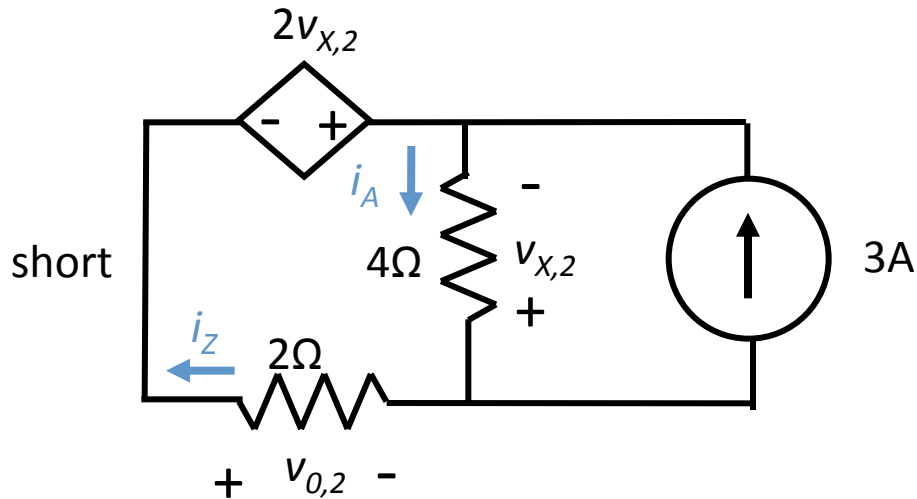

$$\text{KVL: } -2v_{x,2} - v_{x,2} - v_{0,2} = 0$$

$$\text{KCL: } i_A - 3A - i_Z = 0 \rightarrow i_A = 3A + i_Z$$



$$\text{Ohm's Law: } v_{x,2} = -i_A 4\Omega = -(3A + i_Z) 4\Omega, \quad v_{0,2} = -i_Z 2\Omega$$

$$\rightarrow v_{x,2} = -(3A - v_{0,2}/2\Omega) 4\Omega = -12V + 2 v_{0,2}$$

$$\text{substitution: } -2(-12V + 2 v_{0,2}) - (-12V + 2 v_{0,2}) - v_{0,2} = 0$$

$$v_{0,2} = 36/7 \text{ V}$$

Superposition Example 3

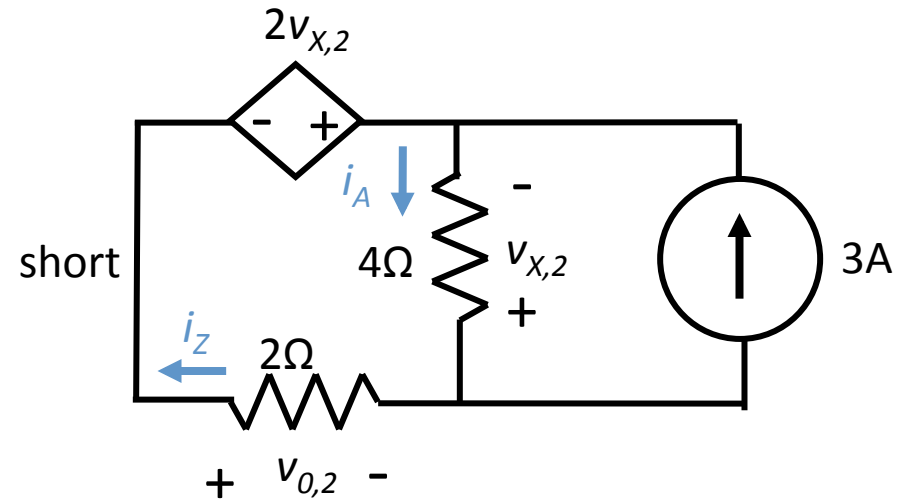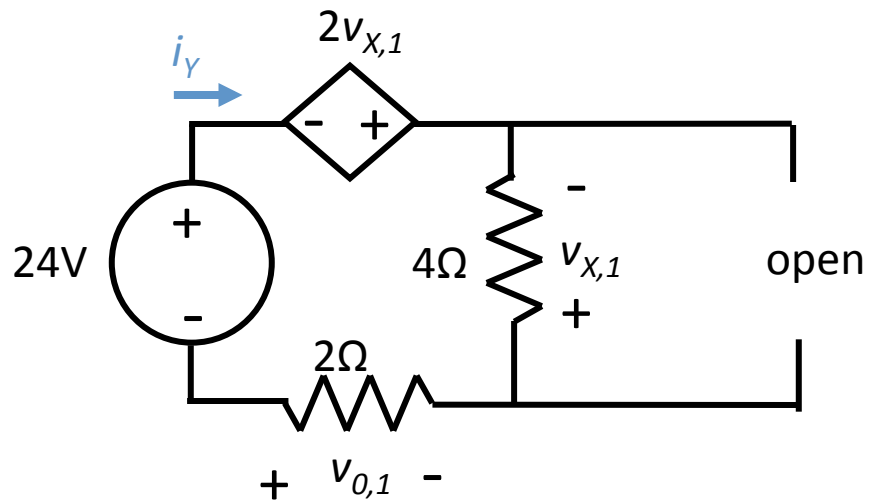

By principle of superposition:

$$v_o = v_{o,1} + v_{o,2} = -24/7 + 36/7 = 12/7 \text{ V}$$