


Today's Outline

6. Energy Storage Elements

- the Inductor
- Coupled Inductors


the inductor

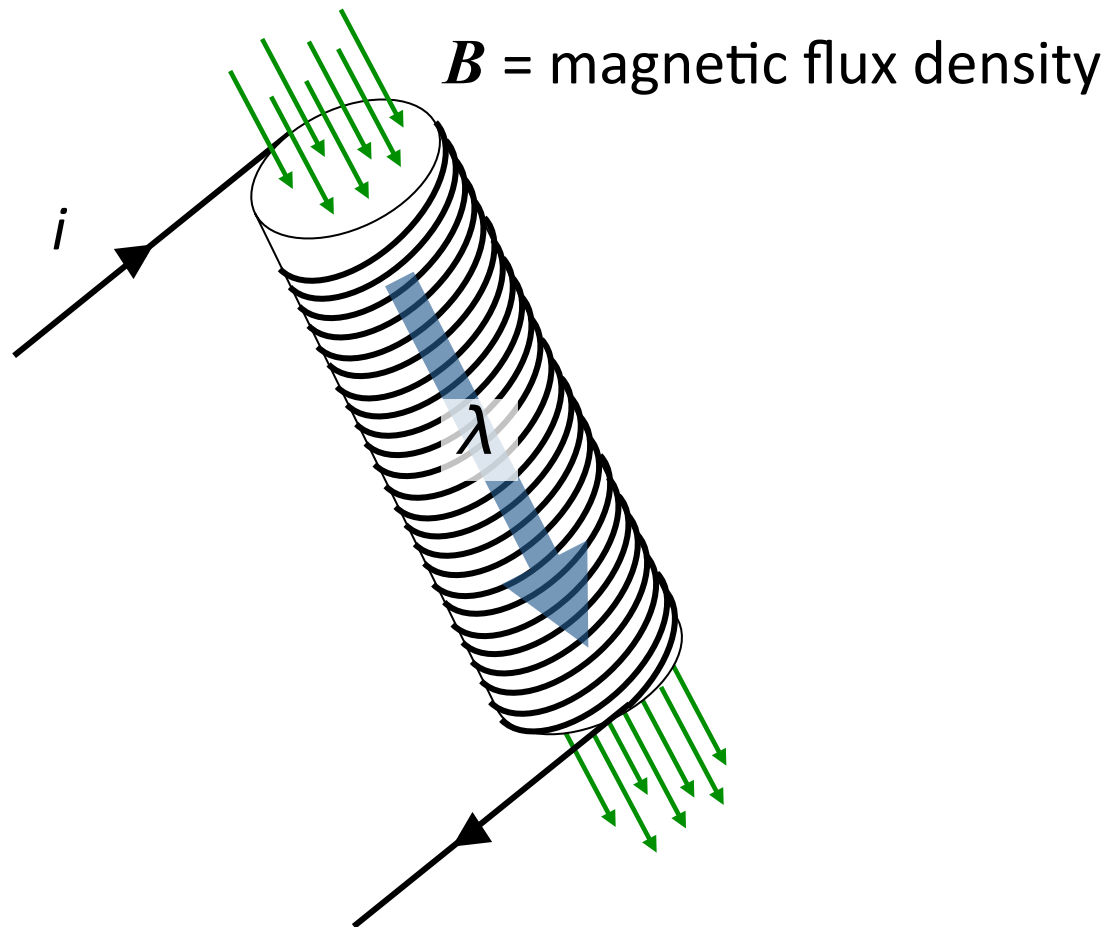Ideal inductor: physically consists of a coiled conductor, with a magnetic flux, called the **flux linkage** λ , threading the coil




the inductor

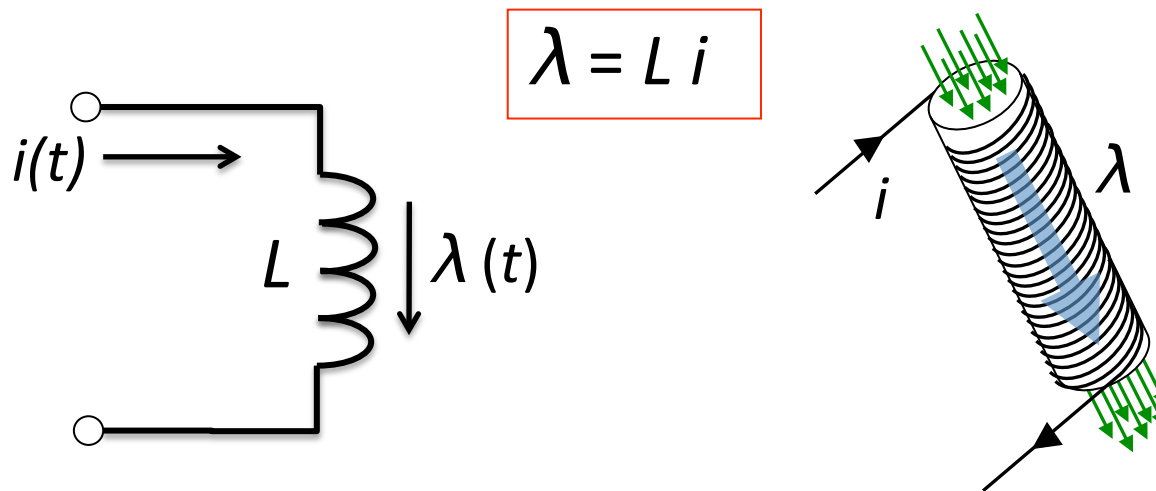Ideal Inductor: the **flux linkage** λ through an ideal inductor is proportional to the current i through the inductor



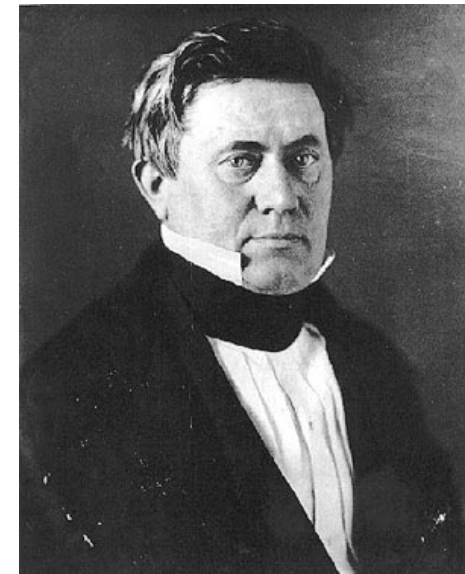
- the inductor is a *passive* circuit element
- the constant of proportionality between flux and current is the **inductance**, given the symbol L
- SI unit of inductance is the Henry (abbreviated H)
 $1 \text{ H} = 1 \text{ Wb} / \text{A} = 1 \text{ V s} / \text{A}$



Joseph Henry
(1797-1878)


the inductor

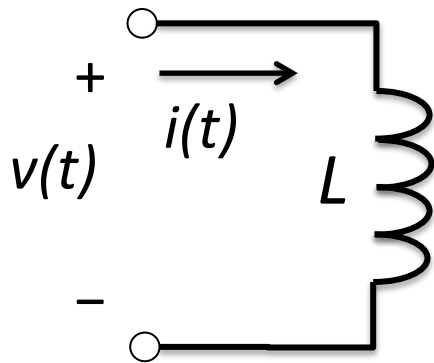Although made of an ideal conductor, a voltage v equal to the time rate of change of flux linkage λ can develop “across” the inductor (Faraday’s Law).




$$v = \frac{d\lambda}{dt} = L \frac{di}{dt}$$

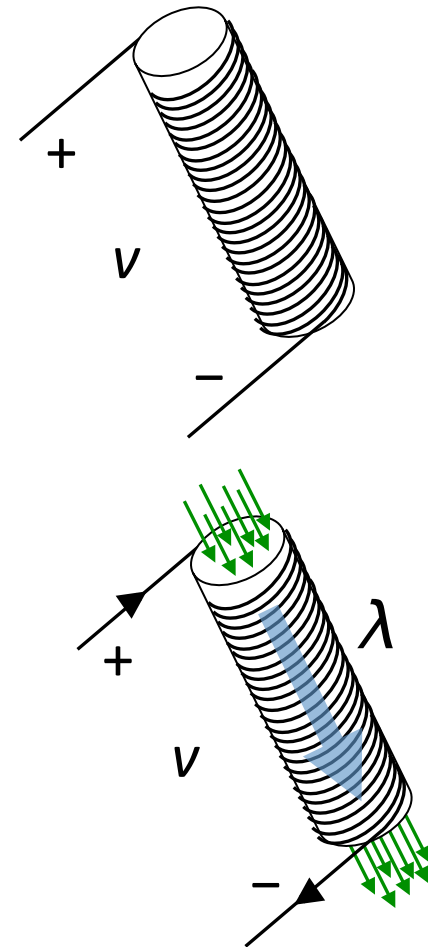- the voltage v and current i are defined above to satisfy **passive sign convention**
- the voltage v and current i are related to each other by a linear operator (differentiation / integration)



the inductor

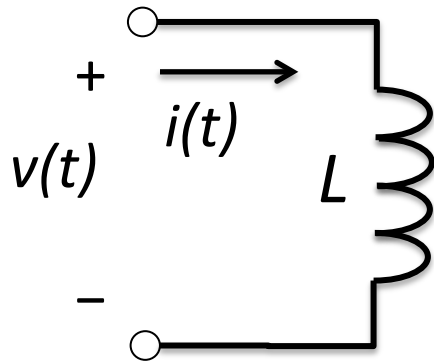There are alternative but equivalent forms of the equations describing terminal behaviour of ideal inductors.



differential form:


$$v = L \frac{di}{dt} = \frac{d\lambda}{dt}$$

integral form:

$$i(t) - i(t_0) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau = \frac{\lambda(t) - \lambda(t_0)}{L}$$

the inductor

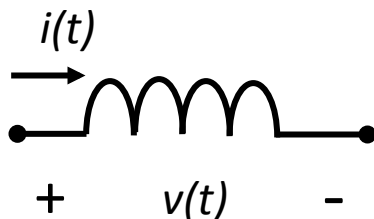Consider the energy *stored* in an inductor. The instantaneous power *absorbed* (note the *passive sign convention*) by an inductor is:



$$p(t) = i(t) \cdot v(t) = Li(t) \frac{di(t)}{dt}$$

The energy absorbed by the inductor from time t_0 to time t is:

$$W_{t_0 \rightarrow t} = \int_{t_0}^t p(t') dt' = \int_{t_0}^t Li(t') \frac{di(t')}{dt'} dt' = \int_{i(t_0)}^{i(t)} Li(t') di(t') = \frac{1}{2} Li^2(t) - \frac{1}{2} Li^2(t_0)$$


The energy absorbed is *stored* as magnetic potential energy $U(t)$:

$$U(t) = \frac{1}{2} Li^2(t) = \frac{1}{2} \frac{\lambda^2(t)}{L} \quad W_{t_0 \rightarrow t} = U(t) - U(t_0)$$

continuity of inductor current


The current flow through a inductor is:
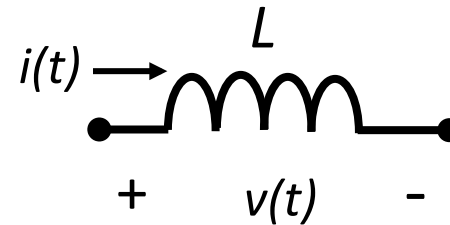
$$v = L \frac{di}{dt} = L \lim_{\Delta t \rightarrow 0} \frac{i(t + \Delta t) - i(t)}{\Delta t}$$



where we restate the definition of the derivative.

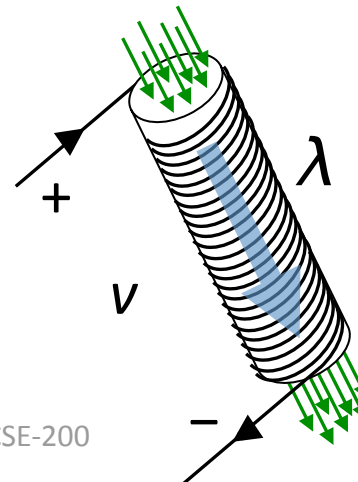
An instantaneous change in inductor current (and flux linkage) requires an infinite (unphysical) voltage. For a finite terminal voltage, we require that the inductor current $i(t)$ is **continuous**.



continuity of inductor current



Continuity of inductor current ensures that:

- the voltage v is finite
- the power absorbed $p = iv$ by the inductor is finite
- the flux linkage λ is continuous
- the magnetic energy stored $U = \frac{1}{2} Li^2$ is continuous, satisfying the **conservation of energy**

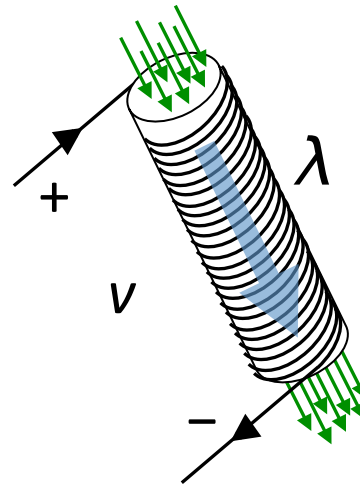


Example 1

An ideal $30\mu\text{H}$ inductor has a current $i(t)$ flow through its terminals, as specified below. Plot the voltage $v(t)$ as a function of time. How much energy is stored in the inductor at $t = 5\mu\text{s}$?

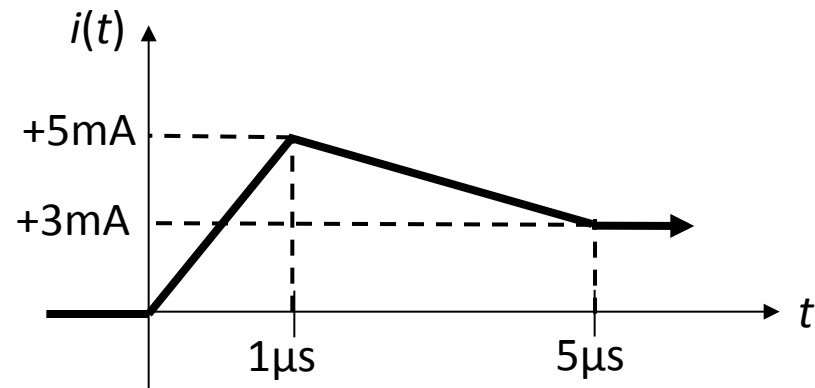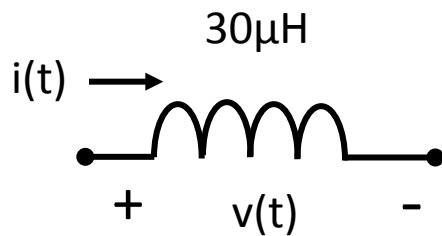

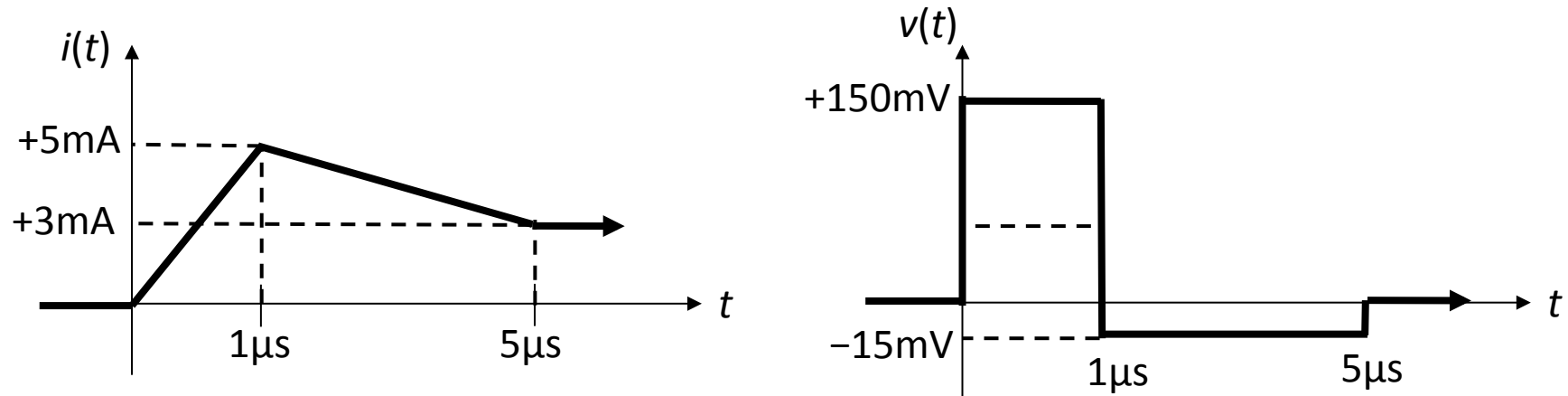Example 1

Voltage is given by $v = L di/dt$, meaning in proportion to the slope of $i(t)$ vs t .



$$t < 0\mu s : L di/dt = 0V$$

$$0 < t < 1\mu s : L di/dt = 30\mu H \times 5mA/1\mu s = 150 \text{ mV}$$



$$1\mu s < t < 5\mu s : L di/dt = 30\mu H \times (-2mA)/4\mu s = -15 \text{ mV}$$

$$5\mu s < t : L di/dt = 0V$$

The stored energy at $t = 5\mu s$ is:
$$U(5\mu s) = \frac{1}{2} Li^2(5\mu s) = \frac{1}{2} \cdot 30mH \cdot (3mA)^2 = 135nJ$$



Example 2

An ideal inductor has a voltage and current as plotted below. What is the value of the inductance L ?

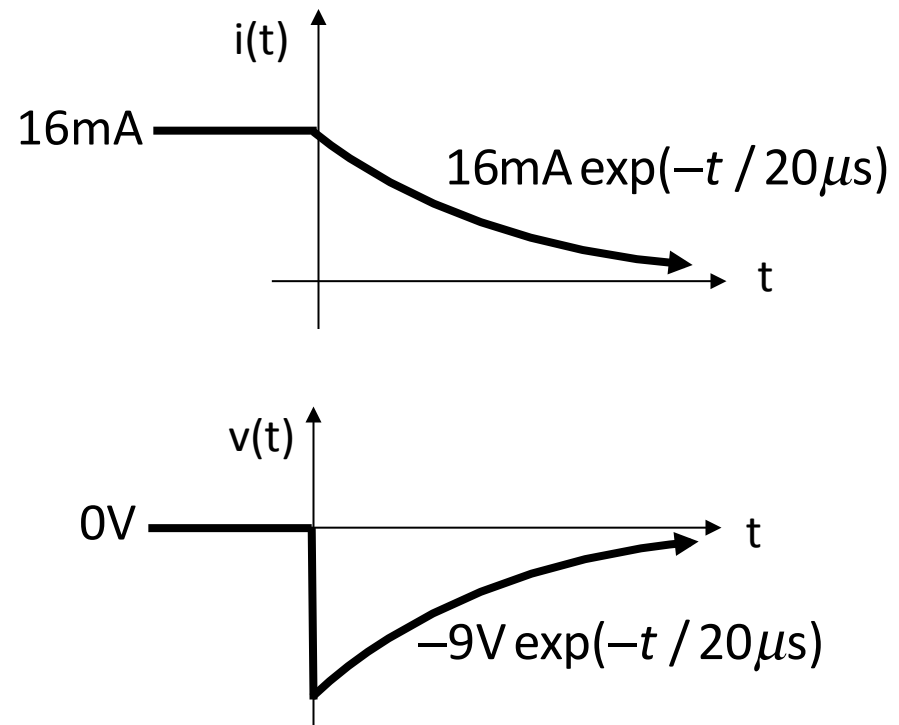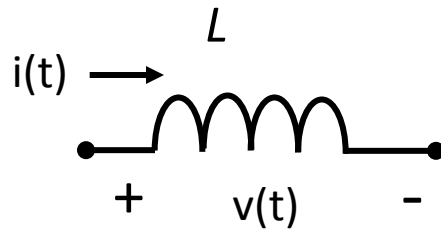

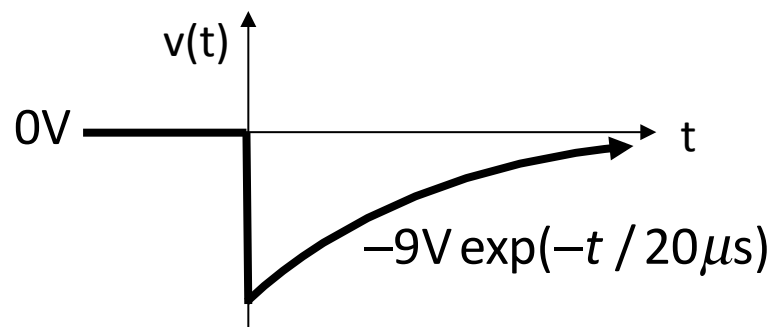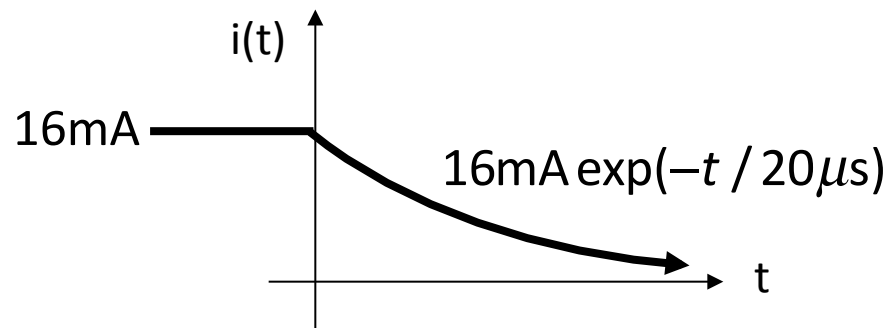Example 2

The inductance is given by the ratio $L = v / [di/dt]$, which is indeed a constant for the given curves.




$$\begin{aligned} \frac{di}{dt} &= 16\text{mA} \cdot \frac{-1}{20\mu\text{s}} \exp(-t / 20\mu\text{s}) \\ &= -\frac{4}{5} \frac{\text{A}}{\text{ms}} \exp(-t / 20\mu\text{s}) \end{aligned}$$

$$\begin{aligned} L &= \frac{v}{di/dt} \\ &= \frac{-9\text{V} \exp(-t / 20\mu\text{s})}{-\frac{4}{5} \frac{\text{A}}{\text{ms}} \exp(-t / 20\mu\text{s})} \\ &= 11.25\text{mH} \end{aligned}$$

inductors in series

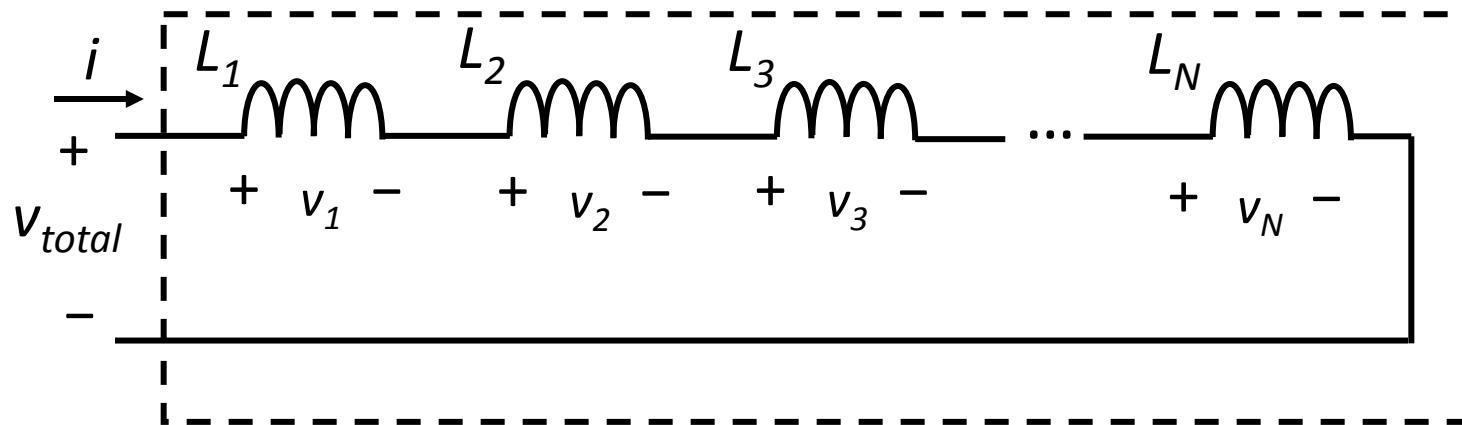A series combination of inductors has an equivalent inductance L_{eq} .




Voltage across each inductor: $v_m = L_m \frac{di}{dt}$

Total voltage (KVL):
$$v_{total} = v_1 + v_2 + \dots + v_N = (L_1 + L_2 + \dots + L_N) \frac{di}{dt}$$

Equivalent inductance:
$$\frac{v_{total}}{di/dt} = L_{eq} = L_1 + L_2 + \dots + L_N$$

inductors in parallel

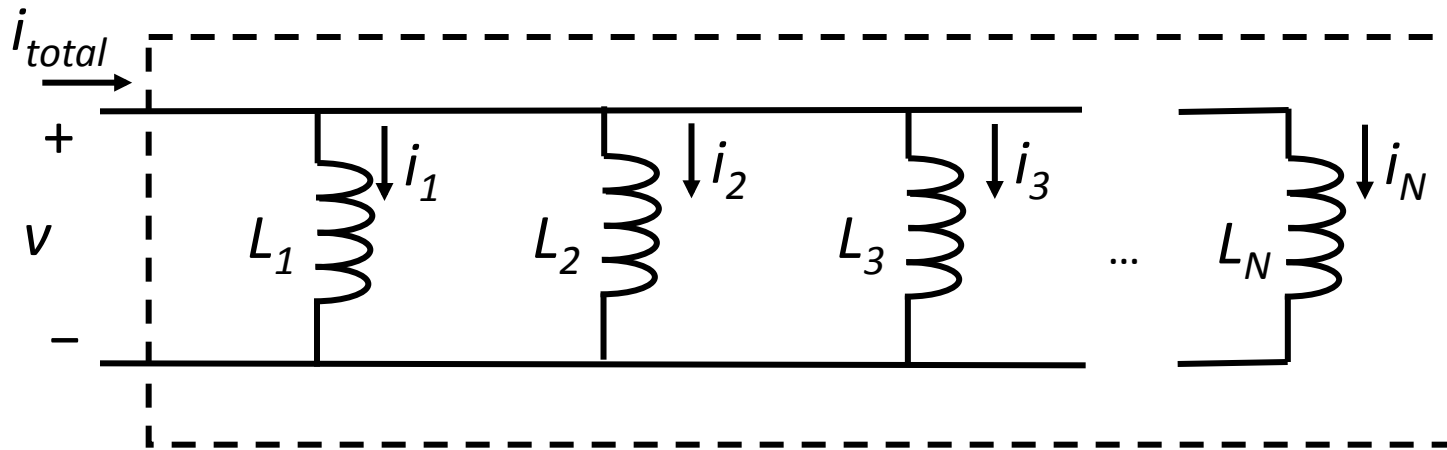A parallel combination of inductors has an equivalent inductance L_{eq} .



Voltage across each inductor: $v = L_m di_m/dt$

Total current:

(time derivative of KCL)


$$\frac{di_{total}}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} + \dots + \frac{di_N}{dt} = v \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right)$$

Equivalent inductance:

$$\frac{di_{total}/dt}{v} = \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

coupled inductors

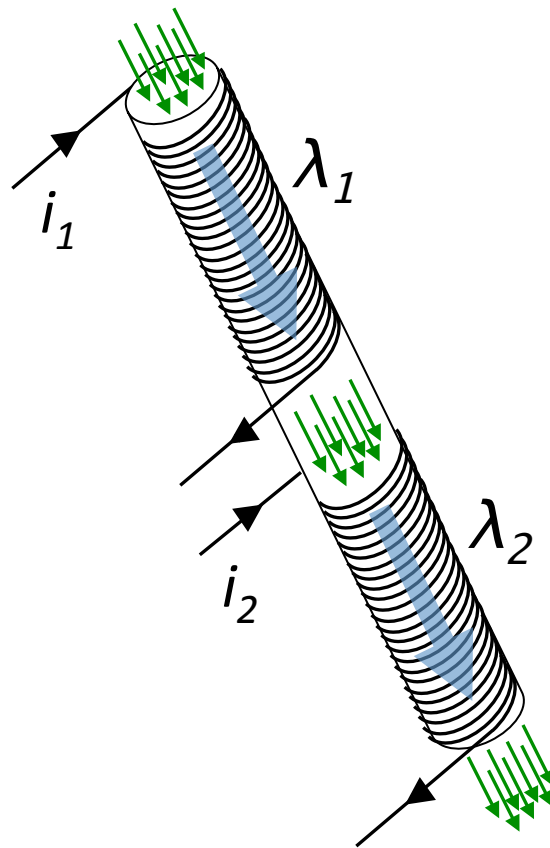coupled inductors: physically consists of ideal inductors whose physical arrangement leads to a *sharing of flux linkage*.



- both currents i_1 and i_2 generate non-zero flux linkage in both inductors.

$$\lambda_1 = L_1 i_1 + M i_2$$

$$\lambda_2 = L_2 i_2 + M i_1$$



- L_1 and L_2 are **self-inductances**, and M is the **mutual inductance**.

- The SI unit for M is the Henry.

$$1 \text{ H} = 1 \text{ Wb} / \text{A} = 1 \text{ V s} / \text{A}$$

coupled inductors

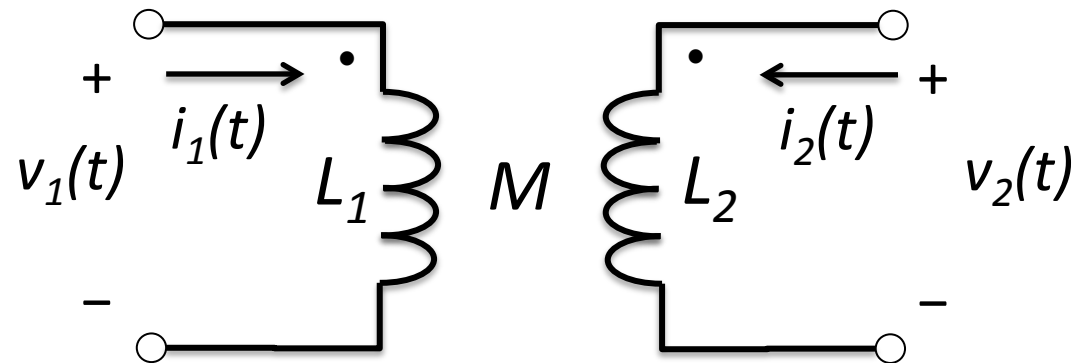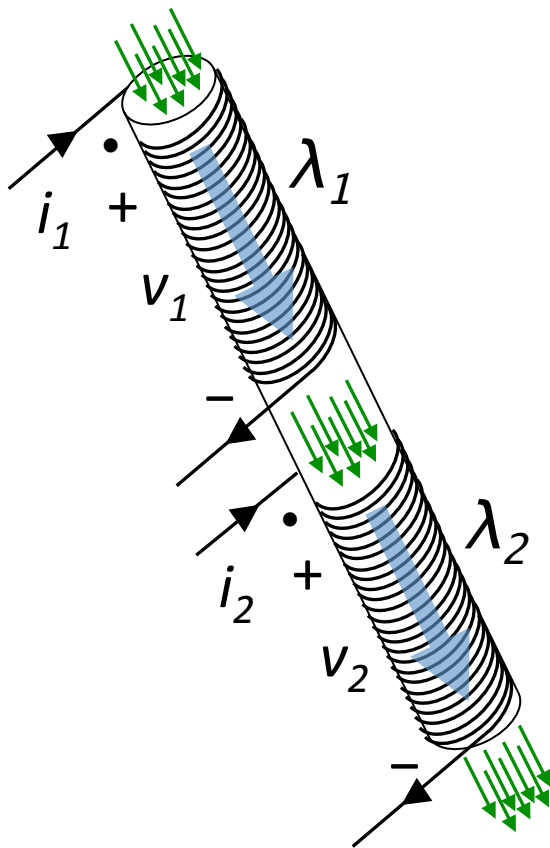The **dot convention** indicates the polarity of the mutual flux linkage for coil windings. The • indicates the terminals leading to additive mutual linkage.





$$v_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = \frac{d\lambda_2}{dt} = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

ideal transformer

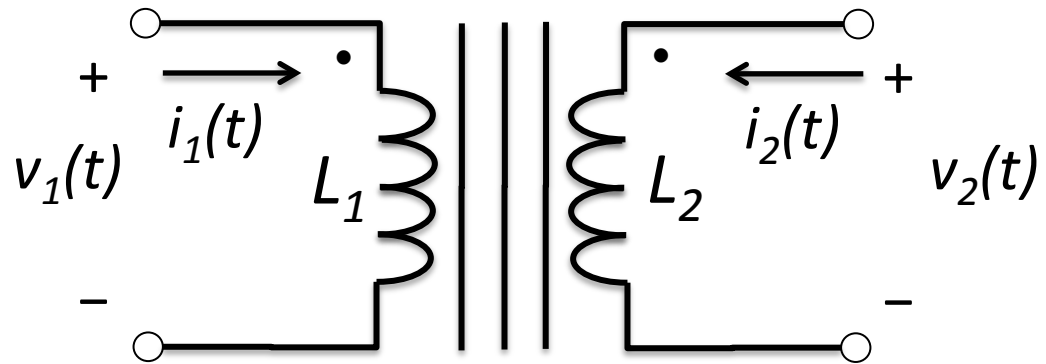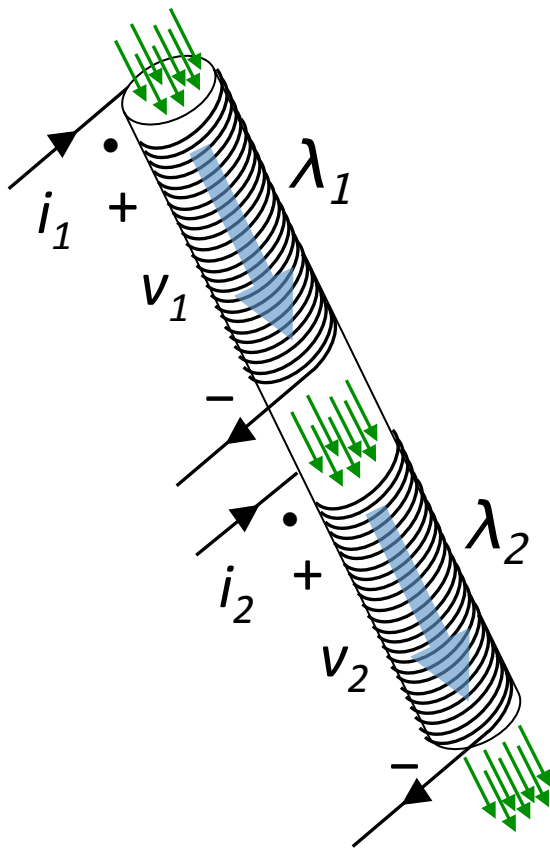An ideal **transformer** is an ideal coupled inductor where the mutual inductance is the maximum physically allowed, $M^2 = L_1 L_2$.




$$v_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = \frac{d\lambda_2}{dt} = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$


$$M = \sqrt{L_1 L_2}$$

Example 3

What are the mesh current equations for the coupled inductor circuit below?

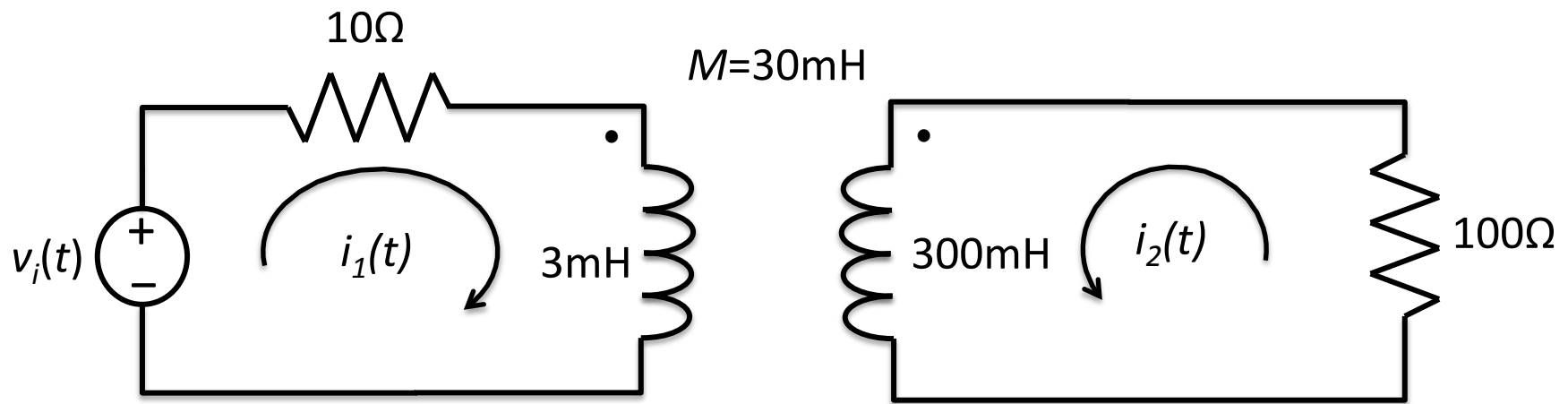

Example 3

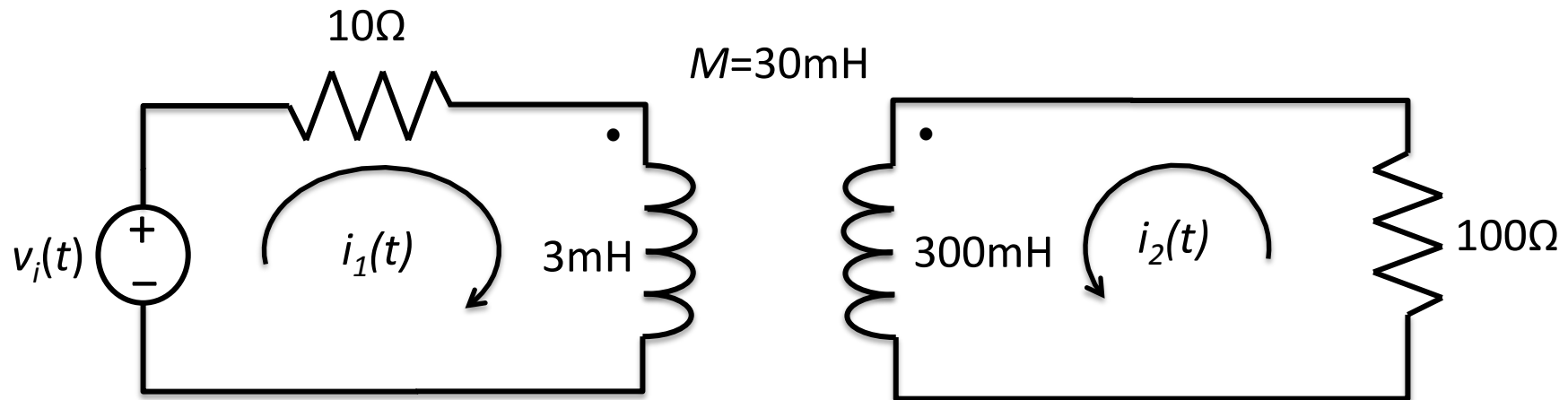


$$0 = -v_i + 10\Omega \cdot i_1 + 3\text{mH} \cdot \frac{di_1}{dt} + \underline{30\text{mH} \cdot \frac{di_2}{dt}}$$

$$0 = 100\Omega \cdot i_2 + 300\text{mH} \cdot \frac{di_2}{dt} + \underline{30\text{mH} \cdot \frac{di_1}{dt}}$$

The current definition with respect to the dots leads to mutual inductance terms with the same sign as self inductance terms.

practical inductors

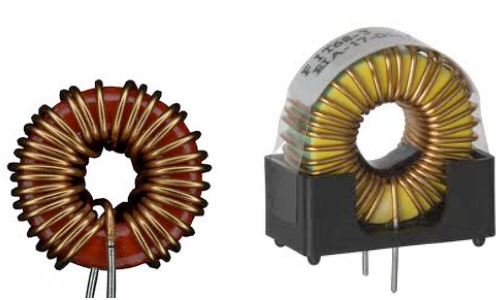Practical inductors come in a variety of shapes, sizes and materials.



toroids with ferrite cores



air core wire wound



variable roller




ferrite core wire wound

practical coupled inductors

Practical coupled inductors and transformers come in a variety of shapes and sizes as well.





laminated ferrite cores


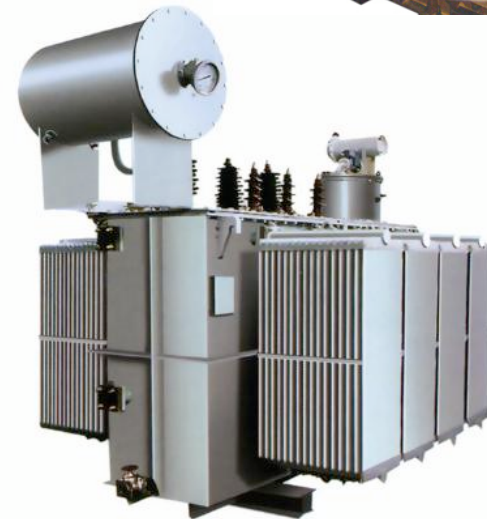


oil cooled power transformers

the capacitor and the inductor

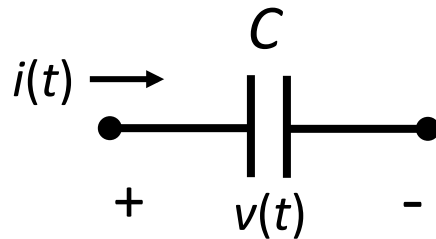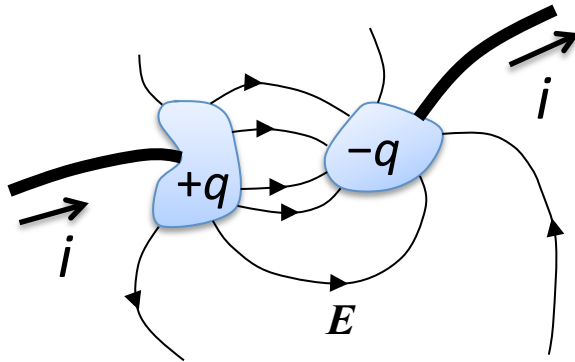


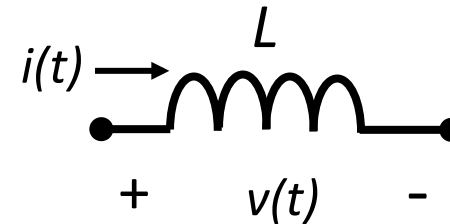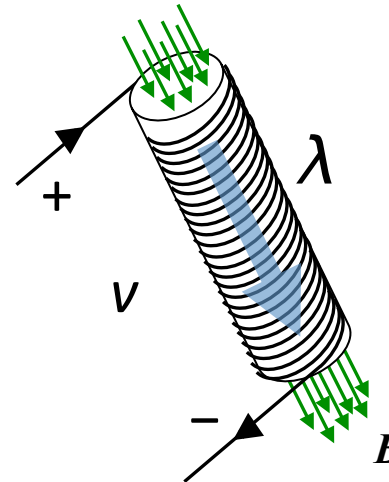electric potential energy
stored in charge separation q



magnetic potential energy
stored in flux linkage λ

the capacitor and the inductor

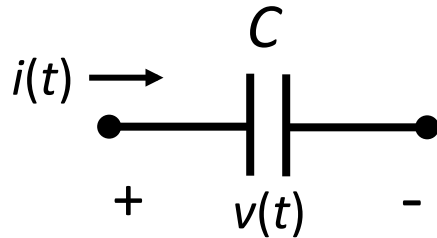


$$q = Cv$$

$$i = C \frac{dv}{dt} = \frac{dq}{dt}$$

$$v(t) - v(t_0) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

$$U = \frac{1}{2} C v^2$$

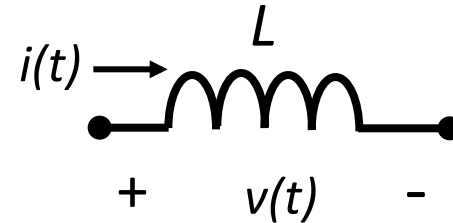

$$\lambda = Li$$

$$v = L \frac{di}{dt} = \frac{d\lambda}{dt}$$

$$i(t) - i(t_0) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

$$U = \frac{1}{2} L i^2$$