



Electric Circuits 1  
ECSE-200 Section: 1

26 April 2012, 2:00PM


Examiner: Thomas Szkopek

Assoc Examiner: Zetian Mi

INSTRUCTIONS:


- This is a **CLOSED BOOK** examination.
- **NO CRIB SHEETS** are permitted.
- Provide your answers in an **EXAM BOOKLET**.
- **STANDARD CALCULATOR** permitted ONLY.
- This examination consists of 4 questions, with a total of 6 pages, including the cover page.
- This examination is **PRINTED ON BOTH SIDES** of the paper

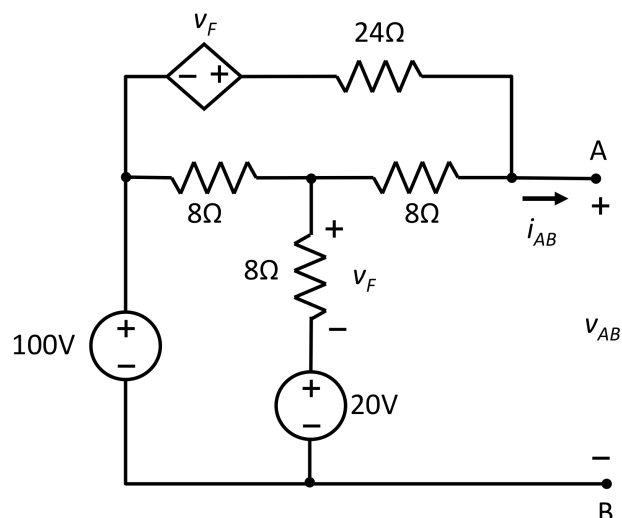1. Consider the circuit below. Answer the questions. [12 pts]




- What is the physical basis of Kirchoff's Voltage Law? [1pt]
- What is the value of  $v_F$  when an open circuit is applied to terminals A and B? [2pts]
- What is the value of  $v_F$  when a short circuit is applied to terminals A and B? [2pts]
- What is the Thévenin equivalent circuit with respect to the terminals A and B? Clearly label A and B on your circuit diagram. [5pts]
- What is the maximum power that the circuit can deliver to an optimally chosen load resistor attached to the terminals A and B? What is the value of the optimally chosen load resistor? [2pts]

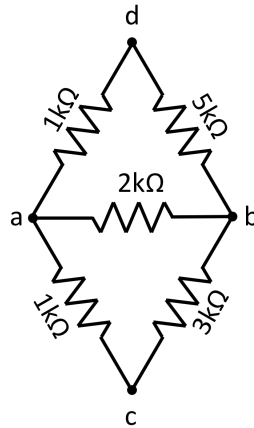2. Consider the circuit below. Answer the questions. [12 pts]




- a) What is the definition of a passive element? [1pt]
- b) What is the equivalent resistance between terminals a and b? [2pts]
- c) What is the equivalent resistance between terminals b and c? [2pts]
- d) What is the equivalent resistance between terminals b and d? [2pts]
- e) What is the equivalent resistance between terminals d and c? [3pts]
- f) A capacitor is attached to the terminals d and c, resulting in a first order circuit. How should the capacitance be chosen to give a time constant of  $10\mu\text{s}$ ? [1pt]

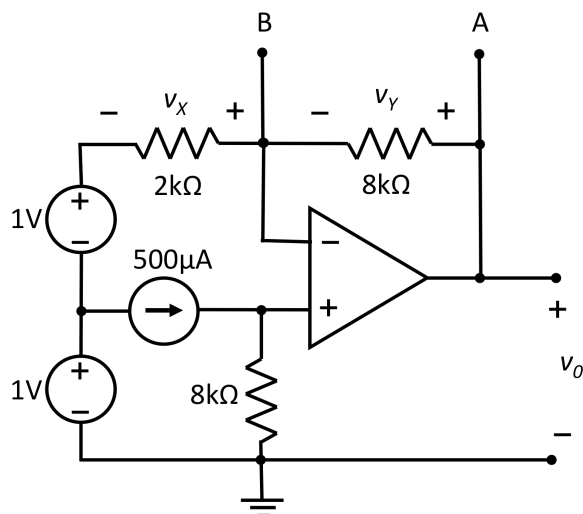3. Consider the circuit below. Assume ideal op-amp behaviour. Answer the questions. [12 pts]



- Give one reason why negative feedback is used in op-amp circuits? [1pt]
- How much power does the independent current source deliver or absorb? [2pts]
- What is the voltage  $v_x$ ? [2pts]
- What is the voltage  $v_y$ ? [2pts]
- What is the voltage  $v_o$ ? [2pts]
- What is the Thévenin resistance with respect to the terminals A and B? [2pts]
- If a  $10\mu\text{H}$  inductor is attached to the terminals A and B, what is the time constant for the resulting first order circuit? [1pt]

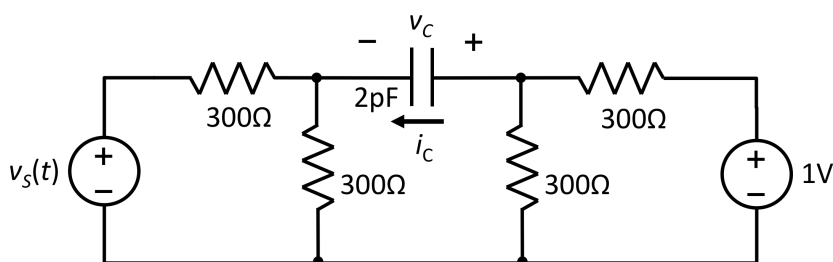4. Consider the circuit and equation below. Assume dc steady state behaviour for  $t < 0$ . The function  $u(t)$  is the unit step function. Answer the questions. [12 pts]




$$v_s(t) = 1V \times u(t) - 1V \times u(t-1.2ns)$$

- Plot the voltage  $v_s(t)$  versus  $t$ . [1pt]
- What is  $v_c(t)$  for  $t < 0$ ? [1pt]
- What is  $v_c(t)$  for  $0 < t < 1.2ns$ ? [3pts]
- What is  $v_c(t)$  for  $1.2ns < t$ ? [3pts]
- Plot  $v_c(t)$  versus  $t$ . Be sure to label your axes. [2pts]
- Plot  $i_c(t)$  versus  $t$ . Be sure to label your axes. [2pts]

end

1. a) conservation of energy [1]

b)

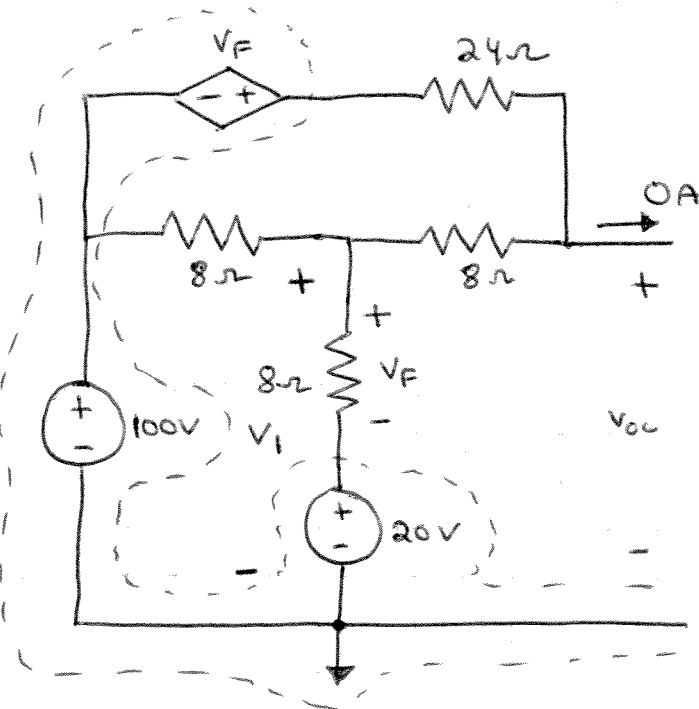

node voltage method [1]


$$0 = \frac{V_1 - 20V}{8\Omega} + \frac{V_1 - 100V}{8\Omega} + \frac{V_1 - V_F - 100V}{32\Omega}$$

$$V_F = V_1 - 20V$$

$$\therefore 0 = \frac{V_F}{8\Omega} + \frac{V_F - 80V}{8\Omega} + \frac{-80V}{32\Omega}$$

$$V_F = 50V \quad [1]$$

c)

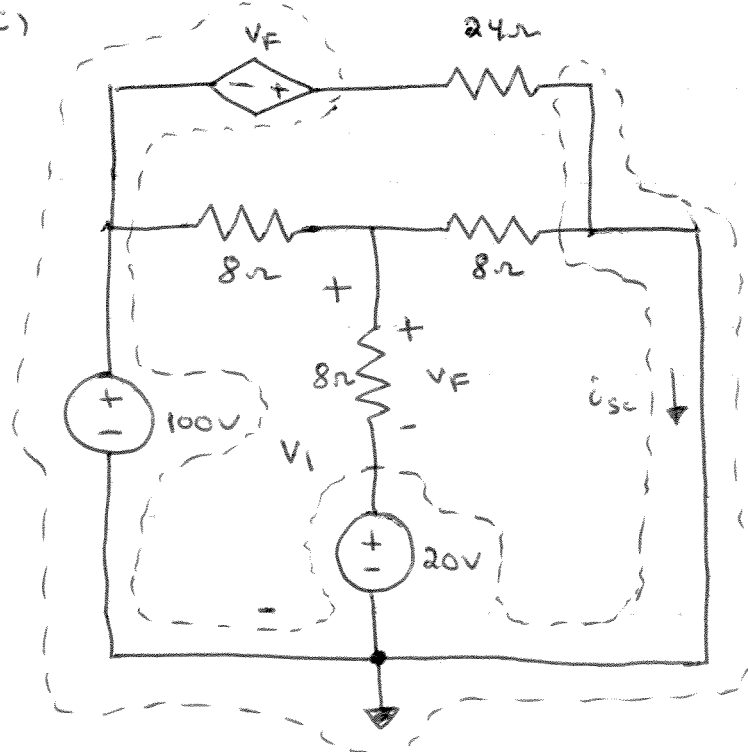

node voltage method [1]

$$0 = \frac{V_1 - 20V}{8\Omega} + \frac{V_1 - 100V}{8\Omega} + \frac{V_1}{8\Omega}$$

$$V_F = V_1 - 20V$$

$$\therefore 0 = \frac{V_F}{8\Omega} + \frac{V_F - 80V}{8\Omega} + \frac{V_F + 20V}{8\Omega}$$

$$V_F = 20V \quad [1]$$


d) From b):

$$\begin{aligned}V_{oc} &= V_1 - 8\Omega \cdot \left( \frac{V_1 - V_F - 100V}{32\Omega} \right) \\&= V_F + 20V - 8\Omega \left( \frac{-80V}{32\Omega} \right) \\&= 90V \quad [+1]\end{aligned}$$

From c):

$$\begin{aligned}i_{sc} &= \frac{V_1}{8\Omega} + \frac{V_F + 100V}{24\Omega} \\&= \frac{V_F + 20V}{8\Omega} + \frac{V_F + 100V}{24\Omega} \\&= 10A \quad [+1]\end{aligned}$$
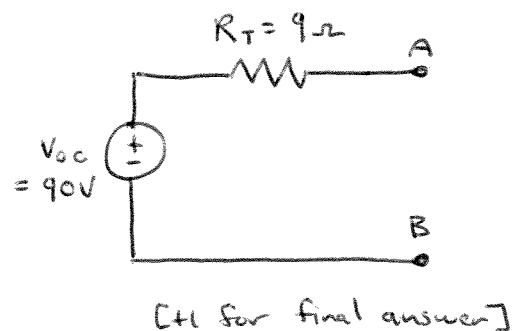
$$R_T = \frac{V_{oc}}{i_{sc}} = \frac{90V}{10A} = 9\Omega \quad [+1]$$




e) Maximum power occurs when  $R_L = R_T$ . [+1]

$$P_{max} = \frac{V_{oc}}{2} \cdot \frac{i_{sc}}{2} = \frac{90V \cdot 10A}{4} = 225W \quad [+1]$$




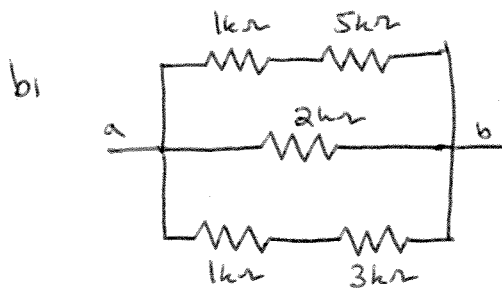2. a) an element that never delivers more energy to a circuit than it has received from a circuit. (+1)




$$R_{ab} = (1k\Omega + 5k\Omega) // 2k\Omega // (1k\Omega + 3k\Omega) \quad (+1)$$

$$= 1.091 k\Omega \quad (+1)$$

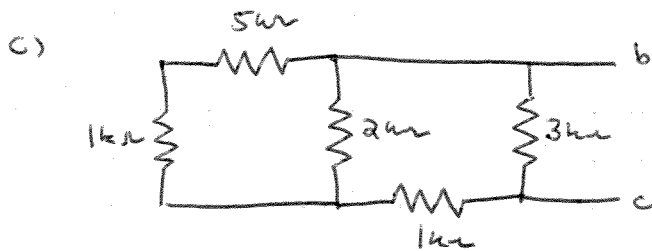

$$R_{bc} = 3k\Omega // [1k\Omega + 2k\Omega // (5k\Omega + 1k\Omega)] \quad (+1)$$


$$= 1.364 k\Omega \quad (+1)$$

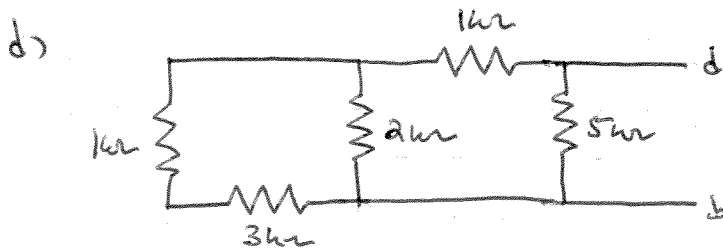

$$R_{bd} = 5k\Omega // [1k\Omega + 2k\Omega // (1k\Omega + 3k\Omega)] \quad (+1)$$

$$= 1.591 k\Omega \quad (+1)$$

e)

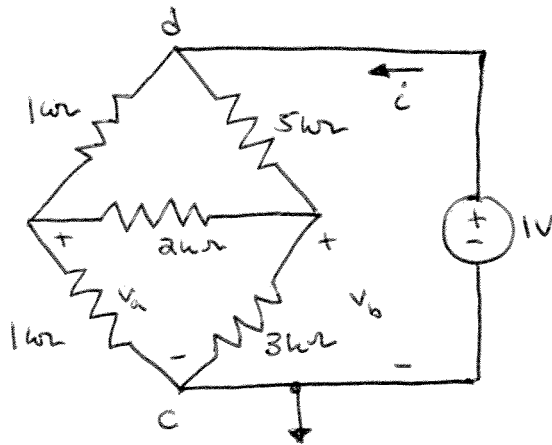

node voltage method:

$$\frac{V_a}{1k\Omega} + \frac{V_a - V_b}{2k\Omega} + \frac{V_a - 1V}{1k\Omega} = 0 \quad [1]$$

$$\frac{V_b}{3k\Omega} + \frac{V_b - V_a}{2k\Omega} + \frac{V_b - 1V}{5k\Omega} = 0 \quad [2]$$

$$5V_a - V_b = 2V$$

$$-15V_a + 31V_b = 6V$$

$$V_a = 0.486V \quad V_b = 0.429V$$

$$i = \frac{V_a}{1k\Omega} + \frac{V_b}{3k\Omega} = 0.629 \text{ mA}$$


$$R_{dc} = \frac{1V}{i} \quad [1]$$

$$= 1.590 \text{ k}\Omega$$

f)  $\tau = R_{dc} \cdot C$

$$C = \frac{\tau}{R_{dc}} = \frac{10\mu s}{1.590 \text{ k}\Omega} = 6.29 \text{ nF} \quad [1]$$

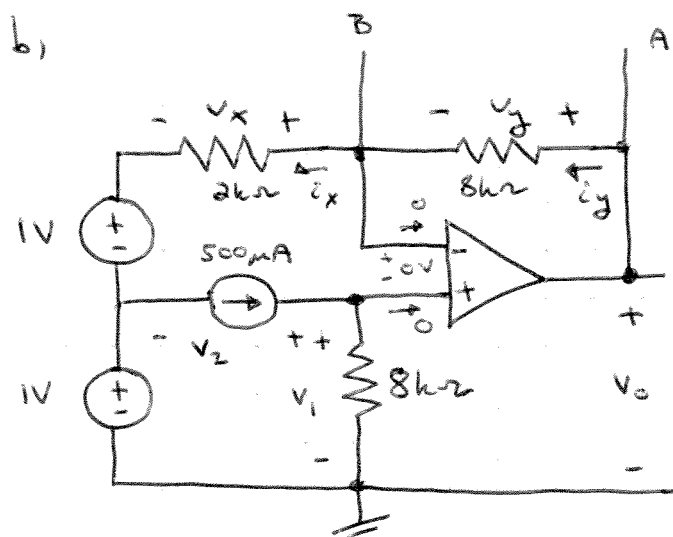3. a) stability  
 programmability  
 operation independent of open-loop gain



Ohm:  $v_1 = 8k\Omega \cdot 500\mu A = 4V$

KVL:  $0 = -4V - v_2 + v_1$

$v_2 = v_1 - 4V = 3V \quad [+]$

$P_{del} = v_2 \cdot 500\mu A = 1.5mW \text{ delivered } [+]$

c) KVL:  $0 = -4V - 4V - v_x + v_1 \quad [+]$



$v_x = -4V - 4V + v_1$

$= 2V \quad [+]$



4.


a)

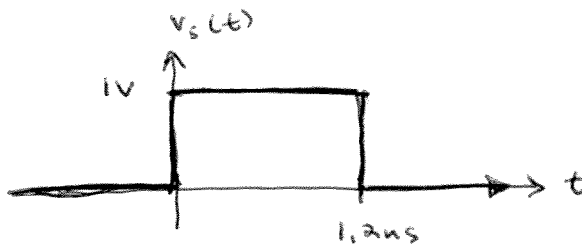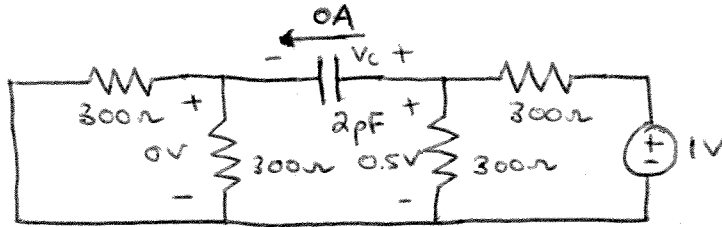b)  $t < 0$ 

$$v_c(t) = 0.5V \quad (t) \\ t < 0$$

$$c) \quad v_c(0+) = v_c(0) = 0.5V$$

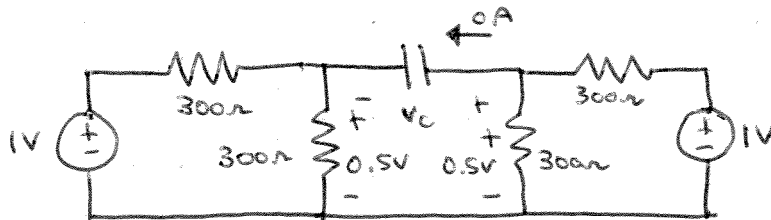as  $t \rightarrow \infty$  neglecting 2<sup>nd</sup> switching:



$$v_c(\infty) = 0V \quad (t)$$

$$R_{TH} = 300\Omega // 300\Omega + 300\Omega // 300\Omega = 300\Omega$$


$$\tau = R_{TH} C = 600ps \quad (t)$$

$$v_c(t) = v_c(\infty) + (v_c(0) - v_c(\infty)) \exp(-t/\tau)$$

$$= 0.5V \exp(-t/600ps) \quad (t) \\ 0 < t < 1.2ns$$

$$d) \quad v_c(1.2\text{ns}+) = v_c(1.2\text{ns}-) = 0.5\text{V} \exp(-1.2\text{ns}/600\text{ps}) \\ = 0.0677\text{V} \quad (+1)$$

as  $t \rightarrow \infty$

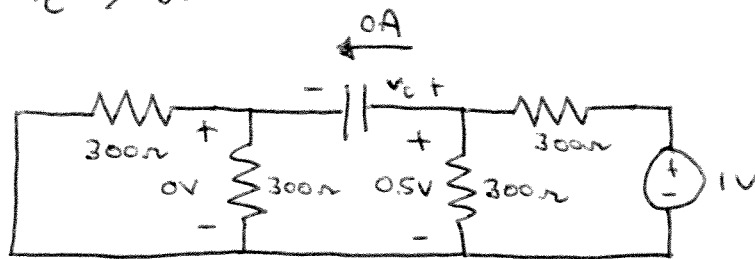


$$v_c(\infty) = 0.5\text{V} \quad (+1)$$

$$R_{TH} = 300\Omega // 300\Omega + 300\Omega // 300\Omega = 300\Omega$$

$$\tau = R_{TH} \cdot C = 600\text{ps}$$
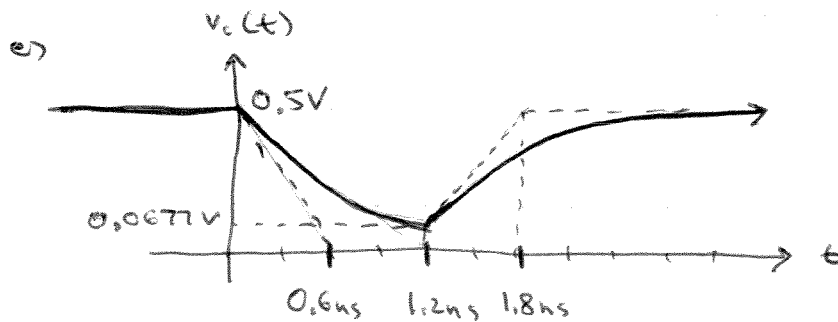
$$v_c(t) = v_c(\infty) + (v_c(1.2\text{ns}) - v_c(\infty)) \exp(-(t - 1.2\text{ns})/600\text{ps}) \\ = 0.5\text{V} - 0.432\text{V} \exp(-(t - 1.2\text{ns})/600\text{ps}) \quad (+1) \\ 1.2\text{ns} < t$$




(+1) for shape  
(+1) for values

$$f) \quad i_c = C \frac{dv_c}{dt}$$

$$i_c(0+) = 2\text{pF} \cdot \frac{-0.5\text{V}}{0.6\text{ns}} = -1.667\text{mA}$$

$$i_c(1.2\text{ns}-) = 2\text{pF} \cdot \frac{-0.0677\text{V}}{0.6\text{ns}} = -0.226\text{mA}$$
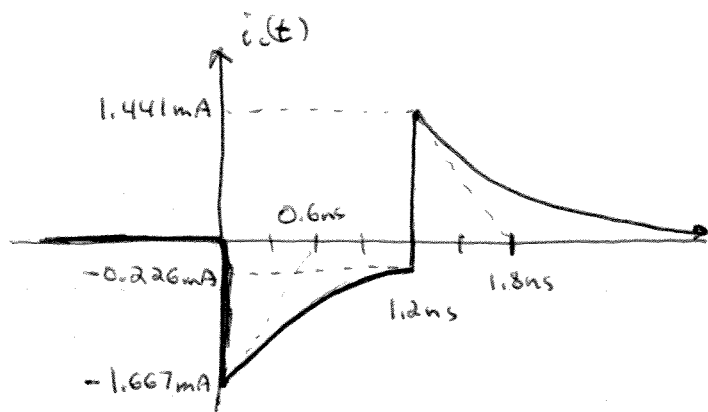
$$i_c(1.2\text{ns}+) = 2\text{pF} \cdot \frac{(0.5\text{V} - 0.0677\text{V})}{0.6\text{ns}} = 1.441\text{mA}$$



C+D for shape  
C+D for values