



Electric Circuits 1  
ECSE-200 Section: 1

16 April 2015, 2:00PM


Examiner: Thomas Szkopek

Assoc Examiner: Michael Rabbat

INSTRUCTIONS:


- This is a **CLOSED BOOK** examination.
- **NO CRIB SHEETS** are permitted.
- Provide your answers in an **EXAM BOOKLET**.
- **STANDARD CALCULATOR** permitted ONLY.
- This examination consists of 4 questions, with a total of 6 pages, including the cover page.
- This examination is **PRINTED ON BOTH SIDES** of the paper

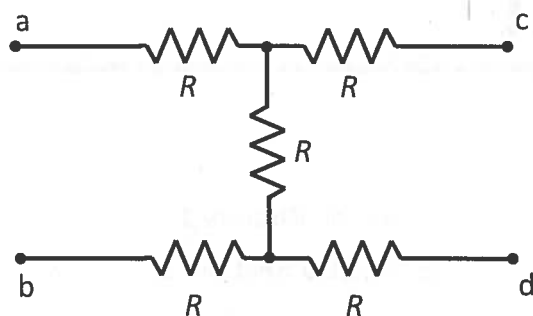1. Consider the circuit below. Answer the questions. [12 pts]







- a) What is the definition of a passive element? [1pt]
- b) What is the definition of a linear element? [1pt]
- c) What is the physical law at the origin of Kirchoff's current law? [1pt]
- d) What is the physical law at the origin of Kirchoff's voltage law? [1pt]
- e) What is the equivalent resistance between terminals a and b, if there is an open circuit between the terminals c and d ? [2pts]
- f) What is the equivalent resistance between terminals a and b, if there is a short circuit attached between the terminals c and d ? [2pts]
- g) What is the equivalent resistance between terminals a and b, if a resistance  $R$  is attached between the terminals c and d ? [2pts]
- h) What is the equivalent resistance between terminals a and b, if terminal a is connected to terminal d and terminal b is connected to terminal c ? [2pts]

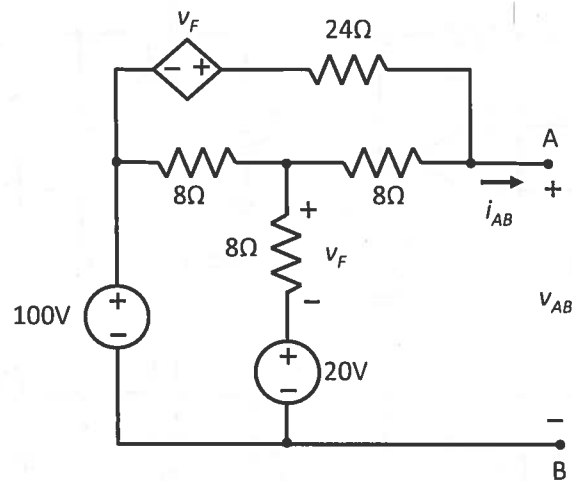2. Consider the circuit below. Answer the questions. [12 pts]




- What is Thévenin's theorem? [1pt]
- Draw the Thévenin equivalent circuit with respect to terminals A and B. Be sure to label the terminals A and B in your diagram. [5pts]
- Draw the  $i_{AB}$  versus  $v_{AB}$  diagram for the circuit. [2pts]
- What is the voltage  $v_{AB}$  measured by a voltmeter with a  $1\text{k}\Omega$  total internal resistance that is attached to the terminals A and B? [2pts]
- What is the maximum power that the circuit can deliver to an optimally chosen load resistor attached to the terminals A and B? [2pts]

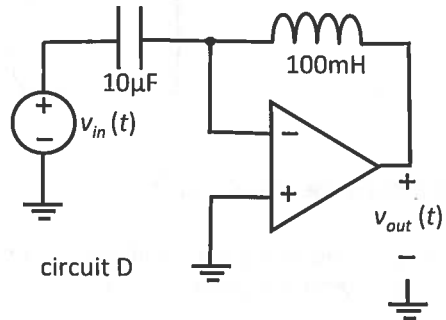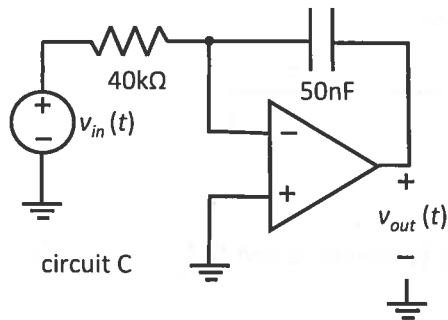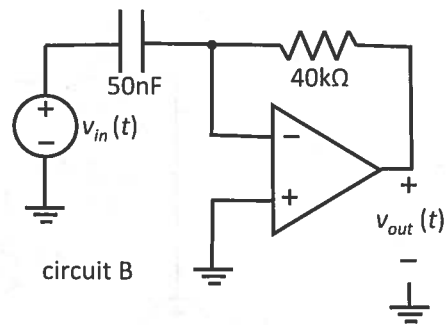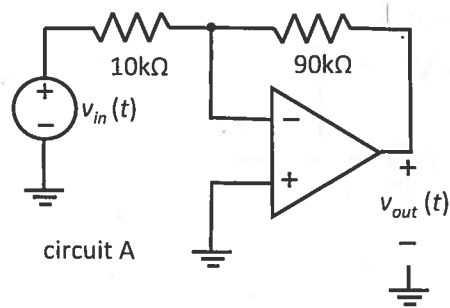3. Consider the circuits below. Assume ideal op-amp behaviour. Answer the questions. [12 pts]



- Give one reason why negative feedback is used in op-amp circuits. [2pts]
- How is  $v_{out}$  related to  $v_{in}$  for circuit A ? [2pts]
- How is  $v_{out}$  related to  $v_{in}$  for circuit B ? [2pts]
- How is  $v_{out}$  related to  $v_{in}$  for circuit C ? [2pts]
- How is  $v_{out}$  related to  $v_{in}$  for circuit D ? [2pts]
- Assume an input voltage  $v_{in}(t) = 1V \sin(2\pi \times 1000Hz \times t)$ , where  $Hz = s^{-1}$ . Which of the circuits above produces an output voltage  $v_{out}(t)$  of largest amplitude?

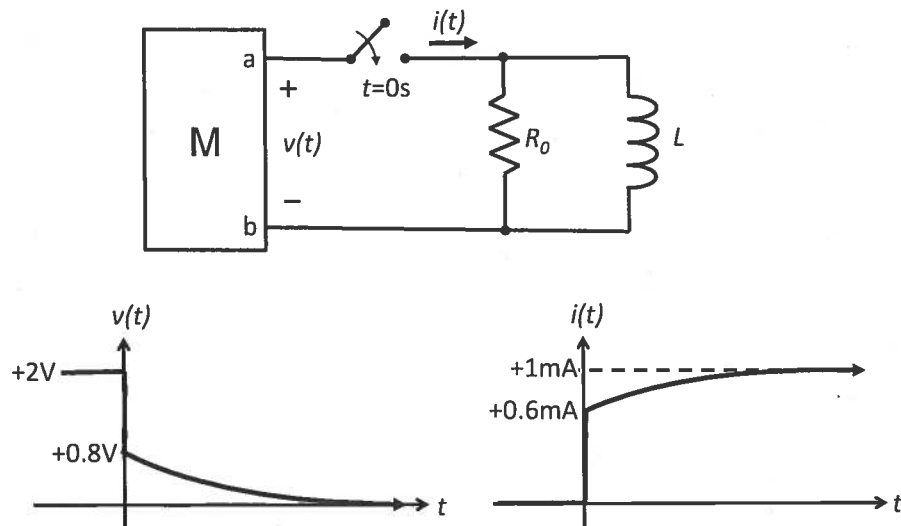4. Consider the circuit below. The circuit M is a Thévenin equivalent circuit. The circuit is in dc steady state for  $t < 0$  with the switch open. The switch closes instantaneously at  $t = 0$ s. The circuit reaches a new dc steady state as  $t \rightarrow \infty$ . The voltage  $v(t)$  and the current  $i(t)$  are plotted versus  $t$ . Answer the questions. [12 pts]



- Give one physical reason why inductor current is continuous. [2pts]
- What is the open circuit voltage of M? [2pts]
- What is the short circuit current of M? [2pts]
- What is the Thévenin resistance of M? [2pts]
- What is the value of  $R_0$ ? [2pts]
- The time constant for  $t > 0$  is found to be  $5\mu s$ . What is the inductance  $L$ ? [2pts]




end

1 a) an element that cannot deliver more energy than it has absorbed [+1]



b) an element with terminal current and voltage related by a linear function or linear operator [+1]

c) conservation of charge [+1]

d) conservation of energy [+1]

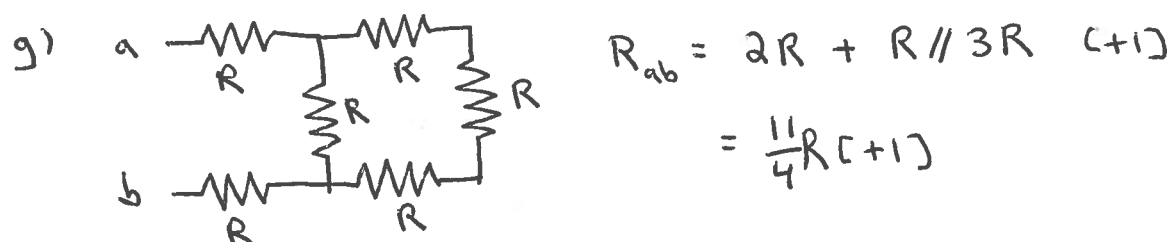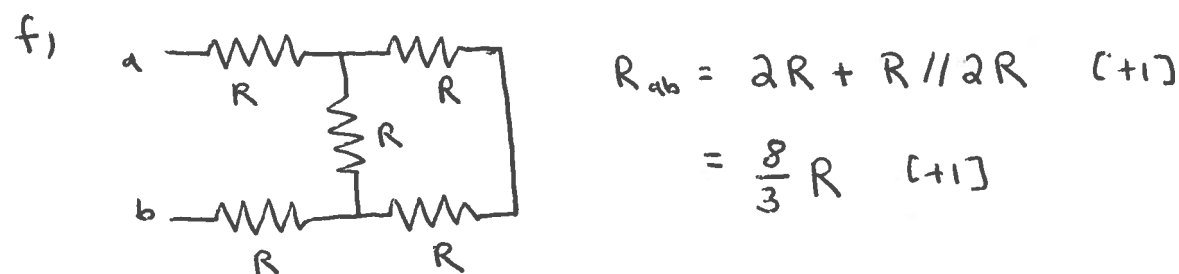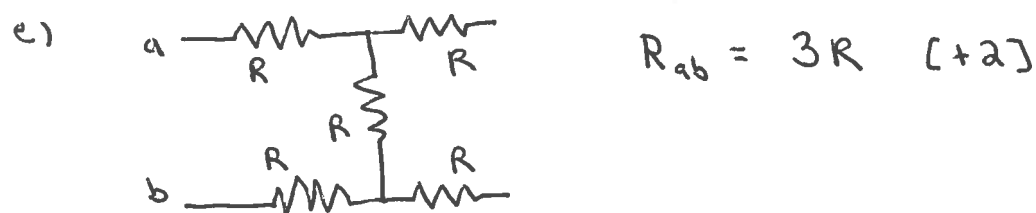

h)

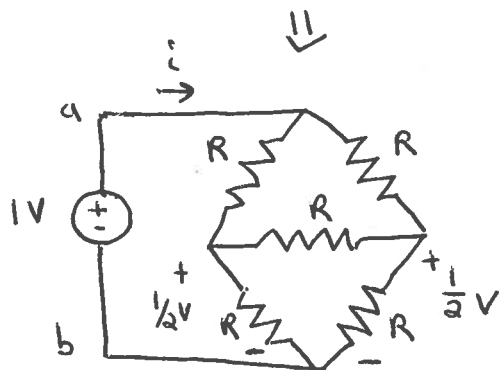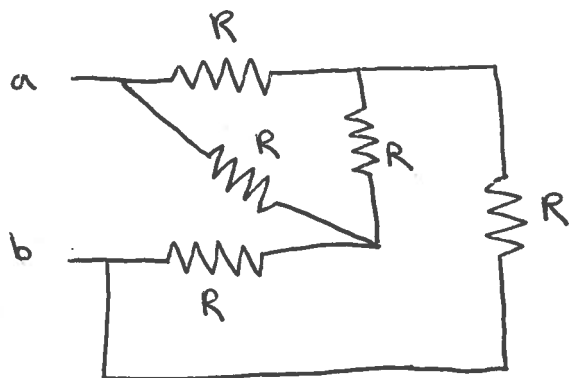

$$i = \frac{\frac{1}{2}V}{R} + \frac{\frac{1}{2}V}{R} = \frac{1V}{R}$$


$$R_{ab} = \frac{1V}{i} \quad (+1)$$

$$= R \quad (+1)$$



- 2 a) a circuit composed of independent sources, dependent sources and resistors is equivalent to a Thévenin circuit [1]

b) Find  $v_{oc}$ . [1]

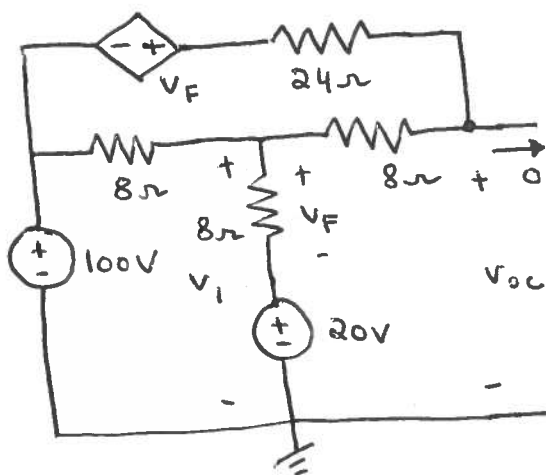

$$0 = \frac{v_1 - 100V}{8\Omega} + \frac{v_1 - 20V}{8\Omega} + \frac{v_1 - (100V + v_F)}{32\Omega}$$

$$v_F = v_1 - 20V$$


$$0 = v_1 \left( \frac{1}{8} + \frac{1}{8} + \frac{1}{32} - \frac{1}{32} \right) + \left( \frac{-100}{8} - \frac{20}{8} - \frac{100}{32} + \frac{20}{32} \right)$$

$$v_1 = 70V \quad v_F = 50V$$

$$v_{oc} = v_1 - 8\Omega \cdot \left( \frac{v_1 - (100V + v_F)}{32\Omega} \right)$$

$$= 90V$$

Find  $i_{sc}$ . [11]

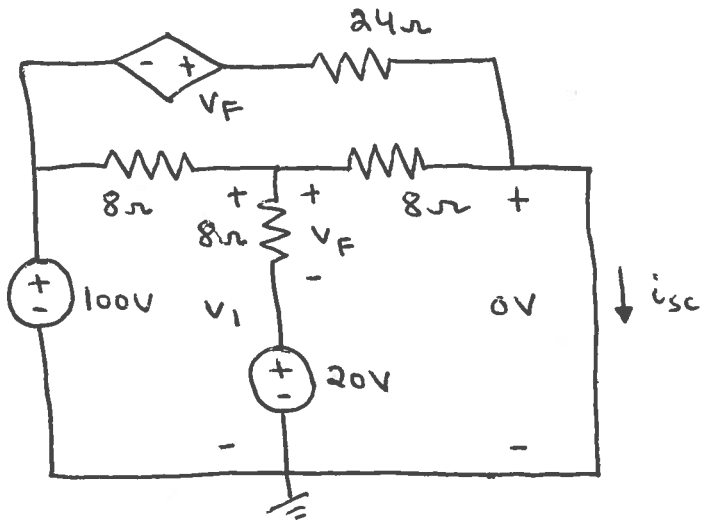

$$0 = \frac{v_1 - 100V}{8\Omega} + \frac{v_1 - 20V}{8\Omega} + \frac{v_1}{8\Omega}$$


$$0 = v_1 \left( \frac{1}{8} + \frac{1}{8} + \frac{1}{8} \right) + \left( -\frac{100}{8} - \frac{20}{8} \right)$$

$$v_1 = 40V \quad v_F = v_1 - 20V = 20V$$


$$i_{sc} = \frac{v_1}{8\Omega} + \frac{100V + v_F}{24\Omega} = 10A$$

$$R_T = \frac{V_{oc}}{i_{sc}} \text{ [11]}$$

$$= 9\Omega$$

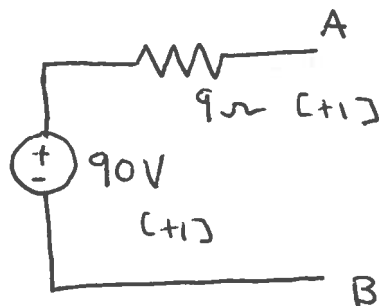


c)

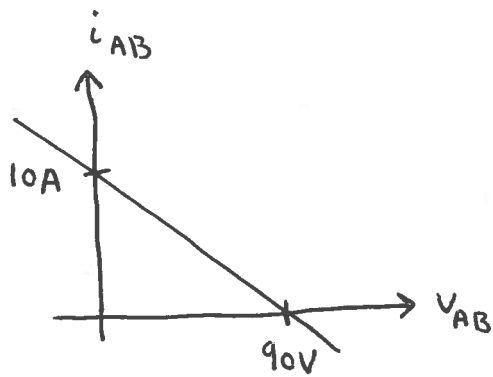

[+1] for shape

[+1] for values

d)

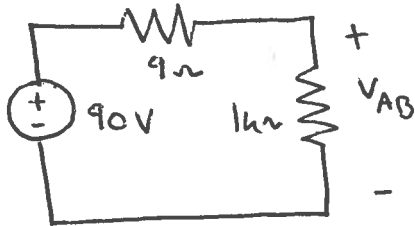

$$V_{AB} = V_{oc} \cdot \frac{1\Omega}{1\Omega + R_T} \quad [+1]$$

$$= 89.20 \text{ V} \quad [+1]$$

e)

$$P_{max} = \frac{V_{oc}}{2} \cdot \frac{i_{sc}}{2} \quad [+1]$$

$$= 225 \text{ W} \quad [+1]$$

3 a) stability  
programmability

$$b) \quad 0 = \frac{-v_{in}}{10k\Omega} + \frac{-v_{out}}{90k\Omega} \quad (+1)$$

$$v_{out} = -9 v_{in} \quad (+1)$$

$$c) \quad 0 = -50nF \cdot \frac{dv_{in}}{dt} + \frac{-v_{out}}{40k\Omega} \quad (+1)$$

$$v_{out} = -2ms \frac{dv_{in}}{dt} \quad (+1)$$

$$d) \quad 0 = \frac{-v_{in}}{40k\Omega} - 50nF \frac{dv_{out}}{dt} \quad (+1)$$

$$v_{out}(t) = v_{out}(t_0) - \frac{1}{2ms} \int_{t_0}^t v_{in}(t') dt' \quad (+1)$$

$$e) \quad 0 = -10\mu F \frac{dv_{in}}{dt} - \frac{1}{100mH} \int v_{out}(t) dt \quad (+1)$$

$$v_{out} = -10^{-6} s^2 \frac{d^2 v_{in}}{dt^2} \quad (+1)$$

f) compare amplitudes:

$$A = 9$$

$$B: \quad 1V \cdot 2ms \cdot 2\pi \cdot 1000 s^{-1} \\ = 12.57 V$$


$$C: \quad 1V \cdot \frac{1}{2ms} \cdot \frac{1}{2\pi \cdot 1000 s^{-1}} \\ = 79.6 mV$$

$$D: \quad 1V \cdot 10^{-6} s^2 \cdot (2\pi \cdot 1000 s^{-1})^2 \\ = 39.48 V$$

circuit D produces the largest amplitude  
output [x2]


4 a) finite voltage  
finite power  
conservation of energy [+2]

b)  $t < 0$

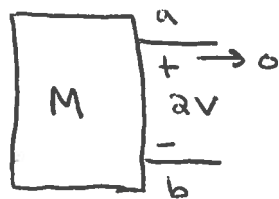

$$V_{oc} = 2V \quad [+2]$$

c)  $t \rightarrow \infty$

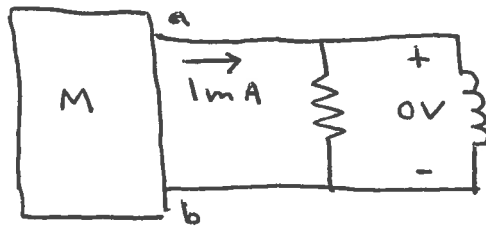


$$i_{sc} = 1mA \quad [+2]$$

$$d) R_T = \frac{V_{oc}}{i_{sc}} \quad [+1]$$

$$= 2k\Omega \quad [+1]$$

e)  $t = 0+$

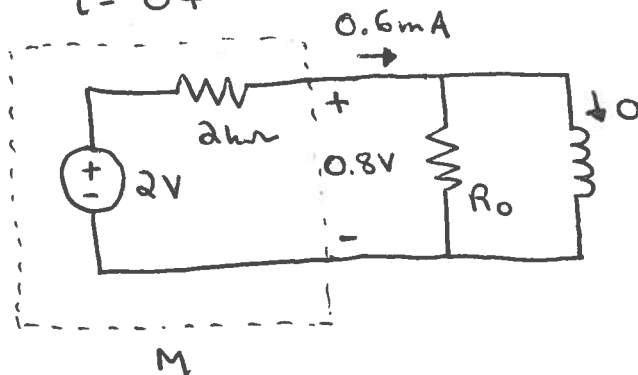

$$R_o = \frac{0.8V}{0.6mA} \quad [+1]$$

$$= 1.333k\Omega \quad [+1]$$

$$f) \quad \tau = \frac{L}{R_{T,ab}} = \frac{L}{R_o // R_T} \quad (+1)$$

$$L = 5 \mu s \cdot 2 k\Omega // 1.333 k\Omega$$

$$= 4 mH \quad (+1)$$