


LAST NAME SOLUTION MCGILL ID# _____

FIRST NAME _____ SIGNATURE _____

- Carefully read the questions
- Show all your work
- Clearly indicate your final answer
- Plagiarism will have important consequences
- Provide symbol for both the multiplier and SI unit in your final answer where applicable
- Only standard calculator is accepted
- You have 45 minutes to complete this quiz

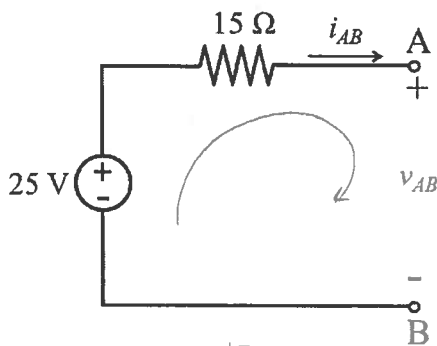Question 1: Consider the Thévenin circuit below showing the voltage variable v_{AB} at the output of the two terminals (A and B) and the current variable i_{AB} . Answer the following questions.


- Derive the equation relating the current variable i_{AB} to the voltage variable v_{AB} . [1 pt]
- Draw the i_{AB} - v_{AB} diagram corresponding to the circuit shown. Have the voltage v_{AB} on the x-axis and the current i_{AB} on the y-axis. Clearly indicate the value of the voltage v_{AB} when $i_{AB} = 0$ A, and the value of the current i_{AB} when $v_{AB} = 0$ V. [2 pt]
- What is the power delivered by the independent voltage source when a load resistor of $20\ \Omega$ is connected between the two terminals A and B? [2 pt]
- Indicate on your diagram in part b), the i_{AB} - v_{AB} point corresponding to the circuit in part c) (i.e., when a load resistor of $20\ \Omega$ is connected). [1 pt]



a) Using KVL & ohm's law $-25V + 15\Omega i_{AB} + v_{AB} = 0$


$$v_{AB} = 25V - 15\Omega i_{AB}$$

b)

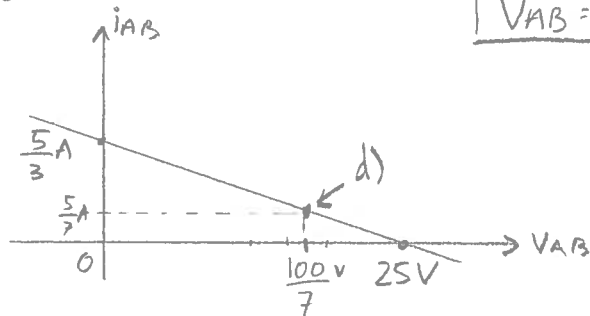

$v_{AB} = 25V$ when $i_{AB} = 0A$

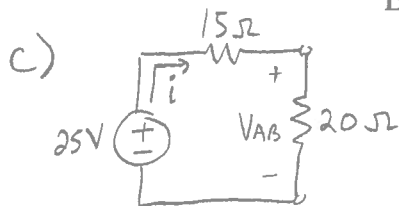$i_{AB} = \frac{25V}{15\Omega} = \frac{5}{3}A$ when $v_{AB} = 0V$



$P = I \cdot V = i \cdot 25V = \frac{25V}{35\Omega} \cdot 25V = \frac{125V^2}{7\Omega} = \frac{125}{7}W = \boxed{17.86W}$




d) $v_{AB} = 25V \cdot \frac{20\Omega}{15\Omega + 20\Omega} = 25V \cdot \frac{4\Omega}{7\Omega} = \frac{100}{7}V = v_{AB}$

$i_{AB} = \frac{25V}{15\Omega} - \frac{v_{AB}}{15\Omega}$ (from a)


$i_{AB} = \frac{5}{3}A - \frac{100V}{7} \cdot \frac{1}{15\Omega} = \frac{5A}{3} - \frac{20V}{21\Omega} = \frac{35-20}{21}A = \frac{15}{21}A = \frac{5}{7}A = i_{AB}$

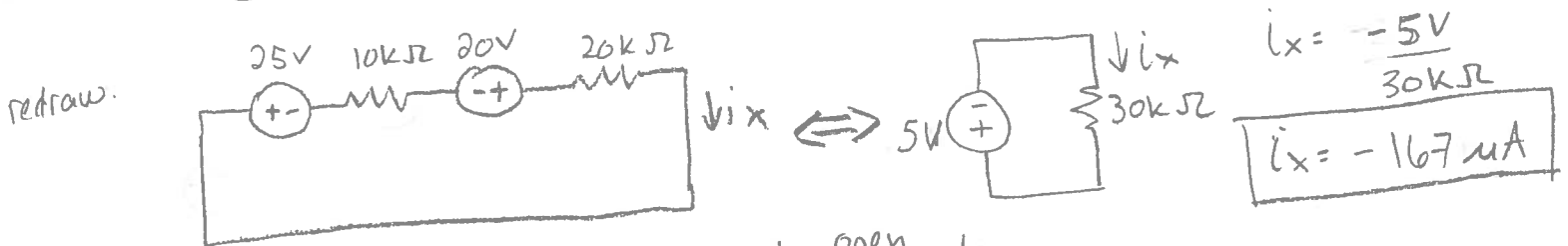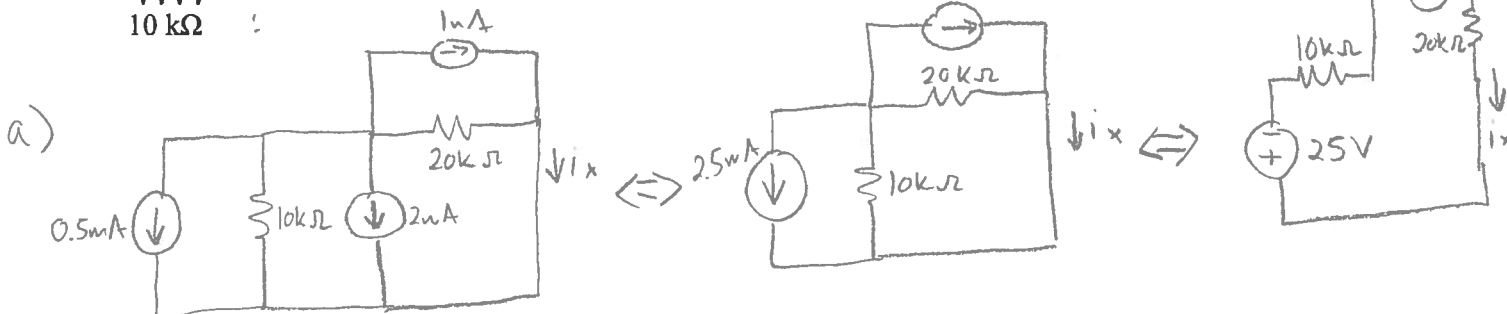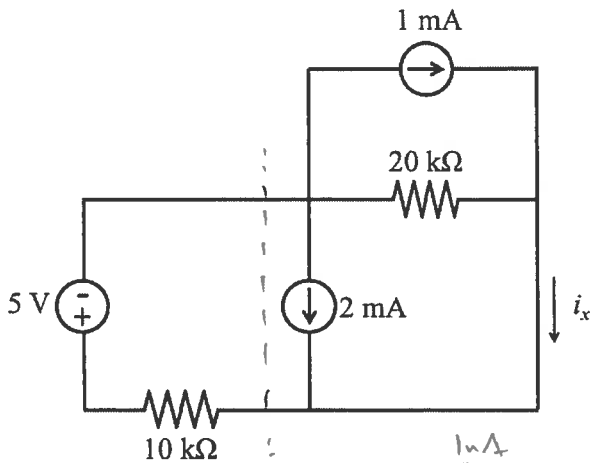Question 2: Considering the circuit below. Answer the following questions.

- Use source transformation to find the value of the current i_x . [3 pt]
- Use the principle of superposition to find the value of the power delivered by the independent voltage source. [3 pt]




b) all src off, 5V on

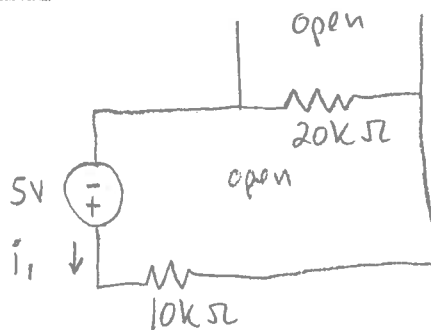

$$i_1 = \frac{5V}{30k\Omega} = \frac{1}{6} \text{ mA}$$

(for b) you need to find the current out of the 5V supply to find power)

all src off, 2mA on

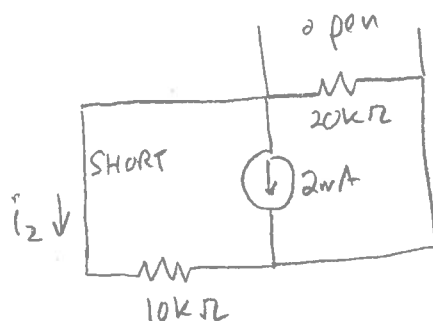

$$i_2 = -2 \text{ mA} \cdot \frac{20k\Omega}{10k\Omega + 20k\Omega}$$

$$i_2 = -2 \cdot \frac{2}{3} \text{ mA} = -\frac{4}{3} \text{ mA}$$

c) all src off, 1mA ON

$$i_3 = -1\text{mA} \cdot \frac{20\text{K}\Omega}{10\text{K}\Omega + 20\text{K}\Omega}$$

$$i_3 = -\frac{2}{3}\text{mA}$$

$$\therefore i = i_1 + i_2 + i_3 = \left(\frac{1}{6} - \frac{4}{3} - \frac{2}{3}\right)\text{mA} = \left(\frac{1}{6} - \frac{6}{3}\right)\text{mA}$$

$$i = -\frac{11}{6}\text{mA}$$

$$P_{wr} = 5\text{V} \cdot \left(-\frac{11}{6}\text{mA}\right) = -\frac{55}{6}\text{mW}$$

power delivered
- 9.167mW

