

## 2. Resistive Circuits

- Circuit Topology
- Kirchhoff's Current and Voltage Laws
- Equivalent Circuits
- Series and Parallel Resistors
- Equivalent Resistance and Circuit Analysis
- Ammeters, Voltmeters, Ohmmeters

# Today's Outline

## **2. Resistive Circuits**

- Circuit Topology
- Kirchhoff's Current Law
- Kirchhoff's Voltage Law

# Circuit Topology

Precise language is needed to describe the parts of a circuit:

**Element:** a model for a physical component


**Node:** a point where multiple elements meet

**Branch:** a path that connects two nodes

**Loop:** a closed path through a circuit with no node passed more than once


**Mesh:** a loop that cannot be broken up into smaller loops

*Examples:*

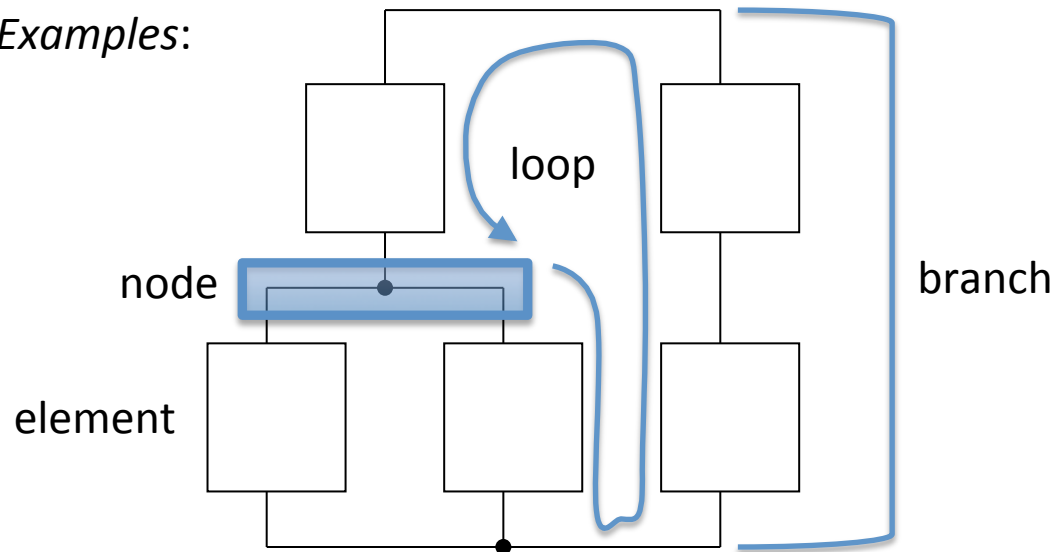
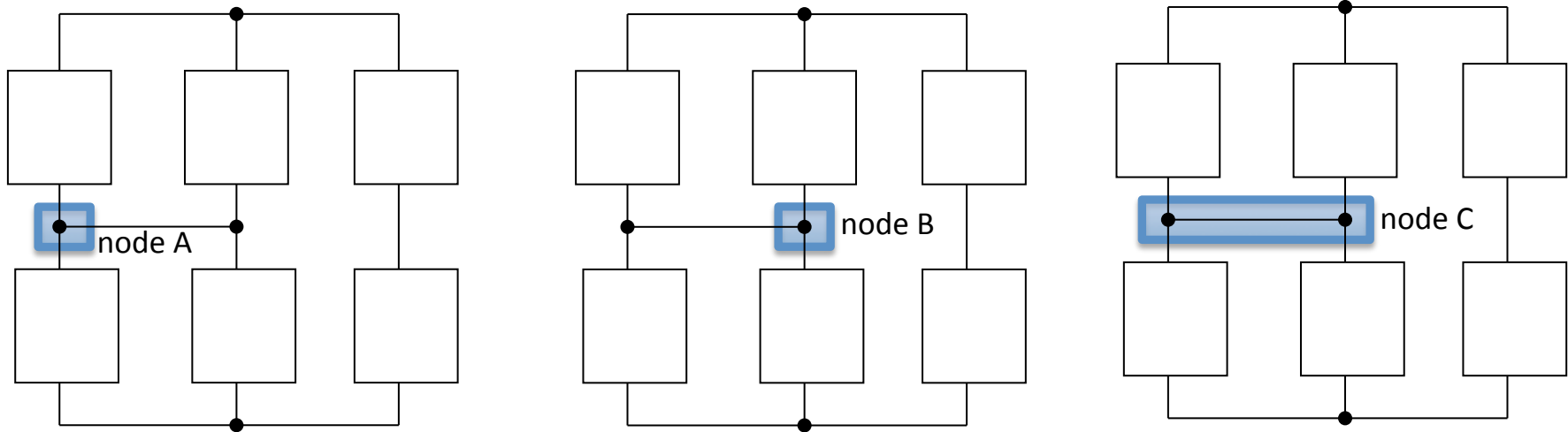
# a note on nodes



A **node**, being the point where multiple elements meet, can be identified in several ways on the same portion of a circuit. Consider the examples below:



It is important to be clear about precisely which node one is discussing.
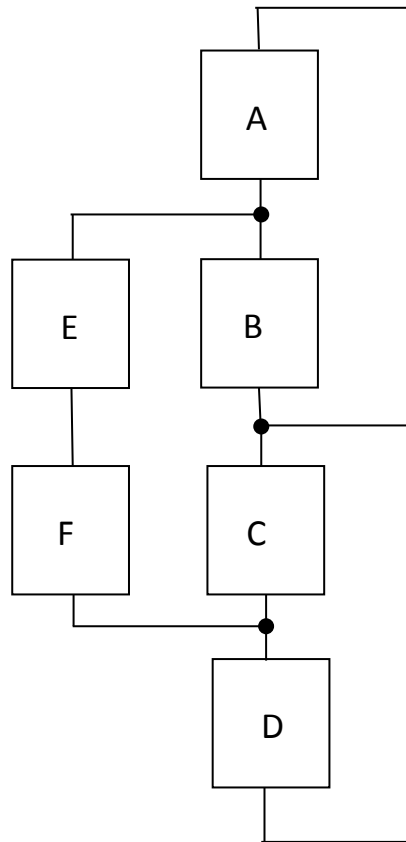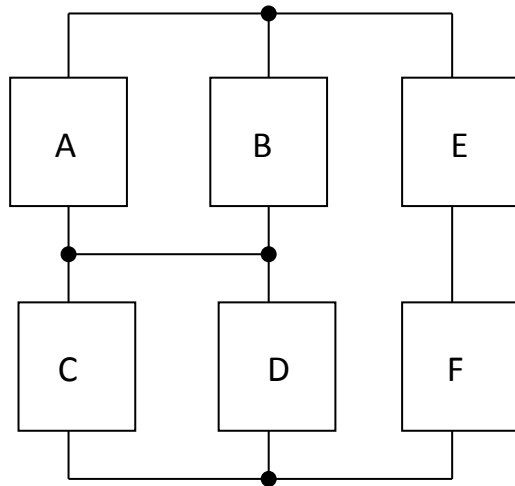
# Circuit Topology


A circuit is defined by the connections between elements, meaning the **topology** of the circuit. The two circuits below are equivalent.



# Kirchoff's Current Law (KCL)

**Kirchoff's Current Law:** The algebraic sum of currents leaving a *node* is zero,

$$\sum_m i_m(t) = 0$$

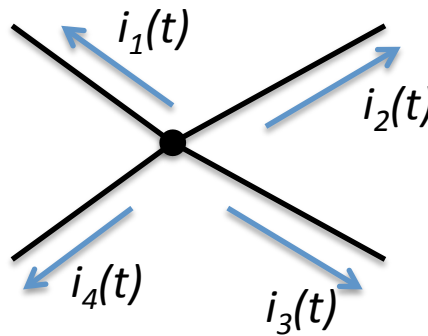


The physical basis for KCL is the ***conservation of charge*** (charge cannot be created or destroyed at a node).



Gustav Robert Kirchhoff  
(1824-1887)

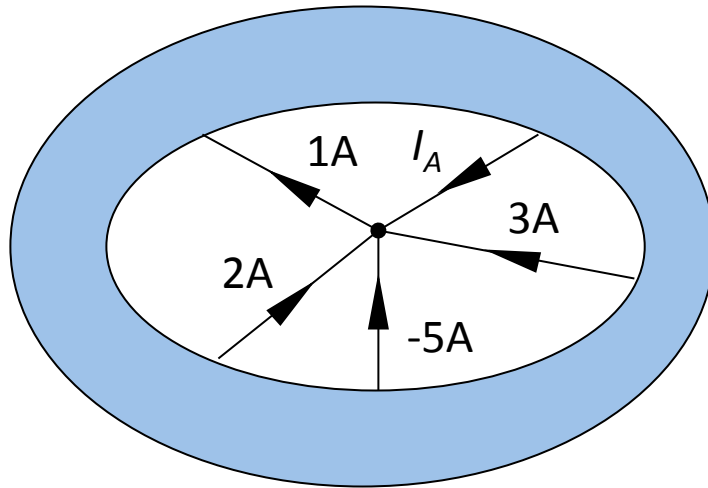
# Example 1

Use KCL to find the unknown current  $I_A$  below.


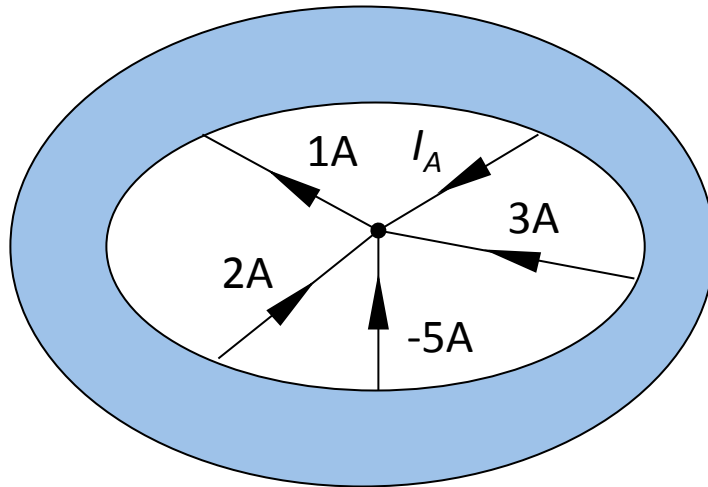
# Example 1

Use KCL to find the unknown current  $I_A$  below.



We sum the currents leaving the node:

$$0 = 1A + (-2A) + 5A + (-3A) + (-I_A)$$


$$I_A = 1A$$



# Kirchoff's Voltage Law (KVL)

**Kirchoff's Voltage Law:** The algebraic sum of voltage drops around a loop is zero,

$$\sum_m v_m(t) = 0$$

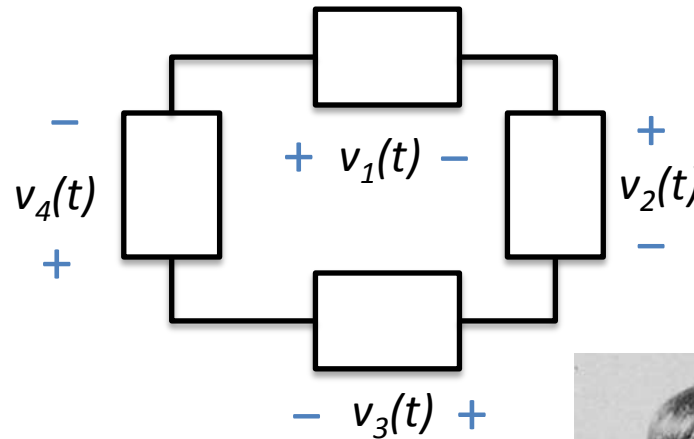


The physical basis for KVL is the ***conservation of energy*** (the potential energy of a particle cannot be increased by traversing a closed loop).



Gustav Robert Kirchhoff  
(1824-1887)

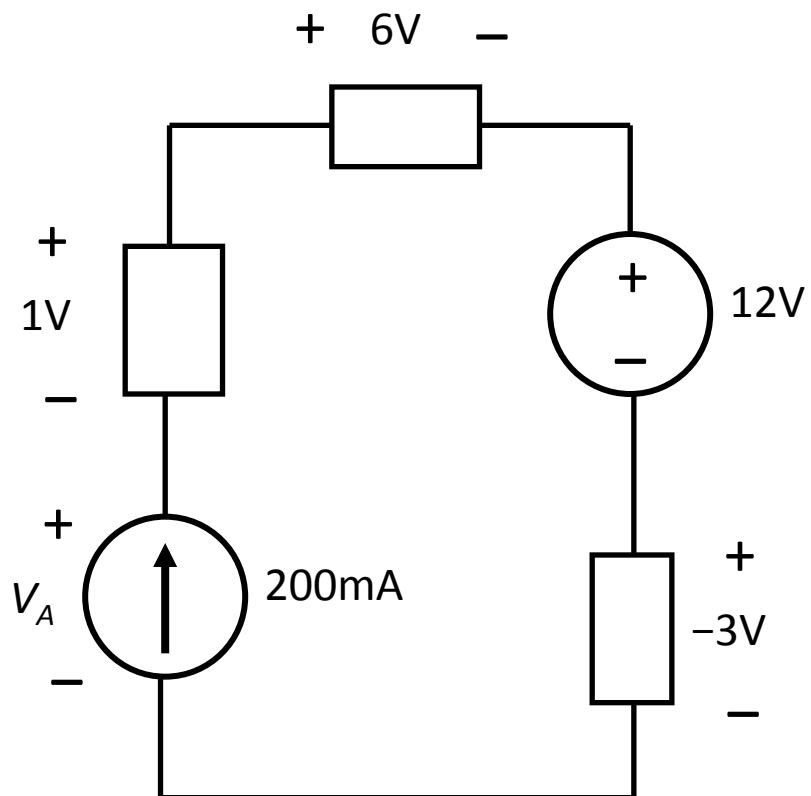
## Example 2

Use KVL to find the unknown voltage  $V_A$  below.


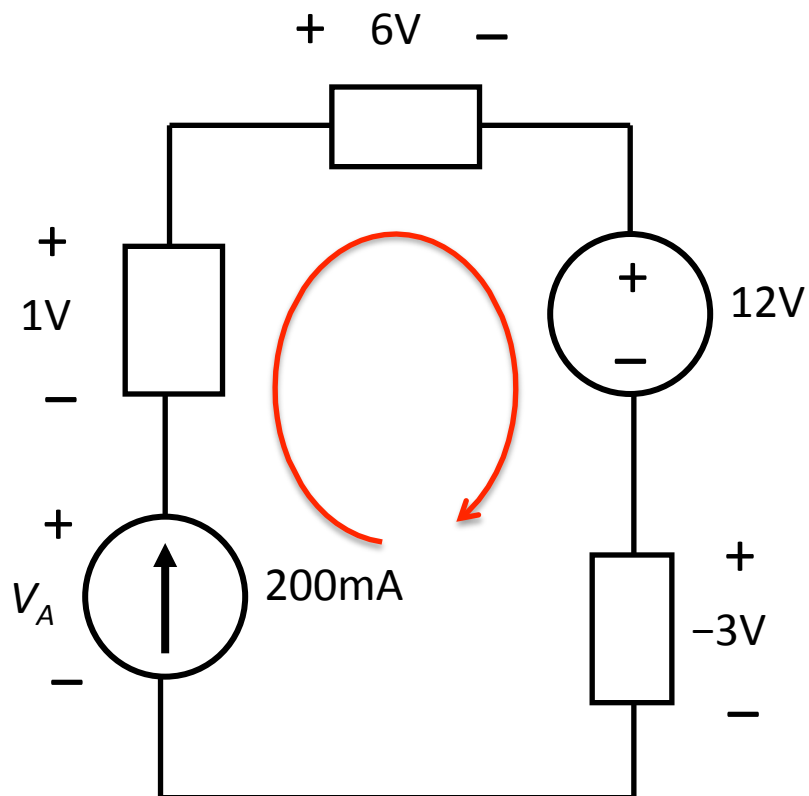
## Example 2

Use KVL to find the unknown voltage  $V_A$  below.



We sum the voltage drops across the loop, choosing a clockwise direction:

$$0 = (-V_A) + (-1V) + 6V + 12V + (-3V)$$


$$V_A = 14V$$

Note that the same answer will be found by taking the loop in counter-clockwise direction.

# Equivalent Forms of KCL and KVL


**KCL:** The algebraic sum of currents leaving a node is zero, as is the algebraic sum of currents entering the node. Also, currents leaving are equal to currents entering.

$$\sum_m i_m(t) = 0$$

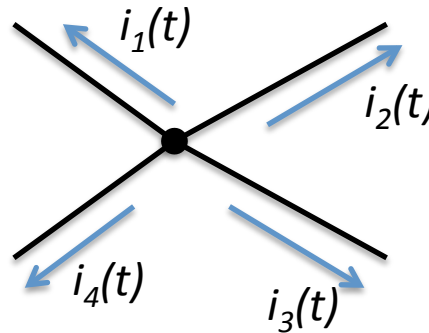

**KVL:** The algebraic sum of voltage drops around a loop is zero, as is the sum of voltage rises around the loop. Also, voltage drops are equal to voltage rises.

$$\sum_m v_m(t) = 0$$

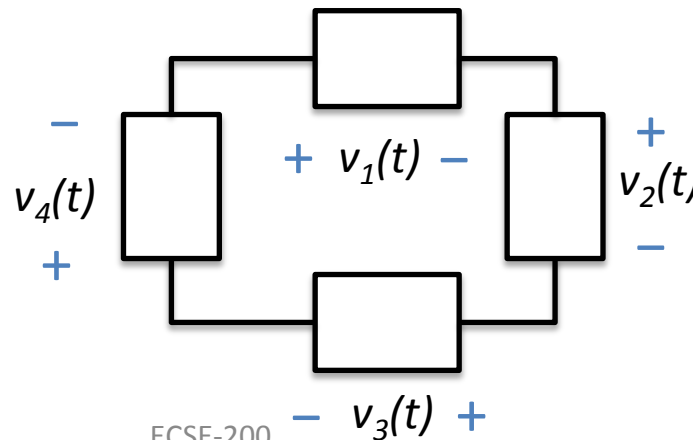


# Keeping it Simple

To keep equations simple, we will use the following explicit forms:

**KCL:** The algebraic sum of currents leaving a node is zero.

**KVL:** The algebraic sum of voltage drops around a loop is zero.

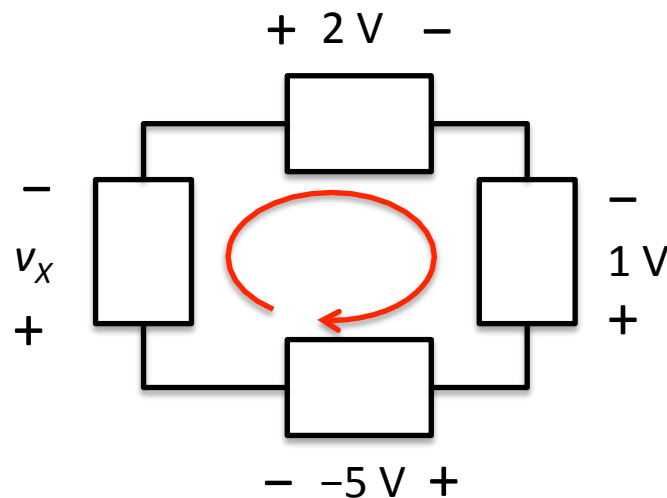
*Example:* KVL can be written in multiple ways for the following single-loop circuit. Note that it is very simple to express everything as a voltage drop.




$$\text{KVL: } 0 = v_x + 2V - (1V) + (-5V)$$

$$v_x = 5V + 1V - 2V = 4V$$

# KCL and KVL

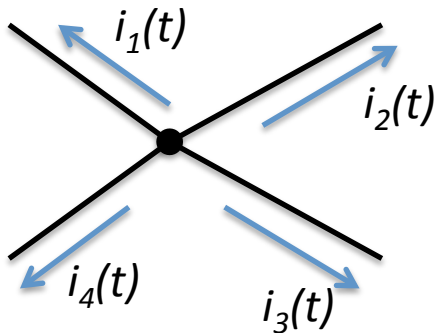

$$\sum_m i_m(t) = 0$$

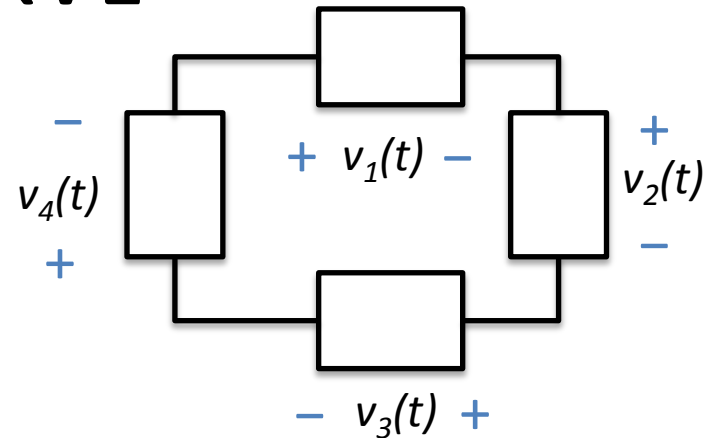


$$\sum_m v_m(t) = 0$$

- KCL and KVL are based on ***fundamental physical laws***
- KCL is satisfied at every node, and KVL is satisfied on every loop, at all time, in a physical circuit
- KCL and KVL *do not* give insight into how charge “knows” where to flow and exchange energy
- KCL and KVL, together with I-V relations for each element, uniquely determine the currents and voltages in a circuit

# Consistency with KCL and KVL


- all physical circuits obey KCL and KVL
- there are connections of elements that are inconsistent with KCL and KVL, and thus represent unphysical situations
- *circuit models incapable of predicting physical circuit behaviour are nonsense!*

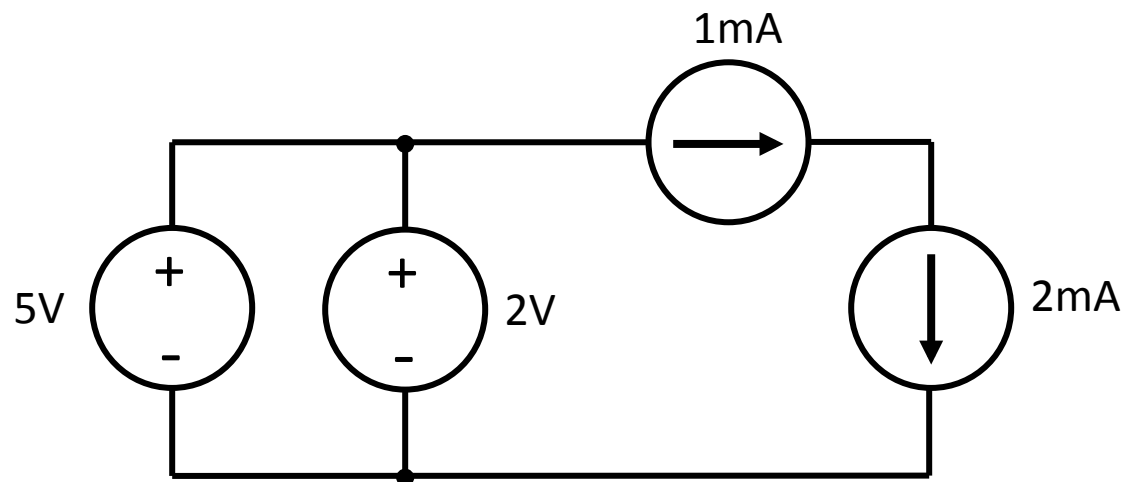Example: what is wrong with the circuit below?


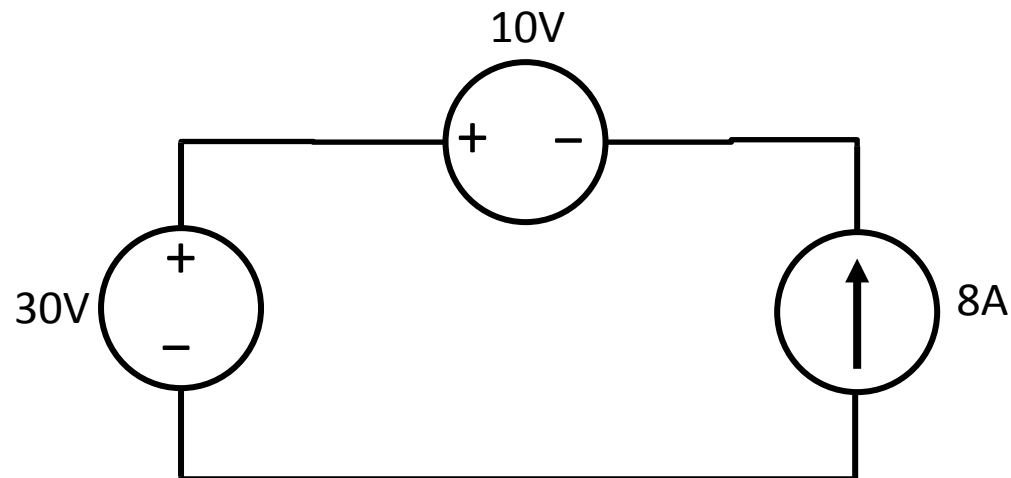
## Example 3


For the circuit below, how much power is being delivered or absorbed by each source?





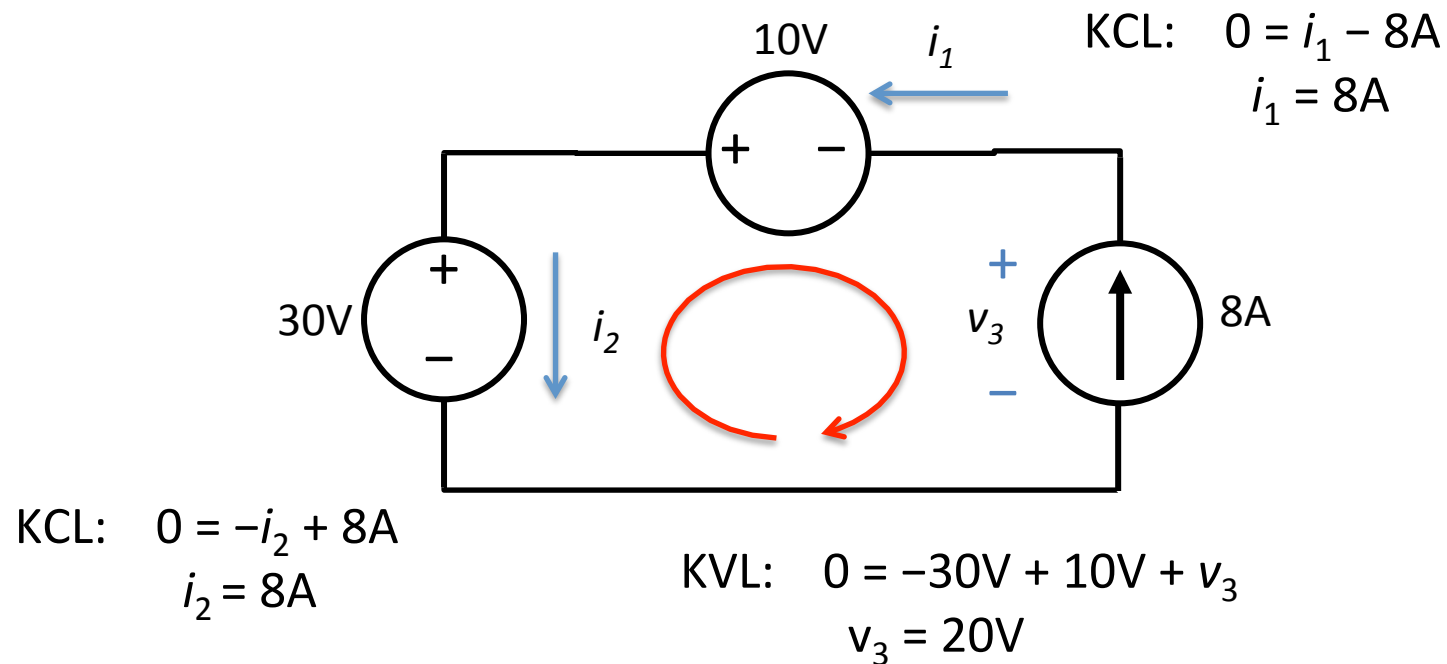
## Example 3

Define the necessary variables, and apply KCL and KVL.


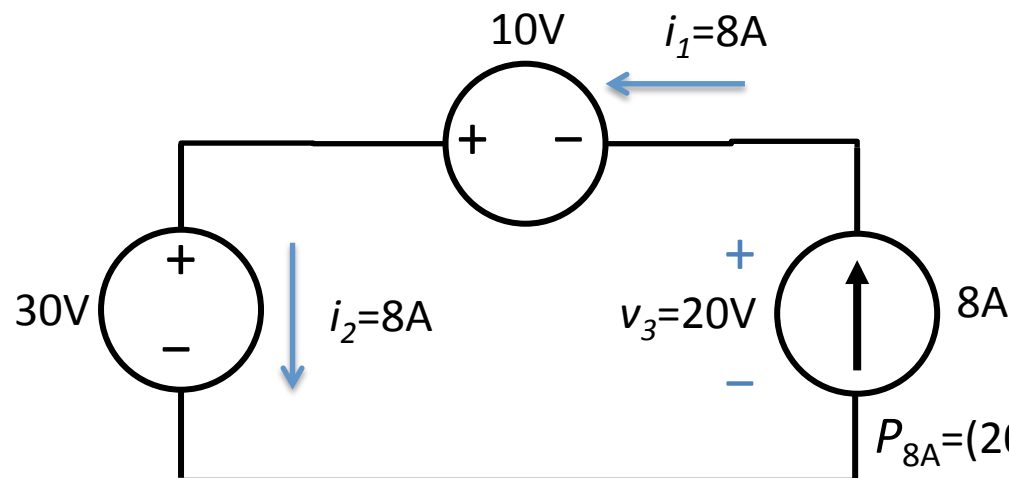
## Example 3

$P_{10V} = (10V)(8A) = 80W$  delivered  
(opposite of passive sign convention)




$P_{30V} = (30V)(8A) = 240W$  absorbed  
(passive sign convention)

$P_{8A} = (20V)(8A) = 160W$  delivered  
(opposite of passive sign convention)


**Note:** The total power delivered by circuit elements to the flowing charges is equal to the total power absorbed by circuit elements from the flowing charges.
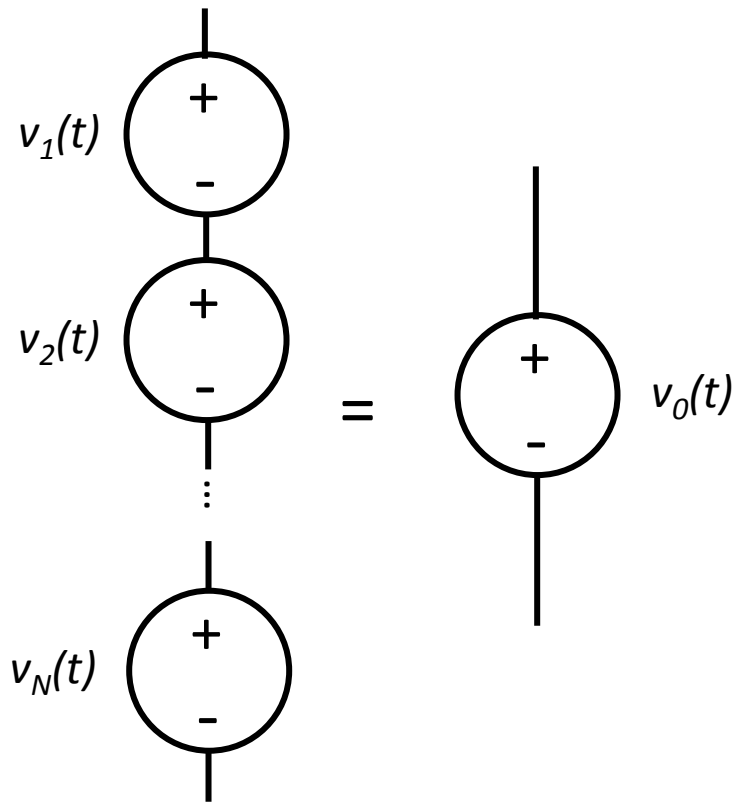
# Exercise

Use KCL, KVL and the definitions of independent voltage sources and independent current sources to show the two following equivalences.


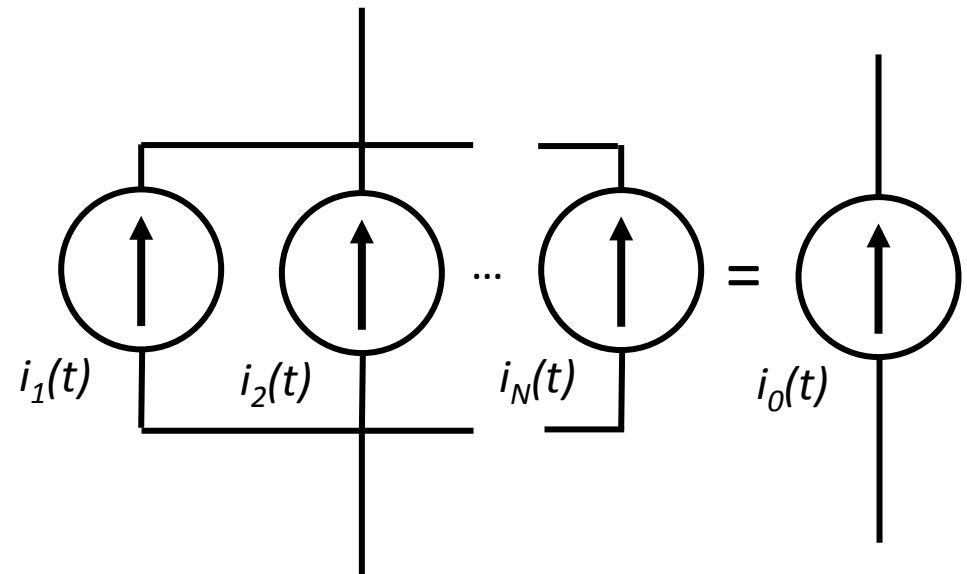
$$v_o(t) = v_1(t) + v_2(t) + \dots + v_N(t)$$



$$i_o(t) = i_1(t) + i_2(t) + \dots + i_N(t)$$