


# ECSE 200 - Electric Circuits 1

## Tutorial 6

ECE Dept., McGill University
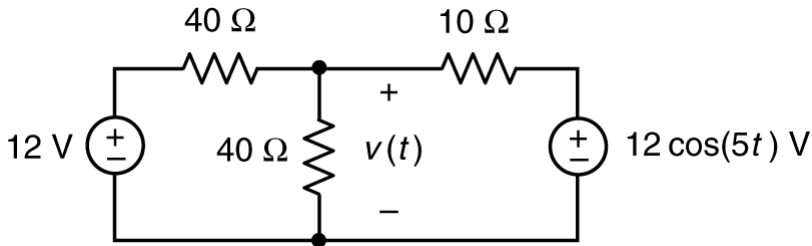
## Problem P 5.3-5



Determine  $v(t)$ , the voltage across the vertical resistor in the circuit in the figure.



## Problem P 5.3-5 Solution
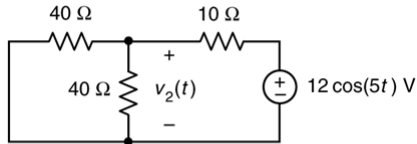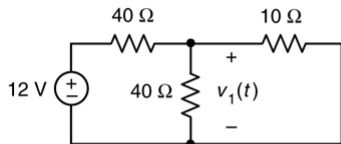
### Solution;

We'll use superposition. Let  $v_1(t)$  be the part of  $v(t)$  due to the voltage source acting alone. Similarly, let  $v_2(t)$  be the part of  $v(t)$  due to the voltage source acting alone. We can use these circuits to calculate  $v_1(t)$  and  $v_2(t)$ .



Notice that  $v_1(t)$  is the voltage across parallel resistors. Using equivalent resistance, we calculate  $40\parallel 10 = 8\ \Omega$ . Next, using voltage division we calculate

$$v_1(t) = \frac{8}{8+40}(12) = 2\text{ V}$$

Similarly  $v_2(t)$  is the voltage across parallel resistors. Using equivalent resistance we first determine  $40\parallel 40 = 20\ \Omega$  and then calculate


$$v_2(t) = \frac{20}{10+20}(12\cos(5t)) = 8\cos(5t)\text{ V}$$

Using superposition

$$v(t) = v_1(t) + v_2(t) = 2 + 8\cos(5t)\text{ V}$$
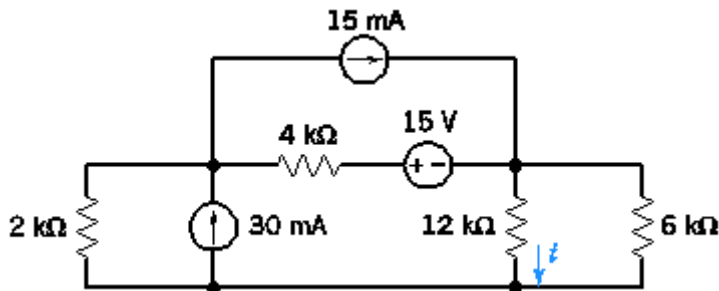
## Problem P 5.3-6



Use superposition to find the value of the current  $i$  in the figure.



## Problem P 5.3-6 Solution
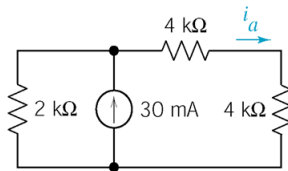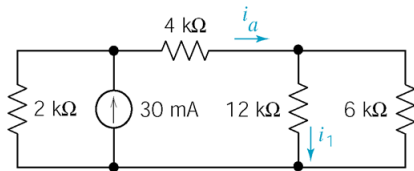
### Solution:



Consider 30 mA source only (open 15 mA and short 15 V sources). Let  $i_1$  be the part of  $i$  due to the 30 mA current source.



$$i_a = 30 \left( \frac{2}{2+8} \right) = 6 \text{ mA} \Rightarrow i_1 = i_a \left( \frac{6}{6+12} \right) = \underline{2 \text{ mA}}$$

Consider 15 mA source only (open 30 mA source and short 15 V source) Let  $i_2$  be the part of  $i$  due to the 15 mA current source.



## Problem P 5.3-6 Solution

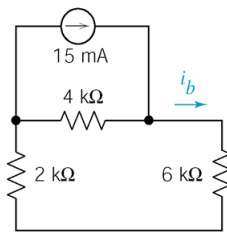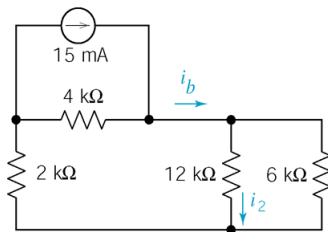

$$i_b = 15 \left( \frac{4}{4+6} \right) = 6 \text{ mA} \Rightarrow i_2 = i_b \left( \frac{6}{6+12} \right) = \underline{2 \text{ mA}}$$

Consider 15 V source only (open both current sources). Let  $i_3$  be the part of  $i$  due to the 15 V voltage source.

## Problem P 5.3-6 Solution

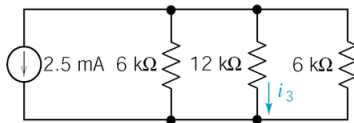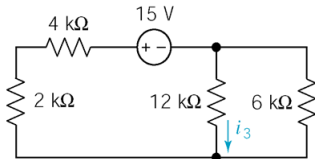


$$i_3 = -2.5 \left( \frac{6 \parallel 6}{(6 \parallel 6) + 12} \right) = -10 \left( \frac{3}{3 + 12} \right) = \underline{-0.5 \text{ mA}}$$

Finally,  $\underline{i = i_1 + i_2 + i_3 = 2 + 2 - 0.5 = 3.5 \text{ mA}}$
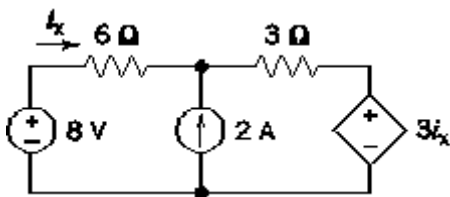
## Problem P 5.3-8


Use superposition to find the value of the current  $i_x$  in the figure.





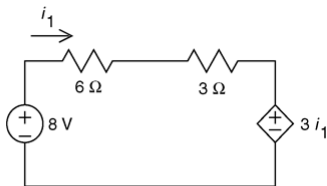
## Problem P 5.3-8 Solution

Consider 8 V source only (open the 2 A source)



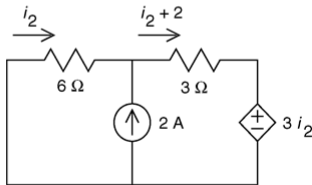Consider 2 A source only (short the 8 V source)



Finally, 
$$i_x = i_1 + i_2 = \frac{2}{3} - \frac{1}{2} = \frac{1}{6} \text{ A}$$

Let  $i_1$  be the part of  $i_x$  due to the 8 V voltage source.

Apply KVL to the supermesh:

$$6(i_1) + 3(i_1) + 3(i_1) - 8 = 0$$

$$i_1 = \frac{8}{12} = \frac{2}{3} \text{ A}$$

Let  $i_2$  be the part of  $i_x$  due to the 2 A current source.


Apply KVL to the supermesh:

$$6(i_2) + 3(i_2 + 2) + 3i_2 = 0$$

$$i_2 = \frac{-6}{12} = -\frac{1}{2} \text{ A}$$

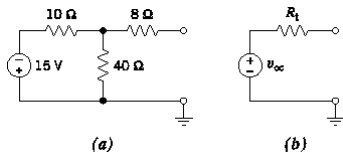
## Problem P 5.4-2

The circuit shown in Figure (b) is the Thvenin equivalent circuit of the circuit shown in Figure (a). Find the value of the open-circuit voltage,  $v_{oc}$ , and Thvenin resistance,  $R_t$ .



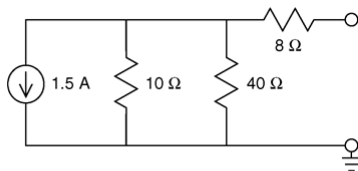
## Problem P 5.4-2 Solution


The circuit from Figure P5.4-2a can be reduced to its Thevenin equivalent circuit in four steps:




(a)

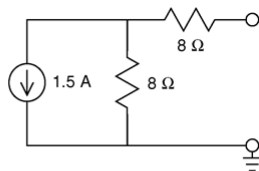

(b)

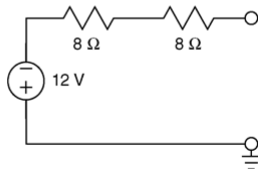

(c)

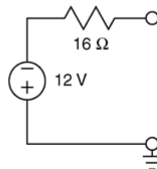


(d)

Comparing (d) to Figure P5.4-2b shows that the Thevenin resistance is  $R_t = 16\ \Omega$  and the open circuit voltage,  $v_{oc} = -12\ \text{V}$ .
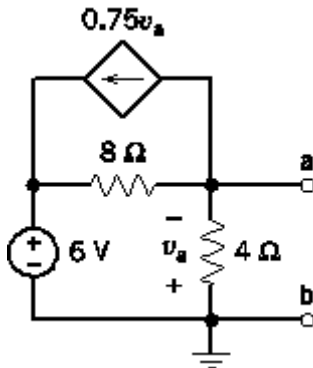
## Problem P 5.4-5

Find the Thvenin equivalent circuit for the circuit shown in the figure.



## Problem P 5.4-5 Solution

### Solution:

Find  $v_{oc}$ :


Notice that  $v_{oc}$  is the node voltage at node a. Express the controlling voltage of the dependent source as a function of the node voltage:

$$v_a = -v_{oc}$$

Apply KCL at node a:

$$-\left(\frac{6 - v_{oc}}{8}\right) + \frac{v_{oc}}{4} + \left(-\frac{3}{4}v_{oc}\right) = 0$$
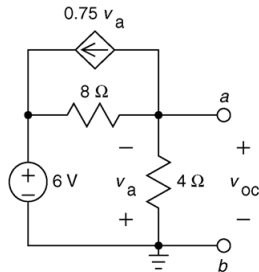
$$-6 + v_{oc} + 2v_{oc} - 6v_{oc} = 0 \Rightarrow v_{oc} = -2 \text{ V}$$



## Problem P 5.4-5 Solution

Find  $R_t$ :

We'll find  $i_{sc}$  and use it to calculate  $R_t$ . Notice that the short circuit forces


$$v_a = 0$$

Apply KCL at node a:

$$-\left(\frac{6-0}{8}\right) + \frac{0}{4} + \left(-\frac{3}{4}0\right) + i_{sc} = 0$$


$$i_{sc} = \frac{6}{8} = \frac{3}{4} \text{ A}$$
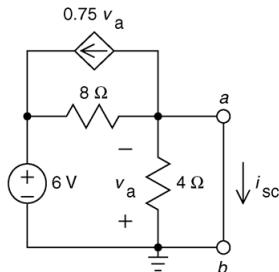
$$R_t = \frac{v_{oc}}{i_{sc}} = \frac{-2}{3/4} = -\frac{8}{3} \Omega$$



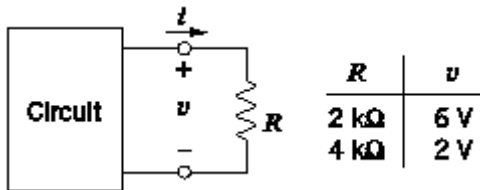
## Problem P 5.4-8

A resistor,  $R$ , was connected to a circuit box as shown in the figure. The voltage,  $v$ , was measured. The resistance was changed, and the voltage was measured again. The results are shown in the table. Determine the Thvenin equivalent of the circuit within the box and predict the voltage,  $v$ , when  $R = 8k\Omega$ . Assume the circuit in the box is a linear circuit.



## Problem P 5.4-8 Solution

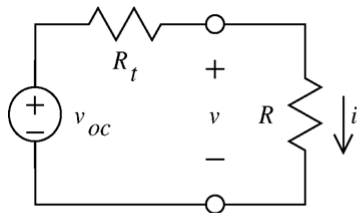

$$v = \frac{R}{R_t + R} v_{oc}$$

From the given data:

$$\left. \begin{aligned} 6 &= \frac{2000}{R_t + 2000} v_{oc} \\ 2 &= \frac{4000}{R_t + 4000} v_{oc} \end{aligned} \right\} \Rightarrow \begin{cases} v_{oc} = 1.2 \text{ V} \\ R_t = -1600 \Omega \end{cases}$$


When  $R = 8000 \Omega$ ,

$$v = \frac{8000}{-1600 + 8000} (1.2) = 1.5 \text{ V}$$



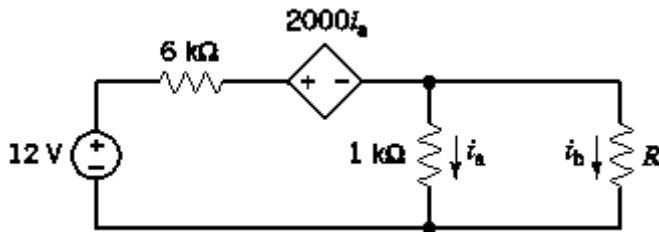
## Problem P 5.4-10

For the circuit of the figure, specify the resistance  $R$  that will cause current  $i_b$  to be 2 mA. The current  $i_a$  has units of amps.




# Problem P 5.4-10 Solution

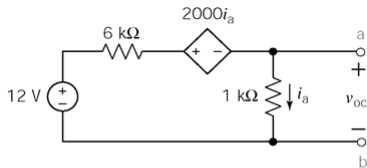

$$-12 + 6000i_a + 2000i_a + 1000i_a = 0$$

$$i_a = 4/3000 \text{ A}$$

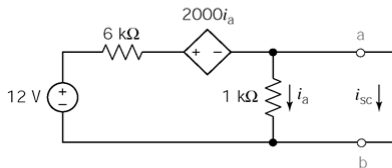
$$v_{oc} = 1000 i_a = \frac{4}{3} \text{ V}$$



$i_a = 0$  due to the short circuit

$$-12 + 6000 i_{sc} = 0 \Rightarrow i_{sc} = 2 \text{ mA}$$
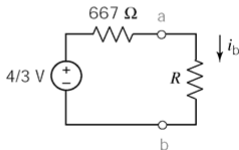
$$R_T = \frac{v_{oc}}{i_{sc}} = \frac{\frac{4}{3}}{.002} = 667 \text{ } \Omega$$



$$i_b = \frac{\frac{4}{3}}{667 + R}$$


$i_b = 0.002 \text{ A}$  requires

$$R = \frac{\frac{4}{3}}{0.002} - 667 = 0$$
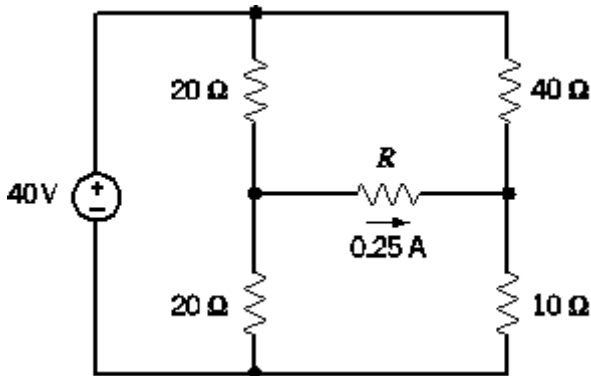
## Problem P 5.4-14


The circuit shown in the figure contains an unspecified resistance,  $R$ . Determine the value of  $R$  in each of the following two ways.

- Write and solve mesh equations.
- Replace the part of the circuit connected to the resistor  $R$  by a Thvenin equivalent circuit. Analyze the resulting circuit.



## Problem P 5.4-14 Solution

(a)

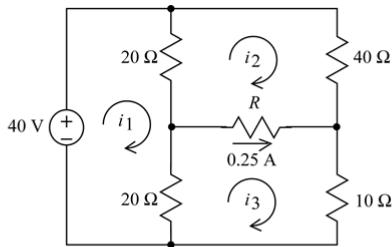

$$i_3 - i_2 = 0.25 \text{ A}$$

Apply KVL to mesh 1 to get

$$20(i_1 - i_2) + 20(i_1 - i_3) - 40 = 0$$

Apply KVL to the supermesh corresponding to the unspecified resistance to get

$$40i_2 + 10i_3 - 20(i_1 - i_3) - 20(i_1 - i_2) = 0$$

## Problem P 5.4-14 Solution

Solving, for example using MATLAB, gives


$$\begin{bmatrix} 0 & -1 & 1 \\ 40 & -20 & -20 \\ -40 & 60 & 30 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0.25 \\ 40 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1.875 \\ 0.750 \\ 1.000 \end{bmatrix}$$

Apply KVL to mesh 2 to get


$$40i_2 + R(i_2 - i_3) - 20(i_1 - i_2) = 0 \Rightarrow R = \frac{20(i_1 - i_2) - 40i_2}{i_2 - i_3} = 30 \, \Omega$$

# Problem P 5.4-14 Solution


(b)

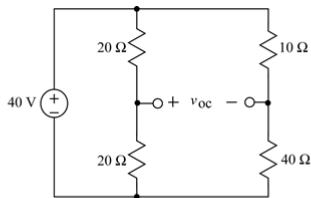
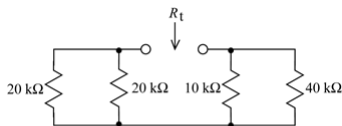
$$v_{oc} = \left( \frac{20}{20+20} \right) 40 - \left( \frac{40}{10+40} \right) 40 = -12 \text{ V}$$




$$R_t = 18 \Omega$$

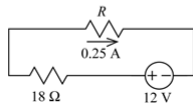

$$0.25 = \frac{12}{18+R} \Rightarrow R = 30 \Omega$$

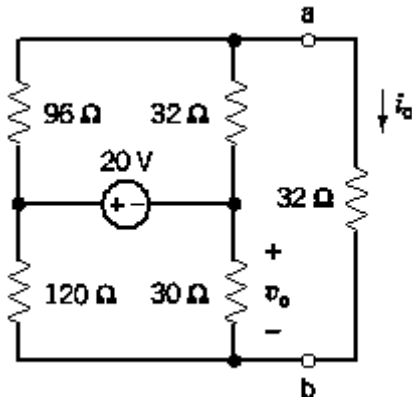
## Problem P 5.4-15

Consider the circuit shown in the figure. Replace the part of the circuit to the left of terminals  $ab$  by its Thvenin equivalent circuit. Determine the value of the current  $i_o$ .



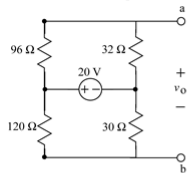
# Problem P 5.4-15 Solution

Find the Thevenin equivalent circuit for the part of the circuit to the left of the terminals a-b.




Using voltage division twice
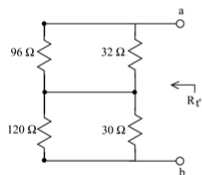
$$v_{oc} = \frac{32}{32+96} 20 - \frac{30}{120+30} 20 = 5 - 4 = 1 \text{ V}$$



$$R_t = (96 \parallel 32) + (120 \parallel 30) = 24 + 24 = 48 \Omega$$

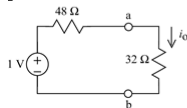Replacing the part of the circuit to the left of terminals a-b by its Thevenin equivalent circuit gives




$$i_o = \frac{1}{48+32} = 0.0125 \text{ A} = 12.5 \text{ mA}$$

(checked: LNAP 5/24)



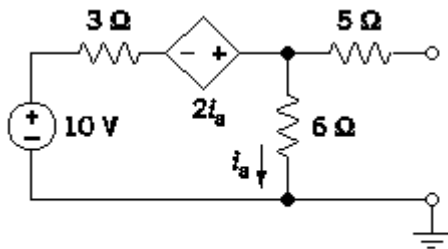
## Problem P 5.5-5

The circuit shown in Figure (b) is the Norton equivalent circuit of the circuit shown in Figure (a). Find the value of the short-circuit current,  $i_{sc}$ , and Thvenin resistance,  $R_t$ .



(a)

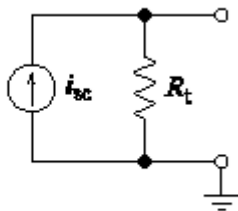

(b)

## Problem P 5.5-5 Solution

To determine the value of the short circuit current,  $i_{sc}$ , we connect a short circuit across the terminals of the circuit and then calculate the value of the current in that short circuit. Figure (a) shows the circuit from Figure 5.6-4a after adding the short circuit and labeling the short circuit current. Also, the meshes have been identified and labeled in anticipation of writing mesh equations. Let  $i_1$  and  $i_2$  denote the mesh currents in meshes 1 and 2, respectively.

In Figure (a), mesh current  $i_2$  is equal to the current in the short circuit. Consequently,  $i_2 = i_{sc}$ . The controlling current of the CCVS is expressed in terms of the mesh currents as

$$i_a = i_1 - i_2 = i_1 - i_{sc}$$

Apply KVL to mesh 1 to get

$$3i_1 - 2(i_1 - i_2) + 6(i_1 - i_2) - 10 = 0 \Rightarrow 7i_1 - 4i_2 = 10 \quad (1)$$

Apply KVL to mesh 2 to get

$$5i_2 - 6(i_1 - i_2) = 0 \Rightarrow -6i_1 + 11i_2 = 0 \Rightarrow i_1 = \frac{11}{6}i_2$$

Substituting into equation 1 gives

$$7\left(\frac{11}{6}i_2\right) - 4i_2 = 10 \Rightarrow i_2 = 1.13 \text{ A} \Rightarrow i_{sc} = 1.13 \text{ A}$$

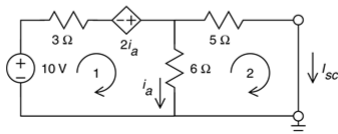


Figure (a) Calculating the short circuit current,  $i_{sc}$ , using mesh equations.

## Problem P 5.5-5 Solution

To determine the value of the Thevenin resistance,  $R_t$ , first replace the 10 V voltage source by a 0 V voltage source, i.e. a short circuit. Next, connect a current source across the terminals of the circuit and then label the voltage across that current source as shown in Figure (b). The Thevenin resistance will be calculated from the current and voltage of the current source as

$$R_t = \frac{v_T}{i_T}$$

In Figure (b), the meshes have been identified and labeled in anticipation of writing mesh equations. Let  $i_1$  and  $i_2$  denote the mesh currents in meshes 1 and 2, respectively.

In Figure (b), mesh current  $i_2$  is equal to the negative of the current source current. Consequently,  $i_2 = -i_T$ . The controlling current of the CCVS is expressed in terms of the mesh currents as

$$i_a = i_1 - i_2 = i_1 + i_T$$

# Problem P 5.5-5 Solution

Apply KVL to mesh 1 to get

$$3 i_1 - 2(i_1 - i_2) + 6(i_1 - i_2) = 0 \Rightarrow 7 i_1 - 4 i_2 = 0 \Rightarrow i_1 = \frac{4}{7} i_2$$

Apply KVL to mesh 2 to get


$$5 i_2 + v_T - 6(i_1 - i_2) = 0 \Rightarrow -6 i_1 + 11 i_2 = -v_T$$

Substituting for  $i_1$  using equation 2 gives

$$-6\left(\frac{4}{7} i_2\right) + 11 i_2 = -v_T \Rightarrow 7.57 i_2 = -v_T$$

Finally,
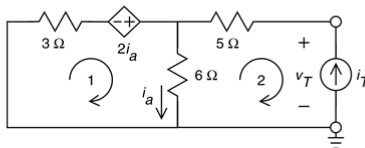
$$R_t = \frac{v_T}{i_T} = \frac{-v_T}{-i_T} = \frac{-v_T}{i_2} = 7.57 \Omega$$



## Problem P 5.5-5 Solution

To determine the value of the open circuit voltage,  $v_{oc}$ , we connect an open circuit across the terminals of the circuit and then calculate the value of the voltage across that open circuit. Figure (c) shows the circuit from Figure 4.6-4a after adding the open circuit and labeling the open circuit voltage. Also, the meshes have been identified and labeled in anticipation of writing mesh equations. Let  $i_1$  and  $i_2$  denote the mesh currents in meshes 1 and 2, respectively.

In Figure (c), mesh current  $i_2$  is equal to the current in the open circuit. Consequently,  $i_2 = 0$  A. The controlling current of the CCVS is expressed in terms of the mesh currents as


$$i_a = i_1 - i_2 = i_1 - 0 = i_1$$

Apply KVL to mesh 1 to get

$$\begin{aligned} 3i_1 - 2(i_1 - i_2) - 10 &= 0 \Rightarrow 3i_1 - 2(i_1 - 0) + 6(i_1 - 0) - 10 = 0 \\ \Rightarrow i_1 &= \frac{10}{7} = 1.43 \text{ A} \end{aligned}$$


Apply KVL to mesh 2 to get
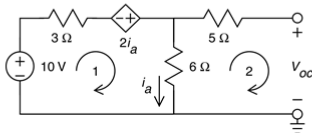
$$5i_2 + v_{oc} - 6(i_1 - i_2) = 0 \Rightarrow v_{oc} = 6(i_1) = 6(1.43) = 8.58 \text{ V}$$



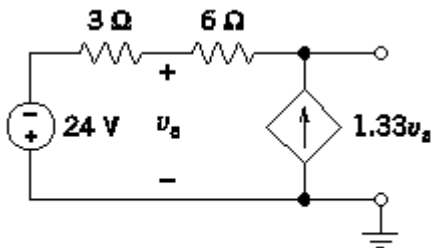
## Problem P 5.5-6

The circuit shown in Figure (b) is the Norton equivalent circuit of the circuit shown in Figure (a). Find the value of the short-circuit current,  $i_{sc}$ , and Thvenin resistance,  $R_t$ .



(a)

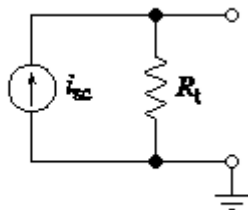

(b)


## Problem P 5.5-6 Solution

Apply KCL at node 2 to get

$$\frac{v_1 - v_2}{3} = \frac{v_2 - v_3}{6} \Rightarrow 2v_1 + v_3 = 3v_2 \Rightarrow -48 = 3v_a \Rightarrow v_a = -16 \text{ V}$$

Apply KCL at node 3 to get
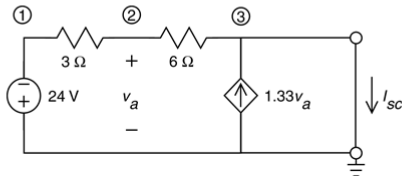
$$\frac{v_2 - v_3}{6} + \frac{4}{3}v_2 = i_{sc} \Rightarrow \frac{9}{6}v_a = i_{sc} \Rightarrow i_{sc} = \frac{9}{6}(-16) = -24 \text{ A}$$



# Problem P 5.5-6 Solution

Apply KCL at node 2 to get


$$\frac{v_1 - v_2}{3} = \frac{v_2 - v_3}{6} \Rightarrow 2v_1 + v_3 = 3v_2 \Rightarrow v_T = 3v_a$$

Apply KCL at node 3 to get

$$\begin{aligned} \frac{v_2 - v_3}{6} + \frac{4}{3}v_2 + i_T &= 0 \Rightarrow 9v_2 - v_3 + 6i_T = 0 \\ &\Rightarrow 9v_a - v_T + 6i_T = 0 \\ &\Rightarrow 3v_T - v_T + 6i_T = 0 \Rightarrow 2v_T = -6i_T \end{aligned}$$

Finally,

$$R_t = \frac{v_T}{i_T} = -3\Omega$$

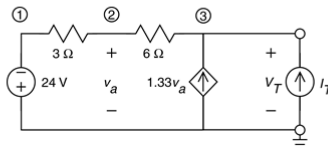



# Problem P 5.5-6 Solution

Apply KCL at node 2 to get


$$\frac{v_1 - v_2}{3} = \frac{v_2 - v_3}{6} \Rightarrow 2v_1 + v_3 = 3v_2 \Rightarrow -48 + v_{oc} = 3v_a$$

Apply KCL at node 3 to get

$$\frac{v_2 - v_3}{6} + \frac{4}{3}v_2 = 0 \Rightarrow 9v_2 - v_3 = 0 \Rightarrow 9v_a = v_{oc}$$


Combining these equations gives
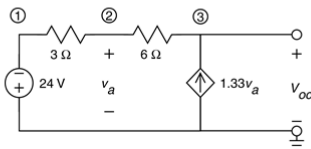
$$3(-48 + v_{oc}) = 9v_a = v_{oc} \Rightarrow v_{oc} = 72 \text{ V}$$



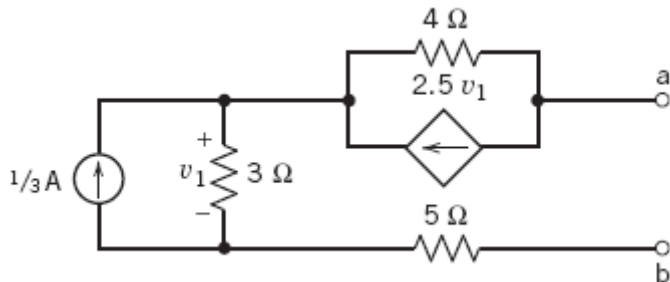
## Problem P 5.5-9

Find the Norton equivalent circuit of this circuit.


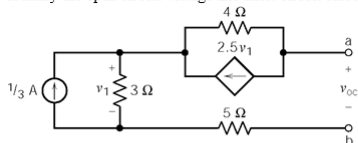
# Problem P 5.5-9 Solution


Identify the open circuit voltage and short circuit current.



$$v_1 = \left(\frac{1}{3}\right)3 = 1 \text{ V}$$

Then
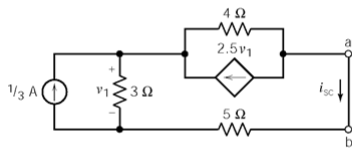
$$v_{oc} = v_1 - 4(2.5 v_1) = -9 \text{ V}$$



$$v_1 = 3\left(\frac{1}{3} - i_{sc}\right) = 1 - 3 i_{sc}$$

$$4(2.5 v_1 + i_{sc}) + 5 i_{sc} - v_1 = 0$$


$$\Rightarrow 9 v_1 + 9 i_{sc} = 0$$

$$9(1 - 3 i_{sc}) + 9 i_{sc} = 0 \Rightarrow i_{sc} = \frac{1}{2} \text{ A}$$

The Thevenin resistance is


$$R_t = \frac{-9}{0.5} = -18 \Omega$$

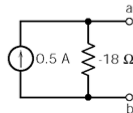Finally, the Norton equivalent circuit is



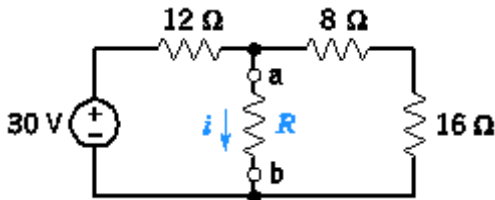
## Problem P 5.5-12

Use Nortons theorem to formulate a general expression for the current  $i$  in terms of the variable resistance  $R$  shown in the figure.




## Problem P 5.5-12 Solution

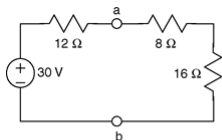

$$R_t = \frac{12 \times 24}{12 + 24} = \frac{12 \times 24}{36} = 8 \, \Omega$$
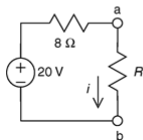
$$v_{\alpha} = \frac{24}{12 + 24}(30) = 20 \, \text{V}$$



$$i = \frac{20}{8 + R}$$

Thank you !