

# ECSE 200 - Electric Circuits 1

## Tutorial 3

ECE Dept., McGill University

# Recall

- **N Resistors in series**

$$R_{eq} = \sum_{i=1}^{i=N} R_i$$

The current passes through each resistor is the same. However, the voltage of  $i$ th component is

$$V_i = \frac{R_i}{R_{eq}} V_{total}$$

- **N Resistors in parallel**


$$R_{eq} = \frac{1}{\sum_{i=1}^{i=N} \frac{1}{R_i}}$$

The voltage across each resistor is the same. However, the current of  $i$ th component is


$$I_i = \frac{R_{eq}}{R_i} I_{total}$$
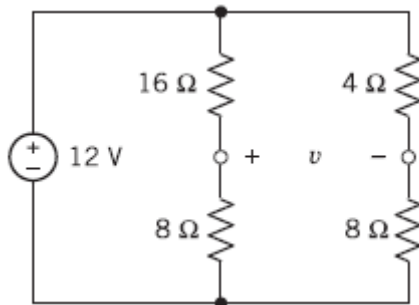
## Problem P 3.3-4

Determine the voltage  $v$  in the circuit shown in the figure.



## Problem P 3.3-4 Solution

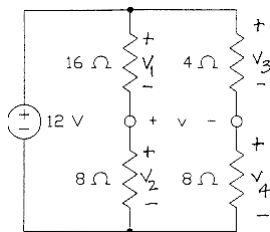

Voltage division

$$v_1 = \frac{16}{16+8} 12 = 8 \text{ V}$$

$$v_3 = \frac{4}{4+8} 12 = 4 \text{ V}$$

$$\text{KVL: } v_3 - v - v_1 = 0$$


$$\underline{v = -4 \text{ V}}$$

## Problem P 3.3-6

The input to the circuit shown in the figure is the voltage of the voltage source,  $v_a$ . The output of this circuit is the voltage measured by the voltmeter,  $v_b$ . This circuit produces an output that is proportional to the input, that is  $v_b = kv_a$  where  $k$  is the constant of proportionality.

- Determine the value of the output,  $v_b$ , when  $R = 240\Omega$  and  $v_a = 18(V)$ .
- Determine the value of the power supplied by the voltage source when  $R = 240\Omega$  and  $v_a = 18(V)$ .
- Determine the value of the resistance,  $R$ , required to cause the output to be  $v_b = 2(V)$  when the input is  $v_a = 18(V)$ .
- Determine the value of the resistance,  $R$ , required to cause  $v_b = 0.2v_a$  (that is, the value of the constant of proportionality is  $k = 0.2$ )

### Problem P 3.3-6 Solution

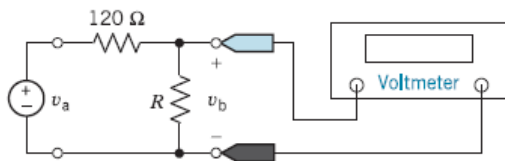

$$\text{a.) } \left( \frac{180}{120+180} \right) 18 = 10.8 \text{ V}$$


$$\text{b.) } 18 \left( \frac{18}{120 + 180} \right) = 1.08 \text{ W}$$

$$c.) \left( \frac{R}{R+120} \right) 18 = 2 \Rightarrow 18R = 2R + 2(120) \Rightarrow R = 15 \, \Omega$$


$$\text{d.) } 0.2 = \frac{R}{R+120} \Rightarrow (0.2)(120) = 0.8R \Rightarrow R = 30 \, \Omega$$
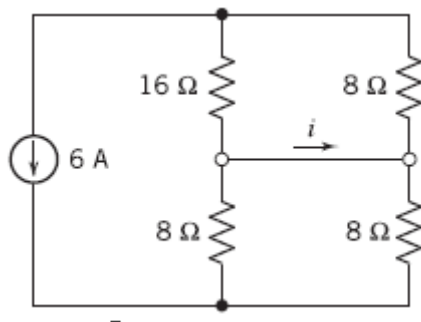
## Problem P 3.4-4

Determine the current  $i$  in the circuit shown in the figure.



## Problem P 3.4-4 Solution

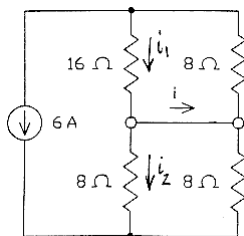

Current Division:

$$i_1 = \frac{8}{16 + 8}(-6) = -2(A)$$

$$i_2 = \frac{8}{8 + 8}(-6) = -3(A)$$


KCL:

$$i = i_1 - i_2 = -2 - (-3) = 1(A)$$



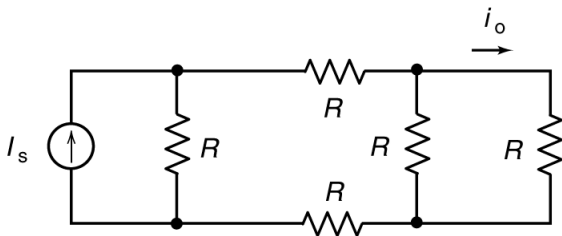
## Problem P 3.4-19


The input to the circuit shown in the figure is the current source current  $I_s$ . The output is the current  $i_o$ . The output of this circuit is proportion to the input, that is  $i_o = kI_s$ . Determine the value of the constant of proportionality,  $k$ .



## Problem P 3.4-19 Solution

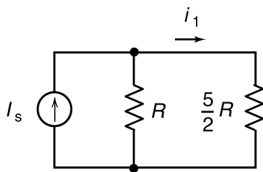

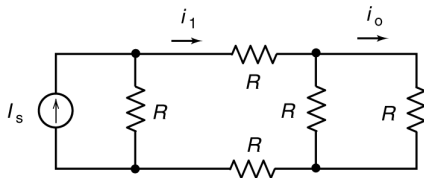
$$i_1 = \left( \frac{\frac{5}{2}R}{R + \frac{5}{2}R} \right) I_s = \frac{2}{7} I_s$$




$$i_o = \frac{R}{R + R} i_1 = \frac{i_1}{2} = \frac{1}{7} I_s \Rightarrow k = \frac{1}{7}$$
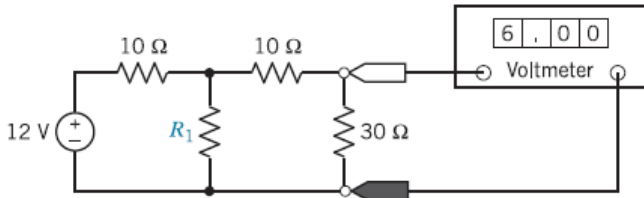
## Problem P 3.6-5


The voltmeter in the circuit shown in the figure shows that the voltage across the  $30\Omega$  resistor is 6 volts. Determine the value of the resistance  $R_1$ . **Hint:** Use the voltage division twice.



## Problem P 3.6-5 Solution

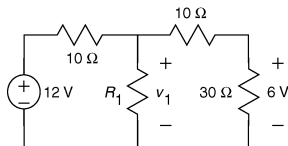

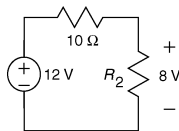
$$6 = \frac{30}{10 + 30} v_1 \Rightarrow v_1 = 8(V)$$




$$8 = \frac{R_2}{R_2 + 10} 12 \Rightarrow R_2 = 20\Omega \Rightarrow$$
$$20 = \frac{R_1(10 + 30)}{R_1 + 10 + 30} \Rightarrow R_1 = 40\Omega$$
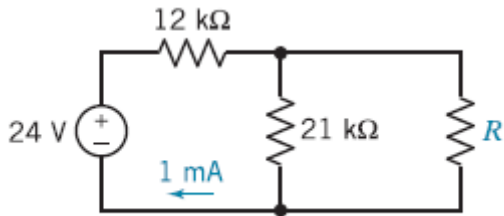
## Problem P 3.6-7

Determine the value of the resistance  $R$  in the figure.



## Problem P 3.6-7 Solution

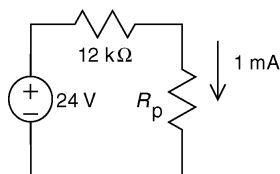


$$1 \times 10^{-3} = \frac{24}{12 \times 10^3 + R_p} \Rightarrow R_p = 12 \times 10^3 = 12 \text{ k}\Omega$$


$$12 \times 10^3 = R_p = \frac{(21 \times 10^3) R}{(21 \times 10^3) + R} \Rightarrow R = 28 \text{ k}\Omega$$
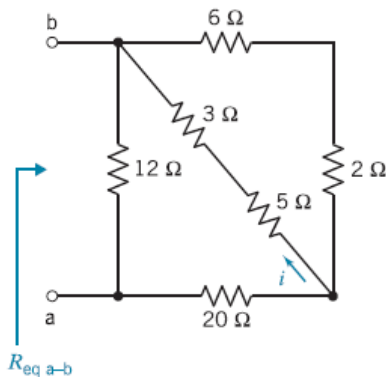
## Problem P 3.6-11


Find  $i$  and  $R_{eq\ ab}$  if  $v_{ab} = 40(V)$  in the circuit of the figure.



## Problem P 3.6-11 Solution

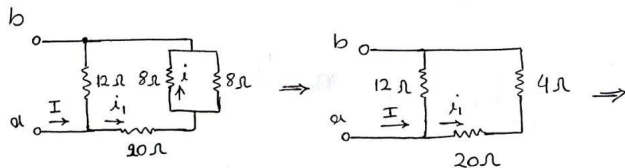
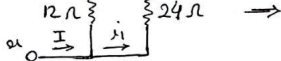
$$R_{eq} = \frac{1}{\frac{1}{12} + \frac{1}{24}} = \frac{24}{\frac{24}{12} + 1} = 8 \Omega$$



$$I = \frac{V_{ab}}{R_{eq}} = \frac{40}{8} = 5 \text{ (A)}$$

$$i_1 = \frac{12}{12 + 24} I = \frac{5}{3} \text{ (A)} \Rightarrow i = \frac{i_1}{2} = \frac{\frac{5}{3}}{2} = \frac{5}{6} \text{ (A)}$$



Thank you !