

ECSE 200 - Electric Circuits 1

Tutorial 1 - Problem set 2

ECE Dept., McGill University

September 20, 2018

Recall

- **Passive element:** a circuit element that **cannot** deliver more energy than it has already received from a circuit. In other words, the absorbed energy of this element is **non-negative**.

$$U(t) = \int_{-\infty}^t p(t') dt' = \int_{-\infty}^t v(t') i(t') dt' \geq 0$$

- **Active element:** a circuit element that **can** deliver more energy than it has already received from a circuit. In other words, the absorbed energy of this element is **non-positive**.

$$U(t) = \int_{-\infty}^t p(t') dt' = \int_{-\infty}^t v(t') i(t') dt' \leq 0$$

Recall (cnt.)

- **Linear circuit element:** a circuit element which has the terminal voltage and current related to each other by a linear function.
- **Ohm's Law:** the voltage drop v across an **ideal resistor** is proportional to the current i flowing through this resistor.

$$v = iR \text{ (V)}$$

⇒ An **idea resistor** is a linear circuit element.

Recall (cnt.)

- **Resistance, R , and Conductance, G :**

$$G = \frac{1}{R} \text{ (S)}, \text{ and } R = \frac{1}{G} \text{ (}\Omega\text{)}$$

- **Power**

$$p(t) = i(t)v(t) = i^2(t)R = \frac{v^2(t)}{R} \text{ (W)}$$

Recall (cnt.)

- **Independent voltage source:** $V_s = \text{const.}$ regardless of I_{V_s}
- **Dependent voltage source:** V_s is independent of I_{V_s} , but is dependent on a voltage or a current elsewhere in the circuit.

- ▶ Voltage-controlled voltage source (VCVS)

$V_{VCVS} = \mu V_0$ (V), where V_0 is a voltage elsewhere in the circuit.

- ▶ Current-controlled voltage source (CCVS)

$V_{CCVS} = r I_0$ (V), where I_0 is a current elsewhere in the circuit.

Recall (cnt.)

- **Independent current source:** $I_s = \text{const.}$ regardless of V_{I_s}
- **Dependent current source:** I_s is independent of V_{I_s} , but is dependent on a voltage or a current elsewhere in the circuit.

- ▶ Voltage-controlled current source (VCCS)


$I_{VCCS} = gV_0$ (A), where V_0 is a voltage elsewhere in the circuit.

- ▶ Current-controlled current source (CCCS)

$I_{CCCS} = \beta I_0$ (A), where I_0 is a current elsewhere in the circuit.

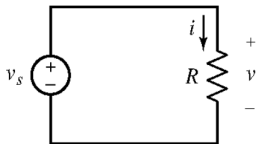
Problem P 2.4-4

Given a voltage source and a resistor connected as shown in the below circuit. Elements connected in parallel have the same voltage. Suppose that $v_s = 24\text{ V}$ and $i = 3\text{ A}$. Calculate the resistance R and the power absorbed by the resistor.



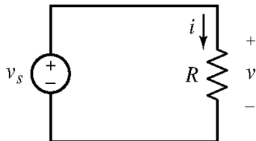Problem P 2.4-4

Given a voltage source and a resistor connected as shown in the below circuit. Elements connected in parallel have the same voltage. Suppose that $v_s = 24 \text{ V}$ and $i = 3 \text{ A}$. Calculate the resistance R and the power absorbed by the resistor.



Solution:

$$R = \frac{v}{i} = \frac{v_s}{i} = \frac{24}{3} = 8 \text{ } (\Omega)$$

$$p = vi = 24 \times 3 = 72 \text{ (W)}$$

Problem P 2.4-7

An electric heater is connected to a constant 250-V source and absorbs 1000 W. Subsequently, this heater is connected to a constant 220-V source. What power does it absorb from the 220-V source ? What is the resistance of the heater ?

Problem summary:

Given a resistor R , $p_1 = 1000 \text{ W}$ when $v_1 = 250 \text{ V} \Rightarrow R = ?$

If $v_2 = 220 \text{ V}$ then $p_2 = ?$

Problem P 2.4-7

An electric heater is connected to a constant 250-V source and absorbs 1000 W. Subsequently, this heater is connected to a constant 220-V source. What power does it absorb from the 220-V source ? What is the resistance of the heater ?

Problem summary:

Given a resistor R , $p_1 = 1000 \text{ W}$ when $v_1 = 250 \text{ V} \Rightarrow R = ?$
If $v_2 = 220 \text{ V}$ then $p_2 = ?$

Solution:

$$\text{Since } p_1 = \frac{v_1^2}{R} \Rightarrow R = \frac{v_1^2}{p_1} = 62.5 \text{ } (\Omega)$$

$$p_2 = \frac{v_2^2}{R} = 774.4 \text{ (W)}$$

Problem P 2.5-4

Given a current source and a voltage source connected as shown in the below circuit. Suppose that $v_s = 12\text{ V}$ and $i_s = 2\text{ A}$. Calculate the power **supplied** by each source.

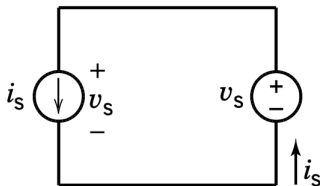


Figure P 2.5-4

Problem P 2.5-4

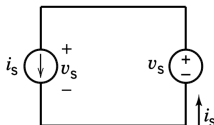


Figure P 2.5-4

- Consider the **voltage source** as a **passive element**, the power received by the voltage source is: $p_{VS} = v_s(-i_s) = 12 \times (-2) = -24$ (W). Hence, the **voltage source supplies** 24 (W).
- Consider the **current source** as a **passive element**, the power received by the current source is: $p_{CS} = v_s i_s = 12 \times 2 = 24$ (W). Hence, the **current source supplies** -24 (W).

Problem P 2.6-1

For the circuit of Fig. P 2.6-1, find the value of the resistance R the power **delivered by** the voltage source.

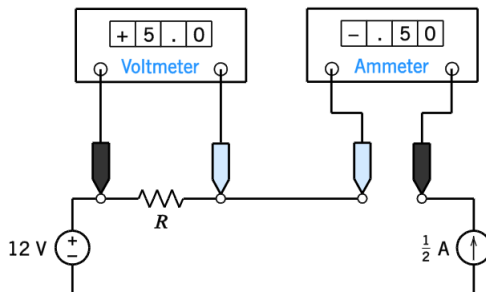


Figure P 2.6-1

Problem P 2.6-1

Solution:

- Since the resistor R is a passive element, therefore
$$R = \frac{5}{-(-0.5)} = 10 \text{ } (\Omega).$$
- Consider the voltage source as an **active element**, the power delivered by this source is $P = V_s I_s = 12 \times (-0.5) = -6 \text{ (W)}.$

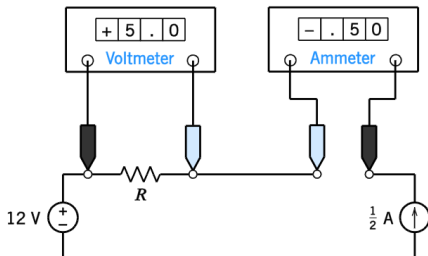


Figure P 2.6-1

Problem P 2.7-2

The ammeter in circuit shown in Fig. P 2.7-2 indicates that $i_a = 2$ (A), and the voltmeter indicates that $v_b = 8$ (V). Determine the gain value, g , of the voltage-controlled current source (VCCS) shown in the circuit.

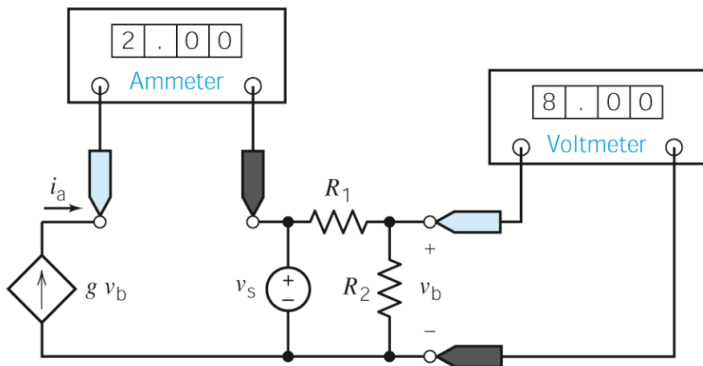


Figure P 2.7-2

Problem P 2.7-2

Solution: The current i_a has a positive value of 2 (A), which indicates that i_a is produced by the VCCS, therefore $i_a = g v_b \Rightarrow g = \frac{i_a}{v_b} = \frac{2}{8} = 0.25 \frac{\text{A}}{\text{V}}$

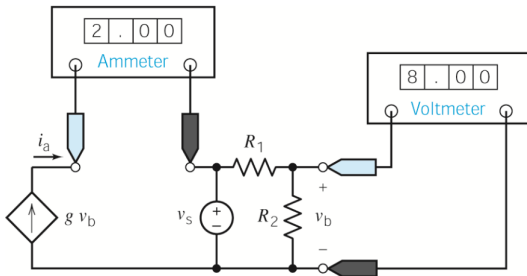


Figure P 2.7-2

Problem P 2.7-4

The voltmeters in circuit shown in Fig. P 2.7-4 indicates that $v_a = 2$ (V), and $v_b = 8$ (V). Determine the gain value, g , of the voltage-controlled voltage source (VCVS) shown in the circuit.

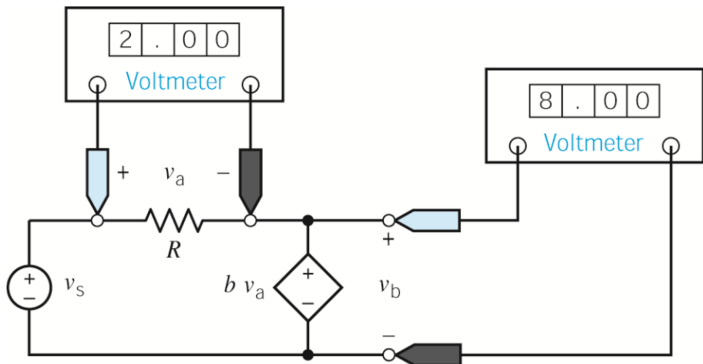


Figure P 2.7-4

Problem P 2.7-4

Solution: $v_b = b v_a \Rightarrow b = \frac{v_b}{v_a} = \frac{8}{2} = 4 \frac{\text{V}}{\text{V}}$

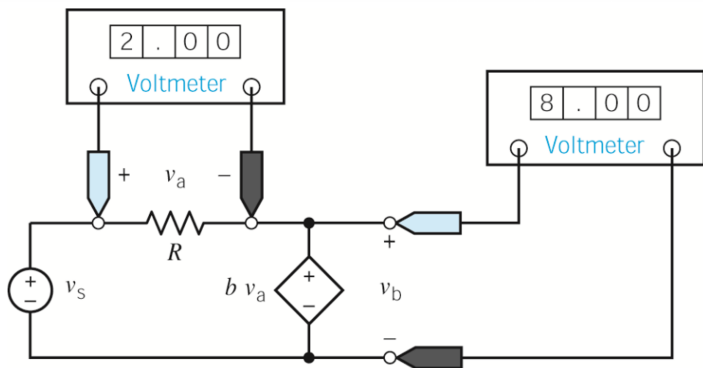


Figure P 2.7-4

Problem P 2.7-5

The values of the current and voltage of each circuit element are shown in Figure P 2.7-5. Determine the values of the resistance, R , and the gain of the dependent source, A .

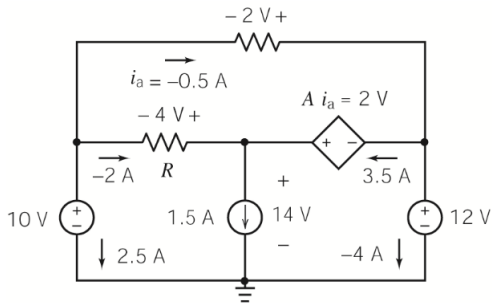


Figure P 2.7-5

Problem P 2.7-5

$$R = \frac{-4}{-2} = 2 \text{ } (\Omega) \text{ and } A = \frac{2}{i_a} = \frac{2}{-0.5} = -4 \left(\frac{\text{V}}{\text{A}} \right)$$

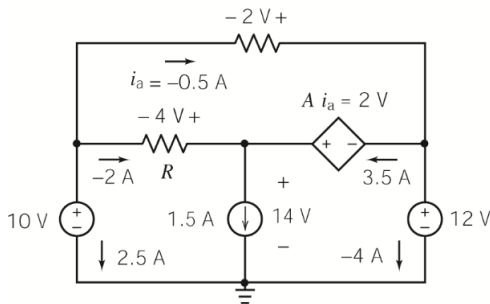


Figure P 2.7-5

Problem P 2.7-6

Find the power supplied by the VCCS in Fig. P 2.7-6.

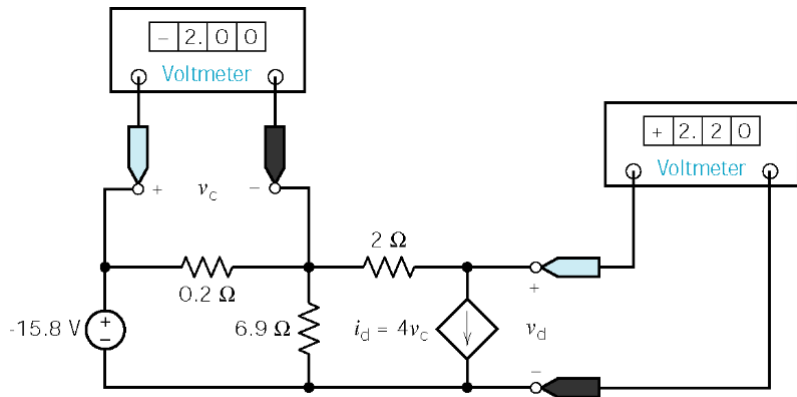


Figure P 2.7-6

Problem P 2.7-6

Solution: From the values indicated by the voltmeters, we have $i_d = 4v_c = 4 \times (-2) = -8$ (A). Consider the VCCS as a passive element, the power absorbed from this source is:

$$p_{VCCS} = v_d i_d = 2.2 \times (-8) = -17.6 \text{ (W)}.$$

Therefore, the power supplied by this source is 17.6 (W).


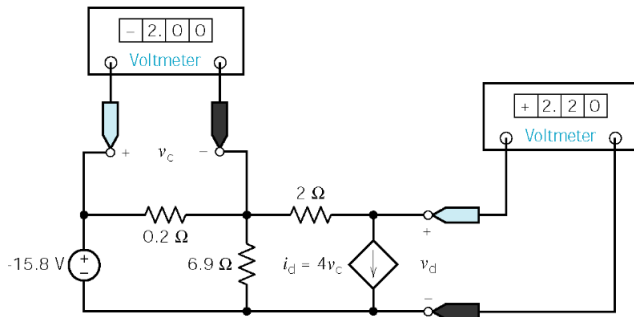


Figure P 2.7-6

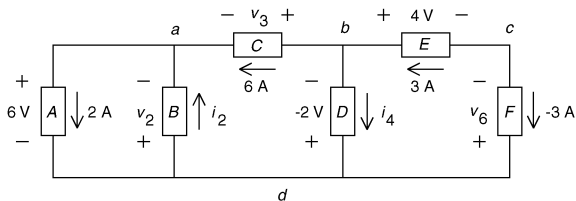Problem P 3.2-2

Determine the values of i_2 , i_4 , v_2 , v_3 and v_6 in the following figure.



Problem P 3.2-2

Solution:


- Apply KCL at node (a) to get $2 + i_2 + 6 = 0 \Rightarrow i_2 = 4(A)$.
- Apply KCL at node b to get $3 = i_4 + 6 \Rightarrow i_4 = -3(A)$.
- Apply KVL to the loop consisting of elements A and B to get $-v_2 - 6 = 0 \Rightarrow v_2 = -6(V)$.
- Apply KVL to the loop consisting of elements C, D, and A to get $-v_3 - (-2) - 6 = 0 \Rightarrow v_4 = -4(V)$.
- Apply KVL to the loop consisting of elements E, F and D to get $4 - v_6 + (-2) = 0 \Rightarrow v_6 = 2(V)$.

Check: The sum of the power supplied by all branches is

$$-(6)(2) - (-6)(-4) - (-4)(6) + (-2)(-3) + (4)(3) + (2)(-3) = -12 - 24 + 24 + 6 + 12 - 6 = 0. \text{ Yes!}$$

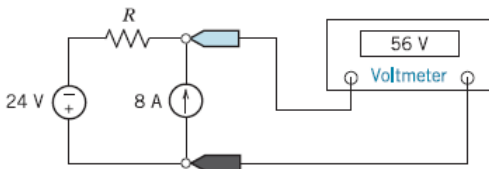Problem P 3.2-8


The voltmeter in Figure P 3.2-8 measures the value of the voltage across the current source to be 56 V. What is the value of the resistance R ? *Hint:* Assume an ideal voltmeter. An ideal voltmeter is equivalent to an open circuit.



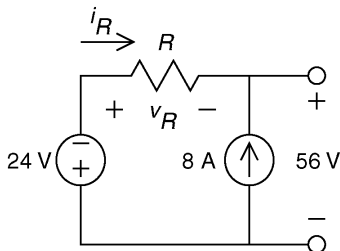Problem P 3.2-8


Solution:

- Apply KCL at node b to get $i_R + 8 = 0 \Rightarrow V_R = -8(A)$.
- Apply KVL to the loop to get $V_R + 56 + 24 = 0 \Rightarrow V_R = -80(V)$.
- Then, we have $R = \frac{-80}{-8} = 10(\Omega)$



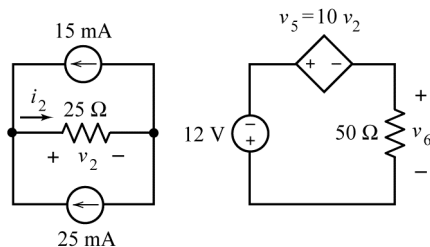Problem P 3.2-20

Determine the value of the voltage v_6 for the circuit shown in the following figure.




Problem P 3.2-20

Solution:

- Apply KCL at the left node: $i_2 = 0.015 + 0.025 = 0.04(A)$
- From Ohm's law $v_2 = 25i_2 = 25(0.04) = 1(V)$
- Use the element equation of the dependent source:
 $v_5 = 10v_2 = 10(V)$
- Apply KVL to the right mesh
 $v_5 + v_6 + 12 = 0 \Rightarrow v_6 = -v_5 - 12 = -10 - 12 = -22(V)$

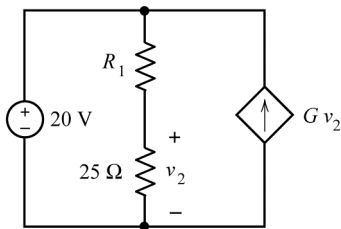Problem P 3.2-25

The voltage source in the circuit shown in Figure P3.2-25 supplies 2 W of power. The value of the voltage across the 25Ω resistor is $v_2 = 4$ V. Determine the values of the resistance R_1 and of the gain, G , of the CCVS.



Problem P 3.2-25

Solution:

- The voltage source current is calculated from the values of the source voltage and power: $i_s = \frac{2}{20} = 0.1(A)$
- Apply KCL at the bottom node to get:
$$i_s + Gv_2 = \frac{v_2}{25} \Rightarrow 0.1 + 4G = \frac{4}{25} \Rightarrow G = 15(mA/V)$$
- Next, use Ohm's law to determine the value of the resistance R1:
$$R_1 = \frac{20 - v_2}{\frac{v_2}{25}} = 100(\Omega).$$

Thank you !