



**ELECTRIC CIRCUIT 1**  
**ECSE-200A**  
**16 December 2013, 18:00 – 21:00**

Examiner: Professor O. Liboiron-Ladouceur

Co-Examiner: Professor G. Roberts

<b>Student Name:</b>		<b>McGill ID:</b>											
----------------------	--	-------------------	--	--	--	--	--	--	--	--	--	--	--

**Signature:** \_\_\_\_\_

**INSTRUCTIONS:**


- Print your name, fill in your student ID number and sign on the line.
- **Initialize each page** of the exam at the top right corner and be sure to have a complete exam.
- This is a **CLOSED BOOK** examination. **NO CRIB SHEET** allowed.
- **FACULTY STANDARD CALCULATOR** permitted **ONLY**.
- This is, in part, a **MULTIPLE CHOICE** examination. As such, the following warning applies:  

The Examination Security Monitor Program detects pairs of students with unusually similar answer patterns on multiple-choice exams. Data generated by this program can be used as admissible evidence, either to initiate or corroborate an investigation or a charge of cheating under Section 16 of the Code of Student Conduct and Disciplinary Procedures.
- **Mark your answer to the multiple choice questions on the computer sheet PENCIL ONLY.**  
Each question is worth 1 mark. No answer or incorrect answer to a multiple choice question receives 0 mark.
- Answer the problems in the exam booklet provided. Show your work and clearly indicate your answer.
- Read through all of the questions and ensure that you have a complete examination (see page number at the bottom). The examination consists of a total of 7 pages including this cover page.
- The examination consists of 2 parts; Part 1 consists of 15 multiple choice questions (15 marks), part 2 consists of 3 problems (20 marks). This examination consists of a total of 35 marks.
- This examination paper **MUST BE RETURNED**

*PART 1 –Indicate your answer to each question on the computer sheets provided. There is only one possible answer.*


1.1. What is the resistance value of a resistor exhibiting the I-V diagram shown to the right (assume passive sign convention)?

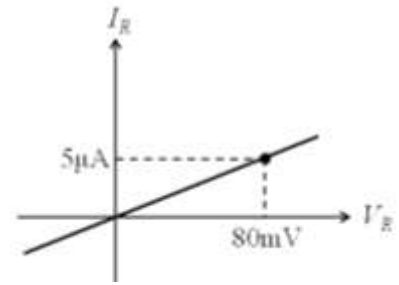- a)  $16\text{m}\Omega$
- b)  $62.5\Omega$
- c)  **$16\text{k}\Omega$**
- d)  $62.5\text{k}\Omega$




1.2. What is the power delivered by the current source in the circuit shown on the right?

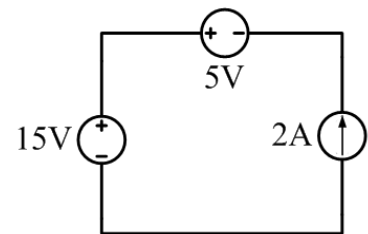- a)  $10\text{W}$
- b)  **$20\text{W}$**
- c)  $30\text{W}$
- d)  $40\text{W}$




1.3. What circuit analysis method between mesh analysis and node analysis should be used to get the fewer equations to solve when analyzing the circuit on the right?

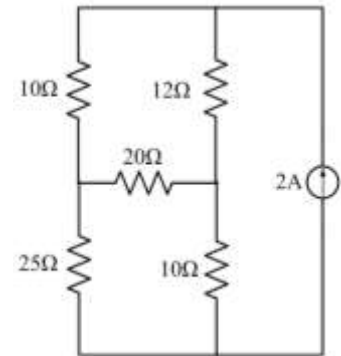- a) Both circuit analysis (mesh and node analysis) will give the same number of equations
- b) **Mesh analysis**
- c) Node analysis
- d) Neither, principle of superposition should be used




1.4. What is the current source value for the Norton circuit equivalence at terminals A and B in the circuit shown to the right?

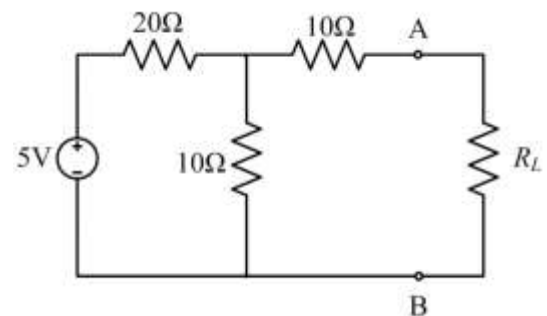- a)  $5\text{mA}$
- b)  $10\text{mA}$
- c)  $62.5\text{mA}$
- d)  **$100\text{mA}$**




1.5. What is the power delivered by the 5V independent source in the circuit shown to the right?

- a) 0W
- b) 0.25W
- c) 1W
- d) 4W

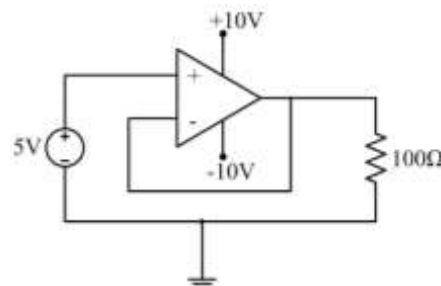


1.6. What is the characteristic equation of the circuit shown to the right?

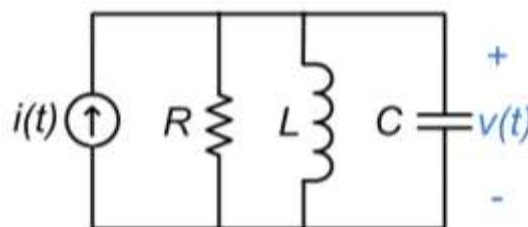- a)  $s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$
- b)  $s^2 + \frac{1}{L/R}s + \frac{1}{LC} = 0$
- c)  $s^2 + \frac{1}{2RC}s + \frac{1}{\sqrt{LC}} = 0$
- d)  $s^2 + \frac{1}{\sqrt{L/R}}s + \frac{1}{RC} = 0$



1.7. What happens to the behavior of the circuit shown to the right if the resistor  $R$  becomes really large ( $R \rightarrow \infty$ )?

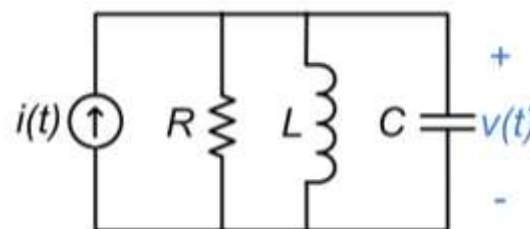
- a) The natural response is critically damped
- b) The natural response is underdamped
- c) The natural response is overdamped
- d) **The natural response is undamped**



1.8. What does 1 Volt represent?


- a) The current required in moving a Coulomb of charge from point A to point B
- b) The power absorbed associated in moving a Coulomb of charge from point A to point B
- c) The power delivered in moving a Coulomb of charge from point A to point B
- d) **The work associated in moving a Coulomb of charge from point A to point B**

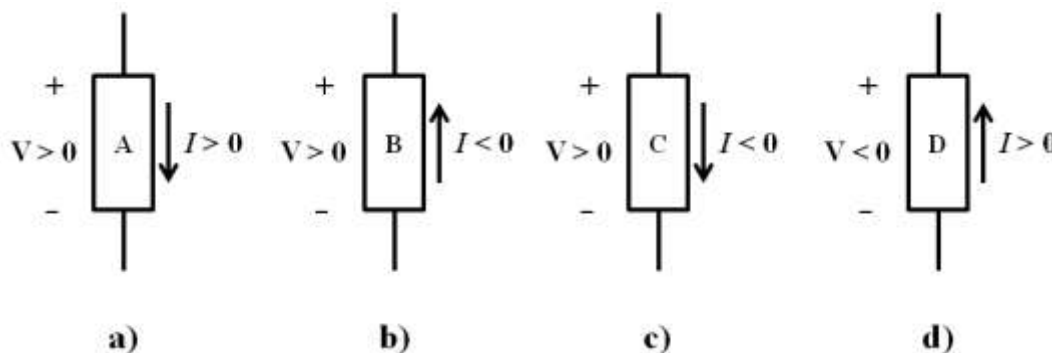1.9. Which one of the elements below (A, B, C, or D) must be an active element?




1.10. How will the voltage gain be affected if the feedback resistance ( $R_F$ ) is changed to  $20\Omega$  and the other resistance ( $R_I$ ) changes to  $10\Omega$  in the circuit shown to the right? Assume that the op-amp is ideal.

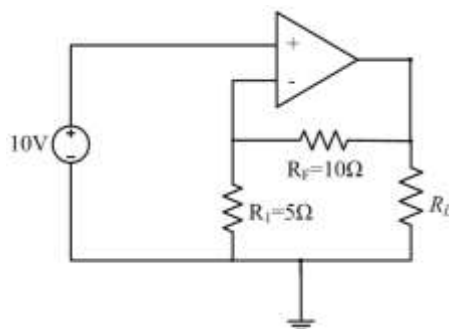- a) The magnitude of the voltage gain decreases
- b) The magnitude of the voltage gain increases
- c) **The magnitude of the voltage gain remains unchanged**
- d) It depends on the load resistor ( $R_L$ )




1.11. In the model of a practical op-amp as shown to the right, what statement below is correct?

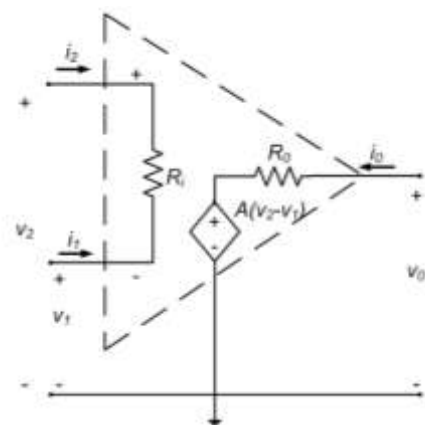- a) The input resistance  $R_i$  is small while the output resistance  $R_o$  is large
- b) For a small open loop gain, the op-amp behaves as predicted by the ideal op-amp model
- c) The gain  $A$  depends on the load resistance
- d) **None of the above**





1.12. What is the total energy stored in the capacitances of the circuit shown to the right? (Assume circuit is in dc steady state)

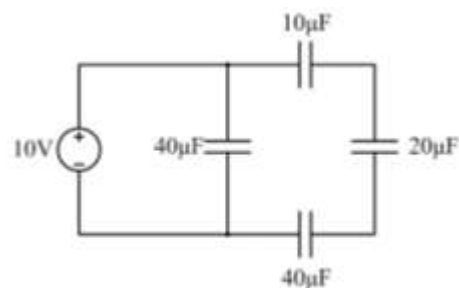- a) 1.2725mJ
- b) **2.286mJ**
- c) 2.545mJ
- d) 4.571mJ



1.13. What is the value of the resistor  $R_I$  in the circuit shown along with the voltage  $v_R(t)$  versus time  $t$  (time constant  $\tau$  is 10ms)?

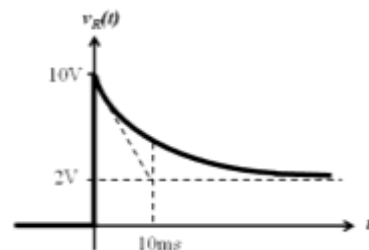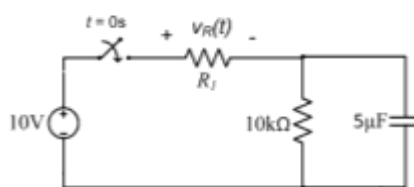- a) **2.5kΩ**
- b) 6.7kΩ
- c) 10kΩ
- d)  $R_I$  can be any value




1.14. What is capacitance?

- a) The charge separation between the two metallic plates of a capacitor
- b) **The constant of proportionality between charge and voltage**
- c) The constant of proportionality between charge and current
- d) The constant of proportionality between magnetic flux and voltage


1.15. What is the voltage  $v$  in the circuit shown to the right?

- a) **-5.5V**
- b) -10V
- c) 2V
- d) 5.5V

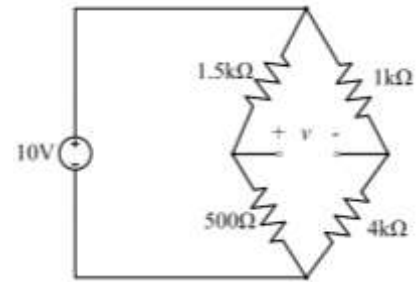


*PART 2 – This part consists of 3 questions. Write your answer in the exam booklet. Show your work and clearly indicate your answer.*

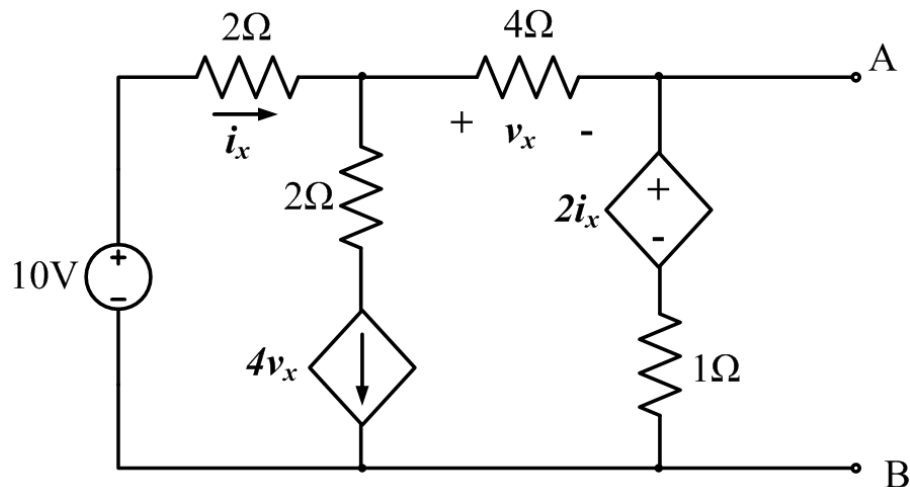2.1. Consider the circuit shown below and answer the questions [8pts]




- What is the Norton equivalent circuit with respect to the terminals A and B?
- What is the maximum power that the circuit can deliver to an optimally chosen load resistor connected at terminals A and B?

a) The Norton equivalent circuit is

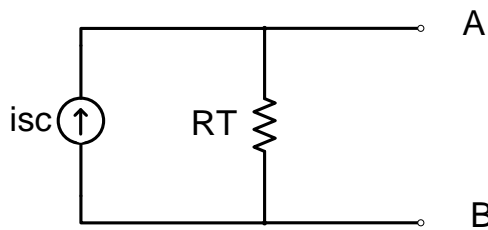

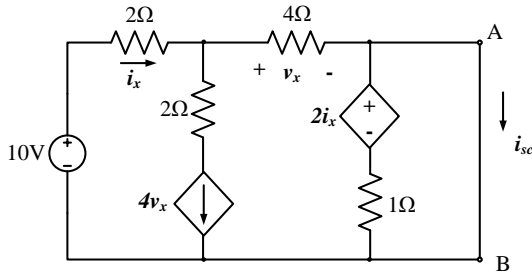So we first find the short-circuit current by shorting the two terminals



Because of the short, the node voltage is  $v_x$ . Using KCL, we find:

$$0 = -i_x + 4v_x + \frac{v_x}{4\Omega}$$


From Ohm's law:  $i_x = \frac{10V - v_x}{2\Omega}$

So the KCL equation becomes:

$$0 = \frac{v_x - 10V}{2\Omega} + 4v_x + \frac{v_x}{4\Omega} \rightarrow 0 = 2v_x - 20 + 16v_x + v_x = 19v_x - 20 \rightarrow v_x = \frac{20}{19}V = 1.053V$$

From Ohm's law:  $i_{sc} = \frac{v_x}{4\Omega} = \frac{20}{19 \cdot 4}V = 0.2632A$

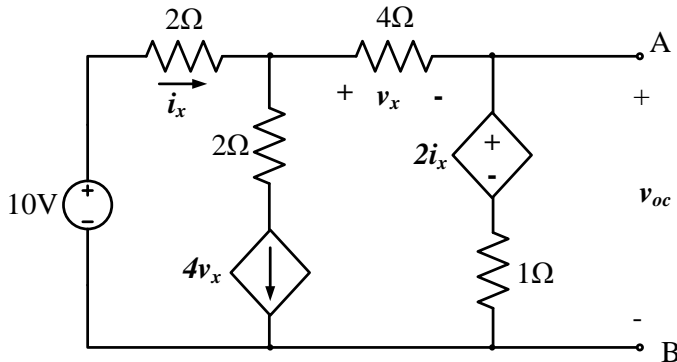To find the Thevenin resistance, we also need to find the open-circuit voltage  $v_{oc}$ :



The open-circuit voltage is the same voltage across the dependent voltage source and the 1ohm resistor. We first do a KCL to get the first equation:

$$0 = -i_x + 4v_x + \frac{v_x}{4\Omega} = -4i_x + 17v_x \rightarrow v_x = \frac{4}{17}i_x$$

Then, a KVL is done to get the 2<sup>nd</sup> equation:

$$0 = -10V + 2\Omega \cdot i_x + v_x + 2i_x + \frac{v_x}{4\Omega} \cdot 1\Omega$$

We replace one variable from the 1<sup>st</sup> equation:

$$0 = -10V + 2\Omega \cdot i_x + \frac{4}{17}i_x + 2i_x + \frac{4}{17} \cdot \frac{1}{4\Omega} \cdot 1\Omega \cdot i_x$$

$$0 = -10V + 2 \cdot i_x + \frac{4}{17}i_x + 2 \cdot i_x + \frac{1}{17}i_x = -170 + 34 \cdot i_x + 4 \cdot i_x + 34 \cdot i_x + i_x$$

$$i_x = \frac{170}{73}A = 2.329A$$


So:

$$v_{oc} = 2i_x + \frac{v_x}{4\Omega} \cdot 1\Omega = 4.658V + \frac{1}{17}2.329A = 4.795V$$

So the Thevenin resistance is:

$$R_T = \frac{v_{oc}}{i_{sc}} = \frac{4.795V}{0.2632A} = 18.2\Omega$$

So the answer is:

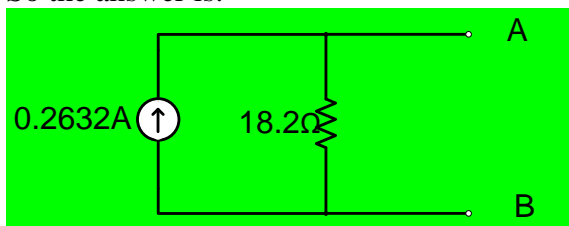


b) The maximum power that the circuit can deliver to an optimally chosen load resistor connected at terminals A and B is when the load resistance is 18.2ohm:

$$P = \frac{i_{sc}}{2} \cdot \frac{v_{oc}}{2} = \frac{0.2632A}{2} \cdot \frac{4.795V}{2} = 0.3159W$$

$P = 315.9mW$



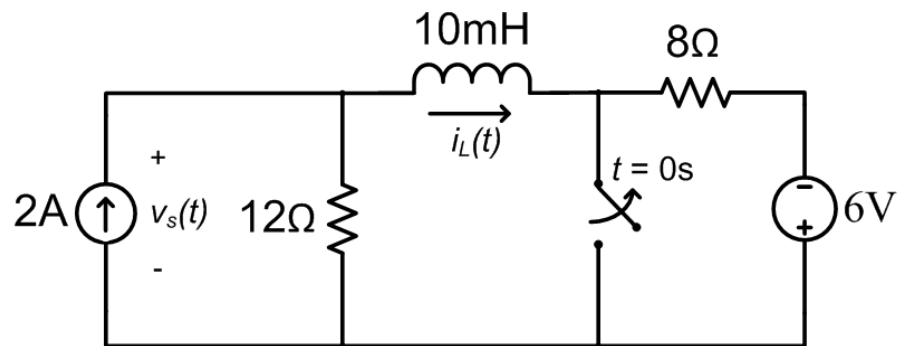- 2.2. Consider the circuit shown below. The circuit is in dc steady state for  $t < 0$  with the switch closes. At  $t = 0$ s, the switch opens and remains open for  $t > 0$ s. Answer the questions. [7pts]




- Find the inductor current  $i_L(t)$  and voltage  $v_s(t)$  across the current source?
- Find the energy stored in the inductor at  $t = 1$ ms?

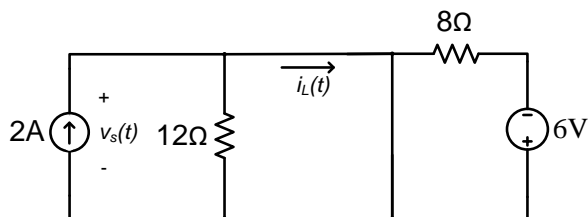a) First, find the inductor current  $i_L(t)$  using the general procedure building the solution:

$$i_L(t) = i_L(\infty) + [i_L(0+) - i_L(\infty)] \exp\left(-\frac{L}{R_T} t\right)$$

For  $t < 0$ : There is a short to the ground reference with no current going through the 12ohm resistor. Thus:  $i_L(0^-) = i_L(0^+) = 2A$




For  $t \rightarrow \infty$ : the inductor current can be found using KCL at the node or through source transformation to simplify the circuit with the two resistances in parallel.


$$\text{KCL: } 0 = -2A + \frac{V_{12\Omega}}{12\Omega} + \frac{V_{12\Omega} - (-6V)}{8\Omega}$$

solve for the node voltage:  $V_{12\Omega} = 6V$
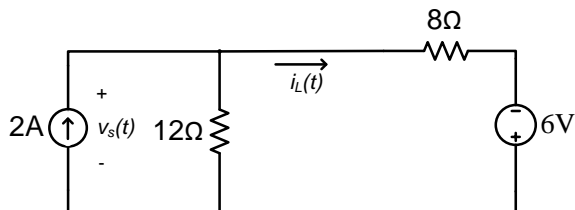
$$\text{The current is: } i_L(\infty) = \frac{6V - (-6V)}{8\Omega} = 1.5A$$



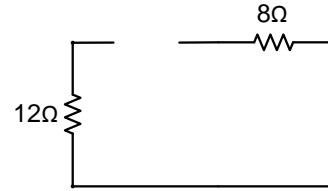Now, the Thevenin resistance seen by the inductor can be found by turning off the independent source



and finding the 'seen' resistance by the inductor:  $18 \Omega$

Building the solution:  $i_L(t) = i_L(\infty) + [i_L(0+) - i_L(\infty)] \exp\left(-\frac{t}{\frac{L}{R_T}}\right)$

$$i_L(t) = 1.5A + [2A - 1.5A] \exp\left(-\frac{t}{\frac{10mH}{18\Omega}}\right)$$

$$i_L(t) = 1.5A + 0.5A \exp(-2000t)$$

To find the voltage at the current supply  $v_s(t)$ , we find its relationship to the inductor current using KCL:

$$0 = -2A + \frac{v_s(t)}{12\Omega} + i_L(t)$$

So the voltage is

$$v_s(t) = 24V - 12i_L(t) = 24 - 12[1.5 + 0.5\exp(-2000t)]$$

$$v_s(t) = 6 - 6\exp(-2000t)$$


c) The energy stored in the inductor at  $t = 1ms$  is:  $\frac{1}{2}Li_L^2$

$$i_L(1ms) = 1.5A + 0.5A \exp(-2000 \times 10^{-3}) = 1.57A$$

$$\frac{1}{2}Li_L^2 = \frac{1}{2} \cdot 10 \times 10^{-3} \cdot 1.57^2$$

$$U = 12.29 \text{ mJ}$$

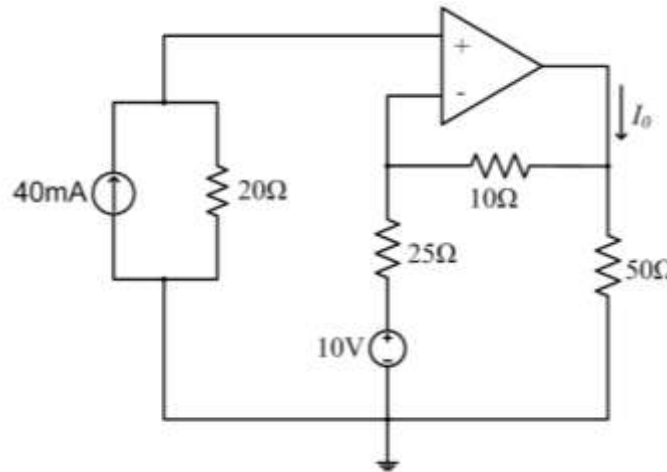- 2.3. Consider the circuit shown below. Assume that the op-amp is ideal. Answer the questions.  
[5pts]



- (a) Find the power absorbed by the  $50\Omega$  load resistor.  
(b) Find the op-amp output current labelled  $I_o$ ?

a) Find the power by finding the voltage at the load resistor node ( $V_o$ ).

i) voltage at the non-inverting node using KCL (ideal opamp):

$$i_{20\Omega} = 40mA; V_+ = 20\Omega \cdot i_{20\Omega} = 800mV = 0.8V$$

ii) Current through the 10ohm resistor using KCL (ideal opamp) at the inverting node:

$$0 = i_{25\Omega} + i_{10\Omega} = \frac{0.8V - 10V}{25\Omega} + \frac{0.8V - V_o}{10\Omega} = \frac{-9.2V}{25\Omega} + \frac{0.8V}{10\Omega} - \frac{V_o}{10\Omega}$$

$$V_o = \frac{-9.2V}{25\Omega} \cdot 10\Omega + 0.8V = -3.68V + 0.8V = -2.88V$$

iii) Power absorbed:  $P_{abs} = V_o \cdot i_{50\Omega} = \frac{V_o^2}{50\Omega} = \frac{(-2.88V)^2}{50\Omega} = \frac{8.2944}{50} = 0.1659W = 165.9mW$

$$P_{abs} = 165.9mW$$

b) Find the current  $I_o$  using a KCL at the opamp output node:

$$0 = -I_o + \frac{V_o - V^-}{10\Omega} + \frac{V_o}{50\Omega}$$

$$I_o = \frac{-2.88V - 0.8V}{10\Omega} + \frac{-2.88V}{50\Omega} = \frac{-3.68V}{10\Omega} + \frac{-2.88V}{50\Omega} = -0.368A - 0.0576A = -0.4256A$$

$$I_o = -425.6mA$$