

# Today's Outline

## 2. Resistive Circuits


- Equivalent Resistance in Circuit Analysis

# Example 1

Should there be any concern about the following situation?

Physiological Reaction	Current
Barely Perceptible	3-5mA
Extreme Pain	35-50mA
Muscle Paralysis	50-70mA
Heart Stoppage	500mA

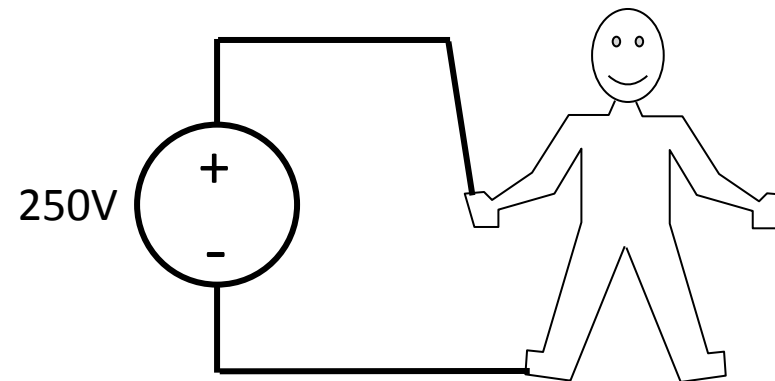
W.F. Cooper, *Electrical Safety Engineering*, 2<sup>nd</sup> ed., Butterworth, 1986.



To answer this question, we need an electrical model...

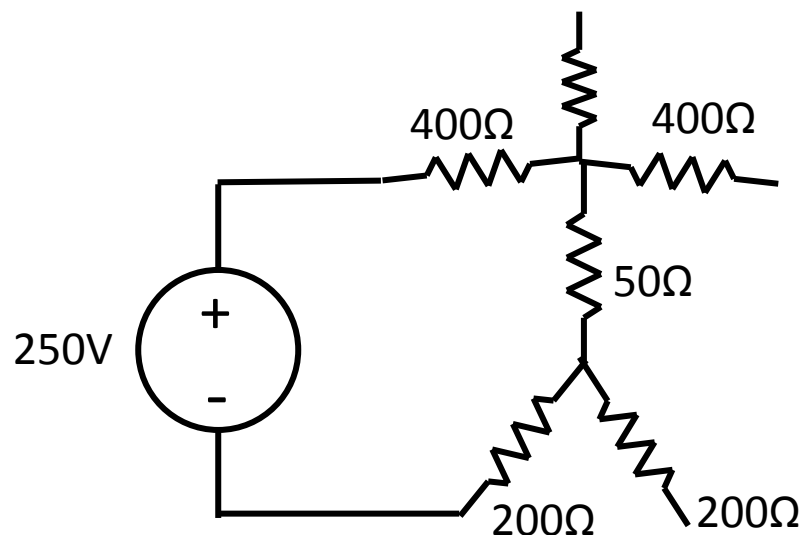
# Example 1

An approximate electrical model is given by a resistor network from experimental data on a “typical” human, and the current can be easily found.




Note that we are neglecting the resistance of contact with the skin here. Note also that human tissue is very crudely modeled by ideal resistors.

# Example 1

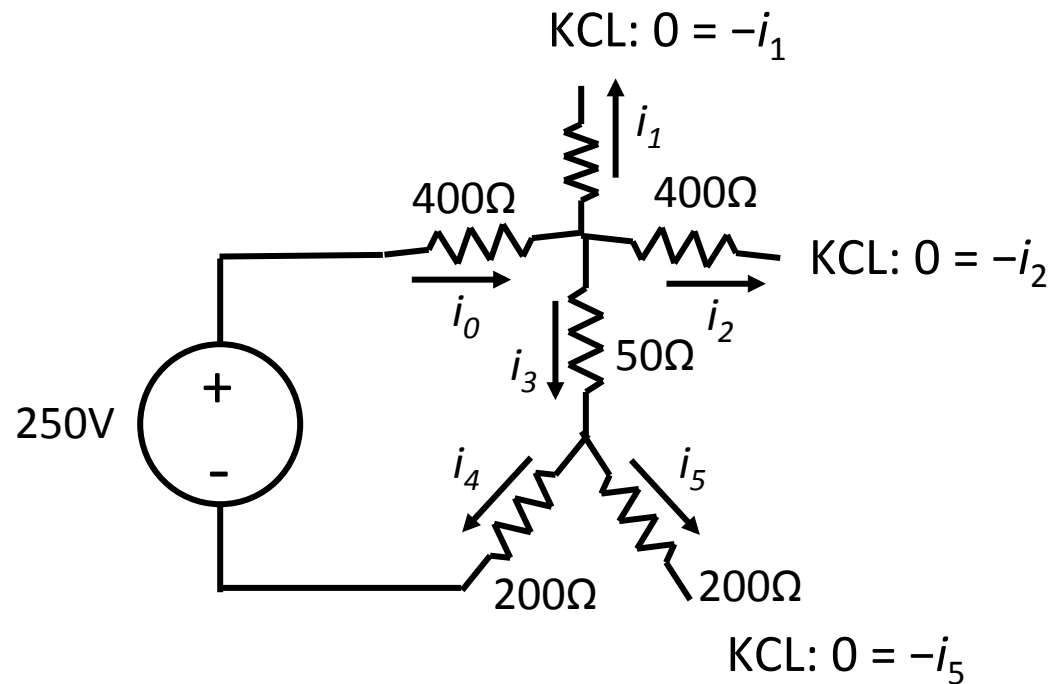


# Example 1

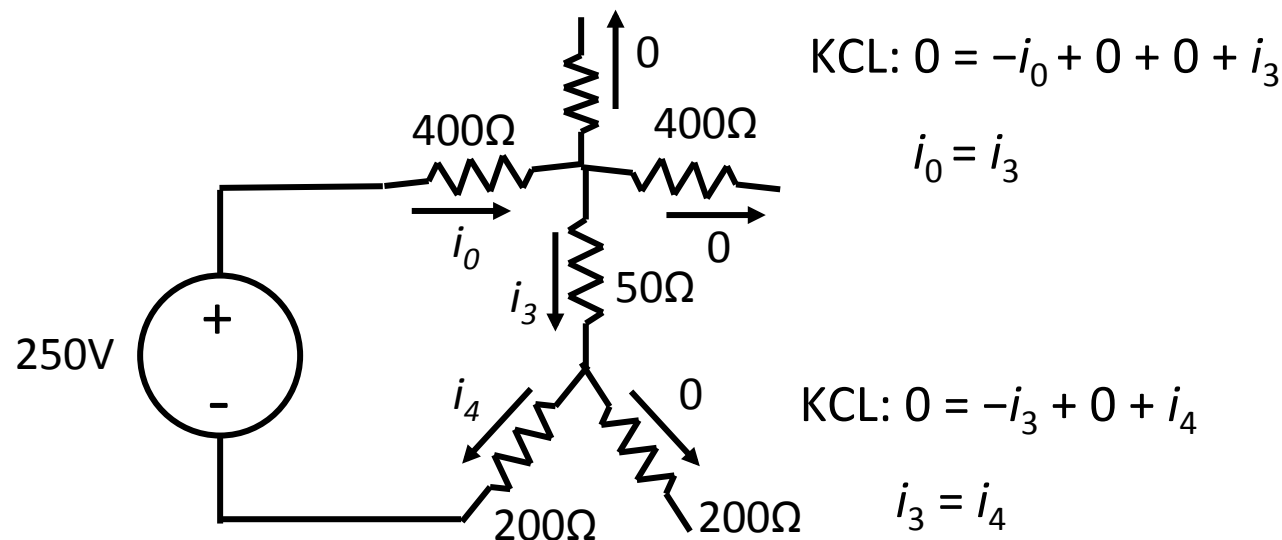

From KCL, the “dangling” resistors do not conduct current. We therefore have a current  $i_0 = i_3 = i_4$  flowing through the series combination of 400Ω, 50Ω and 200Ω resistors.

*Recall that resistors in series carry the same current.*

# Example 1

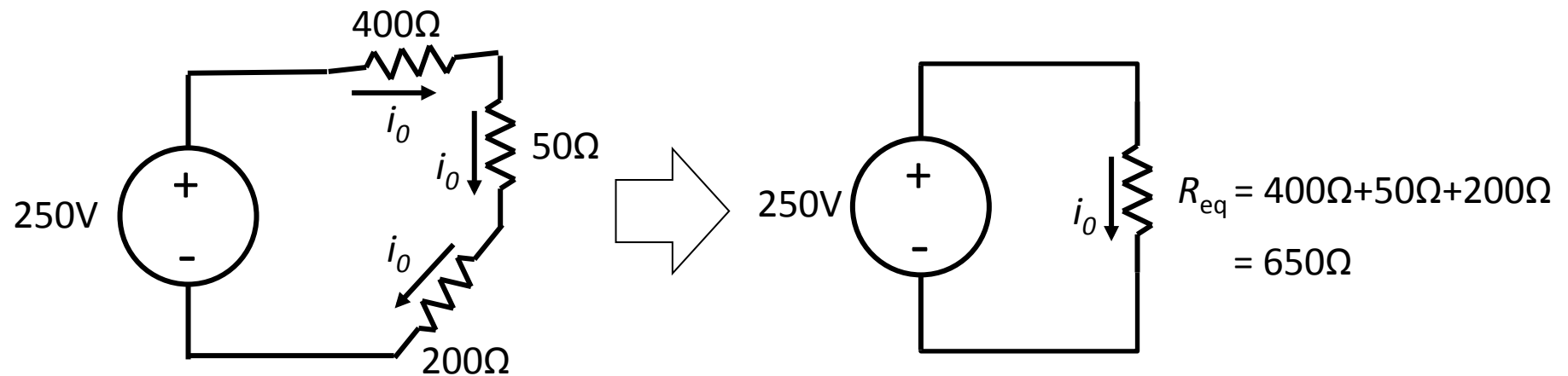

Ohm's Law:  $i_0 = 250V / 650\Omega = 385mA$

*The current flow is dangerous*




Physiological Reaction	Current
Barely Perceptible	3-5mA
Extreme Pain	35-50mA
Muscle Paralysis	50-70mA
Heart Stoppage	500mA

W.F. Cooper, *Electrical Safety Engineering*, 2<sup>nd</sup> ed., Butterworth, 1986.
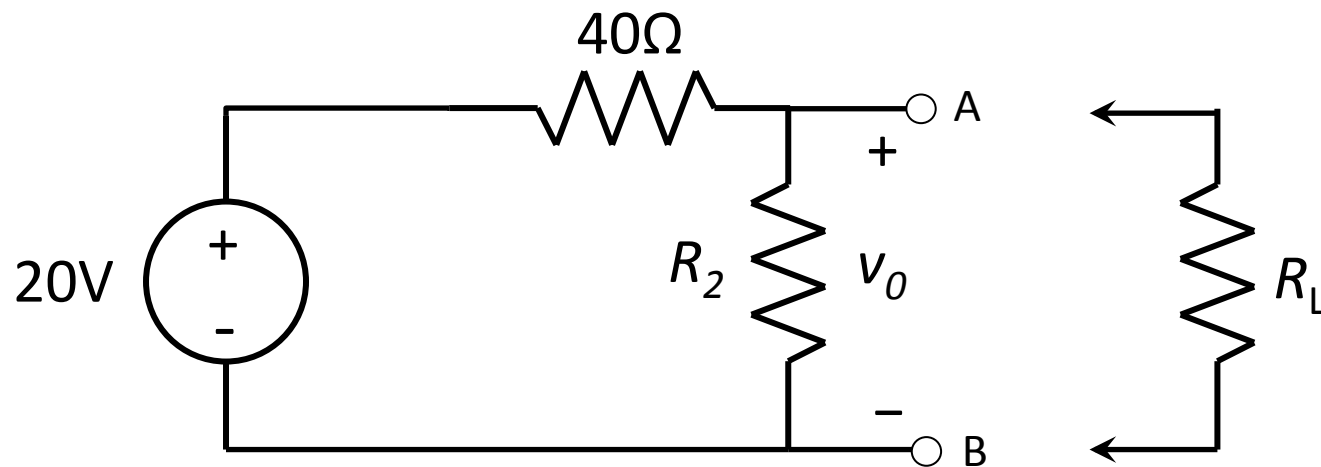
## Example 2

In the absence of the load resistor  $R_L$ , the voltage divider produces  $v_0 = 4V$ .  
When the load resistor is attached to the terminals A B, the voltage  $v_0 = 3V$ .  
What is the value of  $R_L$ ?




Strategy:

- find  $R_2$  using the voltage divider equation
- find  $R_2 \parallel R_L$  using the voltage divider equation, and thus find  $R_L$
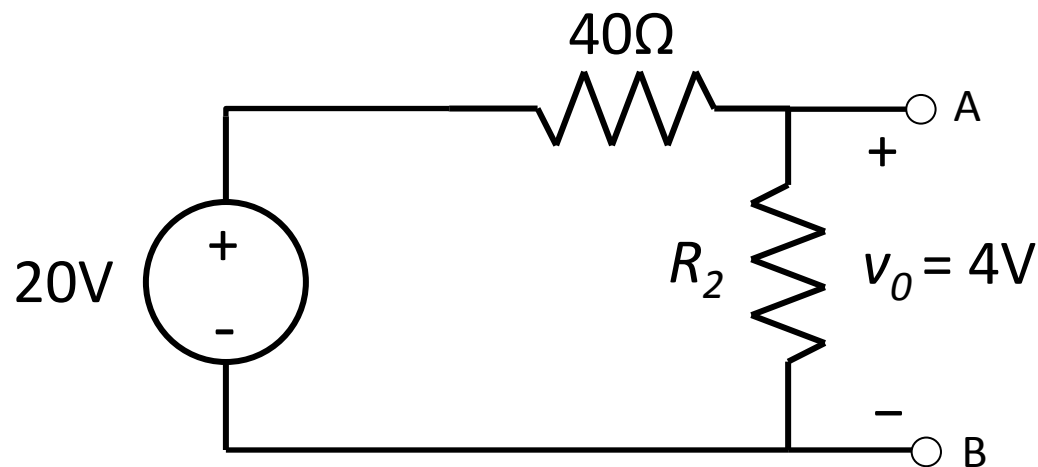
## Example 2

Find  $R_2$  using the voltage divider equation.



$$\frac{4V}{20V} = \frac{R_2}{40\Omega + R_2}$$

$$\frac{1}{5}(40\Omega + R_2) = R_2$$


$$8\Omega = R_2 \left(1 - \frac{1}{5}\right)$$

$$R_2 = \frac{5}{4} \cdot 8\Omega = 10\Omega$$



## Example 2

Find  $R_2 || R_L$  using the voltage divider equation.

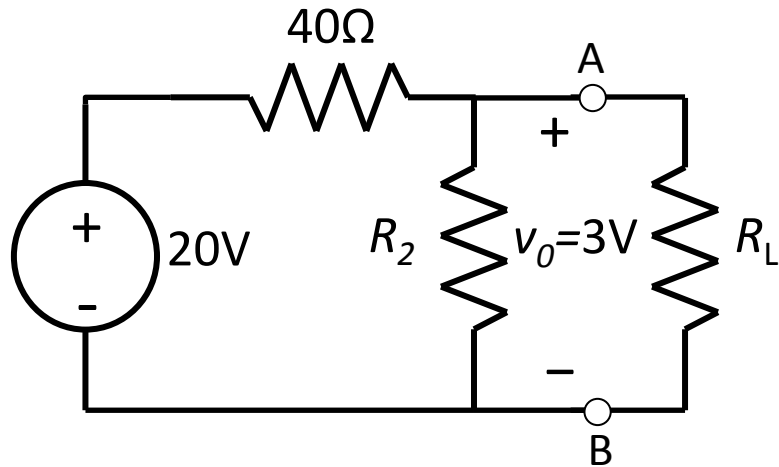

$$\frac{3V}{20V} = \frac{R_2 || R_L}{40\Omega + R_2 || R_L}$$


$$\frac{3}{20} (40\Omega + R_2 || R_L) = R_2 || R_L$$

$$6\Omega = R_2 || R_L \left( 1 - \frac{3}{20} \right)$$

$$R_2 || R_L = \frac{20}{17} \cdot 6\Omega$$


$$= \frac{120}{17} \Omega$$

$$= 7.059\Omega$$

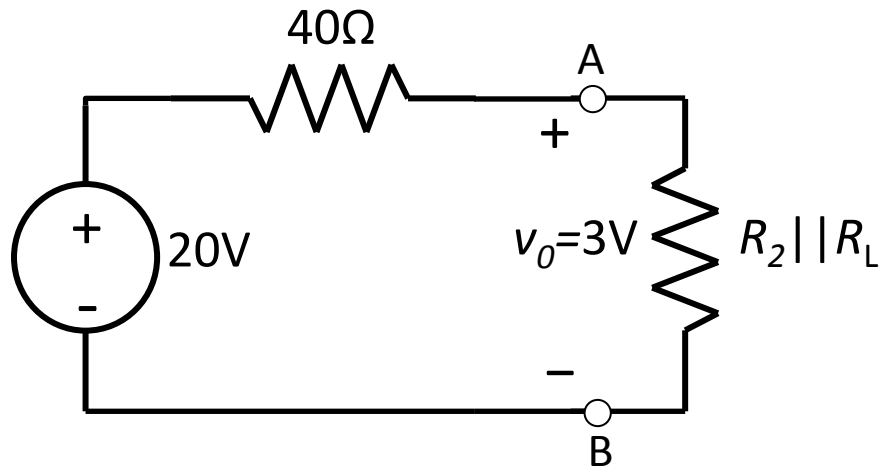

## Example 2

Find  $R_L$  from the value of  $R_2$  and  $R_2 || R_L$ .

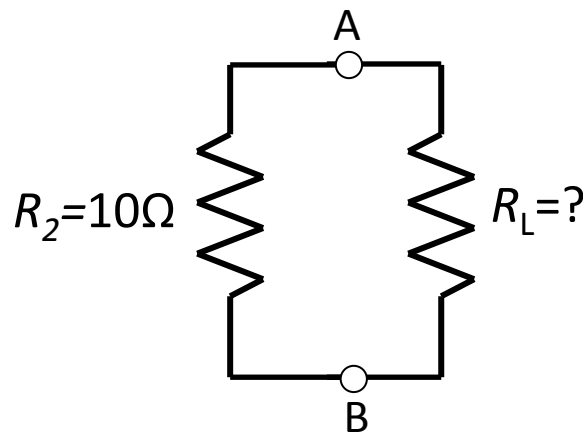

$$R_2 || R_L = (120/17)\Omega$$

$$\frac{1}{R_2 || R_L} = \frac{1}{R_2} + \frac{1}{R_L} \quad \text{For parallel combinations, we add conductances.}$$

$$\frac{17}{120\Omega} = \frac{1}{10\Omega} + \frac{1}{R_L}$$

$$\frac{1}{R_L} = \frac{17}{120\Omega} - \frac{1}{10\Omega} = \frac{17}{120\Omega} - \frac{12}{120\Omega}$$


$$= \frac{5}{120\Omega}$$

$$R_L = 24\Omega$$

We could of course use decimals or fractions for this calculation. If you elect to use decimals, use 4 significant digits (*A.BCD*).

## Example 3

Find the current  $i_0$ .

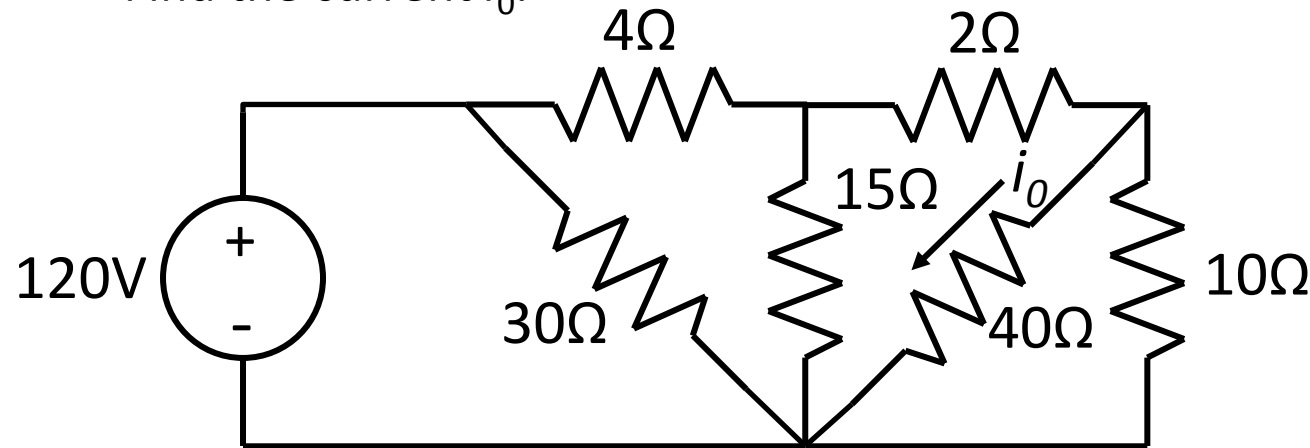



Strategy:

- reduce the circuit to a source and single equivalent resistor
- work through the equivalent circuits to find  $i_0$




*We could also use KVL and KCL directly, but this example shows how creative one can be in using resistor equivalence and voltage/current dividers to solve a problem.*
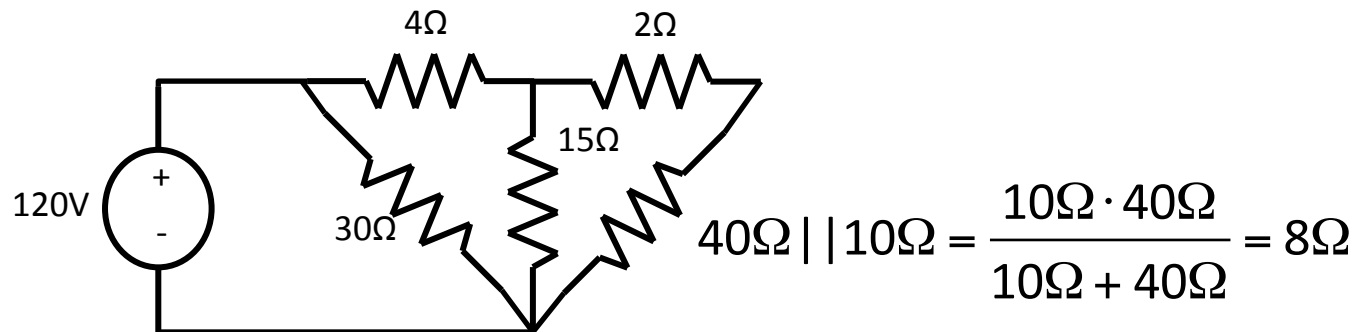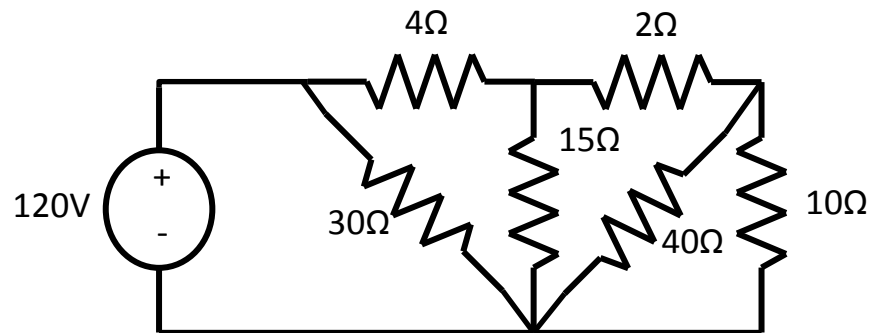
## Example 3



Reduce the circuit to a single equivalent resistor.



## Example 3

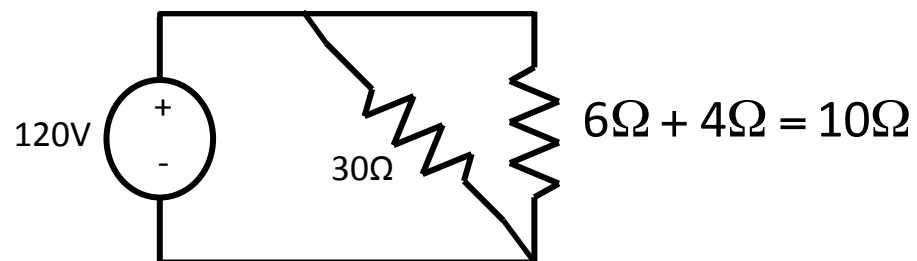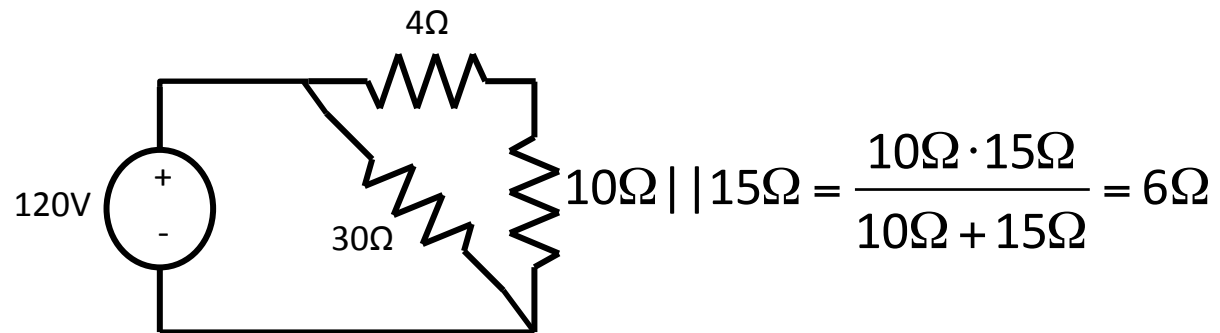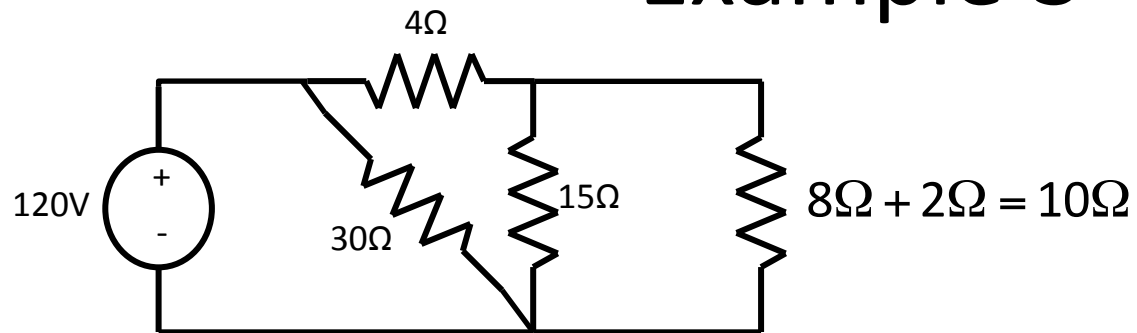




## Example 3

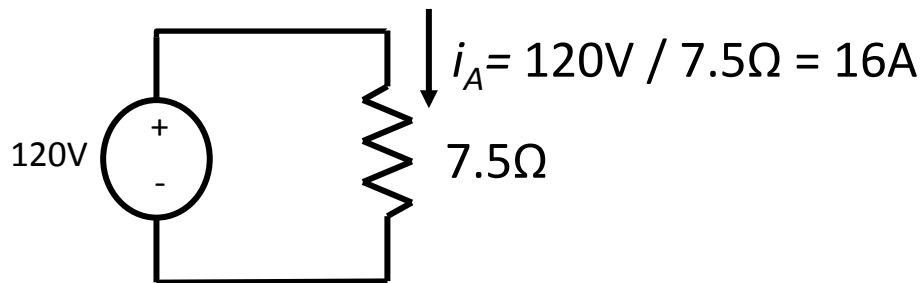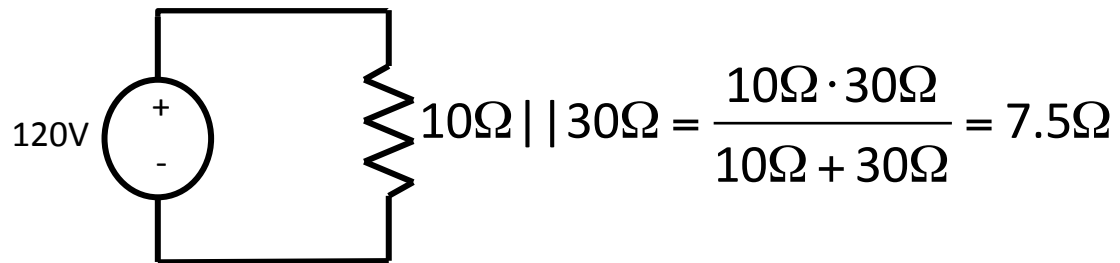



Note that the entire network of *resistors* is equivalent to a single  $7.5\Omega$  resistor across the terminals of the 120V source.

We now work forward through the equivalent circuits, solving for currents along the way.

## Example 3

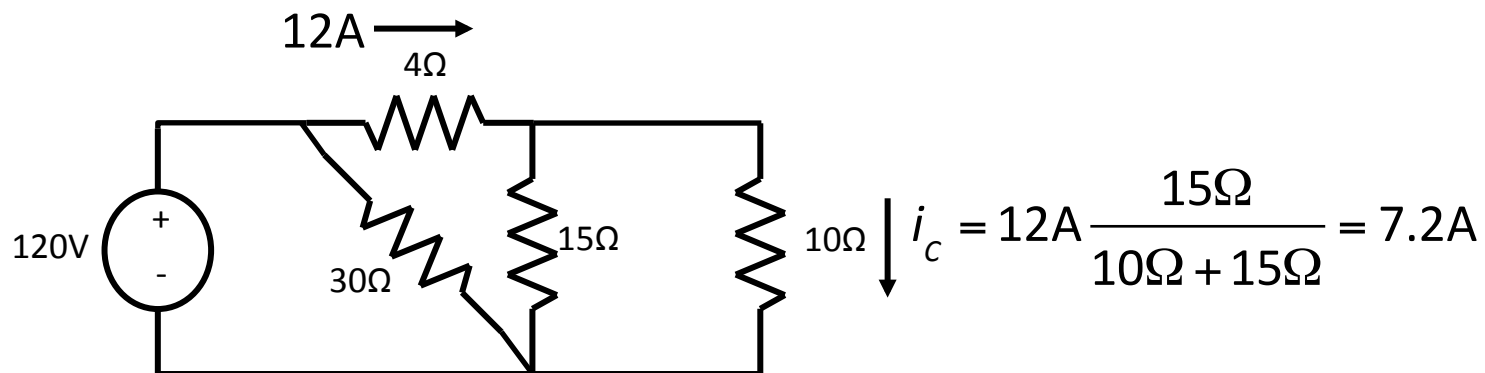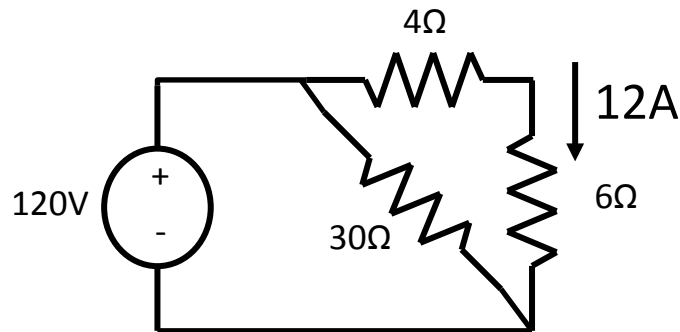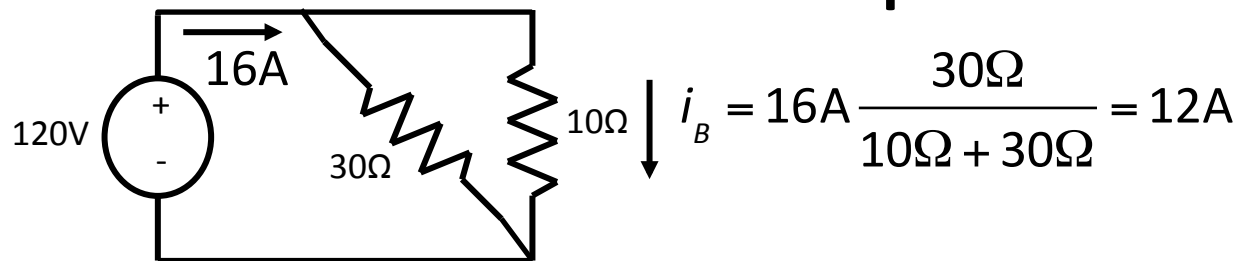

## Example 3

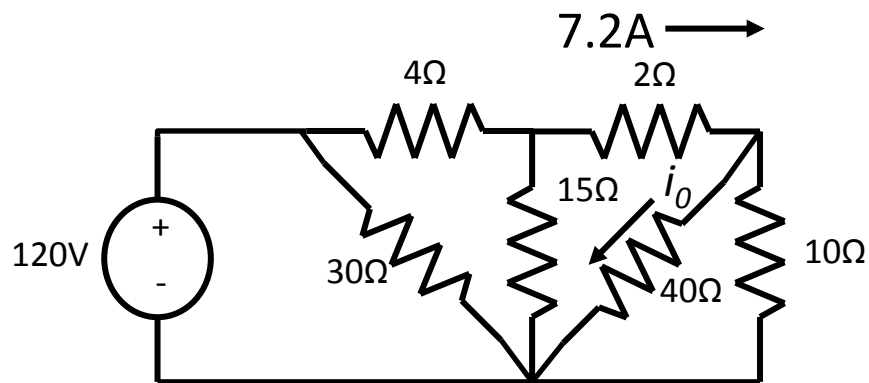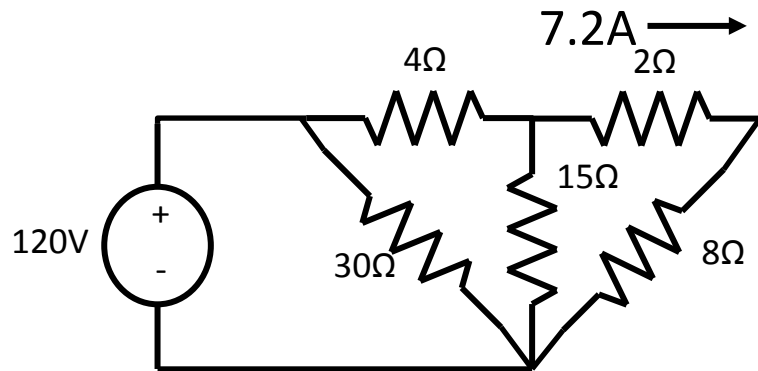


$$i_0 = 7.2\text{A} \frac{10\Omega}{10\Omega + 40\Omega} = 1.44\text{A}$$

Note that we have reduced the “large” circuit problem to a series of small, easily solvable problems.


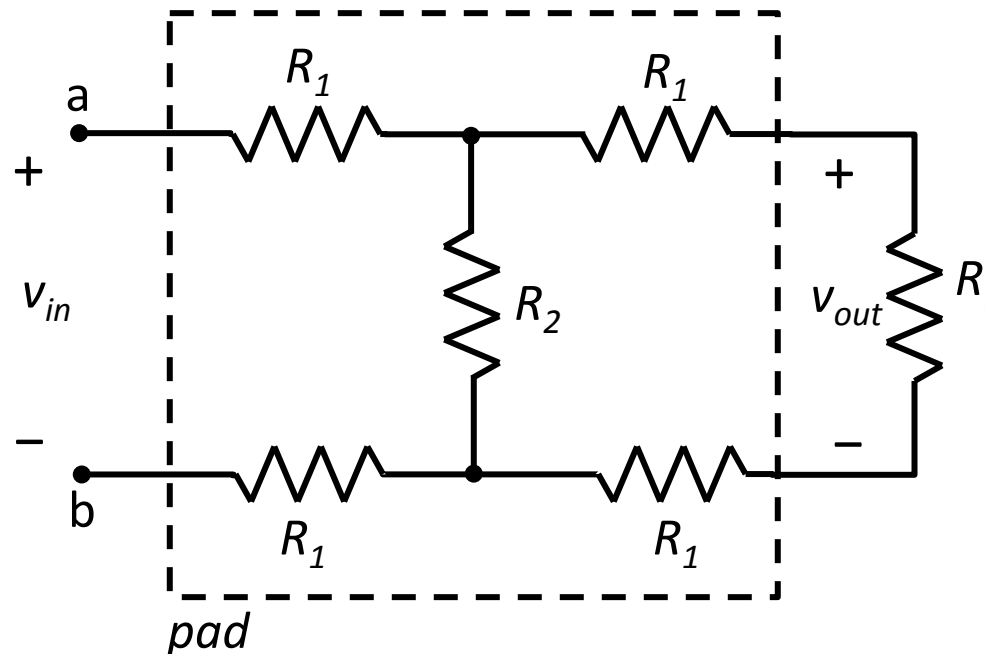
## Example 4

The circuit below is an **attenuator pad**, often used in volume control circuits. What is the equivalent resistance at terminals a and b? What is the ratio of  $v_{out}$  to  $v_{in}$ ?




Strategy:


– *apply equivalent resistance rules for series and parallel (if that doesn't work, revert to definition of equivalent resistance)*

# Example 4


step #1

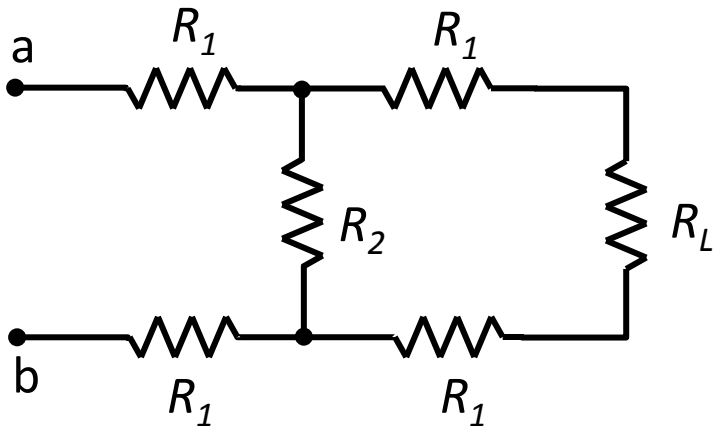


step #3

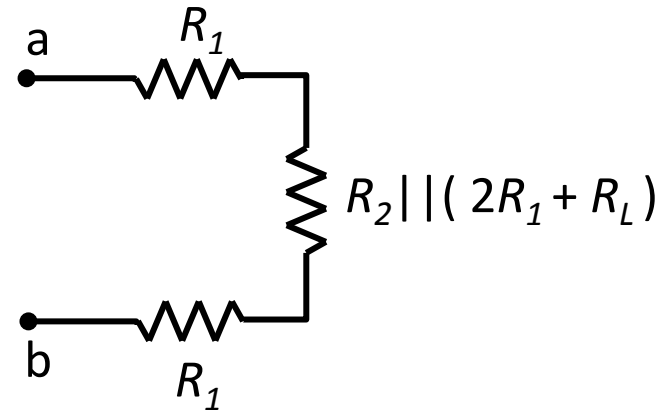


step #2

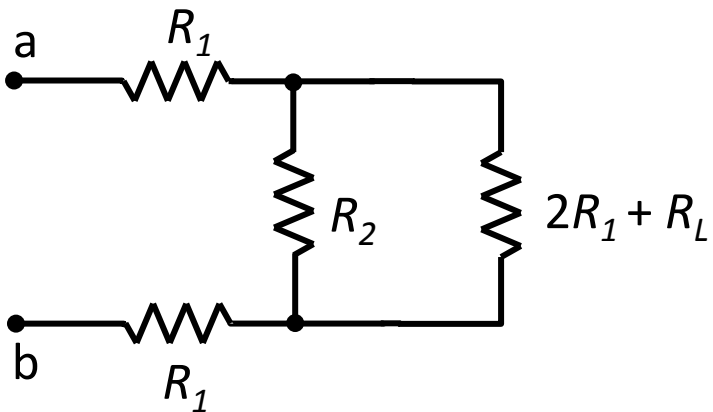

step #4

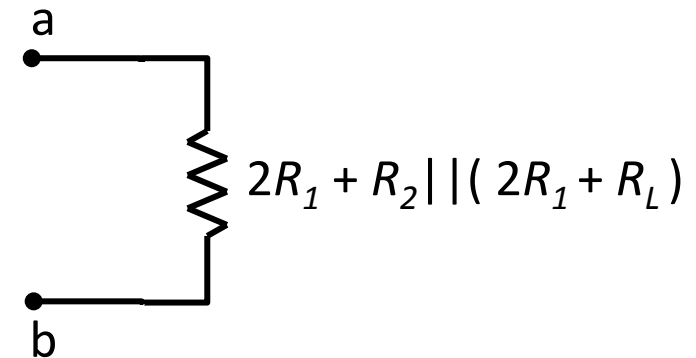


## Example 4

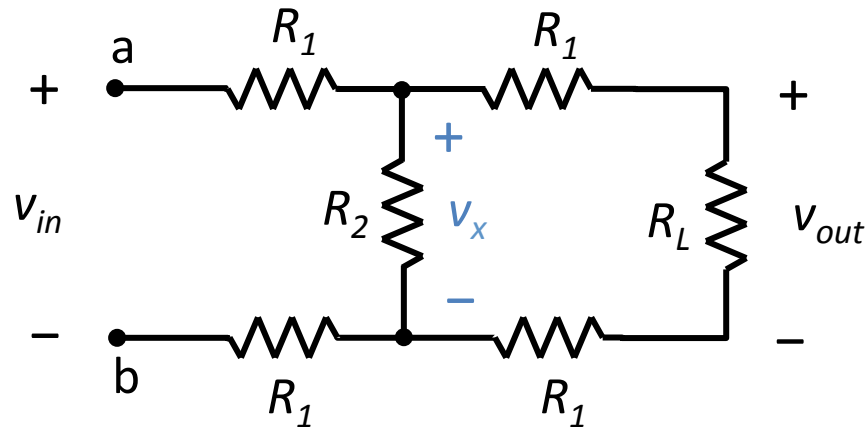

Applying a voltage divider equation:

$$v_{out} = v_x \frac{R_L}{2R_1 + R_L}$$

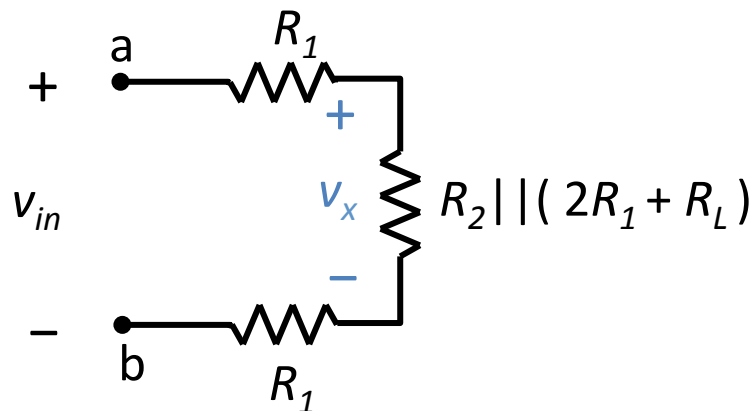


Applying another voltage divider equation:

$$v_x = v_{in} \frac{R_2 || (2R_1 + R_L)}{2R_1 + R_2 || (2R_1 + R_L)}$$

Combining results:

$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_x} \frac{v_x}{v_{in}} = \frac{R_L}{2R_1 + R_L} \cdot \frac{R_2 || (2R_1 + R_L)}{2R_1 + R_2 || (2R_1 + R_L)}$$

## Example 4

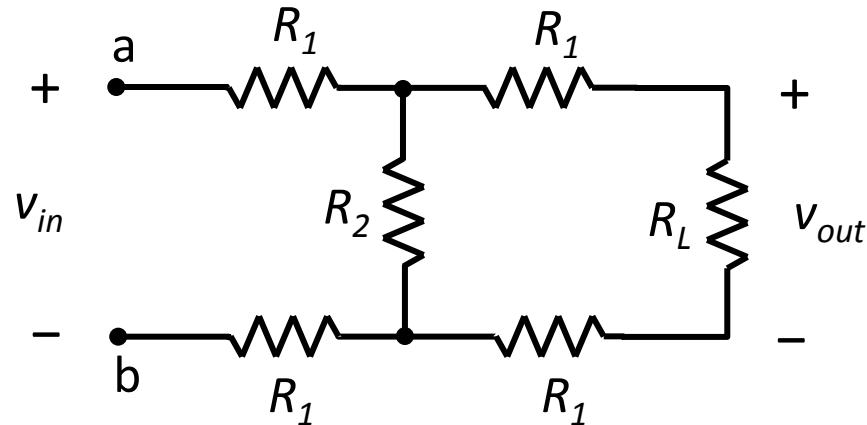

The equivalent resistance at terminals a and b, and the voltage ratio  $v_{out}/v_{in}$  are given by:

$$R_{ab} = 2R_1 + R_2 \parallel (2R_1 + R_L)$$

$$\frac{v_{out}}{v_{in}} = \frac{R_L}{2R_1 + R_L} \cdot \frac{R_2 \parallel (2R_1 + R_L)}{2R_1 + R_2 \parallel (2R_1 + R_L)}$$

In practice, one specifies the load resistance  $R_L$ , the equivalent resistance  $R_{ab}$  and the voltage ratio  $v_{out}/v_{in}$  to determine the required  $R_1$  and  $R_2$  of the pad.

Note that there are many other attenuator pad geometries.