


Today's Outline

7. First Order Circuits

- response to a constant input
 - RL circuits
 - general procedure

response to a constant input

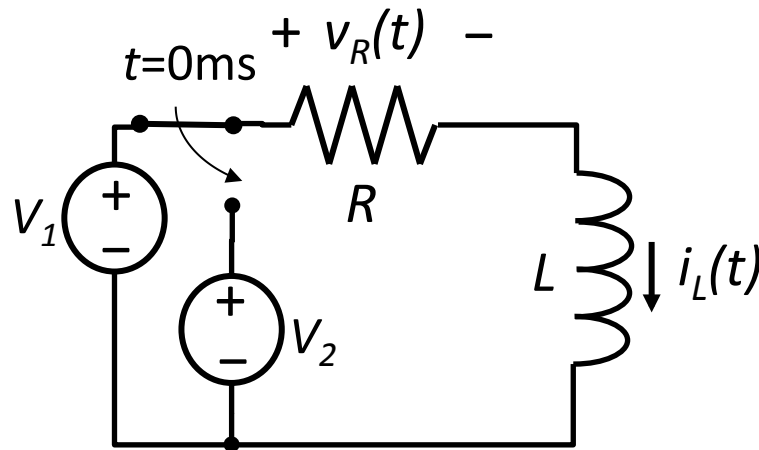
Consider an RL circuit being switched at $t=0$ between two different open circuit voltages. Assume steady state has been reached for $t<0$. What is the inductor current?



constant input: inductor current

Consider first the steady state conditions for $t < 0$.

$t < 0$

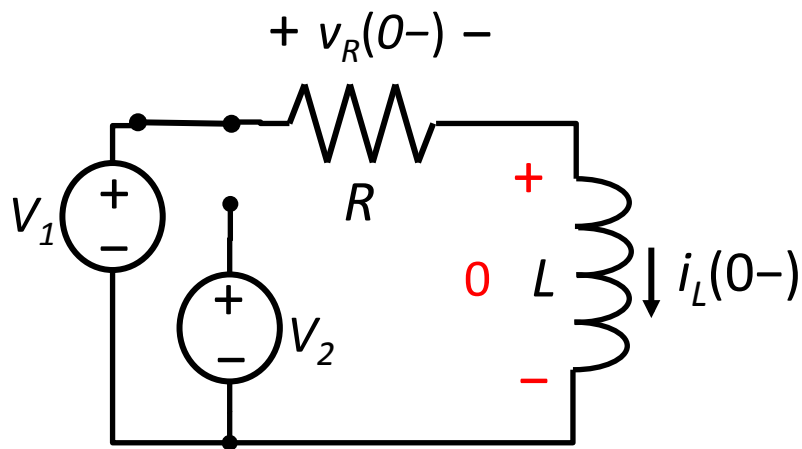

$$\begin{aligned} \text{KVL: } 0 &= -V_1 + v_R(0-) + v_L(0-) \\ &= -V_1 + i_L(0-) \cdot R + 0 \end{aligned}$$


$$i_L(0-) = \frac{V_1}{R}$$

$$\text{Steady state: } v_L = L \frac{di_L}{dt} = 0$$

constant input: inductor current

Consider the circuit equations for $t > 0$.

$t > 0$

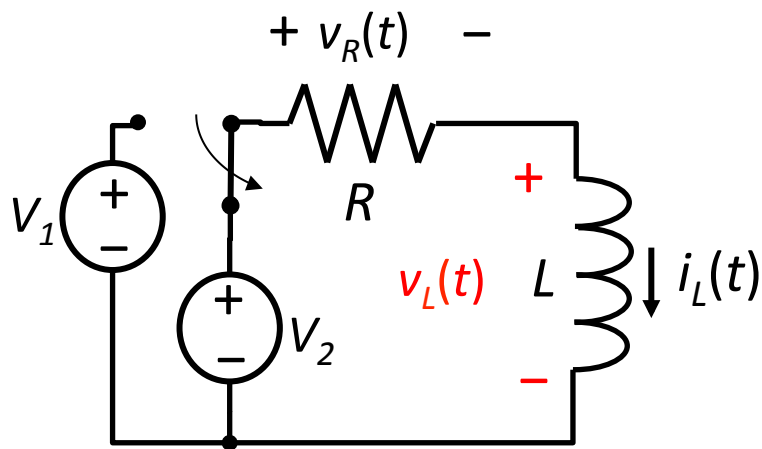

$$\begin{aligned} \text{KVL: } 0 &= -V_2 + v_R + v_L \\ &= -V_2 + R \cdot i_L + L \frac{di_L}{dt} \end{aligned}$$

$$\frac{di_L}{dt} + \frac{R}{L} i_L = \frac{V_2}{L} \quad t > 0$$

continuity of inductor current:


$$i_L(0+) = i_L(0-) = \frac{V_1}{R}$$

We have a first-order linear differential equation with initial conditions.

constant input: inductor current

Consider steady state as $t \rightarrow \infty$.

$t \rightarrow \infty$

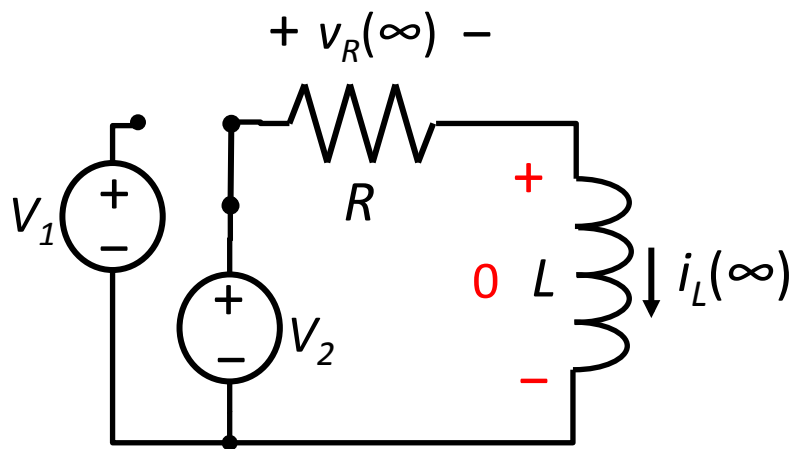

Steady state: $v_L = L \frac{di_L}{dt} = 0$

KVL:
$$0 = -V_2 + v_R(\infty) + v_L(\infty)$$
$$= -V_2 + R \cdot i_L(\infty) + 0$$

$$i_L(\infty) = \frac{V_2}{R}$$

This can also be concluded from the circuit equation for $t > 0$:

$$\left. \frac{di_L}{dt} \right|_{t \rightarrow \infty} + \frac{R}{L} i_L(\infty) = \frac{V_2}{L}$$

$$0 + \frac{R}{L} i_L(\infty) = \frac{V_2}{L}$$

$$i_L(\infty) = \frac{V_2}{R}$$

constant input: inductor current

Solve the differential equation.

$$\frac{di_L}{dt} + \frac{R}{L}i_L = \frac{V_2}{L} \quad t > 0$$

$$i_L(0+) = \frac{V_1}{R}$$

Recall:

$$\frac{dx}{dt} + kx = G$$

$$x(t) = c_1 + c_2 \exp(-kt)$$

The form of the solution is: $i_L(t) = c_1 + c_2 \exp\left(-\frac{t}{L/R}\right)$


Use our initial and final conditions: $i_L(\infty) = \lim_{t \rightarrow \infty} \left[c_1 + c_2 \exp\left(-\frac{t}{RC}\right) \right] = c_1$

$$\therefore c_1 = i_L(\infty) = \frac{V_2}{R}$$

$$i_L(0+) = c_1 + c_2 \exp(0) = c_1 + c_2$$


$$\therefore c_2 = i_L(0+) - c_1 = \frac{V_1 - V_2}{R}$$

constant input: inductor current

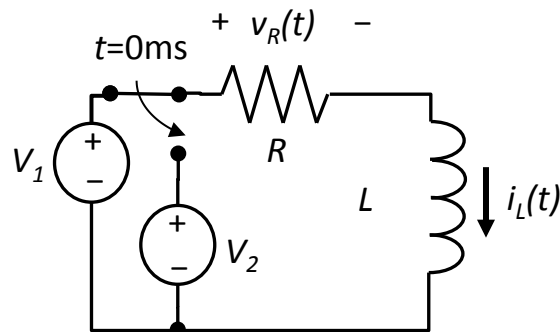

The response is again a sum of a natural / transient response and a forced / steady-state response.
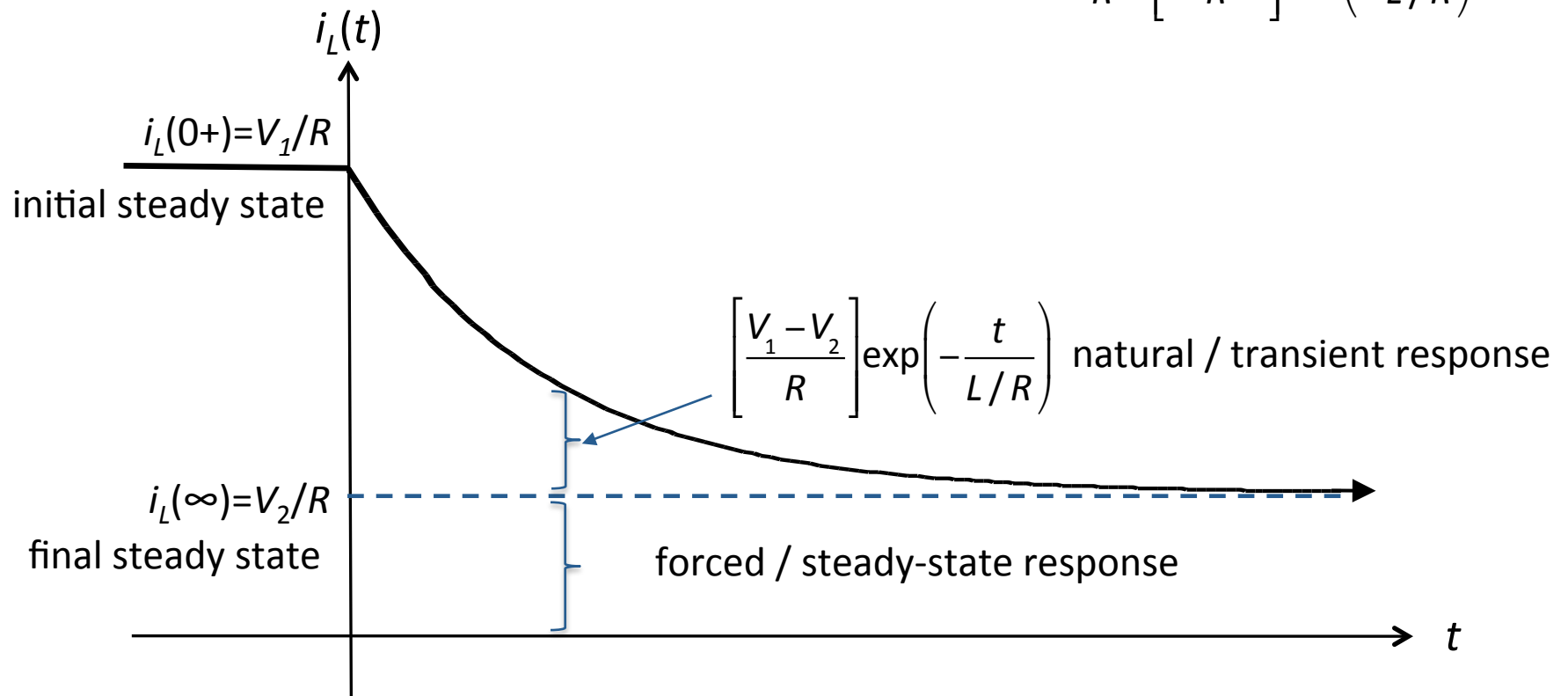
$$\text{solution for } i_L(t) \text{ for } t > 0 : \quad i_L(t) = \frac{V_2}{R} + \left[\frac{V_1 - V_2}{R} \right] \exp\left(-\frac{t}{L/R}\right)$$



* We assume $V_1 > V_2$ in this graph.


time constant

The time constant τ of an RL circuit is thus easily identified:

$$i_{\text{natural}}(t) = \Delta i \exp\left(-\frac{t}{L/R}\right) = \Delta i \exp\left(-\frac{t}{\tau}\right)$$

$$\therefore \tau = L/R$$

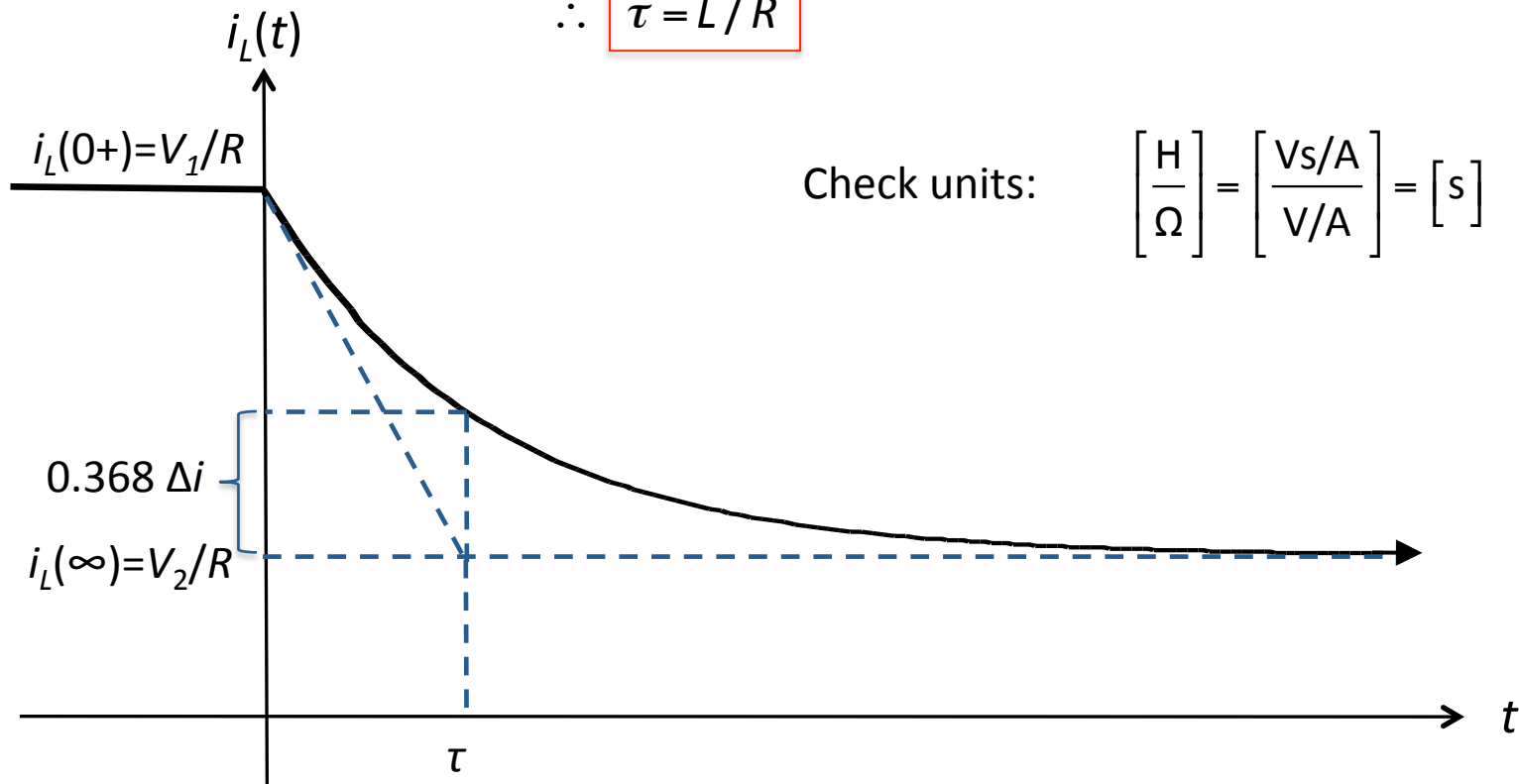
Check units: $\left[\frac{\text{H}}{\Omega}\right] = \left[\frac{\text{Vs/A}}{\text{V/A}}\right] = [\text{s}]$



* We assume $V_1 > V_2$ in this graph.

time constant

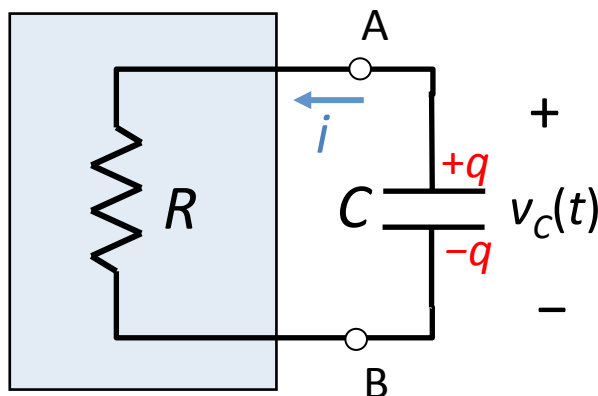
Question: The time constant $\tau = RC$ for an RC circuit and $\tau = L/R$ for an RL circuit, so that a larger R lengthens the transient response for an RC circuit, while a larger resistance shortens the transient response of an RL circuit. To see why, consider two circuits converting stored energy to heat.



$$\frac{dq}{dt} = -i = -\frac{v_c}{R}$$

$$\frac{dv_c}{dt} = \frac{-i}{C} = -\frac{v_c}{RC}$$

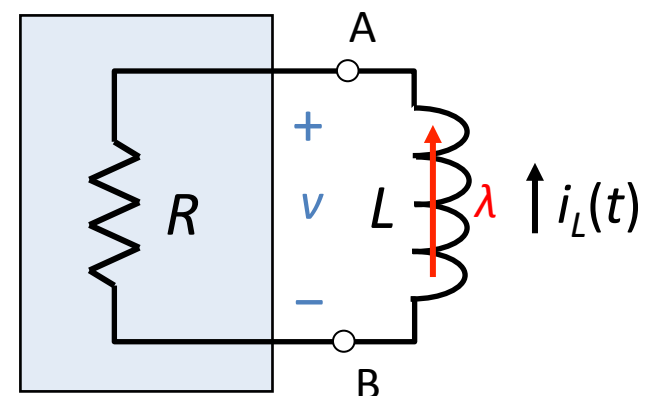increasing R **decreases**
the rate at which charge
separation decays



$$\frac{d\lambda}{dt} = -v = -i_L R$$

$$\frac{di_L}{dt} = \frac{-v}{L} = -\frac{i_L R}{L} = -\frac{i_L}{L/R}$$

increasing R **increases**
the rate at which flux
linkage decays


constant input: general procedure

step #1: Find the initial value of the circuit variable of interest, $x(0+)$, using circuit analysis and continuity of *capacitor voltage* or *inductor current*.

step #2: Find the final value of the variable of interest, $x(\infty)$, using dc steady state models for the capacitor or inductor.


step #3: Find the Thévenin equivalent resistance R_T as seen from the terminals of the capacitor or inductor. The time constant $\tau = R_T C$ or $\tau = L/R_T$.

step #4: Construct the solution.

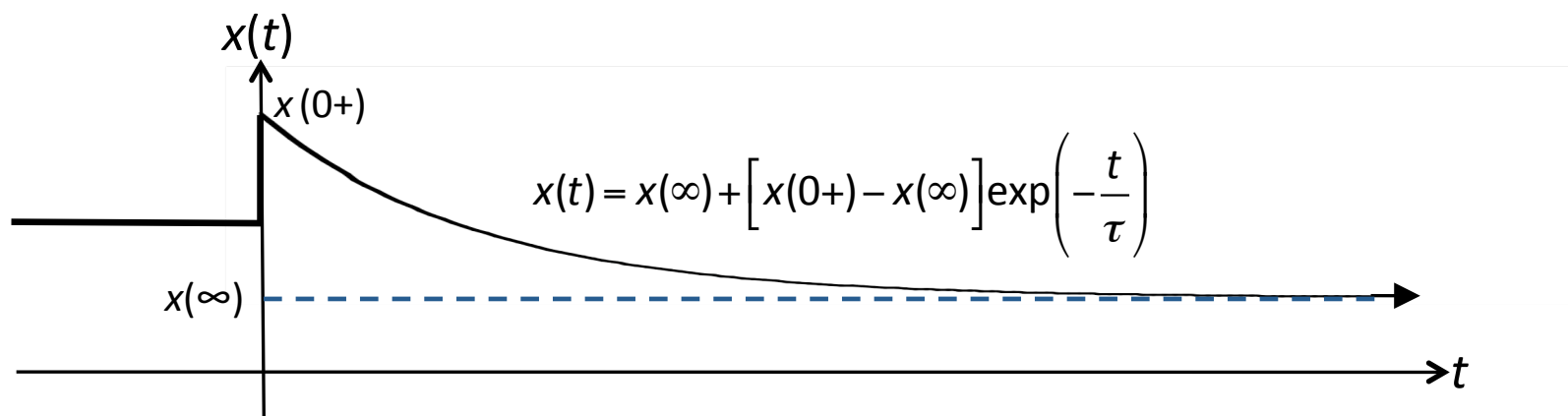

example 1


The circuit is in dc steady state at $t=0^-$. At $t = 0$, the switch changes position. Find $i(t)$ for $t > 0$.

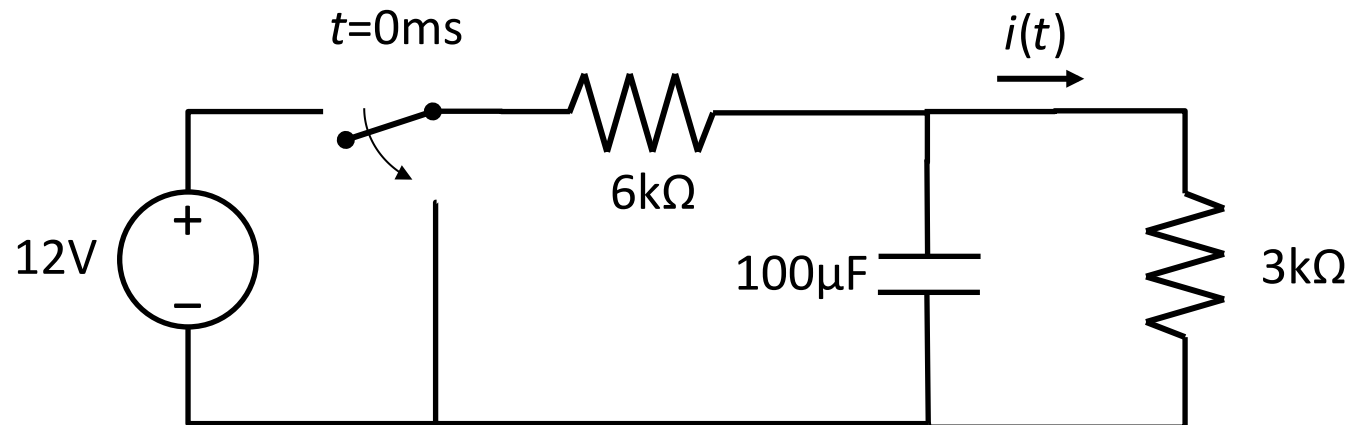

example 1

step #1: At $t < 0$, the circuit is in dc steady state, so the capacitor acts as an open and the capacitor voltage is found by voltage division.

$$v(0-) = 12V \frac{3k\Omega}{3k\Omega + 6k\Omega} = 4V$$

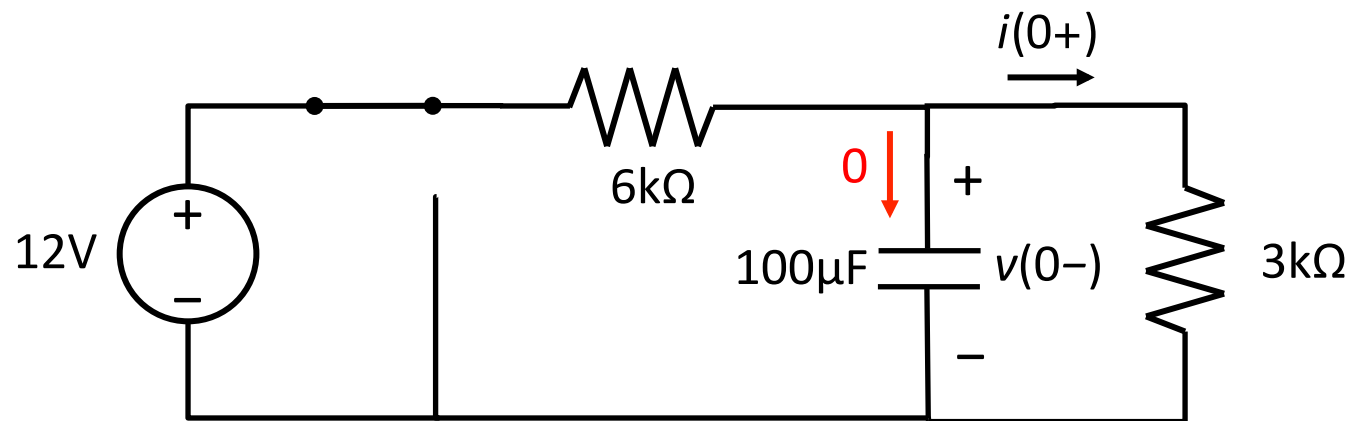


example 1

step #1: At $t = 0+$ the switch has just moved, and we find the current $i(0+)$ using capacitor voltage continuity.

$$\text{continuity: } v(0+) = v(0-) = 4V$$

$$\text{Ohm's Law: } i(0+) = \frac{v(0+)}{3k\Omega} = 1.33\text{mA}$$

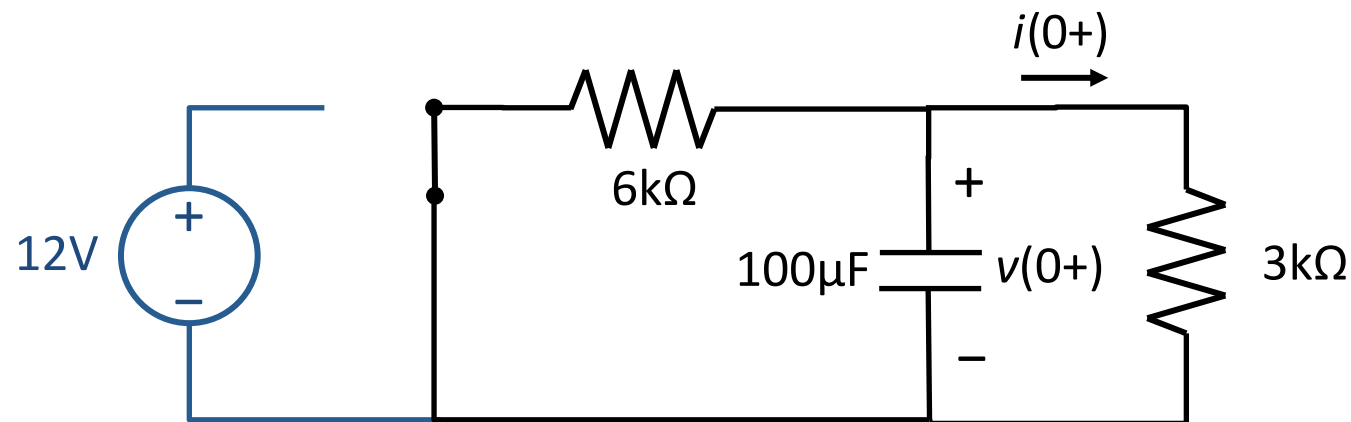


example 1

step #2: As $t \rightarrow \infty$, the circuit again reaches dc steady state. We find the current $i(\infty)$.

$$\text{node equation: } 0 = \frac{v(\infty)}{3\text{k}\Omega} + 0 + \frac{v(\infty)}{6\text{k}\Omega}$$

$$v(\infty) = 0$$

$$i(\infty) = \frac{v(\infty)}{3\text{k}\Omega} = 0$$

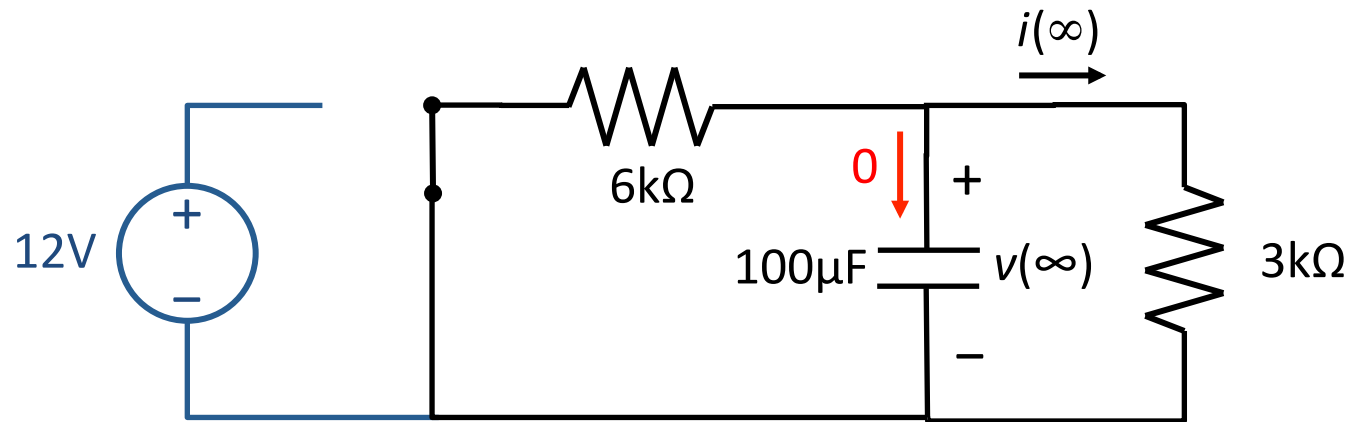


example 1

step #3: Find R_T as seen from the capacitor terminals (identified A and B).
Find the time constant $\tau = R_T C$.

$$R_T = 3\text{k}\Omega \parallel 6\text{k}\Omega = \frac{3 \cdot 6}{3 + 6} \text{k}\Omega = 2\text{k}\Omega$$

$$\begin{aligned} \tau &= R_T C = 2\text{k}\Omega \cdot 100\mu\text{F} \\ &= 200\text{ms} \end{aligned}$$

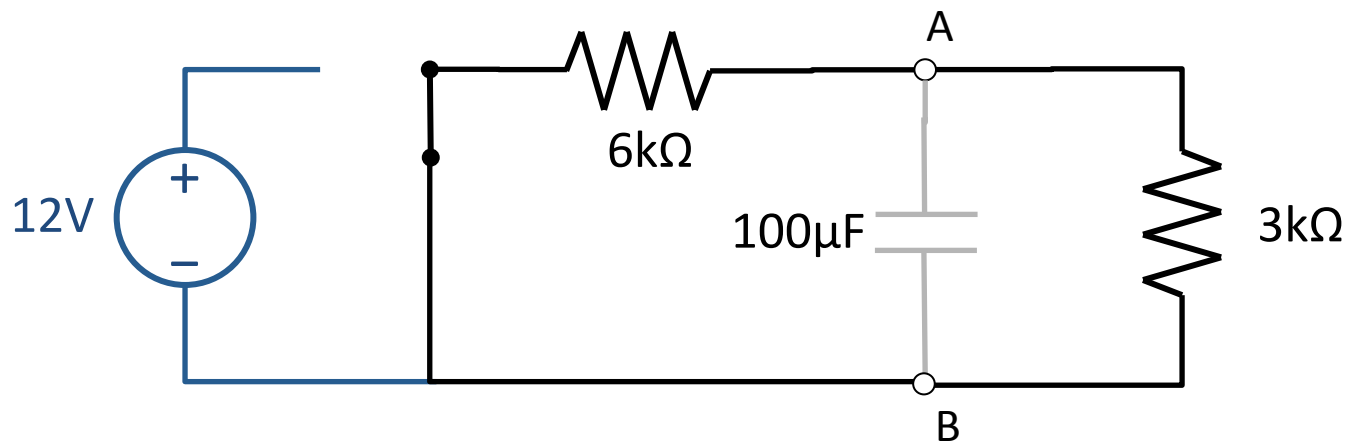



example 1

step #4: Assemble the solution.

$$i(t) = i(\infty) + [i(0+) - i(\infty)] \exp\left(-\frac{t}{\tau}\right)$$


$$i(\infty) = 0\text{mA} \quad i(0+) = 1.333\text{mA} \quad \tau = 200\text{ms}$$

$$i(t) = 1.333\text{mA} \exp\left(-\frac{t}{200\text{ms}}\right)$$

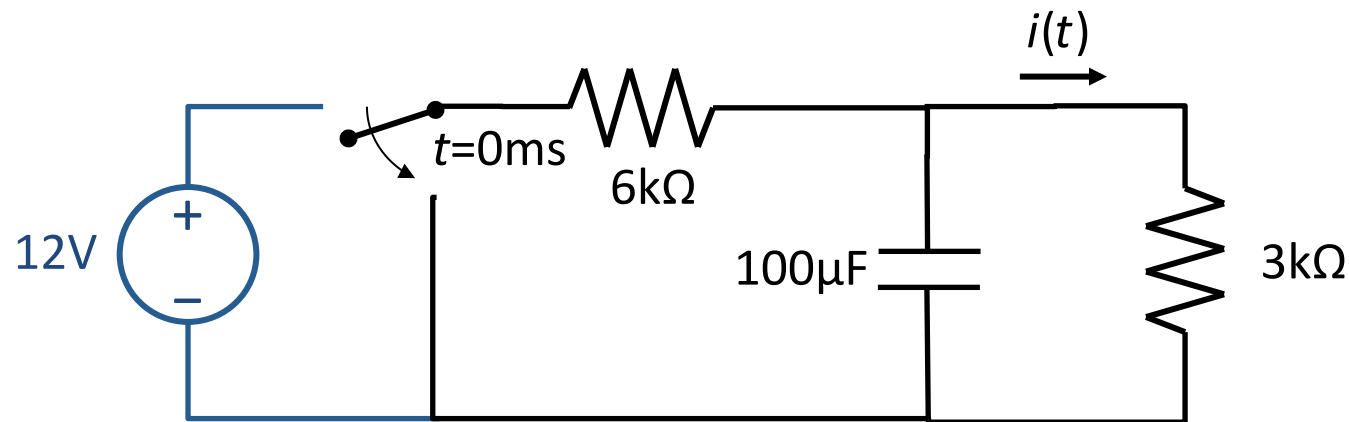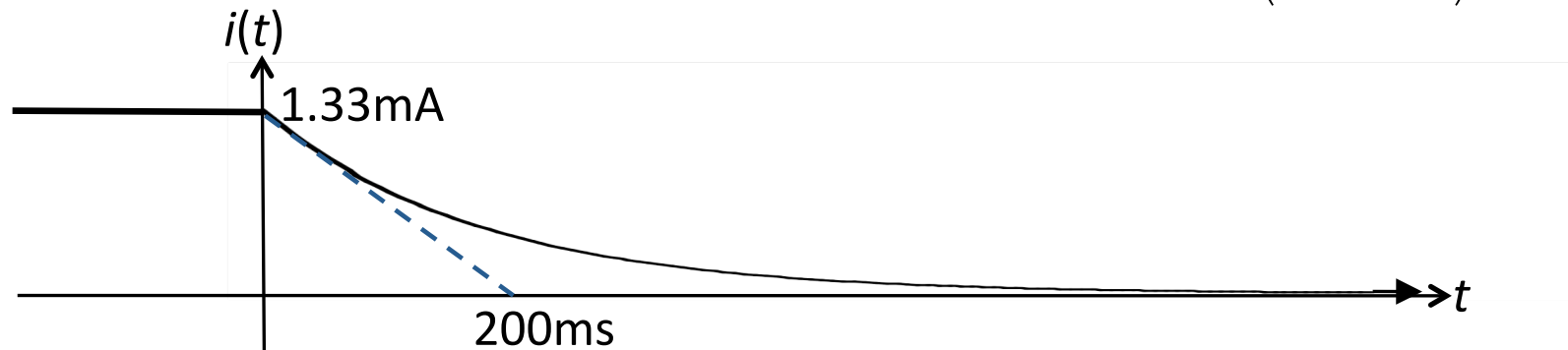

example 2

The circuit is in dc steady state at $t=0^-$. At $t = 0$, the switch changes position. Find $v(t)$ for $t > 0$.

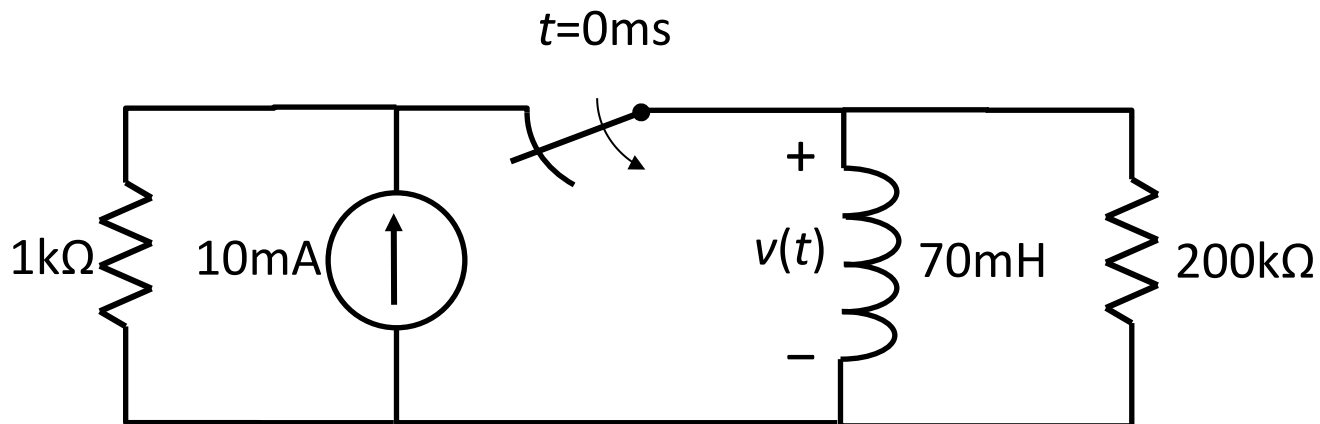


example 2

step #1: At $t < 0$, the circuit is in dc steady state, so the inductor acts as a short.

$$0 = \frac{0}{1\text{k}\Omega} - 10\text{mA} + i(0-) + \frac{0}{200\text{k}\Omega}$$

$$i(0-) = 10\text{mA}$$

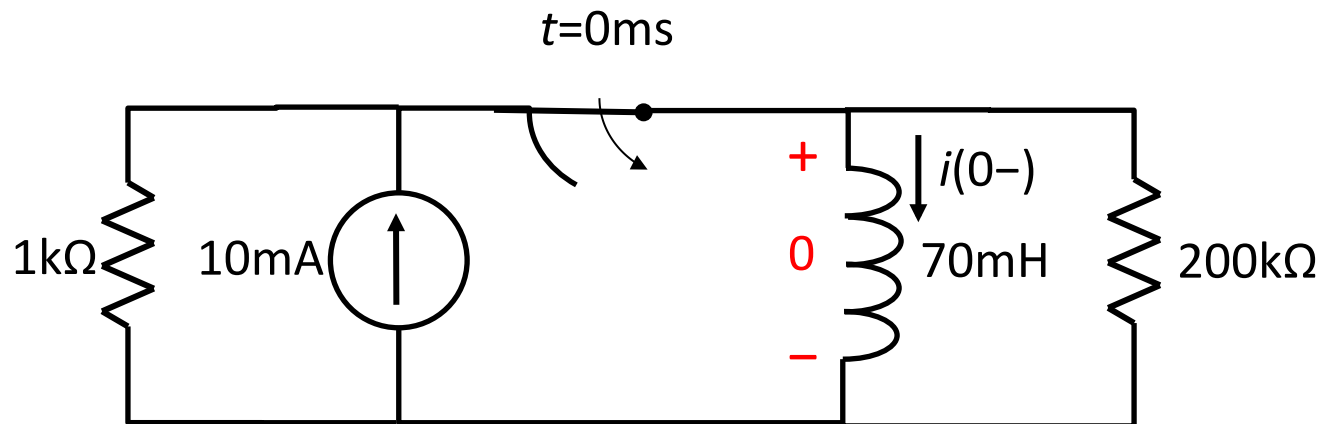


example 2

step #1: At $t = 0+$, the switch moves, and we find $v(0+)$ using inductor current continuity (the inductor supplies current to the $200\text{k}\Omega$ resistor).

$$\text{continuity: } i(0+) = i(0-) = 10\text{mA}$$

$$\text{node eqn.: } 0 = i(0+) + \frac{v(0+)}{200\text{k}\Omega}$$


$$v(0+) = -i(0+) \cdot 200\text{k}\Omega = -2\text{kV}$$

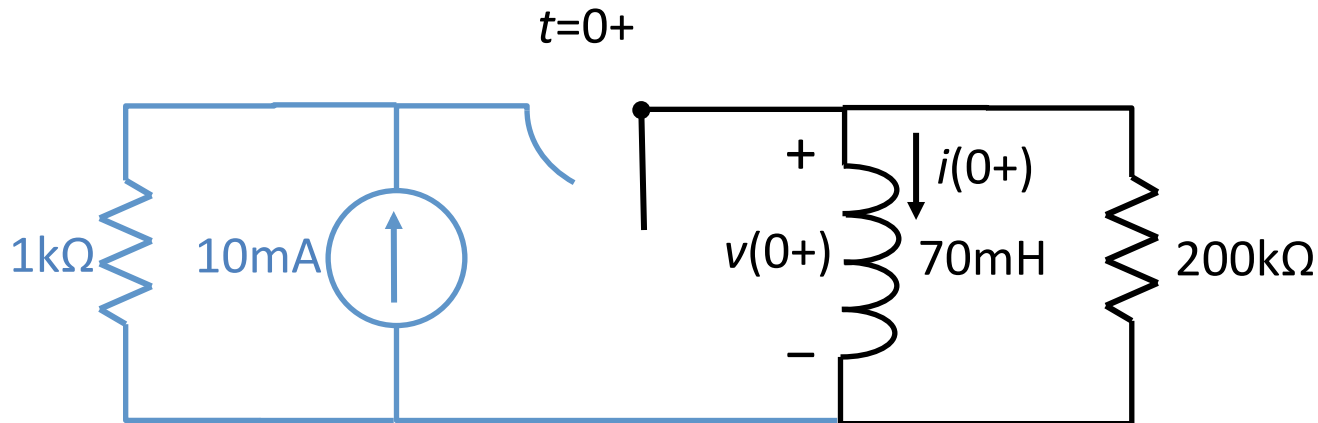

example 2

step #2: As $t \rightarrow \infty$, the circuit approaches dc steady state so the inductor acts as a short.

$$v(\infty) = L \left. \frac{di}{dt} \right|_{t \rightarrow \infty} = 0$$

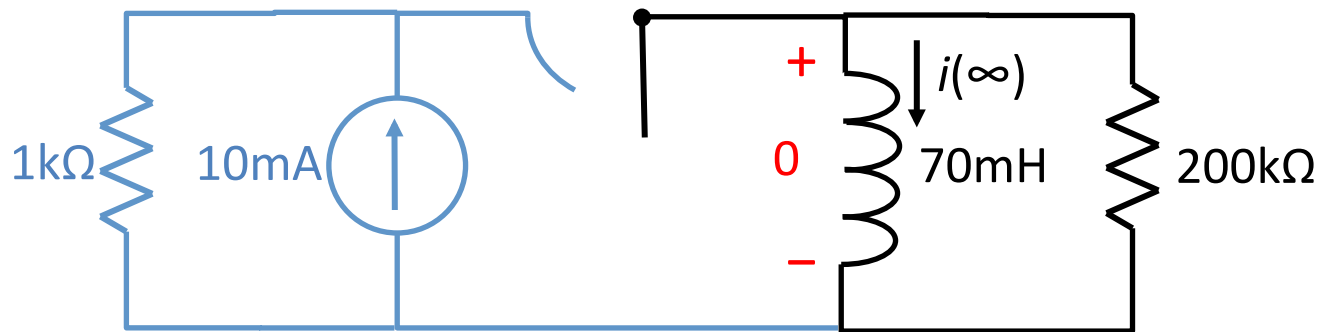


example 2

step #3: Find R_T as seen from the inductor terminals (identified A and B). Find the time constant $\tau = L/R_T$.

$$R_T = 200\text{k}\Omega$$

$$\tau = \frac{L}{R_T} = \frac{70\text{mH}}{200\text{k}\Omega} = 0.35\mu\text{s} = 350\text{ns}$$

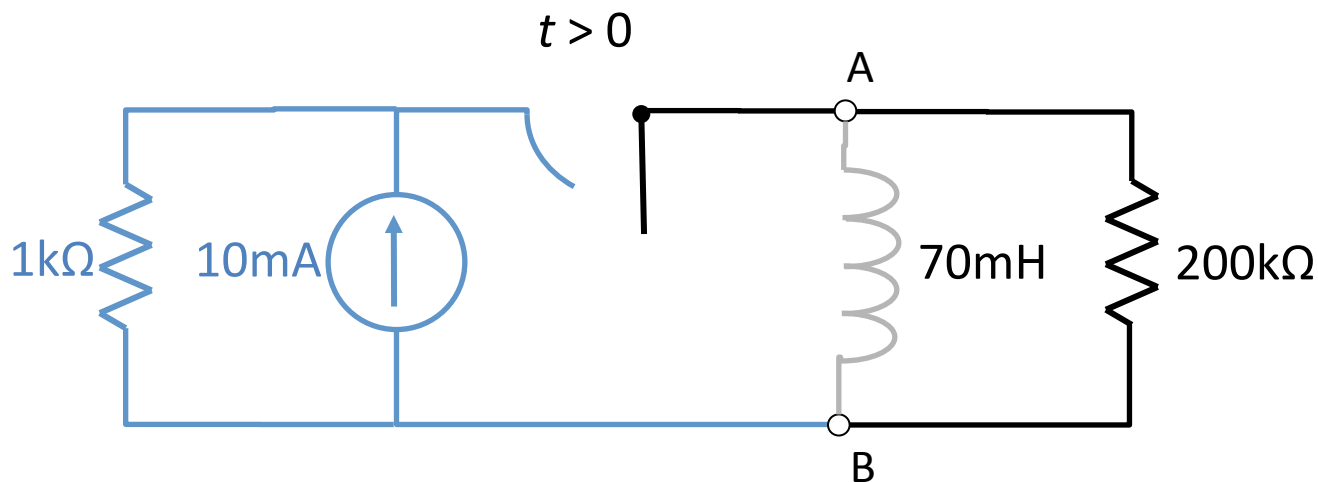


example 2

step #4: Assemble the solution.

$$v(t) = v(\infty) + [v(0+) - v(\infty)] \exp\left(-\frac{t}{\tau}\right)$$

$$v(\infty) = 0V \quad v(0+) = -2kV \quad \tau = 350ns$$
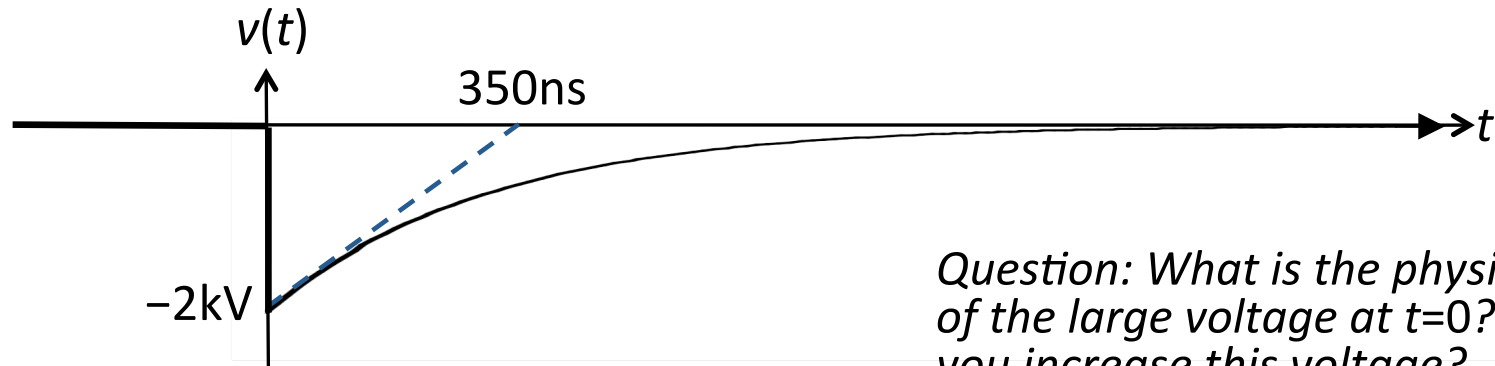
$$v(t) = -2kV \exp\left(-\frac{t}{350ns}\right)$$



Question: What is the physical origin of the large voltage at $t=0$? How can you increase this voltage?

