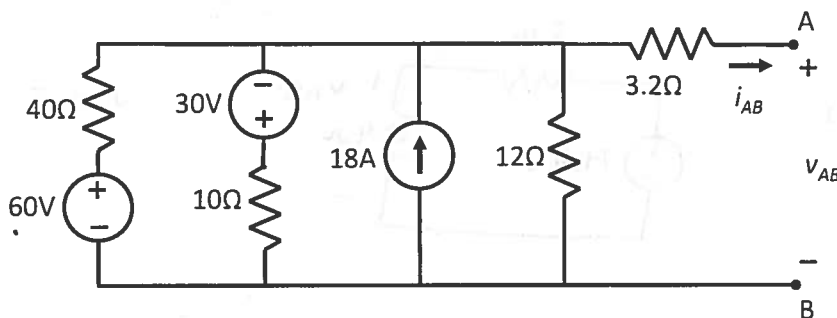


NAME _____ McGill ID# _____

READ each question carefully. Do your work independently. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

- 1) Write the equation that relates open circuit voltage v_{oc} , short circuit current i_{sc} and Thévenin resistance R_T . [1pt]

Consider the circuit diagram.



- 2) What is the Thévenin equivalent circuit (voltage source in series with resistance) with respect to the terminals A and B? [3pts]


- 3) Draw the diagram of i_{AB} versus v_{AB} . Clearly indicate in your diagram the open circuit voltage and short circuit current. [2pts]

- 4) What is v_{AB} if a 16Ω resistor is attached across terminals A and B? [1pt]


- 5) What is v_{AB} if a 4Ω resistor is attached across terminals A and B? [1pt]

1) $V_{oc} = i_{sc} \cdot R_T$ [+1]

2) Use source transformations. [+2]

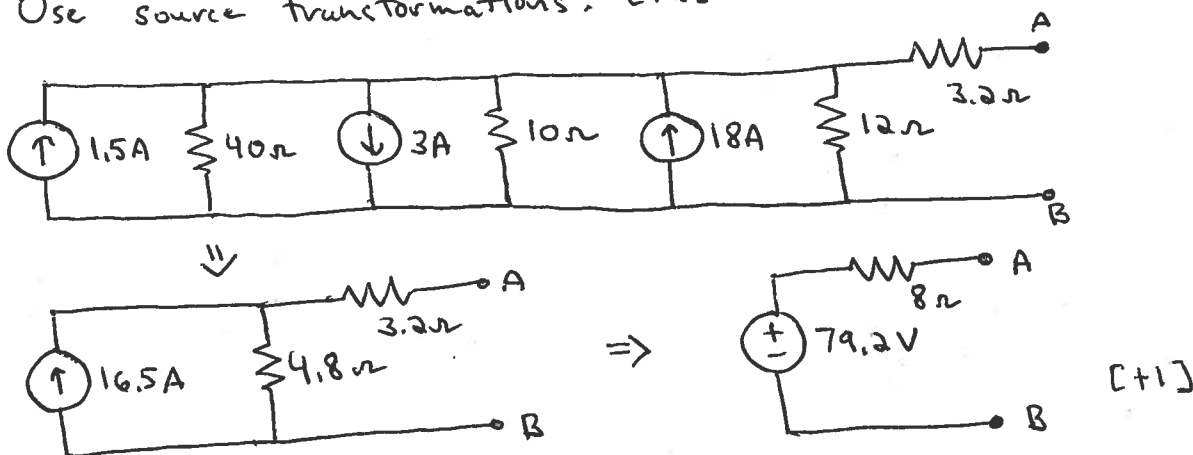

3)

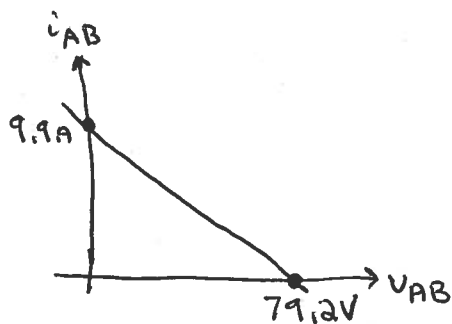


$$i_{sc} = \frac{79.2V}{8\Omega} = 9.9A$$

[+1] for shape

[+1] for values


4)

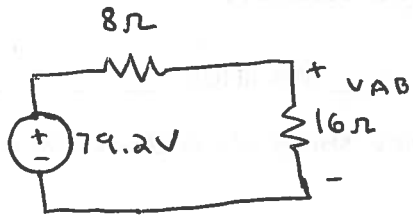

$$V_{AB} = \frac{79.2V \cdot 16\Omega}{8\Omega + 16\Omega}$$

$$= 52.8V \quad [+]]$$

5)

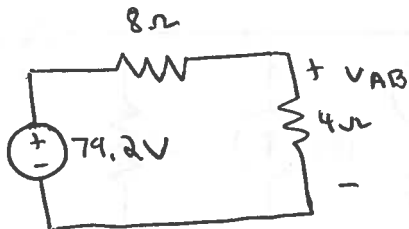

$$V_{AB} = \frac{79.2V \cdot 4\Omega}{8\Omega + 4\Omega}$$

$$= 26.4V \quad [+]]$$