



Electric Circuits 1
ECSE-200 Section: 1

12 December 2016, 2:00PM


Examiner: Thomas Szkopek

Assoc Examiner: Michael Rabbat

INSTRUCTIONS:


- This is a **CLOSED BOOK** examination.
- **NO CRIB SHEETS** are permitted.
- Provide your answers in an **EXAM BOOKLET**.
- **STANDARD CALCULATOR** permitted ONLY.
- This examination consists of 4 questions, with a total of 6 pages, including the cover page.
- This examination is **PRINTED ON BOTH SIDES** of the paper

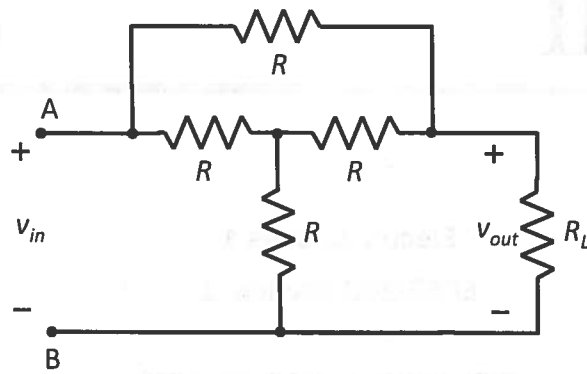1. Consider the circuit below. Answer the questions. [12 pts]








- What is the physical law at the origin of Kirchoff's current law? [1pt]
- What is the physical law at the origin of Kirchoff's voltage law? [1pt]
- What is the equivalent resistance between nodes A and B if R_L is an open circuit? [2pts]
- What is the equivalent resistance between nodes A and B if R_L is a short circuit? [2pts]
- What is the equivalent resistance between nodes A and B if $R_L = R$? [2pts]
- What is the ratio v_{out}/v_{in} if $R_L = R$? [2pts]
- What is the equivalent resistance between nodes A and B if $R_L = 3R$? [2pts]

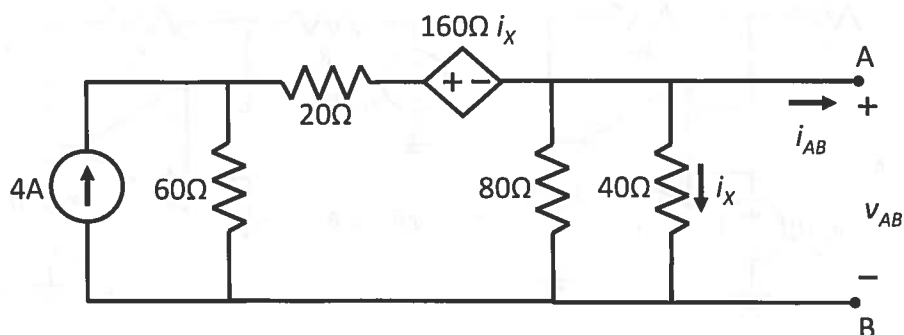2. Consider the circuit below. Answer the questions. [12 pts]




- What is Thévenin's theorem? [1pt]
- Write the equation that relates the quantities v_{oc} , i_{sc} and R_T . [1pt]
- Draw the Thévenin equivalent circuit with respect to the nodes A and B. Be sure to label the nodes A and B in your diagram. [4pts]
- Draw the i_{AB} versus v_{AB} diagram for the circuit. Label your axes. [2pts]
- What is the maximum power that the circuit can deliver to an optimally chosen load resistor attached to the nodes A and B? [2pts]
- It is desired that 10W is delivered to a load resistor R attached to the nodes A and B. What value(s) of R achieve this condition? [2pts]

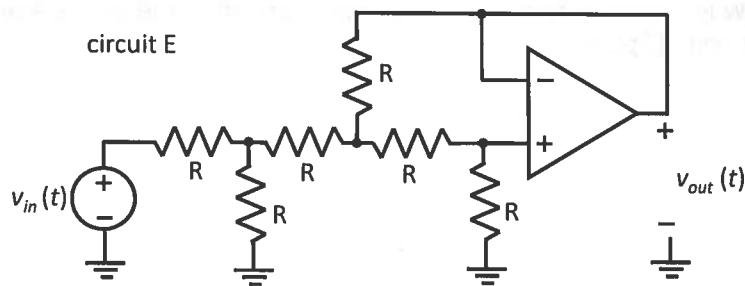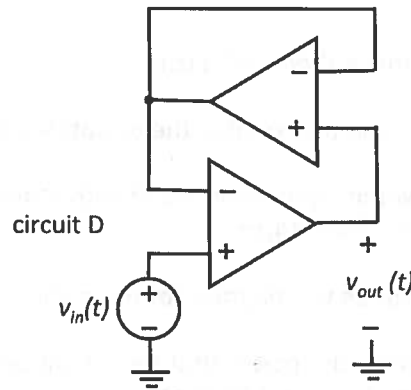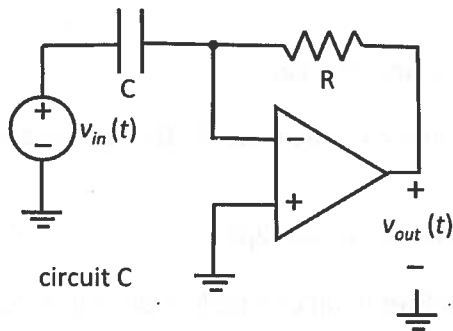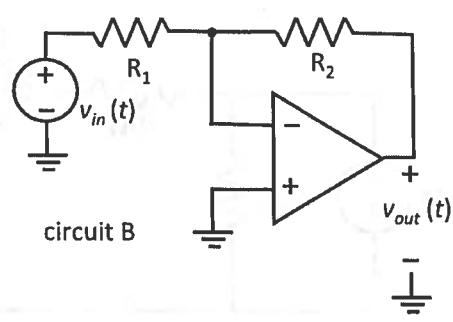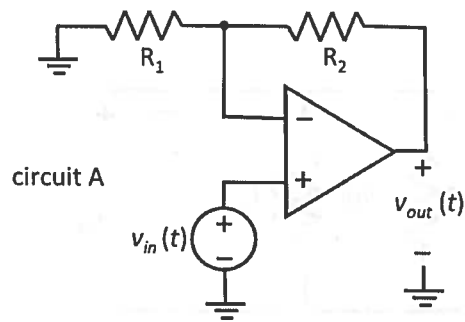3. Consider the circuits below. Assume ideal op-amp behaviour. Answer the questions. [12 pts]



- Give two reasons why negative feedback is useful for op-amp circuits. [2pts]
- Express v_{out} in terms of v_{in} for circuit A ? [2pts]
- Express v_{out} in terms of v_{in} for circuit B ? [2pts]
- Express v_{out} in terms of v_{in} for circuit C ? [2pts]
- Express v_{out} in terms of v_{in} for circuit D ? [2pts]
- Express v_{out} in terms of v_{in} for circuit E ? [2pts]

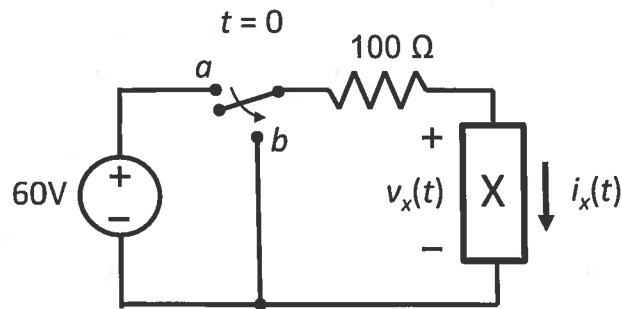4. Consider the circuit below. The circuit is in dc steady state for $t < 0$ with the switch in position a. The switch instantaneously moves to position b at $t = 0$ s. The circuit reaches a new dc steady state as $t \rightarrow \infty$. Answer the questions. [12 pts]



Assume X is a 50 μ H inductor.

a) What is $i_x(t)$ for $t > 0$? [2pts]

b) What is $v_x(t)$ for $t > 0$? [2pts]

Assume X is a 500 pF capacitor.

c) What is $v_x(t)$ for $t > 0$? [2pts]

d) What is $i_x(t)$ for $t > 0$? [2pts]

e) At what time t does the capacitor deliver the maximum power to the circuit? [2pts]

Assume X is a parallel combination of a 10 nF capacitor and a 100 μ H inductor.


f) What are the roots of the characteristic equation describing the natural response of the circuit for the time $t > 0$? [2pts]

end


1.

a) conservation of charge (+1)


b) conservation of energy (+1)

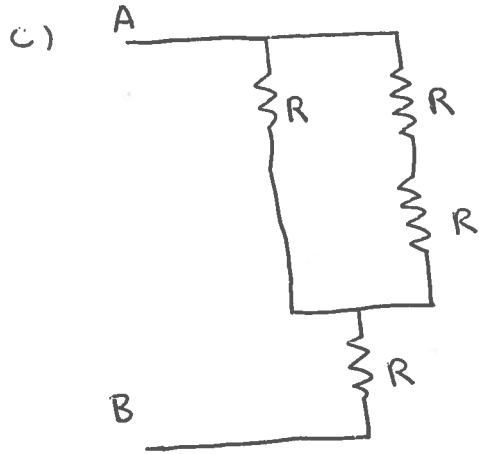
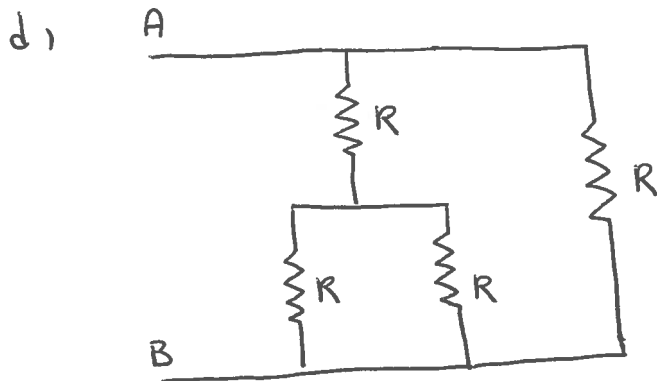
$$\begin{aligned}
 R_{AB} &= R // 2R + R \\
 &= \frac{R \cdot 2R}{R + 2R} + R \\
 &= \frac{5}{3} R \quad [+2]
 \end{aligned}$$


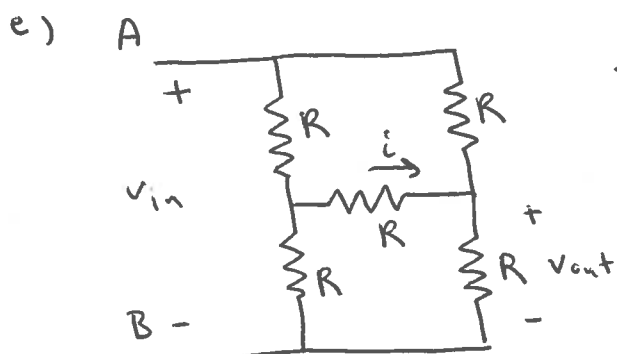
$$\begin{aligned}
 R_{AB} &= (R + R // R) // R \\
 &= \frac{\frac{3}{2} R \cdot R}{\frac{3}{2} R + R} \\
 &= \frac{3}{5} R \quad [+2]
 \end{aligned}$$




This is a balanced Wheatstone bridge, and it can be shown that $i = 0$.

$$\begin{aligned}
 R_{AB} &= (R + R) // (R + R) \\
 &= 2R // 2R \\
 &= R \quad [+2]
 \end{aligned}$$

f)

$$\frac{V_{out}}{V_{in}} = \frac{R}{R + R} = \frac{1}{2} \quad [+2]$$

g)

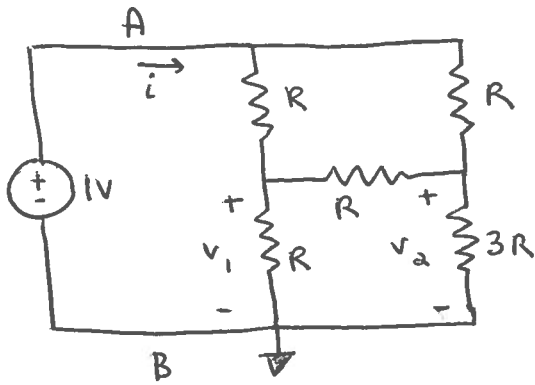

$$0 = \frac{v_1}{R} + \frac{v_1 - v_2}{R} + \frac{v_1 - 1V}{R} \quad \rightarrow \quad 1 = 3v_1 - v_2$$

$$0 = \frac{v_2}{3R} + \frac{v_2 - v_1}{R} + \frac{v_2 - 1V}{R} \quad \rightarrow \quad 3 = -3 + 7v_2$$

$$v_1 = \frac{\begin{vmatrix} 1 & -1 \\ 3 & 7 \end{vmatrix}}{\begin{vmatrix} 3 & -1 \\ -3 & 7 \end{vmatrix}} = \frac{5}{9} V$$

$$v_2 = \frac{\begin{vmatrix} 3 & 1 \\ -3 & 3 \end{vmatrix}}{\begin{vmatrix} 3 & -1 \\ -3 & 7 \end{vmatrix}} = \frac{6}{9} V$$

$$i = \frac{v_1}{R} + \frac{v_2}{3R} = \frac{7}{9} \cdot \frac{1V}{R}$$

$$R_{AB} = \frac{1V}{i} = \frac{9}{7} \cdot R \quad [+\alpha]$$


$$= 1.286 \cdot R$$

2.

a) Any two terminal circuit composed of resistors, dependent sources and independent sources is equivalent to a series combination of a resistance and independent voltage source. [+1]

b) $V_{oc} = i_{sc} \cdot R_T$ [+1]

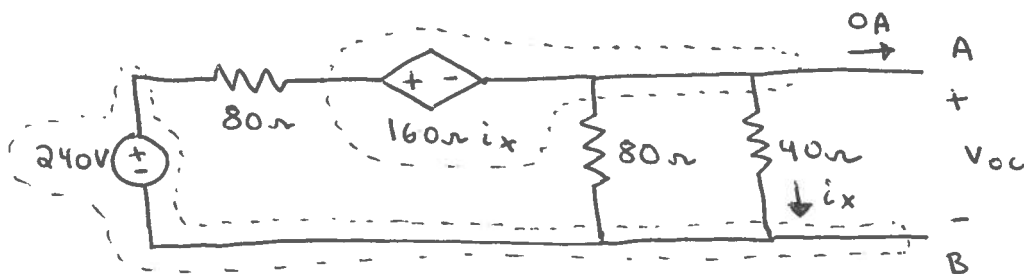c) First simplify the circuit by source transformation.
Find V_{oc} .




$$0 = \frac{V_{oc}}{40\Omega} + \frac{V_{oc}}{80\Omega} + \frac{V_{oc} + 160\Omega i_x - 240V}{80\Omega}$$

$$i_x = V_{oc} / 40\Omega$$

$$\therefore 0 = \frac{V_{oc}}{40} + \frac{V_{oc}}{80} + \frac{V_{oc} + 4V_{oc} - 240V}{80}$$

$$V_{oc} = \frac{240V / 2}{1 + \frac{1}{2} + \frac{1}{2}(1+4)} = 30V \quad [+1]$$

Find i_{sc} .

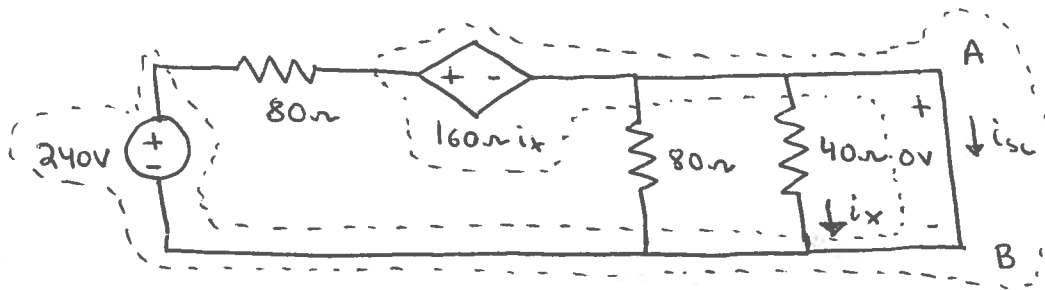


$$i_x = \frac{0V}{40\Omega} = 0A$$


$$0 = i_{sc} + \frac{0V}{40\Omega} + \frac{0V}{80\Omega} + \frac{0 - 240V}{80\Omega}$$

$$i_{sc} = 3A \quad [+1]$$
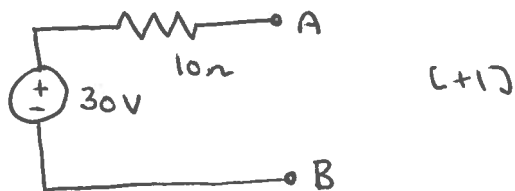
$$R_T = \frac{V_{oc}}{i_{sc}} = \frac{30V}{3A} = 10\Omega \quad [+1]$$



d)

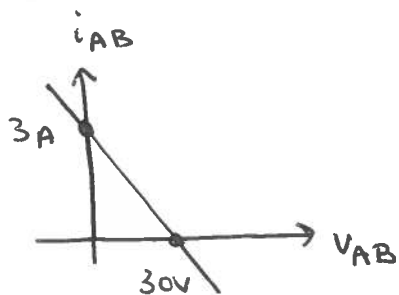


[+2]

$$e) \quad P_{\max} = \frac{V_{oc}}{2} \cdot \frac{i_{sc}}{2} \quad [+1]$$

$$= 22.5 \text{ W} \quad [+1]$$

f)

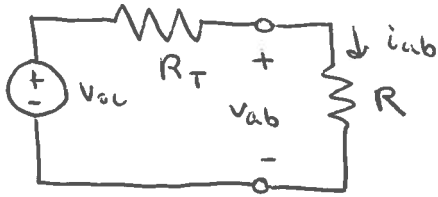

$$V_{ab} = V_{oc} - i_{ab} \cdot R_T$$

$$P_{abs} = V_{ab} \cdot i_{ab}$$

$$\therefore V_{ab} = V_{oc} - \frac{P_{abs} \cdot R_T}{V_{ab}}$$

$$0 = V_{ab}^2 - V_{ab} \cdot V_{oc} + P_{abs} \cdot R_T$$

$$= V_{ab}^2 - V_{ab} \cdot 30 \text{ V} + 10 \text{ W} \cdot 10 \Omega$$

$$V_{ab} = \frac{30 \text{ V} \pm \sqrt{(30 \text{ V})^2 - 4 \cdot 1 \cdot 10 \text{ W} \cdot 10 \Omega}}{2}$$


$$= 26.18 \text{ V}, 3.820 \text{ V}$$

$$i_{ab} = \frac{P_{abs}}{V_{ab}} = 0.3820 \text{ A}, 2.618 \text{ A}$$

$$R = \frac{V_{ab}}{i_{ab}} = 68.5 \Omega, 1.459 \Omega \quad [+2]$$


3.

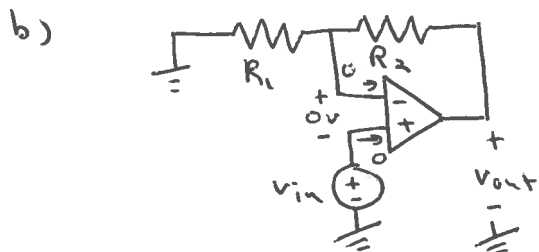- a) stability [+1]
 programmability [+1]




$$0 = \frac{v_{in}}{R_1} + \frac{v_{in} - v_{out}}{R_2}$$
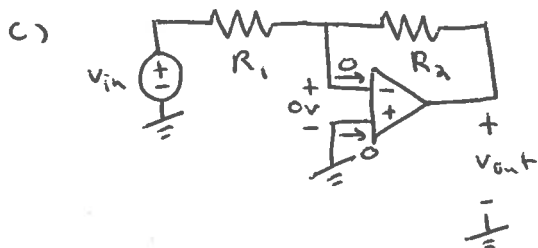
$$v_{out} = \left(1 + \frac{R_2}{R_1}\right) v_{in} \quad [+2]$$




$$0 = \frac{0 - v_{in}}{R_1} + \frac{0 - v_{out}}{R_2}$$
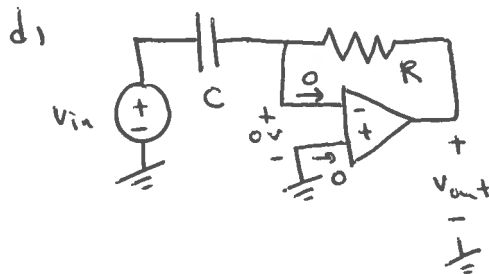
$$v_{out} = -\frac{R_2}{R_1} \cdot v_{in} \quad [+2]$$




$$0 = C \frac{d}{dt} (0 - v_{in}) + \frac{0 - v_{out}}{R}$$
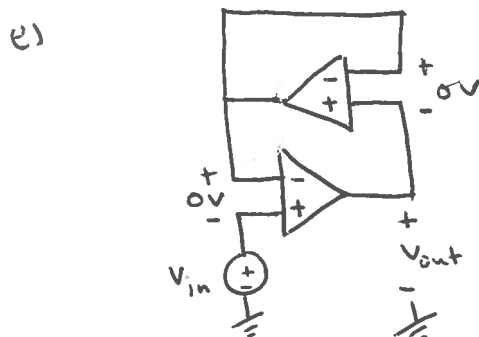
$$v_{out} = -RC \frac{dv_{in}}{dt} \quad [+2]$$



$$v_{out} = v_{in} \quad [+2]$$

f)

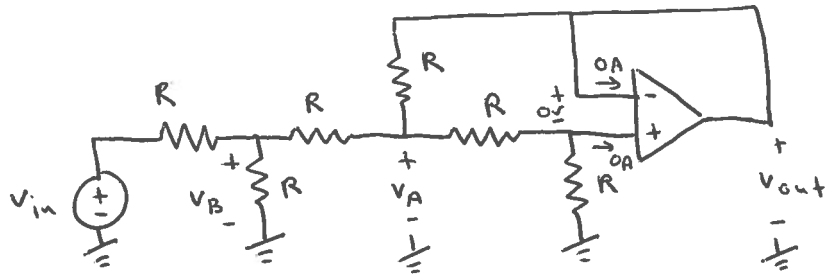

$$0 = \frac{v_{out}}{R} + \frac{v_{out} - V_A}{R} \rightarrow V_A = 2v_{out}$$

$$0 = \frac{V_A - v_{out}}{R} + \frac{V_A - v_{out}}{R} + \frac{V_A - V_B}{R}$$

$$\rightarrow V_B = 3V_A - 2v_{out} = 4v_{out}$$


$$0 = \frac{V_B - V_A}{R} + \frac{V_B}{R} + \frac{V_B - v_{in}}{R}$$

$$\rightarrow v_{in} = 3V_B - V_A = 10v_{out}$$

$$v_{out} = \frac{1}{10} v_{in} \quad [+2]$$


4.

a) $t < 0$

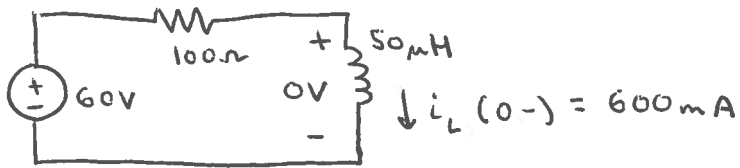


$$i_L(0+) = i_L(0-) = 600\text{mA}$$

$t \rightarrow \infty$

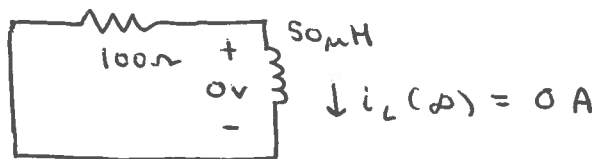

$t > 0$

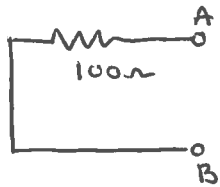

$$\tau = L/R_T = \frac{50\mu\text{H}}{100\Omega} = 500\text{ns} \quad [+1]$$


$$\begin{aligned} i_L(t) &= [i_L(0+) - i_L(\infty)] \exp(-t/\tau) + i_L(\infty) \\ &= 600\text{mA} \exp(-t/500\text{ns}) \quad [+1] \end{aligned}$$

$$b) \quad v_L(t) = L \frac{di_L}{dt} \quad [+1] \quad \text{or} \quad v_L = -R \cdot i_L$$

$$= 50\mu\text{H} \cdot 600\text{mA} \cdot \frac{-1}{500\text{ns}} \exp(-t/500\text{ns})$$


$$= -60\text{V} \exp(-t/500\text{ns}) \quad [+1]$$

c) $t < 0$

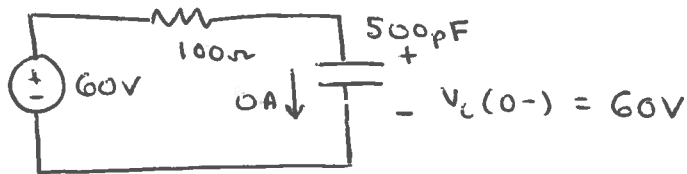


$$V_C(0+) = V_C(0-) = 60V$$

$t \rightarrow \infty$

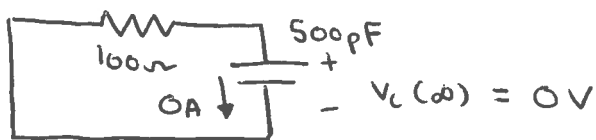

$t > 0$

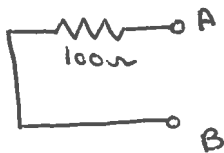

$$\tau = R_T \cdot C = 100\Omega \cdot 500pF = 50ns \quad [+1]$$

$$\begin{aligned} V_C(t) &= [V_C(0+) - V_C(\infty)] \exp(-t/\tau) + V_C(\infty) \\ &= 60V \exp(-t/50ns) \quad [+1] \end{aligned}$$

d) $i_C(t) = C \frac{dV_C}{dt} \quad [+1] \quad \text{or} \quad i_C = -V_C / R$

$$= 500pF \cdot 60V \cdot \frac{-1}{50ns} \exp(-t/50ns)$$

$$= -600mA \exp(-t/50ns) \quad [+1]$$

e)


$$P_{del} = -V_c(t) \cdot i_c(t)$$

$$t < 0 : P_{del} = 0 \text{ W}$$

$$\begin{aligned} t > 0 : P_{del} &= 60 \text{ V} \exp(-t/50 \text{ ns}) \cdot 600 \text{ mA} \exp(-t/50 \text{ ns}) \\ &= 36 \text{ W} \exp(-t/25 \text{ ns}) \end{aligned}$$

P_{del} is maximum at $t = 0^+$. [+2]

f) $t > 0$

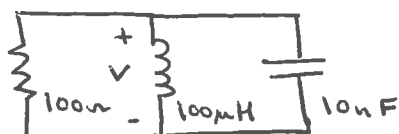

$$0 = \frac{V}{R} + \frac{V}{sL} + \frac{V}{1/sC} = \left(\frac{1}{R} + \frac{1}{sL} + sC \right) \cdot V$$

$$0 = \frac{1}{R} + \frac{1}{sL} + sC$$

$$0 = s^2 + s \cdot \frac{1}{RC} + \frac{1}{LC}$$

$$= s^2 + 10^6 \cdot s + 10^{12}$$

$$s = \frac{-10^6 \pm \sqrt{(10^6)^2 - 4 \cdot 1 \cdot 10^{12}}}{2 \cdot 1}$$

$$= -500,000 \pm i \cdot 866,025 \text{ [s}^{-1}\text{]}$$

[+2]