



Electric Circuits 1
ECSE-200 Section: 1

23 April 2013, 9:00AM


Examiner: Thomas Szkopek

Assoc Examiner: Benoit Champagne


INSTRUCTIONS:

- This is a **CLOSED BOOK** examination.
- **NO CRIB SHEETS** are permitted.
- Provide your answers in an **EXAM BOOKLET**.
- **STANDARD CALCULATOR** permitted ONLY.
- This examination consists of 4 questions, with a total of 6 pages, including the cover page.
- This examination is **PRINTED ON BOTH SIDES** of the paper

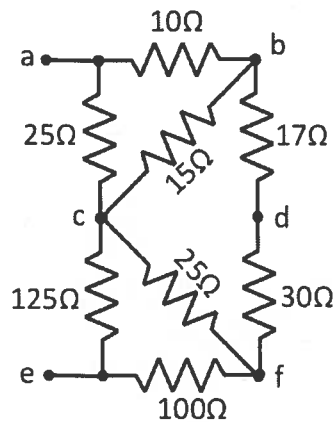1. Consider the circuit below. Answer the questions. [12 pts]




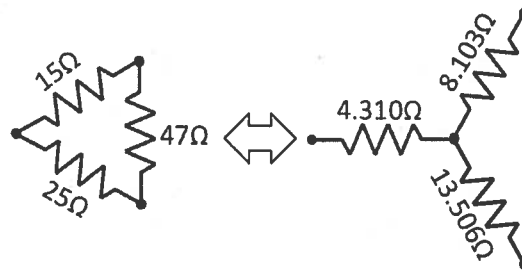- What is the definition of a passive element? [1pt]
 - What is the definition of a linear element? [1pt]
 - What is the equivalent resistance between terminals c and d ? [3pts]
 - What is the equivalent resistance between terminals a and b ? [3pts]
 - What is the equivalent resistance between terminals a and e ? [4pts]
- HINT:** You may find it useful to use the Δ -to-Y transformation below.



- An element that cannot deliver more energy to a circuit than it has received. [1]
- An element where terminal voltage and current are related by a linear function or linear operator. [1]

c)

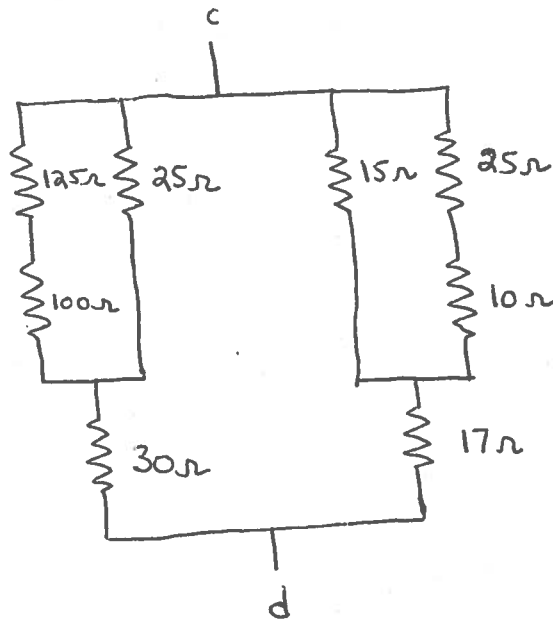


$$R_{cd} = (30\Omega + 225\Omega // 25\Omega) // (17\Omega + 35\Omega // 15\Omega) \quad [+2]$$

$$= 52.5\Omega // 27.5\Omega$$

$$= 18.05\Omega \quad [+1]$$


d)

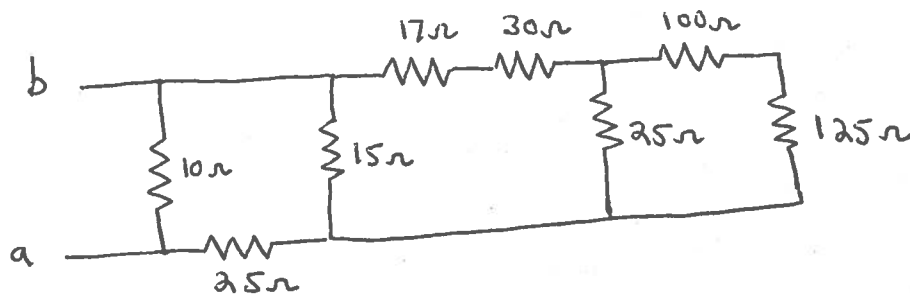

$$R_{ba} = (((225\Omega // 25\Omega + 47\Omega) // 15\Omega) + 25\Omega) // 10\Omega \quad [+2]$$

$$= 7.888\Omega \quad [+1]$$

e)

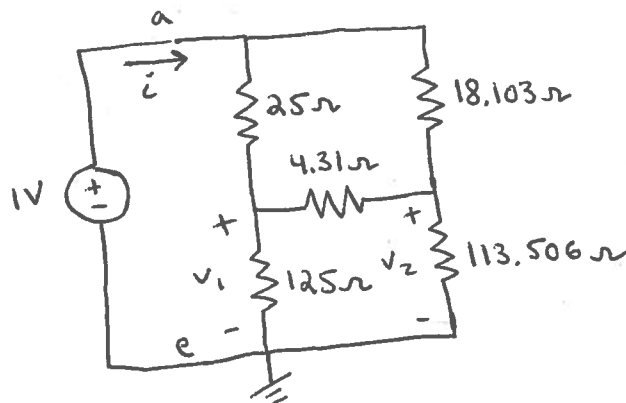

[+1] for equivalent circuit

[+1] for applying source

$$\begin{aligned}
 0 &= \frac{v_1}{125} + \frac{v_1 - v_2}{4.31} + \frac{v_1 - 1}{25} \\
 0 &= \frac{v_2}{113.506} + \frac{v_2 - v_1}{4.31} + \frac{v_2 - 1}{18.103}
 \end{aligned}
 \left\{ \begin{aligned} 0.04 &= 0.2800 v_1 - 0.232 v_2 \\ 0.05524 &= -0.232 v_1 + 0.2961 v_2 \end{aligned} \right.$$

$$v_1 = \frac{\begin{vmatrix} 0.04 & -0.232 \\ 0.05524 & 0.2961 \end{vmatrix}}{\begin{vmatrix} 0.2800 & -0.232 \\ -0.232 & 0.2961 \end{vmatrix}} = 0.848 \text{ V}$$


$$v_2 = \frac{\begin{vmatrix} 0.2800 & 0.04 \\ -0.232 & 0.05524 \end{vmatrix}}{\begin{vmatrix} 0.2800 & -0.232 \\ -0.232 & 0.2961 \end{vmatrix}} = 0.851 \text{ V}$$

$$i = \frac{v_1}{125 \Omega} + \frac{v_2}{113.506 \Omega} = 14.28 \text{ mA}$$

$$R_{ae} = \frac{1 \text{ V}}{i} = 70.0 \Omega \text{ [+1]}$$

[+1]

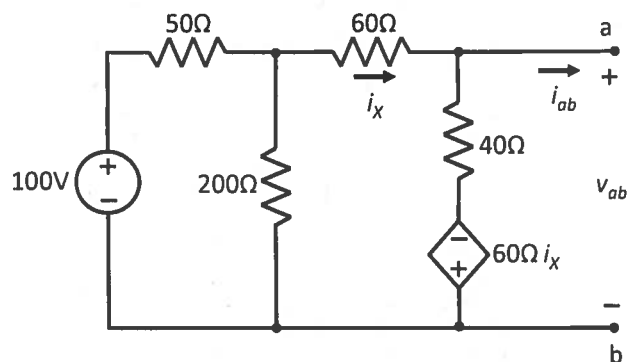2. Consider the circuit below. Answer the questions. [12 pts]



a) What is Thévenin's theorem? [1pt]


b) Draw the Thévenin equivalent circuit with respect to terminals a and b. Be sure to label the terminals a and b in your diagram. [6pts]

c) What is the maximum power that can be delivered to an optimally chosen load resistor attached to the terminals a and b? [2pts]


d) A load resistor R is attached to the terminals a and b. What are the two values of R that will cause a power of 1.5W to be absorbed by R ? [3pts]

a) Any circuit composed of ideal resistors, dependent sources and independent sources is equivalent to a Thévenin circuit (voltage source in series with a resistor). C+17

b) First simplify circuit:

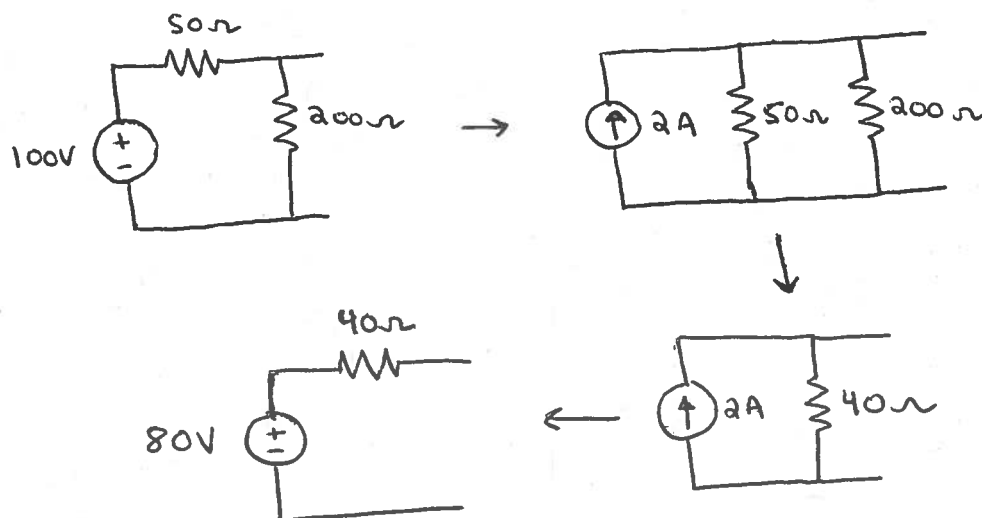

Find V_{oc} . [+]

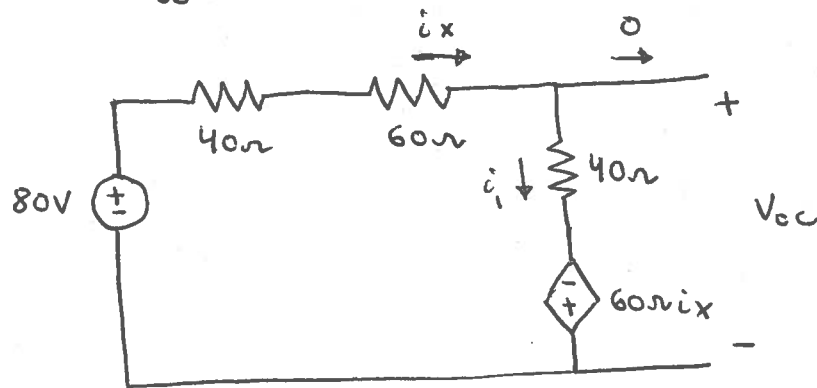

$$KCL: i_1 = i_x$$

$$KVL: 0 = -80V + 40\Omega i_x + 60\Omega i_x + 40\Omega i_x - 60\Omega i_x$$


$$80V = 80\Omega \cdot i_x$$

$$i_x = 1A$$

$$KVL: 0 = 60\Omega i_x - 40\Omega i_x + V_{oc}$$

$$V_{oc} = -20\Omega i_x = -20V \text{ [+]}$$

Find i_{sc} . [+]

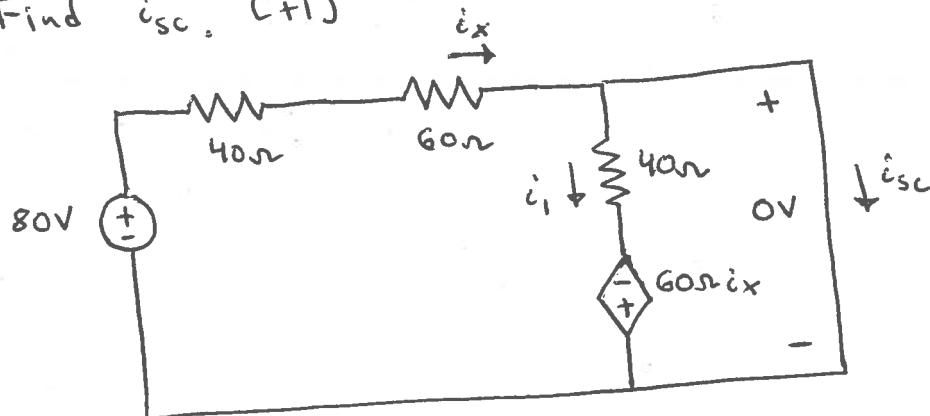

$$KVL: 0 = -80V + 40\Omega i_x + 60\Omega i_x$$

$$i_x = \frac{80V}{100\Omega} = 0.8A$$


$$KVL: 0 = 60\Omega i_x - 40\Omega i_1$$

$$i_1 = \frac{60\Omega \cdot i_x}{40\Omega} = 1.2A$$

$$KCL: i_{sc} = i_x - i_1 = -0.4A \text{ [+]}$$


$$R_T = \frac{V_{oc}}{i_{sc}} = 50\Omega$$

[+1]

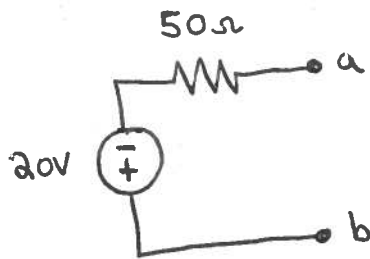

[+1] for diagram
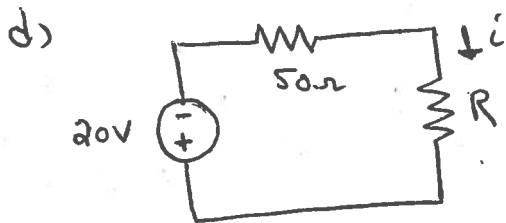
$$\begin{aligned} c) \quad P_{max} &= \frac{V_{oc}}{2} \cdot \frac{i_{sc}}{2} \quad [+1] \\ &= 2W \quad [+1] \end{aligned}$$



$$P_{abs} = i^2 \cdot R$$

$$1.5W = \left(\frac{20V}{R + 50\Omega} \right)^2 \cdot R \quad [+1]$$

$$1.5(R + 50)^2 = 400R$$

$$1.5R^2 + 150R + 3750 = 400R$$

$$1.5R^2 - 250R + 3750 = 0$$


$$R = \frac{250 \pm \sqrt{250^2 - 4 \cdot 1.5 \cdot 3750}}{2 \cdot 1.5}$$

$$= 150\Omega \quad \text{and} \quad 16.67\Omega$$

[+1]

[+1]

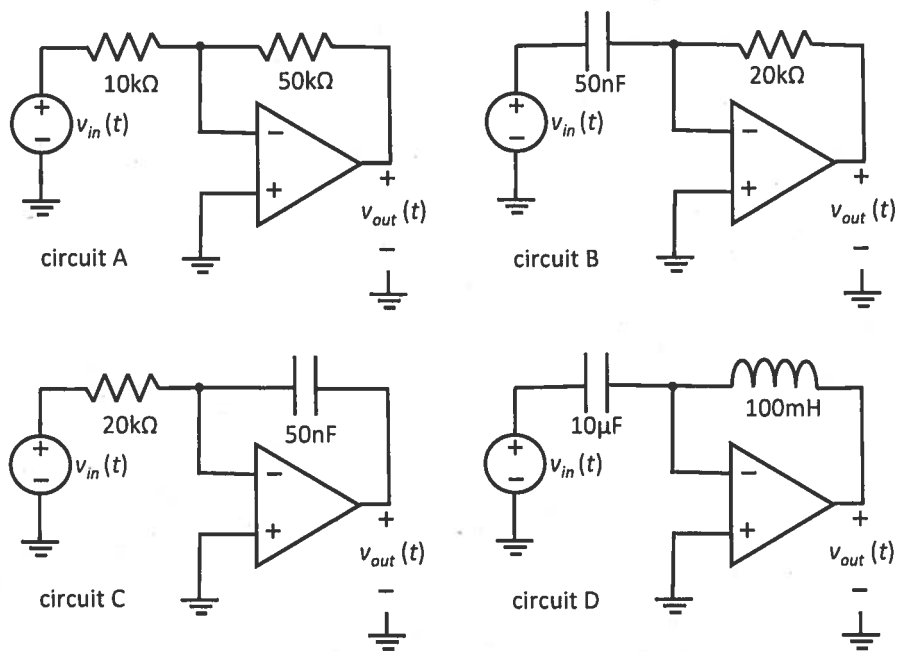3. Consider the circuit below. Assume ideal op-amp behaviour. Answer the questions. [12 pts]



- Give one reason why negative feedback is used in op-amp circuits. [2pts]
- How does the output voltage $v_{out}(t)$ depend upon the input voltage $v_{in}(t)$ for circuit A? [2pts]
- How does the output voltage $v_{out}(t)$ depend upon the input voltage $v_{in}(t)$ for circuit B? [2pts]
- How does the output voltage $v_{out}(t)$ depend upon the input voltage $v_{in}(t)$ for circuit C? Assume that the capacitor stores zero energy at $t = 0s$, and consider only $t \geq 0$. [2pts]
- How does the output voltage $v_{out}(t)$ depend upon the input voltage $v_{in}(t)$ for circuit D? [2pts]
- Voltage sources of $+10V$ and $-10V$ are used to power the op-amp circuit A. What is the range of input voltages that can be used without causing the op-amp to saturate? [2pts]

a) programmable gain
 gain independent of open-loop gain
 stable output

} any one
 [+2]

$$b) \quad 0 = \frac{0 - v_{in}}{10k\Omega} + \frac{0 - v_{out}}{50k\Omega} \quad [1]$$

$$v_{out} = -5 v_{in} \quad [1]$$

$$c) \quad 0 = 50nF \frac{d}{dt} (0 - v_{in}) + \frac{0 - v_{out}}{20k\Omega} \quad [1]$$

$$v_{out} = -1ms \cdot \frac{dv_{in}}{dt} \quad [1]$$

$$d) \quad 0 = \frac{0 - v_{in}}{20k\Omega} + 50nF \frac{d}{dt} (0 - v_{out}) \quad [1]$$

$$v_{out} = \frac{-1}{1ms} \int_0^t v_{in} dt' \quad [1]$$

$t \geq 0$


$$f) \quad -10V < v_{out} < +10V \quad [1]$$

$$\therefore -2V < v_{in} < +2V \quad [1]$$

$$e) \quad 0 = 10\mu F \cdot \frac{d}{dt} (0 - v_{in}) + \frac{1}{100mH} \int_0^t (0 - v_{out}) dt' \quad [1]$$

$$v_{out} = -(1ms)^2 \cdot \frac{d^2 v_{in}}{dt^2} \quad [1]$$

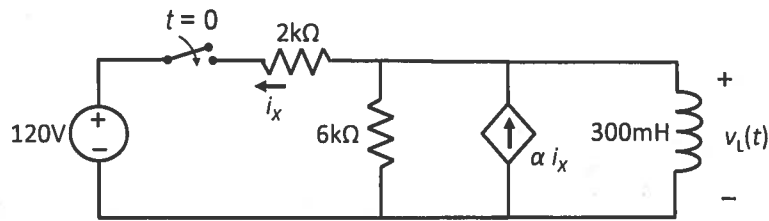4. Consider the circuit below (useful for firing sparks). The switch is open for $t < 0$ s, and closes instantaneously at $t = 0$ s. Assume dc steady state behaviour for $t < 0$. Answer the questions. [12 pts]




- What is the definition of a passive element? [1pt]
- Assume that $\alpha = 0$. What is the voltage $v_L(t)$ for $t > 0$? Plot your solution for $v_L(t)$ versus t . [6pts]
- What is the value of α that causes the Thévenin resistance with respect to the inductor terminals to become $-3k\Omega$ for $t > 0$? [2pts]
- For the value of α found in part c), at what time t will $v_L(t) = 36kV$? [3pts]

a) An element that cannot deliver more energy to a circuit than it has received. [1]

b) Assume $\alpha = 0$.

$$t \leq 0 \quad i_L(0) = 0 \text{ A. [1]}$$

$$t = 0+$$

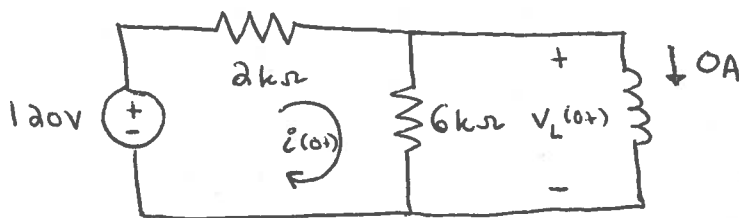


$$i(0+) = \frac{120V}{2k\Omega + 6k\Omega} = 15mA$$

$$v_L(0+) = 6k\Omega \cdot i(0+) = 90V \quad [1]$$

$$t \rightarrow \infty$$

dc steady state is reached, thus $v_L(\infty) = 0V$ [1]

$$\tau = \frac{L}{R_{th}}$$

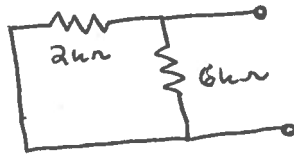

$$R_{th} = 2k\Omega \parallel 6k\Omega$$

$$= 1.5k\Omega$$

$$= \frac{300mH}{1.5k\Omega}$$


$$= 200\mu s \quad [+1]$$

$$V_L(t) = V_L(\infty) + (V_L(0+) - V_L(\infty)) \exp(-t/\tau) \quad [+1]$$

$$= 90V \exp(-t/200\mu s) \quad [+1]$$

$$t > 0$$

c) Find R_{th} in terms of α :

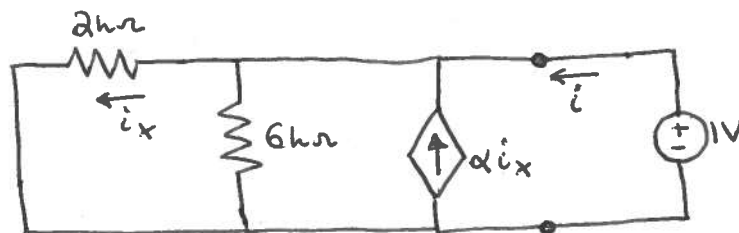

$$0 = \frac{1V}{2k\Omega} + \frac{1V}{6k\Omega} - \alpha i_x - i$$

$$i_x = \frac{1V}{2k\Omega} = 0.5mA$$

$$i = 1V \cdot \left(\frac{1}{2k\Omega} + \frac{1}{6k\Omega} - \frac{\alpha}{2k\Omega} \right)$$


$$R_{th} = \frac{1V}{i} = -3k\Omega \quad [+1] \quad \left(\text{or } R_{th} = \frac{V_{oc}}{i_{sc}} = -3k\Omega \quad [+1] \right)$$

$$\frac{1V}{1V \cdot \left(\frac{1}{2k\Omega} + \frac{1}{6k\Omega} - \frac{\alpha}{2k\Omega} \right)} = -3k\Omega$$

$$\alpha = 2 \quad [+1]$$

d)

$t = 0^+$

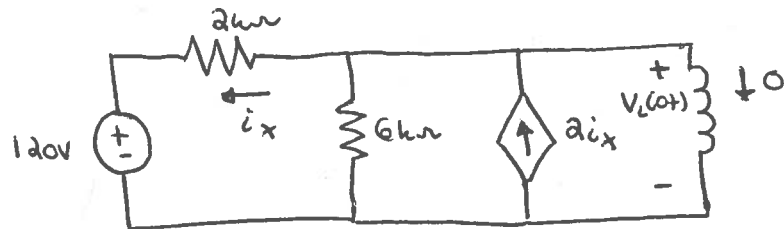

$$0 = \underbrace{\frac{v_L(0^+) - 120V}{2k\Omega}}_{i_x} + \frac{v_L(0^+)}{6k\Omega} - 2 \cdot \left(\frac{v_L(0^+) - 120V}{2k\Omega} \right) + 0$$

$$v_L(0^+) = \frac{120V / 2k\Omega}{1/2k\Omega - 1/6k\Omega} = 180V$$

$t \rightarrow \infty$ dc steady state would be reached, $v_L(\infty) = 0V$

$$\tau = \frac{L}{R_{th}} = \frac{300mH}{-3k\Omega} = -100\mu s$$

$$\begin{aligned} v_L(t) &= v_L(\infty) + (v_L(0^+) - v_L(\infty)) \exp(-t/\tau) \\ &= 180V \exp(t/100\mu s) \quad [+1] \end{aligned}$$

$$36 \text{ kV} = 180 \text{ V} \exp(t/100 \mu\text{s})$$

$$t = 100 \mu\text{s} \cdot \ln\left(\frac{36000}{180}\right)$$

$$= 530 \mu\text{s} \quad [+1]$$