

ECSE-200 Electric Circuits 1
Quiz #4 (Feb. 8, 2019)

LAST NAME SOLUTIONS

MCGILL ID# _____

FIRST NAME _____


SIGNATURE _____

- Only Faculty standard calculator accepted
- No cellphone allowed
- Show all your work

- Clearly indicate your final answer with SI units and SI multiplier
- You have 45 minutes to complete this quiz

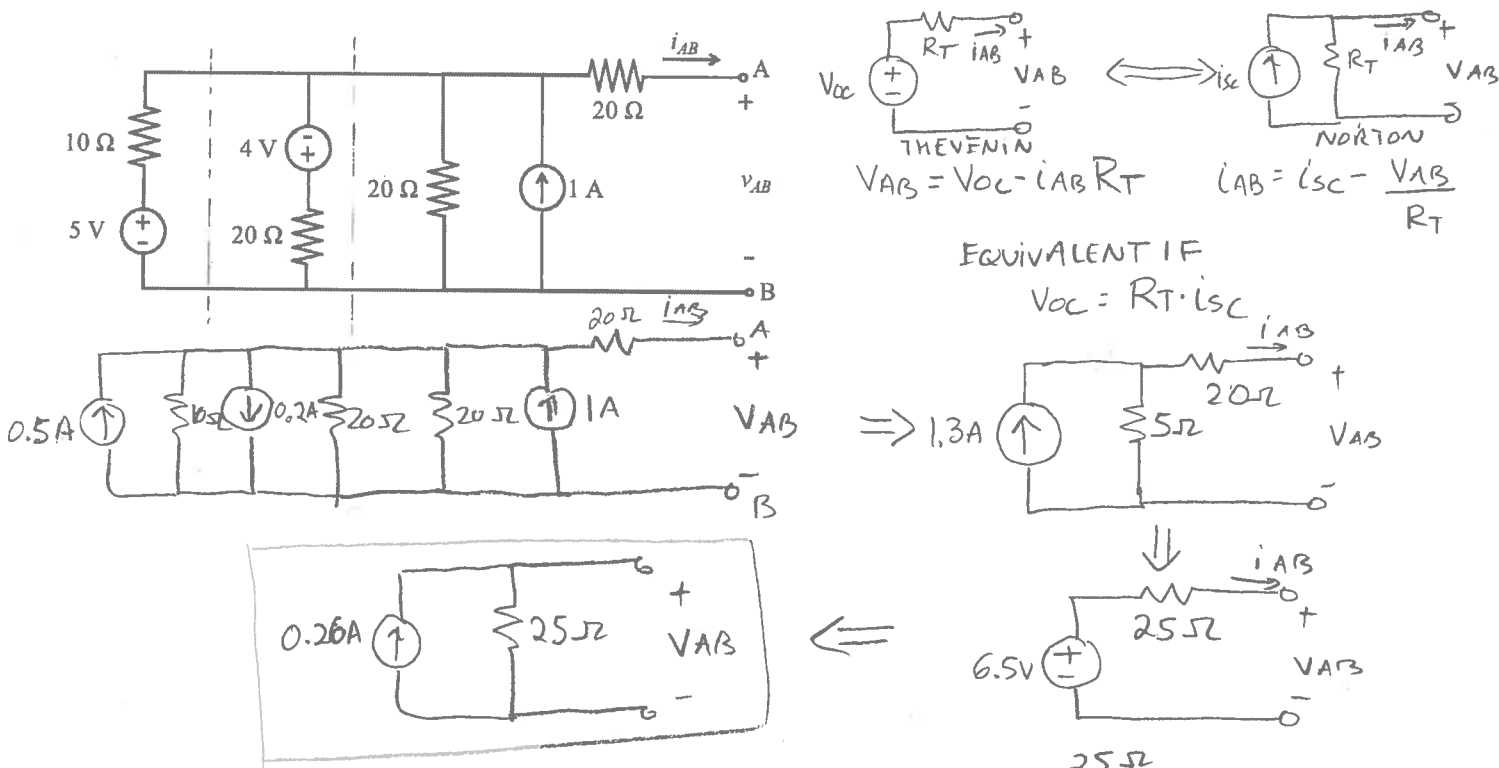Question 1. Consider the circuit shown below. Answer the following questions.

- Using source transformation, simplify the circuit at terminals AB into its Norton's circuit equivalent. [3 pt]
- What resistance value should a load resistor connected across terminals AB have for the voltage v_{AB} to be 5 V? [2 pt]
- If the circuit is loaded with an element connected across terminals AB that has infinite conductance ($G \rightarrow \infty$), what is the power dissipated by the Thévenin resistor in your Norton's circuit equivalent? [1 pt]



b) Use thevenin form + voltage division

$$V_{AB} = 6.5V \cdot \frac{R_L}{R_L + 25\Omega} = 5V$$

$$R_L + 25\Omega \rightarrow R_L - \frac{5}{6.5} R_L = \frac{5 \cdot 25}{6.5}$$

$$R_L = 83 \frac{1}{3} \Omega$$



c) $G = \frac{1}{R} = \infty$ $R_L = 0 \rightarrow$ short-circuit

no current flows in the thevenin resistor of the Norton's circuit

Page 1 of 4 (double-sided)

$$P_{WR} = 0W$$

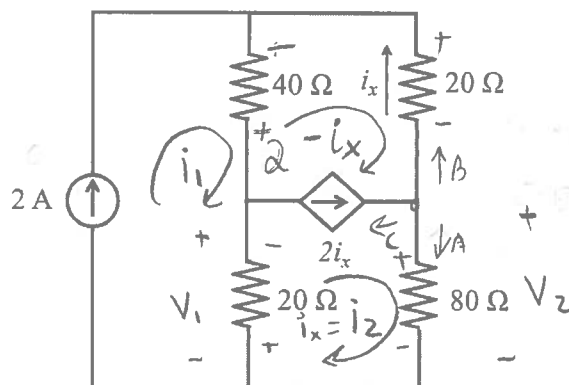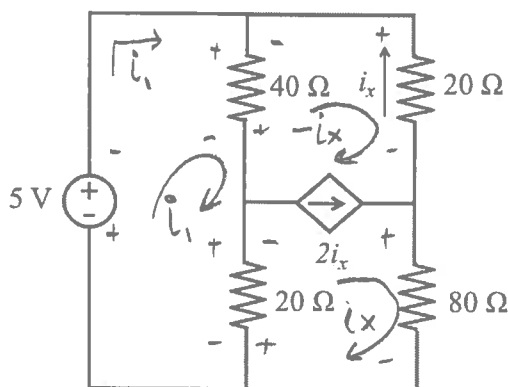Question 2. Consider the two circuits shown. Answer the following questions.




- If you are solving for the circuit variables in the **left** circuit, which circuit method requires fewer equations, the node voltage method or the mesh current method? Justify your answer. [1 pt]
- If you are solving for the circuit variables in the **right** circuit, which circuit method requires fewer equations, the node voltage method or the mesh current method? Justify your answer. [1 pt]
- What is the power dissipated by the dependent current source in the **right** circuit? [3 pt]
- What is the power dissipated by the independent voltage source in the **left** circuit? [3 pt]

a) 2 nodes ; one mesh + one super-mesh
both method requires same number of equations

b) 3 nodes ; one mesh + one super-mesh
the mesh current method should be used.

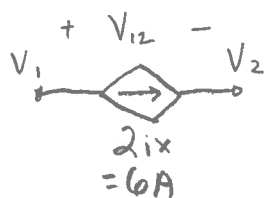c) current in top mesh of the super mesh $i_1 + i_2 + i_3 = 0$
 $i_2 + i_x - 2i_x = 0$
 $i_2 = i_x$
 KVL on super-mesh
 $40(-i_x - i_1) + 20(-i_x) + 80(i_x) + 20(i_x - i_1)$
 $-40i_x - 80 - 20i_x + 80i_x + 20i_x - 40 = 0$
 $40i_x = 120 \quad i_x = 3A = i_2$
 From the other mesh
 $i_1 = 2A$



$$\left. \begin{aligned} V_1 &= 20\Omega(i_1 - i_2) = 20\Omega(2 - 3) = -20V \\ V_2 &= 80\Omega \cdot i_2 = 240V \\ V_{12} &= V_1 - V_2 = -20V - 240V = -260V \end{aligned} \right\} \begin{aligned} P &= (6A)(-260V) \\ P &= -1.56kW \\ &\text{dissipated} \end{aligned}$$

d) To Find i_1 using mesh analysis

KVL on super-mesh

$$\begin{aligned}40(-i_x - i_1) + 20(-i_x) + 80(i_x) + 20(i_x - i_1) &= 0 \\-40i_x - 40i_1 - 20i_x + 80i_x + 20i_x - 20i_1 &= 0 \\40i_x &= 60i_1 \quad i_x = \frac{3}{2}i_1\end{aligned}$$

KVL on other mesh

$$\begin{aligned}-5 + 40(i_1 - (-i_x)) + 20(i_1 - i_x) &= 0 \\-5 + 40i_1 + 40i_x + 20i_1 - 20i_x &= 0 \\-5 + 40i_1 + 60i_1 + 20i_1 - 30i_1 &= 0 \\90i_1 &= 5 \quad i_1 = \frac{5}{90} \text{ A}\end{aligned}$$

$$P = \left(\frac{5}{90} \text{ A}\right)(5 \text{ V}) = 277.8 \text{ mW}$$

+ 277.8 mW delivered

- 277.8 mW dissipated/absorbed.