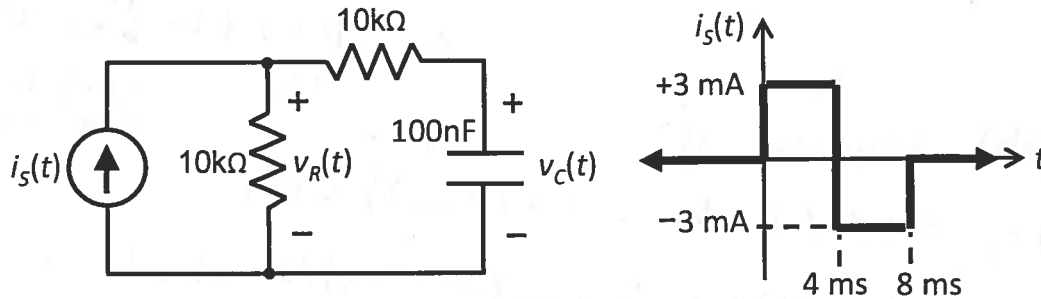


NAME _____ McGill ID# _____

READ each question carefully. Do your work independently. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

Consider the circuit diagram and the plot of current $i_S(t)$ versus time t . The circuit is in dc steady-state for $t < 0$. Answer the questions.



- 1) Express the input $i_S(t)$ shown in the figure above in terms of the unit step function $u(t)$. [3pts]
- 2) What is the voltage $v_C(t)$ in response to the input $i_S(t) = 1\text{ A } u(t)$? [2pts]
- 3) What is the voltage $v_C(t)$ in response to the input $i_S(t)$ as shown in the figure above? [3pts]
- 4) What is the voltage $v_R(t)$ in response to the input $i_S(t)$ as shown in the figure above? [2pts]

$$1) i_S(t) = 3\text{ mA} \cdot u(t) - 6\text{ mA} u(t-4\text{ ms}) + 3\text{ mA} u(t-8\text{ ms})$$

[+1] [+1] [+1]

2) initial condition: $v_C(0+) = v_C(0-) = 0\text{ V}$

final condition:

$v_C(\infty) = 1\text{ A} \cdot 10\text{ k}\Omega = 10\text{ kV}$


time constant:

$\tau = R_T C = 20\text{ k}\Omega \cdot 100\text{ nF} = 2\text{ ms}$ [+1]



$$v_C(t) = 10\text{ kV} (1 - \exp(-t/2\text{ ms})) u(t) \quad [+1]$$

$$3) v_C(t) = 30\text{ V} (1 - \exp(-t/2\text{ ms})) u(t) \\ + (-60\text{ V}) (1 - \exp(-(t-4\text{ ms})/2\text{ ms})) u(t-4\text{ ms}) \\ + 30\text{ V} (1 - \exp(-(t-8\text{ ms})/2\text{ ms})) u(t-8\text{ ms})$$

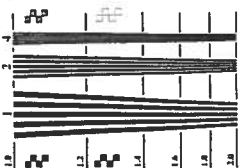[+1 for correct amplitudes]
 [+1 for correct delays]
 [+1 for correct functional form]



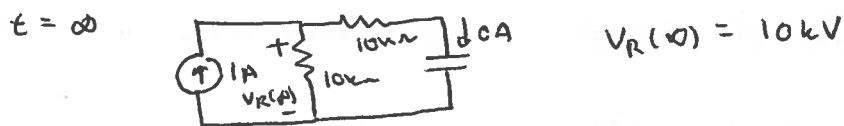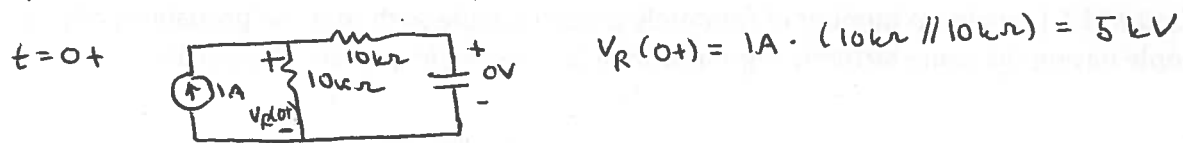4) Find unit step response, $i_s = 1A u(t)$



$\tau = 2ms$ \therefore unit response $V_R(t) = (10kV - 5kV \exp(-t/2ms)) u(t)$
 $= 10kV (1 - \frac{1}{2} \exp(-t/2ms)) u(t)$
 [+1 for correct form of step response]

The total response is:

$$V_R(t) = 30V (1 - \frac{1}{2} \exp(-t/2ms)) u(t) \\ + (-60V) (1 - \frac{1}{2} \exp(-(t-4ms)/2ms)) u(t-4ms) \\ + 30V (1 - \frac{1}{2} \exp(-(t-8ms)/2ms)) u(t-8ms)$$

[+1]