


Today's Outline

5. Operational Amplifiers

- Op-Amp Circuits
- Practical Op-Amp Model
- Negative Feedback (revisited)


Example 8

Assuming ideal op-amp behaviour, what is the relationship between the output v_o and the inputs v_A and v_B ?

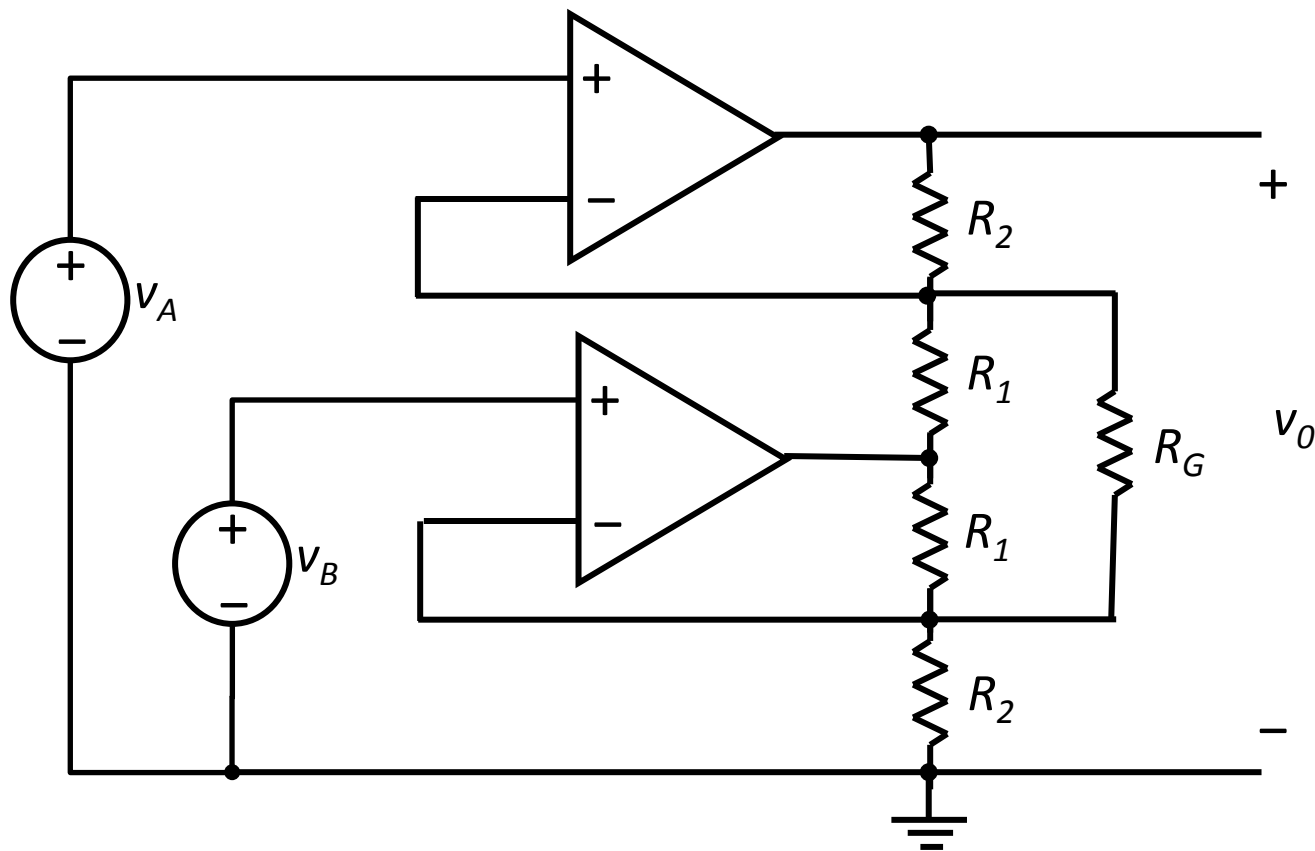


Example 8

Apply ideal op-amp equations.

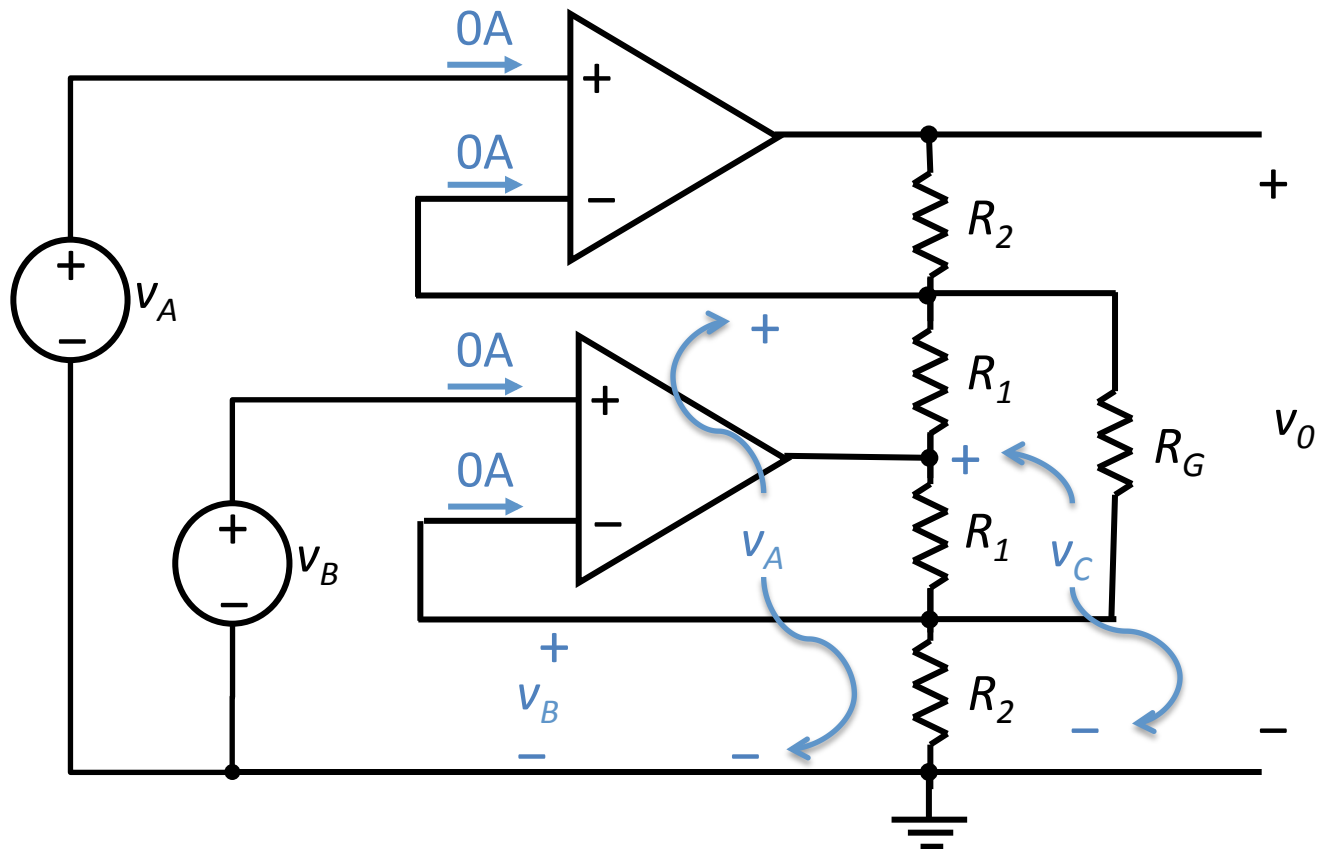

Example 8

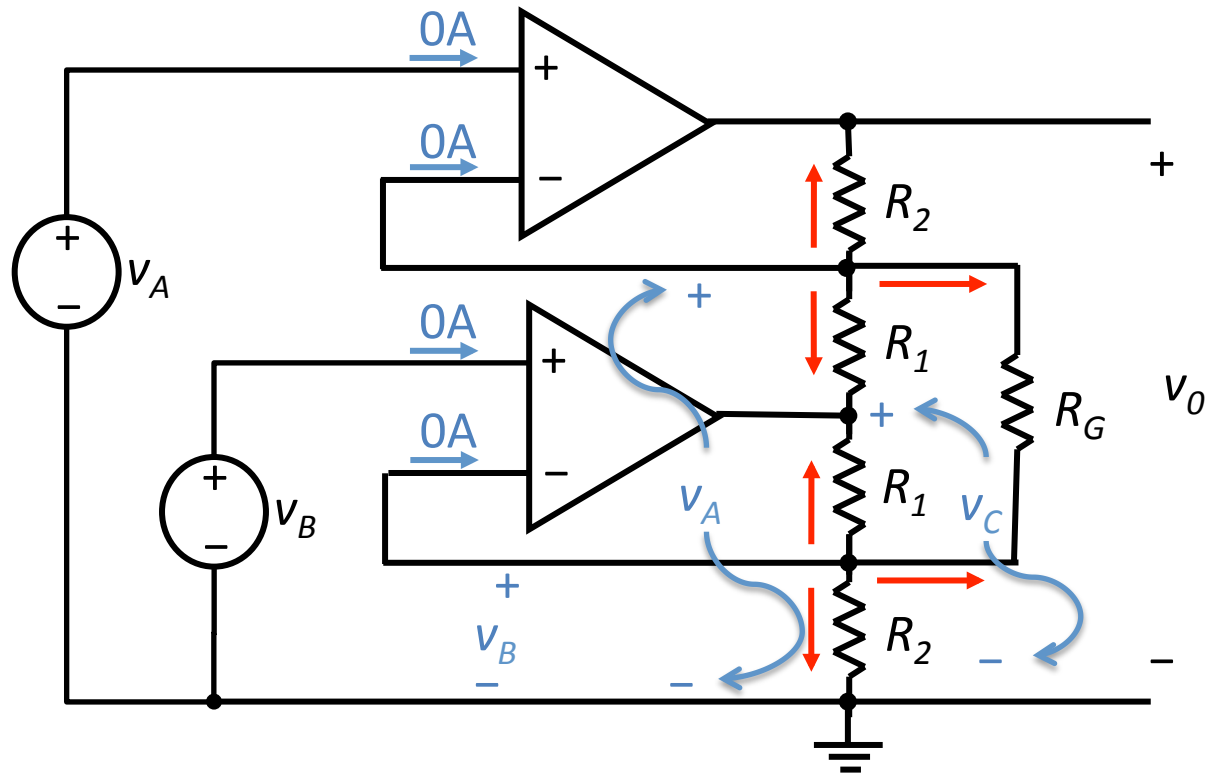


Write out node-voltage equations:

$$\text{B: } 0 = \frac{v_B}{R_2} + \frac{v_B - v_A}{R_G} + \frac{v_B - v_C}{R_1} \quad \rightarrow \quad v_C = R_1 \left(\frac{v_B}{R_2} + \frac{v_B - v_A}{R_G} + \frac{v_B}{R_1} \right)$$

$$\text{A: } 0 = \frac{v_A - v_0}{R_2} + \frac{v_A - v_B}{R_G} + \frac{v_A - v_C}{R_1} \quad \rightarrow \quad v_0 = R_2 \left(\frac{v_A}{R_2} + \frac{v_A - v_B}{R_G} + \frac{v_A - v_C}{R_1} \right)$$

Example 8

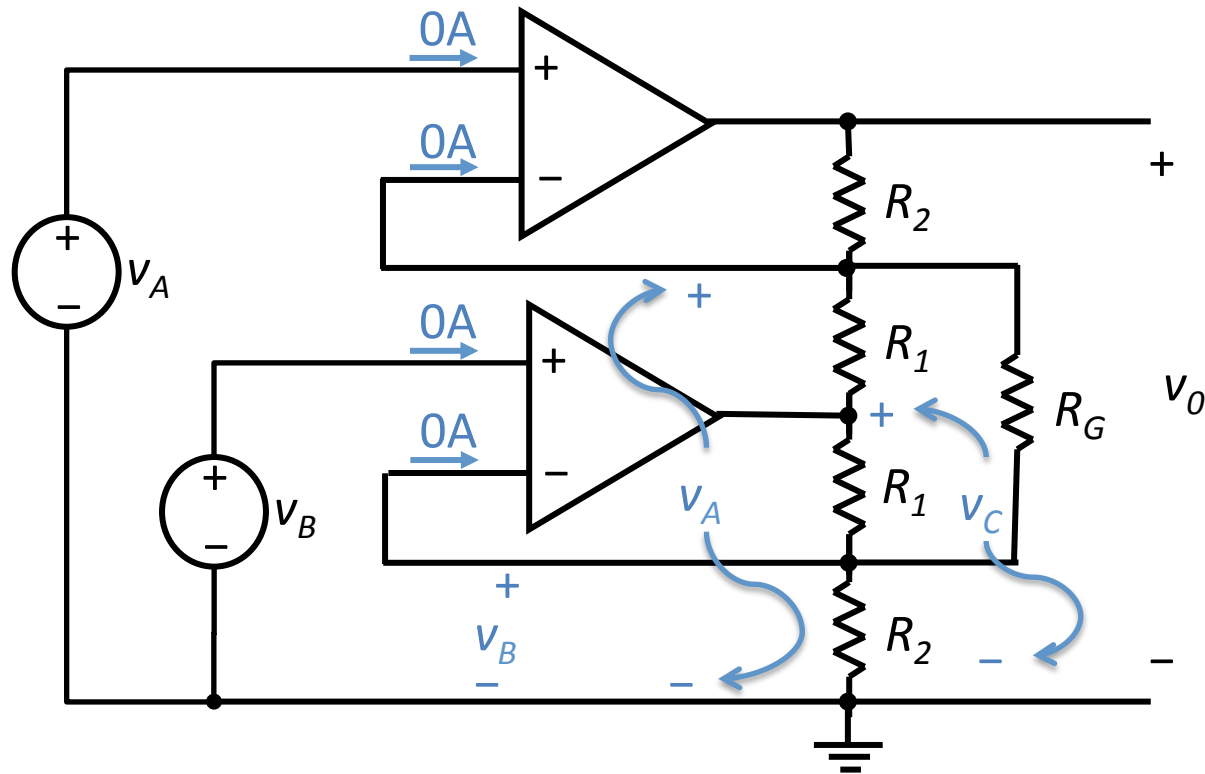


Substitution gives:

$$v_0 = (v_A - v_B) \left(1 + \frac{R_2}{R_1} + 2 \frac{R_2}{R_G} \right)$$

This circuit is a ***precision differential voltage amplifier***, with the output being proportional to the difference in input voltages.

Application: Electrocardiography

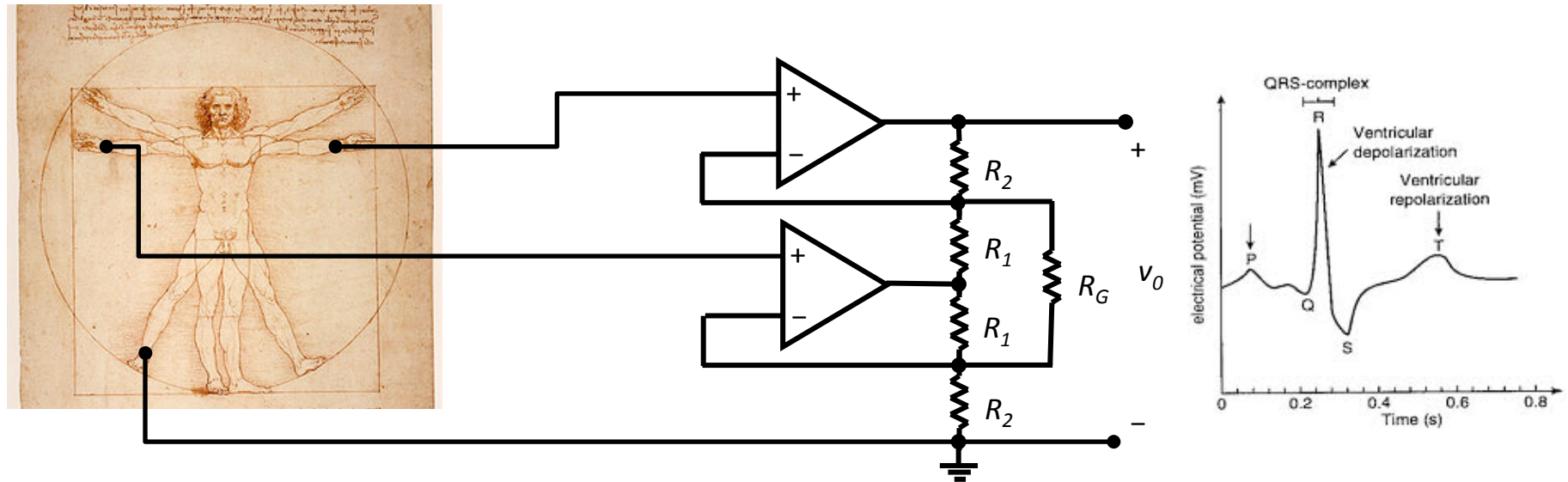


A simplified electrocardiogram (ECG or EKG) setup.

The heart generates an electric potential (voltage) across the arms, which can be measured and used to diagnose disorders. There are many other electrode configurations possible.



Willem Einthoven
1860-1927

Application: Electrocardiography

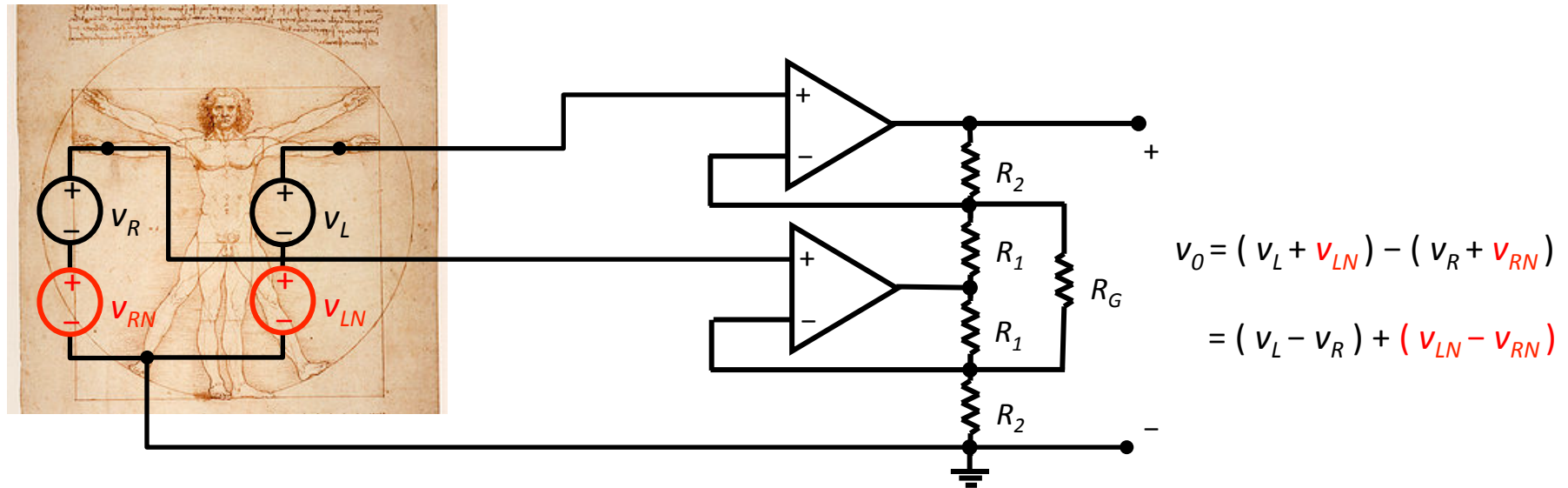

v_L = left arm signal
 v_{LN} = left arm noise


v_R = right arm signal
 v_{RN} = right arm noise

The output v_O includes a differential signal $v_L - v_R$.

The output v_O also includes the **differential noise** $v_{LN} - v_{RN}$. The average noise that is common to both electrodes $\frac{1}{2}(v_{LN} + v_{RN})$, called **common mode noise**, is rejected by the differential amplifier.


Example 9

Assume the circuit element D terminal variables follow the relationship $v_D = F(i_D)$. How is v_{out} related to v_{in} ?

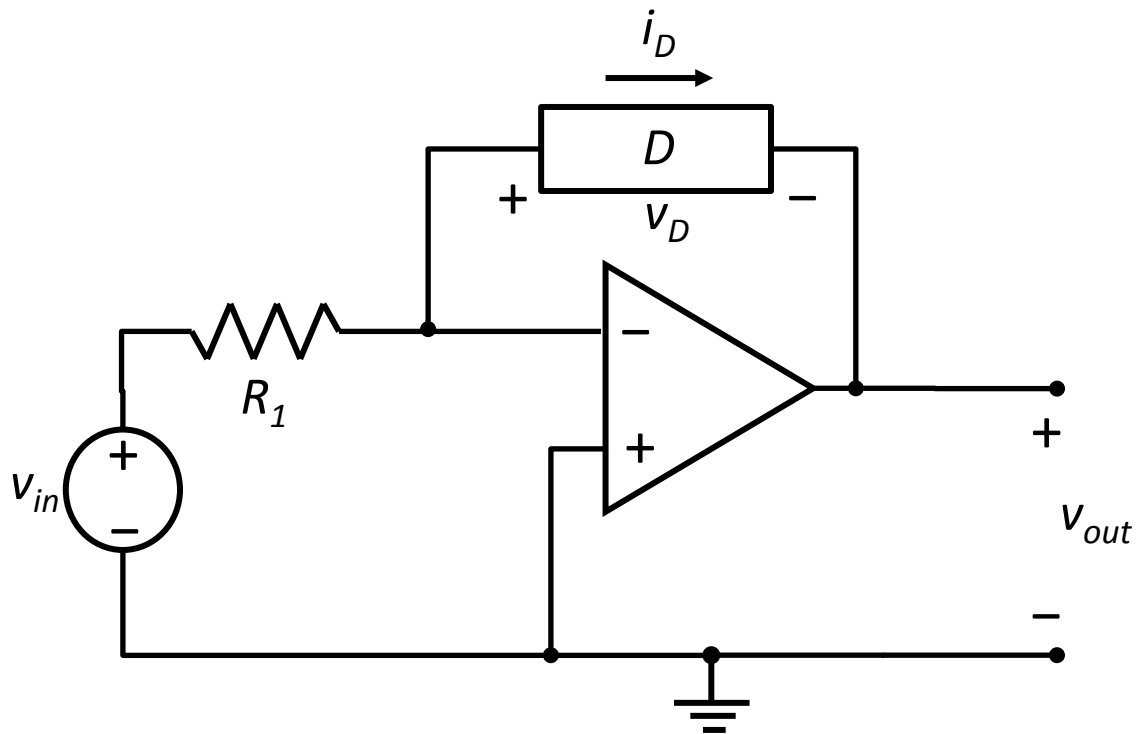

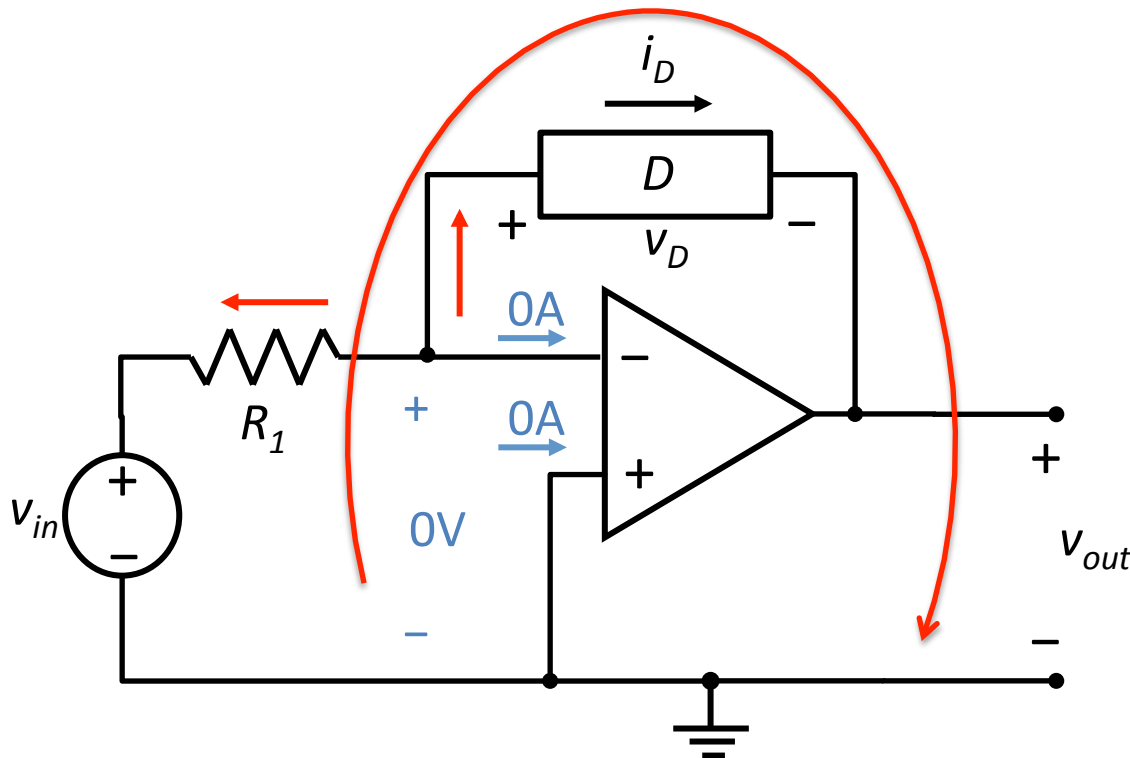Example 9

Apply ideal op-amp equations, write out node equation and KVL equation.



$$\text{node: } 0 = \frac{0 - v_{in}}{R_1} + i_D$$

$$i_D = \frac{v_{in}}{R_1}$$

$$v_D = F(i_D) = F\left(\frac{v_{in}}{R_1}\right)$$

$$\text{KVL: } 0 = v_D + v_{out}$$


$$v_{out} = -F\left(\frac{v_{in}}{R_1}\right)$$

This configuration can be very useful. If D is a **diode**, then the circuit can take logarithms:

$$i_D \approx 1\text{nA} \cdot \exp(v_D / 26\text{mV}) \rightarrow v_D \approx 26\text{mV} \cdot \ln\left[\frac{i_D}{1\text{nA}}\right] \rightarrow v_{out} = -26\text{mV} \cdot \ln\left[\frac{v_{in}}{1\text{nA} \cdot R_1}\right]$$


Example 10

Assume the circuit element D terminal variables follow the relationship $i_D = G(v_D)$. How is v_{out} related to v_{in} ?

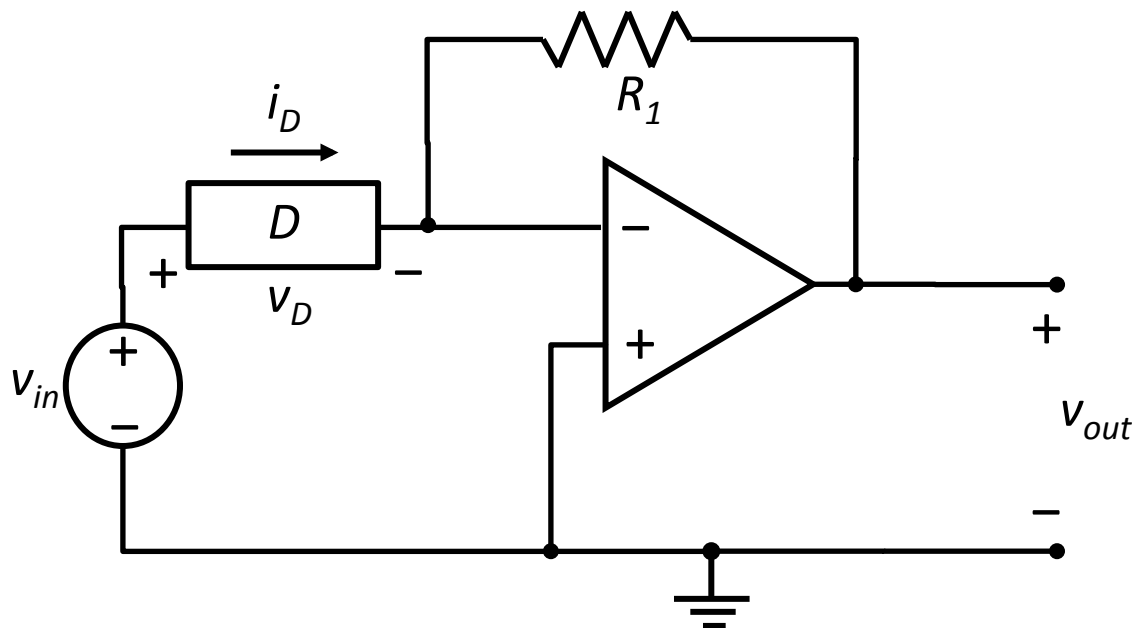

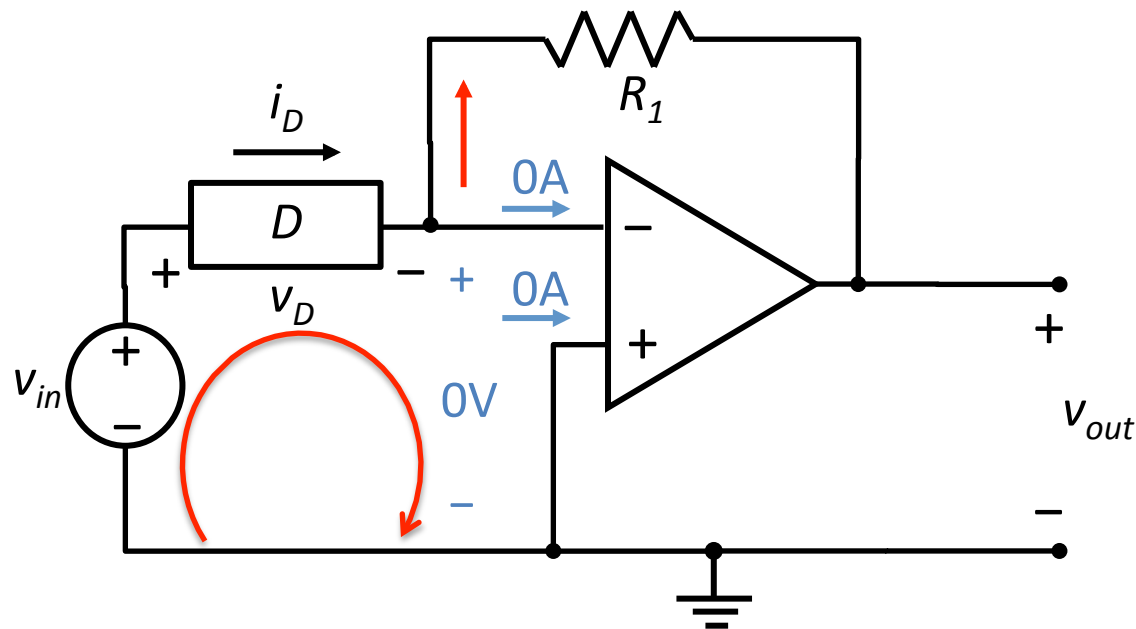Example 10

Apply ideal op-amp equations, write out KVL equation and node equation.



$$\text{KVL: } 0 = -v_{in} + v_D$$

$$v_D = v_{in}$$

$$\text{node: } 0 = -i_D + \frac{0 - v_{out}}{R_1}$$

$$v_{out} = -R_1 i_D$$


$$v_{out} = -R_1 G(v_{in})$$

This configuration can be very useful. If D is a **diode**, then the circuit can take exponentials:

$$i_D \approx 1\text{nA} \cdot \exp(v_D / 26\text{mV}) \rightarrow v_{out} = -R_1 \cdot 1\text{nA} \cdot \exp(v_D / 26\text{mV})$$

“Practical” Op-Amp Model

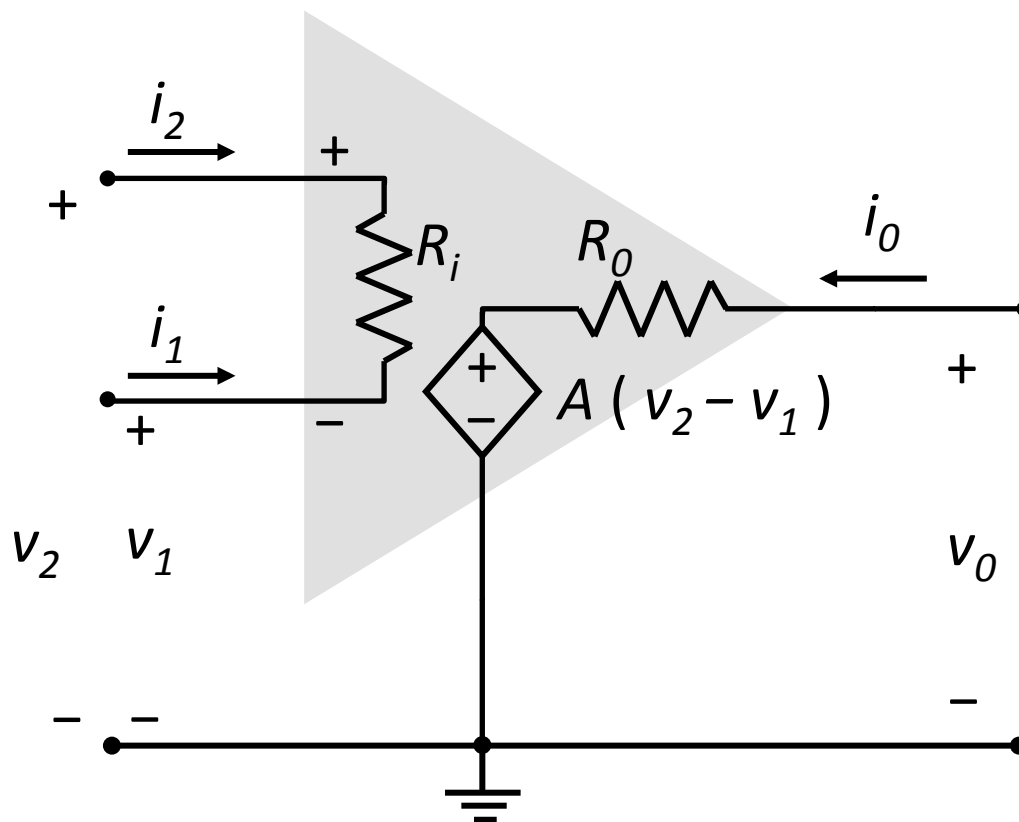Practical Op-Amp Circuit Model: A circuit model for the op-amp that consists of an **input resistance** R_i , an **output resistance** R_o , and an **open-loop gain** A .



Note:


- the voltage across the source is proportional to the difference $v_2 - v_1$
- the connection to the reference terminal is explicit
- the theorems of section 4 can be applied to op-amp circuits

“Practical” Op-Amp Model

Op-amp model values are often in the range:

- input resistance $R_i = 100\text{k}\Omega$ to $1\text{T}\Omega$ ($10^{12}\Omega$)
- output resistance $R_o = 1\Omega$ to 50Ω
- open loop gain $A = 10^5\text{V/V}$ to 10^7V/V


this suggests a simpler model...

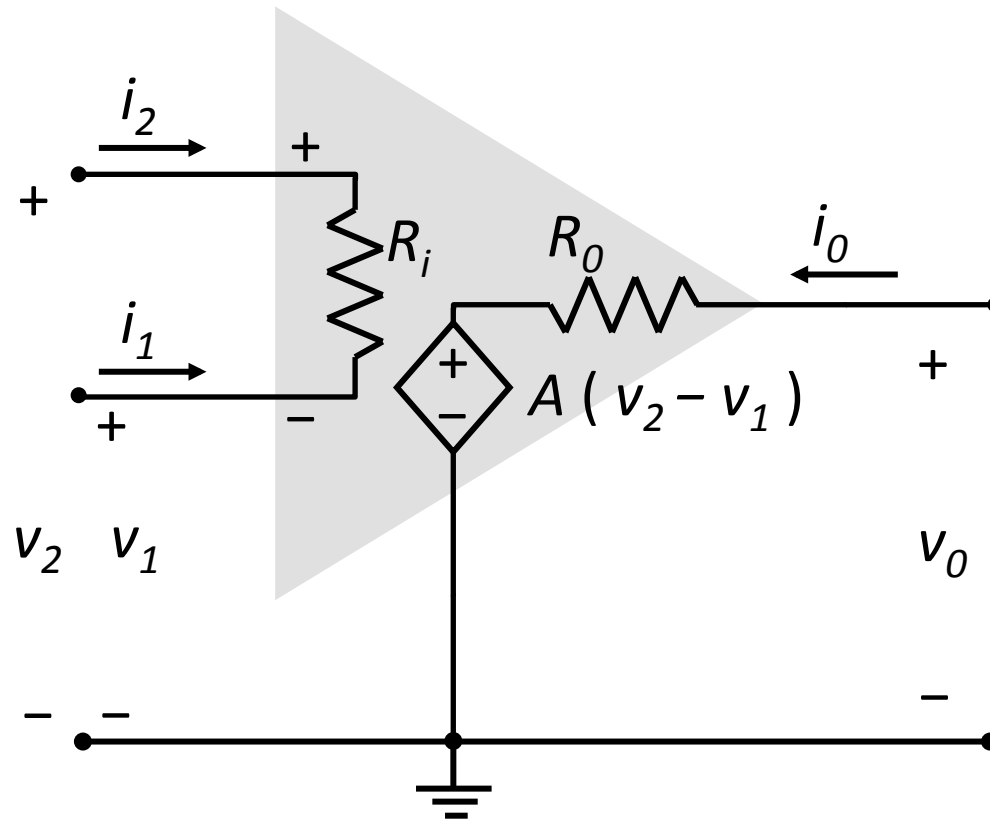

Finite Gain Op-Amp Model


A simpler circuit model arises in the limit:

$$R_i \rightarrow \infty$$
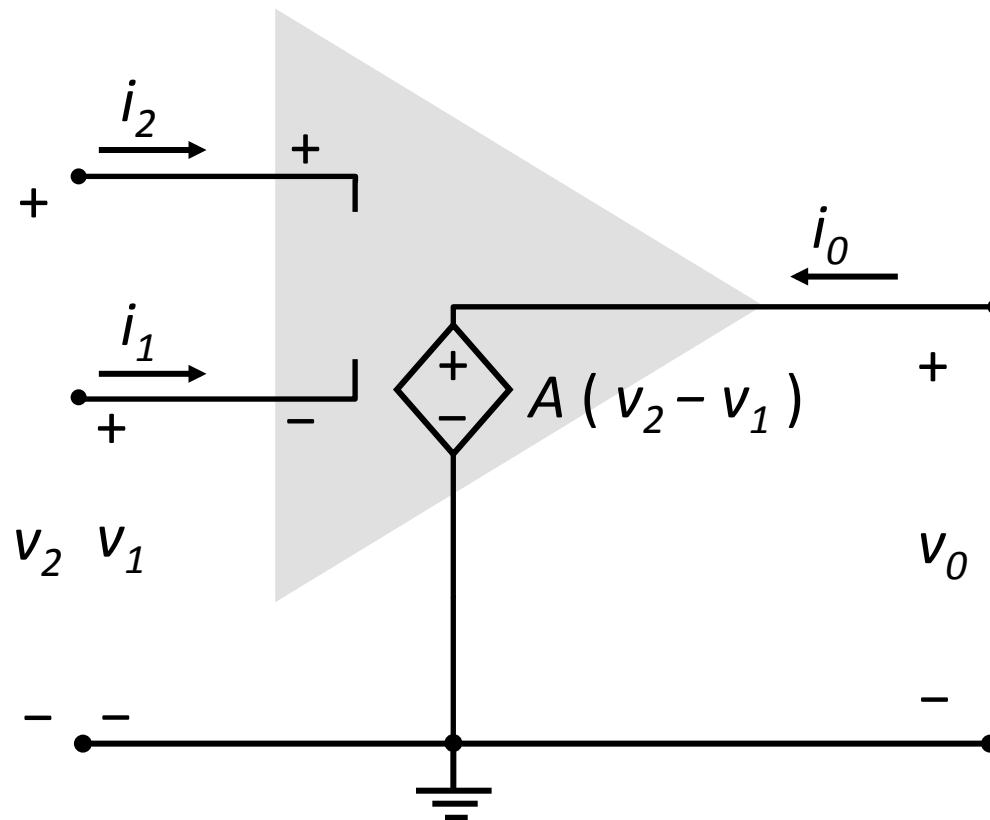
$$R_o \rightarrow 0$$

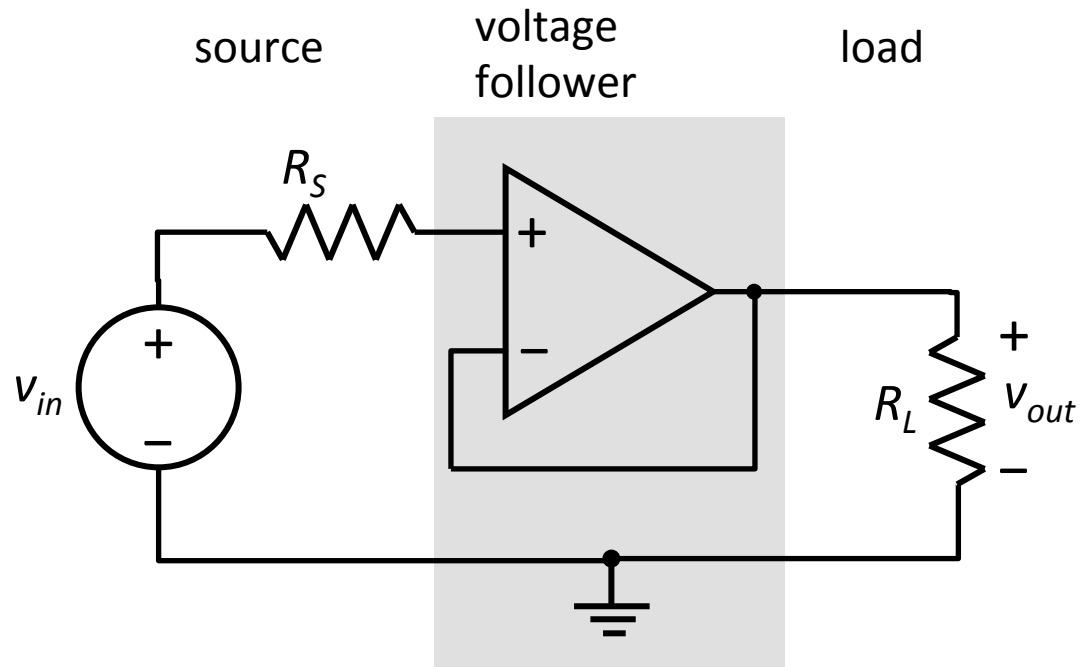
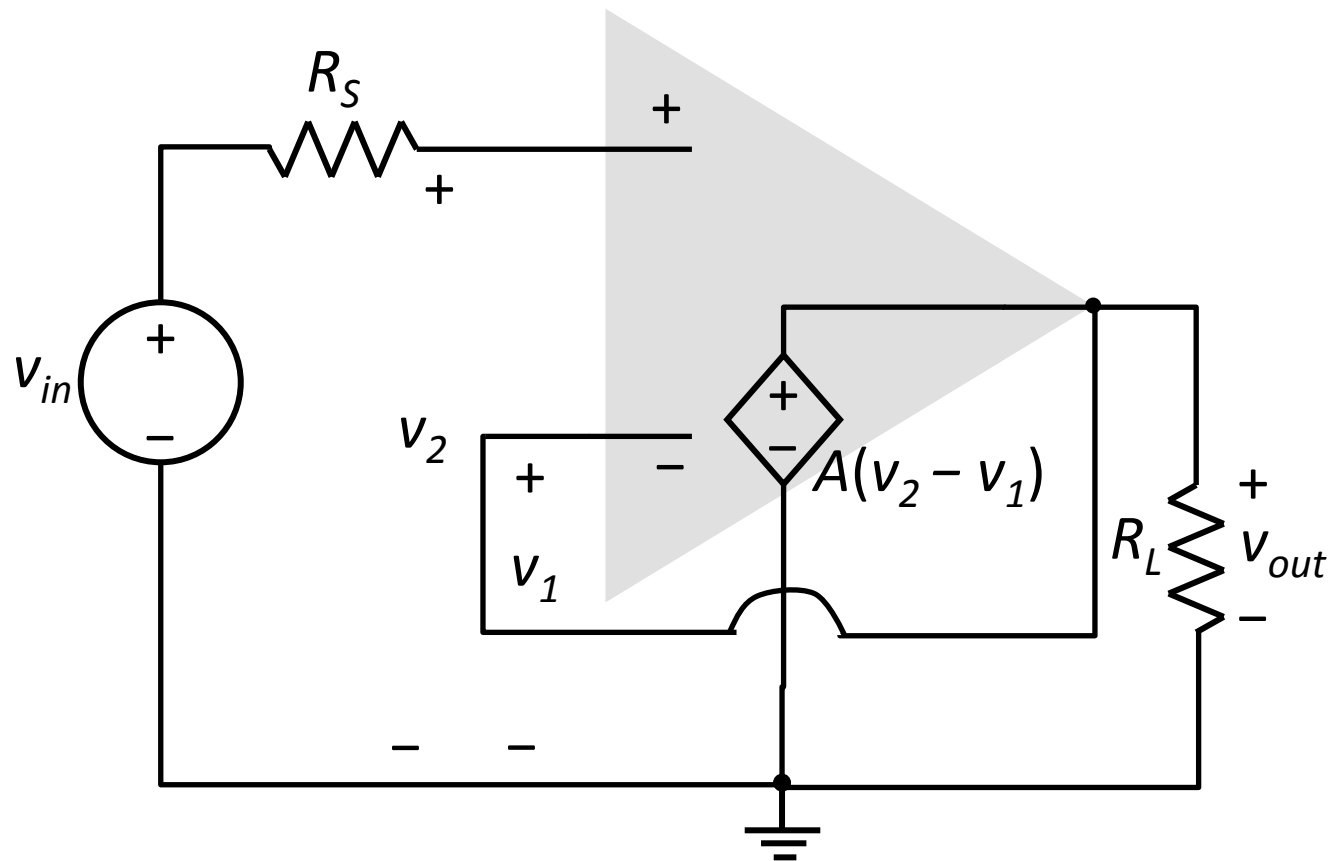
Example

Find the ratio v_{out} / v_{in} , assuming a finite gain op-amp model.



Example

Replace the op-amp with the finite gain model.




Example

Redraw the circuit. KVL gives: $0 = -v_{in} + 0 \times R_S + v_2$ thus: $v_2 = v_{in}$

$$v_{out} = v_1 = A(v_2 - v_1) \quad \text{thus: } v_1(A+1) = Av_2$$

$$v_1 = \frac{A}{A+1} v_2$$

$$v_{out} = \frac{A}{A+1} v_{in}$$

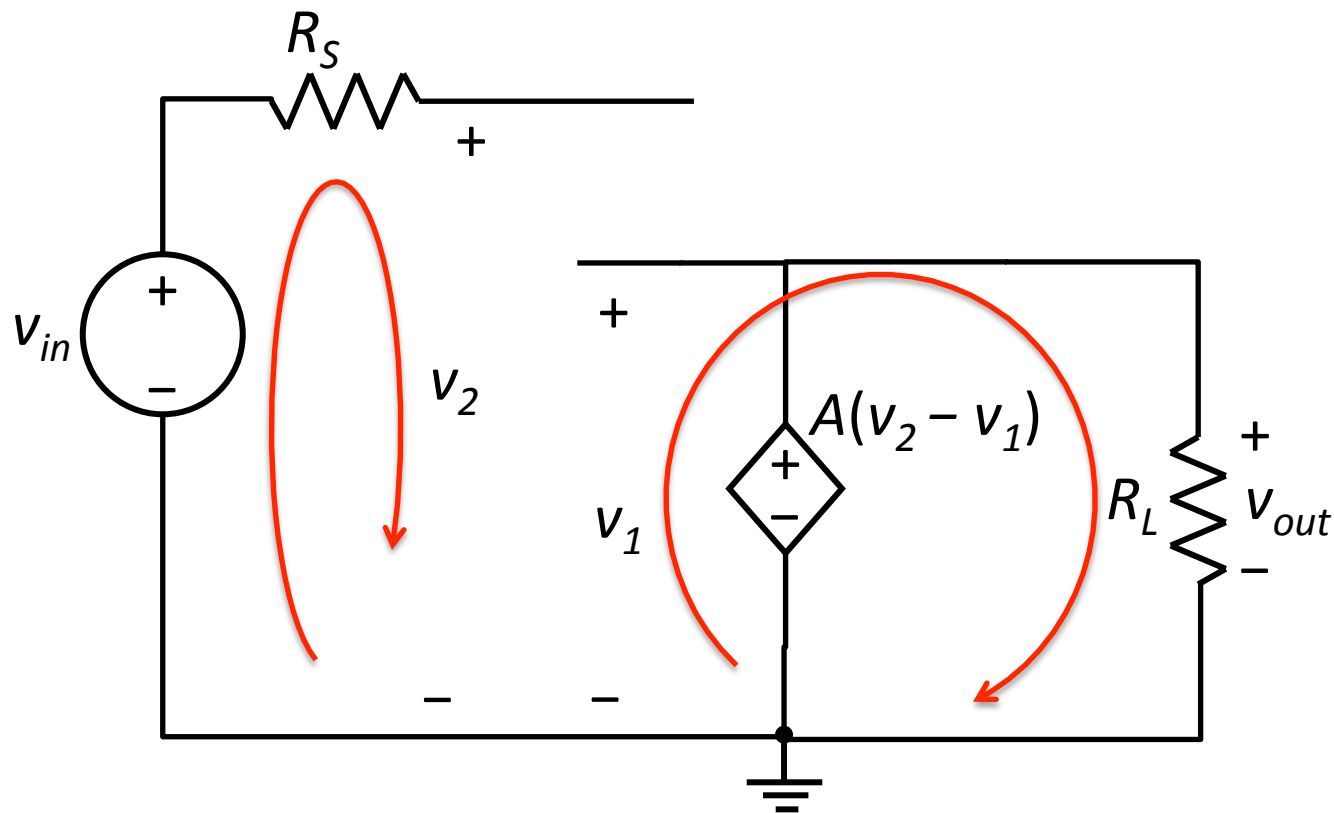


Example

For “small” open-loop gain A , the circuit output is explicitly dependent upon the value of A .



If $A \gg 1$, the circuit output becomes independent of the open-loop gain A , and behaves as predicted by the ideal op-amp model.

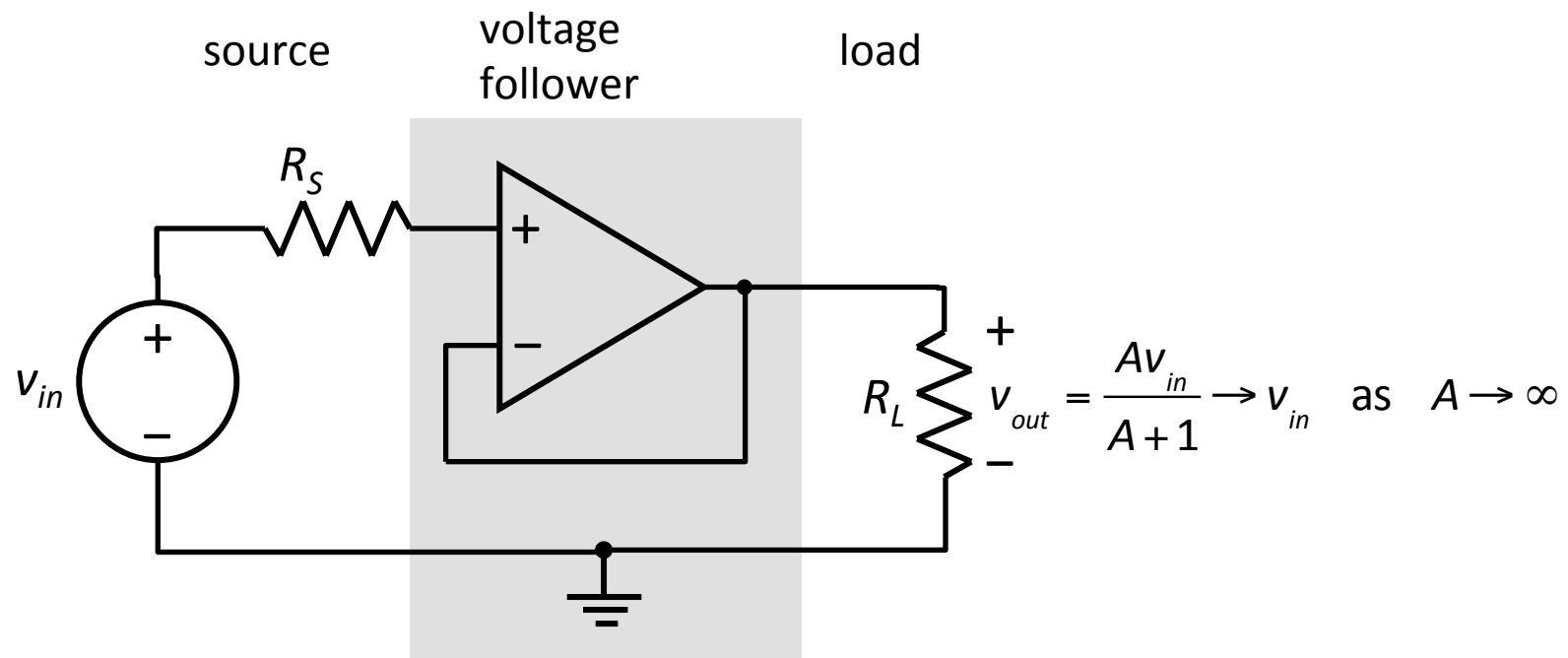Note: *So long as A is large enough, circuit behaviour is relatively insensitive to variation in A (due to temperature, age, manufacturer, unit to unit variability). This is one reason why we use op-amp circuits with a negative feedback loop.*



Negative Feedback

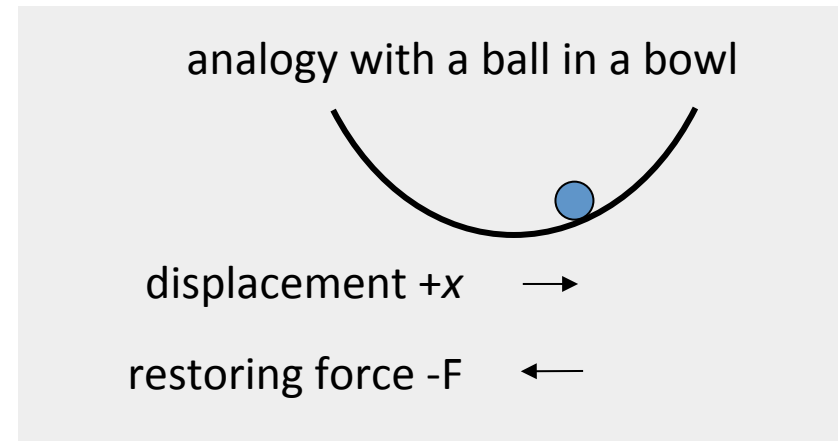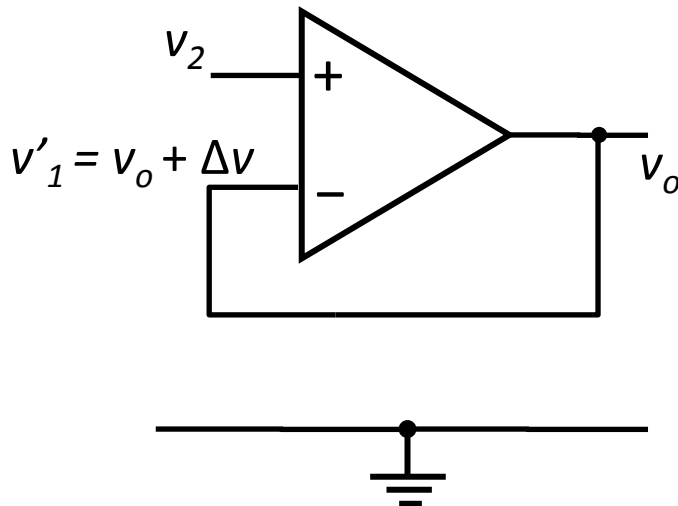The negative feedback loop is **stable** against output fluctuations.
Consider the voltage follower as an example:



“displacement” $v_1 \rightarrow v'_1 = v_0 + \Delta v$



“restoring force” $v_0 \rightarrow v'_0 = A[v_2 - v'_1] = A[v_2 - (v_1 + \Delta v)] = v_0 - A\Delta v$

$$v'_1 \rightarrow v''_1 = v'_1 - A\Delta v$$

A rigorous analysis is required for quantitative understanding of stability, but it is clear negative feedback suppresses fluctuations.

Positive Feedback

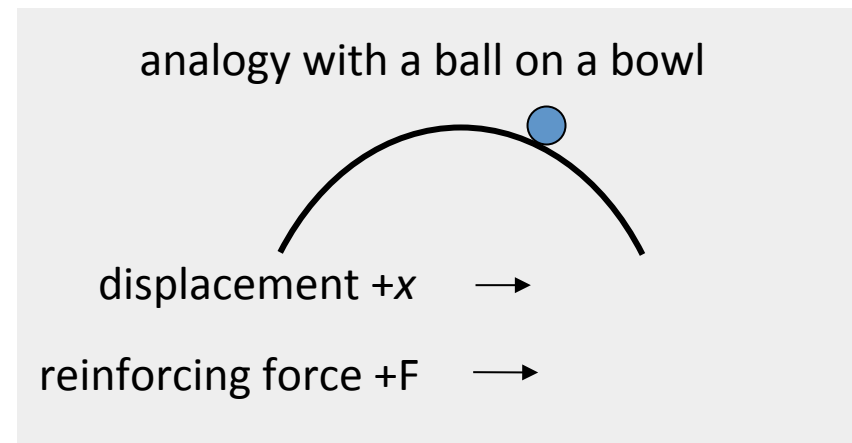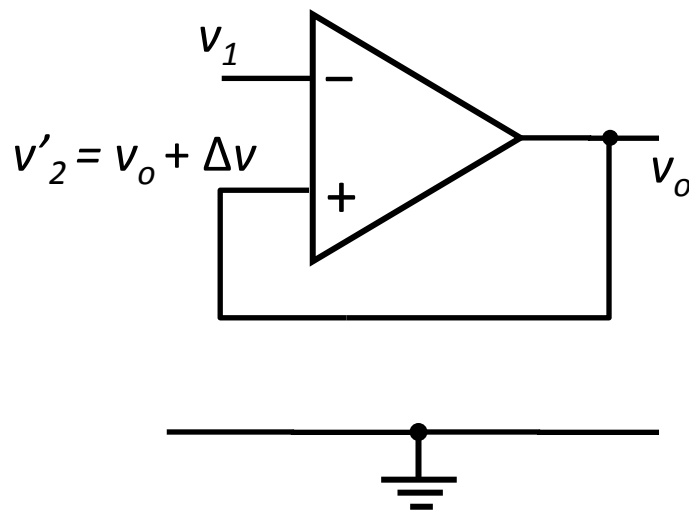In contrast, a **positive feedback loop** is **unstable** against output fluctuations (just like audio feedback into a microphone). The following circuit is unstable and difficult to control (*take careful note of input terminal labels!*)



“displacement” $v_2 \rightarrow v'_2 = v_0 + \Delta v$

“reinforcing force” $v_0 \rightarrow v'_0 = A[v'_2 - v_1] = A[(v_2 + \Delta v) - v_1] = v_0 + A\Delta v$

$$v'_2 \rightarrow v''_2 = v'_2 + A\Delta v$$

Section 5 Summary

Ideal Op-Amp Model: The open input and virtual short approximations give a simple pair of op-amp equations.

Negative Feedback: The connection of output to inverting input through a circuit element, which gives rise to stability and programmable function in an op-amp circuit.

Op-Amp Circuits: Programmed by external elements, op-amp circuits can perform a wide range of useful signal operations. Easily analyzed with node voltage analysis.

Practical Op-Amp Model: An op-amp model that incorporates finite open-loop gain, input resistance and output resistance.