



Electric Circuits 1  
ECSE-200 Section: 1, 2

8 Dec 2010, 9:00AM

Examiner: Thomas Szkopek


Assoc Examiner: Zeljko Zilic

Student Name:		McGill ID:											
---------------	--	------------	--	--	--	--	--	--	--	--	--	--	--


INSTRUCTIONS:

- This is a **CLOSED BOOK** examination.
- **NO CRIB SHEETS** are permitted.
- **SPACE IS PROVIDED** on the examination to answer all questions.
- **STANDARD CALCULATOR** permitted **ONLY**.
- This examination consists of 4 questions, with a total of 18 pages, including the cover page.
- This examination is **PRINTED ON BOTH SIDES** of the paper
- This examination paper **MUST BE RETURNED**

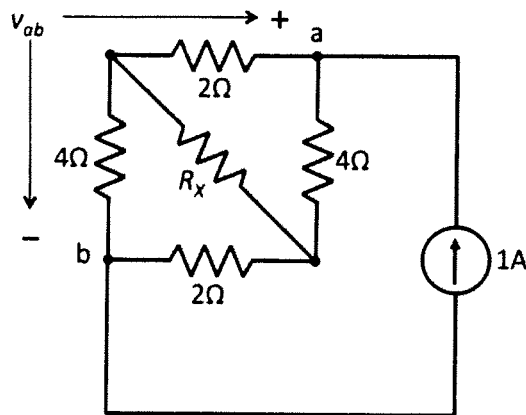1. Consider the circuit below. Answer the questions. [12 pts]



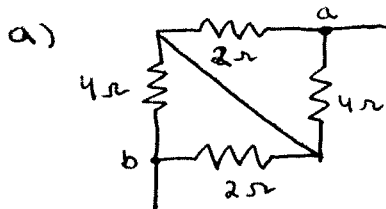
- What is the voltage  $v_{ab}$  if  $R_x = 0\Omega$ ? [2pts]
- What is the voltage  $v_{ab}$  if  $1/R_x = 0\Omega^{-1}$ ? [2pts]
- What is the voltage  $v_{ab}$  if  $R_x = 6\Omega$ ? [5pts]
- What should the value of  $R_x$  be in order to absorb the maximum power by  $R_x$  possible? [3pts]



$$R_{ab} = (2\Omega // 4\Omega) + (2\Omega // 4\Omega) \quad [+1]$$

$$= \frac{8}{3} \Omega$$

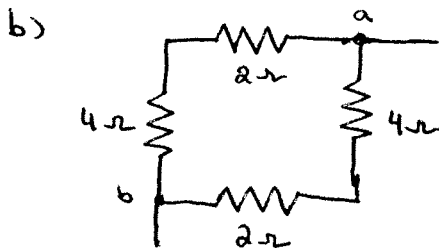
$$V_{ab} = 1A \cdot \frac{8}{3} \Omega = \frac{8}{3} V \quad [+1]$$



$$R_{ab} = (2\Omega + 4\Omega) // (2\Omega + 4\Omega) \quad [+1]$$

$$= 3\Omega$$
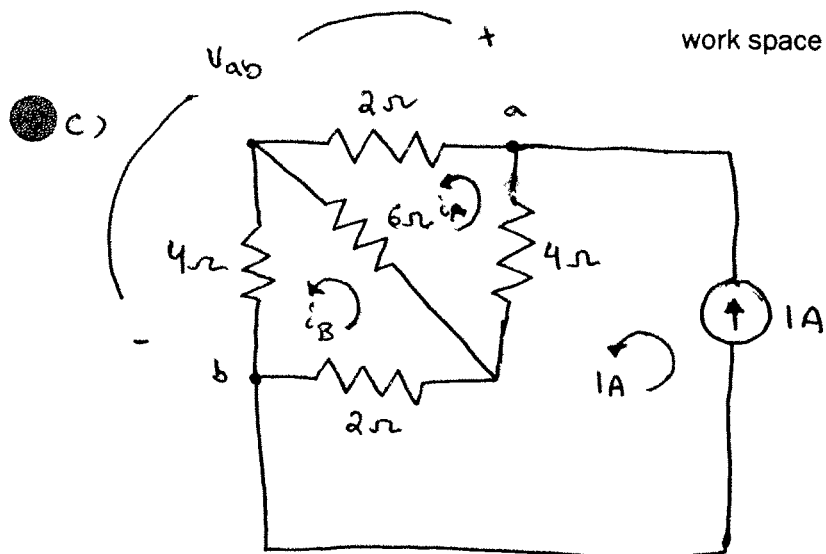
$$V_{ab} = 1A \cdot 3\Omega = 3V \quad [+1]$$



$$0 = 4\Omega (i_A - 1A) + 2\Omega i_A + 6\Omega (i_A - i_B) \quad [+1]$$

$$0 = 2\Omega (i_B - 1A) + 6\Omega (i_B - i_A) + 4\Omega i_B \quad [+1]$$

$$\begin{pmatrix} 4 \\ 2 \end{pmatrix} = \begin{pmatrix} 12 & -6 \\ -6 & 12 \end{pmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix}$$

$$i_A = \frac{\begin{vmatrix} 4 & -6 \\ 2 & 12 \end{vmatrix}}{\begin{vmatrix} 12 & -6 \\ -6 & 12 \end{vmatrix}} = \frac{5}{9} A \quad [+1/2]$$


$$i_B = \frac{\begin{vmatrix} 12 & 4 \\ -6 & 2 \end{vmatrix}}{\begin{vmatrix} 12 & -6 \\ -6 & 12 \end{vmatrix}} = \frac{4}{9} A \quad [+1/2]$$

$$V_{ab} = 2\Omega i_A + 4\Omega i_B \quad [+1]$$

$$= 2\Omega \cdot \frac{5}{9} A + 4\Omega \frac{4}{9} A$$

$$= 2 \frac{8}{9} V \quad [+1]$$

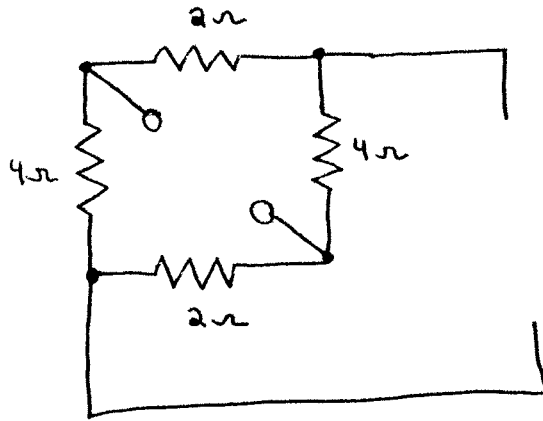d) Turn off sources, look at equivalent resistance:



[+1]


$$R_{TH} = R_{eq} = (2\Omega + 4\Omega) // (2\Omega + 4\Omega) \quad [+1]$$

$$= 3\Omega$$


Maximum power transfer theorem:  $R_L = R_{TH} = 3\Omega$  [+1]

work space

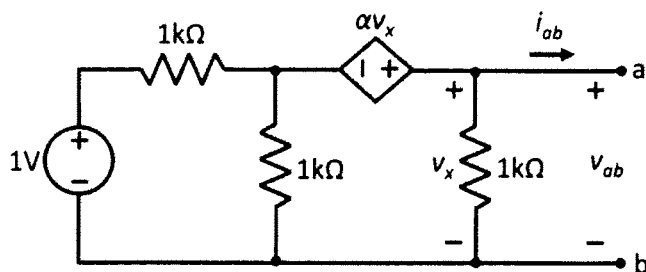2. Consider the circuit below. Answer the questions. [12 pts]



- What is the short circuit current  $i_{sc}$  at the terminals a and b? [3pts]
- If the open circuit voltage  $v_{oc}=0.5V$  at the terminals a and b, what is the value of  $\alpha$ ? [3pts]
- For the value of  $\alpha$  satisfying part b), what is the power delivered or absorbed by the dependent source under open circuit conditions? [3pts]
- Assume again that  $v_{oc}=0.5V$ . What is the maximum power that can be delivered to a load resistance attached to terminals a and b, under the restriction that  $v_{ab} \geq 0.4V$ ? [3pts]

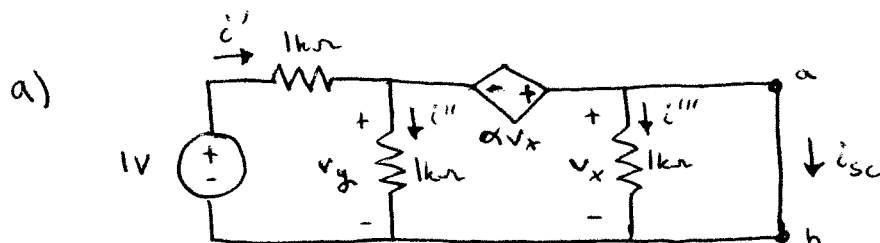

$$\text{KVL: } v_x = 0V \quad [+1]$$

$$\therefore \alpha v_x = 0V, \quad i''' = 0mA$$


$$\text{KVL: } 0 = -v_y - \alpha v_x + v_x$$

$$v_y = 0V, \quad i'' = 0mA$$

$$\text{KVL + Ohm: } i' = 1V / 1k\Omega = 1mA \quad [+1]$$

$$\text{KCL: } 0 = -i' + i'' + i''' + i_{sc}$$

$$i_{sc} = i' = 1mA \quad [+1]$$

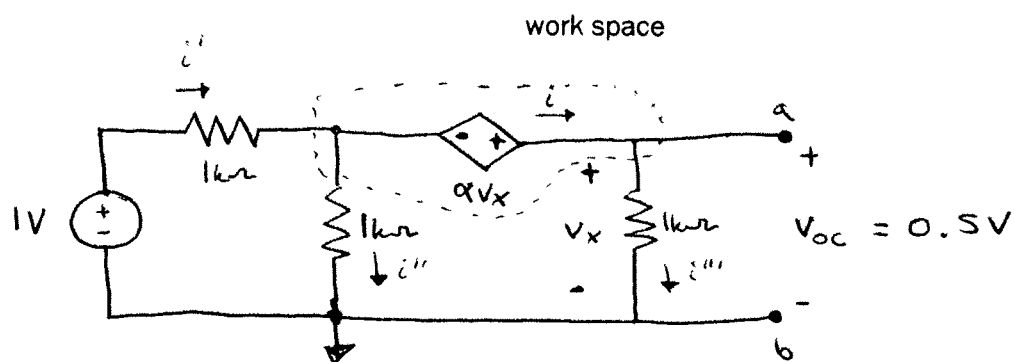

node equation:

$$\frac{V_x}{1k\Omega} + \frac{V_x - \alpha V_x}{1k\Omega} + \frac{(V_x - \alpha V_x) - 1V}{1k\Omega} = 0 \quad [+2]$$

$$(3 - 2\alpha) \frac{V_x}{1k\Omega} - \frac{1V}{1k\Omega} = 0$$

$$\alpha = \frac{3 - 1V/V_x}{2}$$

$$\alpha = \frac{3 - 1V/0.5V}{2}$$

$$\alpha = \frac{1}{2} \quad [+1]$$

c) Ohm:  $i''' = \frac{0.5V}{1k\Omega} = 0.5mA$


KCL:  $0 = -i + i'''$

$$i = i''' = 0.5mA \quad [+1]$$

Power delivered by source =  $(\alpha V_x) \cdot i \quad [+1]$

$$= (0.5 \cdot 0.5V) \cdot 0.5mA$$

$$= 125 \mu W \quad [+1]$$

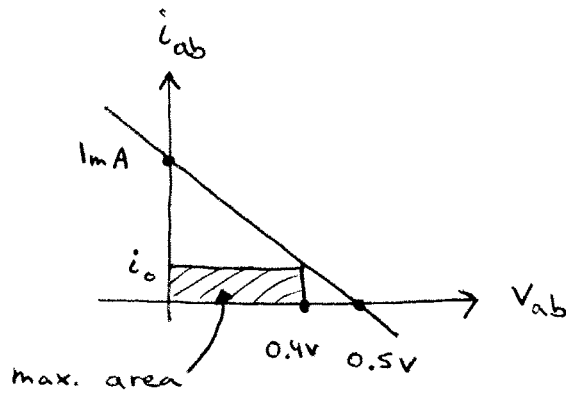

[+1] for diagram

By triangles:  $i_o = 1\text{mA} \cdot \frac{0.5\text{V} - 0.4\text{V}}{0.5\text{V}} = 0.2\text{mA}$  [+1]


$$P_{\text{delivered}} = 0.4\text{V} \cdot 0.2\text{mA}$$

$$= 80\mu\text{W} \quad [+1]$$




work space

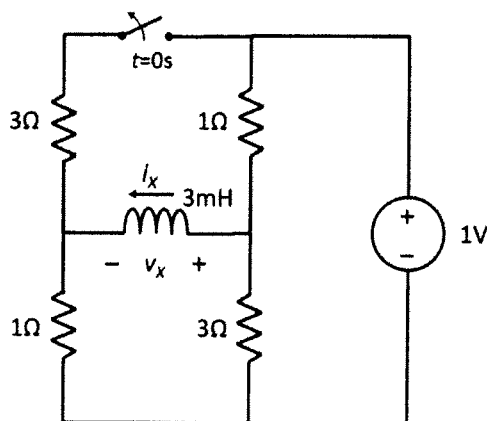3. Consider the circuit below. The circuit is in dc steady state for  $t < 0$  with the switch closed. At  $t = 0$ s, the switch opens instantaneously and remains open. Answer the questions. [12 pts]



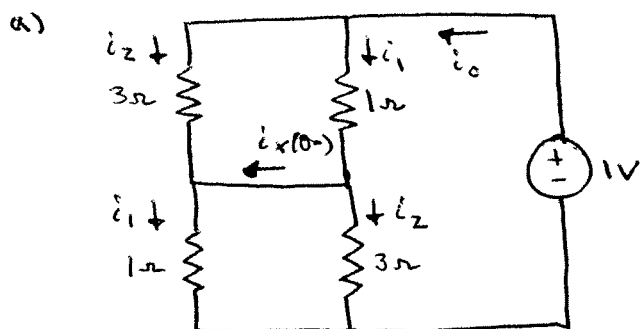- What is the inductor current  $i_x(0+)$ ? [3pts]
- What is the inductor current  $i_x(\infty)$ ? [3pts]
- What is the time constant for the first order response for  $t > 0$ ? [2pts]
- What is the inductor current  $i_x(t)$  for  $t > 0$ ? [2pts]
- What is the inductor voltage  $v_x(t)$  for  $t > 0$ ? [2pts]



dc steady state  $L \rightarrow$  short

$$i_o = \frac{1V}{(1\Omega // 3\Omega) + (1\Omega // 3\Omega)}$$

$$= \frac{2}{3} A$$

$$i_1 = \frac{3\Omega}{1\Omega + 3\Omega} \cdot i_o = \frac{1}{2} A \quad [+1]$$

$$i_2 = \frac{1\Omega}{1\Omega + 3\Omega} \cdot i_o = \frac{1}{6} A \quad [+1]$$


KCL:  $0 = -i_1 + i_x + i_2$

$$i_x = i_1 - i_2 = \frac{1}{3} A$$

$$i_x(0+) = i_x(0-) = \frac{1}{3} A \quad [+1]$$

work space

b)

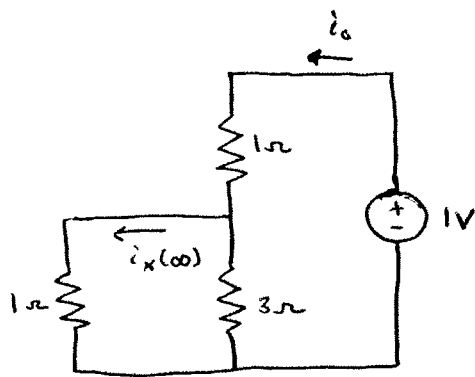

dc steady state  $L \rightarrow$  short


$$i_o = \frac{1V}{1\Omega + 1\Omega \parallel 3\Omega} \quad [+1]$$

$$= \frac{4}{7} A$$

$$i_x(\infty) = \frac{3\Omega}{1\Omega + 3\Omega} \cdot i_o \quad [+1]$$

$$= \frac{3}{7} A \quad [+1]$$

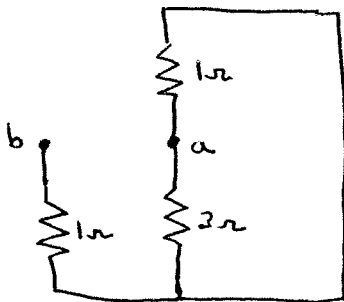c) Find  $R_{TH}$  from inductor terminals.



$$R_{TH} = 1\Omega + 1\Omega \parallel 3\Omega \quad \left[+\frac{1}{2}\right]$$

$$= \frac{7}{4} \Omega$$

$$\tau = \frac{L}{R_{TH}} \quad [+1/2]$$

$$= \frac{3mH}{7/4 \Omega}$$

$$= \frac{12}{7} ms \quad [+1]$$

$$d) \quad i_x(t) = i_x(\infty) + [i_x(0+) - i_x(\infty)] \exp(-t/\tau) \quad [+1]$$

$$= \frac{3}{7} A + \left(\frac{1}{3} - \frac{3}{7}\right) A \exp\left(-\frac{t}{12/7 \text{ ms}}\right)$$

$$= \frac{3}{7} A - \frac{2}{21} A \exp\left(\frac{-t}{12/7 \text{ ms}}\right) \quad [+1] \quad t > 0$$


$$e) \quad v_x(t) = L \frac{di_x}{dt} \quad [+1]$$

$$= 3 \text{ mH} \cdot \left(-\frac{2}{21} A \cdot \frac{-1}{12/7 \text{ ms}}\right) \exp\left(\frac{-t}{12/7 \text{ ms}}\right)$$

$$= \frac{1}{6} \text{ V} \exp\left(\frac{-t}{12/7 \text{ ms}}\right) \quad [+1]$$

work space

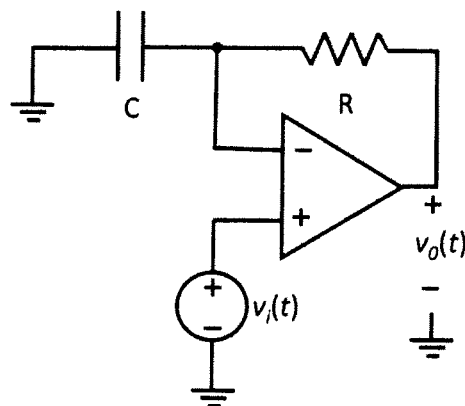4. Consider the circuit below. Assume ideal op-amp behavior. Answer the questions. [12 pts]




a) What is the output voltage  $v_o(t)$  as a function of the input voltage  $v_i(t)$ ? [5pts]

For the remaining questions, consider the case of  $R=10\text{k}\Omega$  and  $C=10\text{nF}$ .

b) If  $v_i(t)=5\text{V}$ , what is the energy stored in the capacitor? [2pts]

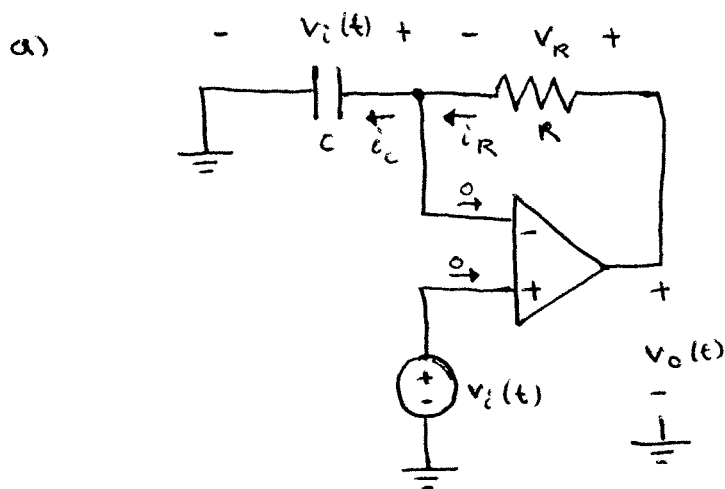c) If at an instantaneous time  $t_0$  it is known that  $v_i(t_0)=2\text{V}$  and  $dv_i/dt(t_0)=100\text{mV}/\mu\text{s}$ , what is the instantaneous power delivered or absorbed by the op-amp at the time  $t_0$ ? [5pts]



By ideal op-amp conditions,  
voltage across capacitor  
is  $v_i(t)$  (virtual short).  
[+1]

$$i_c = C \frac{dv_i}{dt} \quad [+1]$$

$$\text{KCL: } 0 = +i_c - i_R \quad \therefore i_R = i_c \quad [+1]$$

$$\text{Ohm: } v_R = i_R \cdot R = RC \frac{dv_i}{dt} \quad [+1]$$

$$\text{KVL: } 0 = -v_i - v_R + v_o$$

$$v_o = v_i + v_R$$

$$= v_i(t) + RC \frac{dv_i}{dt} \quad [+1]$$

$$b) \quad U = \frac{1}{2} C v_i^2 \quad [+1]$$

$$= \frac{1}{2} \cdot 10 \text{ nF} \cdot (5 \text{ V})^2$$

$$= 125 \text{ nJ} \quad [+1]$$

$$c) \quad \text{Power delivered by op-amp} = P_{OA} = i_R \cdot v_o \quad [+2]$$

$$i_R = C \frac{dv_i}{dt} = 10 \text{ nF} \cdot \frac{100 \text{ mV}}{1 \mu\text{s}}$$

$$= 1 \text{ mA} \quad [+1]$$

$$v_o = v_i + RC \frac{dv_i}{dt}$$

$$= 2 \text{ V} + 10 \text{ k}\Omega \cdot 10 \text{ nF} \cdot \frac{100 \text{ mV}}{1 \mu\text{s}}$$

$$= 12 \text{ V} \quad [+1]$$

$$P_{OA} = 12 \text{ V} \cdot 1 \text{ mA} = 12 \text{ mW} \quad [+1]$$

work space



work space

work space