



ELECTRIC CIRCUITS 1

ECSE 200

24 APRIL 2018, 14h00

EXAMINER: THOMAS SZKOPEK


ASSOC. EXAMINER: LAWRENCE CHEN

STUDENT NAME:		McGILL ID:											
----------------------	--	-------------------	--	--	--	--	--	--	--	--	--	--	--

INSTRUCTIONS:


EXAM:	CLOSED BOOK
	PRINTED ON BOTH SIDES OF THE PAGE
	ANSWER IN BOOKLET , EXTRA BOOKLETS PERMITTED
	THE EXAM SHOULD BE RETURNED
CRIB SHEETS:	NOT PERMITTED
DICTIONARIES:	NONE
CALCULATORS:	PERMITTED (Non-Programmable)
ANY SPECIAL INSTRUCTIONS:	NA

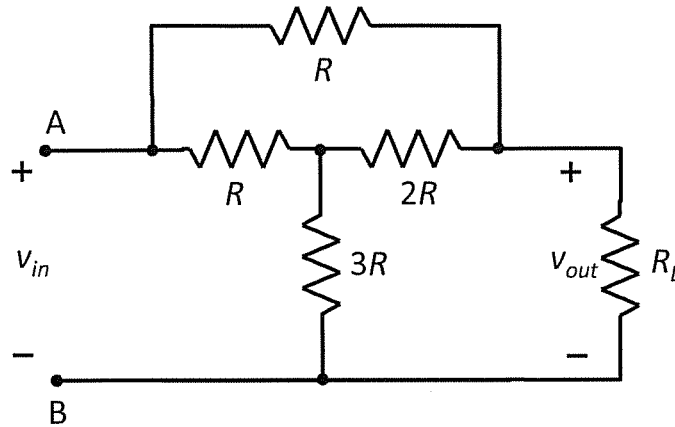1. Consider the circuit below. Answer the questions. [12 pts]









- a) What is the physical law at the origin of Kirchoff's current law? [1pt]
- b) What is the physical law at the origin of Kirchoff's voltage law? [1pt]
- c) What is the equivalent resistance between nodes A and B if R_L is an open circuit? [2pts]
- d) Assume $v_{in} = 1V$ and R_L is an open circuit. What is the total power absorbed by the resistors in the circuit? [2pts]
- e) What is the equivalent resistance between nodes A and B if R_L is a short circuit? [2pts]
- f) What is the equivalent resistance between nodes A and B if $R_L = R$? [3pts]
- g) What is the ratio v_{out}/v_{in} if $R_L = R$? [1pt]

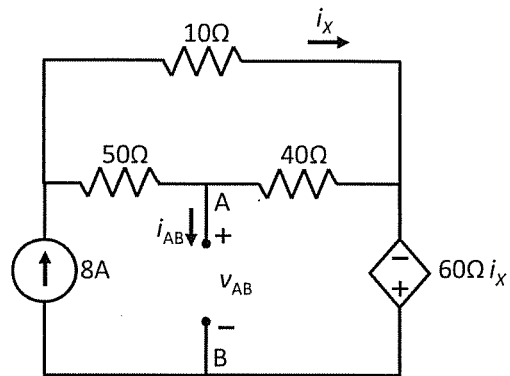2. Consider the circuit below. Answer the questions. [12 pts]





- What is Thévenin's theorem? [1pt]
- Write the equation that relates the quantities v_{oc} , i_{sc} and R_T . [1pt]
- What is the open circuit voltage v_{oc} at the terminals A and B? [2pts]
- What is the short circuit current i_{sc} at the terminals A and B? [2pts]
- Draw the i_{AB} versus v_{AB} diagram for the circuit. Label your axes. [2pts]
- Draw the Thévenin equivalent circuit with respect to the terminals A and B. [2pts]
- What is the maximum power that the circuit can deliver to an optimally chosen load resistor attached to the nodes A and B? [2pts]

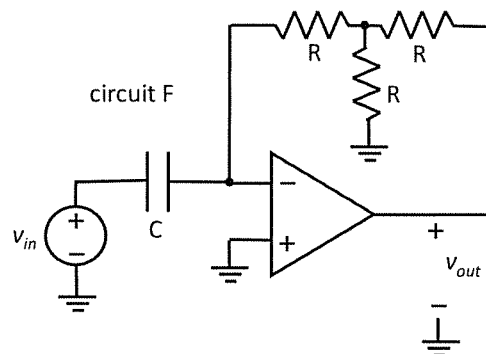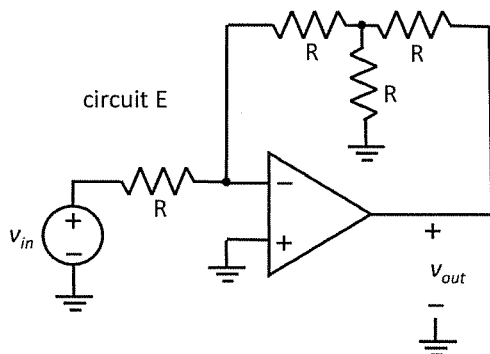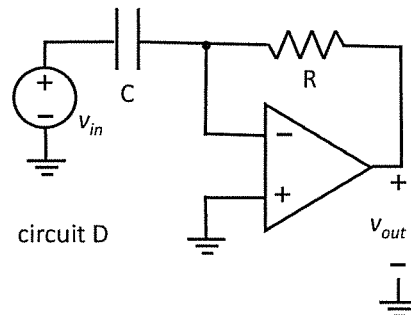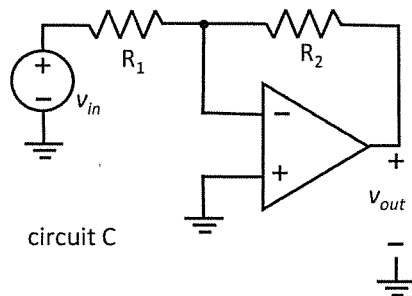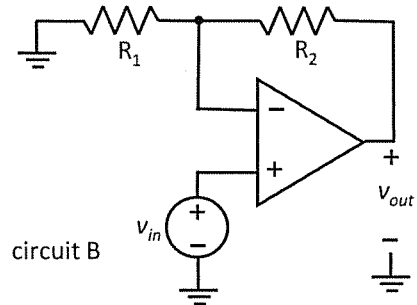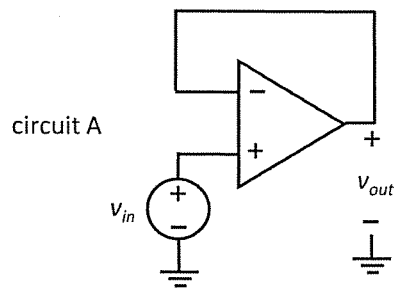3. Consider the circuits below. Assume ideal op-amp behaviour. Answer the questions. [12 pts]



- Express v_{out} in terms of v_{in} for circuit A. [2pts]
- Express v_{out} in terms of v_{in} for circuit B. [2pts]
- Express v_{out} in terms of v_{in} for circuit C. [2pts]
- Express v_{out} in terms of v_{in} for circuit D. [2pts]
- Express v_{out} in terms of v_{in} for circuit E. [2pts]
- Express v_{out} in terms of v_{in} for circuit F. [2pts]

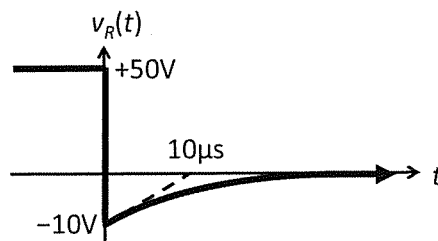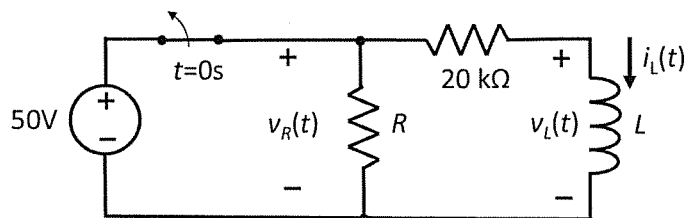4. Consider the circuit below. The circuit is in dc steady state for $t < 0$ with the switch closed. The switch opens instantaneously at $t = 0$ s. The circuit reaches a new dc steady state as $t \rightarrow \infty$. The voltage $v_R(t)$ versus time t is plotted below. Answer the questions. [12 pts]




- Give one reason why inductor current must be continuous versus time. [1pt]
- What is $i_L(t)$ at $t = 0^-$? [1pt]
- What is $i_L(t)$ at $t = 0^+$? [1pt]
- What is $i_L(t)$ as $t \rightarrow \infty$? [1pt]
- What is the value of R ? [2pts]
- What is the value of L ? [2pts]
- What is $i_L(t)$ for $t > 0$? [2pts]
- What is $v_L(t)$ for $t > 0$? [2pts]

end

1. a) conservation of charge [+1]

b) conservation of energy [+1]


c)

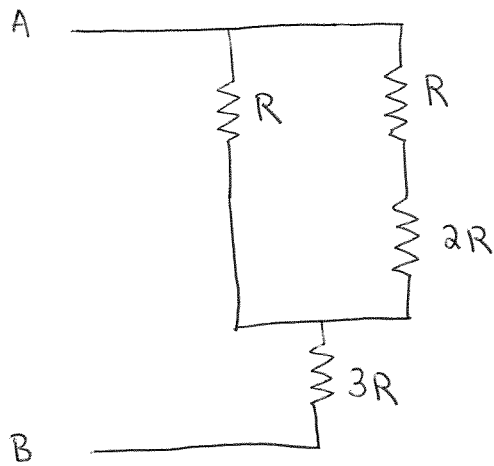

$$\begin{aligned} R_{AB} &= 3R + R \parallel (R + 2R) \quad [+1] \\ &= 3R + \frac{3}{4}R \\ &= 3\frac{3}{4}R \quad [+1] \end{aligned}$$


d)
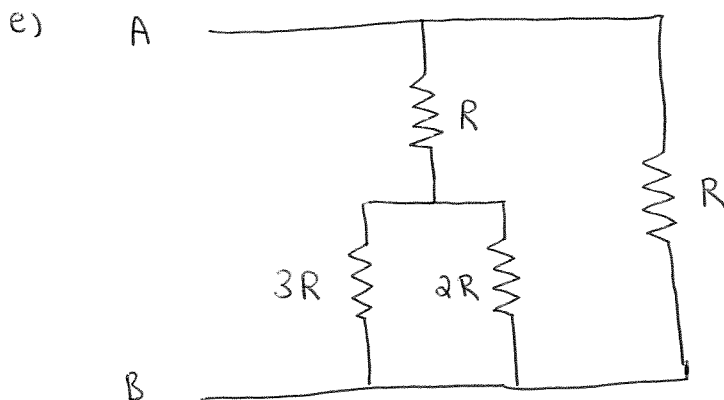
$$\begin{aligned} P_{abs} &= (1V)^2 / R_{AB} \quad [+1] \\ &= \frac{0.267W}{R} \text{ absorbed} \quad [+1] \end{aligned}$$



$$\begin{aligned} R_{AB} &= R \parallel (R + 3R \parallel 2R) \quad [+1] \\ &= R \parallel \frac{11}{5}R \\ &= \frac{11}{16}R \quad [+1] \end{aligned}$$

f)

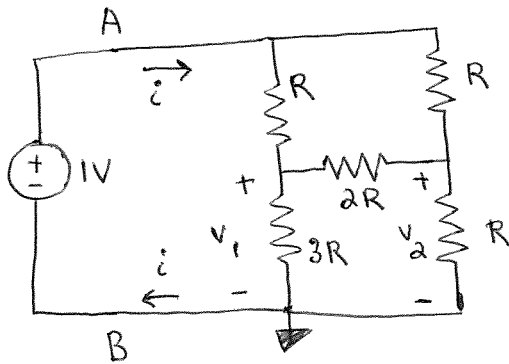

Apply test source. [+1]

$$0 = \frac{v_1}{3R} + \frac{v_1 - v_2}{2R} + \frac{v_1 - 1V}{R}$$

$$0 = \frac{v_2}{R} + \frac{v_2 - v_1}{2R} + \frac{v_2 - 1V}{R}$$

$$1 = \frac{11}{6} v_1 - \frac{1}{2} v_2$$

$$1 = -\frac{1}{2} v_1 + \frac{5}{2} v_2$$

$$\therefore v_1 = \frac{\begin{vmatrix} 1 & -1/2 \\ 1 & 5/2 \end{vmatrix}}{\begin{vmatrix} 11/6 & -1/2 \\ -1/2 & 5/2 \end{vmatrix}} = 0.6923V$$

$$v_2 = \frac{\begin{vmatrix} 11/6 & 1 \\ -1/2 & 1 \end{vmatrix}}{\begin{vmatrix} 11/6 & -1/2 \\ -1/2 & 5/2 \end{vmatrix}} = 0.5385V$$

$$i = \frac{v_1}{3R} + \frac{v_2}{R} = \frac{0.7693V}{R}$$

$$R_{AB} = \frac{1V}{i} \quad [+1]$$


$$= 1.300R \quad [+1]$$

g)

$$\frac{v_{out}}{v_{in}} = 0.5385 \quad [+1]$$

2. a) Any two-terminal circuit composed of resistors, independent sources, and dependent sources is equivalent to a voltage source in series with a resistor. [1]

b) $V_{oc} = i_{sc} \cdot R_T$ [1]

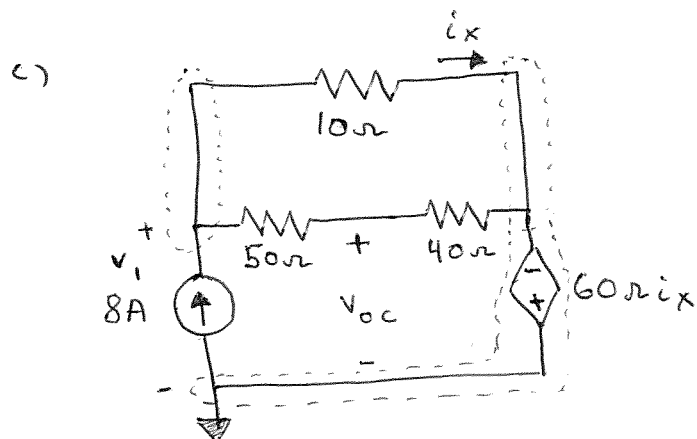

Apply an open circuit. [1]

$$\frac{V_1 + 60\Omega \cdot i_x}{10\Omega} + \frac{V_1 + 60\Omega i_x}{90\Omega} - 8A = 0$$

$$i_x = \frac{V_1 + 60\Omega \cdot i_x}{10\Omega}$$

$$8A = \frac{1}{9\Omega} \cdot V_1 + 6\frac{2}{3} \cdot i_x$$


$$0 = \frac{1}{10\Omega} \cdot V_1 + 5 \cdot i_x$$

$$\therefore V_1 = \frac{\begin{vmatrix} 8 & 6\frac{2}{3} \\ 0 & 5 \end{vmatrix}}{\begin{vmatrix} \frac{1}{9} & 6\frac{2}{3} \\ \frac{1}{10} & 5 \end{vmatrix}} = -360V$$

$$i_x = \frac{\begin{vmatrix} \frac{1}{9} & 8 \\ \frac{1}{10} & 0 \end{vmatrix}}{\begin{vmatrix} \frac{1}{9} & 6\frac{2}{3} \\ \frac{1}{10} & 5 \end{vmatrix}} = 7.200A$$

$$V_{oc} = V_1 - 50\Omega \cdot \left(\frac{V_1 + 60\Omega \cdot i_x}{90\Omega} \right) = -400V \quad [1]$$

d)

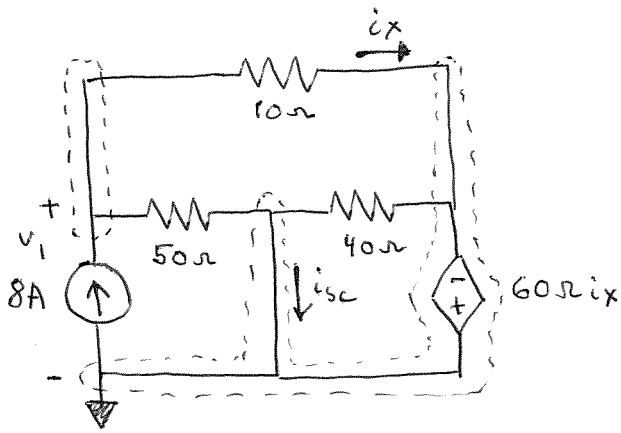

Apply a short circuit. [11]

$$\frac{v_1 + 60\Omega \cdot i_x}{10\Omega} + \frac{v_1}{50\Omega} - 8A = 0$$

$$i_x = \frac{v_1 + 60\Omega \cdot i_x}{10\Omega}$$

$$8A = \frac{3}{25} \cdot v_1 + 6 \cdot i_x$$

$$0 = \frac{1}{10} \cdot v_1 + 5 \cdot i_x$$


$$\therefore v_1 = \frac{\begin{vmatrix} 8 & 6 \\ 0 & 5 \end{vmatrix}}{\begin{vmatrix} 3/25 & 6 \\ 1/10 & 5 \end{vmatrix}} = \text{undefined}$$

$$i_x = \frac{\begin{vmatrix} 3/25 & 8 \\ 1/10 & 0 \end{vmatrix}}{\begin{vmatrix} 3/25 & 6 \\ 1/10 & 5 \end{vmatrix}} = \text{undefined}$$

If short-circuit conditions lead to no solution,
the circuit must be behaving as a voltage source.

i_{sc} is undefined. [11]

Easily confirmed:

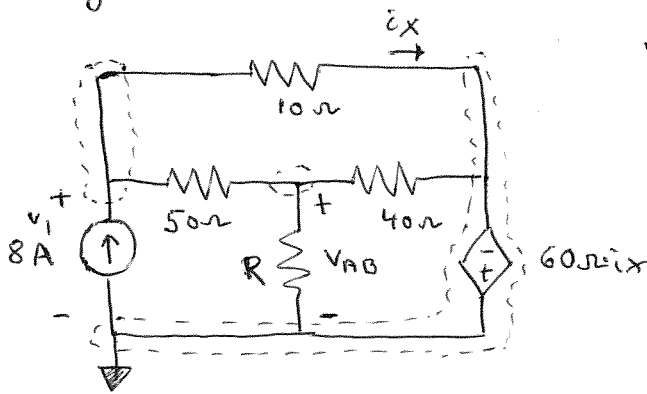

$$\frac{V_1 + 60\Omega \cdot i_x}{10\Omega} + \frac{V_1 - V_{AB}}{50\Omega} - 8A = 0$$


$$i_x = V_1 + 60\Omega \cdot i_x$$

$$\therefore i_x = -V_1 / 50\Omega$$

$$\frac{V_1 + 60\Omega \cdot (-V_1 / 50\Omega)}{10\Omega} + \frac{V_1 - V_{AB}}{50\Omega} - 8A = 0$$


$$-\frac{V_{AB}}{50\Omega} = 8A$$

$$V_{AB} = -400V$$

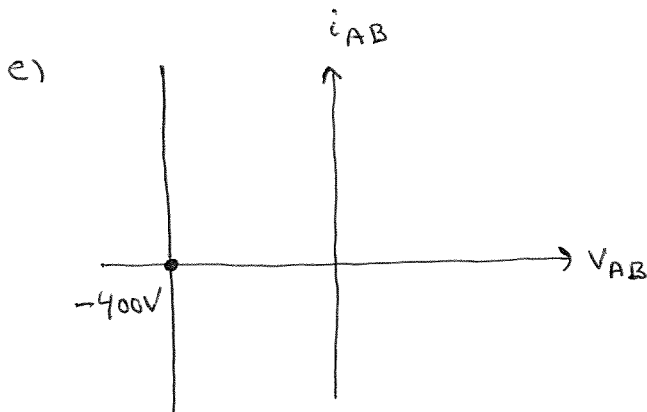

[+1] for an i-v diagram

[+1] for correct diagram

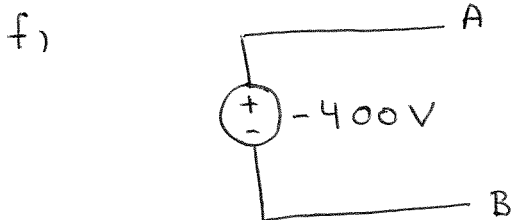

[+1] for a Thévenin circuit

[+1] for correct circuit


g)

$$P_{\max} = \frac{V_{oc}}{2} \cdot \frac{i_{sc}}{2} \quad [+1]$$

\Rightarrow no limit because the Thévenin equivalent circuit is a voltage source. [+1]


3.

a)

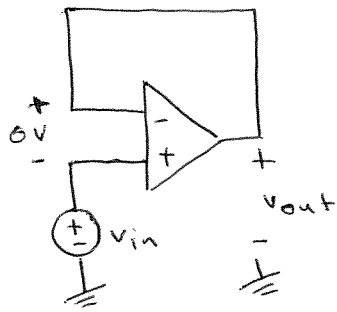

$$V_{out} = V_{in} \quad [+2]$$


b)

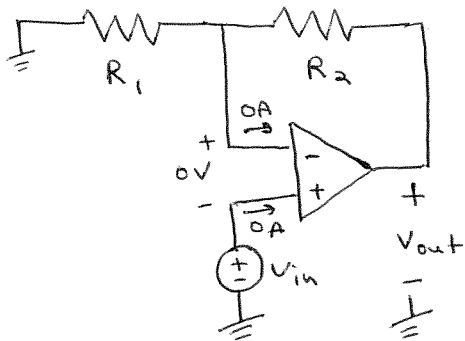

$$\frac{v_{in}}{R_1} + \frac{v_{in} - v_{out}}{R_2} = 0$$

$$V_{out} = V_{in} \cdot \left(1 + \frac{R_2}{R_1} \right) \quad [+2]$$


c)

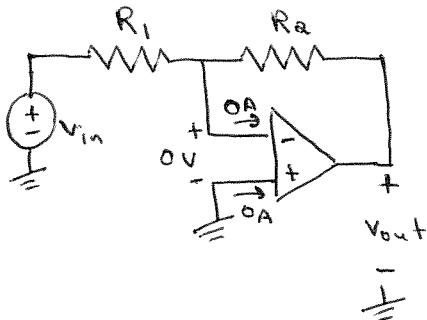

$$\frac{0 - v_{in}}{R_1} + \frac{0 - v_{out}}{R_2} = 0$$

$$V_{out} = v_{in} \cdot \left(-\frac{R_2}{R_1} \right) \quad [+2]$$


d)

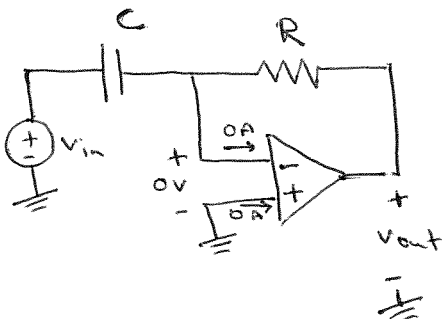

$$C \frac{d}{dt} (0 - v_{in}) + \frac{0 - v_{out}}{R} = 0$$

$$V_{out} = -RC \cdot \frac{dv_{in}}{dt} \quad [+2]$$

e)

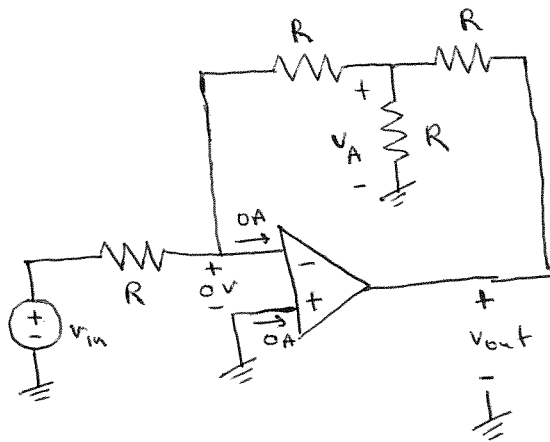

$$\frac{0 - v_{in}}{R} + \frac{0 - V_A}{R} = 0$$


$$V_A = -v_{in}$$

$$\frac{V_A}{R} + \frac{V_A}{R} + \frac{V_A - v_{out}}{R} = 0$$

$$v_{out} = 3V_A$$

$$\therefore v_{out} = -3v_{in} \quad [12]$$

f)

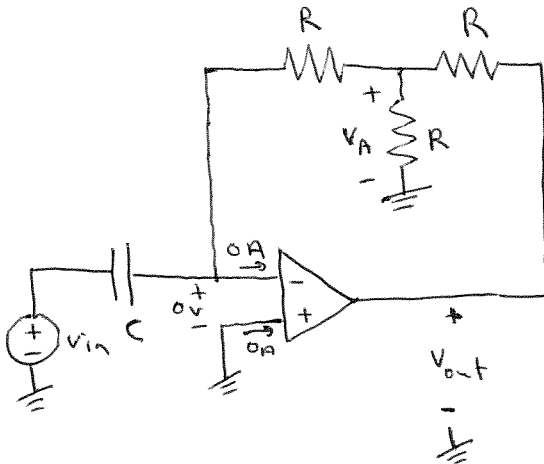

$$C \frac{d}{dt}(0 - v_{in}) + \frac{0 - V_A}{R} = 0$$

$$V_A = -RC \frac{dv_{in}}{dt}$$


$$\frac{V_A}{R} + \frac{V_A}{R} + \frac{V_A - v_{out}}{R} = 0$$

$$v_{out} = 3V_A$$

$$\therefore v_{out} = -3RC \frac{dv_{in}}{dt} \quad [12]$$

4. a) finite voltage
finite power
conservation of energy } [1]


b) $t < 0$

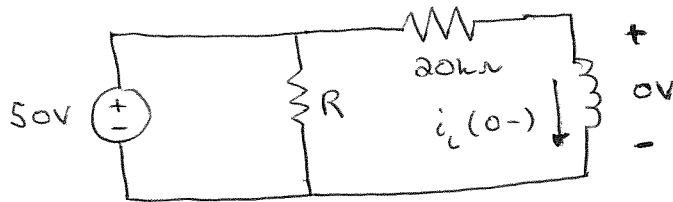

$$i_L(0-) = \frac{50V}{20k\Omega} = 2.5mA \quad [1]$$


c) $i_L(0+) = i_L(0-) = 2.5mA \quad [1]$

d) $t \rightarrow \infty$

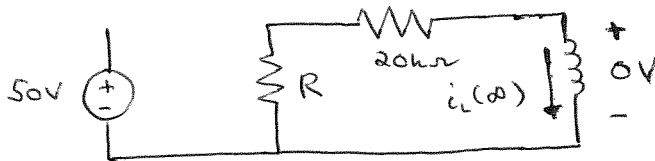

$$i_L(\infty) = 0A \quad [1]$$


e) $t = 0+$ [1]

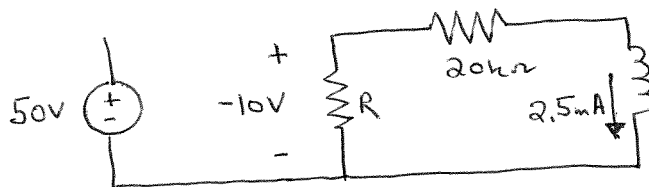

$$(-10V) = -2.5mA \cdot R$$

$$R = 4k\Omega \quad [1]$$

f) $t > 0$

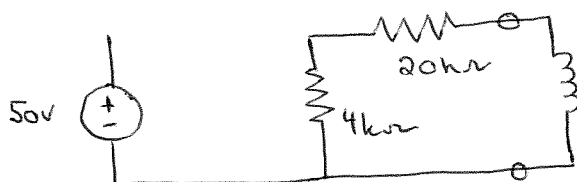

$$R_T = 24k\Omega$$

$$\tau = \frac{L}{R_T} \quad [1]$$

$$L = 10\mu s \cdot 24k\Omega = 240mH \quad [1]$$

$$g) \quad i_L(t) = i_L(\infty) + [i_L(0+) - i_L(\infty)] \exp(-t/\tau) \quad [1]$$

$$= 2.5 \text{ mA} \exp(-t/10 \mu\text{s}) \quad [1]$$

$$h) \quad v_L(t) = L \frac{d}{dt} i_L(t) \quad [1]$$

$$= 240 \text{ mH} \cdot \left(\frac{-1}{10 \mu\text{s}} \right) \cdot 2.5 \text{ mA} \exp(-t/10 \mu\text{s})$$

$$= -60 \text{ V} \exp(-t/10 \mu\text{s}) \quad [1]$$