



Electric Circuits 1  
ECSE-200 Section: 1, 2

13 Dec 2011, 9:00AM


Examiner: Thomas Szkopek

Assoc Examiner: Zetian Mi

INSTRUCTIONS:

- This is a **CLOSED BOOK** examination.
- **NO CRIB SHEETS** are permitted.
- Provide your answers in an **EXAM BOOKLET**.
- **STANDARD CALCULATOR** permitted ONLY.
- This examination consists of 4 questions, with a total of 6 pages, including the cover page.
- This examination is **PRINTED ON BOTH SIDES** of the paper




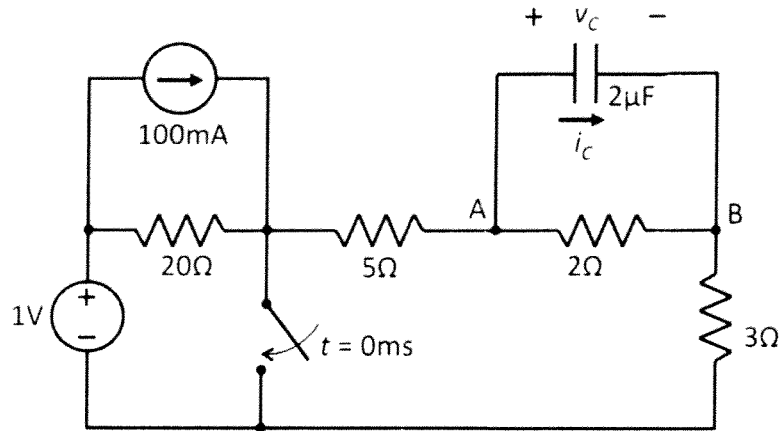
1. Consider the circuit below. The circuit is in dc steady state for  $t < 0$ . The switch closes instantaneously at  $t = 0$ . Answer the questions. [12 pts]



- Give one physical reason why capacitor voltage must be continuous. [1pt]
- Draw an equivalent circuit for  $t < 0$ . Your circuit should be a Thévenin equivalent circuit connected to a capacitor. [2pts]
- Draw an equivalent circuit for  $t > 0$ . Your circuit should be a Thévenin equivalent circuit connected to a capacitor. [1pt]
- What is  $v_C(t)$  for  $t > 0$ ? [4pts]
- What is  $i_C(t)$  for  $t > 0$ ? [2pts]
- Consider the equivalent circuit in part c). What is the total energy absorbed by the Thévenin resistance over the time interval  $0 < t < \infty$ ? [2pts]




- a) conservation of energy  
 conservation of charge  
 finite current  
 finite power
- } [1]

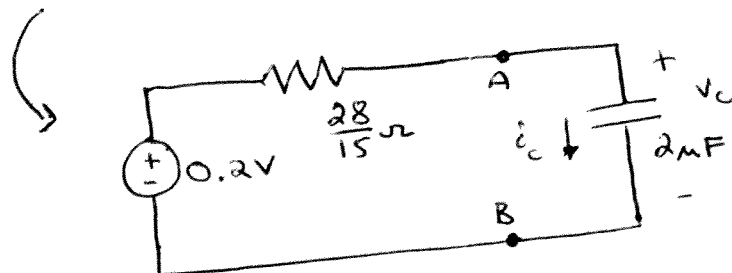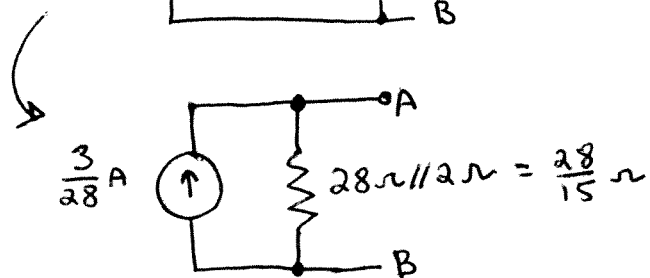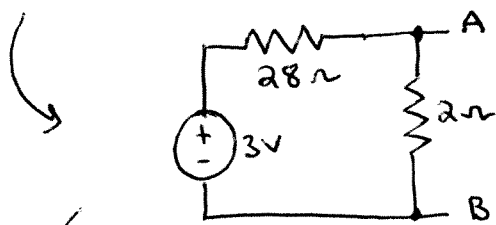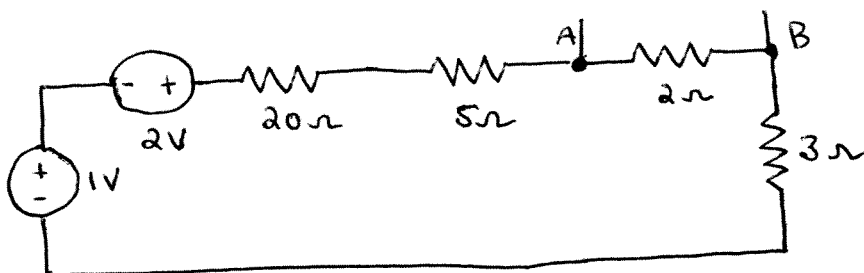b) Use source transformations and equivalent resistance:



[1] for  $V_{OC}$   
 [1] for  $R_T$

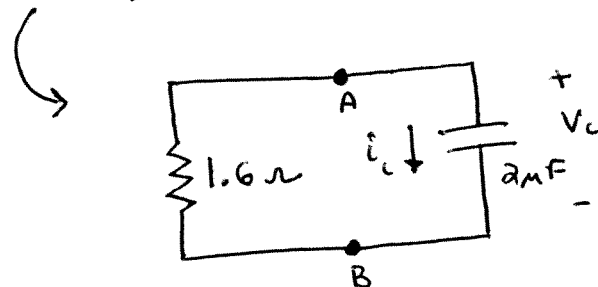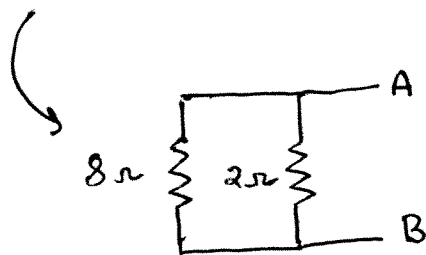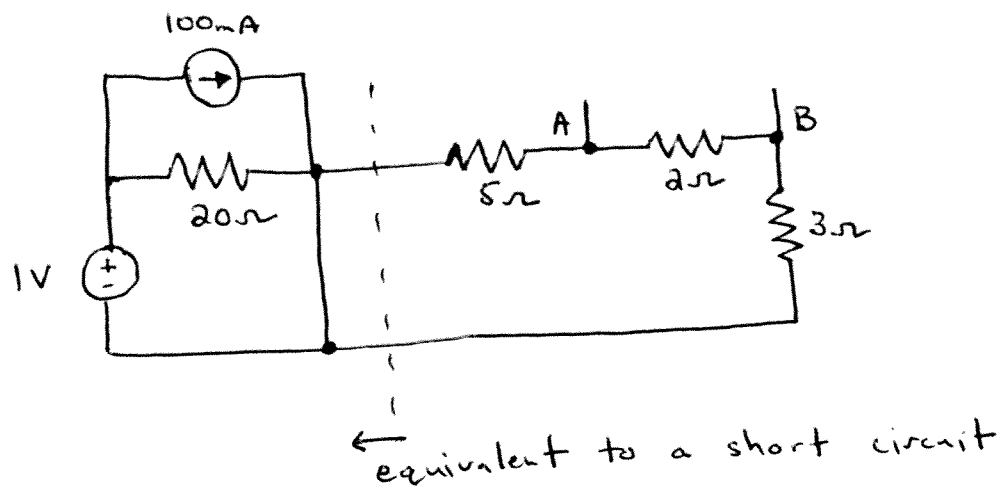c) Use equivalent resistance and Thévenin's theorem:



[+1] for  $R_T$

d)  $V_c(0+) = V_c(0-) = 0.2 \text{ V}$  (from b)  
[+1]

$V_c(\infty) = -i_c(\infty) \cdot 1.6 \Omega = 0 \text{ A} \cdot 1.6 \Omega = 0 \text{ V}$  (from c)  
[+1]

$\tau = R_{TH} \cdot C = 1.6 \Omega \cdot 2 \mu\text{F}$   
 $= 3.2 \mu\text{s}$  [+1]


$$\begin{aligned}
 v_c(t) &= v_c(\infty) + [v_c(0+) - v_c(\infty)] e^{-t/\tau} \quad [112] \\
 &= 0.2V e^{-t/3.2\mu s} \quad t > 0 \quad [11]
 \end{aligned}$$

$$\begin{aligned}
 e) \quad i_c(t) &= C \frac{dv_c}{dt} \quad [11] \\
 &= 2\mu F \cdot \frac{d}{dt} (0.2V e^{-t/3.2\mu s}) \\
 &= 2\mu F \cdot 0.2V \cdot -\frac{1}{3.2\mu s} \cdot e^{-t/3.2\mu s} \\
 &= -125\text{mA} e^{-t/3.2\mu s} \quad [11]
 \end{aligned}$$

f) By conservation of energy:


$$\begin{aligned}
 U_{\text{abs}} &= \frac{1}{2} C (v_c(0+))^2 \quad [11] \\
 &= \frac{1}{2} \cdot 2\mu F \cdot (0.2V)^2 \\
 &= 40\text{nJ} \quad [11]
 \end{aligned}$$

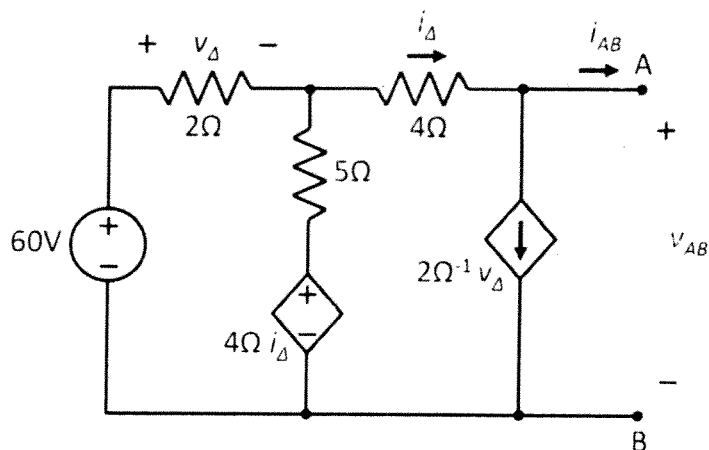2. Consider the circuit below. Answer the questions. [12 pts]



- What is the physical principle behind Kirchoff's Voltage Law? [1pt]
- What is the physical principle behind Kirchoff's Current Law? [1pt]
- Name one circuit theorem or principle that follows from the linearity of a circuit. [1pt]
- What is the Thévenin equivalent circuit with respect to the terminals A and B? Clearly label A and B on your circuit diagram. [4pts]
- What is the Norton equivalent circuit with respect to the terminals A and B? Clearly label A and B on your circuit diagram. [1pt]
- What is the maximum power that the circuit can deliver to an optimally chosen load resistor attached to the terminals A and B? What is the value of the optimally chosen load resistor. [4pts]

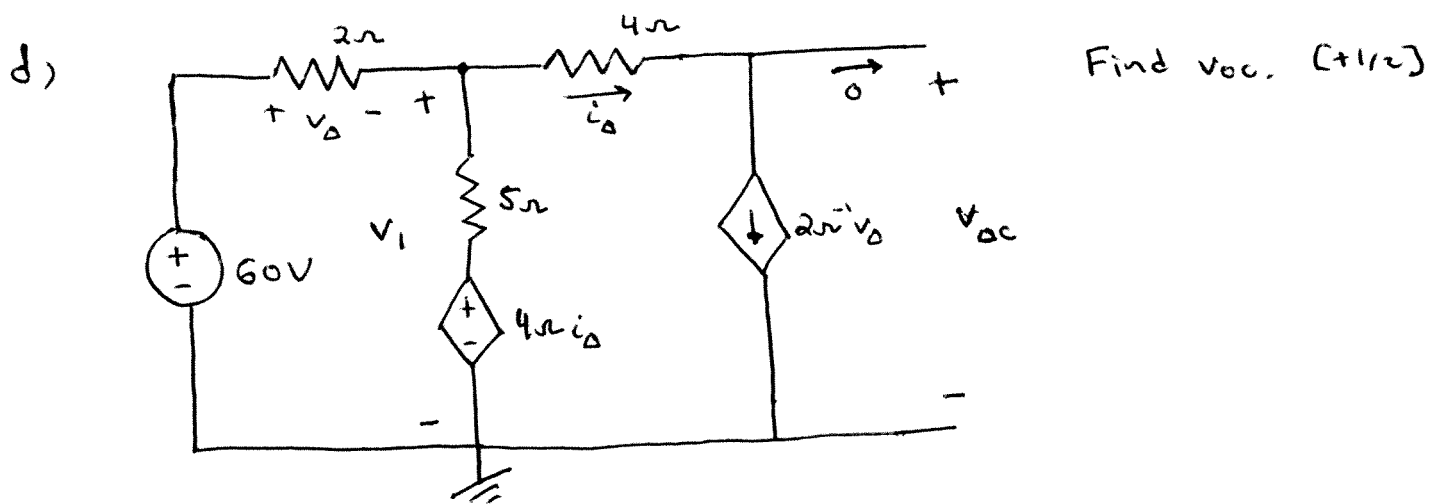- a) conservation of energy (+1)
- b) conservation of charge (+1)
- c) principle of linear superposition  
Thévenin's theorem  
Norton's theorem  
Source transformations  
maximum power transfer theorem } (+1)



node:

$$\frac{V_1 - 60V}{2\Omega} + \frac{V_1 - 4\Omega i_\Delta}{5\Omega} + 2\Omega^{-1} V_\Delta = 0$$

control:  $i_\Delta = 2\Omega^{-1} V_\Delta$


$$V_\Delta = 60V - V_1$$

$$\frac{V_1 - 60V}{2\Omega} + \frac{V_1 - 4\Omega (2\Omega^{-1} (60V - V_1))}{5\Omega} + 2\Omega^{-1} (60V - V_1) = 0$$

$$V_1 \left( \frac{1}{2} + \frac{1}{5} + \frac{2 \cdot 4}{5} - 2 \right) + \left( -\frac{60}{2} - \frac{4 \cdot 2 \cdot 60}{5} + 2 \cdot 60 \right) = 0$$

$$V_1 = \frac{+6}{0.3} = +20V$$

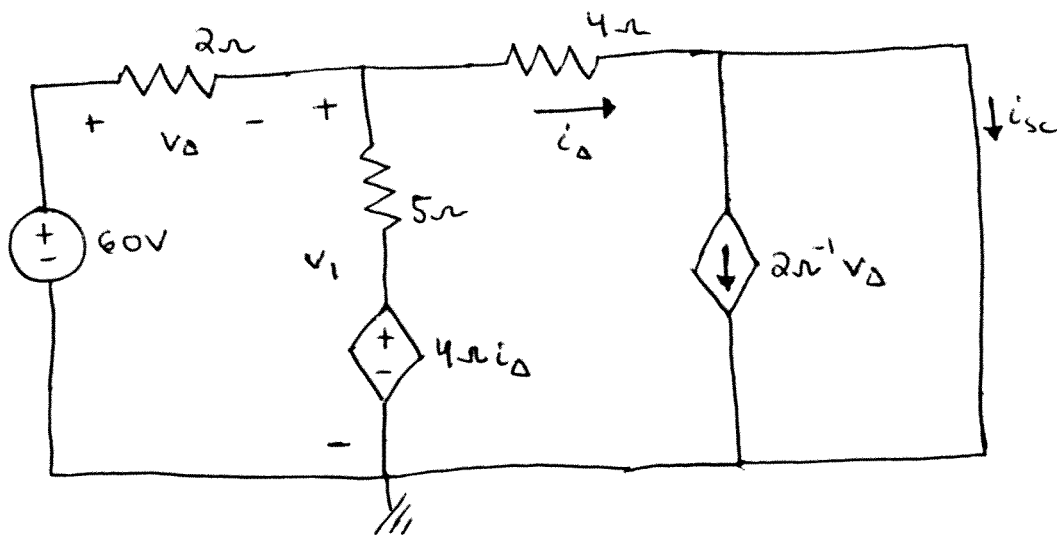KVL:  $V_{OC} = V_1 - i_\Delta \cdot 4\Omega = V_1 - 4\Omega \cdot 2\Omega^{-1} (60V - V_1)$   
 $= -300V$  (+1)



Find  $i_{sc}$ .  
[+1/2]

node: 
$$\frac{v_1 - 60V}{2\Omega} + \frac{v_1 - 4\Omega i_\Delta}{5\Omega} + \frac{v_1}{4\Omega} = 0$$

control:  $i_\Delta = v_1 / 4\Omega$


$v_\Delta = 60V - v_1$

$$\frac{v_1 - 60V}{2\Omega} + \frac{v_1 - v_1}{5\Omega} + \frac{v_1}{4\Omega} = 0$$

$$v_1 = \frac{(60/2)}{(1/2 + 1/4)} = 40V$$

KCL: 
$$\begin{aligned} i_{sc} &= i_\Delta - 2\Omega^{-1} v_\Delta \\ &= \frac{v_1}{4\Omega} - 2\Omega^{-1} (60V - v_1) \\ &= -30A \quad [+1] \end{aligned}$$
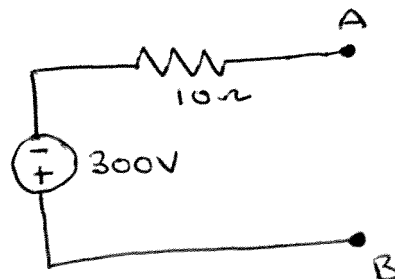
$$R_T = v_{oc} / i_{sc} \quad [+1]$$
  
$$= 10\Omega$$




[max points = 4]

[+1] for circuit



e)

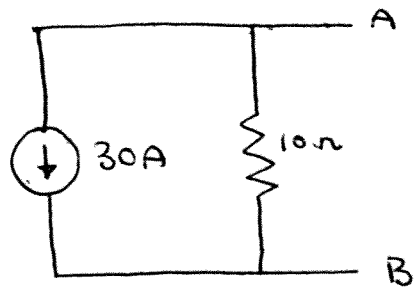

(+1)

f)


$$P_{\max} = \frac{V_{oc}}{2} \cdot \frac{I_{sc}}{2} \quad (+1)$$

$$= 2,25 \text{ kW} \quad (+1)$$

$$R_L = R_T \quad (+1)$$

$$= 10\Omega \quad (+1)$$

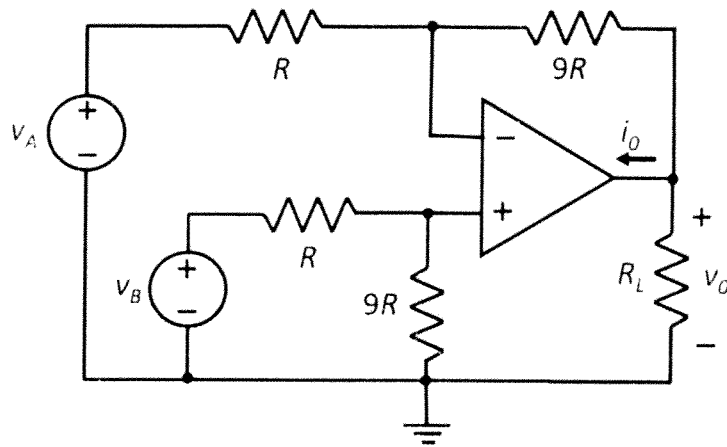3. Consider the circuit below. Assume ideal op-amp behaviour. Answer the questions. [12 pts]



a) Express  $v_o$  as a function of  $v_A$  and  $v_B$ . [2pts]

Assume  $v_A = 1V$ ,  $v_B = 2V$ ,  $R = 1k\Omega$  and  $R_L = 1k\Omega$  for the remainder of this question.

b) What is the total power absorbed by the resistors in this circuit? [2pts]

c) What is the total power delivered or absorbed by the independent voltage sources? [2pts]


d) What is the current  $i_o$ ? [2pts]

e) A voltmeter with  $18k\Omega$  internal resistance is used to measure the voltage of the non-inverting input terminal of the op-amp relative to the reference terminal. What is the measured voltage? [2pts]

f) Does the circuit have a negative feedback loop? [1pt]

g) Give one benefit of using negative feedback in op-amp circuits. [1pt]

a)

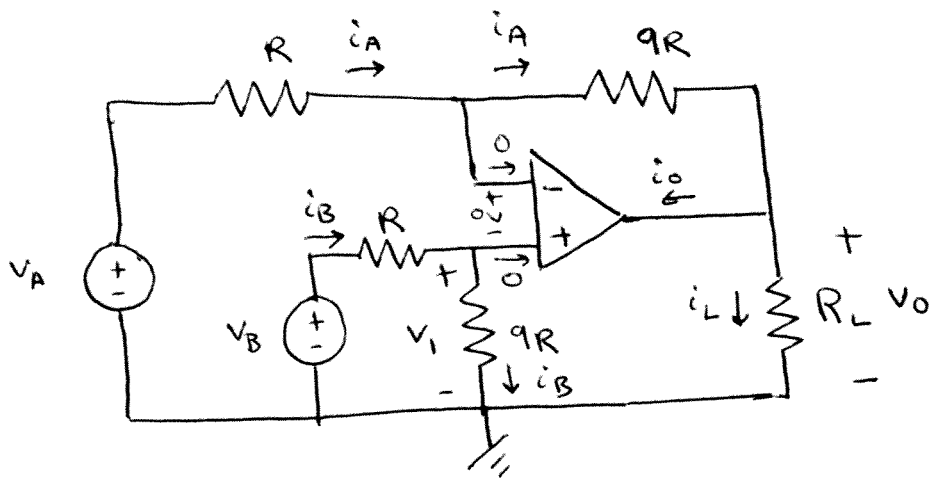

$$V_1 = V_B \cdot \frac{9R}{R+9R} = 9V_B/10 \quad [+1]$$

KCL at inverting node:

$$0 = \frac{V_1 - V_A}{R} + \frac{V_1 - V_o}{9R}$$

$$0 = \frac{9V_B}{10} - V_A + \frac{1}{9} \left( \frac{9V_B}{10} - V_o \right)$$

$$V_o = 9 \left( \frac{V_B}{10} - V_A \right) + \frac{9V_B}{10}$$

$$V_o = 9(V_B - V_A) \quad [+1]$$

$$b) \quad i_B = \frac{V_B}{R+9R} = \frac{2V}{10k\Omega} = 0.2mA$$

$$i_A = \frac{V_A - V_1}{R} = \frac{1V - \frac{9}{10} \cdot 2V}{1k\Omega} = -0.8mA$$

$$i_L = \frac{V_o}{R_L} = \frac{9(2V-1V)}{1k\Omega} = 9mA$$


$$P_{abs} = i^2 R = v^2/R \quad [+1], \text{ sum for each resistor:}$$

$$\begin{aligned}
 P_{\text{abs, total}} &= i_B^2 \cdot R + i_B^2 \cdot 9R + i_A^2 \cdot R + i_A^2 \cdot 9R + i_C^2 \cdot R_L \\
 &= 40 \mu\text{W} + 360 \mu\text{W} + 640 \mu\text{W} + 5760 \mu\text{W} + 81000 \mu\text{W} \\
 &= 87.8 \text{ mW} \quad (+1)
 \end{aligned}$$

$$\begin{aligned}
 \text{c) } P_{\text{del}} &= i_A \cdot V_A + i_B \cdot V_B \quad (+1) \\
 &= -0.8 \text{ mA} \cdot 1\text{V} + 0.2 \text{ mA} \cdot 2\text{V} \\
 &= -400 \mu\text{W} \quad (+1) \\
 &\text{(or } +400 \mu\text{W absorbed)}
 \end{aligned}$$

$$\begin{aligned}
 \text{d) KCL: } i_o &= i_A - i_L \quad (+1) \\
 &= -0.8 \text{ mA} - 9 \text{ mA} \\
 &= -9.8 \text{ mA} \quad (+1)
 \end{aligned}$$

e)

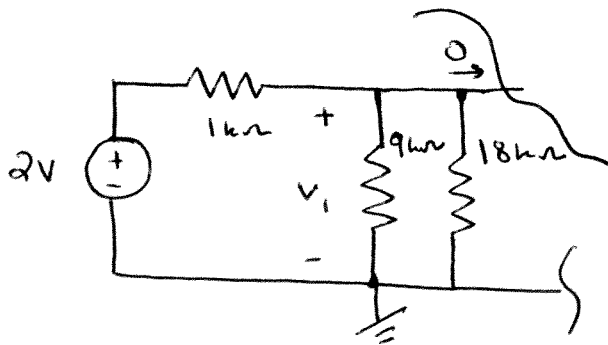

(+1) for circuit

$$\begin{aligned}
 V_1 &= 2\text{V} \cdot \frac{9\text{k}\Omega // 18\text{k}\Omega}{1\text{k}\Omega + 9\text{k}\Omega // 18\text{k}\Omega} \\
 &= 1.714 \text{ V} \quad (+1)
 \end{aligned}$$

f) yes  $[+1]$



g) stability

programmability

independence from open-loop op-amp parameters


}  $[+1]$

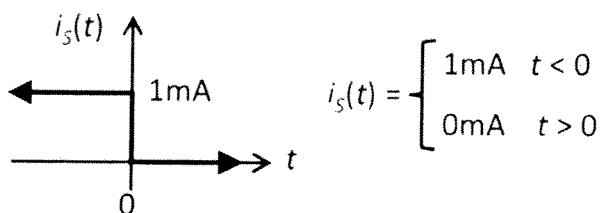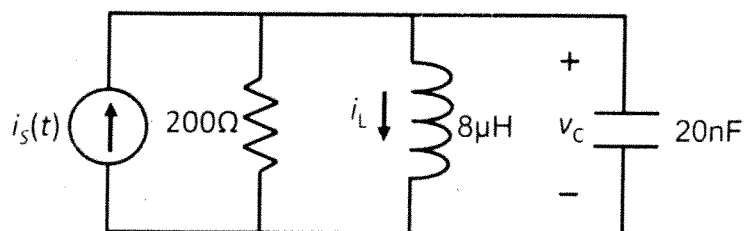4. Consider the circuit and the plot below. Assume dc steady state behaviour for  $t < 0$ . Answer the questions. [12 pts]



- What is  $v_c(0+)$ ? [1pt]
- What is  $i_L(0+)$ ? [1pt]
- What is the total energy stored in this circuit at  $t = 0+$ ? [2pts]
- What is the differential equation for  $v_c(t)$  for the time interval  $t > 0$ ? [3pts]
- Find  $v_c(t)$  for  $t > 0$ . Note that it can be shown that  $dv_c/dt(0+) = -50\text{kV/s}$ . [4pts]
- Is this RLC circuit's natural response underdamped, critically damped, or overdamped? [1pt]

a) b)

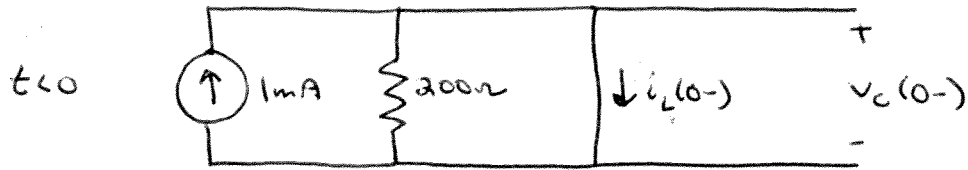


$$i_L(0+) = i_L(0-) = 1\text{mA} \quad (+1)$$

$$v_C(0+) = v_C(0-) = 0\text{V} \quad (+1)$$

$$\begin{aligned} c) \quad U &= \frac{1}{2} C (v_C(0+))^2 + \frac{1}{2} L (i_L(0+))^2 \quad (+1) \\ &= \frac{1}{2} \cdot 20\text{nF} (0\text{V})^2 + \frac{1}{2} \cdot 8\mu\text{H} (1\text{mA})^2 \\ &= 4\text{pJ} \quad (+1) \end{aligned}$$

d)

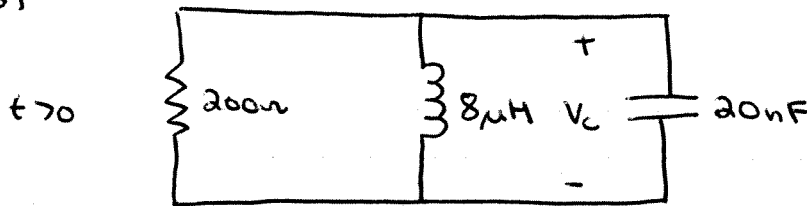

$$0 = \frac{v_C}{200\Omega} + \frac{v_C}{s \cdot 8\mu\text{H}} + \frac{v_C}{1/s \cdot 20\text{nF}}$$

multiply by  $s/20\text{nF}$

$$0 = s^2 \cdot v_C + \frac{1}{200\Omega \cdot 20\text{nF}} \cdot s \cdot v_C + \frac{1}{8\mu\text{H} \cdot 20\text{nF}} \cdot v_C$$

$$0 = \left( s^2 + 2.5 \times 10^5 s + 6.25 \times 10^{12} \right) v_C$$

$$0 = \left[ \frac{d^2}{dt^2} + 2.5 \times 10^5 \frac{d}{dt} + 6.25 \times 10^{12} \right] v_C \quad \begin{matrix} (+1) \\ \text{for} \\ \text{each term} \end{matrix}$$

e)

$$s = \frac{-2.5 \times 10^5 \pm \sqrt{(2.5 \times 10^5)^2 - 4 \cdot 1 \cdot 6.25 \times 10^{12}}}{2 \cdot 1}$$

$$= -1.25 \times 10^5 \pm j 2.497 \times 10^6 \text{ (s}^{-1}\text{)} \quad (+1)$$

$$v_c(t) = e^{-1.25 \times 10^5 s^{-1} t} \left[ A \cos(2.497 \times 10^6 s^{-1} t) + B \sin(2.497 \times 10^6 s^{-1} t) \right]$$

(+1)

initial conditions:  $v_c(0+) = 0V$

$$\therefore v_c(0) = 1 \cdot [A \cdot 1 + B \cdot 0]$$

$$= A$$

$$\therefore A = 0 \quad (+1)$$

$$\frac{dv_c}{dt}(0+) = -\frac{50kV}{s}$$

$$\therefore \frac{dv_c}{dt} = \frac{d}{dt} \left[ e^{-1.25 \times 10^5 s^{-1} t} B \sin(2.497 \times 10^6 s^{-1} t) \right]$$

$$= -1.25 \times 10^5 s^{-1} t \cdot e^{-1.25 \times 10^5 s^{-1} t} \cdot B \sin(2.497 \times 10^6 s^{-1} t)$$

$$+ 2.497 \times 10^6 s^{-1} \cdot e^{-1.25 \times 10^5 s^{-1} t} B \cos(2.497 \times 10^6 s^{-1} t)$$

$$\frac{dv_c}{dt}(0) = 2.497 \times 10^6 s^{-1} \cdot 1 \cdot B \cdot 1$$

$$B = \frac{-50kV/s}{2.497 \times 10^6 s^{-1}} = -20.0 mV \quad (+1)$$

$$\therefore v_c(t) = e^{-1.25 \times 10^5 s^{-1} t} \left[ -20.0 mV \sin(2.497 \times 10^6 s^{-1} t) \right]$$

f) underdamped (+1)



end

;;