

## 6. Energy Storage Elements


- the Capacitor
- the Inductor
- Coupled Inductors
- dc steady state
- op-amp circuits with energy storage elements

# Motivation


Capacitors and inductors are circuit elements that allow one to store and release electric energy, and they appear in most circuits, here are just a few examples:



power sub-stations

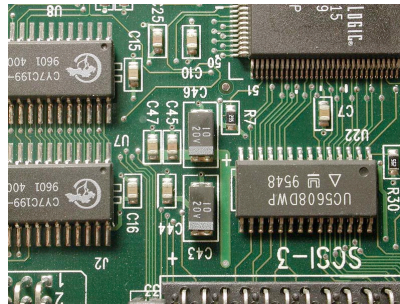

audio + video circuits

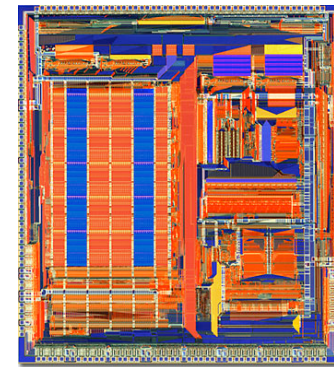


digital integrated circuits



power supplies



turbines

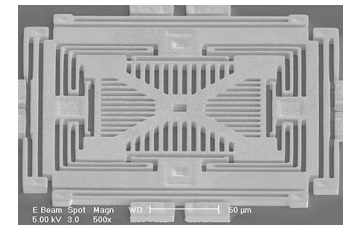

accelerometers,  
manometers and  
other sensors


# Today's Outline

## **6. Energy Storage Elements**

- the Capacitor

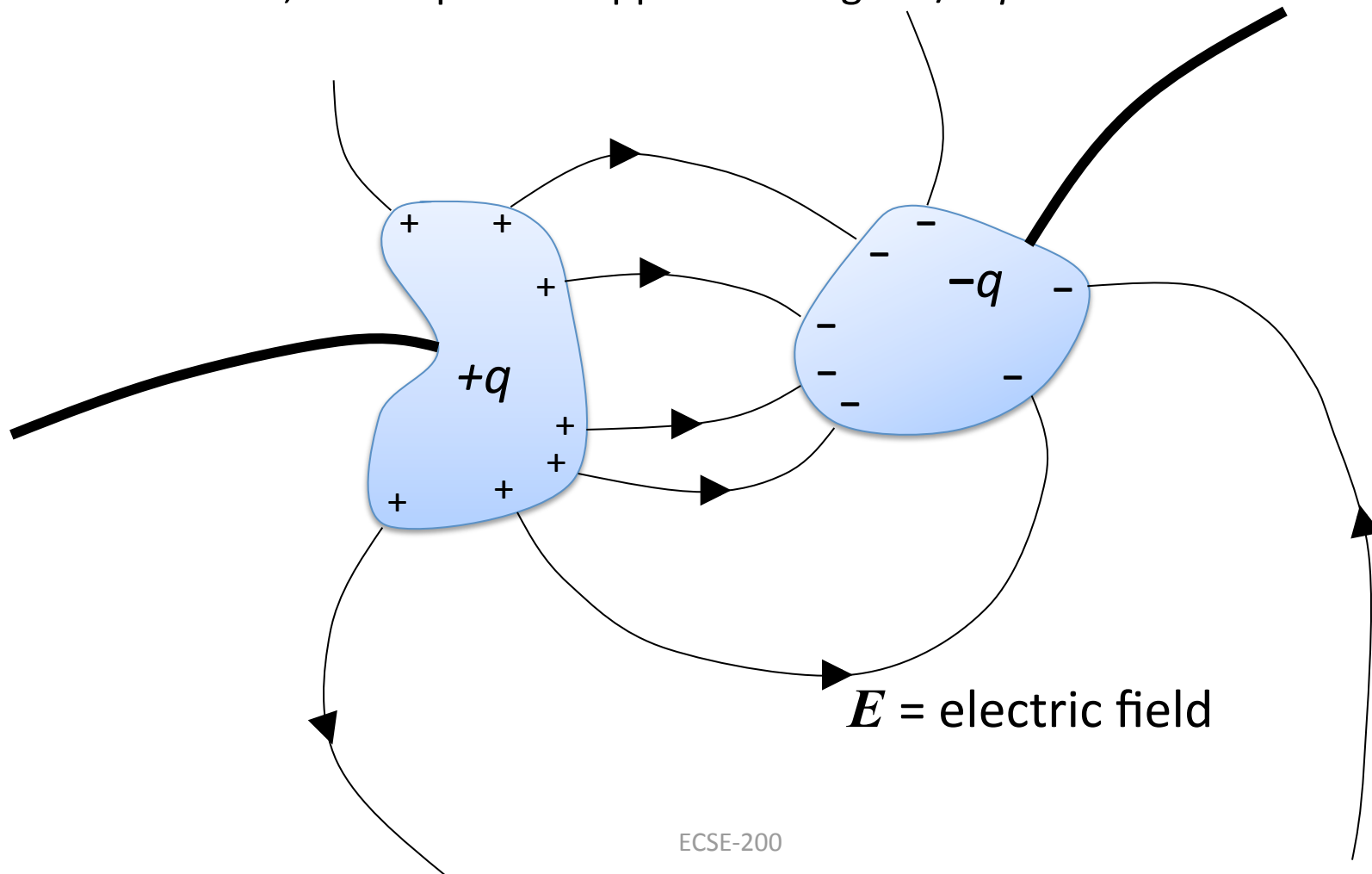
# the capacitor

**Ideal capacitor:** physically consists of two ideal conductors separated by an ideal insulator, with equal but opposite charges  $+/- q$  on each conductor



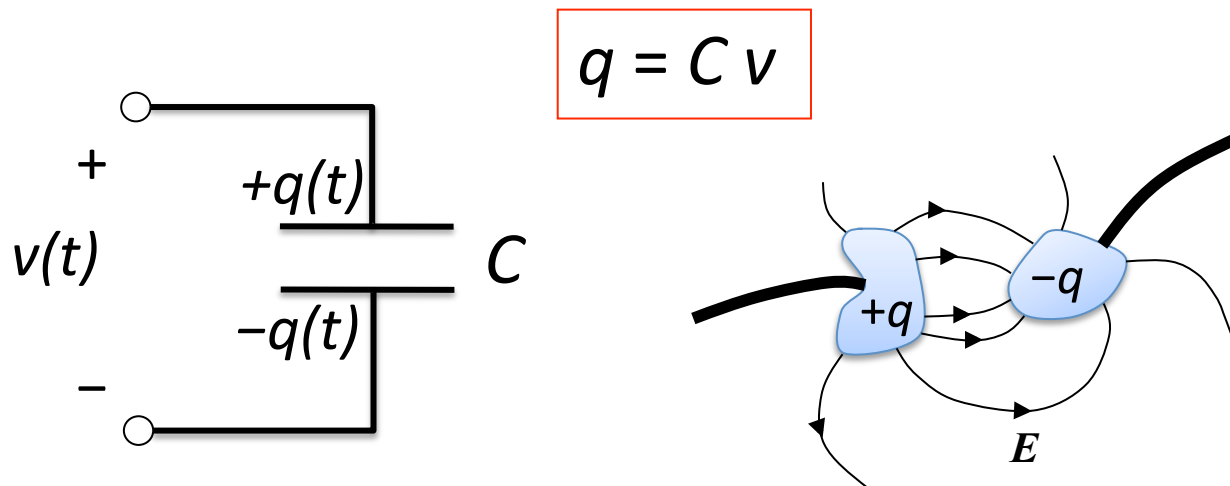
# the capacitor

**Ideal Capacitor:** the **charge separation**  $q$  on an ideal capacitor is proportional to the voltage drop  $v$  across the capacitor



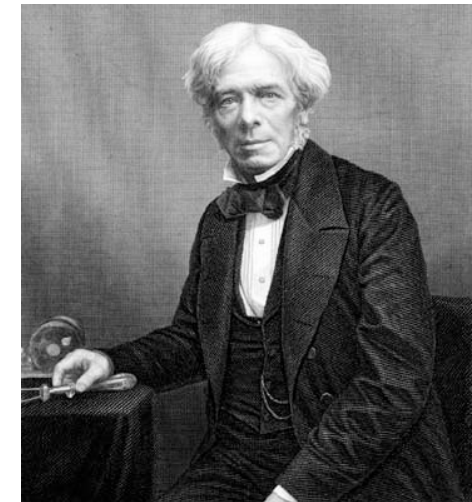
- the capacitor is a *passive* circuit element
- the constant of proportionality between charge and voltage is the **capacitance**, given the symbol  $C$
- SI unit of capacitance is the Farad (abbreviated F)  
 $1 \text{ F} = 1 \text{ C} / \text{V} = 1 \text{ A s} / \text{V}$




Michael Faraday  
(1791-1867)
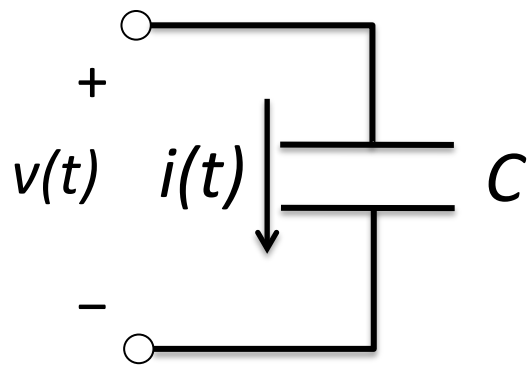
# the capacitor


Although an insulator separates the conductors, a current  $i$  equal to the time rate of change of charge separation  $q$  can flow “through” the capacitor



$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

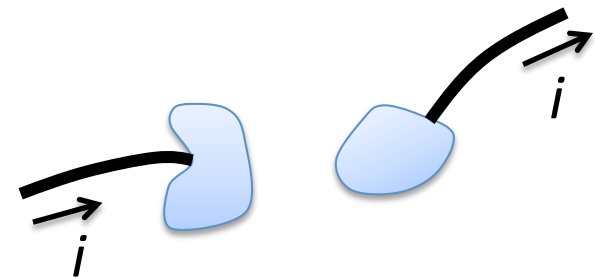


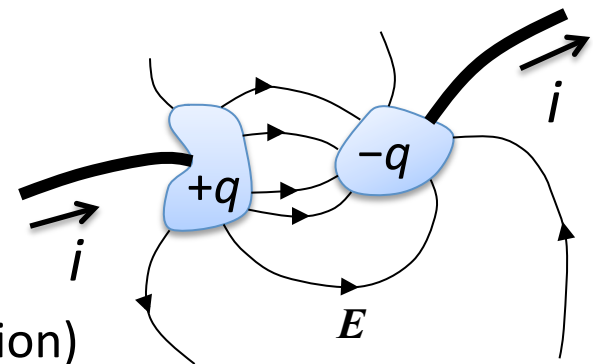- the voltage  $v$  and current  $i$  are defined above to satisfy **passive sign convention**
- the voltage  $v$  and current  $i$  are related to each other by a linear operator (differentiation / integration)


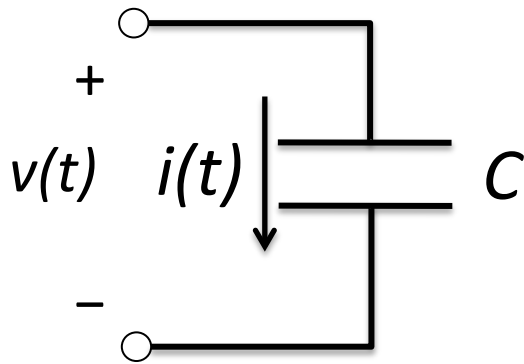
# the capacitor

There are alternative but equivalent forms of the equations describing terminal behaviour of ideal capacitors.



differential form:


$$i = C \frac{dv}{dt} = \frac{dq}{dt}$$

integral form:

$$v(t) - v(t_0) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau = \frac{q(t) - q(t_0)}{C}$$
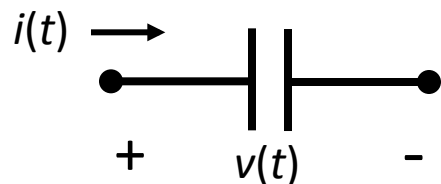
# energy storage in the capacitor

Consider the energy *stored* in a capacitor. The instantaneous power *absorbed* (note the *passive sign convention*) by a capacitor is:



$$p(t) = i(t) \cdot v(t) = C \frac{dv(t)}{dt} v(t)$$

The energy absorbed by the capacitor from time  $t_0$  to time  $t$  is:

$$W_{t_0 \rightarrow t} = \int_{t_0}^t p(t') dt' = \int_{t_0}^t C v(t') \frac{dv(t')}{dt'} dt' = \int_{v(t_0)}^{v(t)} C v(t') dv(t') = \frac{1}{2} C v^2(t) - \frac{1}{2} C v^2(t_0)$$

The energy absorbed is *stored* as electric potential energy  $U(t)$ :


$$U(t) = \frac{1}{2} C v^2(t) = \frac{1}{2} \frac{q^2(t)}{C} \quad W_{t_0 \rightarrow t} = U(t) - U(t_0)$$


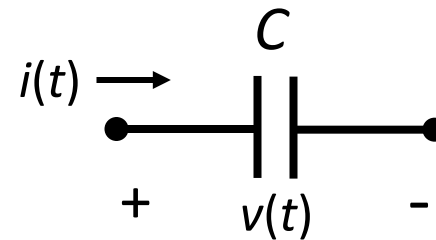
# continuity of capacitor voltage


The current flow through a capacitor is:

$$i = C \frac{dv}{dt} = C \lim_{\Delta t \rightarrow 0} \frac{v(t + \Delta t) - v(t)}{\Delta t}$$



where we restate the definition of the derivative.

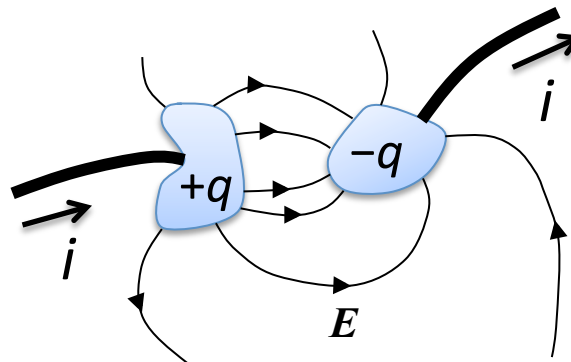
An instantaneous change in capacitor voltage (and charge separation) requires an infinite (unphysical) current. *For a finite current to flow, we require that the capacitor voltage  $v(t)$  is **continuous**.*


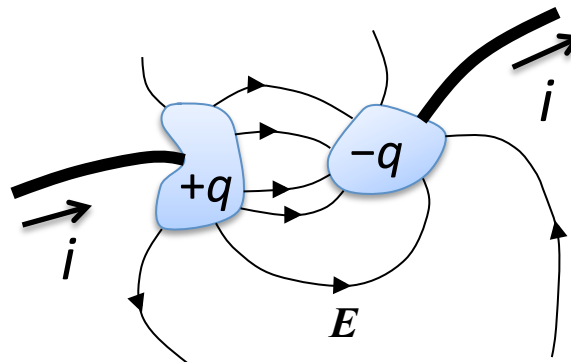
# continuity of capacitor voltage


Continuity of capacitor voltage ensures that:

- the current  $i$  is finite
- the power absorbed  $p = iv$  by the capacitor is finite
- the charge separation  $q$  is continuous, satisfying the **conservation of charge**
- the electric energy stored  $U = \frac{1}{2} Cv^2$  is continuous, satisfying the **conservation of energy**




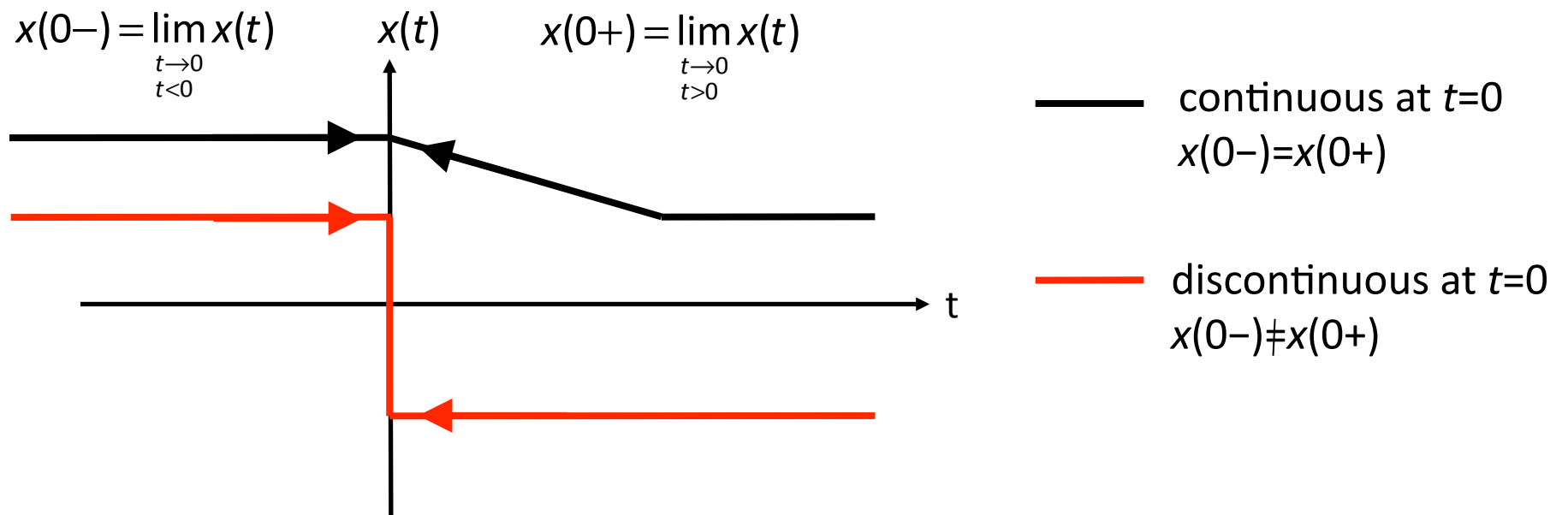
# a note on notation

The notations  $t = 0+$  and  $t = 0-$  are often used in circuit analysis. The value of a circuit variable  $x(t)$  as  $t$  approaches 0 from the past (left) or from the future (right) are identified separately:



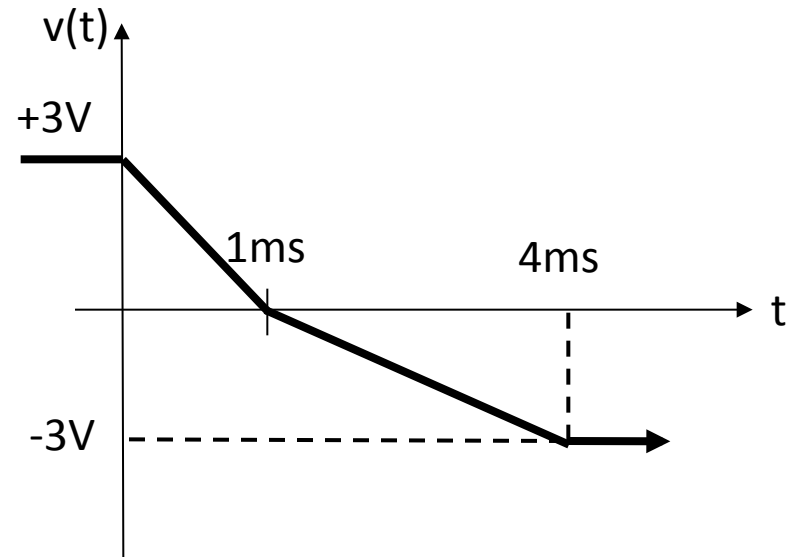
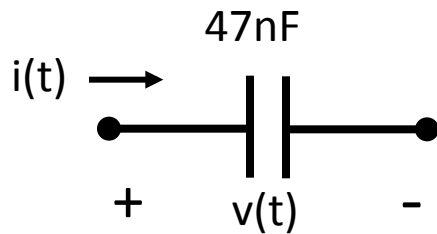
# Example 1

A 47nF capacitor has a voltage across its terminals given by the following diagram. Plot the charge separation and current as a function of time.


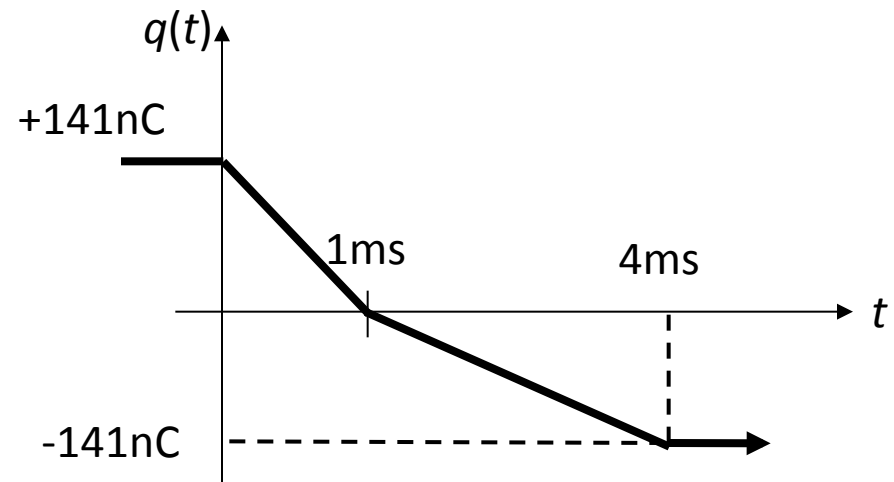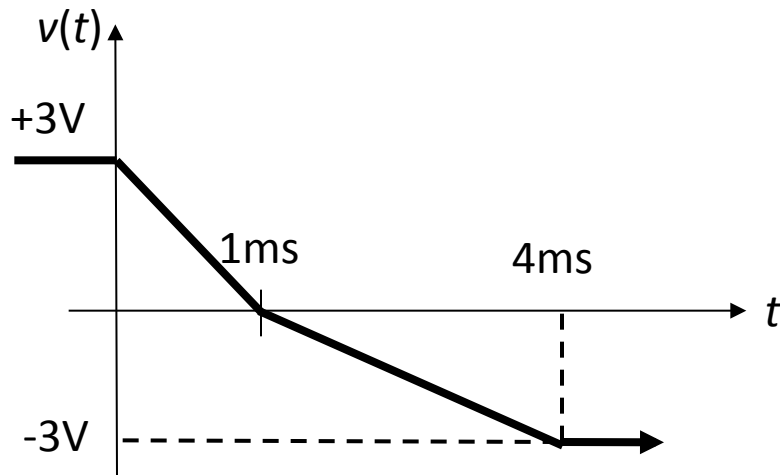
# Example 1

Charge separation is given by  $q(t) = C v(t)$ :  $47\text{nF} \times 3\text{V} = 141\text{nC}$




Current is given by  $i(t) = dq/dt$ , the slope of the charge-time plot:

$$t < 0\text{ms} : dq/dt = 0\text{A}$$

$$0 < t < 1\text{ms} : dq/dt = -141\mu\text{A}$$


$$1\text{ms} < t < 4\text{ms} : dq/dt = -47\mu\text{A}$$

$$4\text{ms} < t : dq/dt = 0\text{A}$$


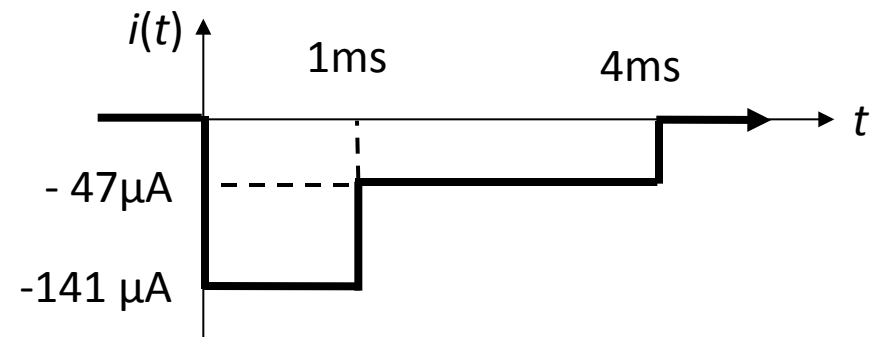

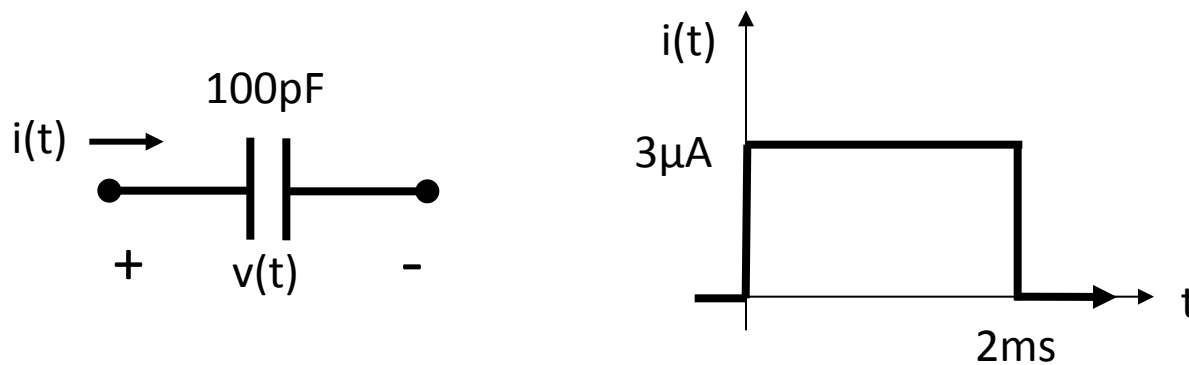
## Example 2

A 100pF capacitor, initially uncharged, passes a current given in the diagram below. Plot the voltage as a function of time.



## Example 2

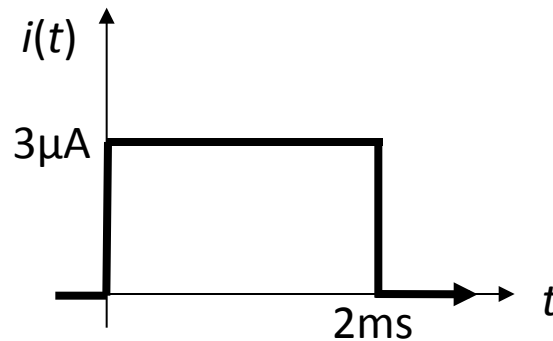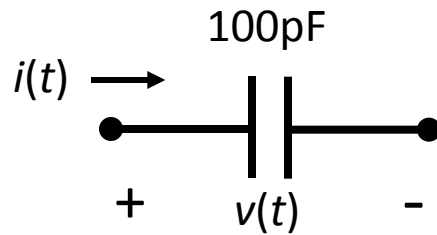


Use the integral form of the capacitor i-v relationship:

$$v(t) - v(0) = \frac{1}{C} \int_0^t i(t') dt'$$

$$v(t) - 0V = \frac{1}{100\text{pF}} \int_0^t 3\mu\text{A} dt' = 30 \frac{\text{kV}}{\text{s}} \cdot t \quad 0 < t < 2\text{ms}$$


$\therefore$
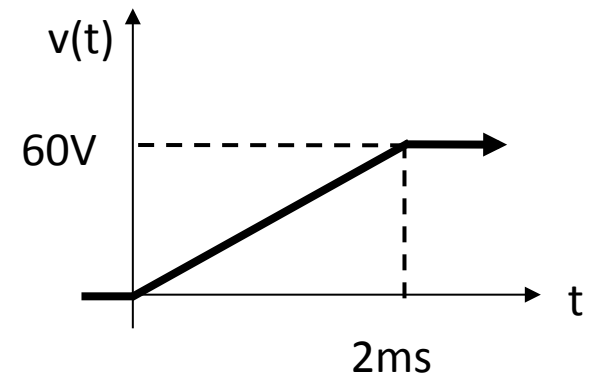
$$v(t) - 0V = 60V + \frac{1}{100\text{pF}} \int_{2\text{ms}}^t 0 dt' = 60V \quad 2\text{ms} < t$$


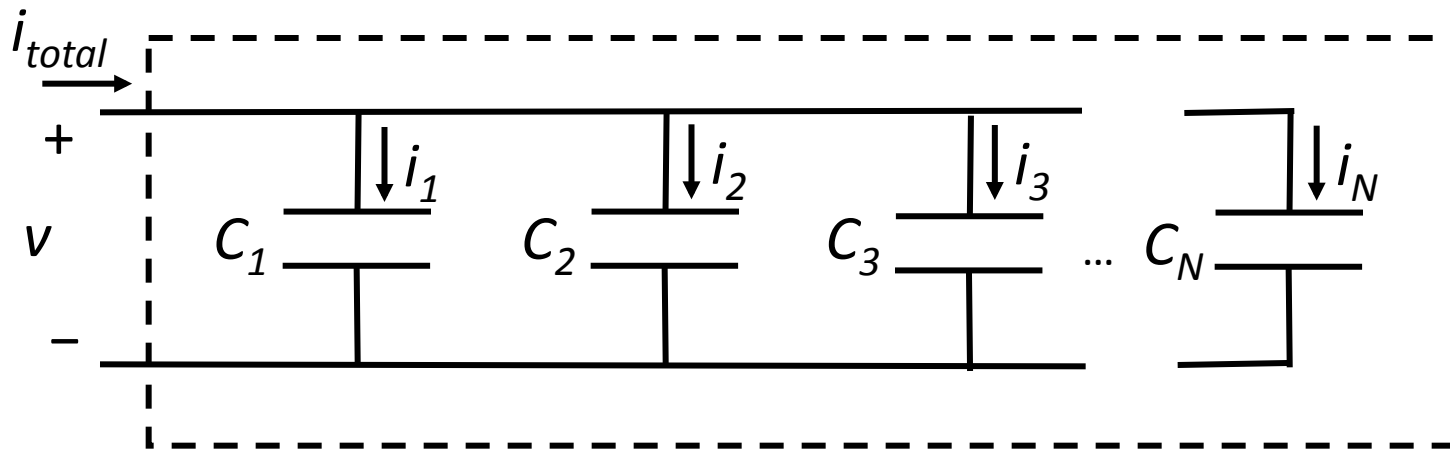
# capacitors in parallel

A parallel combination of capacitors has an equivalent capacitance  $C_{eq}$ .



Current through each capacitor:  $i_m = C_m dv/dt$


Total current (KCL):  $i_{total} = i_1 + i_2 + \dots + i_N = (C_1 + C_2 + \dots + C_N) dv/dt$

Equivalent capacitance:  $\frac{i_{total}}{dv/dt} = C_{eq} = C_1 + C_2 + \dots + C_N$


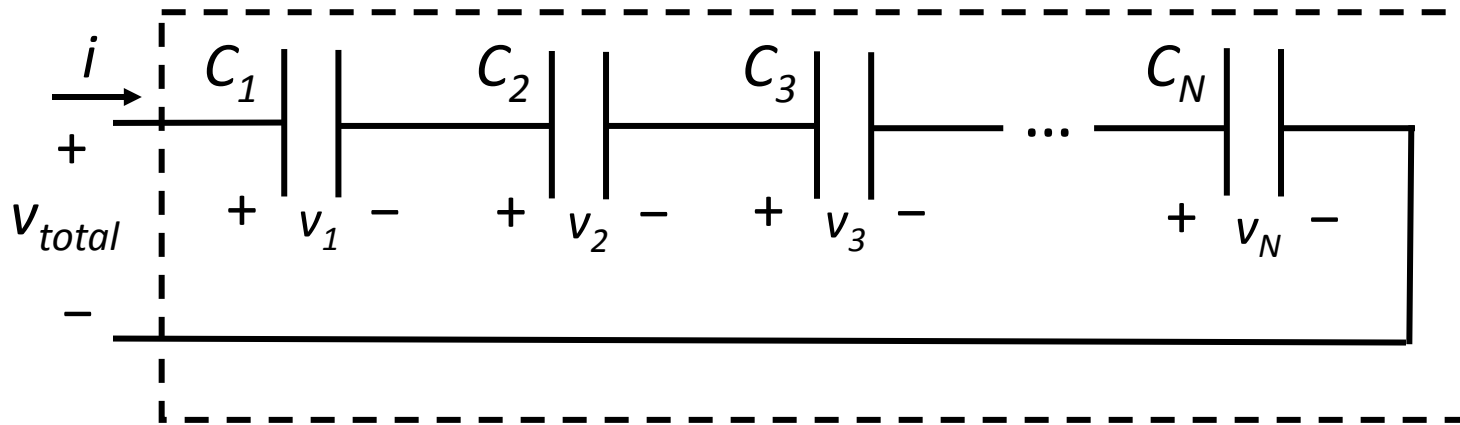
# capacitors in series

A series combination of capacitors has an equivalent capacitance  $C_{eq}$ .



Current through each capacitor:  $i = C_m dv_m/dt$

Total voltage:

(time derivative of KVL)

$$\frac{dv_{total}}{dt} = \frac{dv_1}{dt} + \frac{dv_2}{dt} + \dots + \frac{dv_N}{dt} = i \left( \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right)$$

Equivalent capacitance:

$$\frac{dv_{total}/dt}{i} = \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

# practical capacitors


There is a very wide variety of capacitors, each with characteristics (capacitance range, breakdown voltage, polarity, dielectric leakage, price) that distinguish them for different applications.




**electrolytic capacitors:** large C / volume, polarity due to electrolyte, low cost, high leakage, high dielectric loss



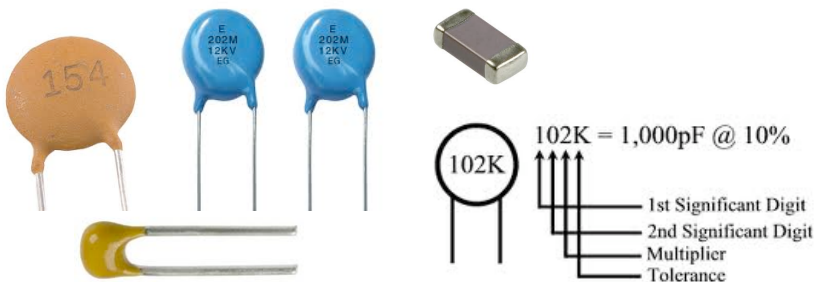**thin-film capacitors:** different polymer films with different temp. and humidity stability, moderate C / volume, very low dielectric loss, low leakage



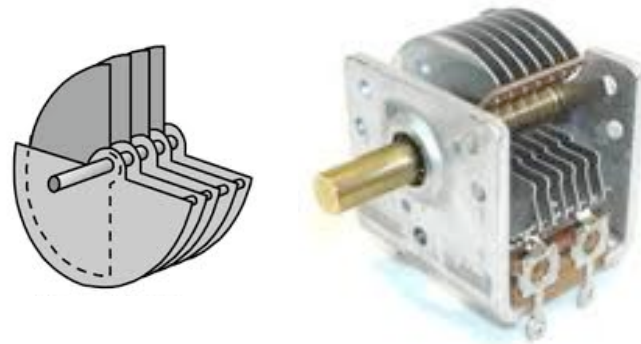**ceramic capacitors:** different ceramics with different temp. stability, moderate C / volume, high dielectric loss, usually low cost



**variable capacitors:** low C / volume, low leakage, high cost