



Electric Circuits 1
ECSE-200 Section: 1

15 December 2014, 9:00AM


Examiner: Thomas Szkopek

Assoc Examiner: Martin Rochette

INSTRUCTIONS:


- This is a **CLOSED BOOK** examination.
- **NO CRIB SHEETS** are permitted.
- Provide your answers in an **EXAM BOOKLET**.
- **STANDARD CALCULATOR** permitted ONLY.
- This examination consists of 4 questions, with a total of 6 pages, including the cover page.
- This examination is **PRINTED ON BOTH SIDES** of the paper

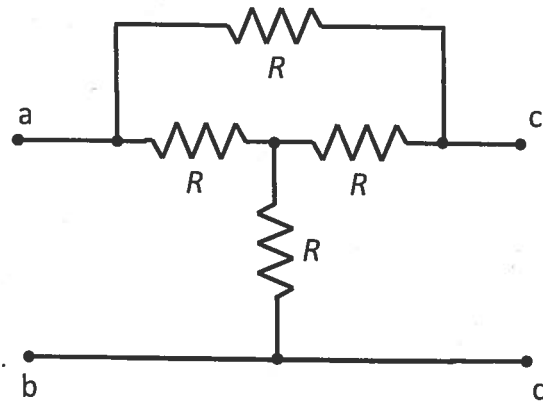1. Consider the circuit below. Answer the questions. [12 pts]




- a) What is the definition of a passive element? [1pt]
- b) What is the definition of a linear element? [1pt]
- c) What is the physical law at the origin of Kirchhoff's current law? [1pt]
- d) What is the physical law at the origin of Kirchhoff's voltage law? [1pt]
- e) What is the equivalent resistance between terminals a and b, if there is an open circuit between the terminals c and d ? [2pts]
- f) What is the equivalent resistance between terminals a and b, if there is a short circuit attached between the terminals c and d ? [2pts]
- g) What is the equivalent resistance between terminals a and b, if a resistance R is attached between the terminals c and d ? [2pts]
- h) What is the equivalent resistance between terminals a and b, if a resistance $2R$ is attached between the terminals c and d ? [2pts]

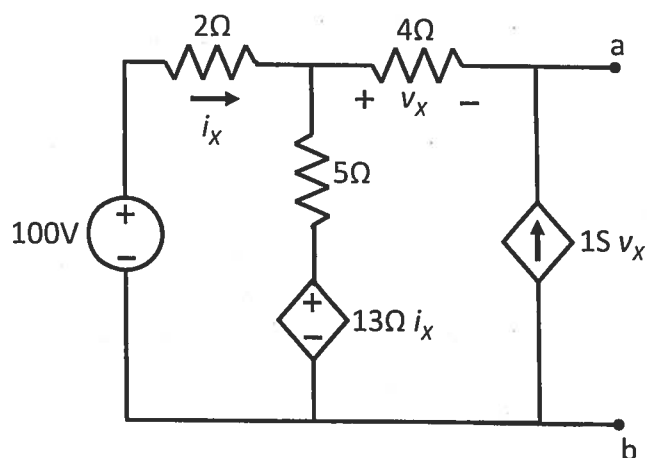2. Consider the circuit below. Answer the questions. [12 pts]



- a) What is Thévenin's theorem? [1pt]
- b) Draw the Thévenin equivalent circuit with respect to terminals a and b. Be sure to label the terminals a and b in your diagram. [5pts]
- c) What is the maximum power that can be delivered to an optimally chosen load resistor attached to the terminals a and b? [2pts]
- d) A load resistor R is attached to the terminals a and b. What are the two values of R that will cause a power of 1kW to be absorbed by R ? [4pts]

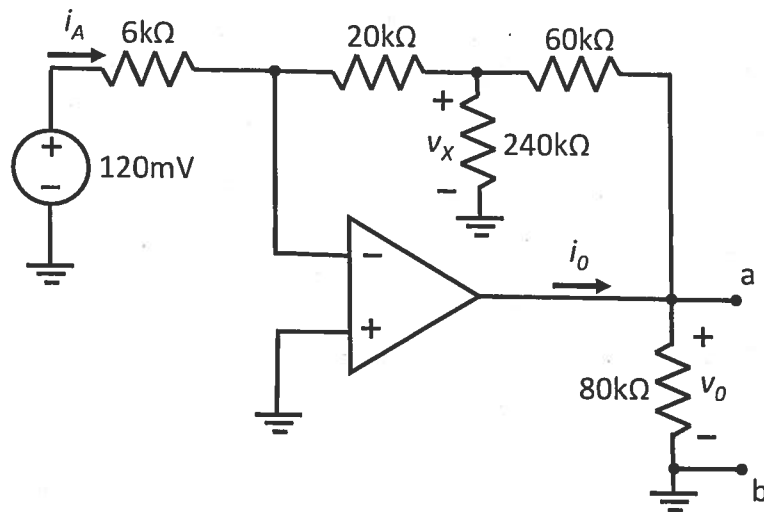3. Consider the circuit below. Assume ideal op-amp behaviour. Answer the questions. [12 pts]



a) Give one reason why negative feedback is used in op-amp circuits. [2pts]

b) What is the current i_A ? [2pts]

c) What is the voltage v_x ? [2pts]

d) What is the voltage v_o ? [1pt]

e) What is the current i_o ? [1pt]



f) How much power does the op-amp deliver? [2pts]

For parts g) and h), a voltmeter with $80\text{k}\Omega$ internal resistance is connected to the terminals a and b.

g) What is the voltage measured by the voltmeter? [1pt]

h) How much power does the op-amp deliver? [1pt]

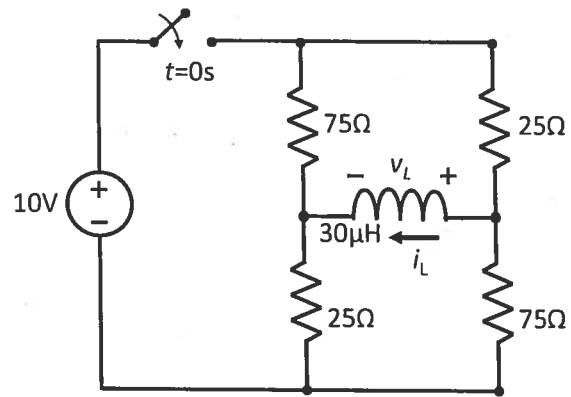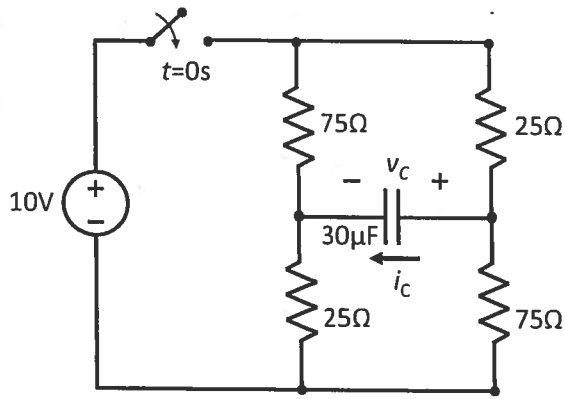4. Consider the circuits below. The switches are open for $t < 0$ s, and close instantaneously at $t = 0$ s. Assume dc steady state behaviour for $t < 0$. Answer the questions. [12 pts]



- What is the voltage $v_c(t)$ for $t > 0$? Plot your solution for $v_c(t)$ versus t . Label your axes. [5pts]
- What is the current $i_L(t)$ for $t > 0$? Plot your solution for $i_L(t)$ versus t . Label your axes. [5pts]
- What is the maximum power absorbed by the capacitor? [1pt]
- What is the maximum power absorbed by the inductor? [1pt]

end


1 a) An element that never delivers more energy to a circuit than it has absorbed from a circuit. [1]

b) An element where terminal current and voltage are related by a linear function or linear operator. [1]

c) Conservation of charge. [1]

d) Conservation of energy. [1]

e)

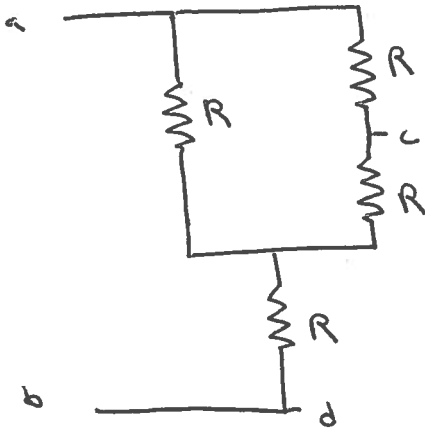


$$R_{ab} = R // (R + R) + R \quad [1]$$

$$= \frac{R \cdot 2R}{R + 2R} + R$$

$$= \frac{5}{3} R \quad [1]$$

f)

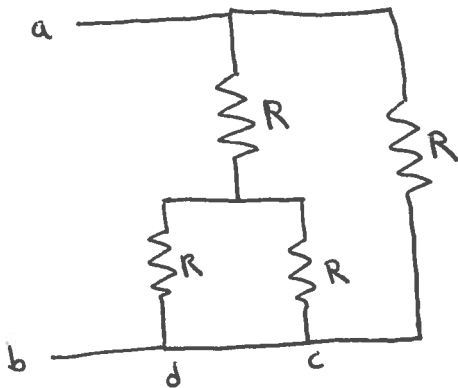


$$R_{ab} = (R + R // R) // R \quad [1]$$

$$= \frac{\frac{3}{2} R \cdot R}{\frac{3}{2} R + R}$$

$$= \frac{3}{5} R \quad [1]$$

g)

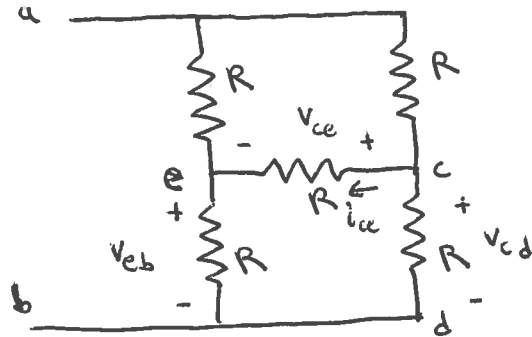


By the symmetry of the network, $v_{cd} = v_{eb}$.

Thus, $v_{ce} = 0V$ by KVL. [+1]

Thus, $i_{ce} = 0A$ by Ohm.

$$\begin{aligned} R_{ab} &= (R+R) // (R+R) \\ &= 2R // 2R \\ &= R \quad [+1] \end{aligned}$$

h)

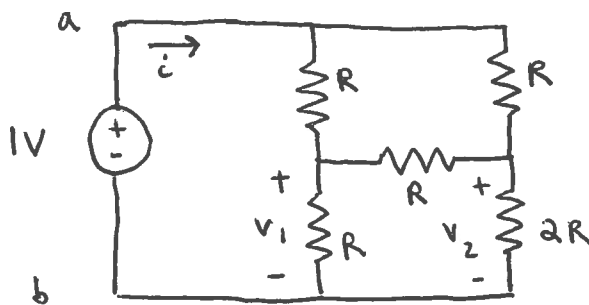

Apply test source. [+1]

$$0 = \frac{v_1}{R} + \frac{v_1 - v_2}{R} + \frac{v_1 - 1V}{R}$$

$$0 = \frac{v_2}{2R} + \frac{v_2 - v_1}{R} + \frac{v_2 - 1V}{R}$$

$$1 = 3v_1 - v_2$$

$$1 = -v_1 + 2.5v_2$$

$$i = \frac{v_1}{R} + \frac{v_2}{2R} = \frac{11}{13} \frac{V}{R}$$


$$v_1 = \frac{\begin{vmatrix} 1 & -1 \\ 1 & 2.5 \end{vmatrix}}{\begin{vmatrix} 3 & -1 \\ -1 & 2.5 \end{vmatrix}} = \frac{7}{13} V$$

$$v_2 = \frac{\begin{vmatrix} 3 & 1 \\ -1 & 1 \end{vmatrix}}{\begin{vmatrix} 3 & -1 \\ -1 & 2.5 \end{vmatrix}} = \frac{8}{13} V$$

$$R_{ab} = \frac{1V}{i} = \frac{13}{11} R \quad [+1]$$

- 2 a) Any circuit with two terminals composed of resistors, dependent sources and independent sources is equivalent to a series combination of one resistor and one independent voltage source. [+1]

b) Find v_{oc} . [+1]

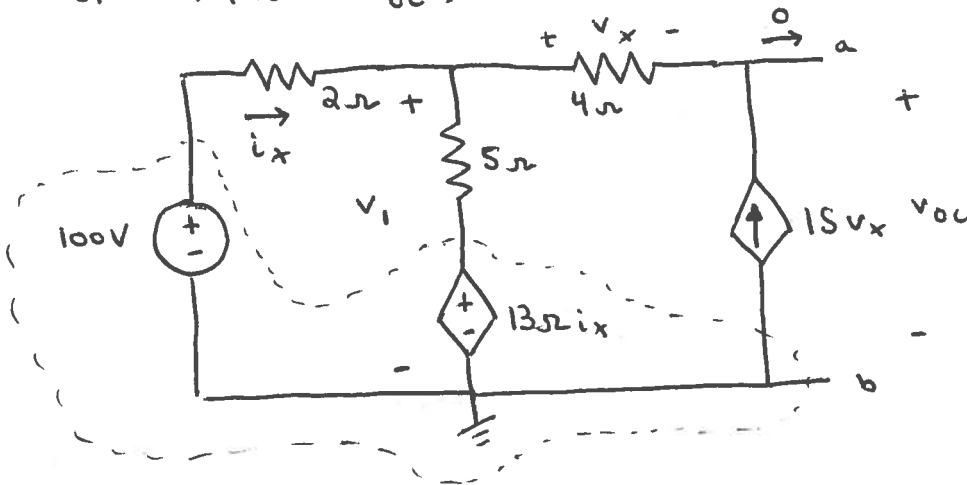

$$0 = \frac{v_1 - 100V}{2\Omega} + \frac{v_1 - 13\Omega i_x}{5\Omega} - 1S v_x$$

$$i_x = \frac{100V - v_1}{2\Omega}$$

$$\frac{v_x}{4\Omega} = -1S v_x \rightarrow v_x = 0V$$


$$\therefore 0 = \frac{v_1 - 100V}{2\Omega} + \frac{v_1 - 13\Omega \left(\frac{100V - v_1}{2\Omega}\right)}{5\Omega} + 0$$

$$\frac{100}{2} + \frac{13 \cdot 100}{2 \cdot 5} = \left(\frac{1}{2} + \frac{1}{5} + \frac{13}{2 \cdot 5} \right) v_1$$

$$v_1 = 90V$$

$$v_{oc} = v_1 - v_x = 90V$$

Find i_{sc} [1]

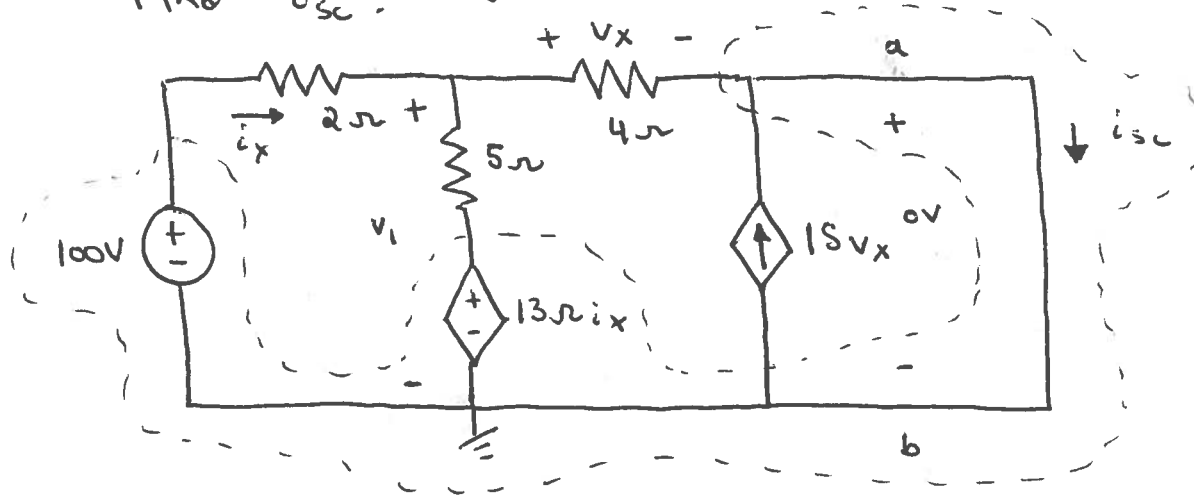

$$0 = \frac{v_1 - 100V}{2\Omega} + \frac{v_1 - 13\Omega i_x}{5\Omega} + \frac{v_1}{4\Omega}$$

$$i_x = \frac{100V - v_1}{2\Omega}$$

$$\therefore 0 = \frac{v_1 - 100V}{2\Omega} + \frac{v_1 - 13\Omega \left(\frac{100V - v_1}{2\Omega} \right)}{5\Omega} + \frac{v_1}{4\Omega}$$

$$\frac{100}{2} + \frac{13 \cdot 100}{2 \cdot 5} = \left(\frac{1}{2} + \frac{1}{5} + \frac{13}{2 \cdot 5} + \frac{1}{4} \right) v_1$$


$$v_1 = 80V$$

$$v_x = v_1 = 80V$$

$$i_{sc} = \frac{v_x}{4\Omega} + 1S v_x = 100A$$

$$R_T = \frac{V_{oc}}{i_{sc}} \quad [1]$$


$$= \frac{90V}{100A} = 0.9\Omega$$

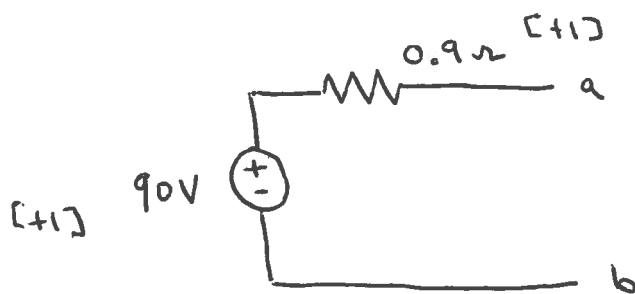

c) $P_{max} = \frac{V_{oc}}{2} \cdot \frac{i_{sc}}{2} \quad [+1]$

$$= \frac{90V \cdot 100A}{4}$$

$$= 2.250 \text{ kW} \quad [+1]$$

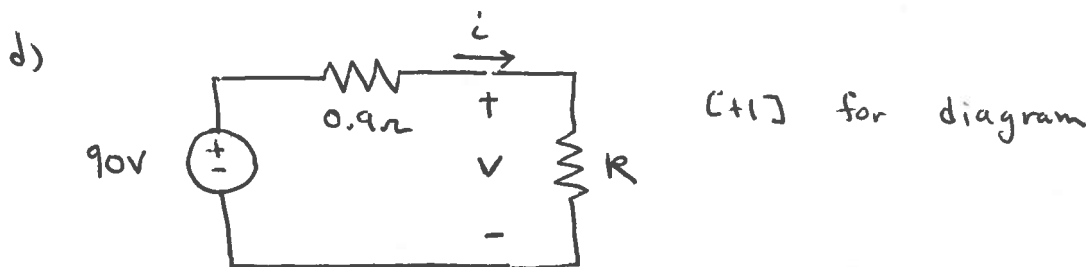

$$V = 90V - 0.9\Omega \cdot i$$

$$Vi = 1000 \text{ W} \quad [+1]$$

$$\therefore V = 90 - 0.9 \left(\frac{1000}{V} \right)$$

$$V^2 = 90V - 900$$

$$0 = V^2 - 90V + 900$$

$$V = \frac{90 \pm \sqrt{(90)^2 - 4 \cdot 1 \cdot 900}}{2} = 78.54 \text{ V}, 11.46 \text{ V}$$


$$i = 1000 \text{ W} / V = 12.73 \text{ A}, 87.27 \text{ A}$$

$$R = V / i = 6.17 \Omega, 0.131 \Omega \quad [+2]$$

3

a) stability
programmable gain

[+1] for any acceptable answer

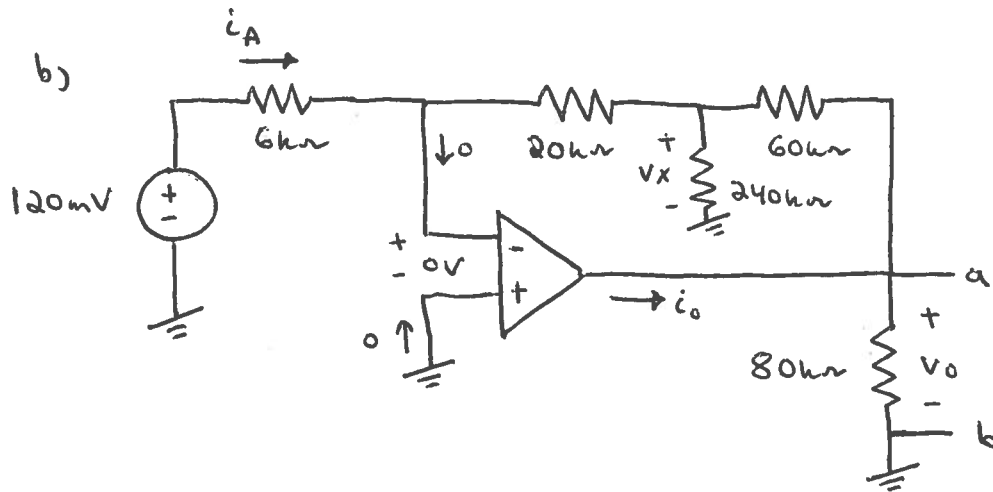

$$i_A = \frac{120\text{mV}}{6\text{k}\Omega} = 20\mu\text{A} \quad [+2]$$

$$c) \quad 0 = -i_A + 0 + \frac{0 - V_x}{20\text{k}\Omega} \quad [+1]$$

$$V_x = -20\text{k}\Omega \cdot i_A \\ = -400\text{mV} \quad [+1]$$

$$d) \quad 0 = \frac{V_x}{20\text{k}\Omega} + \frac{V_x}{240\text{k}\Omega} + \frac{V_x - V_o}{60\text{k}\Omega}$$

$$V_o = 60\text{k}\Omega \cdot \left(\frac{1}{20\text{k}\Omega} + \frac{1}{240\text{k}\Omega} + \frac{1}{60\text{k}\Omega} \right) V_x$$

$$= -1.7\text{V} \quad [+1]$$

$$e) \quad 0 = -i_o + \frac{v_o}{80\text{k}\Omega} + \frac{v_o - v_x}{60\text{k}\Omega}$$

$$i_o = -42.92 \mu\text{A} \quad [+1]$$

$$f) \quad P_{\text{del}} = v_o \cdot i_o \quad [+1]$$

$$= (-1.7\text{V}) \cdot (-42.92 \mu\text{A})$$

$$= 72.96 \mu\text{W} \quad [+1]$$

delivered

$$g) \quad v_o' = -1.7\text{V} \quad [+1]$$

$$h) \quad 0 = -i_o' + \frac{v_o'}{80\text{k}\Omega} + \frac{v_o'}{80\text{k}\Omega} + \frac{v_o' - v_x'}{60\text{k}\Omega}$$

$$v_o' = v_o \quad v_x' = v_x$$


$$i_o' = -64.17 \mu\text{A}$$

$$P_{\text{del}}' = v_o' \cdot i_o'$$

$$= 109.1 \mu\text{W} \quad [+1]$$

4 a) $t = 0 \quad v_c(0+) = v_c(0-) = 0V \quad (+1)$

$t \rightarrow \infty$


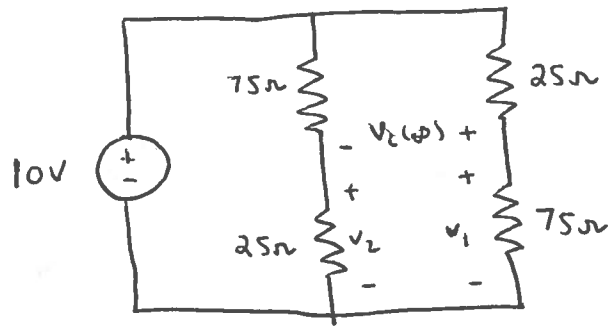


$$v_1 = \frac{10V \cdot 75\Omega}{100\Omega} = 7.5V$$

$$v_2 = \frac{10V \cdot 25\Omega}{100\Omega} = 2.5V$$

$$v_c(\infty) = v_1 - v_2 = 5V \quad (+1)$$

Find τ .

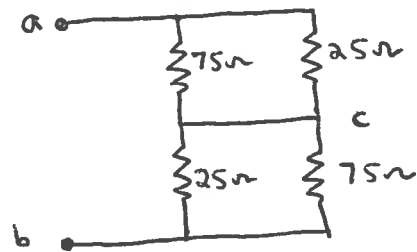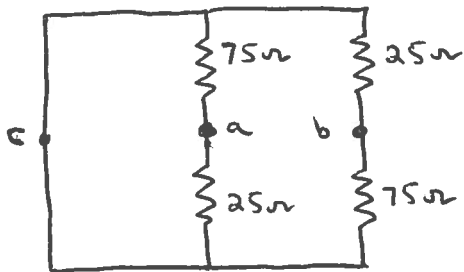


$$R_{TH} = 25\Omega // 75\Omega + 25\Omega // 75\Omega$$

$$= 37.5\Omega$$

$$\tau = R_{TH} \cdot C = 37.5\Omega \cdot 30\mu F = 1.125 \text{ ms} \quad (+1)$$


$$t > 0 \quad v_c(t) = v_c(\infty) + [v_c(0+) - v_c(\infty)] \exp(-t/\tau)$$
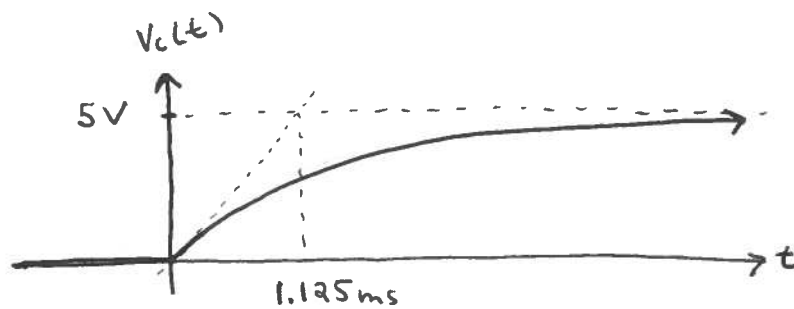
$$= 5V [1 - \exp(-t/1.125\text{ms})] \quad (+1)$$



[+1]

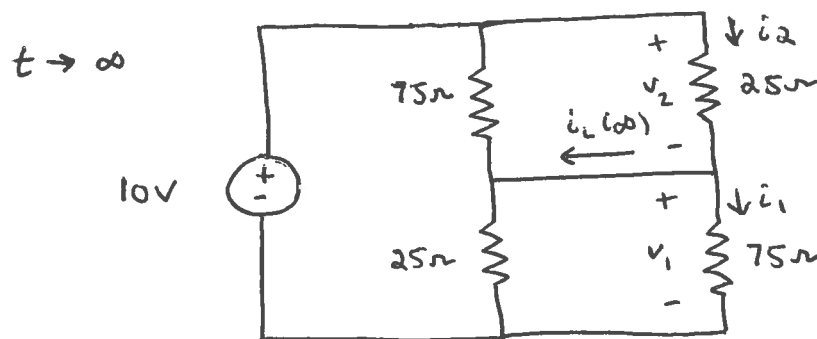b) $t = 0 \quad i_L(0+) = i_L(0-) = 0 \text{ A} \quad [+1]$



$$v_1 = \frac{10\text{V} \cdot 25\Omega // 75\Omega}{25\Omega // 75\Omega + 25\Omega // 75\Omega} = 5\text{V}$$


$$v_2 = \frac{10\text{V} \cdot 25\Omega // 75\Omega}{25\Omega // 75\Omega + 25\Omega // 75\Omega} = 5\text{V}$$

$$i_2 = 5\text{V} / 25\Omega = 0.2\text{A} \quad i_1 = 5\text{V} / 75\Omega = 0.0667\text{A}$$

$$i_L(\infty) = i_2 - i_1 = 0.1333\text{A} \quad [+1]$$

$$\tau = L / R_{TH} = 30\mu\text{H} / 37.5\Omega = 800\text{ns} \quad [+1]$$

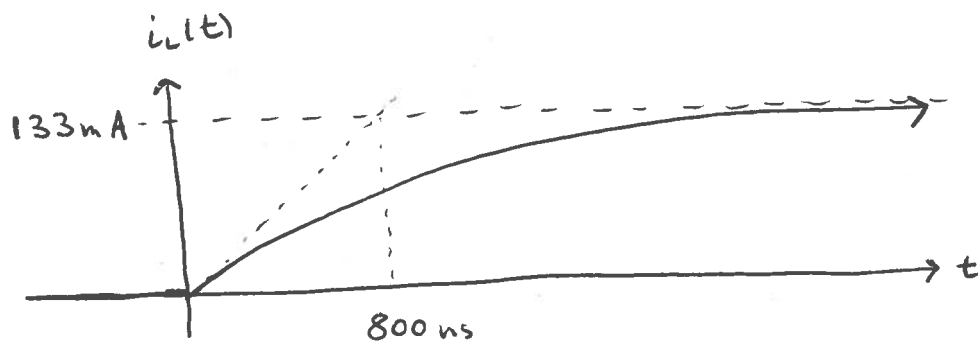
$$\begin{aligned} t > 0 \quad i_L(t) &= i_L(\infty) + [i_L(0+) - i_L(\infty)] \exp(-t/\tau) \\ &= 133\text{mA} [1 - \exp(-t/800\text{ns})] \quad [+1] \end{aligned}$$



$$\begin{aligned}
 c) \quad i_c &= C \frac{dv_c}{dt} = 30 \mu\text{F} \cdot (-5\text{V}) \left(\frac{-1}{1.125 \text{ ms}} \right) \exp(-t/1.125 \text{ ms}) \\
 &= 133 \text{ mA} \exp(-t/1.125 \text{ ms})
 \end{aligned}$$

$$\begin{aligned}
 p_{\text{abs}} &= v_c \cdot i_c \\
 &= 5\text{V} \cdot 133 \text{ mA} (1-x) \cdot x \quad x = \exp(-t/1.125 \text{ ms})
 \end{aligned}$$

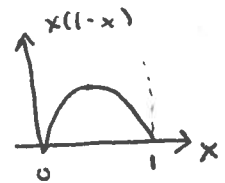Maximum of p_{abs} occurs when $x = 1/2$.



$$\begin{aligned}
 \max(p_{\text{abs}}) &= 5\text{V} \cdot 133 \text{ mA} \cdot 1/4 \\
 &= 167 \text{ mW} \quad [+1]
 \end{aligned}$$

$$\begin{aligned}
 d) \quad v_L &= L \frac{di_L}{dt} = 30 \mu\text{H} \cdot (-133 \text{ mA}) \cdot \left(\frac{-1}{800 \text{ ns}} \right) \exp(-t/800 \text{ ns}) \\
 &= 5\text{V} \exp(-t/800 \text{ ns})
 \end{aligned}$$

$$p_{\text{abs}} = v_L \cdot i_L = 5\text{V} \cdot 133 \text{ mA} \cdot (1-x) \cdot x \quad x = \exp(-t/800 \text{ ns})$$

Maximum of p_{abs} occurs when $x = 1/2$.

$$\max(p_{\text{abs}}) = 5\text{V} \cdot 133 \text{ mA} \cdot 1/4 = 167 \text{ mW} \quad [+1]$$