

ECSE 200 - Electric Circuits 1


Problem set 9

ECE Dept., McGill University

Part 1: Capacitors

Capacitor Recap

- Charge separation of a capacitor: $q(t) = Cv(t)$ (Coulomb)
- Current: $i(t) = \frac{\partial q(t)}{\partial t} = C \frac{\partial v(t)}{\partial t}$ (A)
- Voltage difference: $v(t_1) - v(t_0) = \frac{1}{C} \int_{t_0}^{t_1} i(t) \partial t$ (V)
- Power: $p(t) = i(t)v(t) = C \frac{v(t)\partial v(t)}{\partial t}$ (W)
- Energy: $E(t) = \int_{t_0}^{t_1} p(t) \partial t = C \int_{v(t_0)}^{v(t_1)} v(t) \partial v(t) = \frac{Cv^2(t)}{2} \Big|_{t_0}^{t_1}$ (J)

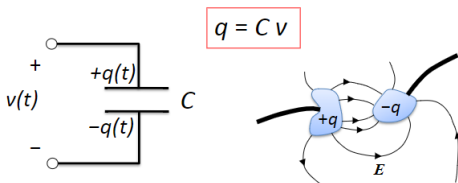

Problem P 7.2-1

A $15\text{-}\mu\text{F}$ capacitor has a voltage of 5 V across it at $t = 0$. If a constant current of 25 mA flows through the capacitor, how long will it take for the capacitor to charge up to $150\text{ }\mu\text{C}$?

Problem P 7.2-1

A $15\text{-}\mu\text{F}$ capacitor has a voltage of 5 V across it at $t = 0$. If a constant current of 25 mA flows through the capacitor, how long will it take for the capacitor to charge up to $150\text{ }\mu\text{C}$?

Solution:
$$v(t) = v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau \quad \text{and} \quad q = Cv$$

In our case, the current is constant so
$$i t = \int_0^t i(\tau) d\tau .$$

$$\therefore Cv(t) = Cv(0) + i t$$

$$\therefore t = \frac{q - Cv(0)}{i} = \frac{150 \times 10^{-6} - (15 \times 10^{-6})(5)}{25 \times 10^{-3}} = \underline{3\text{ ms}}$$

Problem P 7.2-4

Determine $v(t)$ for the circuit shown in Figure P 7.2-4a when the $i_s(t)$ is as shown in Figure P 7.2-4b and $v_0(0^-) = -1$ mV.

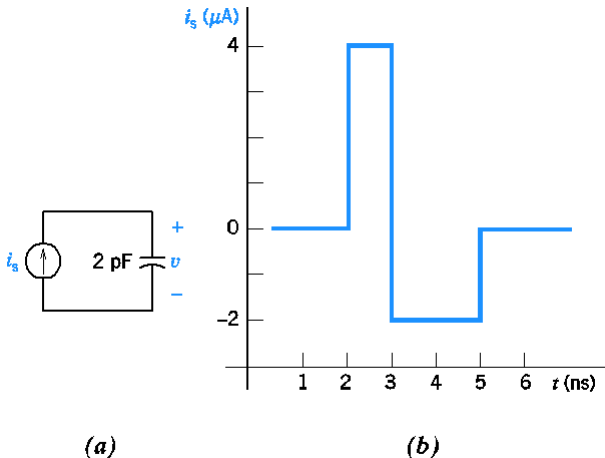


Figure P 7.2-4

Problem P 7.2-4

Solution:

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0) = \frac{1}{2 \times 10^{-12}} \int_0^t i(\tau) d\tau - 10^{-3}$$

$$0 < t < 2 \times 10^{-9}$$

$$i_s(t) = 0 \Rightarrow v(t) = \frac{1}{2 \times 10^{-12}} \int_0^t 0 d\tau - 10^{-3} = -10^{-3}$$

$$2 \times 10^{-9} < t < 3 \times 10^{-9}$$

$$i_s(t) = 4 \times 10^{-6} \text{ A}$$

$$\Rightarrow v(t) = \frac{1}{2 \times 10^{-12}} \int_{2\text{ns}}^t (4 \times 10^{-6}) d\tau - 10^{-3} = -5 \times 10^{-3} + (2 \times 10^6) t$$

$$\text{In particular, } v(3 \times 10^{-9}) = -5 \times 10^{-3} + (2 \times 10^6)(3 \times 10^{-9}) = 10^{-3}$$

$$3 \times 10^{-9} < t < 5 \times 10^{-9}$$

$$i_s(t) = -2 \times 10^{-6} \text{ A}$$

$$\Rightarrow v(t) = \frac{1}{2 \times 10^{-12}} \int_{3\text{ns}}^t (-2 \times 10^{-6}) d\tau + 10^{-3} = 4 \times 10^{-3} - (10^6) t$$

$$\text{In particular, } v(5 \times 10^{-9}) = 4 \times 10^{-3} - (10^6)(5 \times 10^{-9}) = -10^{-3} \text{ V}$$

$$5 \times 10^{-9} < t$$

$$i_s(t) = 0 \Rightarrow v(t) = \frac{1}{2 \times 10^{-12}} \int_{5\text{ns}}^t 0 d\tau - 10^{-3} = -10^{-3} \text{ V}$$

Problem P 7.2-8

Find i for the circuit of Figure P 7.2-8 if $v = 5(1 - 2e^{-2t})$ V.


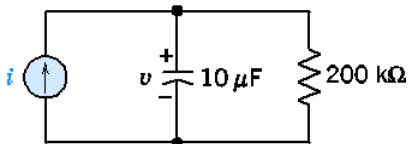


Figure P 7.2-8

Problem P 7.2-8

Solution:

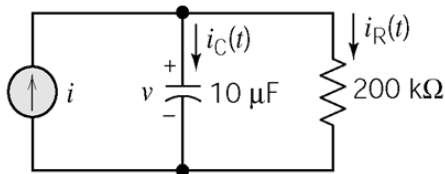

$$i_R = \frac{v}{200 \times 10^3} = \frac{1}{40} (1 - 2e^{-2t}) \times 10^{-3} = 25 (1 - 2e^{-2t})\ \mu\text{A}$$

$$i_C = C \frac{dv}{dt} = (10 \times 10^{-6}) (-2) (-10 e^{-2t}) = 200 e^{-2t}\ \mu\text{A}$$

$$\begin{aligned} i &= i_R + i_C = 200 e^{-2t} + 25 - 50 e^{-2t} \\ &= \underline{25 + 150 e^{-2t}}\ \mu\text{A} \end{aligned}$$

Problem P 7.2-14

The capacitor voltage in the circuit shown in Figure P 7.2-14 is given by

$$v(t) = 10 - 8e^{-5t} \text{ V} \quad \text{for } t \geq 0$$

Determine $i(t)$ for $t > 0$.

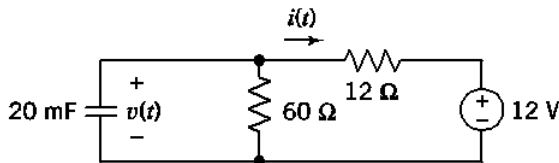


Figure P 7.2-14

Problem P 7.2-14

The capacitor voltage in the circuit shown in Figure P 7.2-14 is given by

$$v(t) = 10 - 8e^{-5t} \text{ V} \quad \text{for } t \geq 0$$

Determine $i(t)$ for $t > 0$.

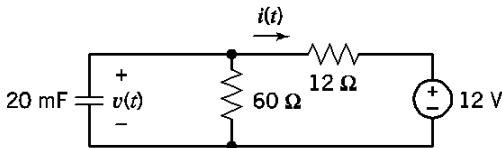


Figure P 7.2-14

Solution: Apply KVL to the outside loop to get

$$12i(t) + 12 - v(t) = 0 \Rightarrow i(t) = \frac{12 - 10 - 8e^{-5t}}{12} = -\frac{1}{6} - \frac{2}{3}e^{-5t} \text{ A} \quad \text{for } t > 0$$

Part 2: Energy Storage in a Capacitor

Problem P 7.3-2

In a pulse power circuit the voltage of a $10\text{-}\mu\text{F}$ capacitor is zero for $t < 0$ and

$$v = 5(1 - e^{-4000t})\text{V } t \geq 0.$$

Determine the capacitor current and the energy stored in the capacitor at $t = 0$ ms and $t = 10$ ms.

Problem P 7.3-2

In a pulse power circuit the voltage of a $10\text{-}\mu\text{F}$ capacitor is zero for $t < 0$ and

$$v = 5(1 - e^{-4000t}) \text{ V} \quad t \geq 0$$

Determine the capacitor current and the energy stored in the capacitor at $t = 0$ ms and $t = 10$ ms.

Solution:

$$i_c = C \frac{dv}{dt} = (10 \times 10^{-6})(-5)(-4000)e^{-4000t} = \underline{0.2e^{-4000t} \text{ A}} \Rightarrow \begin{cases} \underline{i_c(0) = 0.2 \text{ A}} \\ \underline{i_c(10\text{ms}) = 8.5 \times 10^{-19} \text{ A}} \end{cases}$$

$$w(t) = \frac{1}{2} C v^2(t) \quad \text{and} \quad v(0) = 5 - 5e^0 = 0 \Rightarrow \underline{w(0) = 0}$$

$$v(10 \times 10^{-3}) = 5 - 5e^{-40} = 5 - 21.2 \times 10^{-18} \cong 5 \Rightarrow \underline{w(10) = 1.25 \times 10^{-4} \text{ J}}$$

Problem P 7.3-3

If $v_c(t)$ is given by the waveform shown in Figure P 7.3-3, sketch the capacitor current for $-1\text{ s} \leq t \leq 2\text{ s}$. Sketch the power and the energy for the capacitor over the same time interval when $C = 1\text{ mF}$.

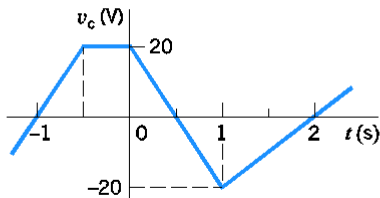


Figure P 7.3-3

Problem P 7.3-3 (Solution)

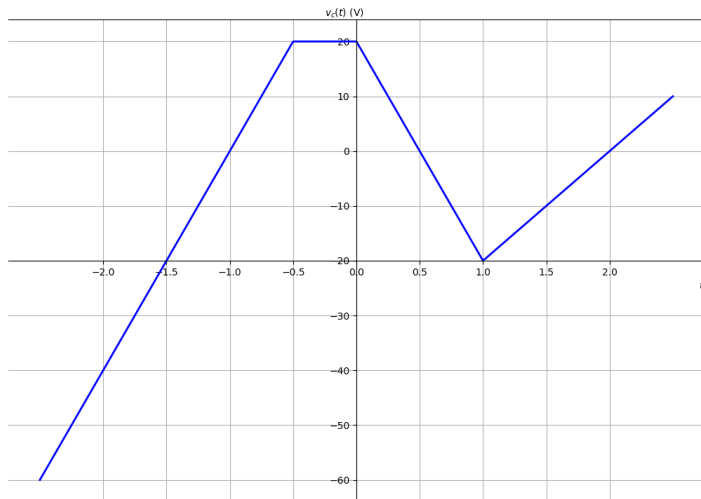


Figure: $v(t)$

Problem P 7.3-3 (Solution-cnt.)

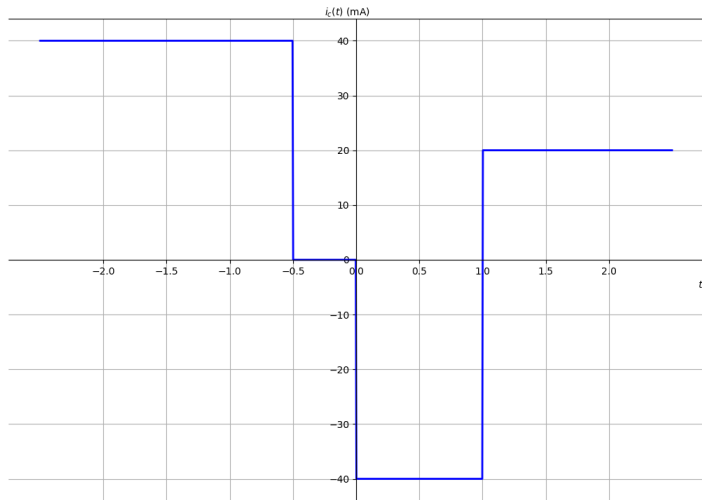


Figure: $i(t)$

Problem P 7.3-3 (Solution-cnt.)

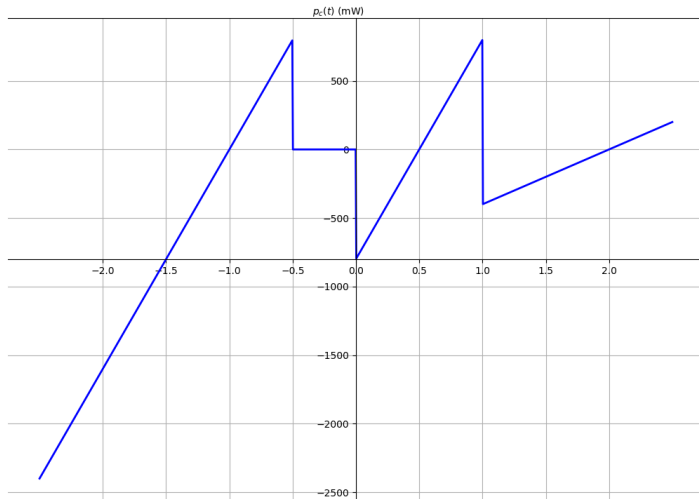


Figure: $p(t)$

Problem P 7.3-3 (Solution-cnt.)

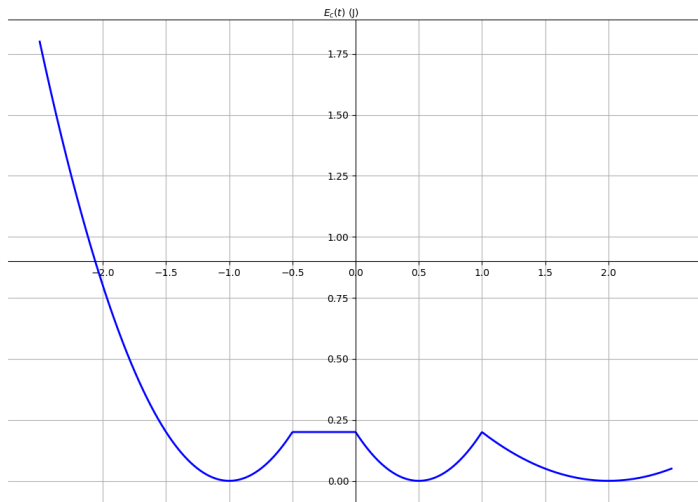


Figure: $E(t)$

Part 3: Series and Parallel Capacitors

Problem P 7.4-1

Find the current $i(t)$ for the circuit of Figure P 7.4-1.

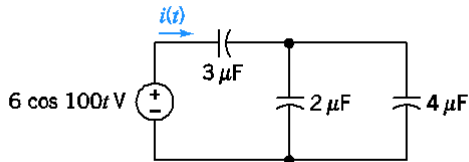


Figure P 7.4-1

Problem P 7.4-1

Find the current $i(t)$ for the circuit of Figure P 7.4-1.

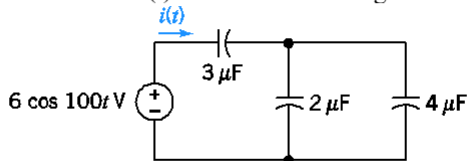


Figure P 7.4-1

Solution:

$$2 \mu\text{F} \parallel 4 \mu\text{F} = 6 \mu\text{F}$$

$$6 \mu\text{F} \text{ in series with } 3 \mu\text{F} = \frac{6 \mu\text{F} \cdot 3 \mu\text{F}}{6 \mu\text{F} + 3 \mu\text{F}} = 2 \mu\text{F}$$

$$i(t) = 2 \mu\text{F} \frac{d}{dt} (6 \cos 100t) = (2 \times 10^{-6}) (6) (100) (-\sin 100t) \text{ A} = \underline{\underline{-1.2 \sin 100t \text{ mA}}}$$

Problem P 7.4-7

The circuit shown in Figure P 7.4-7 consists of nine capacitors having equal capacitance, C . Determine the value of the capacitance C , given that $C_{eq} = 50 \text{ mF}$.


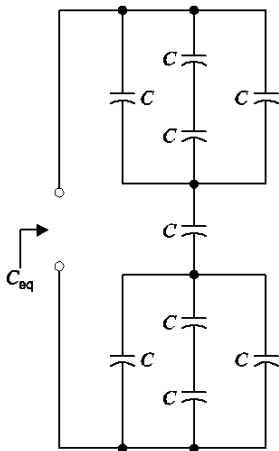


Figure P 7.4-7

Problem P 7.4-7

Solution: First

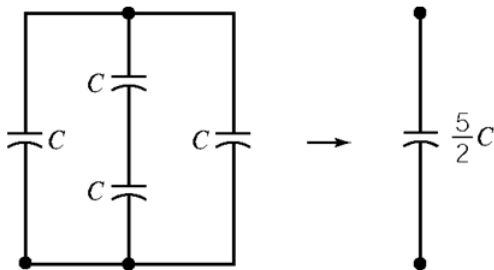


Then

$$50 = C_{\text{eq}} = \frac{1}{\frac{1}{C} + \frac{2}{5C} + \frac{2}{5C}} \Rightarrow C = 90 \text{ mF}$$

Part 4: Inductors

Inductor Recap

- Magnetic flux: $\lambda(t) = Li(t)$ (HA)
- Voltage (Faraday's law of inductor): $v(t) = \frac{\partial \lambda(t)}{\partial t} = \frac{L \partial i(t)}{\partial t}$ (V)
In words: the voltage drop across an inductor is proportional to the rate of change of the total magnetic flux passing through the inductor.
- Current difference: $i(t_1) - i(t_0) = \frac{1}{L} \int_{t_0}^{t_1} v(t) \partial t$ (A)
- Power: $p(t) = i(t)v(t) = L \frac{i(t) \partial i(t)}{\partial t}$ (W)
- Energy: $E(t) = \int_{t_0}^{t_1} p(t) \partial t = L \int_{i(t_0)}^{i(t_1)} i(t) \partial i(t) = \frac{Li^2(t)}{2} \Big|_{t_0}^{t_1}$ (J)

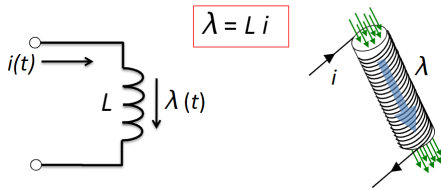


Problem P 7.5-1

Nikola Tesla (1857–1943) was an American electrical engineer who experimented with electric induction. Tesla built a large coil with a very large inductance. The coil was connected to a source current

$$i_s = 100 \sin(400t) \text{ A}$$

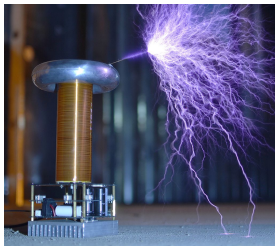so that the inductor current $i_L = i_s$. Find the voltage across the inductor and explain the discharge in the air shown in the figure. Assume that $L = 200 \text{ H}$ and the average discharge distance is 2 m. Note that the dielectric strength of air is $3 \times 10^6 \text{ V/m}$. [▶ Link](#)



Problem P 7.5-1

Solution

Find max. voltage across coil: $v(t) = L \frac{di}{dt} = 200 [100(400) \cos 400t] \text{ V}$

$\therefore v_{\text{max}} = 8 \times 10^6 \text{ V}$ thus have a field of $\frac{8 \times 10^6}{2} \text{ V/m} = 4 \times 10^6 \text{ V/m}$

which exceeds dielectric strength in air of $3 \times 10^6 \text{ V/m}$

\therefore We get a discharge as the air is ionized.

Problem P 7.5-6

Determine $v(t)$ for $t > 0$ for the circuit of Figure P 7.5-6a when $i_L(0) = 0$ and i_s is as shown in Figure P 7.5-6b.

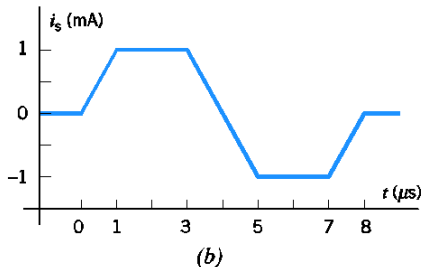
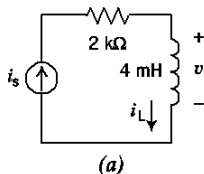


Figure P 7.5-6

Problem P 7.5-6

Solution

In general
$$v(t) = (2 \times 10^3) i_s(t) + (4 \times 10^{-3}) \frac{d}{dt} i_s(t)$$

For $0 < t < 1 \mu s$ $i_s(t) = (1) \left(\frac{1 \times 10^{-3}}{1 \times 10^{-6}} \right) t = 10^3 t \Rightarrow \frac{d}{dt} i_s(t) = 1 \times 10^3$. Consequently

$$v(t) = (2 \times 10^3)(1 \times 10^3) t + 4 \times 10^{-3}(1 \times 10^3) = (2 \times 10^6 t + 4) \text{ V}$$

For $1 \mu s < t < 3 \mu s$ $i_s(t) = 1 \text{ mA} \Rightarrow \frac{d}{dt} i_s(t) = 0$. Consequently

$$v(t) = (2 \times 10^3)(1 \times 10^{-3}) + (4 \times 10^{-3}) \times 0 = 2 \text{ V}$$

For $3 \mu s < t < 5 \mu s$ $i_s(t) = 4 \times 10^{-3} - \left(\frac{1 \times 10^{-3}}{1 \times 10^{-6}} \right) t \Rightarrow \frac{d}{dt} i_s(t) = -\frac{1 \times 10^{-3}}{1 \times 10^{-6}} = -10^3$. Consequently

$$v(t) = (2 \times 10^3)(4 \times 10^{-3} - 10^3 t) + 4 \times 10^{-3}(-10^3) = 4 - (2 \times 10^6) t$$

Problem P 7.5-6

Solution (cnt.)

When $5\mu s < t < 7\mu s$ $i_s(t) = -1 \times 10^{-3}$ and $\frac{d}{dt}i_s(t) = 0$. Consequently

$$v(t) = (2 \times 10^3)(10^{-3}) = -2 \text{ V}$$

When $7\mu s < t < 8\mu s$ $i_s(t) = \left(\frac{1 \times 10^{-3}}{1 \times 10^{-6}}\right)t - 8 \times 10^{-3} \Rightarrow \frac{d}{dt}i_s(t) = 1 \times 10^3$

$$v(t) = (2 \times 10^3)(10^3 t - 8 \times 10^{-3}) + (4 \times 10^{-3})(10^3) = -12 + (2 \times 10^6)t$$

When $8\mu s < t$, then $i_s(t) = 0 \Rightarrow \frac{d}{dt}i_s(t) = 0$. Consequently $v(t) = 0$.

Problem P 7.5-14

The inductor current in the circuit shown in Figure P 7.5-14 is given by

$$i(t) = 3 + 2e^{-3t} \text{ A} \quad \text{for } t \geq 0$$

Determine $v(t)$ for $t > 0$.

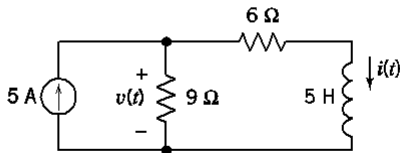


Figure P 7.5-14

Problem P 7.5-14

The inductor current in the circuit shown in Figure P 7.5-14 is given by

$$i(t) = 3 + 2e^{-3t} \text{ A} \quad \text{for } t \geq 0$$

Determine $v(t)$ for $t > 0$.

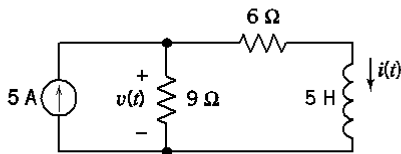



Figure P 7.5-14

Solution: Apply KVL to get

$$v(t) = 6i(t) + 5 \frac{d}{dt} i(t) = 6(3 + 2e^{-3t}) + 5 \frac{d}{dt} (3 + 2e^{-3t}) = 18(1 - e^{-3t}) \text{ V} \quad \text{for } t > 0$$

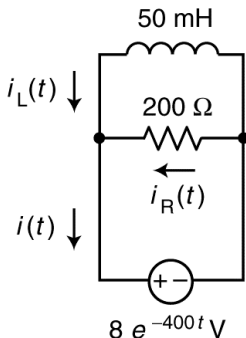Problem P 7.5-18

The source voltage in the circuit shown below is $v(t) = 8e^{-400t}$ after time $t = 0$. The initial inductor current is $i_L(0) = 210$ mA. Determine the source current $i(t)$ for $t > 0$.



Problem P 7.5-18

Solution

Label the resistor current as shown. The resistor, inductor and voltage source are connected in parallel so the voltage across each is $v(t) = 2.5 e^{-400t}$ V. Notice that the labeled voltage and current of both the resistor and inductor do not adhere to the passive convention.


The resistor current is $i_R(t) = -\frac{8 e^{-400t}}{200} = -40 e^{-400t}$ mA

The inductor current is $i_L(t) = 0.21 + \frac{1}{0.05} \int_0^t -8 e^{-400\tau} d\tau$ A

$$\begin{aligned} i_L(t) &= 0.21 + \frac{-8}{0.05(-400)} \int_0^t e^{-400\tau} d\tau \text{ A} \\ &= 0.21 + 0.4(e^{-400t} - 1) \text{ A} \\ &= 400e^{-400t} - 190 \text{ mA} \end{aligned}$$

Using KCL

$$i(t) = 360e^{-400t} - 190 \text{ mA for } t > 0$$

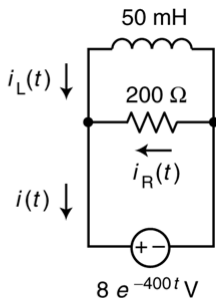

Part 5: Energy Storage in an Inductor

Problem P 7.6-4

The current in an inductor, $L = 1/4$ H, is $i = 4te^{-t}$ A for $t \geq 0$ and $i = 0$ for $t < 0$. Find the voltage, power, and energy in this inductor.

Problem P 7.6-4

The current in an inductor, $L = 1/4$ H, is $i = 4te^{-t}$ A for $t \geq 0$ and $i = 0$ for $t < 0$. Find the voltage, power, and energy in this inductor.

Solution

$$v = L \frac{di}{dt} = \left(\frac{1}{4} \right) \frac{d}{dt} (4t e^{-t}) = \underline{(1-t) e^{-t} \text{ V}}$$

$$P = vi = \left[(1-t) e^{-t} \right] (4t e^{-t}) = \underline{4t(1-t) e^{-2t} \text{ W}}$$

$$\mathcal{W} = \frac{1}{2} Li^2 = \frac{1}{2} \left(\frac{1}{4} \right) (4t e^{-t})^2 = \underline{2t^2 e^{-2t} \text{ J}}$$

Part 6: Series and Parallel Inductors

Problem P 7.7-7

The circuit shown in Figure P 7.7-7 consists of 10 inductors having equal inductance, L . Determine the value of the inductance L , given that $L_{\text{eq}} = 12 \text{ mH}$.

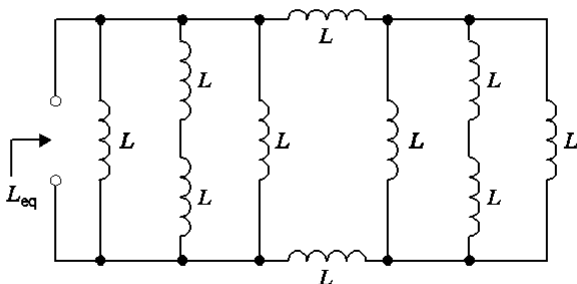


Figure P 7.7-7

Problem P 7.7-7 (Solution)

The circuit shown in Figure P 7.7-7 consists of 10 inductors having equal inductance, L . Determine the value of the inductance L , given that $L_{eq} = 12$ mH.


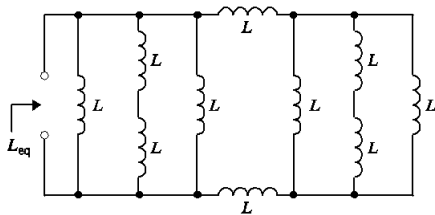


Figure P 7.7-7

Solution:

First

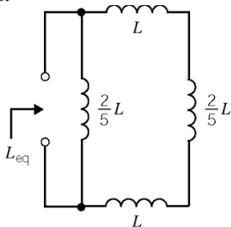

Then

$$12 = L_{eq} = \frac{\left(\frac{2}{5}L\right) \times \left(\frac{2}{5}L + 2L\right)}{\left(\frac{2}{5}L\right) + \left(\frac{2}{5}L + 2L\right)} = \frac{12}{35}L \Rightarrow L = 35 \text{ mH}$$

Thank you !