

Today's Outline

1. Fundamentals


- Active and Passive Elements
- Linear Circuit Elements
- the Ideal Resistor and Ohm's Law
- Physical Resistors

Energy Transfer to and from Elements

We classify circuit elements in terms of their ability or inability to deliver a net positive energy to a circuit.

Let $p(t') = i(t')v(t')$ be the *instantaneous power* that is **absorbed** by a circuit element (passive sign convention for i and v)..

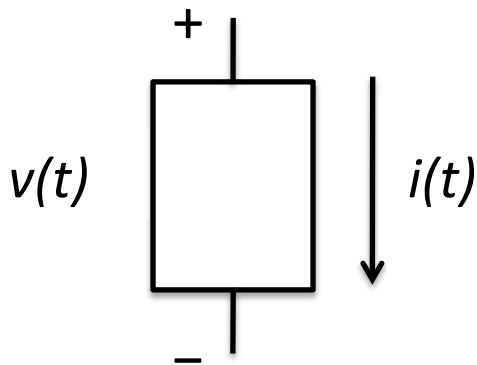The **net energy absorbed** by the circuit element up to time t is:




$$U(t) = \int_{-\infty}^t p(t') dt' = \int_{-\infty}^t i(t')v(t') dt'$$

Passive Elements

Passive element: a circuit element that *cannot* deliver more energy than it has already received from a circuit.

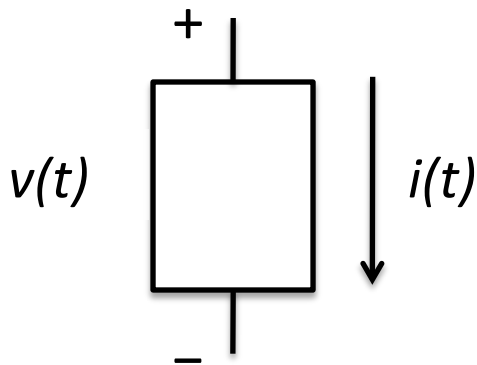In other words, the net energy absorbed by a passive circuit element is always greater than or equal to zero.



$$U(t) = \int_{-\infty}^t p(t') dt' = \int_{-\infty}^t i(t') v(t') dt' \geq 0$$

Example: a piece of copper wire can be modeled by a passive circuit element.

Active Elements

Active element: a circuit element that *can* deliver more energy than it has already received from a circuit.

In other words, all elements that are not passive are active.

Warning: Although active elements *can* deliver energy to a circuit, this does not mean that an active element *is* delivering energy in a particular circuit.

Questions:

Can a rechargeable battery be modeled as an active element or a passive element?

Can a non-rechargeable battery be modeled as an active element or a passive element?

Linear Circuit Element

Linear Circuit Element: An element where terminal voltage and current are related to each other by a linear function (or operator). Examples include ideal resistors, dependent sources and many others.

Linearity

Linearity: A function $f(x)$ is **linear** in the argument x if and only if:

$$f(a x + b y) = a f(x) + b f(y)$$

- To evaluate $f(a x + b y)$, we can evaluate $f(x)$ and $f(y)$, and then sum appropriately.
- In some cases, it may be easier to evaluate $f(x)$ and $f(y)$ instead of $f(a x + b y)$, for example:

$$f(x) = 2x$$

$$\begin{aligned} f(179) &= f(170) + f(9) \quad [\text{for evaluation without pen or paper}] \\ &= 340 + 18 = 358 \end{aligned}$$

Linearity (more general)

Linearity: An operator $F[x(t)]$ is **linear** in the function $x(t)$ if and only if:

$$F[a x(t) + b y(t)] = a F[x(t)] + b F[y(t)]$$


- To evaluate $F[a x(t) + b y(t)]$, we can evaluate $F[x(t)]$ and $F[y(t)]$, and then sum the appropriately.
- In some cases, it may be easier to evaluate $F[x(t)]$ and $F[y(t)]$ instead of $F[x(t) + y(t)]$, for example:

$$F[x(t)] = \frac{d}{dt} [x(t)]$$

$$\begin{aligned} F[C + D \exp(-kt)] &= F[C] + F[D \exp(-kt)] \\ &= 0 - Dk \exp(-kt) \end{aligned}$$

Ohm's Law

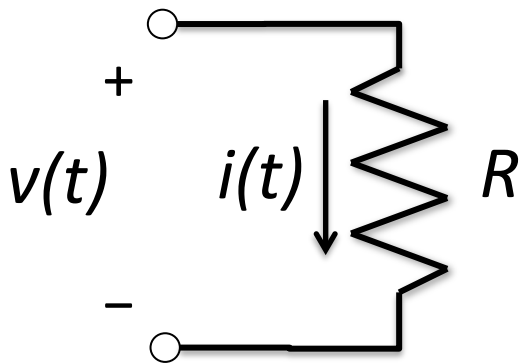Ohm's Law: the voltage drop v across an **ideal resistor** is proportional to the current i flowing through the resistor



$$v = i R$$

- v and i are defined with passive sign convention
- the *positive* constant of proportionality is called the **resistance**, given the symbol r or R
- SI unit of resistance is the Ohm (abbreviated Ω)



$$1 \Omega = 1 \text{ V} / \text{A}$$



Georg Simon Ohm
(1789-1854)

Ideal Resistor

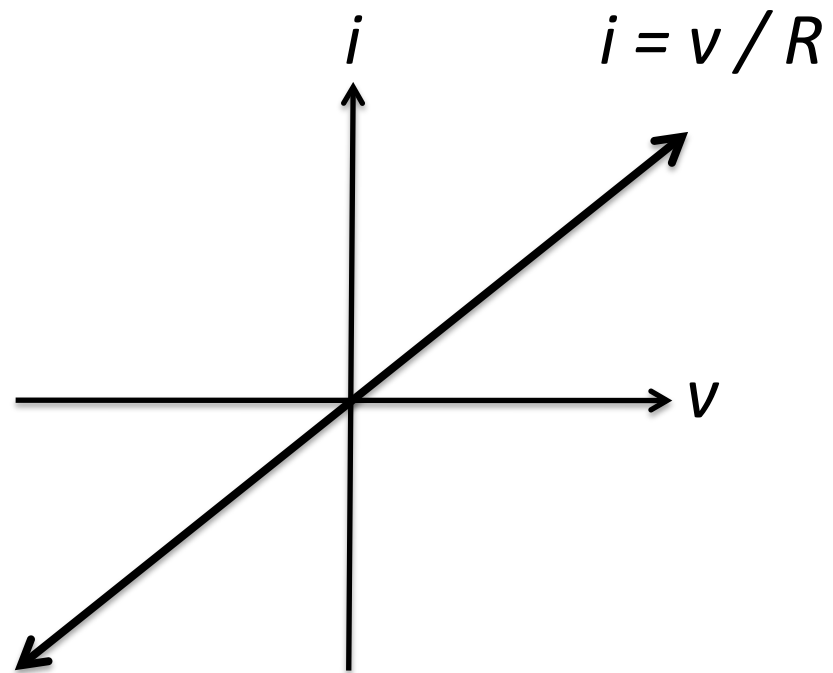
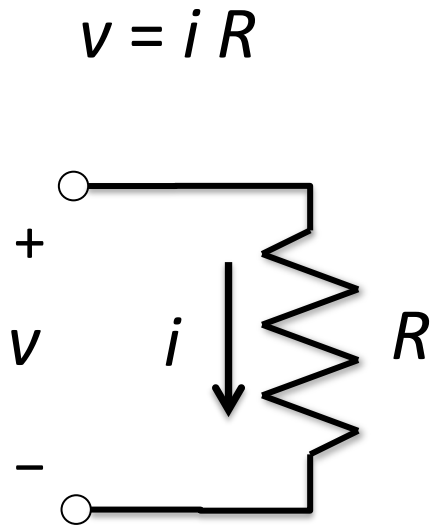
Ideal Resistor: a circuit element that satisfies Ohm's law



Conductance

Conductance can also be used to parameterize a resistor.

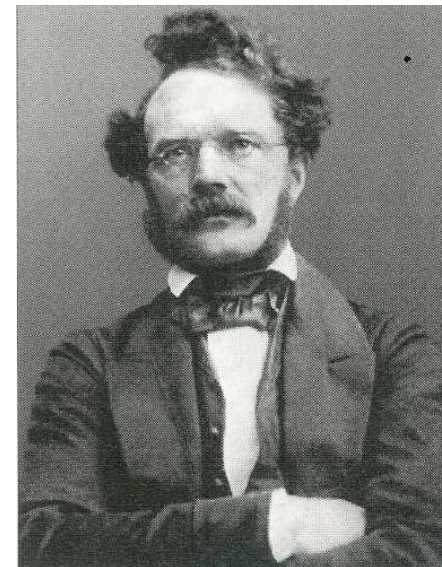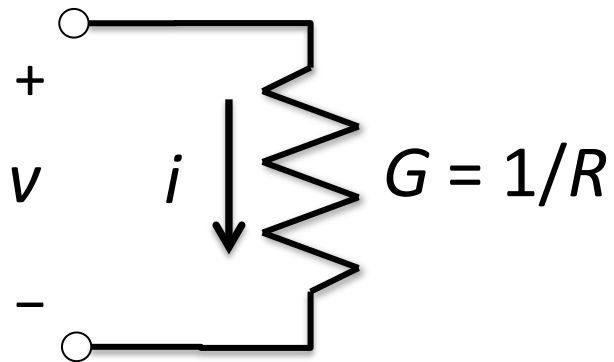
- given the symbol G or g
- related to resistance through $G = 1/R$
- SI unit is the siemens (abbreviated S)
 $1 \text{ S} = 1 \Omega^{-1} = 1 \text{ A} / \text{V}$
- Ohm's law can be restated $i = G v$



Werner von Siemens
(1816-1892)

Resistance and Conductance

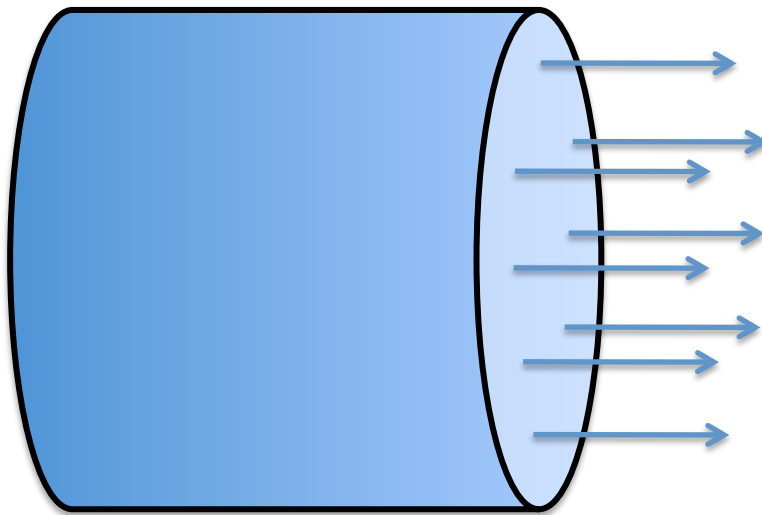The terminology of resistance and conductance is analogous to the terminology of fluid flow through pipes.



larger conductance G

smaller resistance R

more flow with applied pressure
more current I with applied voltage V



smaller conductance G

larger resistance R



less flow with applied pressure
less current I with applied voltage V

Power

A resistor is a **passive element**. The power absorbed by a resistor is always non-negative:

$$p = i v = i^2 R = v^2 / R$$

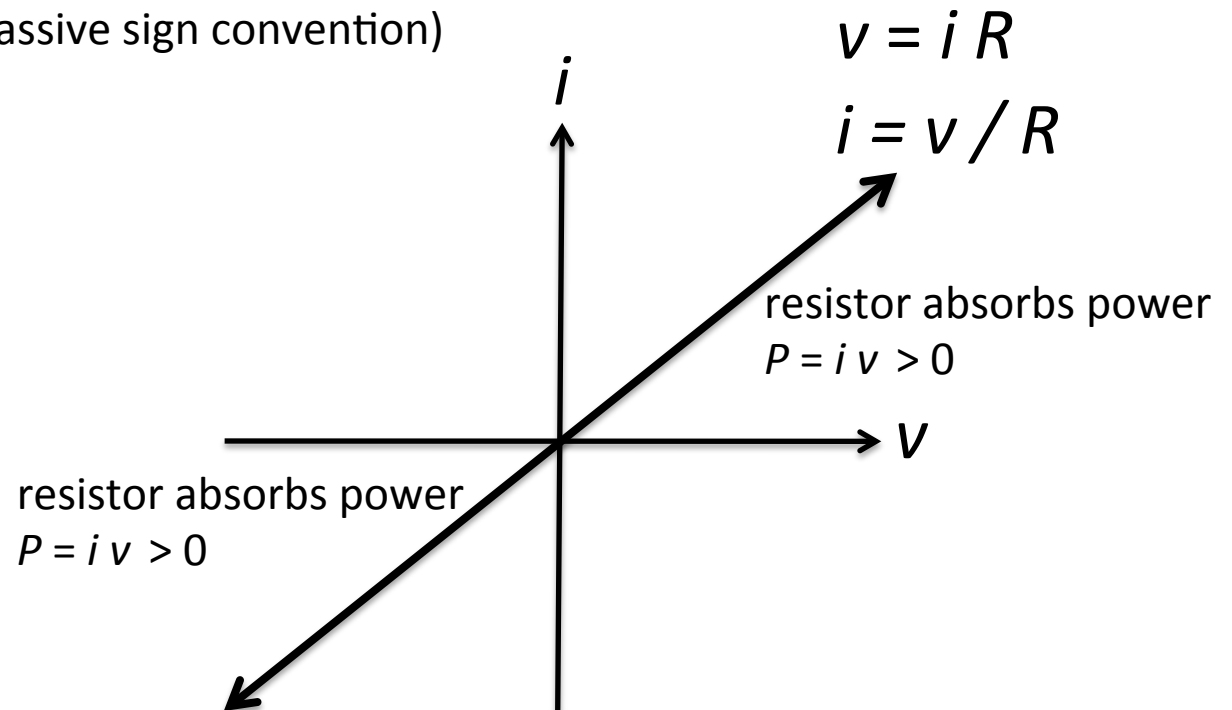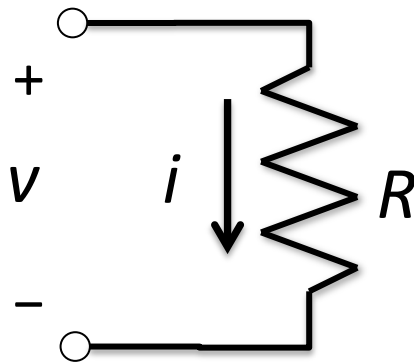(note the importance of passive sign convention)




Physical Resistors

A **wirewound resistor** is typically of “small” resistance and “large” size, designed to dissipate heat effectively.



PostGlover

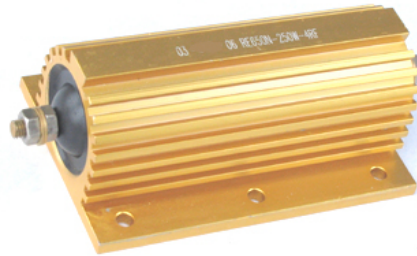

Chengdu Guozheng Electronics



Navatek Systems




Yageo

Ceramic casing, and sometimes a metallic heatsink, is used to increase heat dissipation and maximum power rating.

Physical Resistors

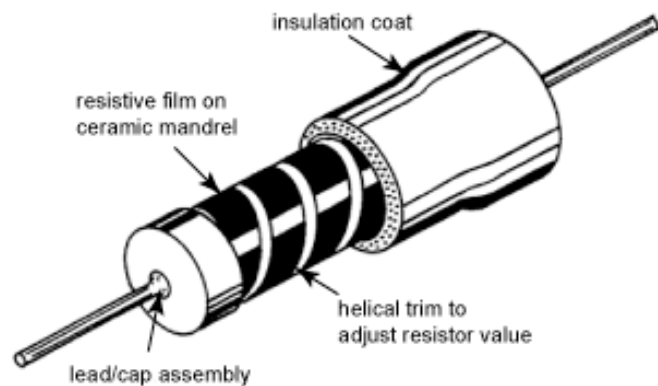A **carbon film resistor** and **metal film resistor** are well suited for resistance values of higher precision, with less power handling capability than a typical wirewound resistor.



Bolton University




Yageo




Ohmcraft



Yageo

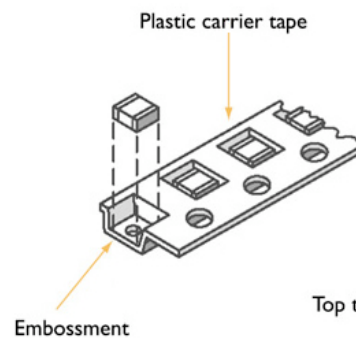


Charcroft Electronics

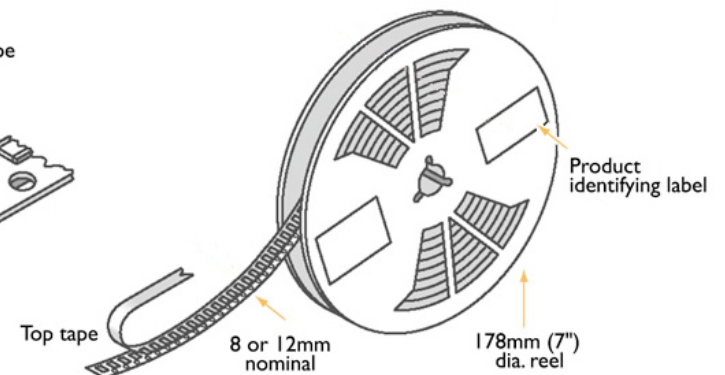


Physical Resistors

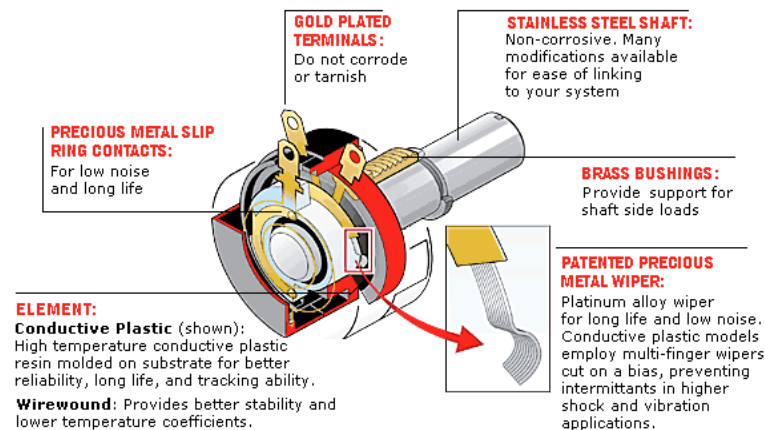
A **rheostat** is a variable resistor with a sliding contact. A **potentiometer** has three terminals, with one terminal being a sliding contact.



The circuit symbols are:

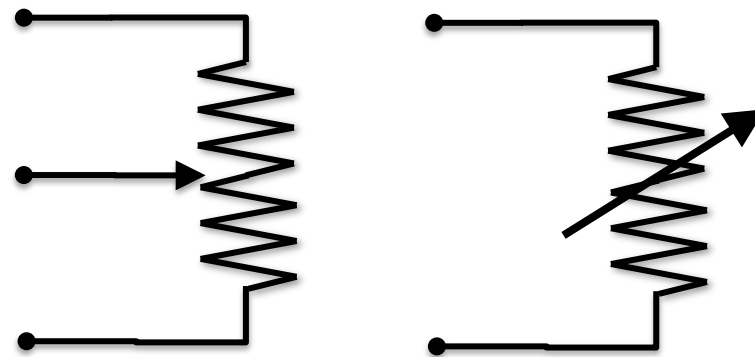

ETI Systems

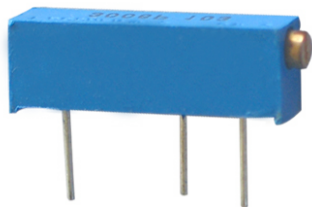

Rongcheng Electronics



Oretronics

ECSE-200

15