

ECSE-200 Electric Circuits 1  
Quiz #3 (Feb. 1, 2019)


LAST NAME SOLUTIONS MCGILL ID# \_\_\_\_\_

FIRST NAME \_\_\_\_\_ SIGNATURE \_\_\_\_\_

- Only Faculty standard calculator accepted
- Show all your work
- Clearly indicate your final answer with SI units and SI multiplier
- You have 45 minutes to complete this quiz
- Plagiarism will have important consequences

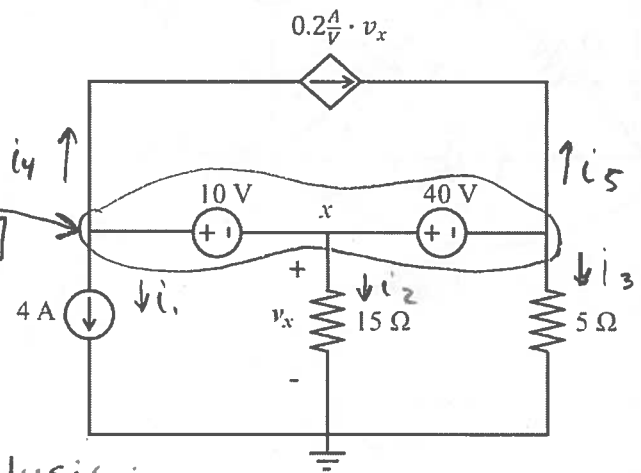**Question 1.** Consider the circuit shown. Answer the following questions.

- How many nodes are there in this circuit? [1 pt] 4 nodes [+1]
- Identify the super-node in the circuit [1 pt] [+1]
- What is the current supplied by the dependent current source? [2 pt]
- What is the total power absorbed by both resistance? [2 pt]




c)  $i = 0.2 \frac{A}{V} \cdot v_x$  use nodal analysis:  
 $\frac{v_x}{15\Omega} + \frac{(v_x - 40V)}{5\Omega} + 0.2 \frac{A}{V} \cdot v_x - 0.2 \frac{A}{V} \cdot v_x = 0$  [+0.5]  
 $\times 15\Omega$   $+60V + v_x + 3v_x - 170V = 0$   
 $4v_x = 60V \rightarrow v_x = 45V$  [+0.5]  
 $i = 0.2 \frac{A}{V} \cdot 15V$   
 $i = 3A$  [+0.5]

d)  $P_{15\Omega} = v_x \cdot i_2 = \frac{v_x^2}{R} = \frac{(45V)^2}{15\Omega} = 15W$  [+0.5]  
 $P_{5\Omega} = (v_x - 40V) \cdot i_3 = \frac{(v_x - 40V)^2}{5\Omega} = \frac{(25V)^2}{5\Omega} = 125W$  [+0.5]  
 $P_{tot} = 140W$

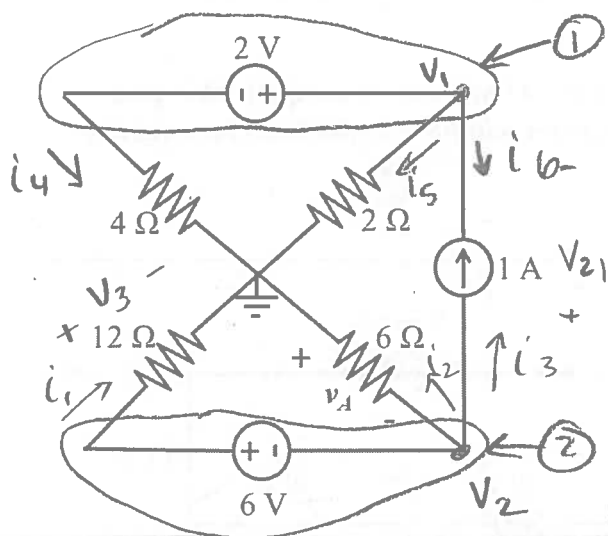**Question 2.** Consider the circuit shown below. Answer the following questions.

- How many super-nodes are there in this circuit? Identify them. [1 pt]
- Using the node voltage method, find the value of the voltage  $v_A$  across the  $6\ \Omega$  resistor. [2 pt]
- How much power does the independent current source deliver or absorb? [1 pt]
- How much power is absorbed by the  $12\ \Omega$  resistor? [1 pt]



a) There are two super-nodes [ +0.5 ]  
identified [ +0.5 ]

b) KCL @ super-node ②

$$i_1 + i_2 + i_3 = 0 \quad [ +0.5 ]$$

$$\frac{(v_2 + 6V)}{12\ \Omega} + \frac{v_2}{6\ \Omega} + 1A = 0 \quad [ +0.5 ]$$

$$(\times 12) \Rightarrow v_2 + 6V + 2v_2 + 12V = 0 \quad [ +0.5 ]$$

$$3v_2 = -18V \quad v_2 = -6V$$

$$v_A = -v_2 = 6V \quad \boxed{v_A = 6V} \quad [ +0.5 ]$$

c) To get  $v_{21}$  (voltage across source)

find  $v_1$  KCL @ 1  $i_4 + i_5 + i_6 = 0$

$$\frac{(v_1 - 2V)}{4\ \Omega} + \frac{v_1}{2\ \Omega} - 1A = 0$$

$$(\times 4) \quad v_1 - 2V + 2v_1 - 4A = 0$$

$$3v_1 = 6V \quad v_1 = 2V \quad [ +0.5 ]$$

$$v_{21} = v_2 - v_1 = -6V - 2V = -8V \rightarrow P = IV = -8W$$



$$\boxed{\text{Power delivered: } 8W} \quad [ +0.5 ]$$

d)  $v_3$  (voltage across  $12\ \Omega$ )  $v_3 = (v_2 + 6V) - 0V = (-6V + 6V) = 0$

There is 0W power absorbed (no power absorbed)


**Question 3.** The practical voltmeter used to measure  $v_x$  in the circuit shown below is a D'Arsonval galvanometer with a full-scale current ( $i_{FS}$ ) of 1 mA ( $i_{FS} = 1\text{mA}$ ), an internal resistance  $R_M$  of  $25\ \Omega$  (due to the wire loop resistance), and a series resistance  $R_s$  chosen such that the full-scale meter current ( $i_{FS}$ ) is reached with 100 V at the voltmeter terminals. Answer the following questions.

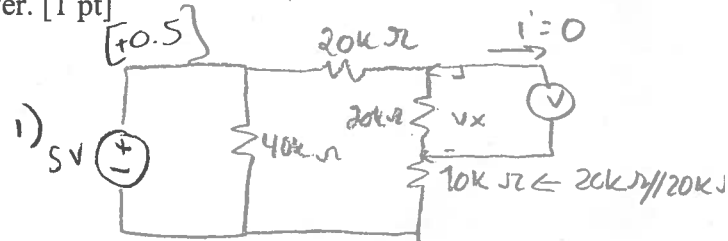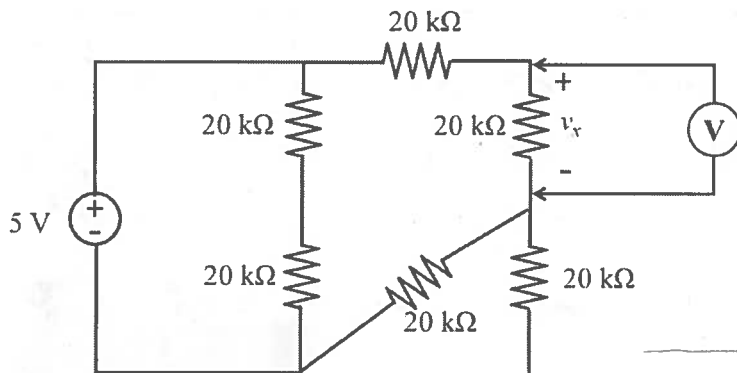- 1) What is the value of  $v_x$  if an ideal voltmeter was used to make the measurement? [1 pt]
- 2) What is the value of the series resistance  $R_s$  in the practical voltmeter used to measure  $v_x$ ? [2 pt]
- 3) What is the measured voltage  $v_x$  by the practical voltmeter? [1 pt]
- 4) To decrease the measurement error on the voltage  $v_x$ , should a larger series resistance  $R_s$  be used or a smaller series resistance  $R_s$  be used? Justify your answer. [1 pt]



$$v_x = 5V \cdot \frac{20k\Omega}{20k\Omega + 20k\Omega + 10k\Omega} = 2V$$

$V_x = 2V$

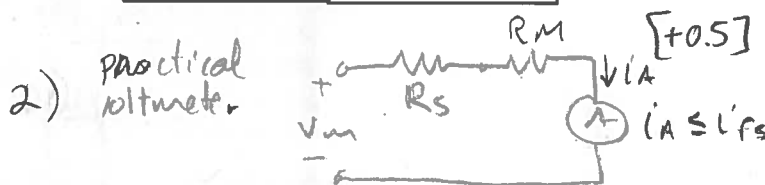


$R_M = 25\Omega$   $i_A = i_{FS} = 1\text{mA}$  when  $V_M = 100V$

$$V_M = i_A (R_s + R_M)$$

$$100V = 1\text{mA} (R_s + 25\Omega)$$

$$R_s = 99.975k\Omega$$

or  $R_s \approx 100k\Omega$  accepted.

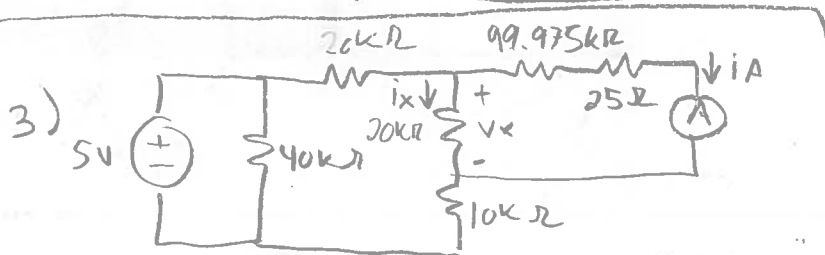

20kΩ is in parallel with  $(99.975k\Omega + 25\Omega)$

$$v_x = 5V \cdot \frac{16.67k\Omega}{16.67k\Omega + 10k\Omega + 20k\Omega} = 1.786V$$

$V_x = 1.786V$

4) A larger resistance  $R_s$  will reduce the current "leaking" through the voltmeter.

Extra working space.

