

Today's Outline

7. First Order Circuits

- unit step response

sequential switching: general procedure


For each time interval of constant input:

step #1: Find the initial value of the circuit variable of interest, $x(t_0+)$, using circuit analysis and continuity of capacitor voltage or inductor current.

step #2: Find the anticipated final value of the variable of interest, $x(\infty)$, using dc steady state models for the capacitor or inductor.

step #3: Find the Thévenin equivalent resistance R_T as seen from the terminals of the capacitor or inductor. The time constant $\tau = R_TC$ or $\tau = L/R_T$.

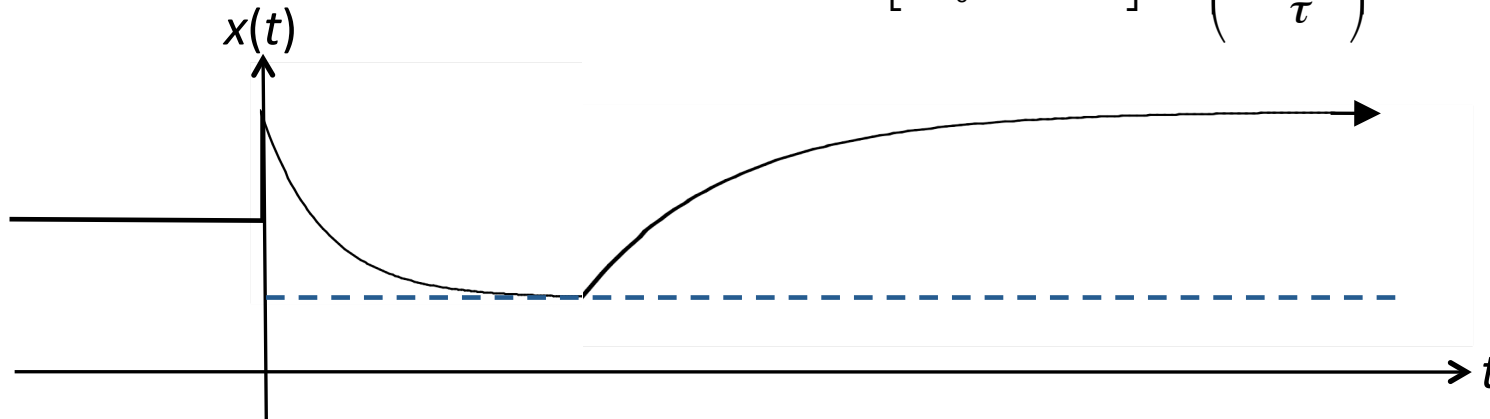step #4: Construct the solution.
$$x(t) = x(\infty) + [x(t_0+) - x(\infty)] \exp\left(-\frac{t-t_0}{\tau}\right)$$




There is an alternative approach using the “unit-step” function.

unit step function

The ***unit step function*** $u(t)$ is defined to be:
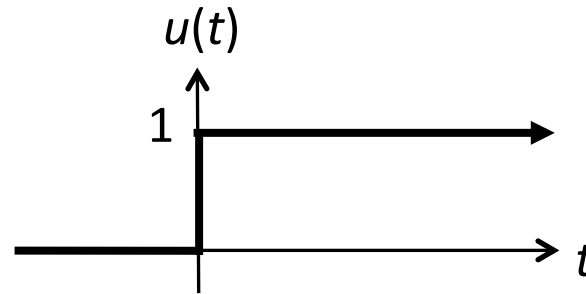
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$




- $u(t)$ is discontinuous at $t = 0$
- the value of $u(0)$ will not be important in this class





Oliver Heaviside
(1850-1924)

general step function

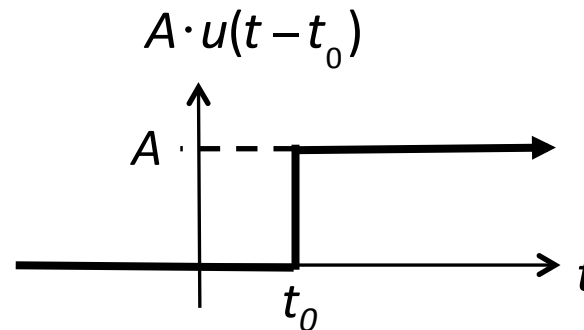The unit step function can be used to describe a general step function in voltage or current of amplitude A at a time t_0 .




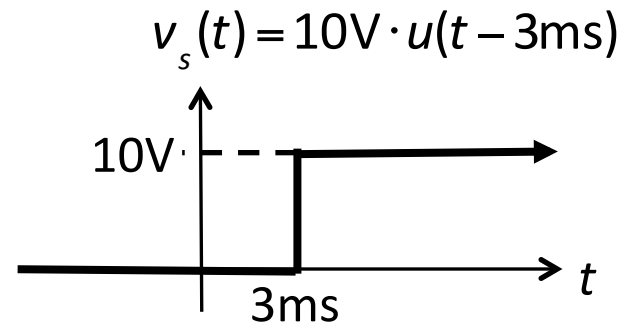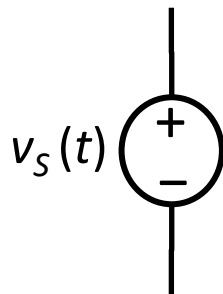The unit step function is very useful in expressing piece-wise constant signals. For example:



unit step response




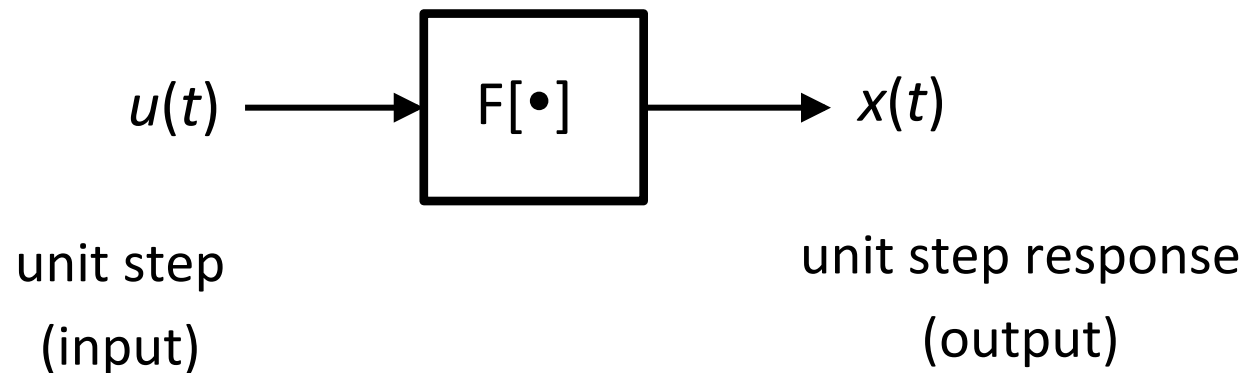
The ***unit step response*** $x(t)=F[u(t)]$ is the circuit variable response to a unit step voltage source or current source. $F[\bullet]$ is the operator mapping the source function to the circuit variable.



- $x(t)$ can be found by solving the differential equation with a unit step source $u(t)$
- *more sophisticated mathematical methods are required to find explicit expressions for the operator $F[\bullet]$.*

unit step response - example

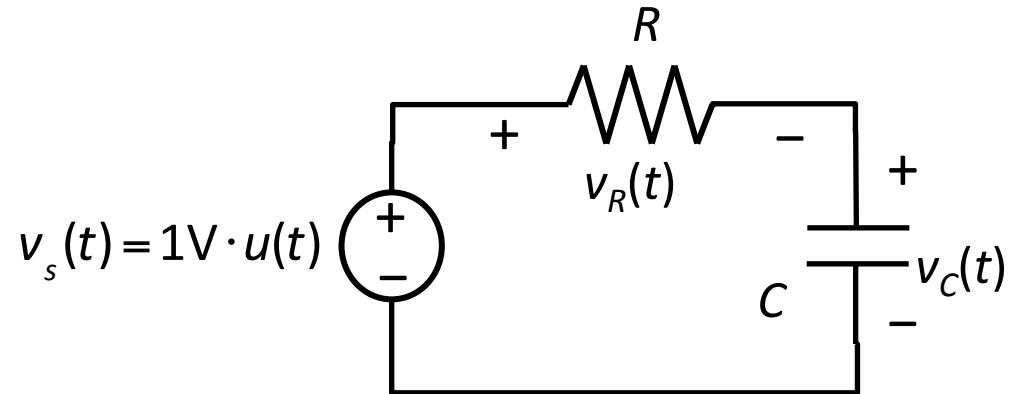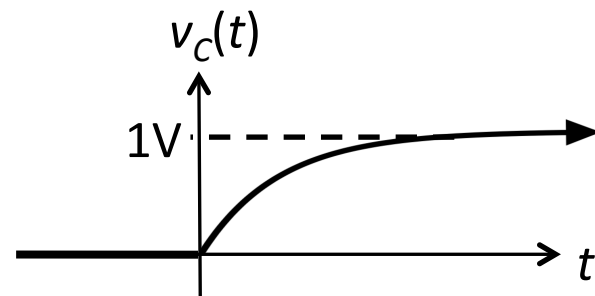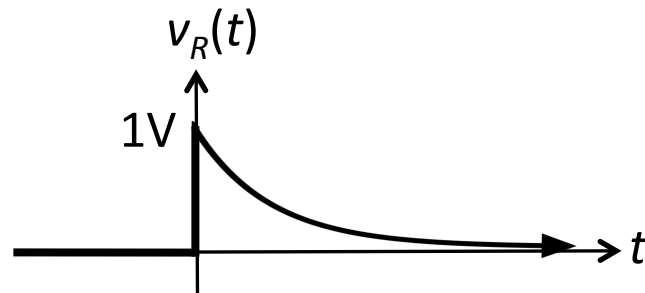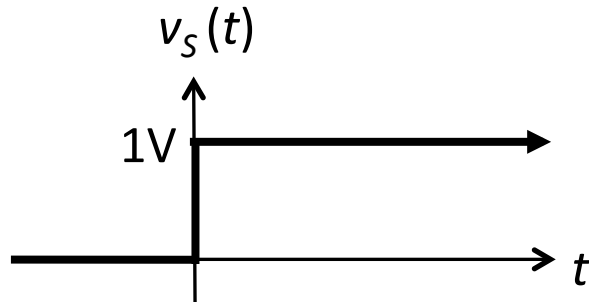Consider the example of an RC circuit, solved earlier in this section:



Unit step response of resistor voltage:


$$v_R(t) = 1V \cdot \exp(-t / \tau) \cdot u(t)$$

Unit step response of capacitor voltage:


$$v_C(t) = 1V \cdot [1 - \exp(-t / \tau)] \cdot u(t)$$

general step response


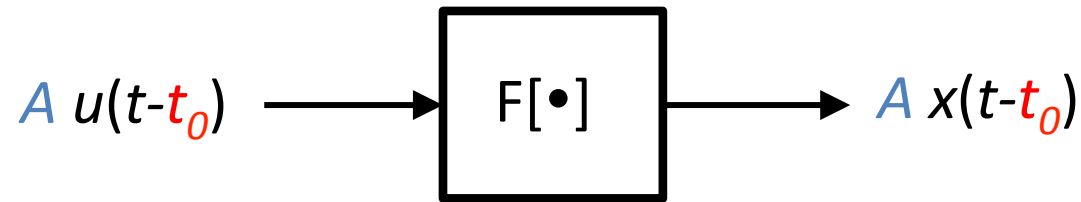
The *general* step response is simply expressed in terms of the unit step response for a **linear** and **time invariant** circuit.



Consider again an RC circuit example:

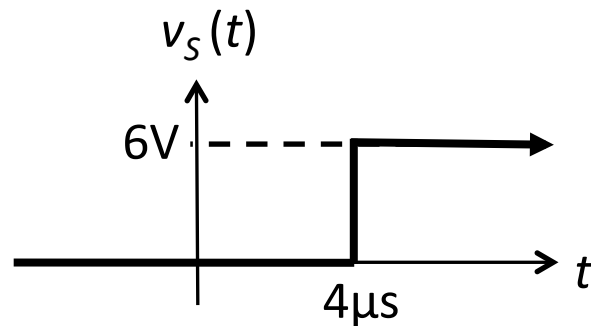
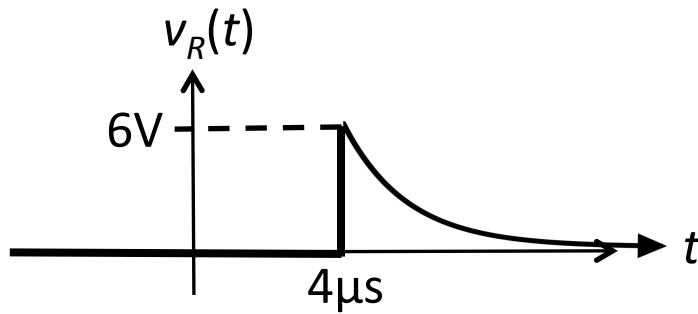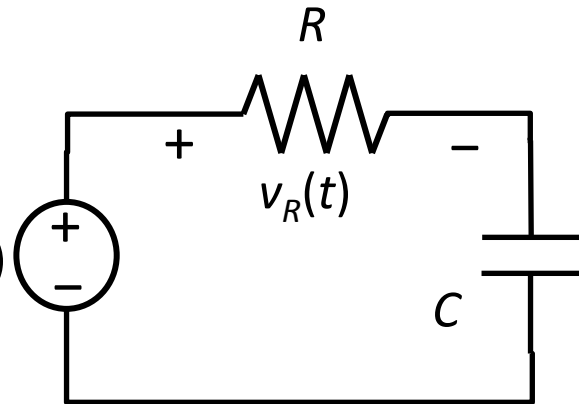
$$v_s(t) = 6V \cdot u(t - 4\mu\text{s})$$




Response of resistor voltage:

$$v_R(t) = 6V \cdot \exp(-(t - 4\mu\text{s}) / \tau) \cdot u(t - 4\mu\text{s})$$

sequential step response

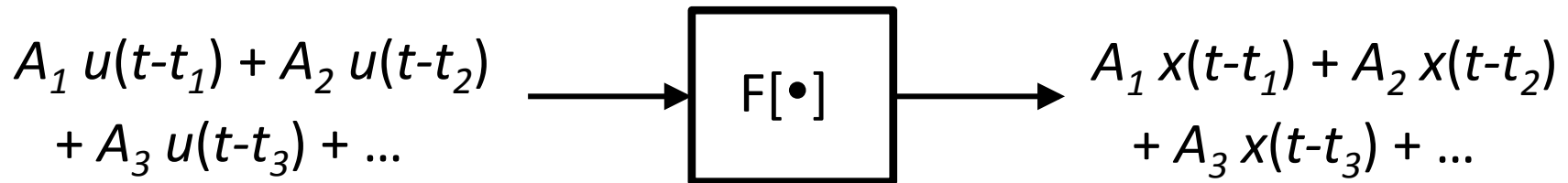The response to sequential steps is simply expressed in terms of the unit step response for a **linear** and **time invariant** circuit.





- **linearity** ensures that the principle of superposition can be applied
- **time invariance** ensures the step response has the same form, independent of the time at which the step occurs

$$F[A_1 u(t-t_1) + A_2 u(t-t_2)] = A_1 x(t-t_1) + A_2 x(t-t_2)$$

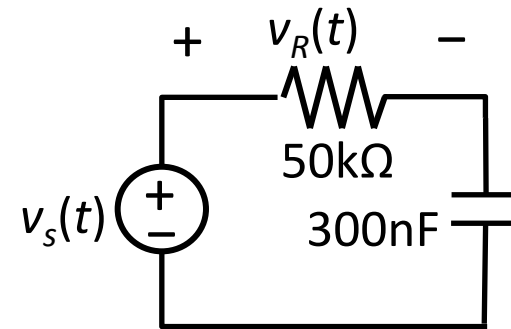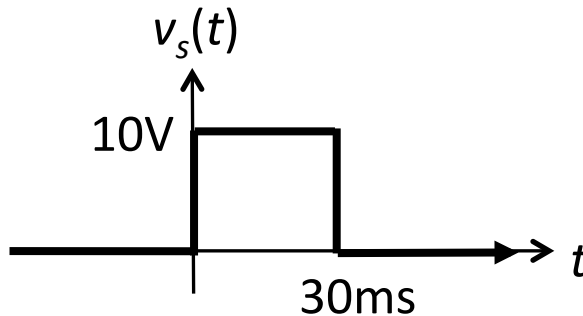
example

Reconsider finding $v_R(t)$ for sequential switching in an RC circuit.




Step #1: We first resolve the input into a sum of steps using $u(t)$.
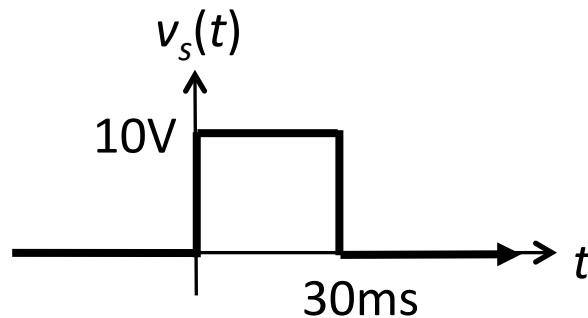
$$v_s(t) = 10V \cdot u(t) - 10V \cdot u(t - 30ms)$$






=

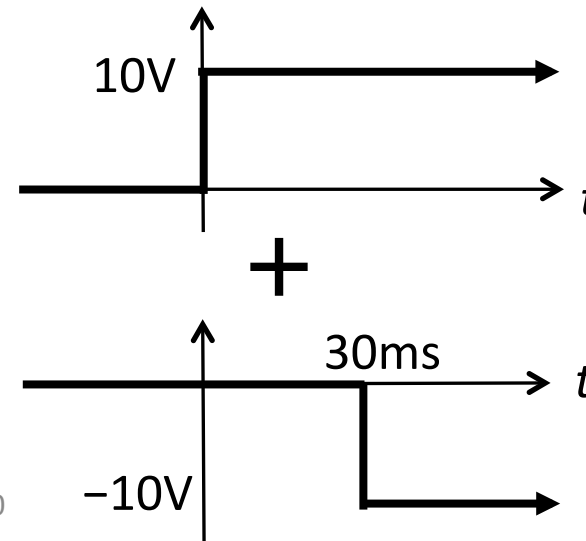

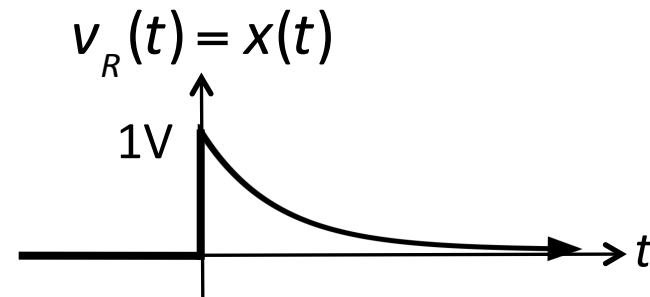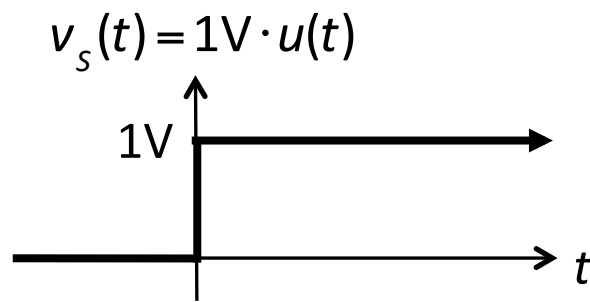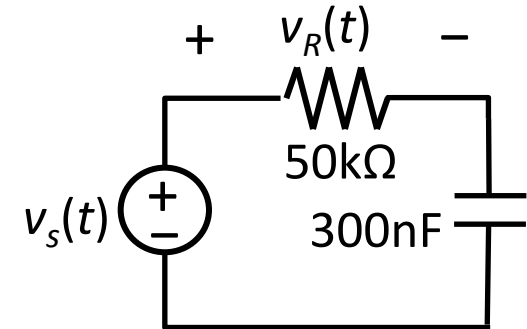example

Step #2: We find the step response $x(t)$ of the desired variable ($v_R(t)$) to the unit step input $u(t)$.




$$v_R(0+) = 1\text{V} \quad v_R(\infty) = 0\text{V} \quad \tau = 15\text{ ms}$$


$$v_R(t) = x(t) = 1\text{V} \cdot \exp(-t / 15\text{ms}) \cdot u(t)$$

example


Step #3: Add the response to each step.

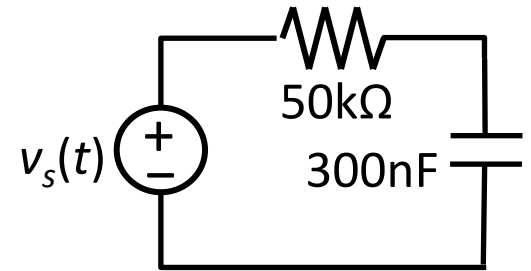


$$v_{s,1}(t) = 10\text{V} \cdot u(t)$$

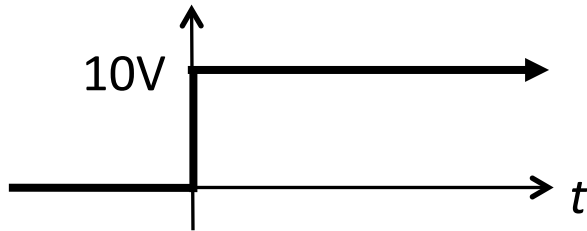

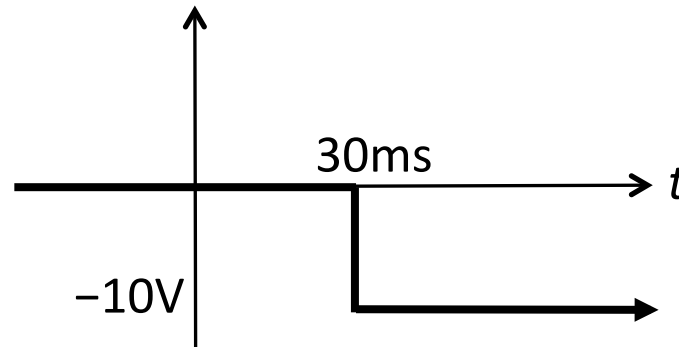
$$v_{s,2}(t) = -10\text{V} \cdot u(t - 30\text{ms})$$


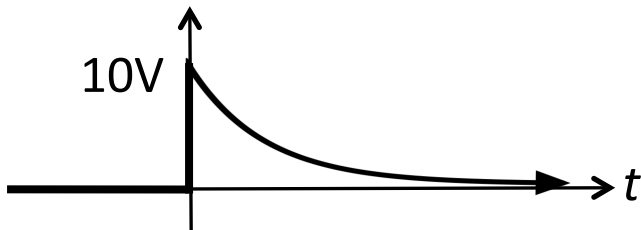
$$v_{R,1}(t) = 10\text{V} \cdot \exp(-t / 15\text{ms}) \cdot u(t)$$




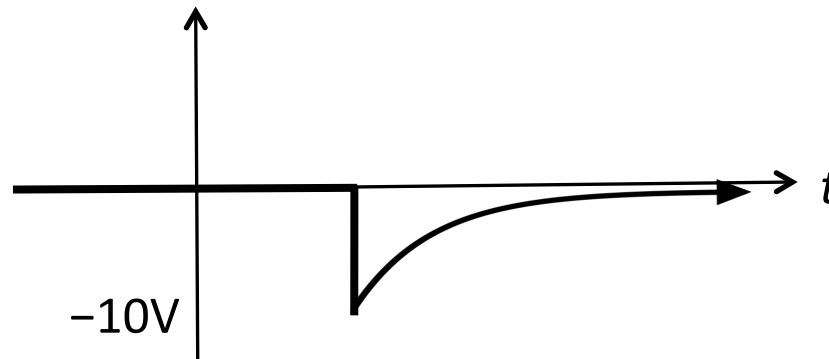
$$v_{R,2}(t) = -10\text{V} \cdot \exp(-(t - 30\text{ms}) / 15\text{ms}) \cdot u(t - 30\text{ms})$$



$$v_R(t) = v_{R,1}(t) + v_{R,2}(t)$$




example : compare solutions

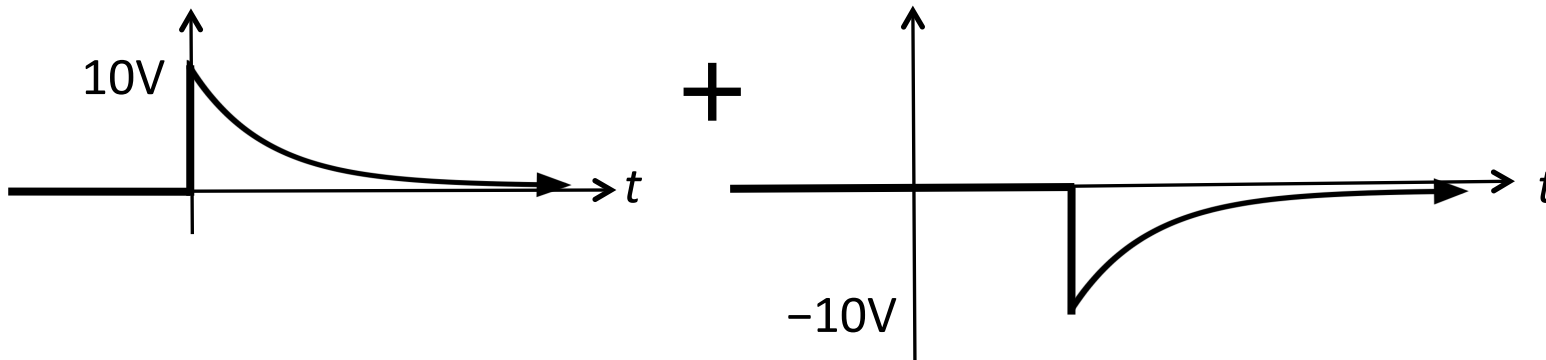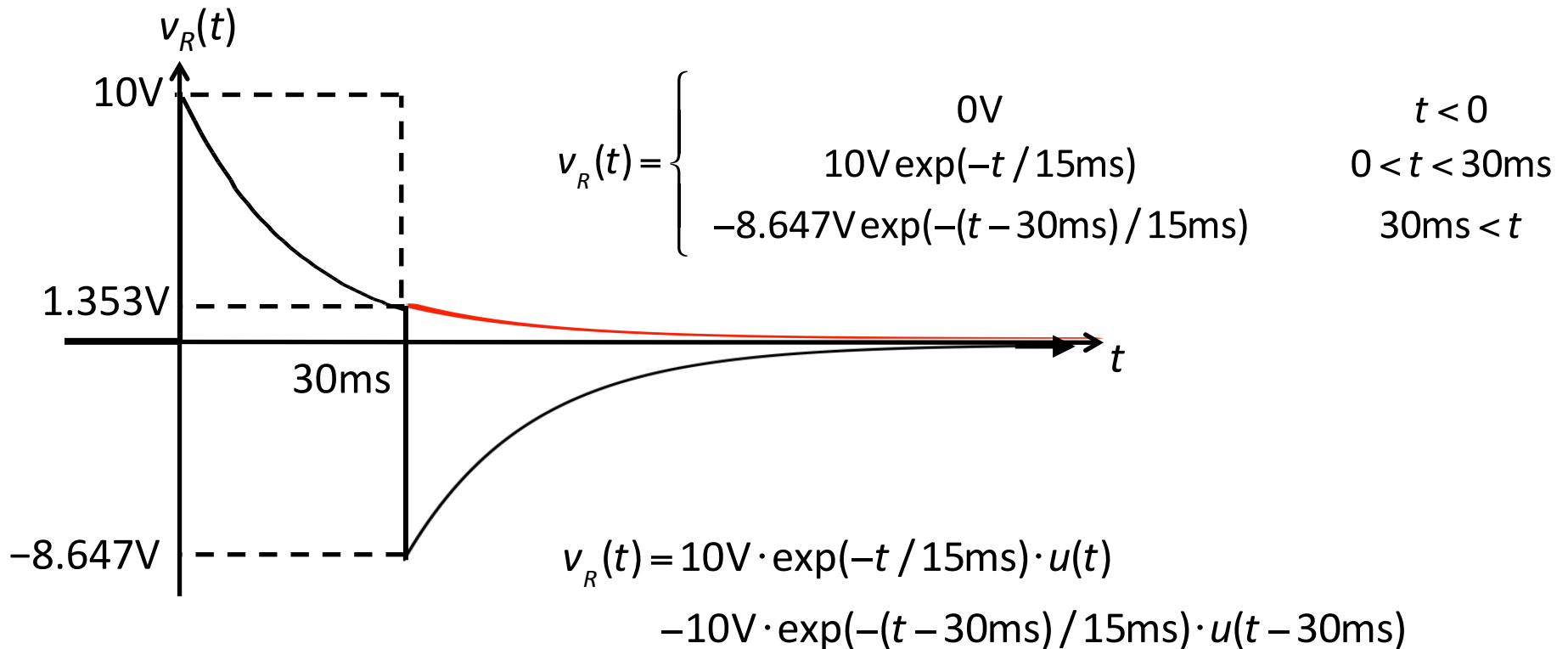

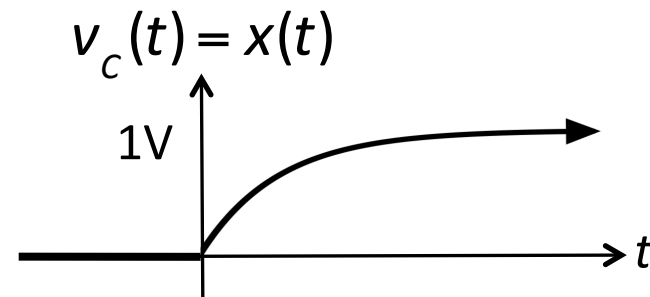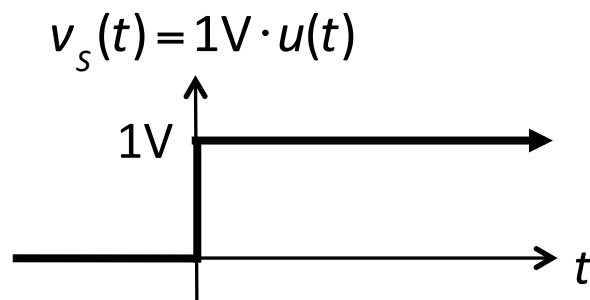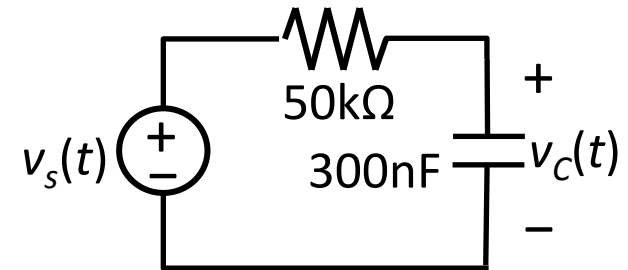example

Consider now $v_C(t)$ for the same RC circuit.

Step #2: We find the step response $x(t)$ of the desired variable ($v_C(t)$) to the unit step input $u(t)$.





$$v_C(0+) = 0V \quad v_C(\infty) = 1V \quad \tau = 15 \text{ ms}$$



$$v_C(t) = x(t) = 1V \cdot [1 - \exp(-t / 15\text{ms})] \cdot u(t)$$

example


Step #3: Add the response to each step.

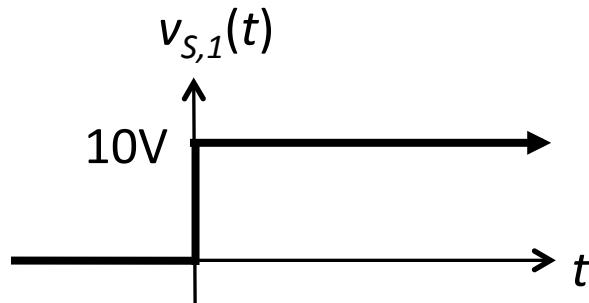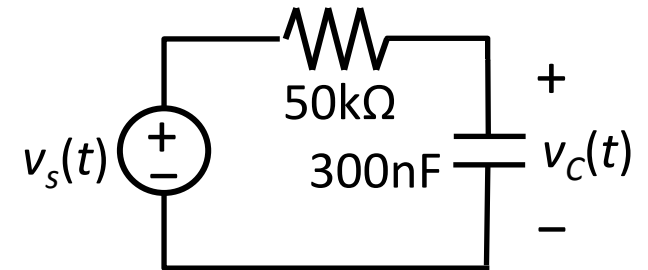
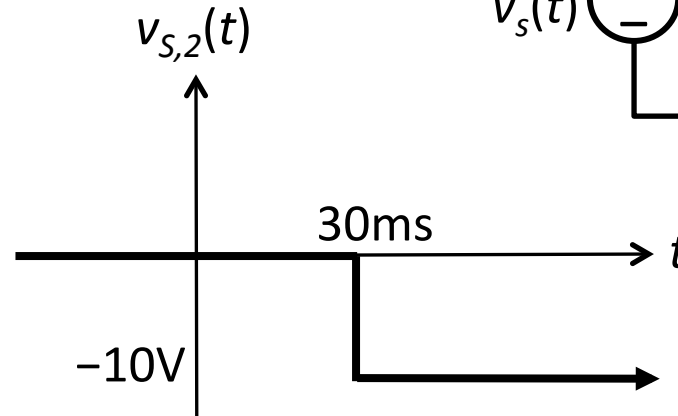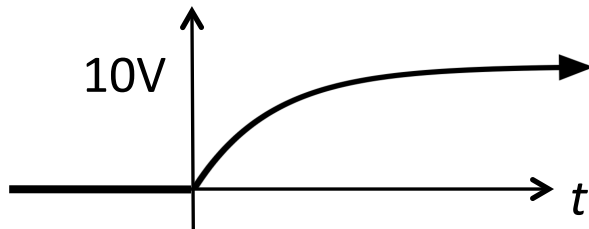
$$v_{c,1}(t) = 10V \cdot [1 - \exp(-t / 15ms)] \cdot u(t)$$



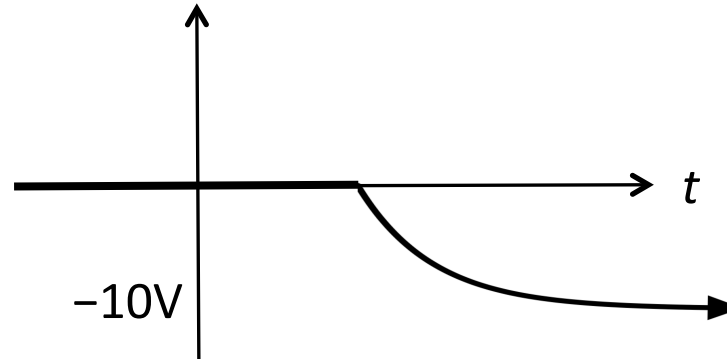
$$v_{c,2}(t) = -10V \cdot [1 - \exp(-(t - 30ms) / 15ms)] \cdot u(t - 30ms)$$




$$v_c(t) = v_{c,1}(t) + v_{c,2}(t)$$

example: compare solutions

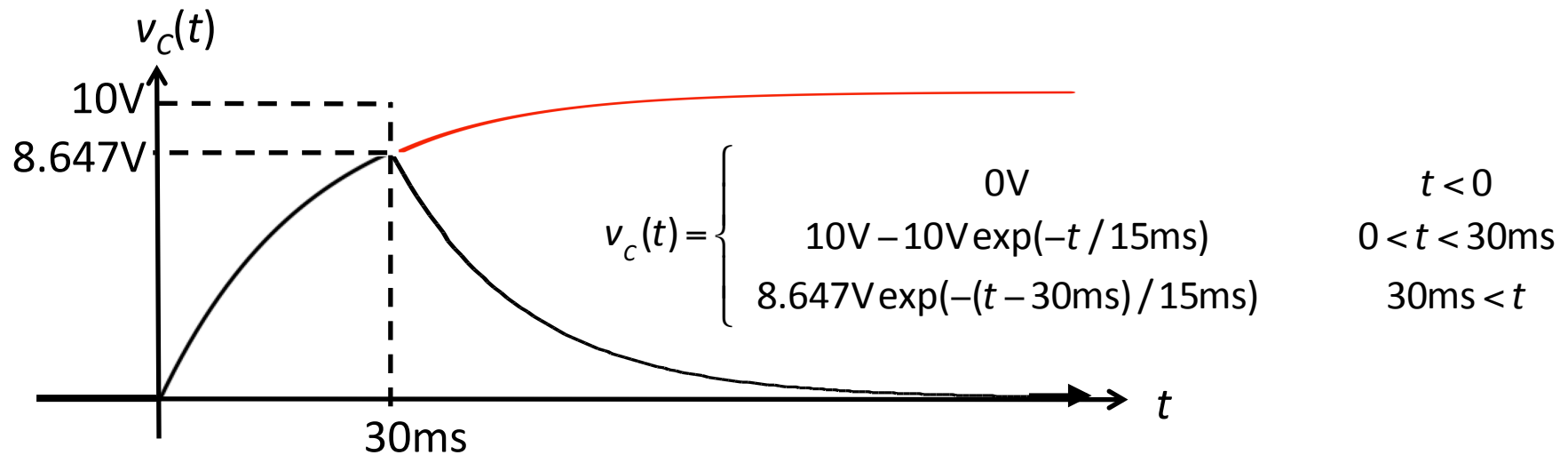
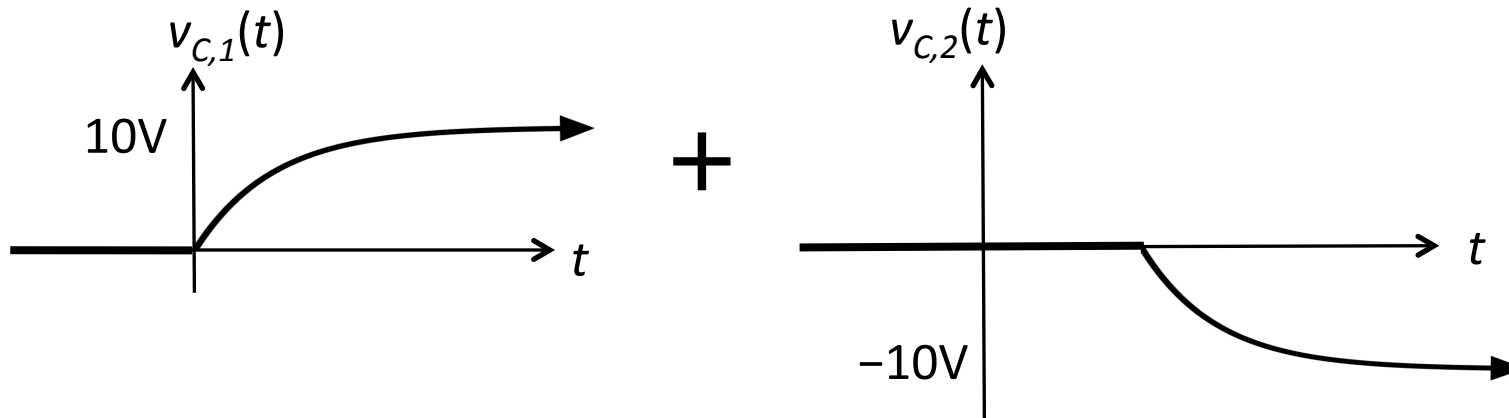
$$v_C(t) = 10V \cdot [1 - \exp(-t / 15\text{ms})] \cdot u(t) - 10V \cdot [1 - \exp(-(t - 30\text{ms}) / 15\text{ms})] \cdot u(t - 30\text{ms})$$



sequential switching: another view

For a piece-wise constant input :

step #1: Resolve the input into a summation of appropriately scaled and delayed unit step functions, $A_1u(t-t_1) + A_2u(t-t_2) + \dots$

step #2: Find the unit step response $x(t)$ of the circuit variable to a unit step function input $u(t)$, using the technique for finding the constant input response of an RC or RL circuit.

step #3: Add the response to each step function at the input.

