

# A warm-up problem...

A spark plug requires *several thousand* to *several tens of thousand* volts to spark and ignite the air-fuel mixture of an internal combustion engine.

A typical battery provides 12V.

How are spark plugs fired in an automobile, motor boat and other instances of internal combustion engines?



## 7. First Order Circuits

- overview of RC and RL circuits
- response to a constant input
- sequential switching
- stability
- unit step response
- response to a non-constant input
- operator method

# Today's Outline

## 7. First Order Circuits

- overview of RC and RL circuits
- response to a constant input
  - RC circuit


# Overview

**First order circuit:** a circuit composed of resistors, sources and either one capacitor (an **RC circuit**) or one inductor (an **RL circuit**).

- “first order” refers to the **first order linear differential equations** that describe the time evolution of the voltage and current variables  $v(t)$  and  $i(t)$
- *RL* and *RC* circuits are extremely useful because of the *time dependence* of voltages and currents in such circuits

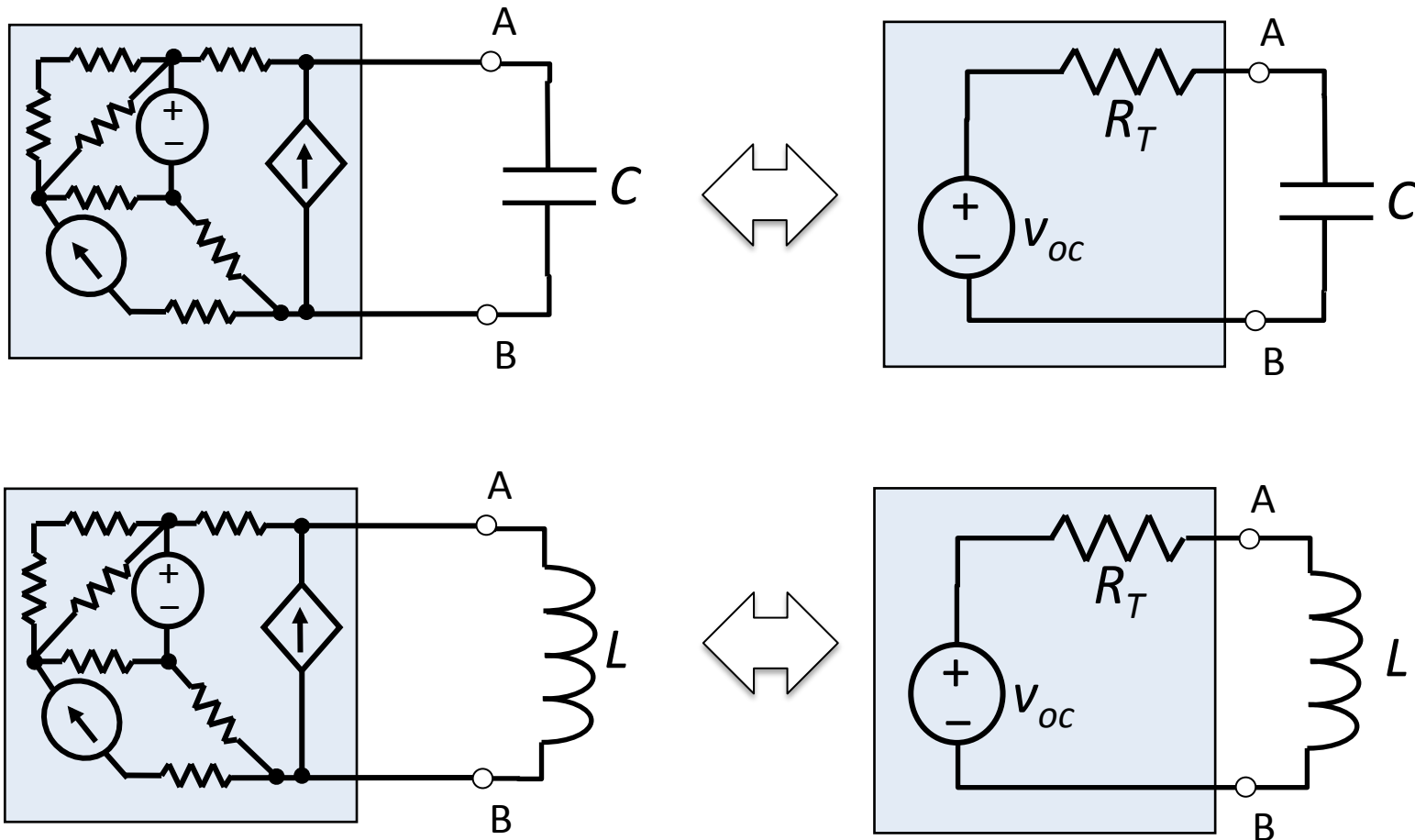
# Overview

Using Thévenin (or Norton) equivalence,  $RC$  and  $RL$  circuits can be reduced to the following simple forms.


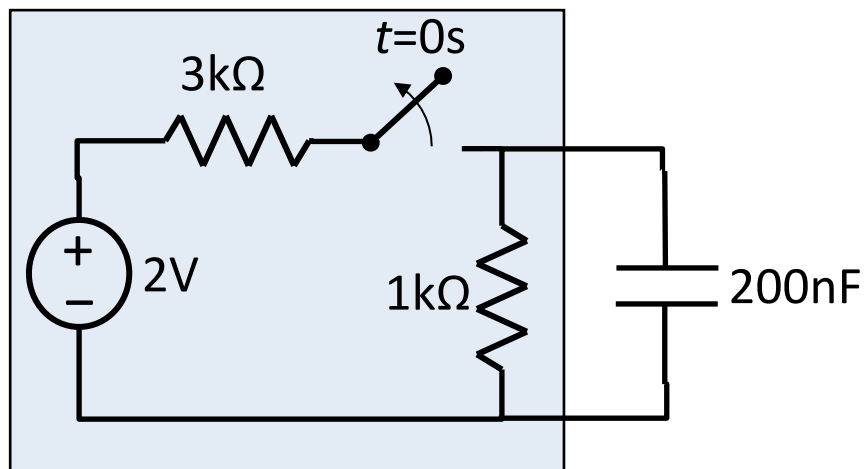
# Overview

The time dependence of voltages and currents are of interest in circuits that include **switches**. The Thévenin equivalent circuit in each time interval should be considered, for example:




$t < 0s$  calculation details:


$$v_{oc} = 2V \frac{1k\Omega}{1k\Omega + 3k\Omega} = 0.5V$$

$$R_T = 1k\Omega \parallel 3k\Omega = 0.75k\Omega$$

$t < 0s$

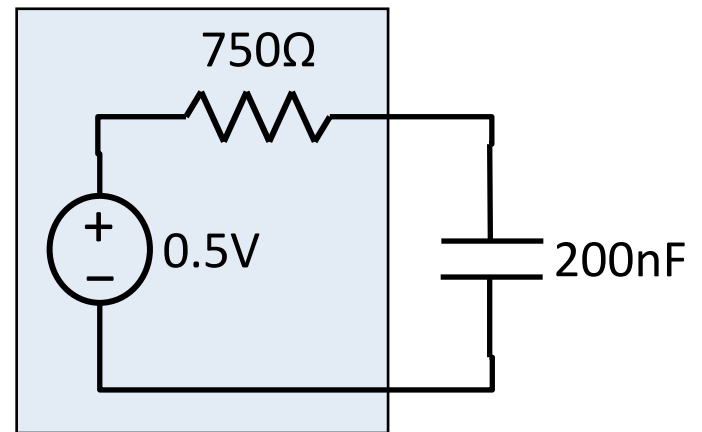

$t \geq 0s$

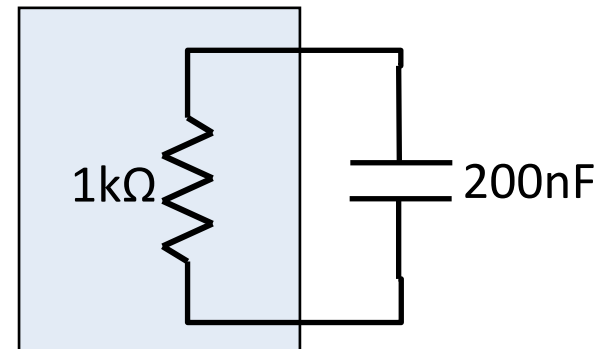

# Overview

It is useful to divide the response of a first order circuit in two ways:

**total response = transient response + steady state response**

*we distinguish the “short-lived” transient and “long-lived” steady-state portions of the circuit response*

**total response = natural response + forced response**

*we distinguish unforced (natural) and forced portions of the circuit response*

# mathematical review 1

Consider the *homogeneous linear first order differential equation*, which corresponds to *unforced (natural)* behaviour:

$$\frac{dx}{dt} + kx = 0$$

The unforced solution is:  
(**natural response**)

$$x_n(t) = X \exp(-kt)$$

Check:

$$\begin{aligned}\frac{dx}{dt} + kx &= \frac{d}{dt} \left( X \exp(-kt) \right) + k \cdot X \exp(-kt) \\ &= -k \cdot X \exp(-kt) + k \cdot X \exp(-kt) \\ &= 0 \quad \checkmark\end{aligned}$$

The value of  $X$  is specified by initial conditions of the circuit variable  $x(t)$ .



# mathematical review 2

Consider the *inhomogeneous linear first order differential equation*, which corresponds to *forced* behaviour:

$$\frac{dx}{dt} + kx = G$$

The particular solution is:  $x_p(t) = G / k$   
(forced response)

Check:  $\frac{dx}{dt} + kx = 0 + k \cdot \frac{G}{k} = G \quad \checkmark$

The complete solution is:  $x(t) = x_p(t) + x_n(t) = G / k + X \exp(-kt)$   
(forced + natural response)  $= c_1 + c_2 \exp(-kt)$

Check:  $\frac{dx}{dt} + kx = -kX \exp(-kt) + k \frac{G}{k} + kX \exp(-kt)$   
 $= G \quad \checkmark$

# mathematical review 3

Consider the general *inhomogeneous linear first order differential equation*, which corresponds to *forced* behaviour:

$$\frac{dx}{dt} + kx = g(t)$$

The particular solution is:  $x_p(t) = \exp(-kt) \int \exp(kt') g(t') dt'$

$$\begin{aligned} \text{Check: } \frac{dx}{dt} &= \frac{d}{dt} \left( \exp(-kt) \right) \cdot \int \dots dt' + \exp(-kt) \cdot \frac{d}{dt} \left( \int \dots dt' \right) \\ &= -k \cdot x_p(t) + \exp(-kt) \cdot \exp(+kt) g(t) \\ &= -k \cdot x_p(t) + g(t) \\ kx &= +k \cdot x_p(t) \end{aligned}$$


$$\frac{dx}{dt} + kx = g(t) \quad \checkmark$$

It is easy to show that the complete solution is:

$$x(t) = x_p(t) + x_n(t)$$
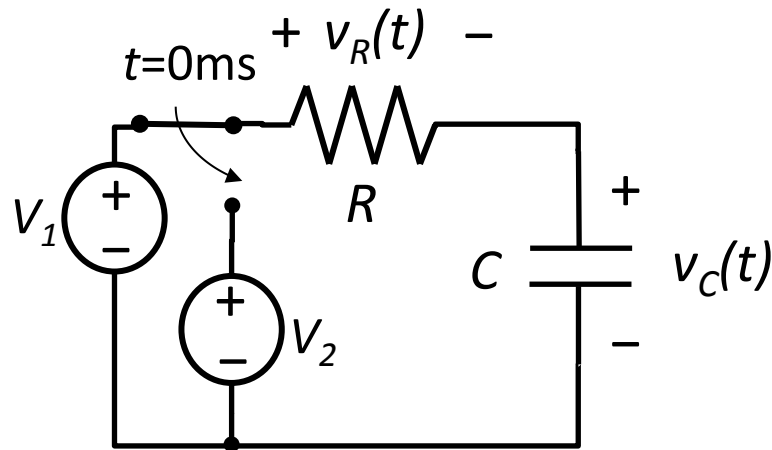
# RC circuit with a (switched) constant input

Consider an  $RC$  circuit being switched at  $t=0$  between two different open circuit voltages. Assume steady state has been reached for  $t < 0$ . We would like to know  $v_C(t)$  and  $v_R(t)$ .




**Note:** The solution to this problem is found with the mathematics of differential equations. However, every feature of the solution can be easily explained by physics ( KCL, KVL, Ohm's Law, and  $q=Cv$  ).

# constant input: capacitor voltage

Consider first the steady state conditions for  $t < 0$ .

$t < 0$

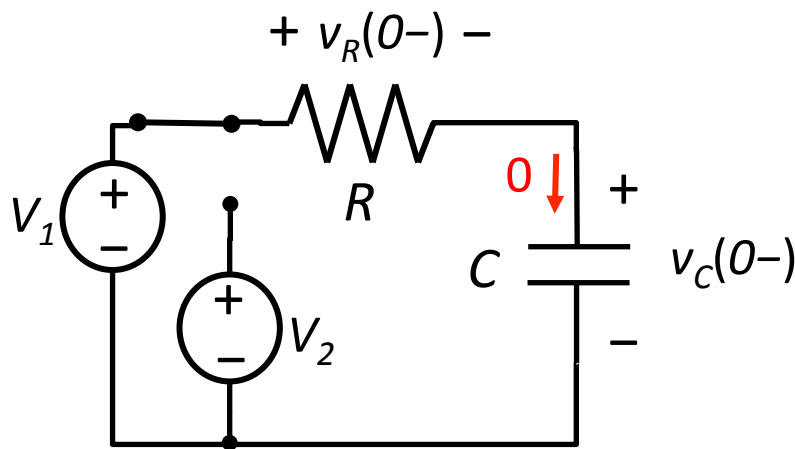

$$\begin{aligned} \text{KVL: } 0 &= -V_1 + v_R + v_C(0-) \\ &= -V_1 + 0 \cdot R + v_C(0-) \end{aligned}$$


$$v_C(0-) = V_1$$

$$\text{Steady state: } i = C \frac{dv_C}{dt} = 0$$

# constant input: capacitor voltage

Consider the circuit equations for  $t > 0$ .

$t > 0$

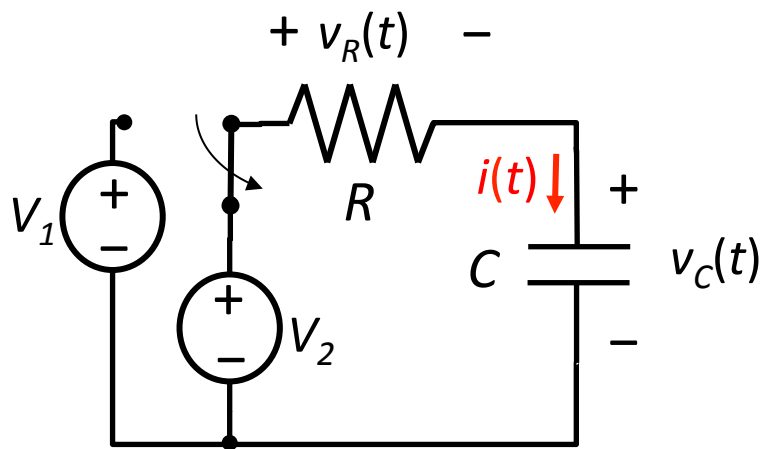

$$\begin{aligned} \text{KVL: } 0 &= -V_2 + v_R + v_C \\ &= -V_2 + R \cdot i + v_C \\ &= -V_2 + R \cdot C \frac{dv_C}{dt} + v_C \end{aligned}$$

$$\frac{dv_C}{dt} + \frac{1}{RC} v_C = \frac{V_2}{RC} \quad t > 0$$

continuity of capacitor voltage:


$$v_C(0+) = v_C(0-) = V_1$$

We have a first-order linear differential equation with initial conditions.

# constant input: capacitor voltage

Consider steady state as  $t \rightarrow \infty$ .

$t \rightarrow \infty$

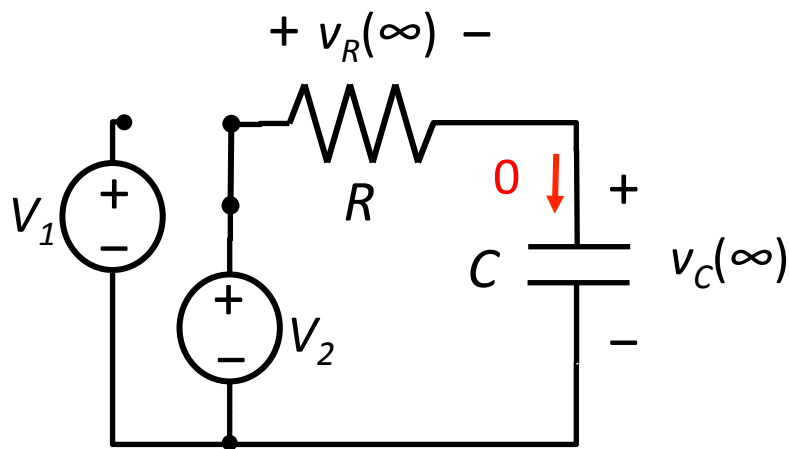

Steady state:  $i = C \frac{dv_c}{dt} = 0$

KVL:  $0 = -V_2 + v_R(\infty) + v_C(\infty)$   
 $= -V_2 + R \cdot 0 + v_C(\infty)$

$$v_C(\infty) = V_2$$

This can also be concluded from the circuit equation for  $t > 0$ :

$$\left. \frac{dv_c}{dt} \right|_{t \rightarrow \infty} + \frac{1}{RC} v_c(\infty) = \frac{V_2}{RC}$$

$$0 + \frac{1}{RC} v_c(\infty) = \frac{V_2}{RC}$$

$$v_c(\infty) = V_2$$

# constant input: capacitor voltage

Solve the differential equation.

$$\frac{dv_c}{dt} + \frac{1}{RC}v_c = \frac{V_2}{RC} \quad t > 0$$

$$v_c(0+) = V_1$$

Recall:

$$\frac{dx}{dt} + kx = G$$

$$x(t) = c_1 + c_2 \exp(-kt)$$

The form of the solution is:  $v_c(t) = c_1 + c_2 \exp\left(-\frac{t}{RC}\right)$


Use our initial and final conditions:  $v_c(\infty) = \lim_{t \rightarrow \infty} \left[ c_1 + c_2 \exp\left(-\frac{t}{RC}\right) \right] = c_1$

$$\therefore c_1 = v_c(\infty) = V_2$$


$$v_c(0+) = c_1 + c_2 \exp(0) = c_1 + c_2$$

$$\therefore c_2 = v_c(0+) - c_1 = V_1 - V_2$$

# constant input: capacitor voltage

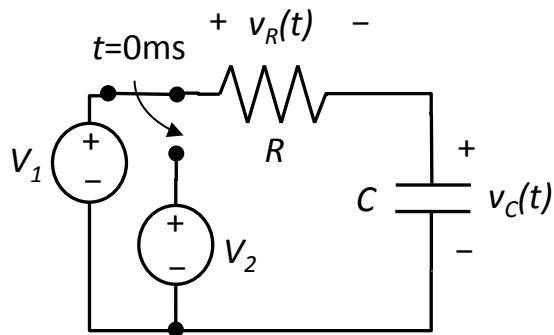

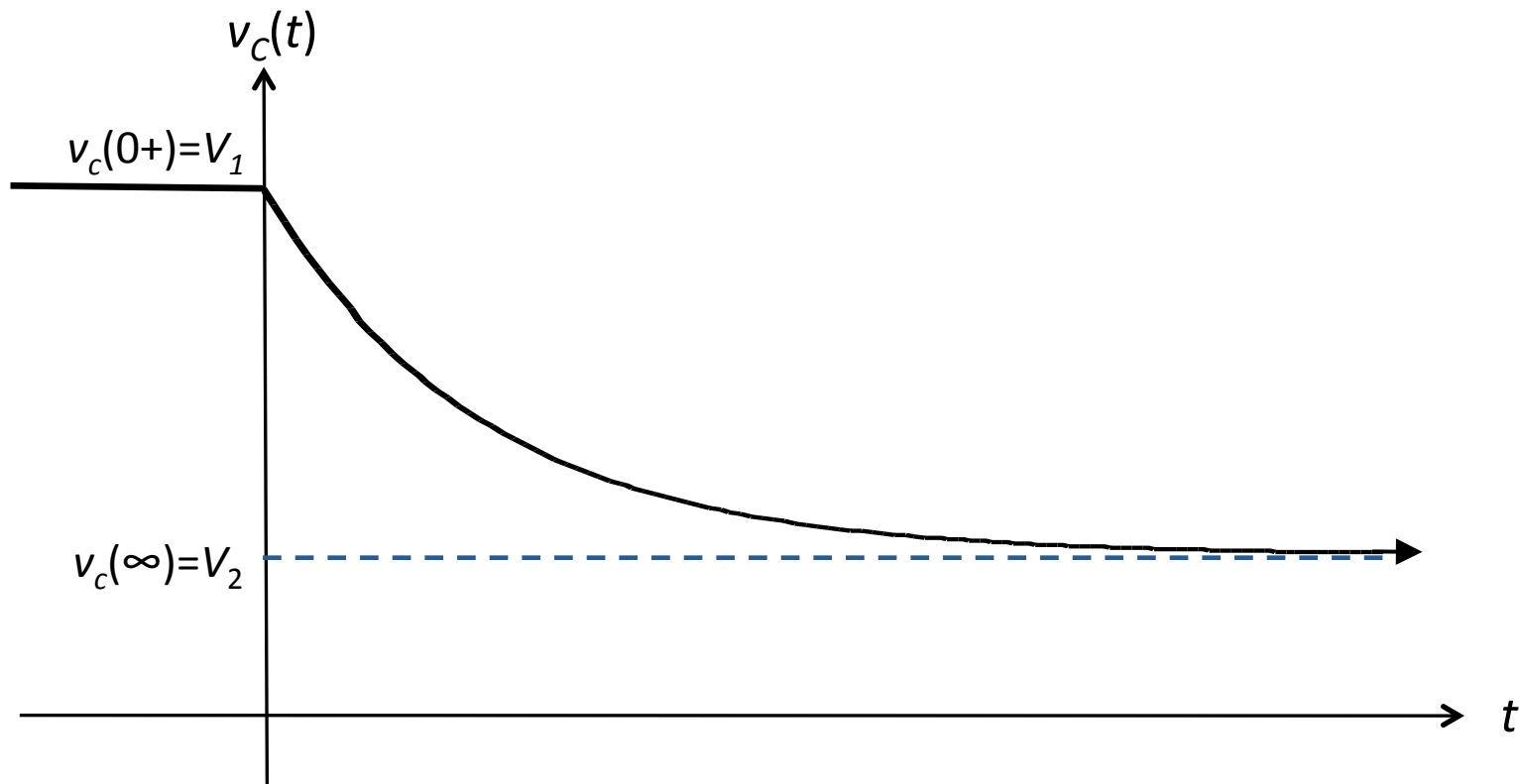solution for  $v_c(t)$  for  $t > 0$  : 
$$v_c(t) = V_2 + [V_1 - V_2] \exp\left(-\frac{t}{RC}\right)$$




\* We assume  $V_1 > V_2$  in this graph.


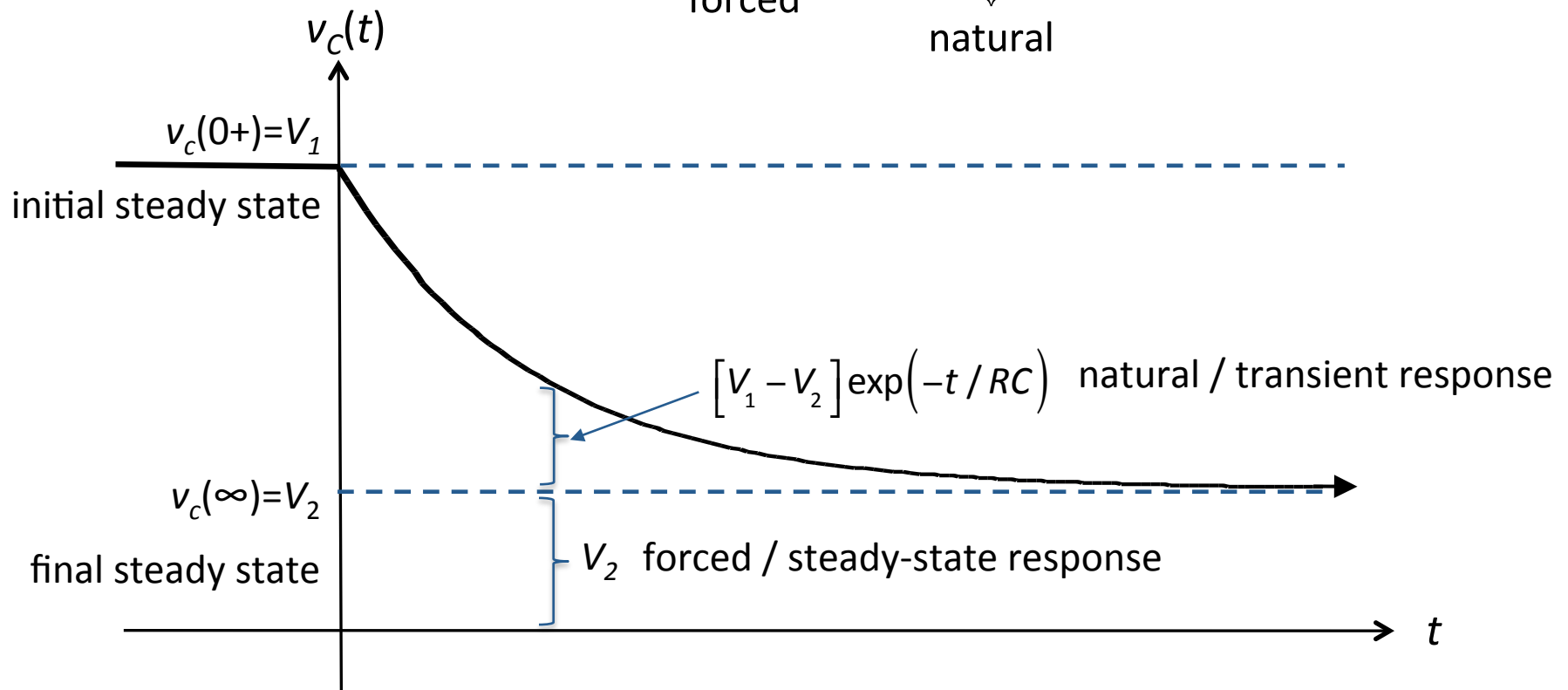
# natural and forced response

The response can be considered as the sum of a natural / transient response and a forced / steady-state response.

$$v_c(t) = \underbrace{V_2}_{\text{forced}} + \underbrace{[V_1 - V_2] \exp\left(-\frac{t}{RC}\right)}_{\text{natural}}$$



\* We assume  $V_1 > V_2$  in this graph.

# time constant


**Time constant:** the characteristic time  $\tau$  of the natural response of a first order circuit. Many important quantities are determined by the time constant.

$$v_{\text{natural}}(t) = \Delta V \exp\left(-\frac{t}{RC}\right) = \Delta V \exp\left(-\frac{t}{\tau}\right)$$

$$\therefore \tau = RC$$

$$\text{Check units: } [\Omega F] = \left[ \frac{V}{A} \frac{C}{V} \right] = \left[ \frac{C}{C/s} \right] = [s]$$

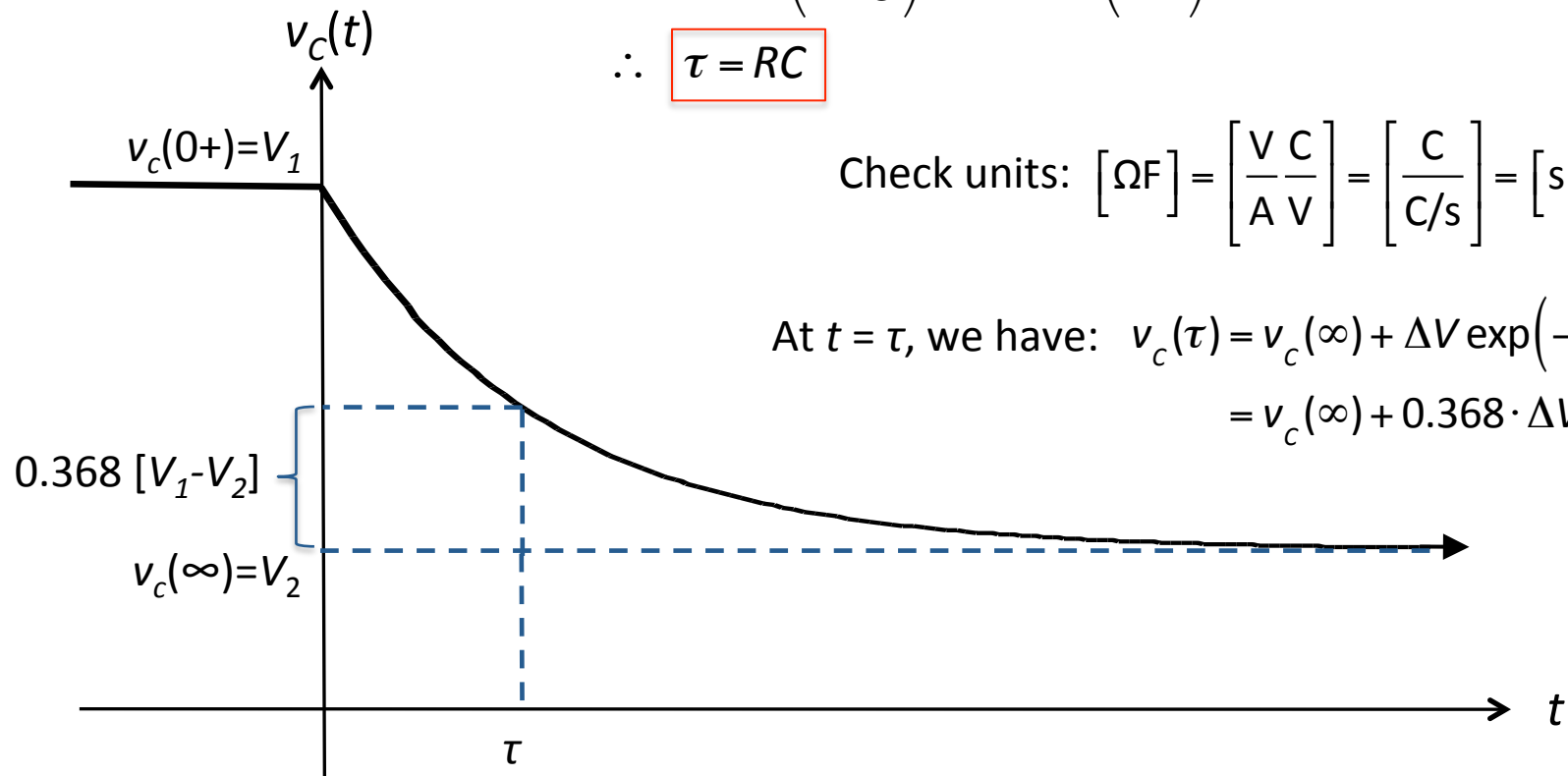
$$\begin{aligned} \text{At } t = \tau, \text{ we have: } v_c(\tau) &= v_c(\infty) + \Delta V \exp(-1) \\ &= v_c(\infty) + 0.368 \cdot \Delta V \end{aligned}$$



\* We assume  $V_1 > V_2$  in this graph.
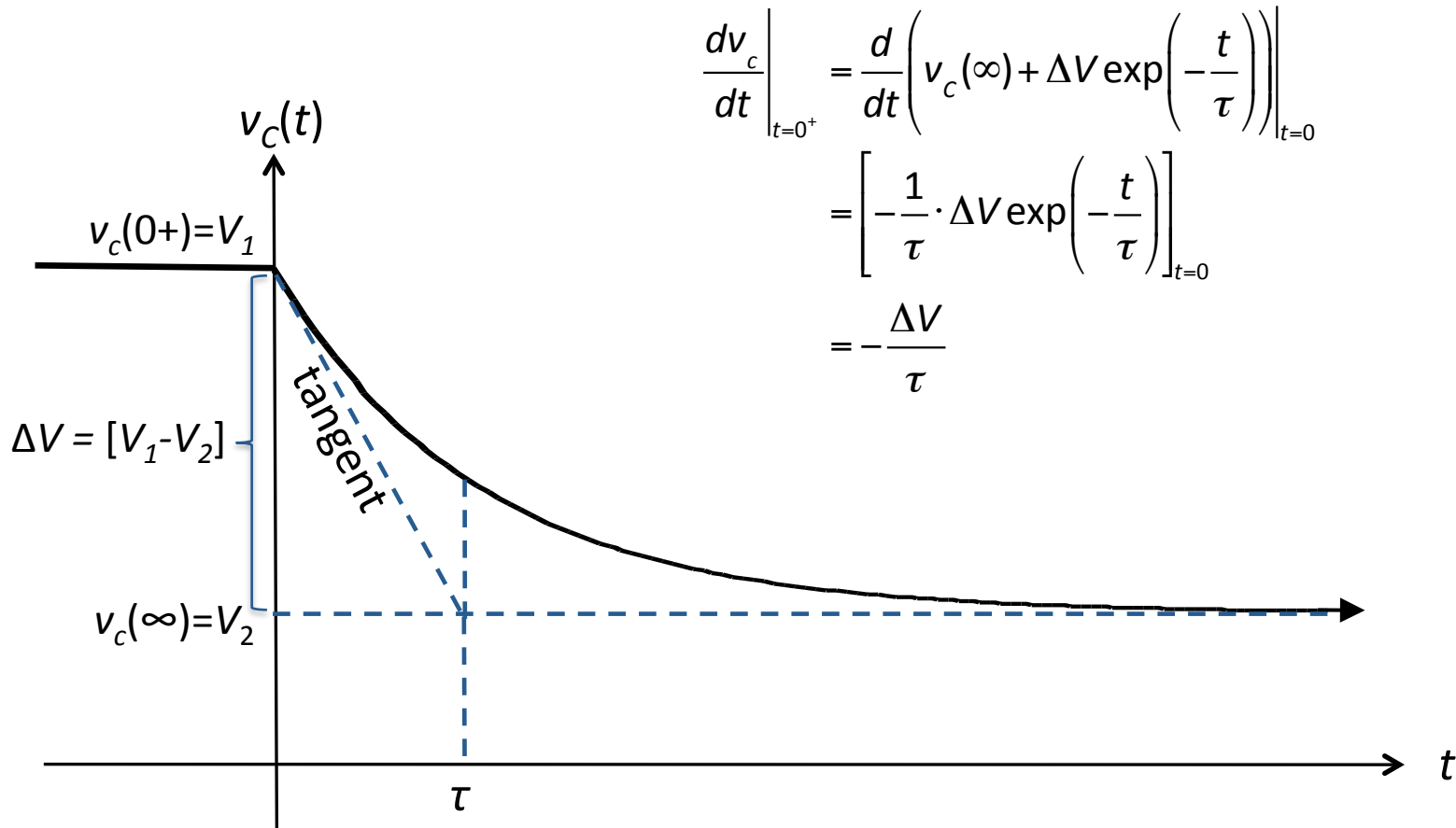
# time constant


The time constant  $\tau$  determines the initial rate of change of voltage, as does the amplitude of the transient response  $\Delta V = v_c(0) - v_c(\infty) = V_1 - V_2$ .



\* We assume  $V_1 > V_2$  in this graph.
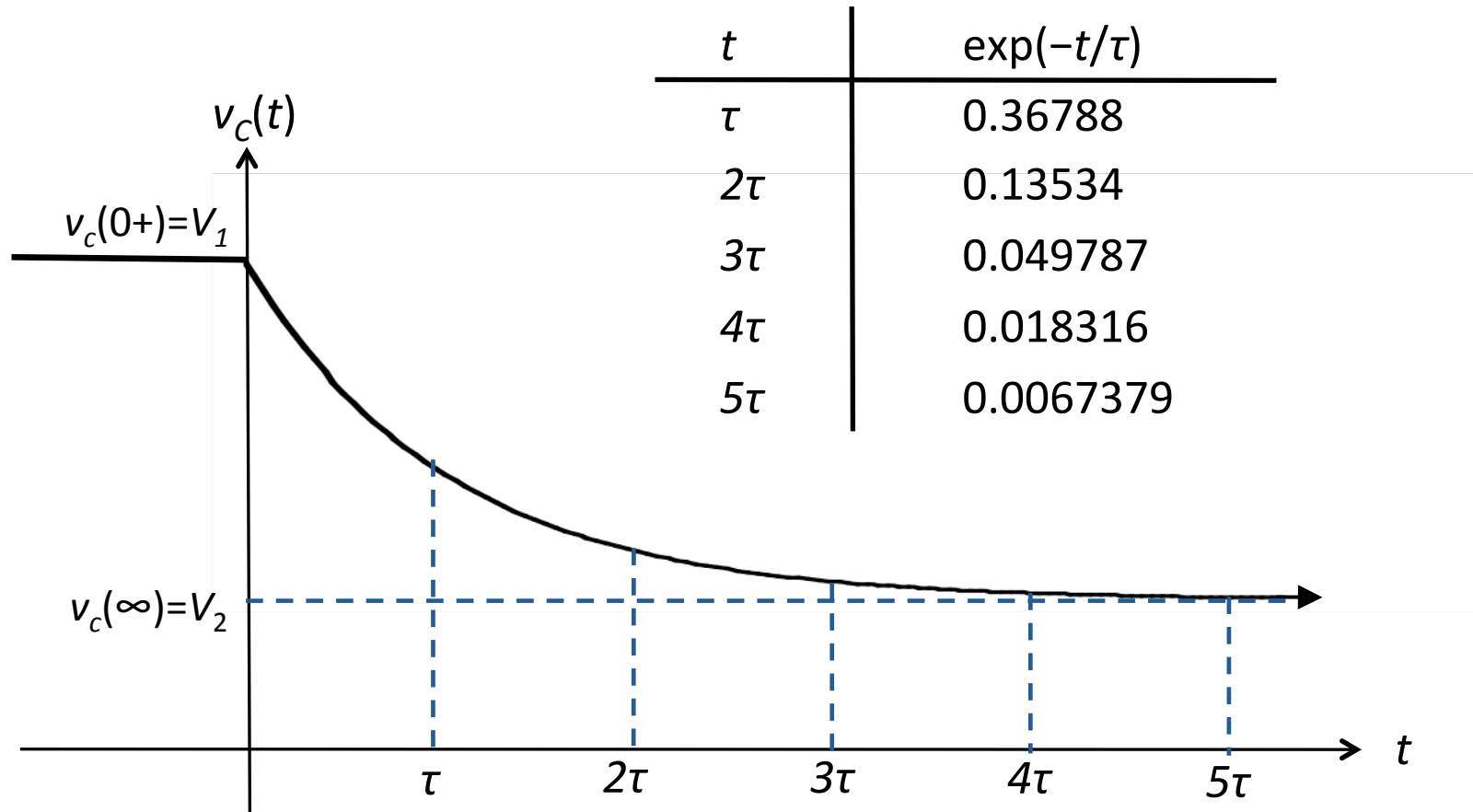
# time constant

After  $5\tau$ , the voltage is within 1% of its final, steady state value. One *often* approximates  $5\tau$  as the “long time” required for a first order circuit to reach steady state conditions.




\* We assume  $V_1 > V_2$  in this graph.

# constant input: resistor voltage

We now consider the resistor voltage  $v_R(t)$ . First consider the interval  $t < 0$ .

$t < 0$

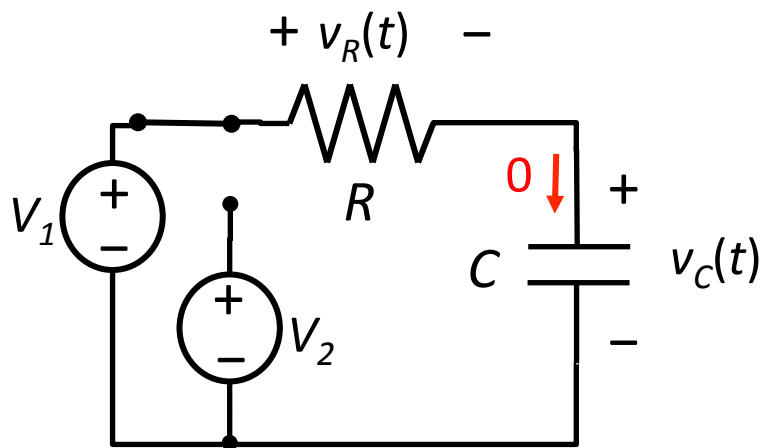

Steady state:  $i = C \frac{dv_C}{dt} = 0$

Ohm:  $v_R(t) = 0 \cdot R$   
 $= 0 \quad t < 0$


It will also be useful to recall our capacitor voltage:

$$\begin{aligned} 0 &= -V_1 + v_R + v_C(0-) \\ &= -V_1 + 0 + v_C(0-) \\ v_C(0-) &= V_1 \end{aligned}$$

# constant input: resistor voltage

Next, consider the circuit equations for  $t > 0$ .

$t > 0$

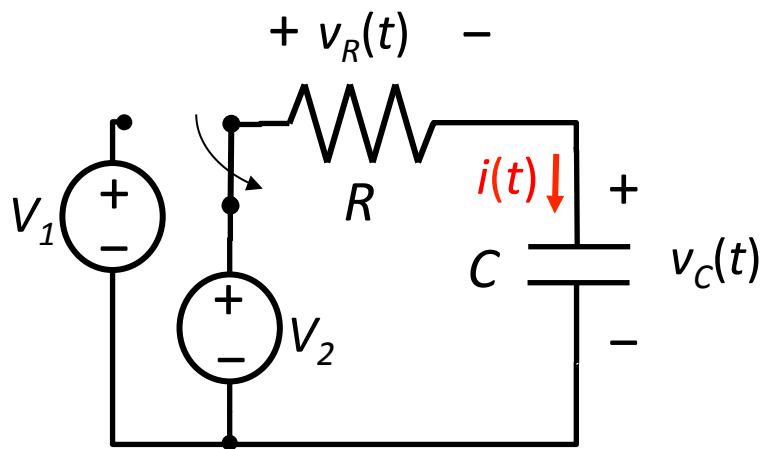

$$\text{KVL: } 0 = -V_2 + v_R + v_C$$

$$= -V_2 + v_R + \frac{1}{C} \int i dt'$$

$$= -V_2 + v_R + \frac{1}{C} \int \frac{v_R}{R} dt'$$

Differentiate the entire equation:

$$0 = \frac{dv_R}{dt} + \frac{1}{RC} v_R$$

The initial value is given by considering *capacitor* voltage continuity:

$$0 = -V_2 + v_R(0+) + v_C(0+)$$


$$= -V_2 + v_R(0+) + V_1$$

$$v_R(0+) = V_2 - V_1$$

# constant input: resistor voltage

Consider steady state as  $t \rightarrow \infty$ .

$t \rightarrow \infty$

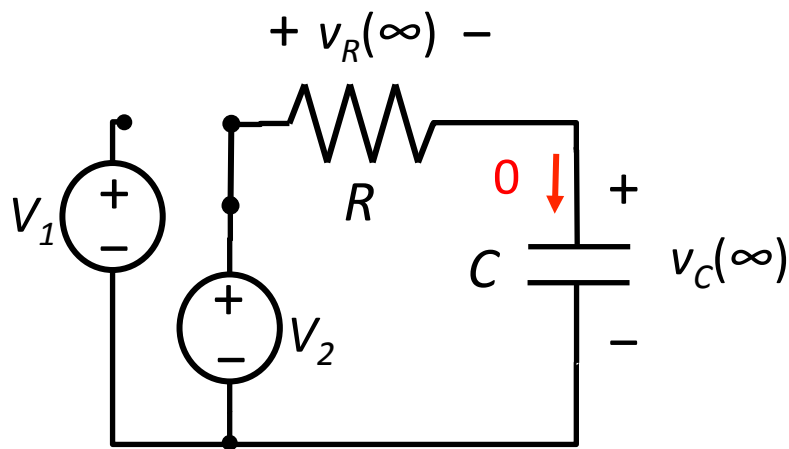

Steady state:  $i = C \frac{dv_C}{dt} = 0$

Ohm:  $v_R(\infty) = 0 \cdot R$   
 $= 0$

This can also be concluded from the circuit equation for  $t > 0$ :

$$\left. \frac{dv_R}{dt} \right|_{t \rightarrow \infty} + \frac{1}{RC} v_R(\infty) = 0$$

$$0 + \frac{1}{RC} v_R(\infty) = 0$$

$$v_R(\infty) = 0$$

# constant input: resistor voltage

Solve the differential equation.

$$\frac{dv_R}{dt} + \frac{1}{RC}v_R = 0 \quad t > 0$$

$$v_R(0+) = V_2 - V_1$$

Recall:

$$\frac{dx}{dt} + kx = 0$$

$$x(t) = c_2 \exp(-kt)$$

The form of the solution is:

$$v_R(t) = c_2 \exp\left(-\frac{t}{RC}\right)$$

Use our initial conditions:

$$v_R(0+) = c_2 \exp(0) = c_2$$

$$\therefore c_2 = v_R(0+) = V_2 - V_1$$


**\*\* Important exercise:** Show that you can find  $v_R(t)$  by

1) Using KVL and our solution for  $v_C(t)$ .


2) Using Ohm's Law and  $i = C dv_C/dt$  with our solution for  $v_C(t)$ .



# constant input: resistor voltage

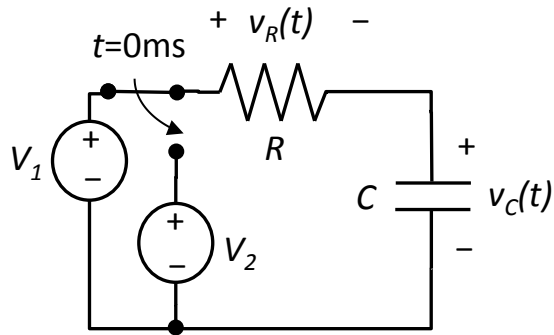


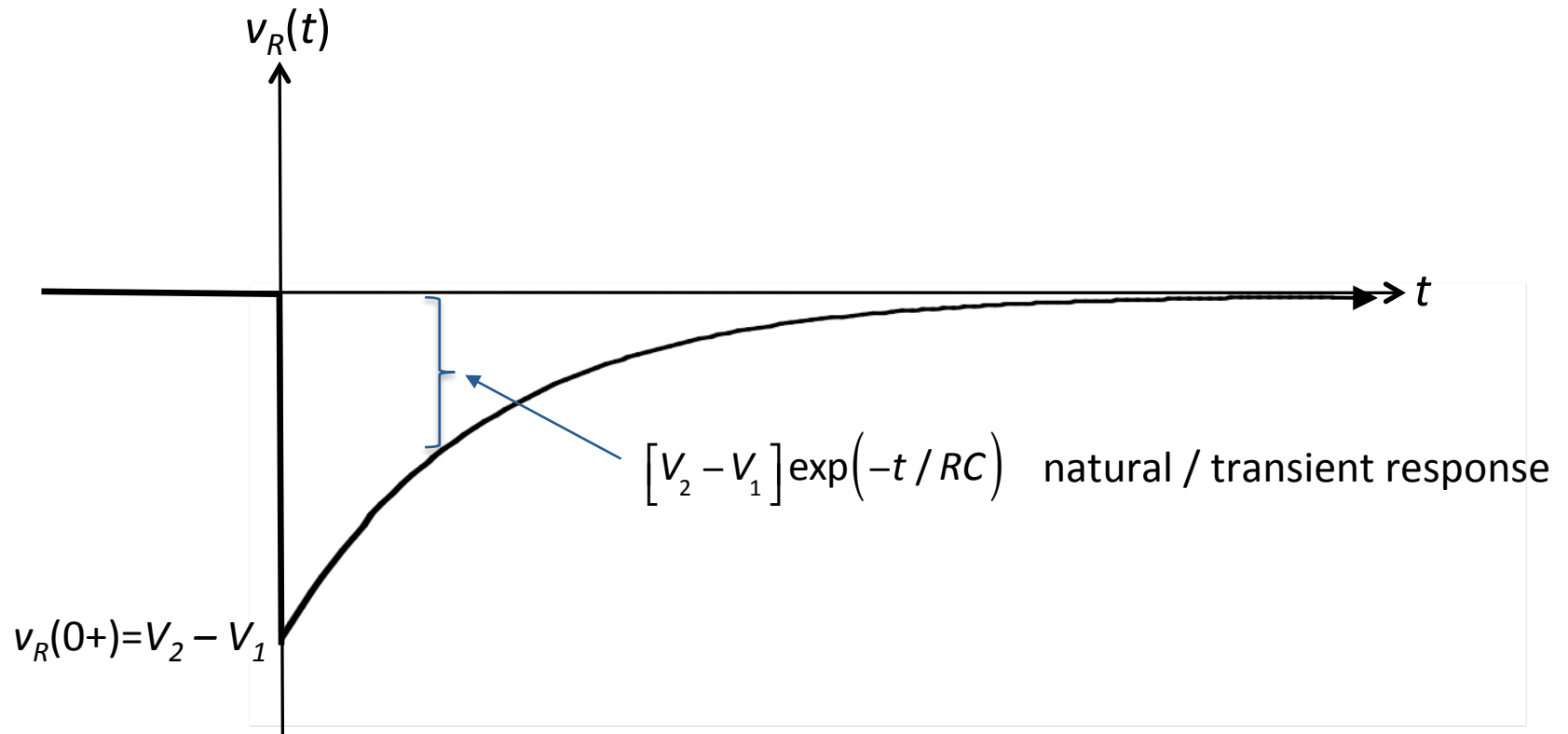solution for  $v_R(t)$  for  $t > 0$  : 
$$v_R(t) = [V_2 - V_1] \exp\left(-\frac{t}{RC}\right)$$




\* We assume  $V_1 > V_2$  in this graph.


# RC circuit: physical explanation

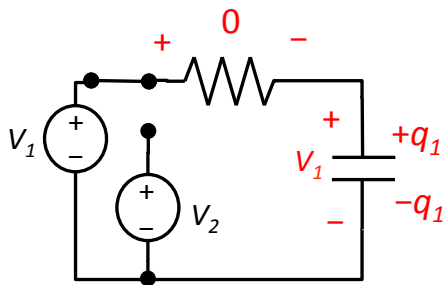



initial steady-state

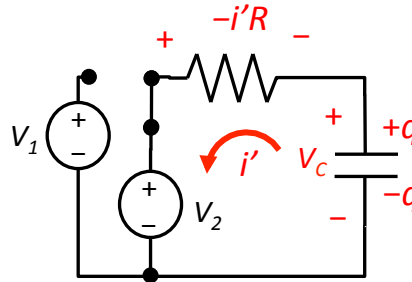

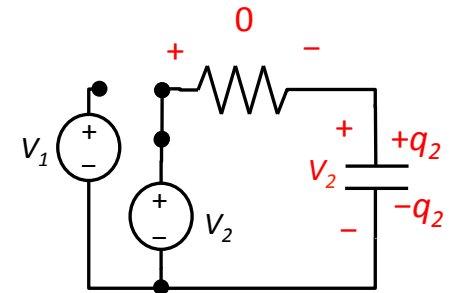transient change in state as  
charge separation is reduced



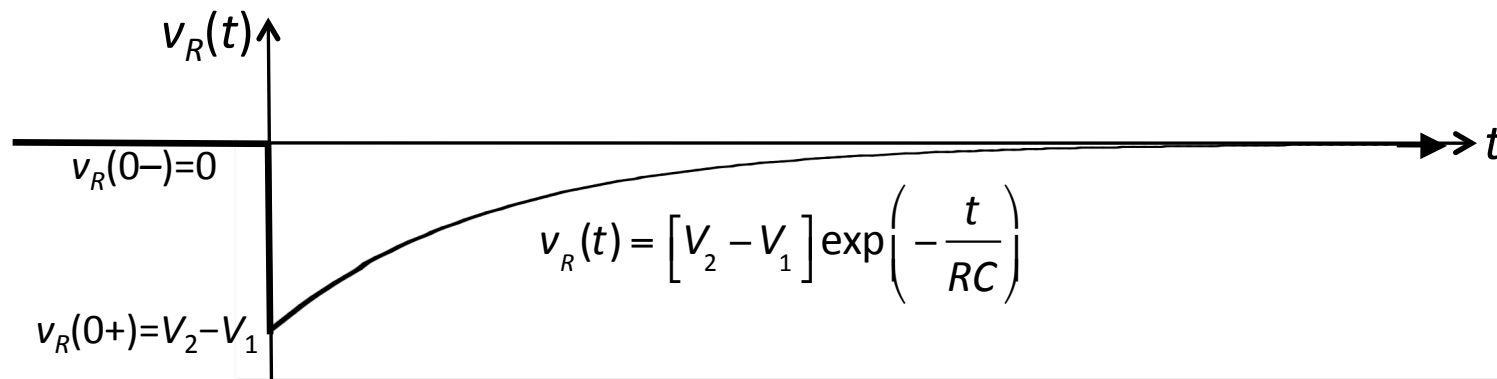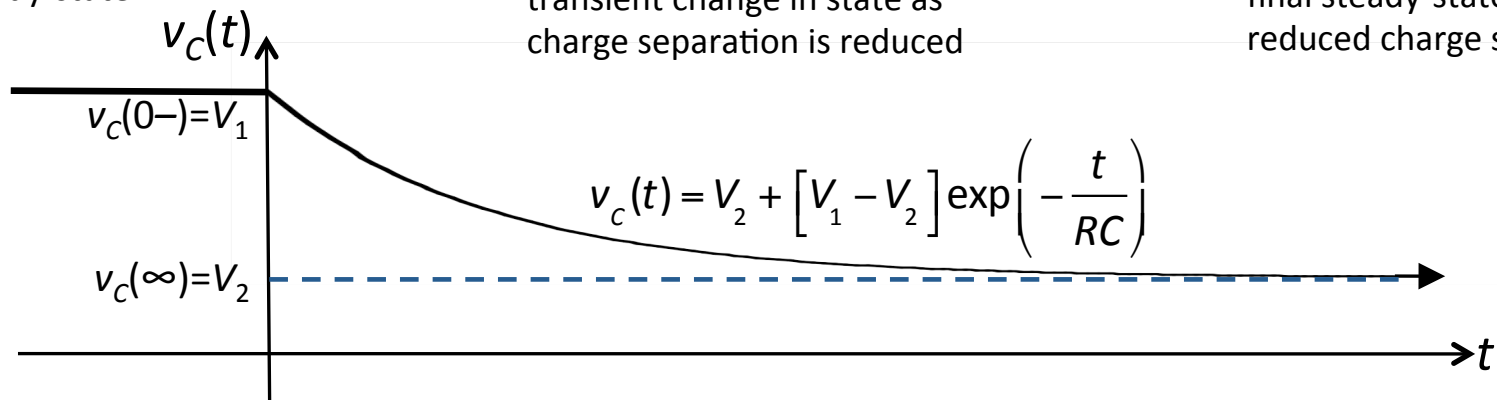final steady-state with  
reduced charge separation



\* We assume  $V_1 > V_2$  in this graph.