

ECSE-200

Electric Circuits 1

February 6, 2019

Lecture 14

4. Circuit Theorems

- Source Transformations (5.2) Today's lecture
 - Linearity and the Principle of Superposition (5.3)
 - Thévenin's Theorem (5.4)
 - Norton's Theorem (5.5)
 - Maximum Power Transfer Theorem (5.6)
-

(subsections in Svoboda & Dorf reference textbook)

Motivation

- Circuit theorems can **greatly simplify** circuit analysis and provide insight into the operation of circuits

Practical Sources

It is commonly observed in practical sources (as opposed to ideal sources) that:

- power is dissipated when a load is attached to the source (for example, a battery warms up when discharged)
- the voltage from a practical voltage source decreases as current is drawn from the source
- the current from a practical current source decreases as voltage develops across the terminals of the source


While the origin and nature of these effects can be very complex, the **Thévenin and Norton equivalent circuits** are **very useful models** for practical sources.

Practical Voltage Source

A practical voltage source can often be modeled as a **Thévenin circuit**:

→ a voltage source v_{OC} called the “**open circuit voltage**” in series with a resistance R_T , called the “**Thévenin resistance**”.

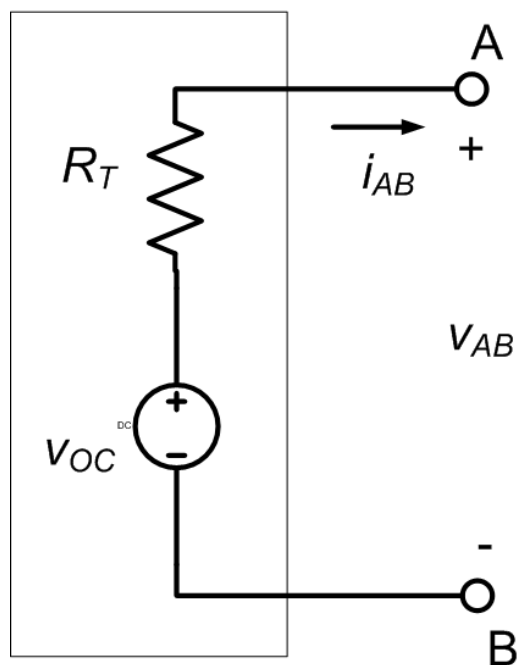
An ideal voltage source is recovered as $R_T \rightarrow 0\Omega$ (corresponding to a short).



practical source
($R_T \neq 0\Omega$)

$$v_{AB} = v_{OC} - i_{AB}R_T$$

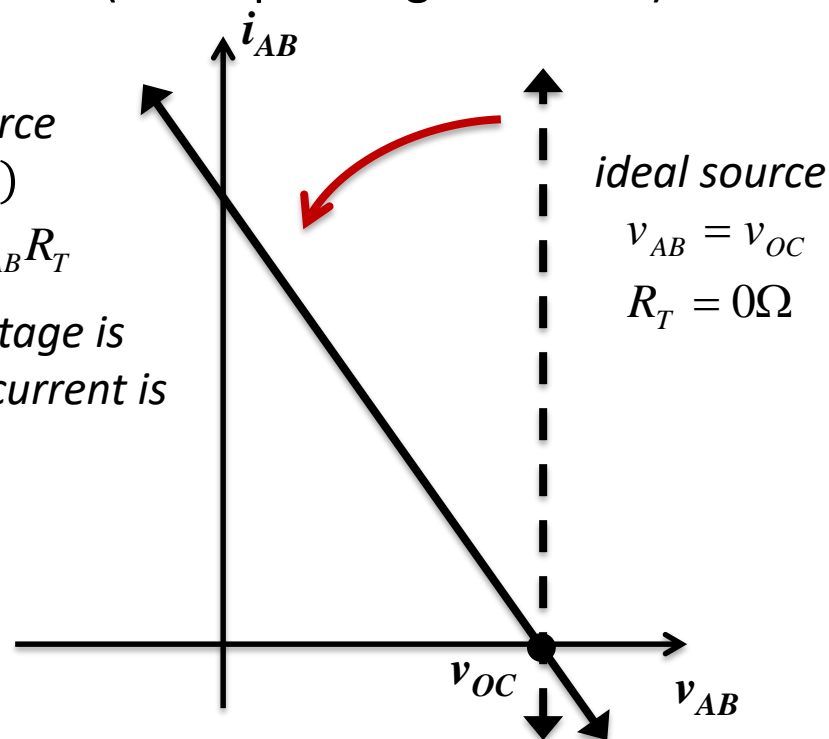*terminal voltage is
reduced as current is
drawn*





Practical Current Source

A practical current source can often be modeled as a **Norton circuit**:

→ an independent current source i_{SC} called the “**short circuit current**” in parallel with a resistance R_T , called the “**Thévenin resistance**.”

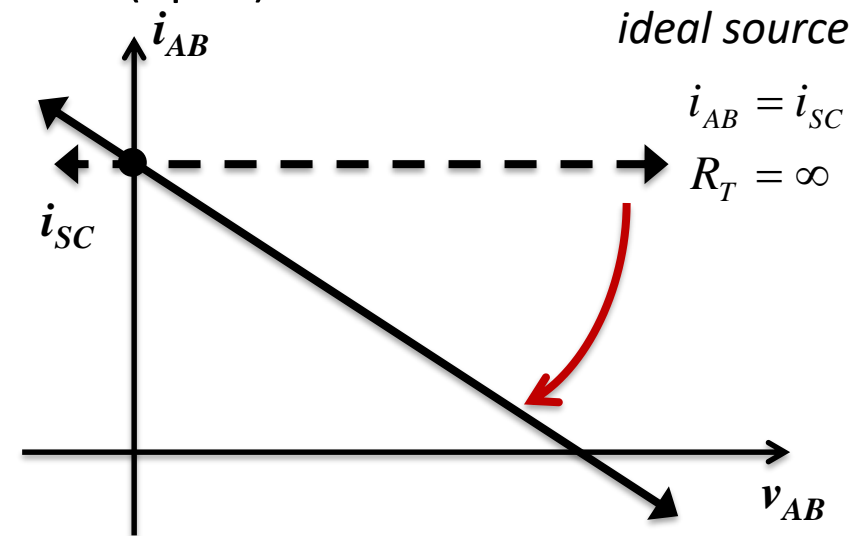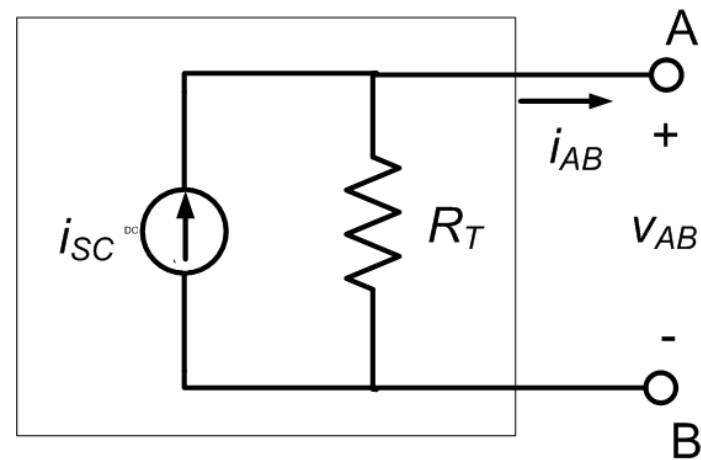An ideal current source is recovered as $R_T \rightarrow \infty$ (open).



practical source $R_T \neq 0\Omega$

$$i_{AB} = i_{SC} - v_{AB} / R_T$$


terminal current is reduced as voltage is developed

Example 1

A portable battery is characterized by an open circuit voltage of 3 V.

The internal (Thévenin) resistance is known to be $200\text{ m}\Omega$.


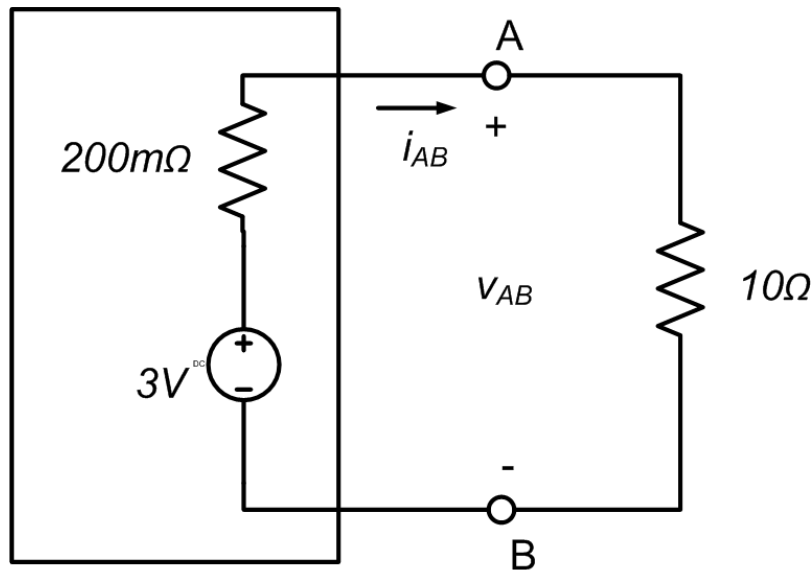
If a resistive load with $10\text{ }\Omega$ equivalent resistance is attached to the battery, what voltage is applied to the load?






Which circuit analysis would you use to find the voltage to the load (i.e. v_{AB})?

- A. Node analysis
- B. Mesh analysis
- C. Current division
- D. Voltage division
- E. Equivalent resistance with ohm's law

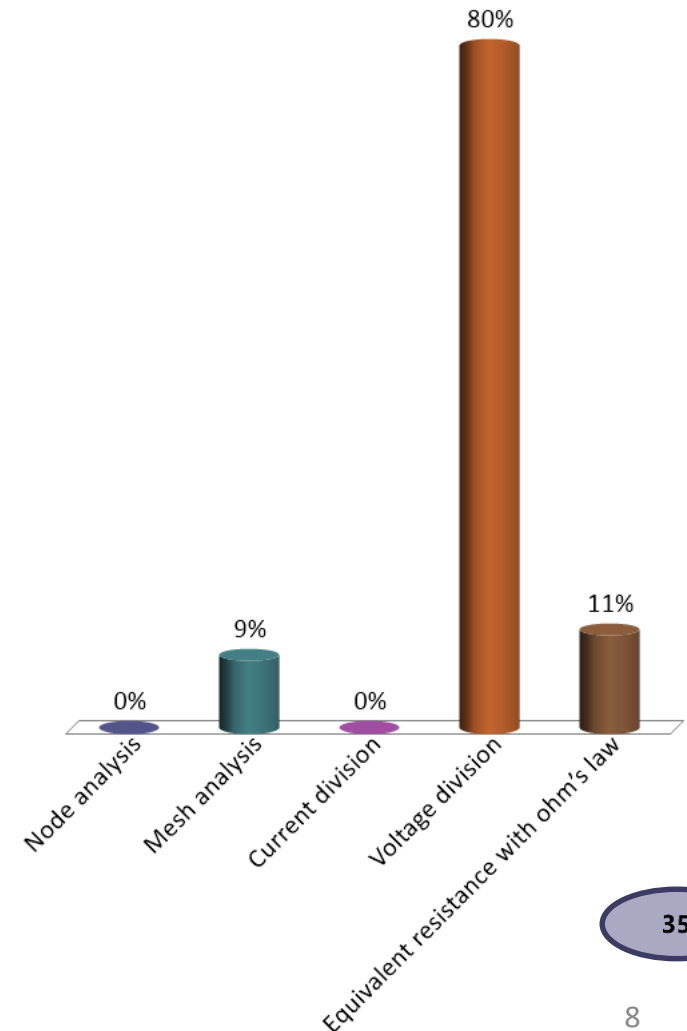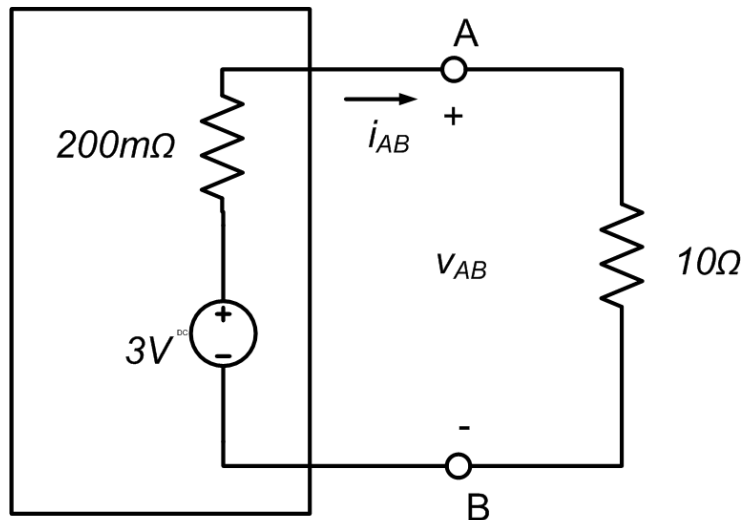

Example 1

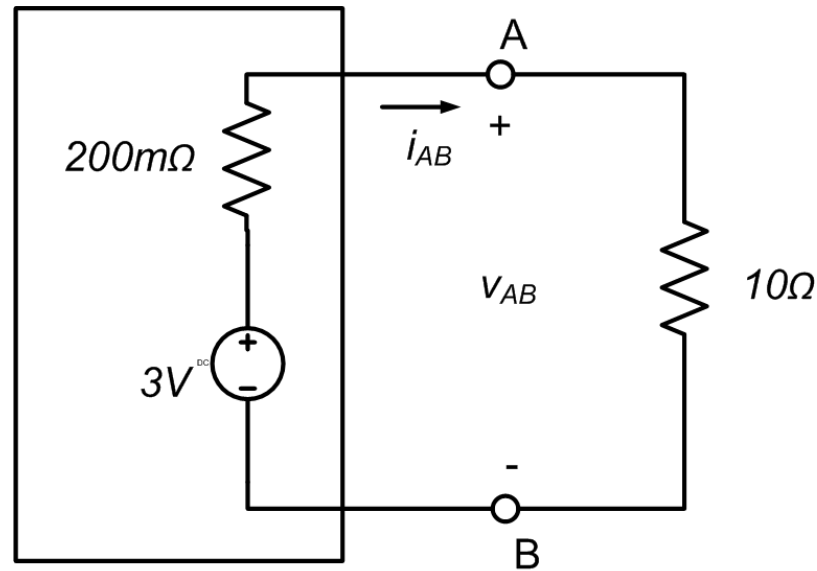

Strategy:

- apply the voltage divider equation

Voltage divider:

$$\frac{v_{AB}}{3V} = \frac{10\Omega}{10\Omega + 0.2\Omega}$$

$$v_{AB} = 0.980 \cdot 3V$$

$$v_{AB} = 2.94V$$

this is a 2% drop in voltage

Example 2

An HVDC (high-voltage direct-current) power supply line is driven by a 800kV source with 2Ω internal resistance.

Of the total 5GW produced by the HVDC source, 10% of the power is lost in internal resistance, including a 3000km transmission line to the load.

What is the resistance of the load, the resistance of the transmission lines, and the voltage at the load?


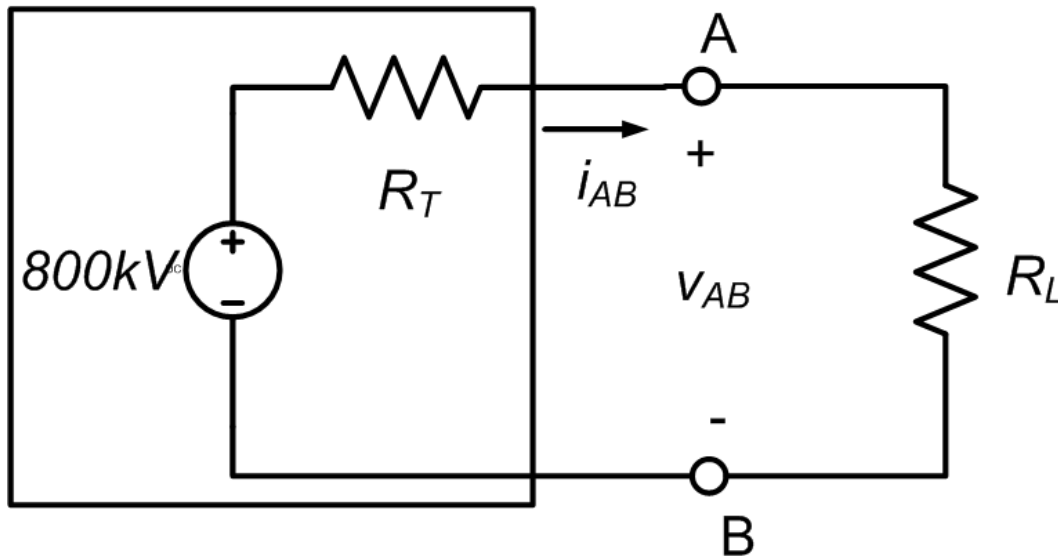


photo: www.alstom.com

Strategy:

- use power and voltage to find resistance

Example 2

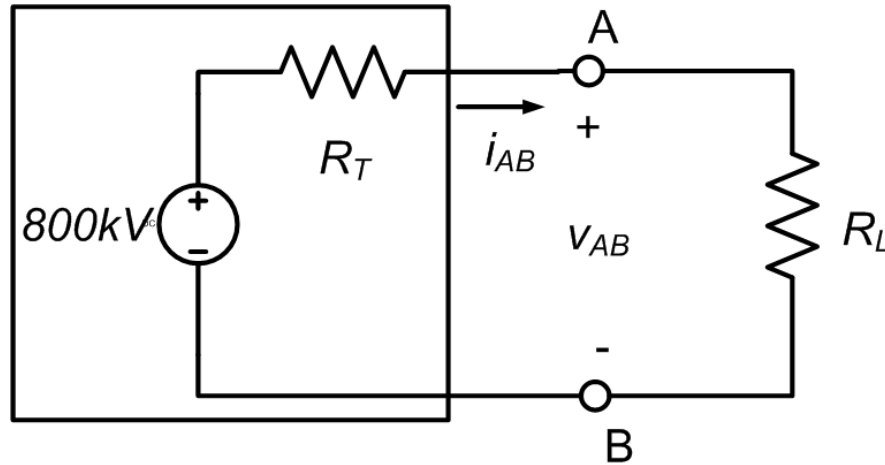

From info given, find current, load and all internal resistances.

$$P_{del} = i_{AB} \cdot 800kV$$

$$i_{AB} = \frac{5GW}{800kV} = 6.25kA$$

$$P_{load} = i_{AB}^2 \cdot R_L$$


$$R_L = \frac{0.9 \times 5GW}{(6.25kA)^2} = 115.2\Omega$$

$$P_{internal} = i_{AB}^2 \cdot R_T$$

$$R_T = \frac{0.1 \times 5GW}{(6.25kA)^2} = 12.8\Omega$$

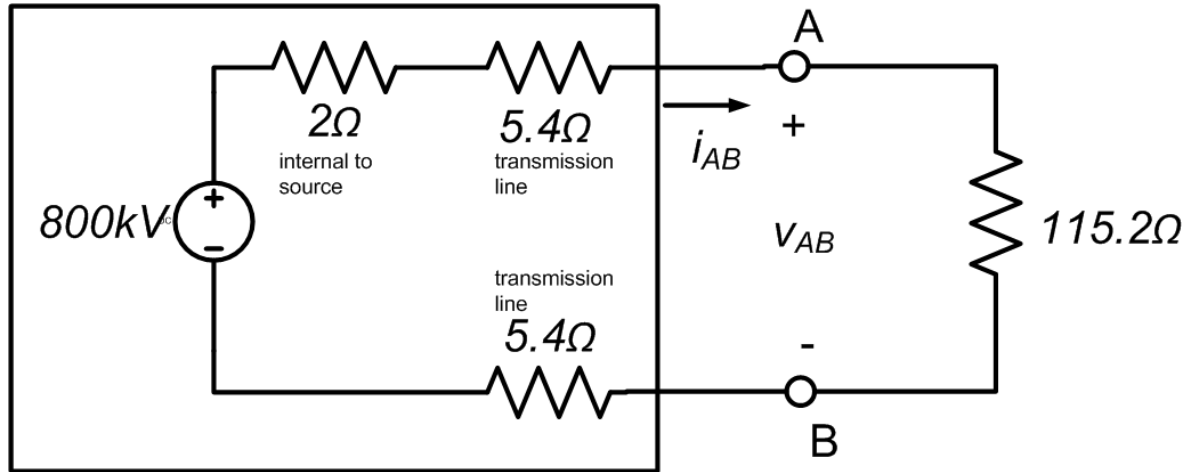Example 2

Model of physical system adjusted based on value found:



Breakdown of internal resistance contributions to find resistance of transmission lines:

$$R_T = R_{source} + 2R_{line} = 12.8\Omega$$

$$R_T = 2\Omega + 2R_{line} = 12.8\Omega$$

$$R_{line} = \frac{12.8 - 2\Omega}{2} = 5.4\Omega$$

voltage divider to find voltage at the load:

$$\frac{v_{AB}}{800kV} = \frac{115.2\Omega}{12.8\Omega + 115.2\Omega}$$

$$v_{AB} = 0.900 \cdot 800kV = 720kV$$


this is a 10% drop in voltage

Source Transformation



Source Transformation:

A Thévenin circuit and a Norton circuit are actually equivalent when their i_{AB} - v_{AB} diagrams are identical!

$$v_{OC} = i_{SC} R_T$$

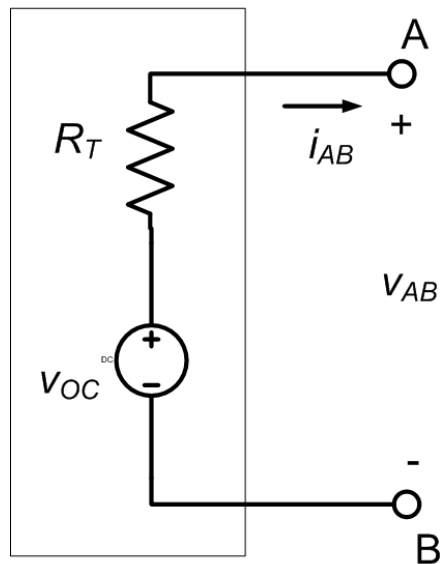


equivalent

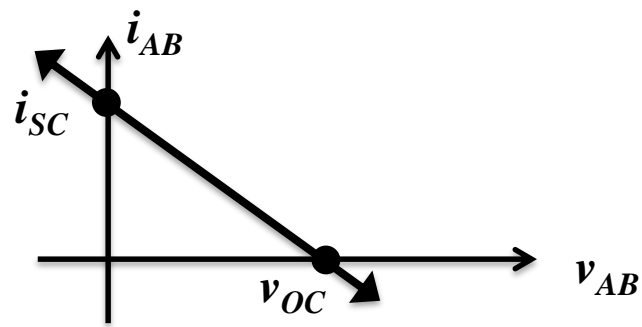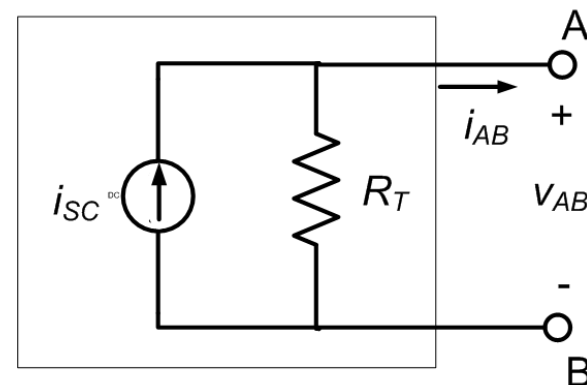

Source Transformation

Proof: Show that the terminal equations relating v_{AB} and i_{AB} are identical for appropriately chosen component values.

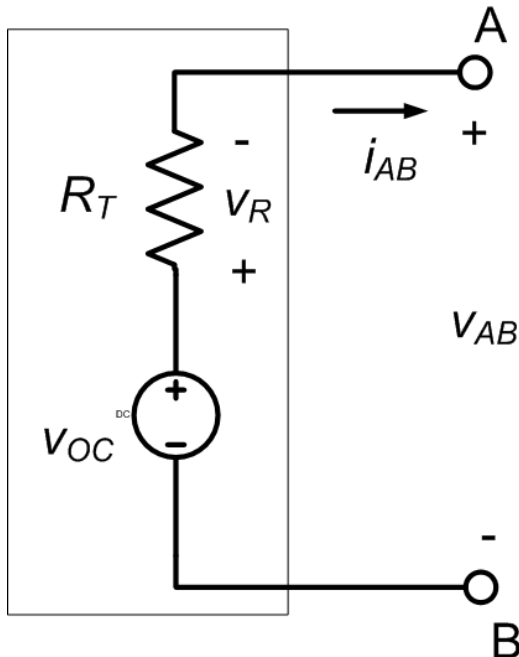In other words, show that the i_{AB} - v_{AB} diagrams are identical:



$$\text{KVL: } 0 = -v_{OC} + v_R + v_{AB}$$


$$\text{Ohm: } v_R = i_{AB} R_T$$

Combining the above:

$$v_{AB} = v_{OC} - i_{AB} R_T$$

Source Transformation

Next, analyze the Norton circuit:

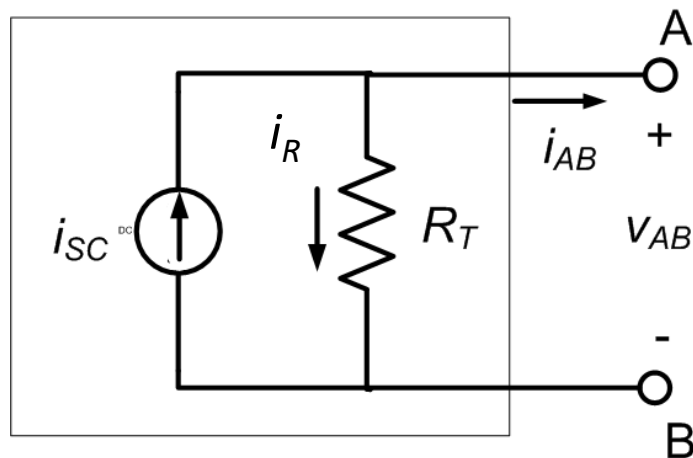

$$\text{KCL: } 0 = -i_{SC} + i_R + i_{AB}$$

$$\text{Ohm: } i_R = v_{AB} / R_T$$

Combining the above:

$$i_{AB} = i_{SC} - v_{AB} / R_T$$

Comparing the two circuit terminal laws:


$$v_{AB} = v_{OC} - i_{AB} R_T$$

$$i_{AB} = i_{SC} - v_{AB} / R_T \rightarrow v_{AB} = i_{SC} R_T - i_{AB} R_T$$

The two circuits are thus equivalent when: $v_{OC} = i_{SC} R_T$

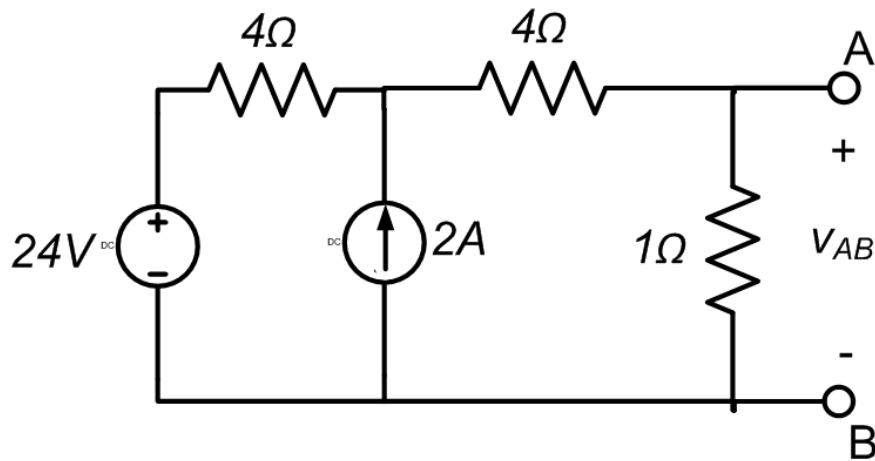Example

Reduce the following circuit to a single **Norton equivalent circuit** with respect to the terminals A and B.




Strategy:

- use transformations between Thévenin and Norton equivalent circuits, working from left to right




Example

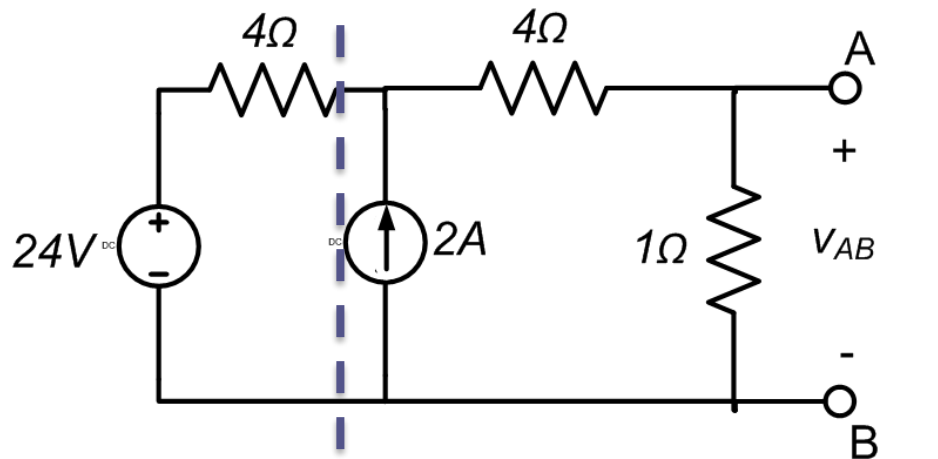


Transform Thévenin circuit on the left into a Norton circuit.
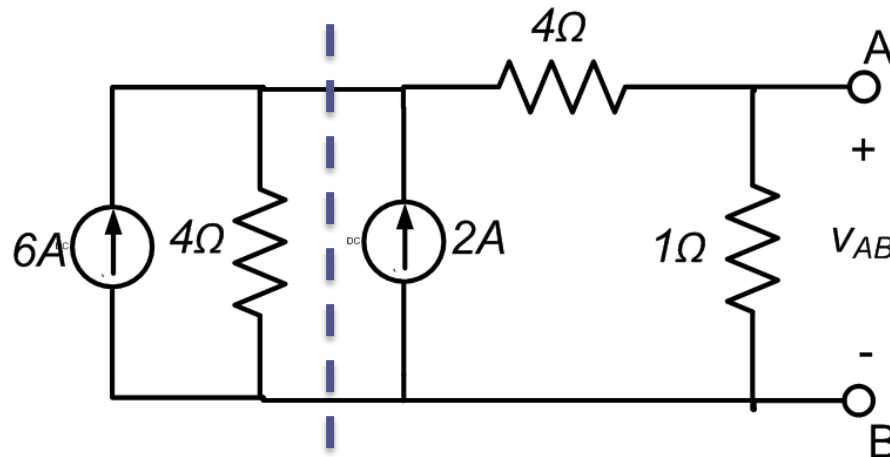
$$\begin{aligned} i_{SC} &= v_{OC} / R_T \\ &= 24V / 4\Omega \\ &= 6A \end{aligned}$$






Example

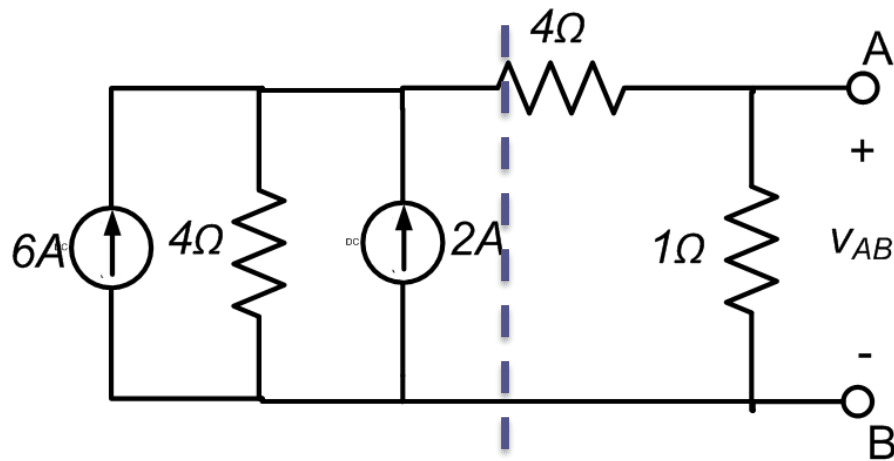


Transform circuit
on the left into
a Norton circuit.

$$i_{SC} = 2A + 6A = 8A$$

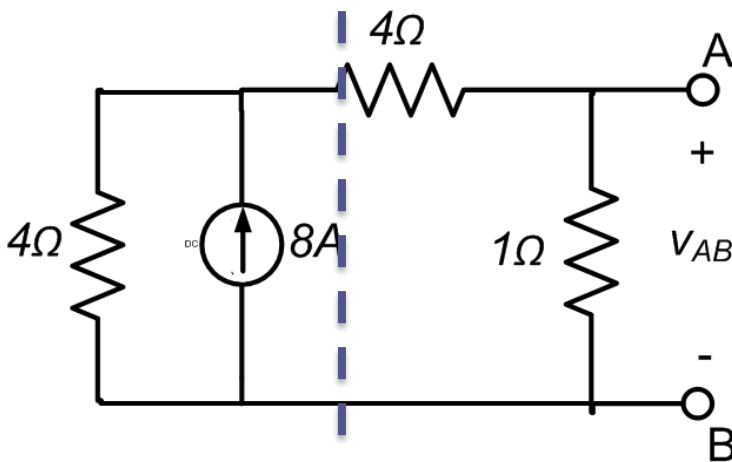


Example

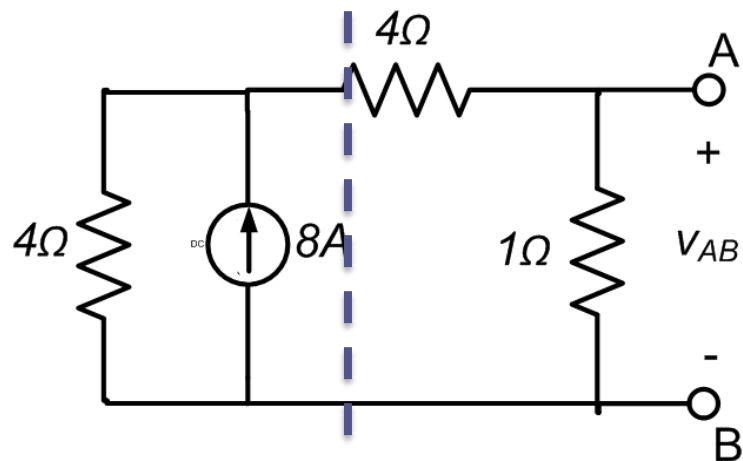


Transform circuit
on the left into
a Thévenin circuit.
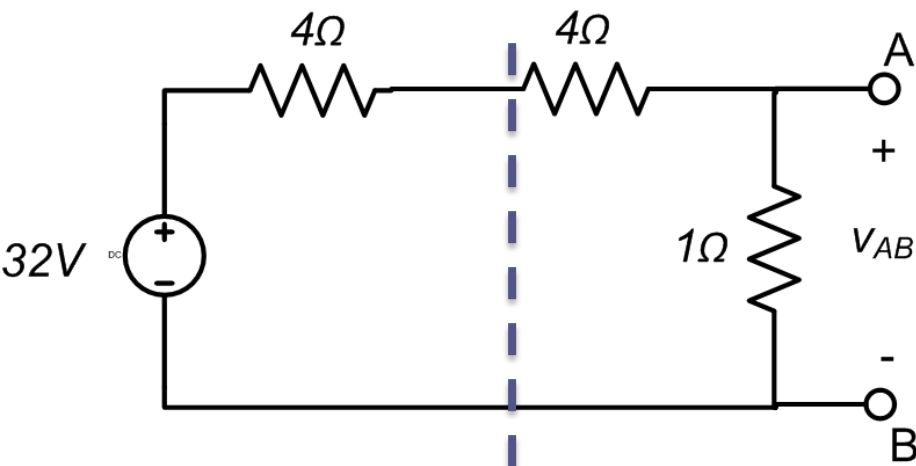
$$\begin{aligned} v_{OC} &= i_{SC} R_T \\ &= 8A \cdot 4\Omega \\ &= 32V \end{aligned}$$



Example

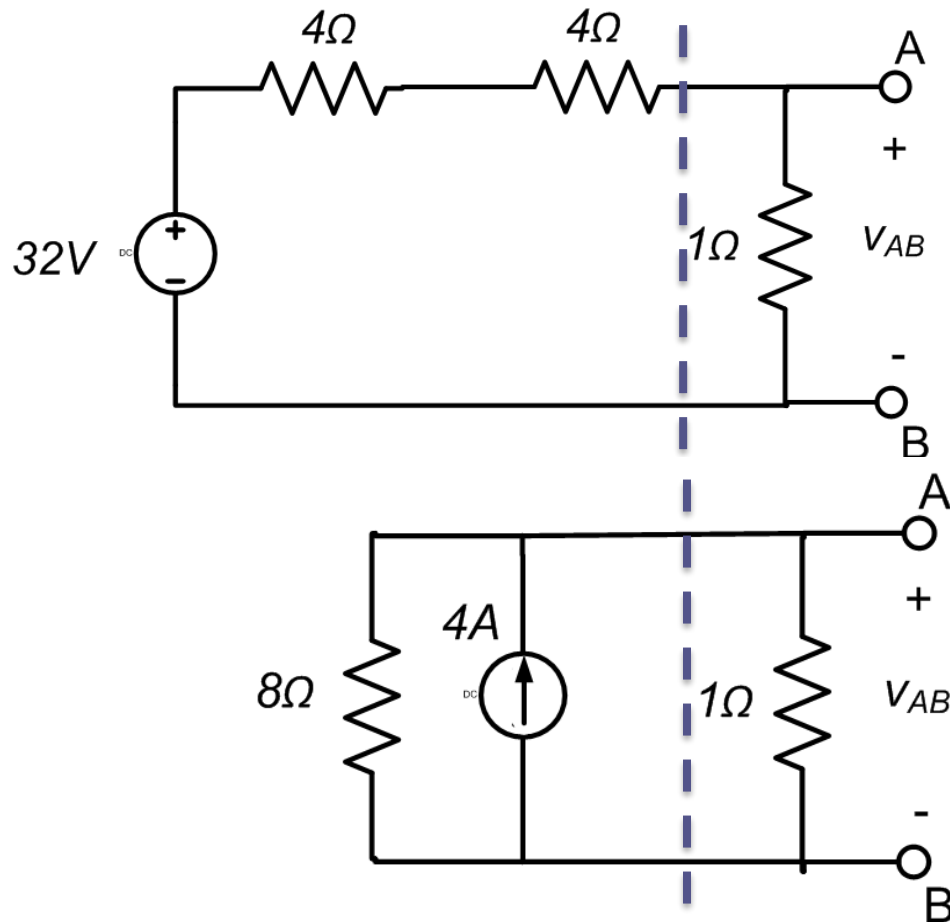


Use series equivalent resistance and transform circuit on the left into a Norton circuit

$$R_T = 4\Omega + 4\Omega = 8\Omega$$

$$\begin{aligned} i_{SC} &= v_{OC} / R_T \\ &= 32V / 8\Omega \\ &= 4A \end{aligned}$$


Example

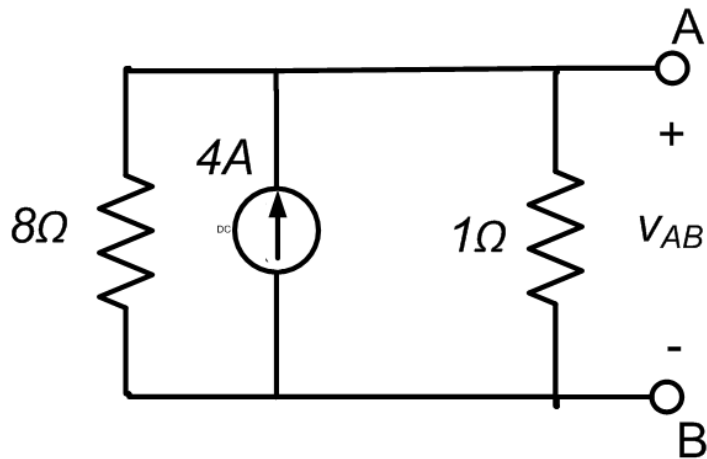

Use parallel equivalent resistance to create a Norton circuit.

$$R_T = 8\Omega \parallel 1\Omega$$
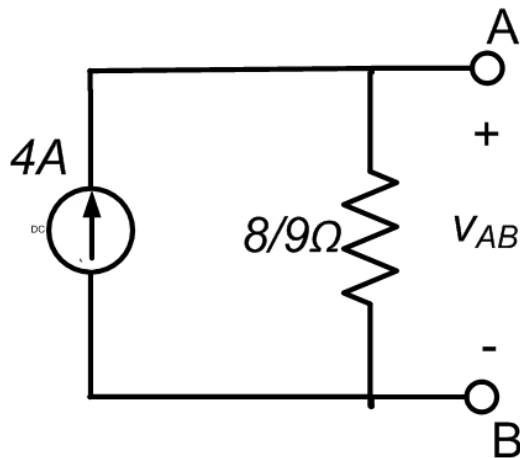
$$R_T = \frac{8\Omega \cdot 1\Omega}{8\Omega + 1\Omega} = \frac{8}{9}\Omega$$



Circuit at the beginning:

