

LAST NAME SOLUTIONS MCGILL ID# _____

FIRST NAME _____ SIGNATURE _____




- Only Faculty standard calculator accepted
- No cellphone allowed
- Show all your work
- Clearly indicate your final answer with the SI unit and multiplier
- You have 45 minutes to complete this quiz

Question 1: Consider the circuit shown. The circuit is in dc steady state for $t < 0$ with the inductor storing zero energy. Answer the following questions.

- a) Plot $v_s(t)$ as a function of time t if $v_s(t) = 5V \cdot u(t)$ where $u(t)$ is the unit step function. [1 pt]
 b) Plot $v_s(t)$ as a function of time t if $v_s(t) = 5V \cdot u(t) - 5V \cdot u(t - 200\mu s)$. [1 pt]

For the following questions, assume $v_s(t) = 5V \cdot u(t) - 5V \cdot u(t - 200\mu s)$.

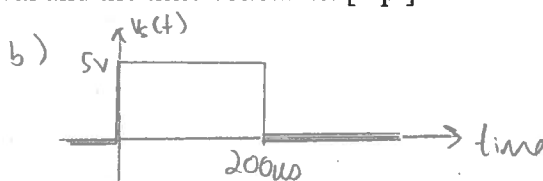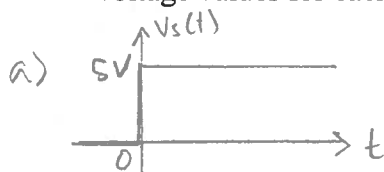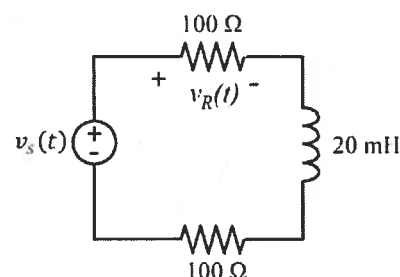- c) Solve for the voltage $v_R(t)$ for $0 < t < 200 \mu s$. [2 pt]
 d) Solve for the voltage $v_R(t)$ for $t > 200 \mu s$. [2 pt]
 e) Plot the voltage $v_R(t)$ versus time t . Clearly indicate the initial and final voltage values for each interval and the time constants. [2 pt]




c) $v_R(t) = 100 \cdot i_L(t)$ $t < 0 \rightarrow v_s(t) = 0V \rightarrow i_L(0^-) = 0A \rightarrow i_L(0^+) = 0A$
 $t \rightarrow \infty \rightarrow v_s(t) = 5V$ (anticipated value) $\rightarrow i_L(\infty) = \frac{5V}{200\Omega} = 25mA$
 $\tau = \frac{L}{R_T} = \frac{20mH}{200\Omega} = 100\mu s$ $\therefore i_L(t) = 25 - 25e^{-t/100\mu s} mA$ $0 < t < 200\mu s$

$$v_R(t) = 2.5 - 2.5e^{-t/100\mu s}, 0 < t < 200\mu s$$


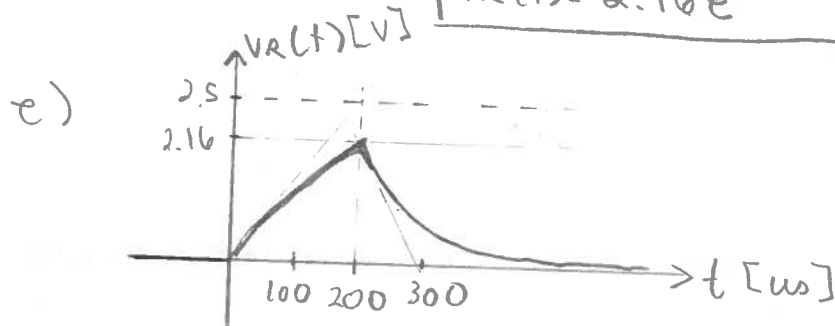
d) $i_L(t_0^-) = i_L(t_0^+) = i_L(200\mu s) = 25 - 25e^{-200/100} = 21.62mA$
 $i_L(\infty) = 0A$
 $i_L(t) = 21.62e^{-(t-200\mu s)/100\mu s} mA, t > 200\mu s$

$$v_R(t) = 2.16e^{-(t-200\mu s)/100\mu s} V, t \geq 200\mu s$$




Question 2: Consider the circuit shown. $u(t)$ is the unit step function and the current-controlled voltage source has a gain of B . The circuit is in dc steady state at $t < 0$ s. Answer the following questions.

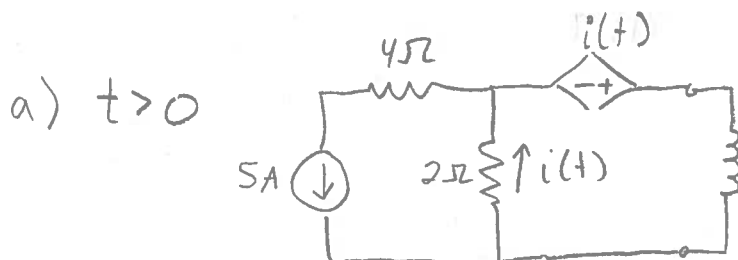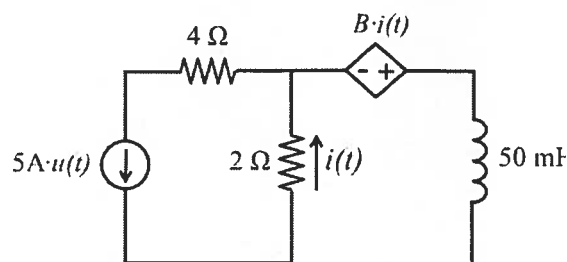- a) Determine if the circuit is stable for $t > 0$ s if $B = 1$ V/A. [2 pt]
 b) Determine the value of the gain B of the dependent source for which the stability condition will change at $t > 0$ s. [2 pt]



Stability if $\tau > 0 \rightarrow \frac{L}{R_T} \geq 0 \therefore R_T \geq 0$

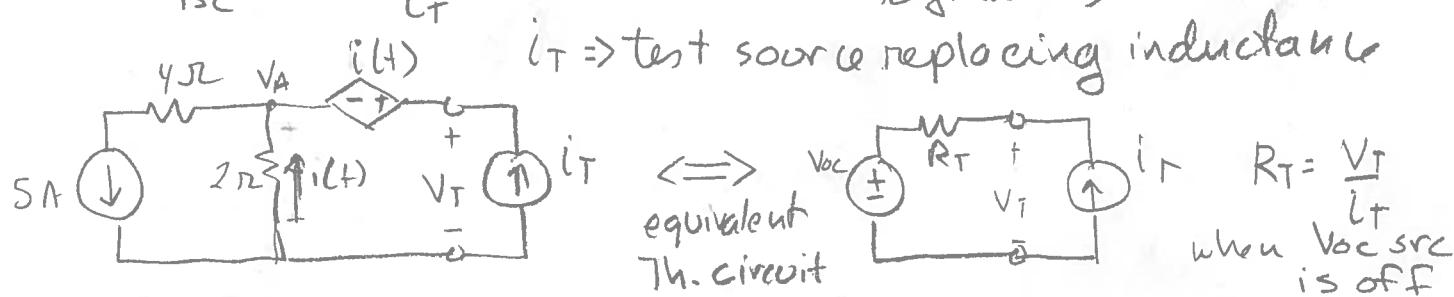$R_T = \frac{V_{oc}}{i_{sc}}$ or $R_T = \frac{V_T}{i_T}$ (more straightforward to find R_T)



KVL $-V_A - i + V_T = 0$

$V_T = V_A + i = -2i + i = -i \quad \underline{V_T = -i}$

KCL @ V_A $5 - i - i_T = 0$

$\underline{i = 5 - i_T} \rightarrow +V_T = -5 + i_T$

if $i_T = 1A \rightarrow V_T = -4V$

$R_T < 0$

unstable

- b) Using PS #13 approach, turning off current src (open) and use test src

KVL: $2i(t) - Bi(t) + V_T = 0$

$V_T = i(t)(B-2) \quad i(t) = -i_T$

$V_T = -i_T(B-2)$

$R_T = \frac{V_T}{i_T} = 2 - B = 0$ when stability changes

$B = 2$