



LAST NAME _____ MCGILL ID# _____

FIRST NAME _____ SIGNATURE _____

- Only Faculty standard calculator accepted
- No cellphone allowed
- Show all your work
- Clearly indicate your final answer with the SI unit and multiplier
- You have 45 minutes to complete this quiz

Question 1: Consider the circuit shown. The switch opens the connection at $t = 0$ s. The circuit reaches steady state before the switch changes its connection state. Answer the following questions.

- Find the solution of the current $i_L(t)$ for $t > 0$ s. [3 pt]
- Plot the current $i_L(t)$ with respect to time t indicating the time constant, the initial and final current values. [2 pt]
- Find the voltage $v_x(t)$ for $t > 0$ s. [2 pt]

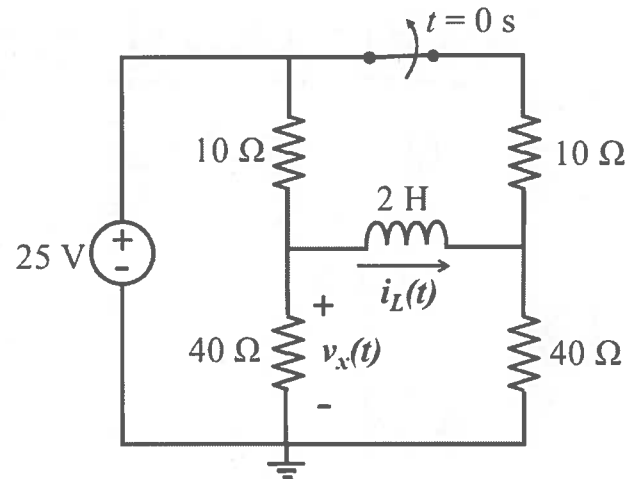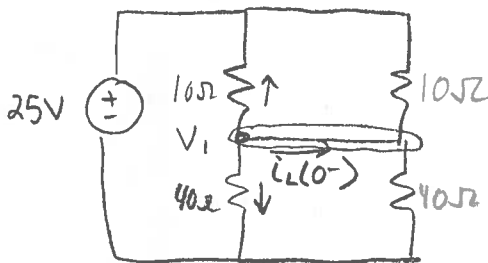
a) $t < 0$ sFIND
INITIAL
CONDITION

$$\text{KCL: } \frac{V_1 - 25\text{V}}{10\Omega} + \frac{V_1}{40} + i_L(0^-) = 0 \quad V_1 = 25\text{V} \cdot \frac{40\Omega // 40\Omega}{40\Omega // 40\Omega + 10\Omega // 10\Omega} = 25\text{V} \cdot \frac{20\Omega}{25\Omega} = 20\text{V}$$

$$\frac{20 - 25}{10} + \frac{20}{40} = -i_L(0^-)$$

$$-\frac{5}{10} + \frac{1}{2} = 0$$

$$i_L(0^-) = i_L(0^+) = 0\text{ A} \quad \text{from continuity of current in voltage}$$

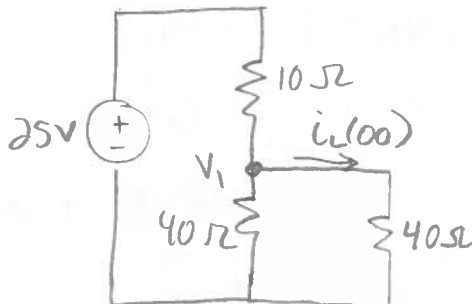 $t \rightarrow \infty$ FIND
FORCED
RESPONSE

$$i_L(\infty) = \frac{V_1}{40\Omega} \quad V_1 = 25\text{V} \cdot \frac{40\Omega // 40\Omega}{40\Omega // 40\Omega + 10\Omega}$$


$$V_1 = 25\text{V} \cdot \frac{20\Omega}{30\Omega} = \frac{50}{3}\text{V}$$

$$i_L(\infty) = \frac{5}{12}\text{V} = 0.417\text{ A}$$

time constant $\tau = L/R_T$

Extra Working Space

R_T

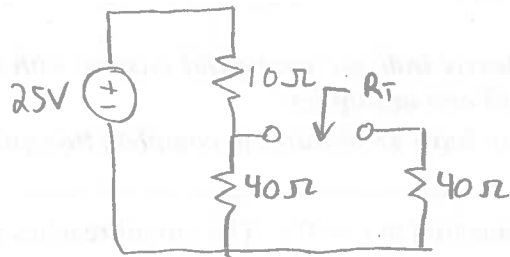


$$R_T = 10\Omega // 40\Omega + 40\Omega = 48\Omega$$

$$R_T = 48\Omega \quad \tau = \frac{2H}{48\Omega} = \frac{1}{24}s = 41.67ms$$


$$i_L(t) = i(\infty) + [i(0^+) - i(\infty)]e^{-t/\tau} \text{ A}$$

$$i_L(t) = \frac{5}{12} \text{ A} - \frac{5}{12} e^{-24t} \text{ A}$$

b)

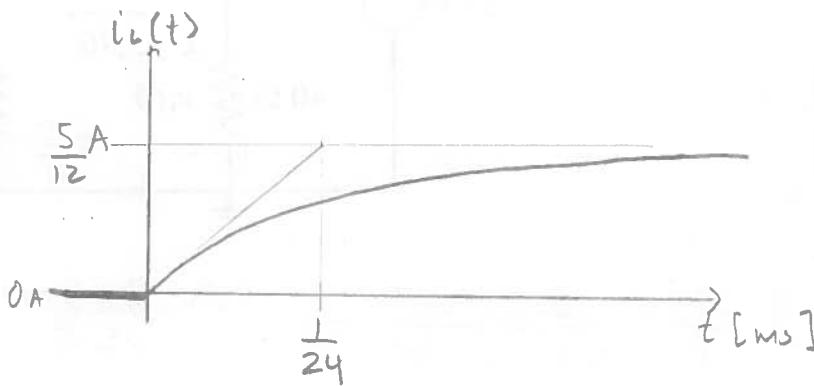

c) $t > 0$

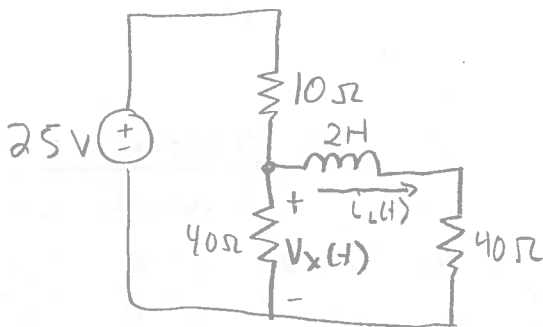

$$\text{KCL: } \frac{V_x(t)}{40\Omega} + \frac{V_x(t) - 25V}{10\Omega} + i_L(t) = 0$$

$$V_x + 4V_x - 100 + 40i_L = 0$$

$$5V_x = 100 - 40i_L$$

$$V_x = 20 - 8i_L$$

$$= 20 - \frac{2}{3} \cdot \frac{5}{12} + \frac{2}{3} \cdot \frac{5}{12} e^{-24t}$$

$$V_x(t) = \frac{50}{3} \text{ V} + \frac{10}{3} e^{-24t} \text{ V}$$


Question 2: Consider the circuit shown. The switch closes and makes the connection at time $t = 0$ s. The circuit reaches steady state before the switch changes its connection.

The voltage across the $10\ \Omega$ resistor as shown in the circuit is

$$v(t) = 6 + 3e^{-2t} \text{ V for } t > 0 \text{ s}$$

Answer the following questions.

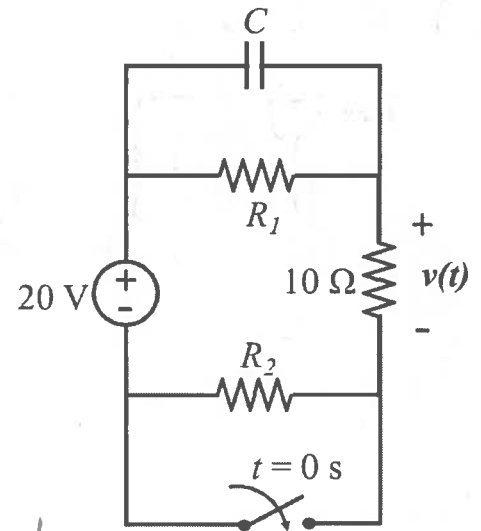
- Determine the time constant of this circuit. [1 pt]
- Find R_1 , R_2 , and C . [3 pt]
- Determine the energy stored in the capacitor at $t = 0$ s. [2 pt]



a) $\tau = \frac{1}{2} \text{ s} = 0.5 \text{ s}$

b) $t \rightarrow \infty$ to find R_1 since steady-state blocks current thru capacitor and $V_{R2} = 0 \text{ V}$ so no current

equiv circuit is

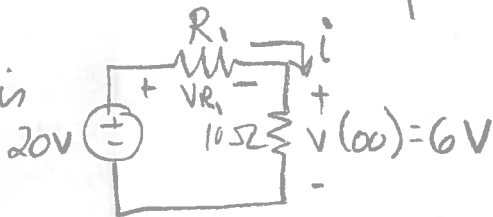

1) current through R_1

$$i = \frac{6 \text{ V}}{10 \Omega} = 0.6 \text{ A}$$


3) $R_1 = \frac{V_{R1}}{i} = \frac{14 \text{ V}}{0.6 \text{ A}}$

2) Voltage across R_1 is (KVL)

$$-20 \text{ V} + V_{R1} + 6 \text{ V} = 0 \quad V_{R1} = 14 \text{ V}$$

$$R_1 = 23\frac{1}{3} \Omega$$

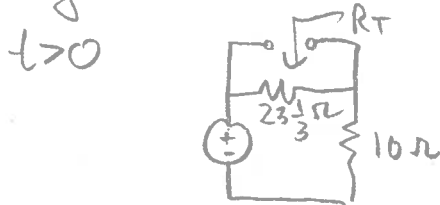ii) To find C , use time constant and R_T





$$R_T = 23\frac{1}{3} \parallel 10 \Omega = 7 \Omega$$

$$\frac{1}{2} \text{ s} = RC = 7 \Omega \cdot C$$

$$C = \frac{1}{14} \text{ F} = 71.429 \mu\text{F}$$

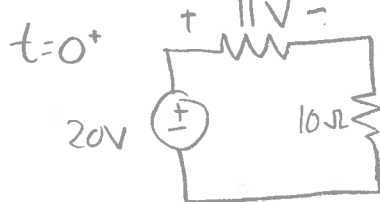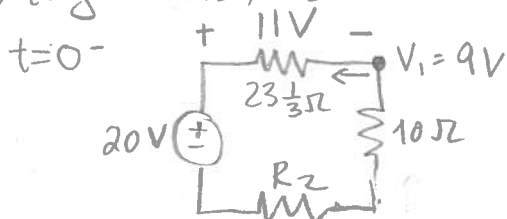iii) To find R_2 , use continuity of voltage in a capacitor



KVL $\rightarrow V_{R1} = +11 \text{ V}$

$$V_C(0^+) = 11 \text{ V}$$


since in parallel

$$\text{KCL: } \frac{-11 \text{ V}}{23\frac{1}{3}} + \frac{9 \text{ V}}{10 \Omega + R_2} = 0 \rightarrow 9 \text{ V} = 0.471(10 \Omega + R_2)$$

$$R_2 = 9.11 \Omega$$

Extra Working Space

c) at $t = 0^+ s$

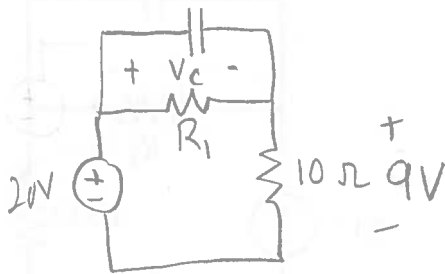

$$V_c(0^+) = 11V$$

$$\frac{1}{2} C V^2 = \frac{1}{2} \cdot \frac{1}{14} \cdot (11)^2$$

$$U = \frac{121}{28} J = 4.321 J$$