

Today's Outline

8. Second Order Circuits

- the parallel RLC circuit
- underdamped, overdamped, and critically damped natural response





Overview

Second order circuit: a circuit composed of resistors, sources and two energy storage components, often one capacitor and one inductor. Some, not all, circuits with two capacitors or two inductors are second order circuits.


- **RLC circuits** include a resistor, an inductor and a capacitor
- “second order” refers to the second order differential equations that describe voltage and current variables, $v(t)$ and $i(t)$
- *RLC* circuits are useful because of the time dependent response of such circuits

Overview

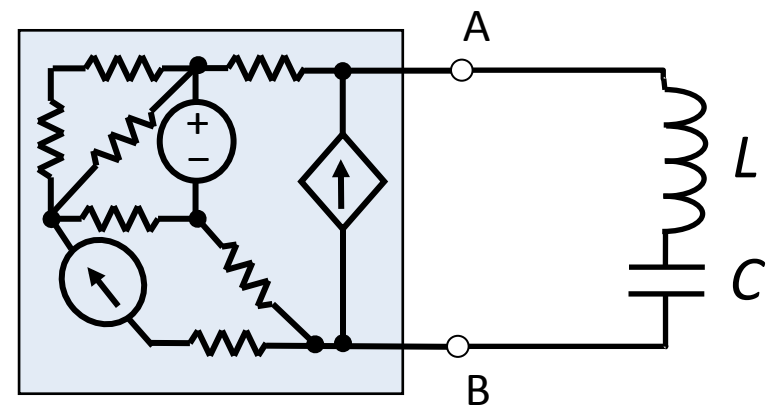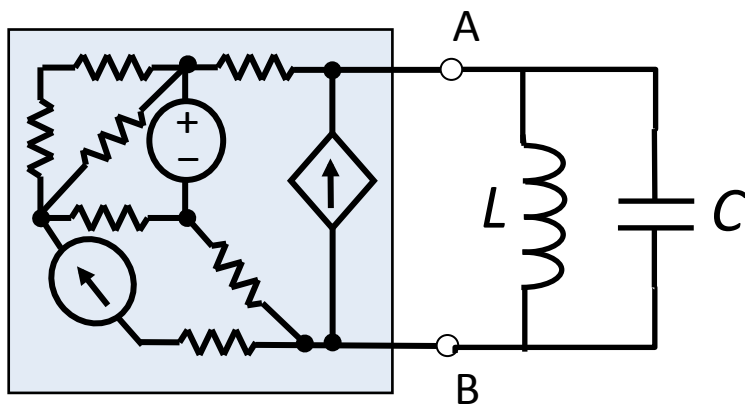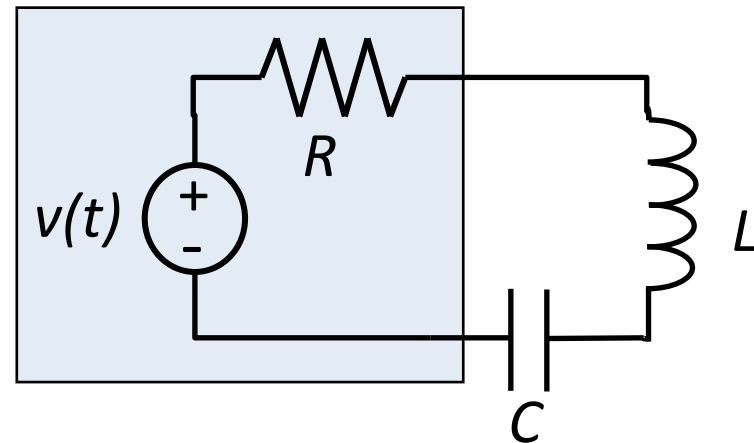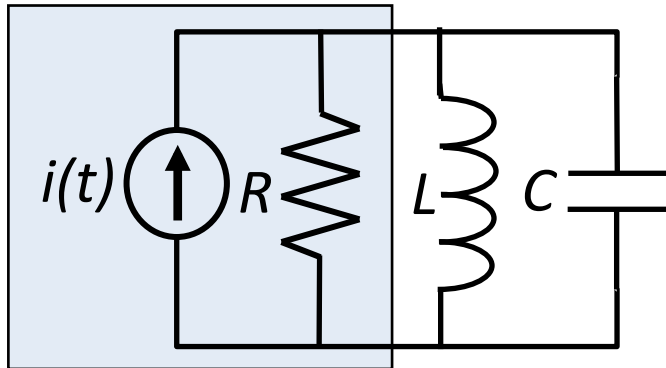There are two classic forms of the *RLC* circuit: the ***parallel RLC*** and the ***series RLC***.



Parallel RLC

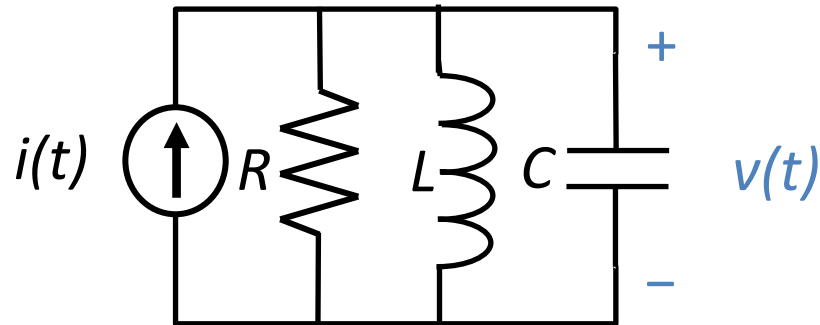

KCL:
$$-i + \frac{v}{1/sC} + \frac{v}{R} + \frac{v}{sL} = 0$$

$$-i + C \frac{dv}{dt} + \frac{v}{R} + \frac{1}{L} \int_0^t v(t') dt' + i_L(0) = 0$$


$$-si + s^2 C \cdot v + \frac{s}{R} \cdot v + \frac{1}{L} \cdot v = 0$$

Replacing s by d/dt :

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{C} \frac{di}{dt}$$

This is an **inhomogeneous linear second order differential equation**.

Series RLC

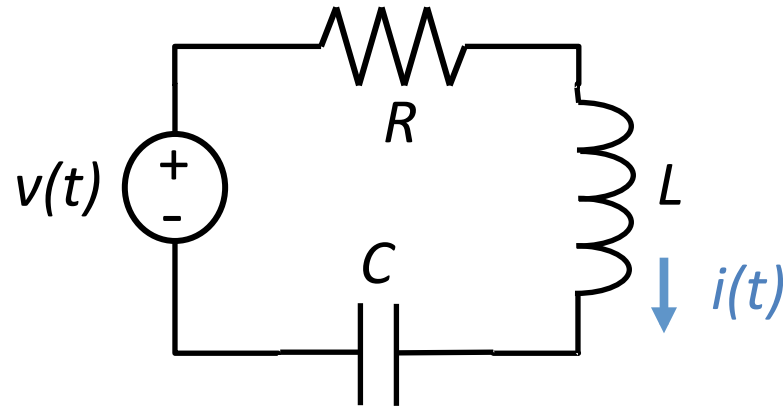

KVL: $-v + R \cdot i + sL \cdot i + \frac{1}{sC} \cdot i = 0$

$$-v + L \frac{di}{dt} + iR + \frac{1}{C} \int_0^t i(t') dt' + v_c(0) = 0$$

$$-sv + sR \cdot i + s^2 L \cdot i + \frac{1}{C} \cdot i = 0$$

Replacing s by d/dt :

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{1}{L} \frac{dv}{dt}$$

This is an **inhomogeneous linear second order differential equation**.

natural response



As in the case of first order circuits, it is useful to divide the response of a second order circuit into two parts.

**total response = transient (natural) response
+ steady state (forced) response**

Solution to the homogeneous equation gives the “short-lived” transient or natural response.

Particular solution of the inhomogeneous equation gives the “long-lived” steady state response.

natural response

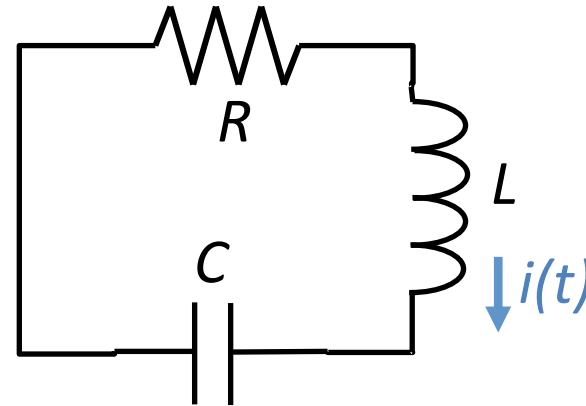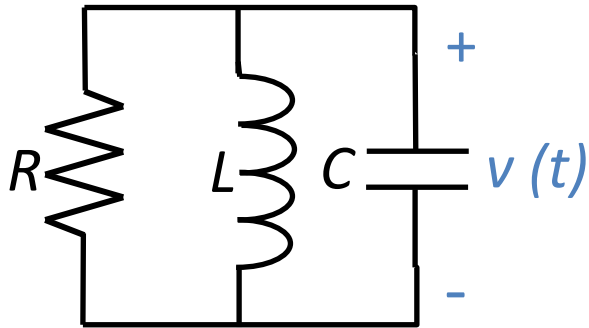

The differential equations that are to be solved are thus:

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0 \quad t > 0$$

$$i_L(0+) = I_0$$

$$v(0+) = V_0$$

$$\frac{d^2 i}{dt^2} + \frac{1}{L/R} \frac{di}{dt} + \frac{1}{LC} i = 0 \quad t > 0$$

$$v_C(0+) = V_0$$

$$i(0+) = I_0$$

mathematical review

Consider the ***homogeneous linear second order differential equation***, which corresponds to ***unforced (natural)*** behaviour:

$$a \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + cx = 0$$

Assume a solution of the form: $x(t) = K \exp(+st)$

Substitution returns an operator equation:

$$as^2 \cdot x + bs \cdot x + c \cdot x = (as^2 + bs + c) \cdot x = 0$$


The ***characteristic equation*** for the value of s is: $as^2 + bs + c = 0$

The roots of the characteristic equation are: $s_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$

parallel RLC

The differential equation to be solved is:
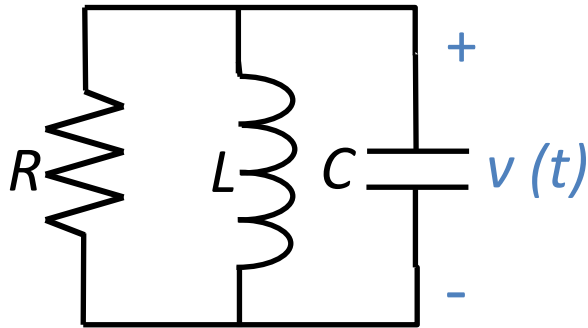
$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$



The characteristic equation to be solved is:

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

We identify the two coefficients as meaningful parameters:


$$s^2 + 2\alpha \cdot s + \omega_0^2 = 0$$

$$\alpha = \frac{1}{2RC} = \text{damping rate}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \text{resonant frequency}$$

undamped parallel RLC

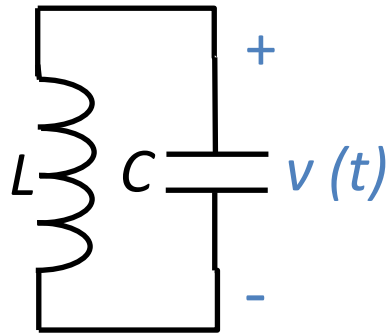Consider the special case where $R \rightarrow \infty$, the damping rate $\alpha \rightarrow 0$ and the characteristic equation:



$$s^2 + \omega_0^2 = 0$$

$$s = \pm j\omega_0 \quad j = \sqrt{-1}$$

The solution to $v(t)$ is:

$$\alpha = \frac{1}{2RC} \rightarrow 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$v(t) = A_1 \exp(+j\omega_0 t) + A_2 \exp(-j\omega_0 t)$$


By Euler's theorem:

$$v(t) = B_1 \sin(\omega_0 t) + B_2 \cos(\omega_0 t)$$

The constants are determined by the initial conditions at $t = 0+$.



undamped parallel RLC

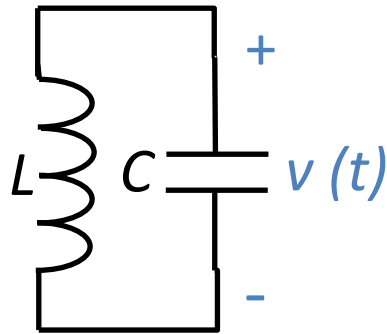The solution is an undamped oscillation, like that of an undamped mechanical pendulum.




$$v(t) = B_1 \sin(\omega_0 t) + B_2 \cos(\omega_0 t) \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

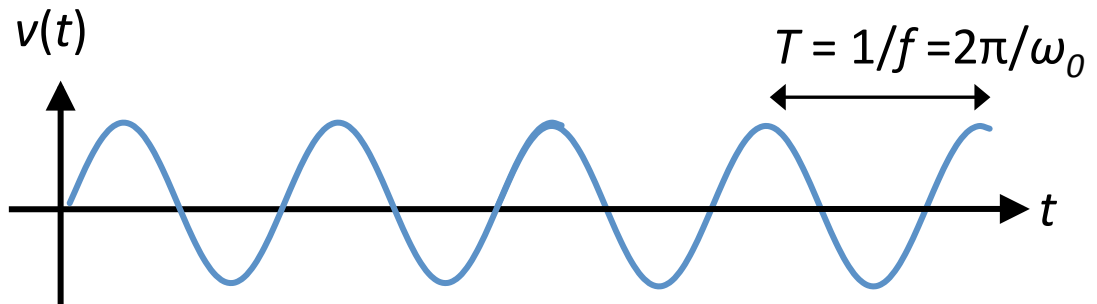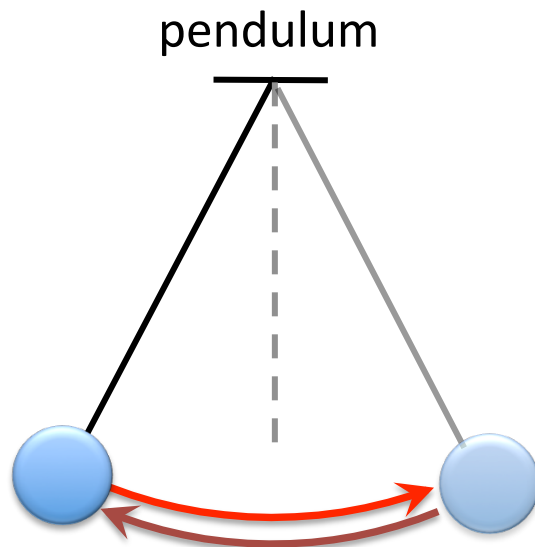The angular frequency ω_0 is called the **undamped resonant frequency** of the LC circuit.



undamped parallel RLC

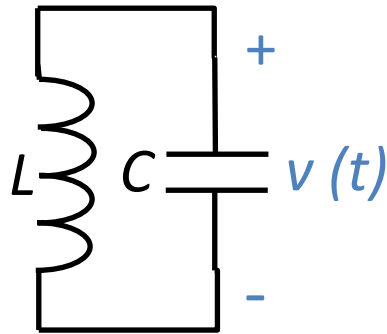
Energy oscillates between electric energy stored in C and magnetic energy stored in L . Without R , there is no energy lost to heat.




$$U_C = \frac{1}{2} C v^2$$

$$U_L = \frac{1}{2} L i^2 = \frac{1}{2} L \left(C \frac{dv}{dt} \right)^2$$
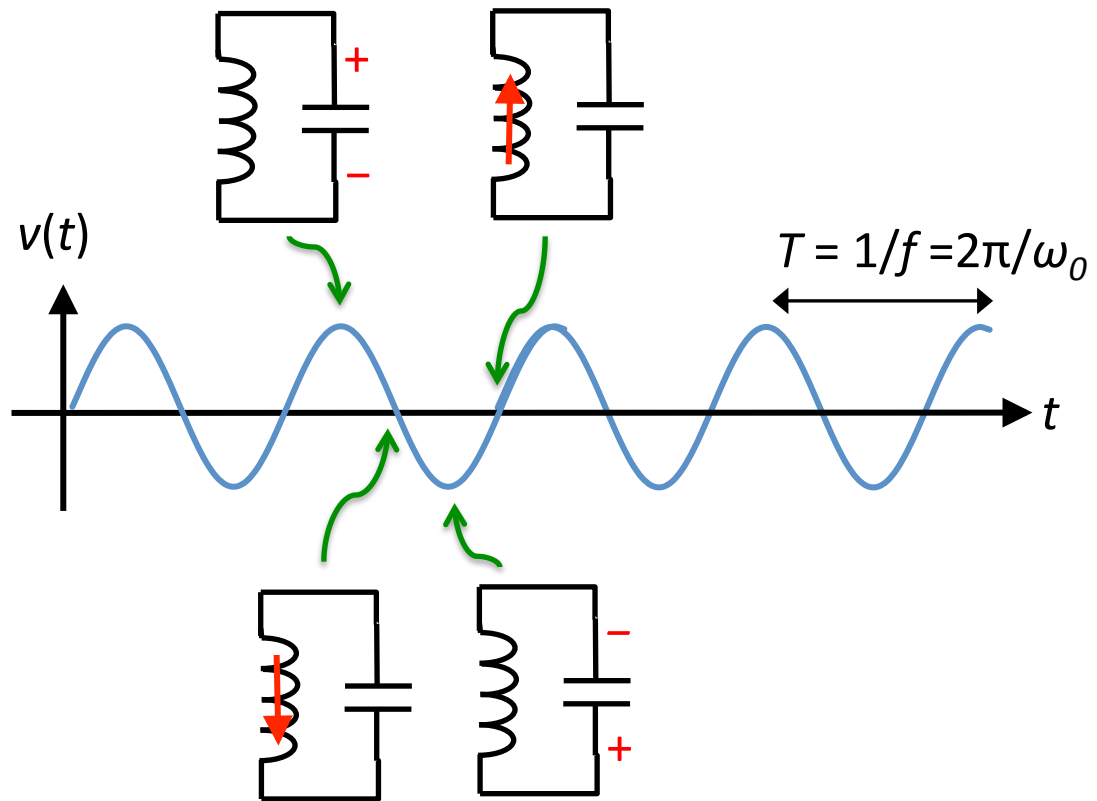
$$U_{tot} = U_L + U_C = \text{constant}$$



parallel RLC

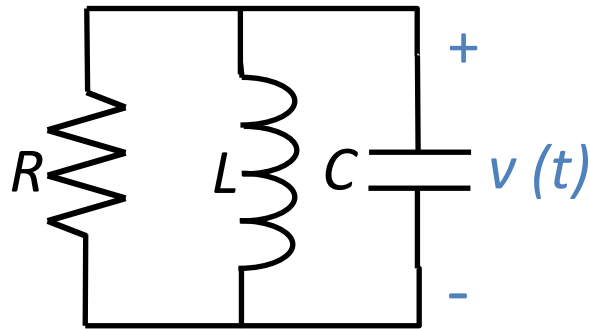

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

The case of non-zero damping gives:

$$s^2 + 2\alpha \cdot s + \omega_0^2 = 0$$

The general solution to the roots are:

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

These roots can be in general complex numbers, with three classes of solution:

$$\alpha < \omega_0 \quad s = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$$

$$\alpha = \omega_0 \quad s = -\alpha$$

$$\alpha > \omega_0 \quad s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

McGill underdamped natural response


underdamped response: $\alpha < \omega_0$

The roots are complex:

$$\begin{aligned} s &= -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2} \\ &= -\alpha \pm j\omega_d \end{aligned}$$

The natural response has an oscillation at the damped frequency ω_d , decaying with time constant α .
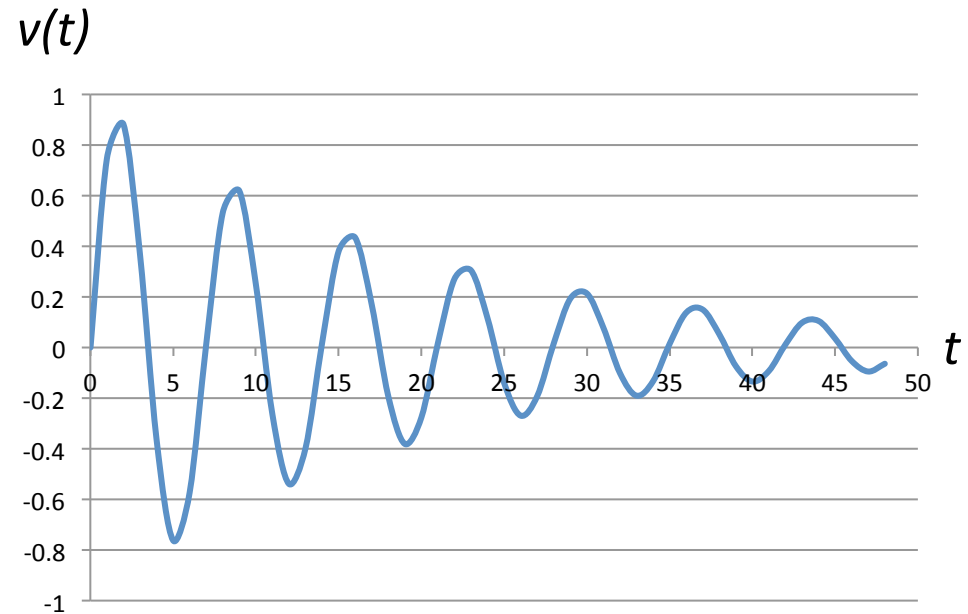
$$\begin{aligned} v(t) &= \exp(-\alpha t) \left[A_1 \exp(+j\omega_d t) + A_2 \exp(-j\omega_d t) \right] \\ &= \exp(-\alpha t) \left[B_1 \sin(\omega_d t) + B_2 \cos(\omega_d t) \right] \end{aligned}$$



The coefficients can be found:

$$v(0+) = B_2$$




$$\frac{dv}{dt}(0+) = -\alpha B_2 - \omega_d B_1$$

underdamped natural response

underdamped response: $\alpha < \omega_0$

$$s = -\alpha \pm j\omega_d$$

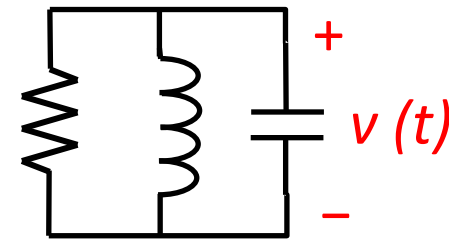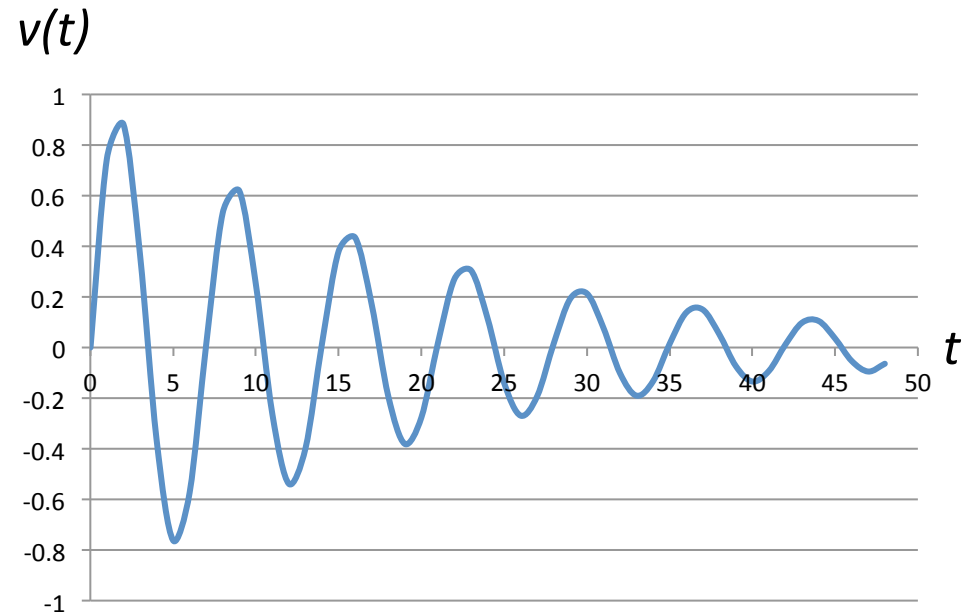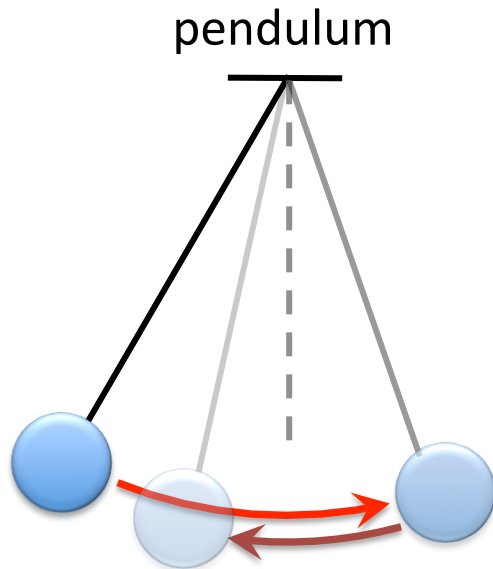By analogy, an underdamped pendulum oscillates, losing a fraction of the initially stored energy during each oscillation (eg. by friction).



The resistor dissipates energy at each moment that $v(t) \neq 0$.

critically damped natural response

critically damped response: $\alpha = \omega_0$

The roots are identical:

$$s = -\alpha = -\omega_0$$


The natural response has the form*:

$$v(t) = \exp(-\alpha t) [A_1 t + A_2]$$

The coefficients can be found by using the initial conditions:

$$v(0+) = A_2$$

$$\frac{dv}{dt}(0+) = A_1 + sA_2$$

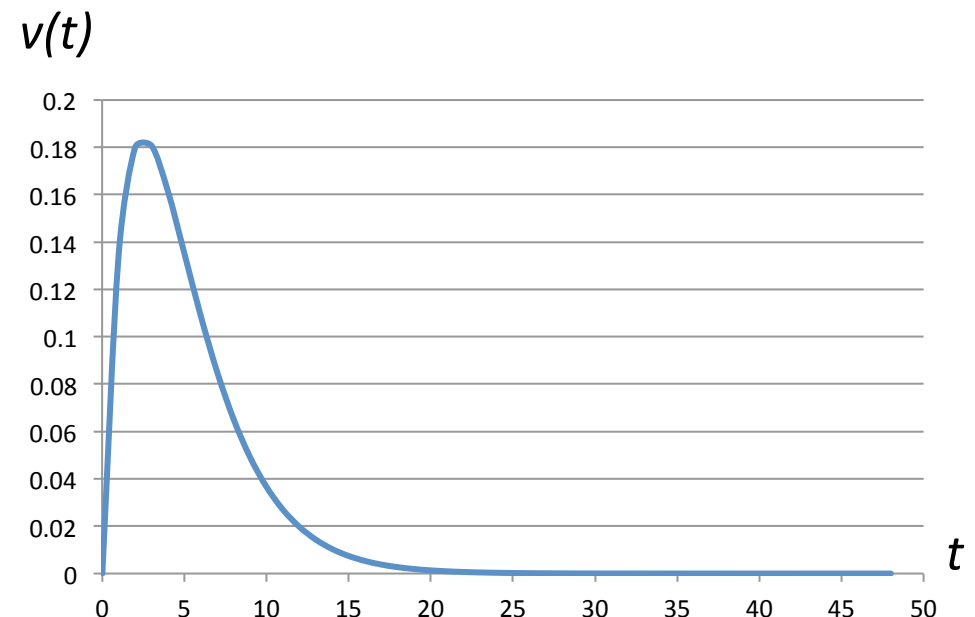



**refer to theory of ordinary differential equations for explanation*

critically damped natural response

critically damped response: $\alpha = \omega_0$

$$s = -\alpha = -\omega_0$$

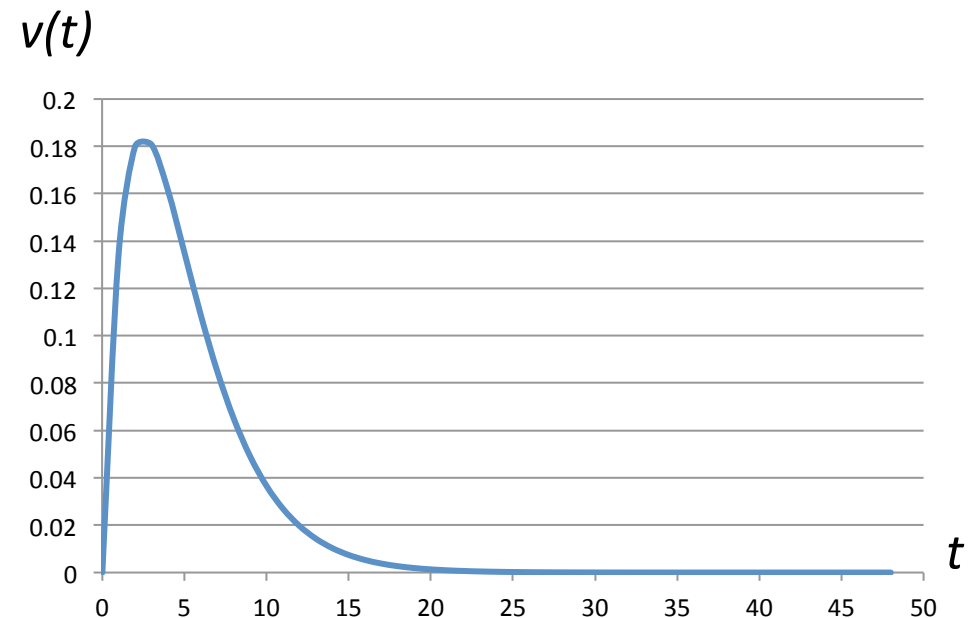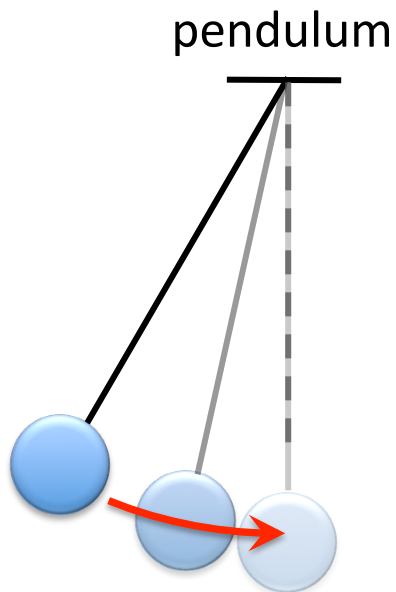By analogy, a critically damped pendulum does not oscillate, but approaches rest.



overdamped natural response

overdamped response: $\alpha > \omega_0$

Two real roots are found.

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


The natural response is:

$$v(t) = A_1 \exp(s_1 t) + A_2 \exp(s_2 t)$$

The coefficients can be found by using the initial conditions:

$$v(0+) = A_1 + A_2$$
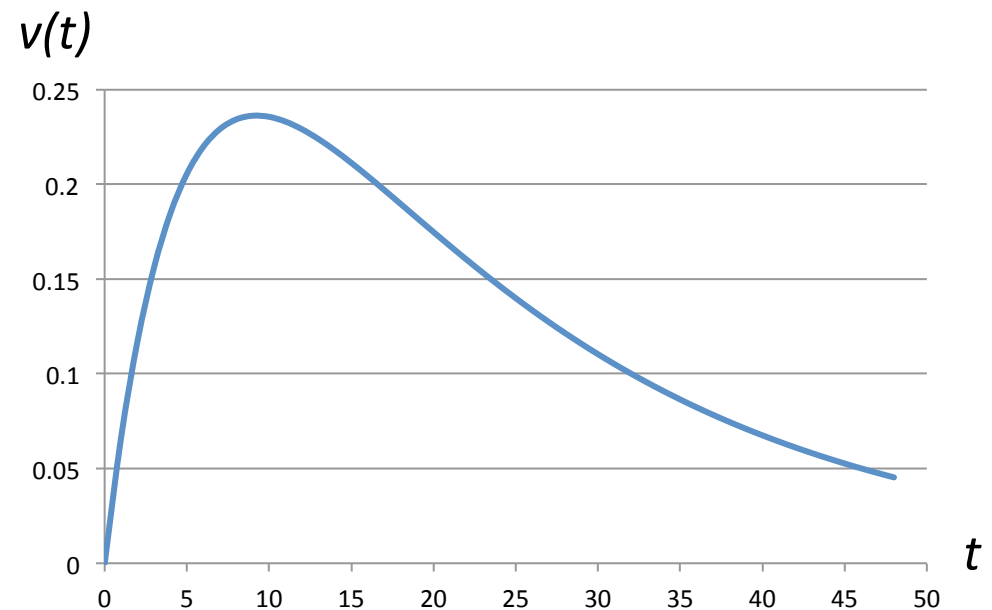
$$\frac{dv}{dt}(0+) = s_1 A_1 + s_2 A_2$$





overdamped natural response

overdamped response: $\alpha > \omega_0$

Two real roots are found.

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

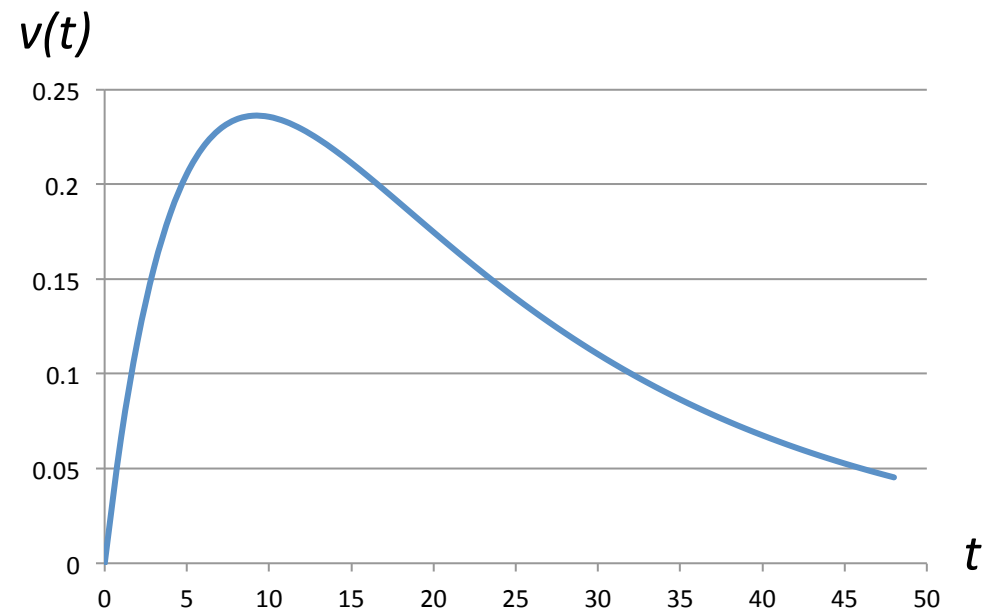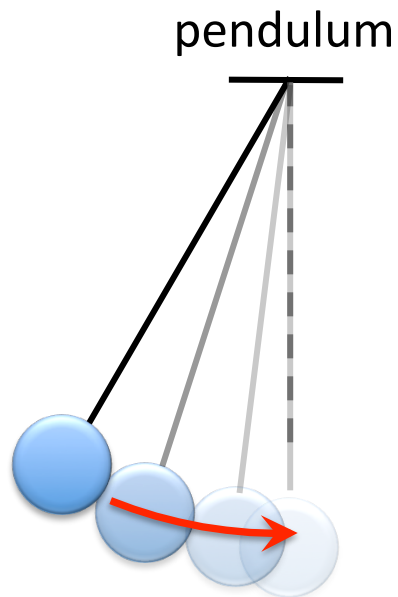
By analogy, an overdamped pendulum approaches rest at a rate dominated by damping (eg. as if placed in a highly viscous fluid)



the complex s-plane

2nd order system
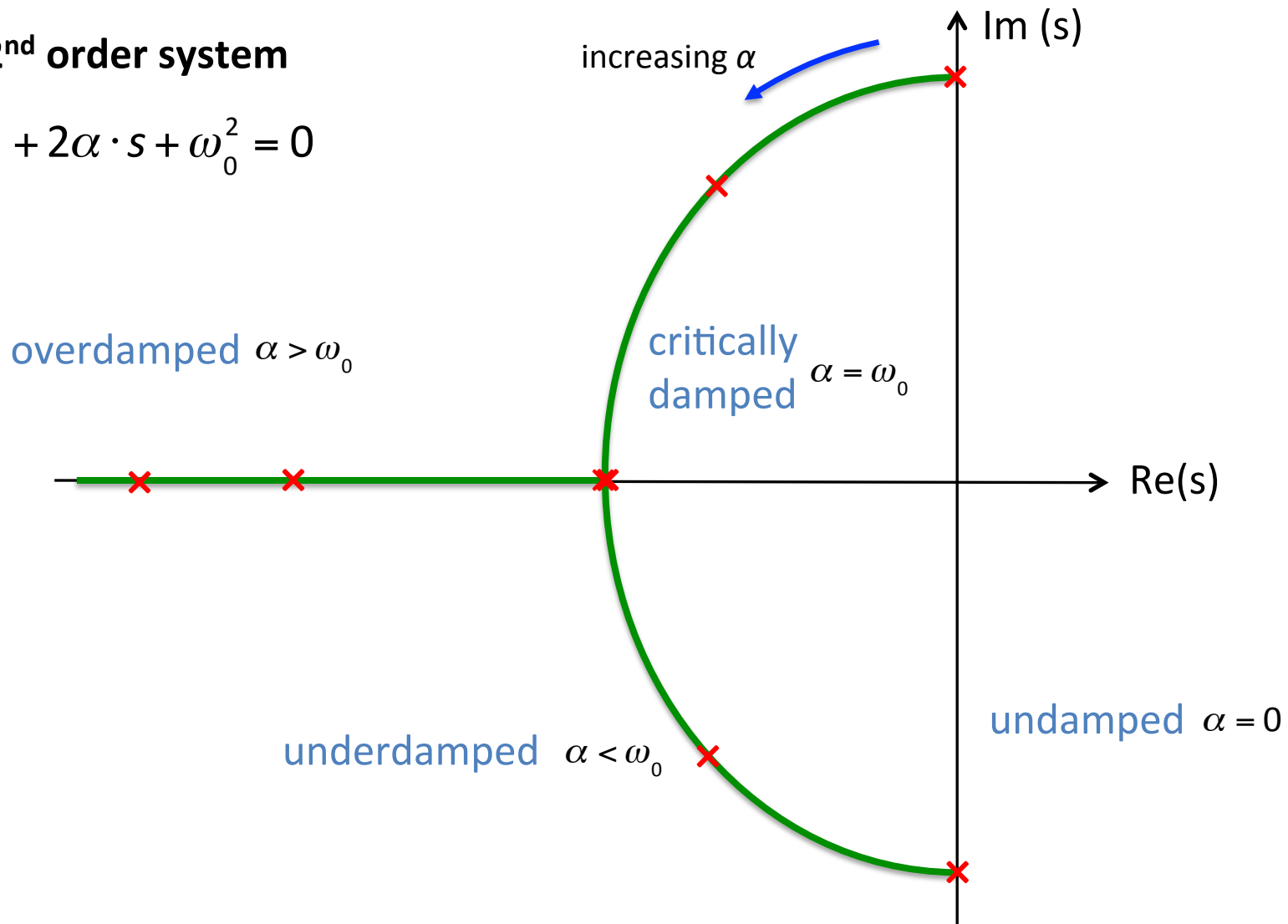
$$s^2 + 2\alpha \cdot s + \omega_0^2 = 0$$




the complex s-plane

2nd order system

$$s^2 + 2\alpha \cdot s + \omega_0^2 = 0$$

overdamped $\alpha > \omega_0$
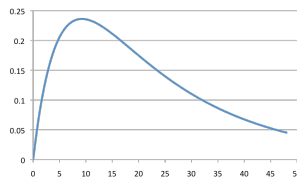
$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$




increasing α

critically damped


$$\alpha = \omega_0$$

$$s = -\alpha$$

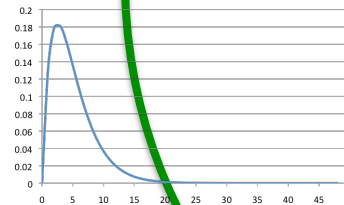


underdamped $\alpha < \omega_0$
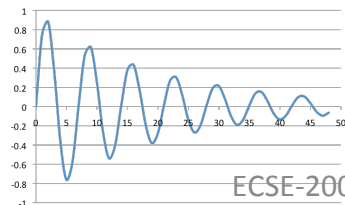
$$s = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2} = -\alpha \pm j\omega_d$$



undamped $\alpha = 0$


$$s = \pm j\omega_0$$

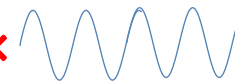

the complex s-plane

1st order system

$$s + 1/\tau = 0$$

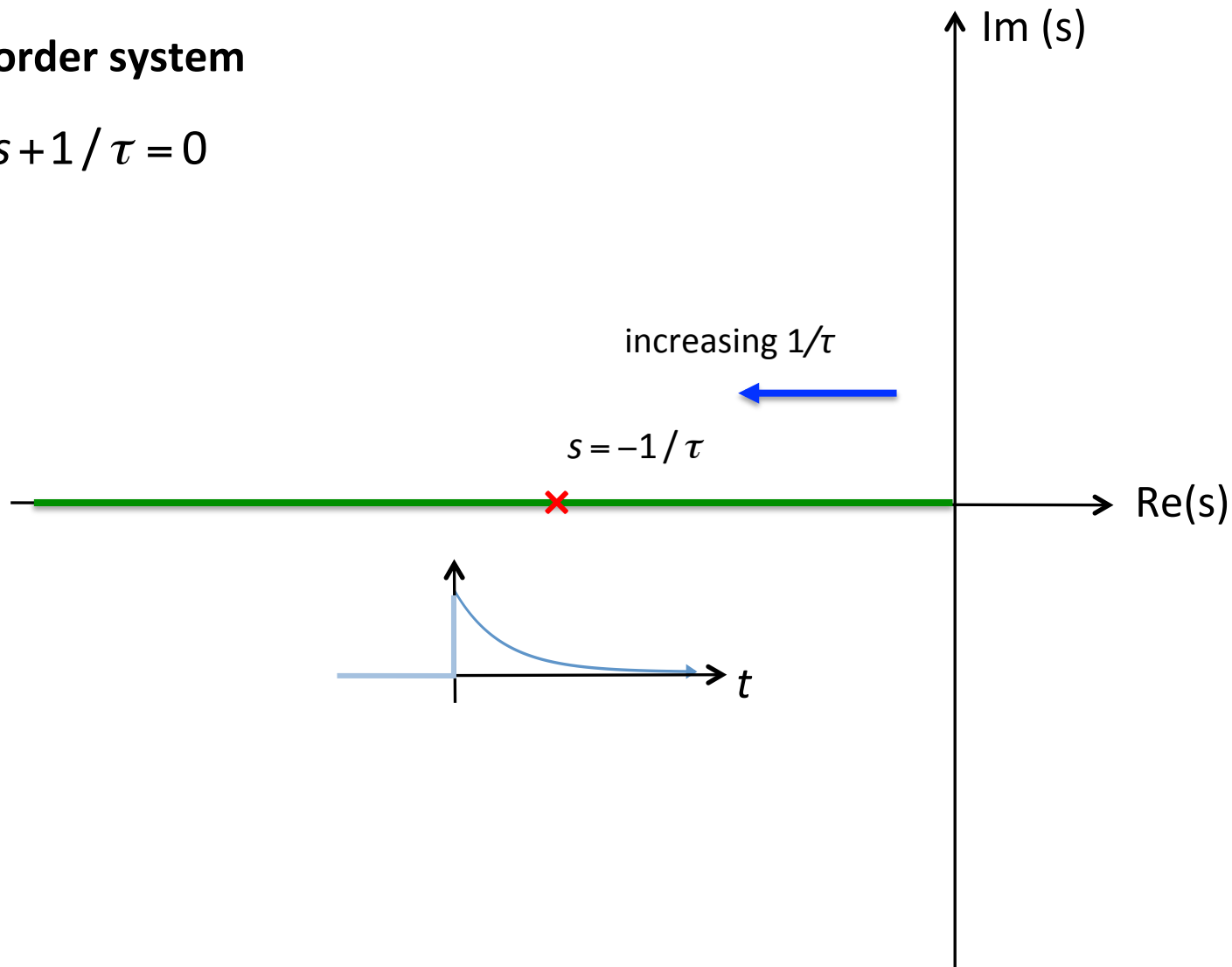

RLC natural response: general procedure

step #1: Find the initial value and initial derivative of the circuit variable of interest, $x(0+)$ and $dx/dt(0+)$, using circuit analysis and continuity of capacitor voltage and inductor current.

step #2: Using the operator method, or by directly writing down the equation, determine the characteristic equation coefficients α and ω_0 in terms of R , L , C .

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

step #3: Find the roots of the characteristic equation:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

step #4: Construct the solution, using the over-/critical/under-damped nature of the response:

$$x(t) = A_1 \exp(s_1 t) + A_2 \exp(s_2 t)$$


$$x(t) = \exp(-\alpha t) [A_1 t + A_2]$$

$$x(t) = \exp(-\alpha t) [B_1 \sin(\omega_d t) + B_2 \cos(\omega_d t)]$$

example: defibrillator



Dr. Bernard Lown

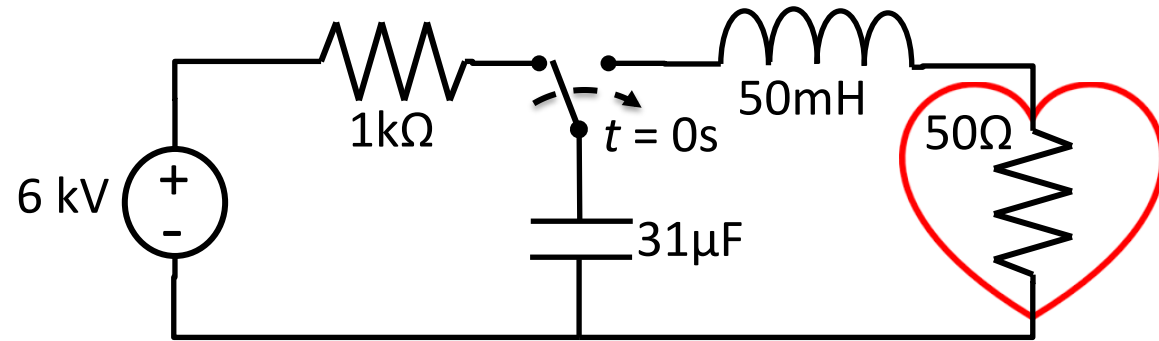


Find the voltage versus time on the heart, crudely approximated as a 50Ω resistor. The circuit is in dc steady state for $t < 0$, and the switch moves instantaneously at $t = 0s$.

The circuit has been designed to deliver a voltage pulse to the human heart, with shape and amplitude that have the desired physiological effect.

example: defibrillator

step #1 : initial conditions

$t = 0^-$ (dc steady state)

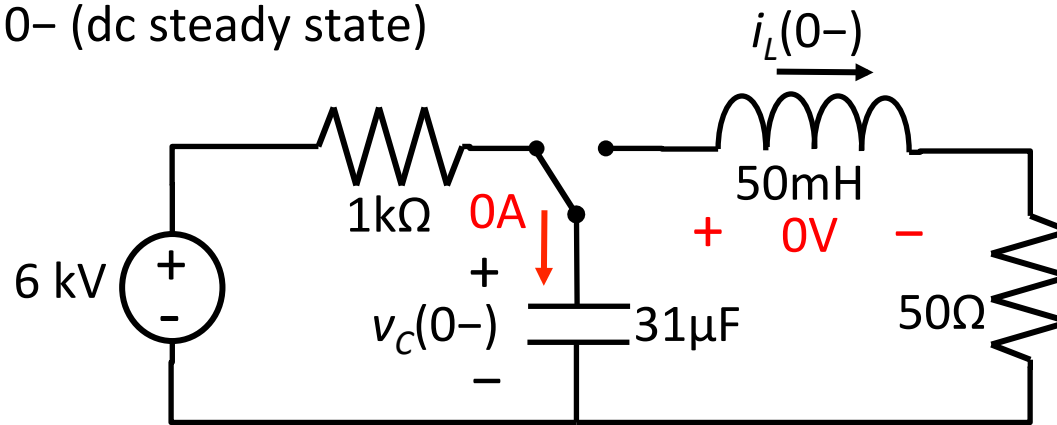

KVL:

$$v_C(0^-) = 6\text{ kV}$$


KCL:

$$i_L(0^-) = 0\text{ A}$$

example: defibrillator

step #1 : initial conditions

$t = 0+$

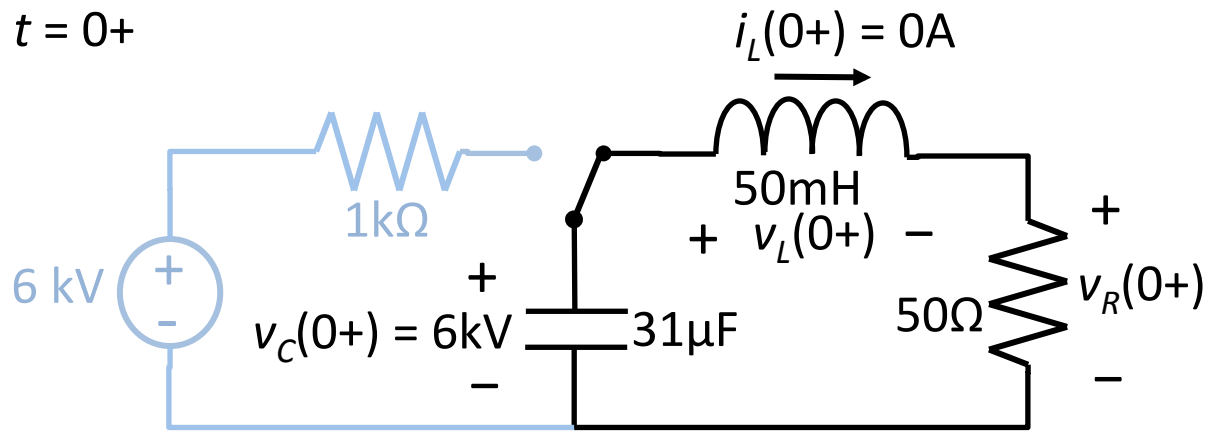

continuity:

$$v_C(0+) = v_C(0-) = 6\text{ kV}$$

$$i_L(0+) = i_L(0-) = 0\text{ A}$$

Ohm: $v_R(0+) = i_L(0+) 50\Omega = 0\text{ V}$

KVL: $0 = -v_C(0+) + v_L(0+) + v_R(0+)$

$$v_L(0+) = v_C(0+) - v_R(0+) = 6\text{ kV}$$

initial conditions:


$$v_R(0+) = 0\text{ V}$$

$$\left. \frac{dv_R}{dt} \right|_{t=0+} = 6\text{ MV/s}$$

Ohm, inductor: $\left. \frac{dv_R}{dt} \right|_{t=0+} = 50\Omega \cdot \left. \frac{di_L}{dt} \right|_{t=0+} = 50\Omega \cdot \frac{v_L(0+)}{50\text{ mH}} = 6\text{ MV/s}$

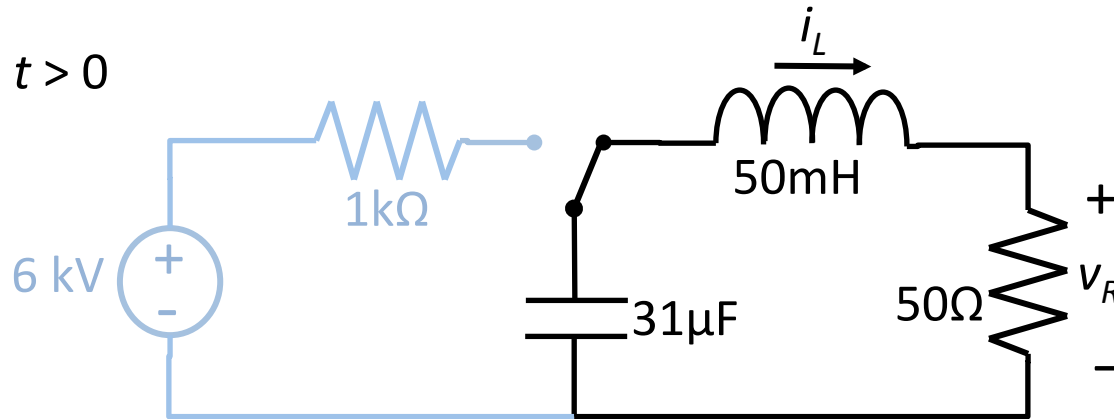example: defibrillator

step #2 : find the characteristic equation



Note that the natural response of v_R and i_L are determined by the same characteristic equation. Why?

mesh equation: $0 = i_L \cdot sL + i_L \cdot R + i_L \cdot \frac{1}{sC}$

$$0 = \left(sL + R + \frac{1}{sC} \right) \cdot i_L$$


$$i_L \neq 0 \quad \therefore 0 = sL + R + \frac{1}{sC} \quad \rightarrow \quad 0 = s^2 + s \cdot \frac{R}{L} + \frac{1}{LC}$$

$$0 = s^2 + s \cdot \frac{50\Omega}{50\text{mH}} + \frac{1}{50\text{mH} \cdot 31\mu\text{F}}$$

$$0 = s^2 + s \cdot 1000 + 645161$$

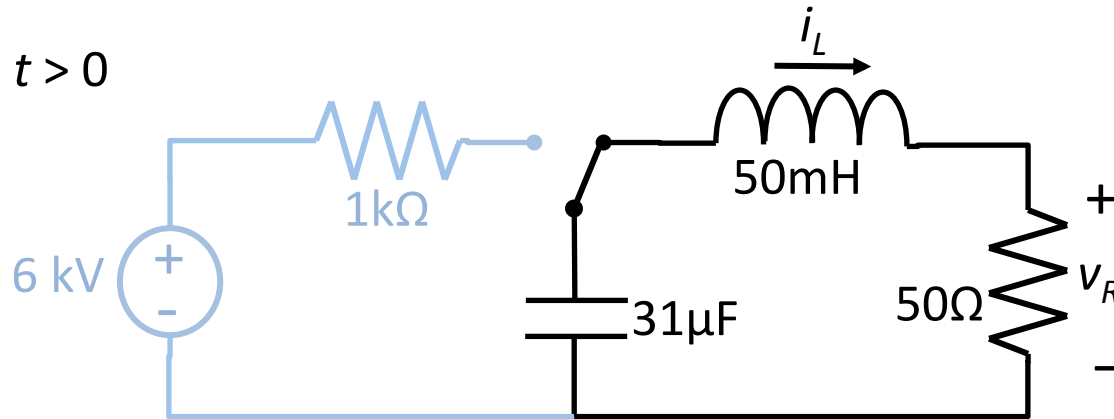example: defibrillator

step #3 : find the roots of the characteristic equation



$$0 = a \cdot s^2 + b \cdot s + c$$

$$= s^2 + s \cdot 1000 + 645161$$

$$s_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$= \frac{-1000 \pm \sqrt{(1000)^2 - 4 \cdot 1 \cdot 645161}}{2 \cdot 1} = -500 \pm i \cdot 629 \quad [s^{-1}] \text{ units}$$

example: defibrillator

step #4 : construct the solution

$$v_R(0+) = 0 \text{ V} \quad \left. \frac{dv_R}{dt} \right|_{t=0+} = 6 \text{ MV/s} \quad s_{1,2} = -500 \pm i \cdot 629 \text{ [s}^{-1}\text{]}$$

Two complex roots correspond to ***underdamped*** natural response.

$$\begin{aligned} v_R(t) &= A_1 \exp(s_1 t) + A_2 \exp(s_2 t) \\ &= \exp(-500s^{-1} \cdot t) \left[B_1 \cos(629s^{-1} \cdot t) + B_2 \sin(629s^{-1} \cdot t) \right] \end{aligned}$$

Apply first of two initial conditions:

$$\begin{aligned} v_R(0+) &= 1 \cdot [B_1 \cdot 1 + B_2 \cdot 0] = B_1 \\ 0\text{V} &= B_1 \end{aligned}$$

example: defibrillator

step #4 : construct the solution

$$v_R(t) = B_2 \cdot \exp(-500s^{-1} \cdot t) \cdot \sin(629s^{-1} \cdot t)$$


Apply second of two initial conditions:

$$\begin{aligned} \frac{dv_R}{dt} &= B_2 \cdot \left[-500s^{-1} \exp(-500s^{-1} \cdot t) \right] \cdot \sin(629s^{-1} \cdot t) \\ &\quad + B_2 \cdot \exp(-500s^{-1} \cdot t) \cdot \left[629s^{-1} \cos(629s^{-1} \cdot t) \right] \end{aligned}$$


$$\left. \frac{dv_R}{dt} \right|_{t=0+} = B_2 \cdot \left[-500s^{-1} \cdot 1 \right] \cdot 0 + B_2 \cdot 1 \cdot \left[629s^{-1} \cdot 1 \right]$$

$$6\text{MV/s} = B_2 \cdot 629s^{-1}$$


$$B_2 = 9.54 \text{ kV}$$

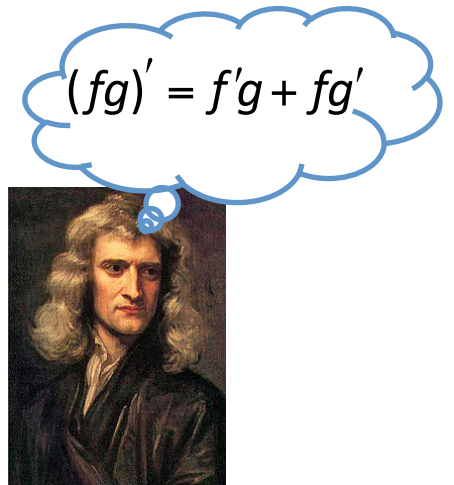

example: defibrillator

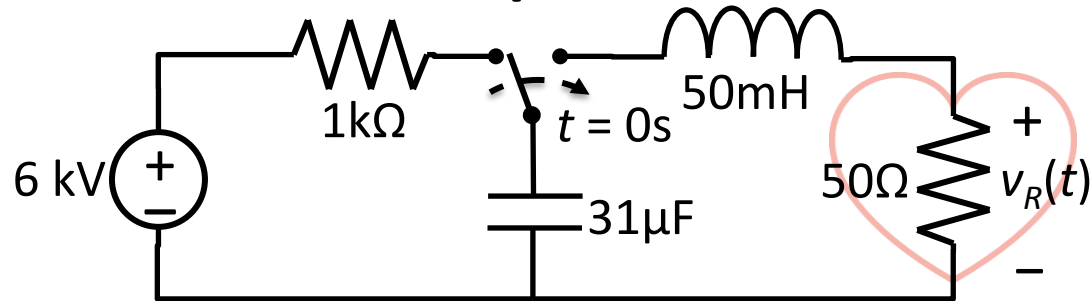

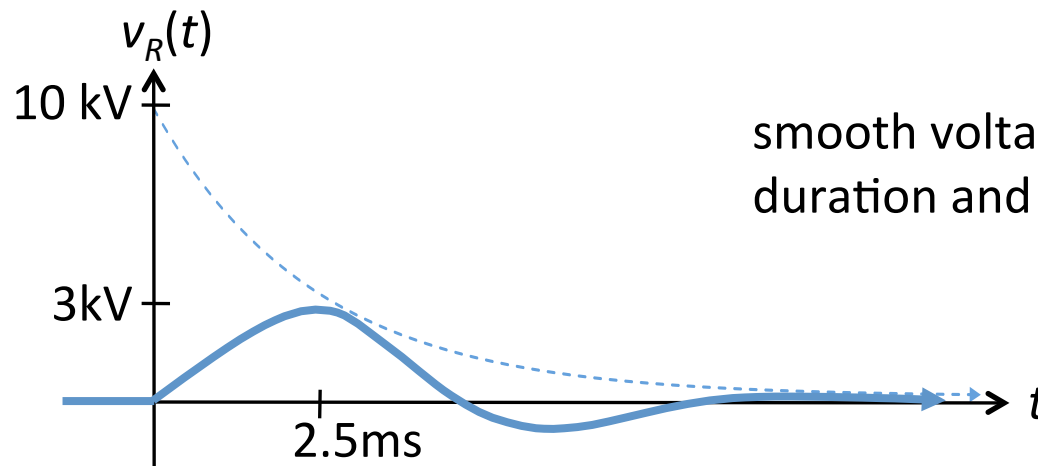solution:
$$v_R(t) = 9.54 \text{ kV} \cdot \exp(-500 \text{ s}^{-1} \cdot t) \cdot \sin(629 \text{ s}^{-1} \cdot t) \quad t > 0$$



smooth voltage pulse of several ms duration and ~3kV amplitude

The energy delivered to the heart is:
$$U = \frac{1}{2} C v_c^2(0) = \frac{1}{2} \cdot 31 \mu\text{F} \cdot (6 \text{ kV})^2 = 558 \text{ J}$$