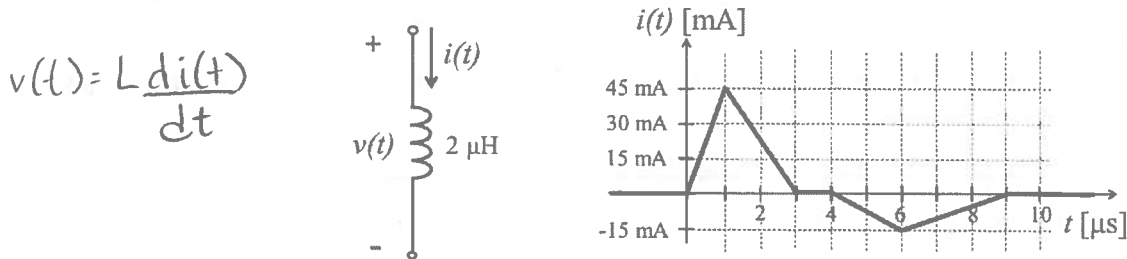


LAST NAME SOLUTIONS MCGILL ID# _____
 FIRST NAME _____ SIGNATURE _____

- Only Faculty standard calculator accepted
- No cellphone allowed
- Show all your work

- Clearly indicate your final answer with the SI unit and multiplier
- You have 45 minutes to complete this quiz

Question 1: Consider the $20\ \mu\text{H}$ inductor ($L = 20\ \mu\text{H}$) shown below along with the diagram illustrating the current $i(t)$ flowing through the inductor. Answer the following questions.



- What is the voltage v at $t = 2\ \mu\text{s}$? [1 pt]
- Plot the voltage $v(t)$ versus time t indicating the voltage values? [2 pt]
- What is the instantaneous power at $t = 10\ \mu\text{s}$? [1 pt]
- What is the energy stored as electric potential energy $U(t)$ in the inductor at time $t = 4\ \mu\text{s}$? [1 pt]

a) $v(2\ \mu\text{s}) = L \left. \frac{di(t)}{dt} \right|_{t=2\ \mu\text{s}} = 2\ \mu\text{H} \cdot \left(\frac{0 - 45\ \text{mA}}{3 - 1\ \mu\text{s}} \right) = \frac{-90\ \text{mA}}{2\ \text{s}} = \boxed{-45\ \text{mV} = v(2\ \mu\text{s})}$

b) $t < 0 \rightarrow v = 0\ \text{V}$


$0 < t < 1\ \mu\text{s} \quad v = 2\ \mu\text{H} \left(\frac{45\ \text{mA}}{1\ \mu\text{s}} \right) = 90\ \text{mV}$

$0\ \mu\text{s} < t < 3\ \mu\text{s} \quad v = -45\ \text{mV} \text{ (from a)}$

$3\ \mu\text{s} < t < 4\ \mu\text{s} \quad v = 0\ \text{V}$

$4\ \mu\text{s} < t < 6\ \mu\text{s} \quad v = 2\ \mu\text{H} \left(\frac{-15\ \text{mA}}{2\ \mu\text{s}} \right) = -15\ \text{mV}$

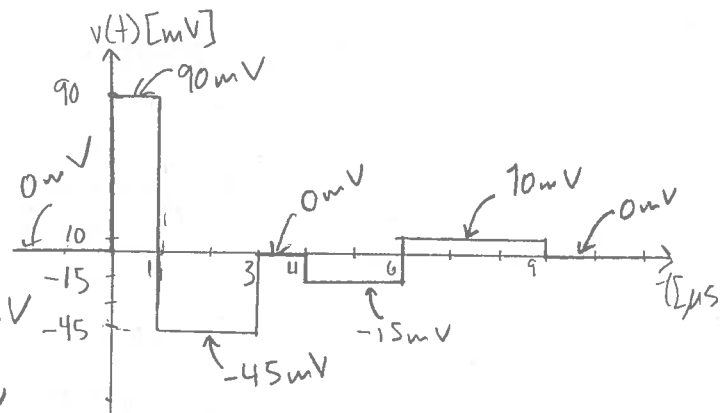$6\ \mu\text{s} < t < 8\ \mu\text{s} \quad v = 2\ \mu\text{H} \left(\frac{15\ \text{mA}}{3\ \mu\text{s}} \right) = 10\ \text{mV}$




c) $p(10\ \mu\text{s}) = i(10\ \mu\text{s}) \cdot v(10\ \mu\text{s}) = 0\ \text{W}$

$\boxed{P(10\ \mu\text{s}) = 0\ \text{W}}$


d) $U(t) = \frac{1}{2} L i^2 \quad i(4\ \mu\text{s}) = 0\ \text{A} \quad U(t) = 0\ \text{J}$

$\boxed{U(4\ \mu\text{s}) = 0\ \text{J}}$

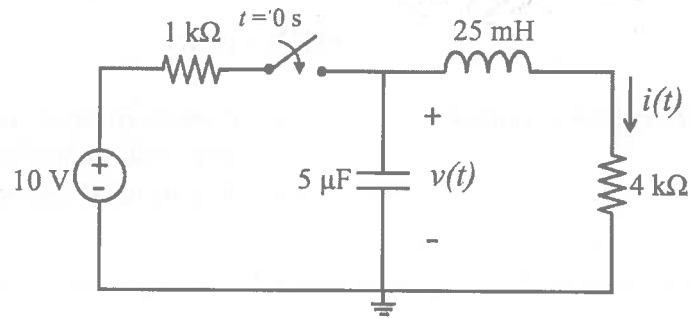Question 2: The switch in the switched circuit shown below has been opened for a long time (in other words, the circuit is in steady-state for $t < 0$ s) before closing the switch at time $t = 0$ s. Answer the following questions.



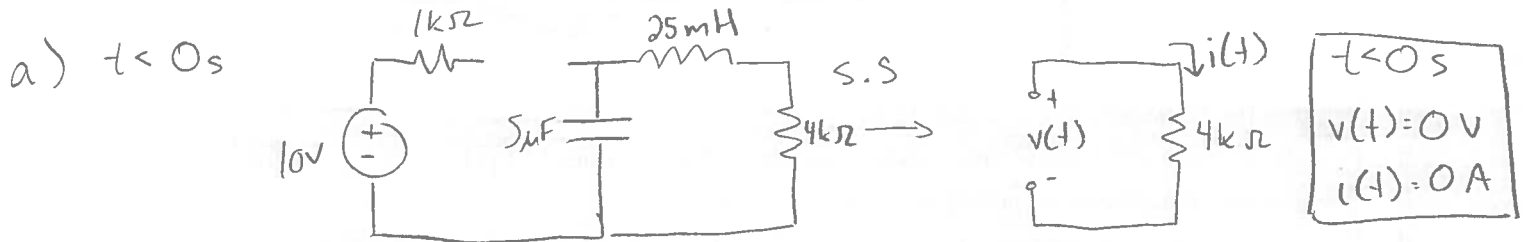- Draw the circuit in steady-state for time $t < 0$ s and find the values for the voltage $v(t)$ and the current $i(t)$ for $t < 0$ s. [2 pt]
- Find the values for the voltage $v(t)$ and the current $i(t)$ immediately after the switch closes ($v(0^+)$ and $i(0^+)$)? [2 pt]
- Draw the circuit in steady-state for time $t \rightarrow \infty$ and find the voltage $v(t)$ and the current $i(t)$. [2 pt]



b) $t = 0^+$ s

from continuity of voltage in capacitor $v(0^+) = 0$ V
 from continuity of current in inductor $i(0^+) = 0$ A

