



ELECTRIC CIRCUIT 1

ECSE-200-001

April 21, 2017, 9am to 12pm

EXAMINER: Odile Liboiron-Ladouceur

ASSOC. EXAMINER: Gordon Roberts


STUDENT NAME:		McGILL ID:											
---------------	--	------------	--	--	--	--	--	--	--	--	--	--	--

**INSTRUCTIONS:**

<b>EXAM:</b>	CLOSED BOOK <input checked="" type="checkbox"/> OPEN BOOK <input type="checkbox"/>
	SINGLE-SIDED <input checked="" type="checkbox"/> PRINTED ON BOTH SIDES OF THE PAGE <input type="checkbox"/>
	MULTIPLE CHOICE <input type="checkbox"/> NOTE: The Examination Security Monitor Program detects pairs of students with unusually similar answer patterns on multiple-choice exams. Data generated by this program can be used as admissible evidence, either to initiate or corroborate an investigation or a charge of cheating under Section 16 of the Code of Student Conduct and Disciplinary Procedures.
	ANSWER IN BOOKLET <input type="checkbox"/> EXTRA BOOKLETS PERMITTED: YES <input type="checkbox"/> NO <input checked="" type="checkbox"/> ANSWER ON EXAM <input checked="" type="checkbox"/>
	SHOULD THE EXAM BE: RETURNED <input checked="" type="checkbox"/> KEPT BY STUDENT <input type="checkbox"/>
<b>CRIB SHEETS:</b>	NOT PERMITTED <input checked="" type="checkbox"/> PERMITTED <input type="checkbox"/> e.g. one 8 1/2X11 handwritten double-sided sheet <u>Specifications:</u>
<b>DICTIONARIES:</b>	TRANSLATION ONLY <input checked="" type="checkbox"/> REGULAR <input type="checkbox"/> NONE <input type="checkbox"/>
<b>CALCULATORS:</b>	NOT PERMITTED <input type="checkbox"/> PERMITTED (Non-Programmable) <input checked="" type="checkbox"/>
<b>ANY SPECIAL INSTRUCTIONS:</b> e.g. molecular models	

PART 1 – Short questions (clearly show your final answer).

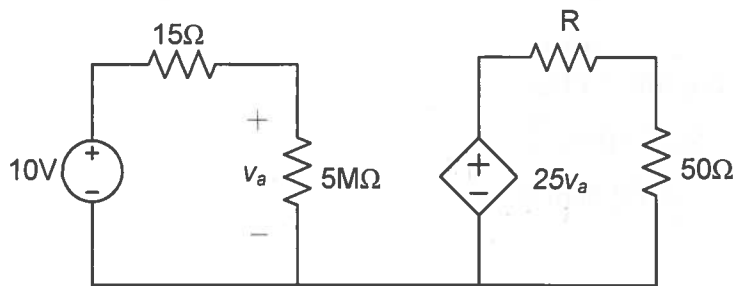- 1.1. In the circuit shown below, assume that the power absorbed by the load resistor of  $50\ \Omega$  is  $5\text{W}$ . Find the resistance value of the resistor  $R$ ? [2pts]



$$V_a = 10\text{V} \cdot \frac{5\text{M}\Omega}{15\Omega + 5\text{M}\Omega} \approx 10\text{V} \quad [\text{voltage division}]$$


$$V_{50\Omega} \rightarrow \frac{(V_{50\Omega})^2}{50\Omega} = 5\text{W} \rightarrow V_{50\Omega} = \sqrt{250}\text{V} \quad [P = V \cdot I = V(\frac{V}{R}) = \frac{V^2}{R}]$$

$$\sqrt{250}\text{V} = 25V_a \cdot \frac{50\Omega}{R + 50} \Rightarrow 250 \cdot \frac{50}{R + 50} = \sqrt{250} \Rightarrow \sqrt{250} \cdot 50 - 50 = R$$


[voltage div.]

$$\boxed{R = 740.57\ \Omega}$$

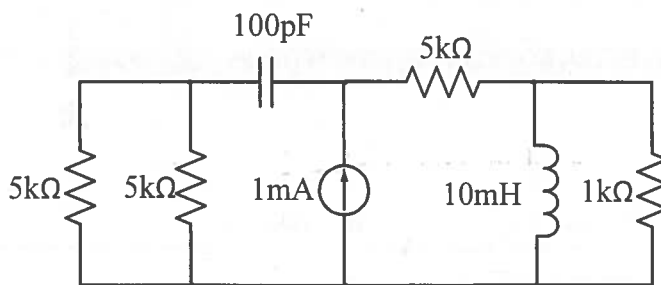- 1.2. Assume that the circuit below has reached dc steady state. What is the power delivered by the independent current source in the circuit? [2pts]



in dc steady-state

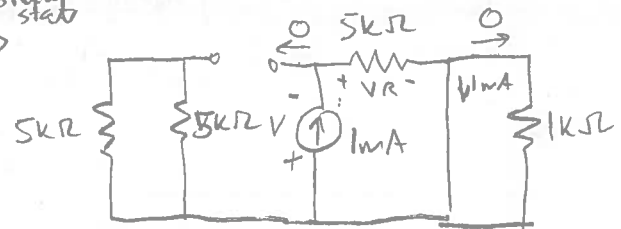


$$[\text{KVL}] \quad V + V_R = 0 \rightarrow V = -(1\text{mA} \times 5\text{k}\Omega) = -5\text{V}$$

$$[P = VI] \quad P = (-5\text{V})(1\text{mA}) = -5\text{mW}$$


Power delivered:  
 $5\text{mW}$

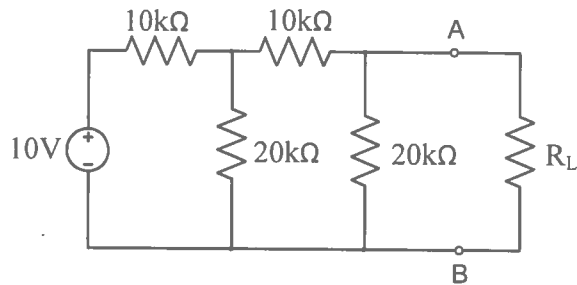- 1.3. A load resistor  $R_L$  is connected to the circuit at the terminals A and B of a resistive circuit with a voltage supply, as shown below. What should the load resistor  $R_L$  be for maximum power transfer from the circuit? [2pts]



$$R_L = R_T$$

Turn off supply

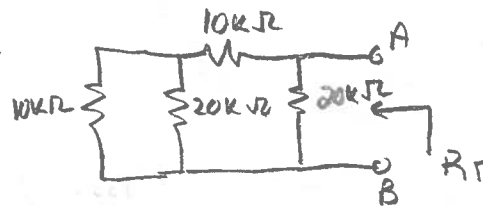


$$R_T = (20k\Omega) // (10k\Omega + (10k\Omega // 20k\Omega))$$

$$R_T = (20k\Omega) // (10k\Omega + 6.67k\Omega)$$

$$R_T = 9.09 k\Omega$$

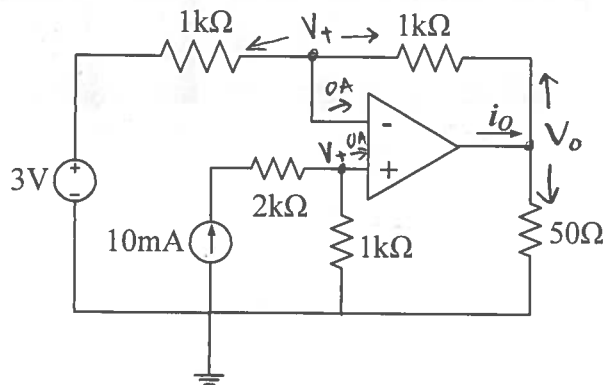- 1.4. Assume an ideal op-amp in the circuit shown below. What is the output current  $i_o$ ? [2pts]



$$V_{+} = 1k\Omega \times 10mA = 10V$$

KCL @ inv. node:

$$\frac{V_{+} - 3V}{1k\Omega} + \frac{V_{+} - V_o}{1k\Omega} = 0$$

$$2V_{+} - 3V = V_o$$

$$17V = V_o$$


KCL @ output node:

$$-i_o + \frac{V_o - V_{+}}{1k\Omega} + \frac{V_o}{50\Omega} = 0$$

$$i_o = \frac{7V}{1k\Omega} + \frac{17V}{50\Omega} = 347mA$$

$$i_o = 347mA$$

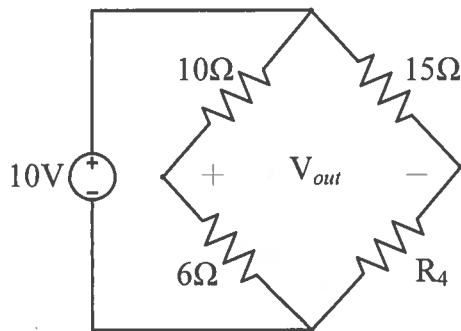- 1.5. The circuit below is called the Wheatstone Bridge which was explored in your lab. The circuit is said to be balanced when  $V_{out} = 0V$ . What is the resistance value  $R_4$  for the Wheatstone Bridge to be balanced? [2pts]



$$V_{out}^+ = 10V \cdot \frac{6\Omega}{6\Omega + 10\Omega}$$

$$V_{out}^- = 10V \cdot \frac{R_4}{15\Omega + R_4}$$

$$V_{out} = V_{out}^+ - V_{out}^-$$

$$V_{out} = 10V \left[ \frac{6\Omega}{16\Omega} - \frac{R_4}{15\Omega + R_4} \right]$$

Balanced  $\rightarrow V_{out} = 0V$

$$\frac{6\Omega}{16\Omega} = \frac{R_4}{15\Omega + R_4}$$


$$90 + 6R_4 = 16R_4$$

$$90R_4 = 10R_4$$

$$\boxed{R_4 = 9\Omega}$$


## PART 2 – Problems

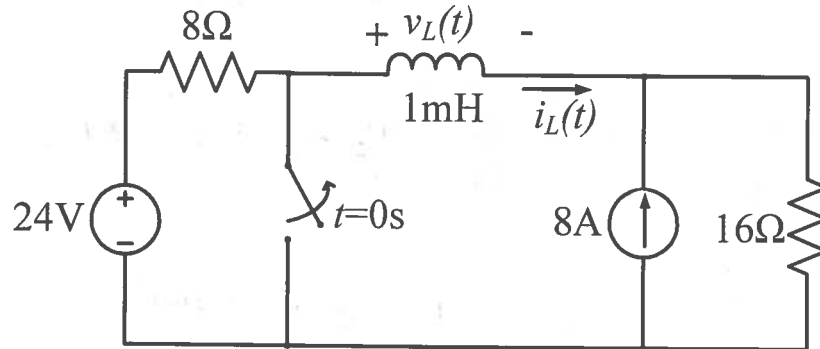- 2.1. Consider the circuit shown below. The switch is closed for  $t < 0$ s. Assume dc steady state behaviour for  $t < 0$ . The switch opens at  $t = 0$ s. Answer the following questions. [10pts]




- Find the solution for the current  $i_L(t)$  for  $t > 0$ .
- Plot your solution in (a) versus time  $t$ . Indicate the value of the current at  $t = 0^+$ ,  $t \rightarrow \infty$ , and indicate the time constant  $\tau$ .
- Find the voltage  $v_L(t)$  for  $t > 0$ .
- If the inductor was replaced by a capacitor, what would be the voltage across the capacitor at  $t = 0^+$ ?

a)  $t > 0$

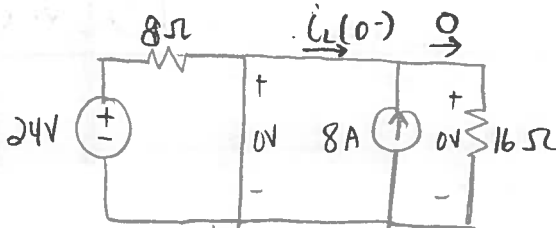

$$i_L(0^-) = -8A = i_L(0^+)$$

$t \rightarrow \infty$

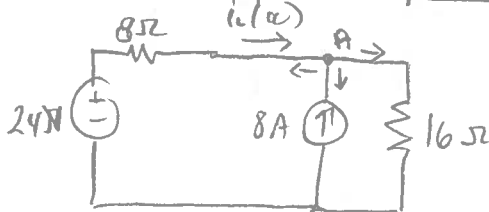

using node analysis:

$$\text{KCL @ A: } \frac{V_A - 24V}{8\Omega} - 8A + \frac{V_A}{16\Omega} = 0$$

$$2V_A - 48V - 128V + V_A = 0$$

$$3V_A = 176V \quad V_A = \frac{176}{3}V$$


$$i_L(\infty) = \frac{24V - 176/3V}{8\Omega} = -4\frac{1}{3}A$$

$$\text{Solution: } i_L(t) = i_L(\infty) + [i_L(0^+) - i_L(\infty)]e^{-t/\tau}$$

$$i_L(t) = -4\frac{1}{3}A + [-8A + 4\frac{1}{3}A]e^{-t/41.67\mu s}$$

$$i_L(t) = -4\frac{1}{3} - 3\frac{2}{3}e^{-t/41.67\mu s} A; t > 0s$$


$$\tau = L/R_T$$

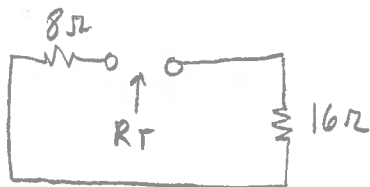

$$R_T = 8 + 16 = 24 \text{ ohm}$$

$$\tau = \frac{1mH}{24 \text{ ohm}} = 41.67 \mu s$$
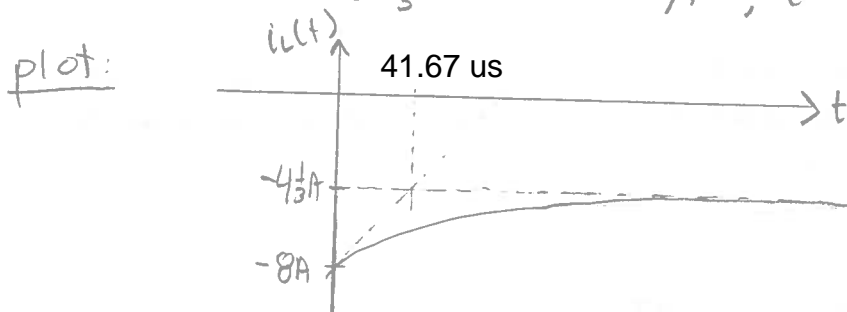
$$i_L(t) = -4\frac{1}{3} - 3\frac{2}{3} e^{-t/41.67 \mu s} \text{ A}, t > 0$$




$$b) \quad v_L(t) = L \frac{di_L(t)}{dt} = 1 \text{ mH} \frac{d}{dt} \left[ -4\frac{1}{3} - 3\frac{2}{3} e^{-t/41.67 \mu s} \right] \text{ V}$$

$$= 1 \text{ mH} \cdot \left[ -3\frac{2}{3} \cdot \frac{-1}{187.5 \mu s} e^{-t/41.67 \mu s} \right] \text{ V}$$

$$v_L(t) = 19.56 \text{ V} e^{-t/41.67 \mu s} \text{ V}, t > 0$$

c)  $t < 0$

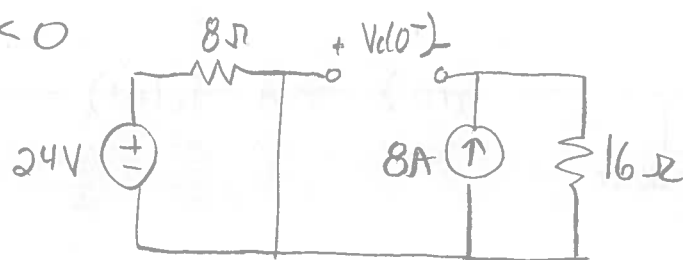


$$V_C(0^-) = V_C(0^+)$$

$$V_C^+(0^-) = 0 \text{ V} \quad V_C^-(0^-) = 8 \text{ A} \cdot 16 \Omega = 128 \text{ V}$$

$$V_C(0^-) = V_C(0^+) = 0 - 128 \text{ V} = -128 \text{ V}$$

$$V_C(0^+) = -128 \text{ V}$$

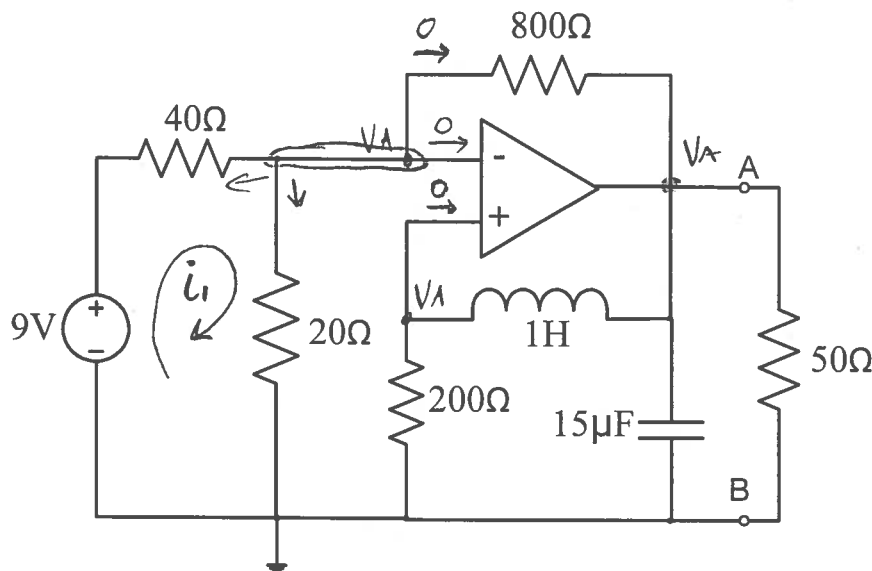- 2.2. Consider the circuit shown below. Assume that the op-amp is ideal and that the circuit is in dc steady state. Answer the following questions. [10pts]



- (a) Find the power dissipated by the independent voltage source of ~~8~~ 9V?  
 (b) Which resistor dissipates the largest amount of energy?  
 (c) What is the energy stored in the capacitor and in the inductor?

a) dc steady state  $\rightarrow$  inductor is a short and capacitor an open.  
 output voltage of opamp sets voltage at non-inverting node,  
 which sets voltage at inverting node. Thus, there is  
 no voltage drop across feedback resistor 800Ω

$$\text{KCL @ inv node: } \frac{V_A - 9V}{40\Omega} + \frac{V_A}{20\Omega} = 0 \rightarrow V_A - 9V + 2V_A = 0 \Rightarrow V_A = 3V$$

$$\text{KVL @ 9V mesh: } -9V + 40i_1 + 20i_1 = 0 \rightarrow i_1 = \frac{9}{60} A \Rightarrow i_1 = 150\mu A$$

$$P = V_1 = 9V \cdot 150\mu A = 1.35W$$

$$P_{9V} = 1.35W$$

b)

$$40\Omega: 6V \cdot 150\mu A = 0.9W$$

$$20\Omega: 3V \cdot 150\mu A = 0.45W$$

$$800\Omega: 0V \cdot 0A = 0W$$

$$200\Omega: \frac{V_A^2}{R} = \frac{9V^2}{200\Omega} = 45mW$$

$$50\Omega: \frac{V_A^2}{R} = \frac{9V^2}{50\Omega} = 0.18W$$

$$40\Omega \text{ resistor}$$

c) capacitor:  $\frac{1}{2} CV^2 = \frac{1}{2} \cdot 15 \times 10^{-6} \cdot 3^2$

inductor


$$\frac{1}{2} Li^2 = \frac{1}{2} \cdot 1H \cdot \left(\frac{3}{200}\right)^2$$

$$\begin{matrix} \text{cap: } 67.5\mu J \\ \text{ind: } 112.5\mu J \end{matrix}$$





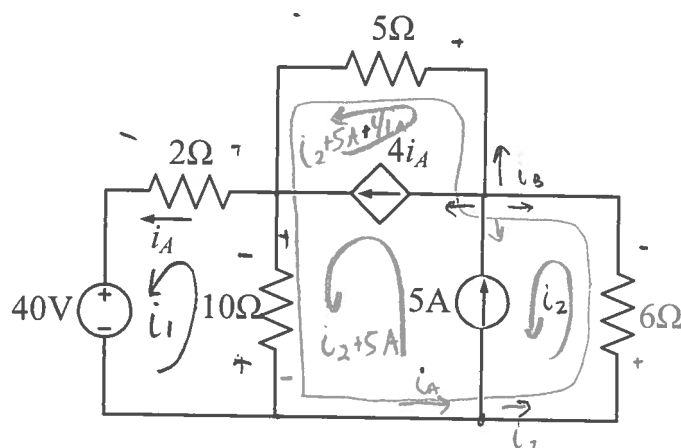2.3. Consider the circuit shown below. Answer the following questions. [10pts]



$$i_3 = i_2 + 5A + 4i_A$$

$$i_B = i_2 + 5A - 4i_A$$

$$-i_A + i_2 + 5A$$

(a) Find the current  $i_A$  using mesh analysis.

(b) What is the power delivered by the current-dependent current source?

a) using super-mesh, KVL:

$$6\Omega \cdot i_2 + 5\Omega [i_2 + 5A + 4i_A] + 10\Omega [i_2 + 5A - i_1] = 0$$

$$6i_2 + 5i_2 + 20 + 20i_A + 10i_2 + 50 - 10i_1 = 0$$

$$11i_2 + 20 + 20i_1 + 10i_2 + 50 - 10i_1 = 0$$

$$10i_1 + 21i_2 + 70 = 0$$

control  
variable:

$$i_1 = i_A$$

other mesh:  $40V + 10\Omega \cdot i_1 + 2\Omega i_1 = 0$

$$i_1 = \frac{40V}{12\Omega} = 3\frac{1}{3}A$$

sufficient to  
answer (a)

$$i_A = 3\frac{1}{3}A$$

b) Voltage across  $5\Omega$  will be the same as the  $4i_A$  source.

cont mesh analysis in (a) to solve for  $i_2$

$$10(3\frac{1}{3}) + 21i_2 + 70 \rightarrow i_2 = -\frac{1}{21} [33\frac{1}{3} + 70] =$$

$$V_{5\Omega} = 5\Omega [i_2 + 5A + 4i_A] = 50 [-4.92 + 5A + 4(3\frac{1}{3})]$$

$$i_2 = -4.92A$$

$$= 670.67V$$

$$P = 4i_A \times 670.67V = 8.94W$$

$$P = 8.94W$$

