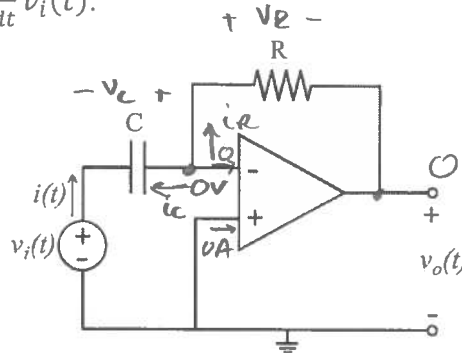


LAST NAME \_\_\_\_\_ MCGILL ID# \_\_\_\_\_

FIRST NAME \_\_\_\_\_ SIGNATURE \_\_\_\_\_

- Only Faculty standard calculator accepted
- No cellphone allowed
- Show all your work
- Clearly indicate your final answer with the SI unit and multiplier
- You have 45 minutes to complete this quiz

**Question 1:** Consider the circuit shown and assume ideal op-amp behavior. The op-amp circuit is configured as a differentiator where  $v_o(t) = -RC \frac{d}{dt} v_i(t)$ .



a) KCL at inverting node

$$i_c + i_R = 0 \quad i_c = C \frac{dv_e(t)}{dt}$$

$$0 = C \frac{d(0V - v_i(t))}{dt} + \frac{0V - v_o(t)}{R} \quad i_R = \frac{v_R(t)}{R}$$

$$-C \frac{dv_i(t)}{dt} - \frac{v_o(t)}{R} = 0$$

$$v_o(t) = -RC \frac{dv_i(t)}{dt}$$

- a) Derive the output voltage  $v_o(t)$  as a function of the input voltage  $v_i(t)$ . [1 pt]
- b) When the input voltage  $v_i(t)$  increases over time at a rate of 0.5 V over 1 milliseconds (0.5 V/ms), the current drawn by the input voltage source is 400  $\mu$ A ( $i(t) = 400 \mu$ A) and the output voltage value is  $v_o(t) = -5$  V. What values should  $R$  and  $C$  be for this to be possible? [3 pt]
- c) Assume now that the resistance of  $R$  is 10 k $\Omega$  ( $R = 10$  k $\Omega$ ) and the capacitance of  $C$  is 20 nF ( $C = 20$  nF). An ac input voltage  $v_i(t) = A_i \sin(\omega t)$  is applied to the input of the circuit where  $A_i = 2$  V. The frequency  $\omega$  is in radians ( $\omega = 2\pi f$ ) where the sinusoidal time period  $T$  is  $1/f$ . At which frequency  $f$  will the amplitude of the output voltage  $v_o(t)$  equal -2 V? [3 pt]

b)  $\frac{dv_i(t)}{dt} = 0.5 \text{ V/ms} \rightarrow i(t) = 400 \mu\text{A} \quad \& \quad v_o(t) = -5 \text{ V}$

from a)  $i(t) = -i_c(t) = -C \frac{d(0 - v_i(t))}{dt} = C \frac{dv_i(t)}{dt}$

$$400 \mu\text{A} = C \left[ \frac{0.5 \text{ V}}{\text{ms}} \right] \rightarrow C = \frac{400 \times 10^{-6} \text{ A} \cdot 1 \times 10^{-3} \text{ s}}{0.5 \text{ V}} = 800 \text{ nF}$$

$$v_o(t) = -RC \frac{d}{dt} v_i(t) = -5 \text{ V}$$

$$RC \left[ \frac{0.5 \text{ V}}{\text{ms}} \right] = 5 \text{ V} \rightarrow R = \frac{5 \text{ V}}{800 \times 10^{-9} \text{ F} \cdot 0.5 \text{ V}} = 12.5 \text{ k}\Omega$$

$$C = 800 \text{ nF}$$

$$R = 12.5 \text{ k}\Omega$$


c)  $v_o(t) = -RC \frac{d}{dt} v_i(t) = -RC \frac{d}{dt} (A_i \sin(\omega t)) = -RC A_i \omega \cos(\omega t)$

$$-RC A_i \omega = -2 \text{ V}$$

$$f = \frac{2 \text{ V}}{2\pi (RC A_i)} = \frac{2 \text{ V}}{2\pi (10 \times 10^3 \Omega \cdot 20 \times 10^{-9} \text{ F} \cdot 2 \text{ V})} = 795.77 \text{ Hz}$$


$$f = 795.77 \text{ Hz}$$

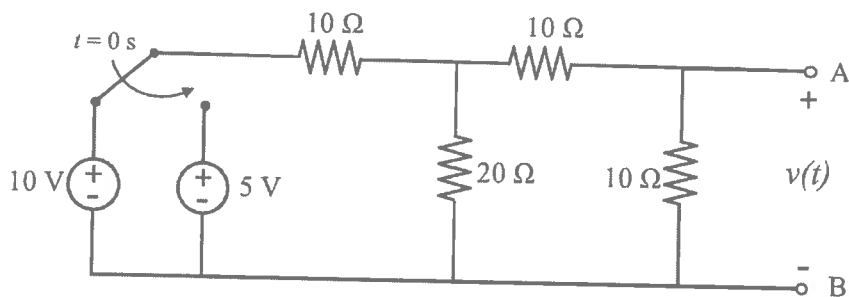**Question 2:** Consider the circuit shown below. The switch connects the 10 V independent voltage source for  $t < 0$  s. The circuit reaches steady state before the switch changes its connection to the other voltage source. For  $t > 0$  s, the switch connects the 5 V independent voltage source. Answer the following questions.



- Find the Thévenin equivalent circuit for  $t > 0$  s providing the open-circuit voltage ( $v_{oc}$ ) and the Thévenin resistance ( $R_T$ ). [2 pt]
- Connect a  $10 \mu\text{F}$  capacitor across the terminals A and B such that  $v(t)$  is the voltage across the capacitor. Find the values of voltage  $v(t)$  at  $t = 0^-$  s,  $t = 0^+$  s, and  $t \rightarrow \infty$ . In other words, find  $v(0^-)$ ,  $v(0^+)$ , and  $v(\infty)$ . [2 pt]
- Draw the Thévenin equivalent circuit found in part a) connecting the  $10 \mu\text{F}$  capacitor described in part b). As seen in class, the solution to the differential equation obtained from the KVL equation where the variable is  $v(t)$  is  $v(t) = c_1 + c_2 e^{-kt}$ . Find the value of  $k$ ,  $c_1$ , and  $c_2$ . Recall that  $k = \frac{1}{\tau} = \frac{1}{R_T C}$ . [2 pt]
- Plot  $v(t)$  as a function of time  $t$ . Clearly indicate the initial and final steady state values as well as the time constant  $\tau$ . At which time  $t$  does the voltage change the most, i.e., fastest rate of change? [2 pt]

a)  $t > 0$

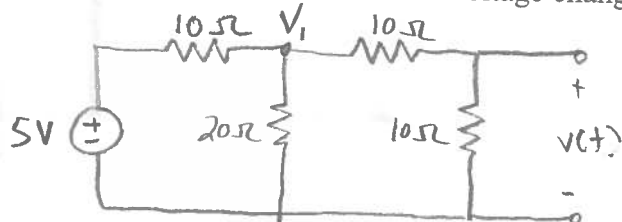

$$V_1 = 5V \cdot \frac{20\Omega // (10\Omega + 10\Omega)}{10\Omega + 20\Omega // (10\Omega + 10\Omega)} = 5V \cdot \frac{10\Omega}{10\Omega + 20\Omega // 20\Omega}$$

$$V_{oc} = V_1 \cdot \frac{10\Omega}{10\Omega + 10\Omega} \quad \boxed{V_{oc} = 1.25V \quad R_T = 6.25\Omega}$$

$$R_T = 10\Omega // (10\Omega + 10\Omega // 20\Omega) = 6.25\Omega$$

b)  $t = 0^-$



$$V(0^-) = V(0^+) = \frac{V_1(0^-) 10\Omega}{10\Omega + 10\Omega} = \frac{1}{2} \cdot 10V \cdot \frac{20\Omega // 20\Omega}{10\Omega + 20\Omega // 20\Omega}$$

$$\boxed{V(0^-) = V(0^+) = 2.5V \quad V(\infty) = 1.25V}$$


c)



$$k = \frac{1}{\tau} = \frac{1}{R_T C} = \frac{1}{6.25\Omega \cdot 10\mu\text{F}} = \frac{1}{62.5\mu\text{s}} = \frac{1}{62.5 \cdot 10^{-6}} = 16 \times 10^3 \text{ s}^{-1} = k$$

$$V(\infty) = c_1 + c_2 e^{-k\infty} = \boxed{c_1 = 1.25V} \quad v(0^+) = 1.25V + c_2 = 2.5V \quad \boxed{c_2 = 1.25V}$$

d)

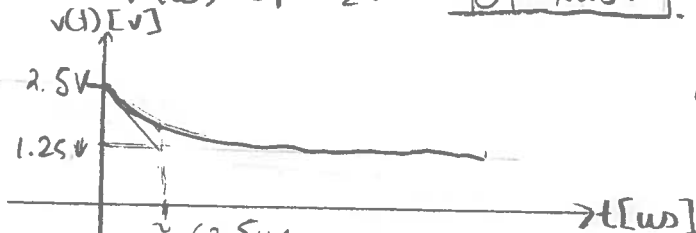

at  $t = 0^+$ ,  
fastest rate  
of change