

Today's Outline

4. Circuit Theorems


- Norton's Theorem

Norton's Theorem

Norton's Theorem: any two terminal circuit composed of independent sources, dependent sources and ideal resistors is equivalent to a parallel combination of a current source and an ideal resistor, known as a **Norton equivalent circuit**. Norton's theorem follows from Thévenin's theorem by a source transformation.




Edward Lawry Norton
(1898-1983)

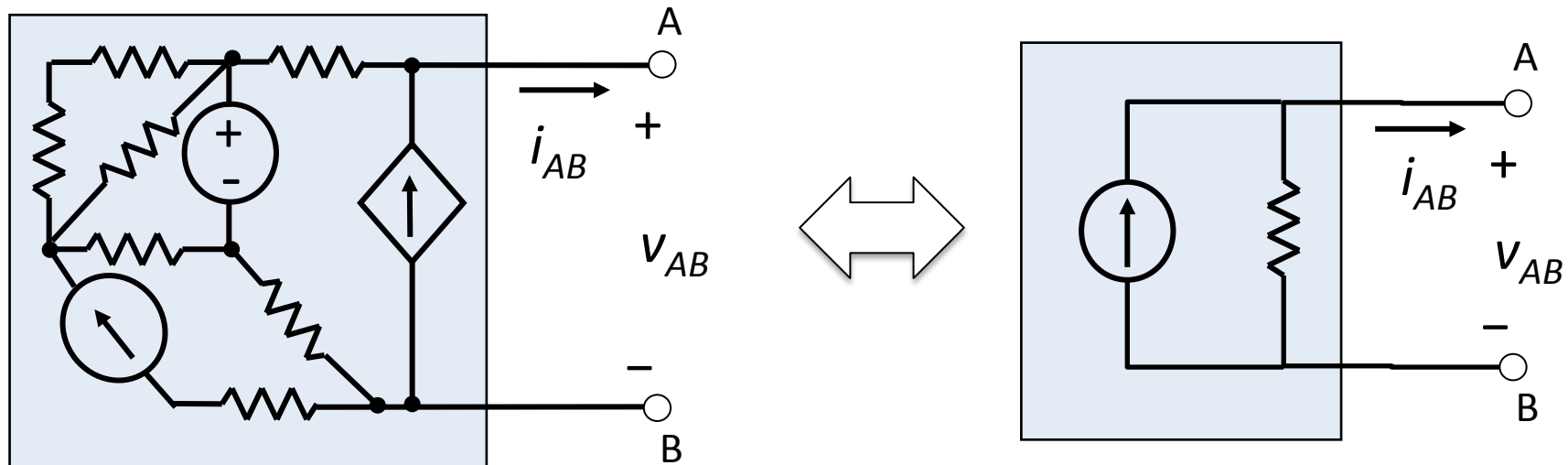

Thévenin and Norton Equivalent Circuits


We can convert between a Thévenin equivalent circuit and a Norton equivalent circuit using the source transformation.

$$V_{oc} = i_{sc} R_T$$

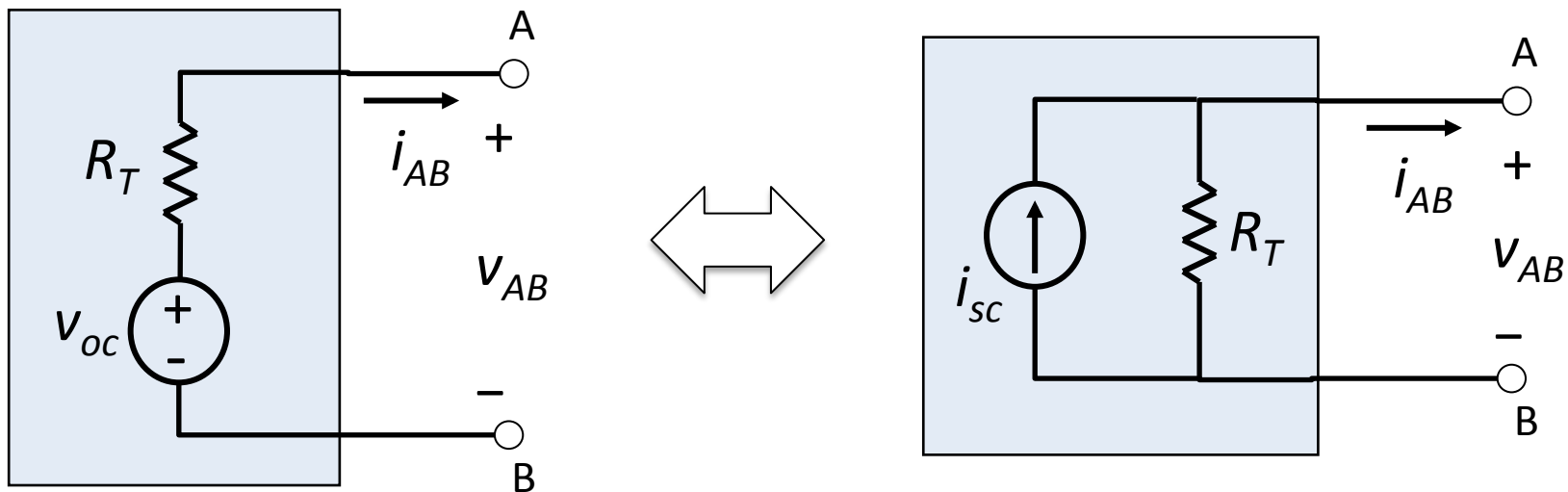

Norton Equivalent Circuit

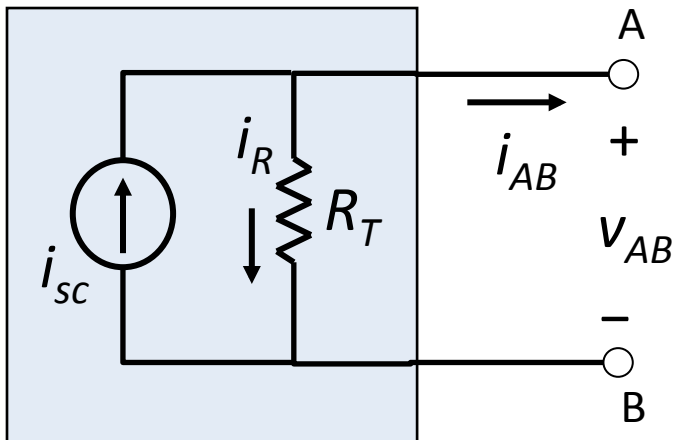To understand the meaning of the current source, which we denote i_{sc} , we analyze the terminal law for the Norton equivalent circuit.




$$\text{KCL: } 0 = -i_{sc} + i_R + i_{AB}$$

$$\text{Ohm: } i_R = v_{AB} / R_T$$

Combining the above:


$$i_{AB} = i_{sc} - v_{AB} / R_T$$

Short Circuit Current

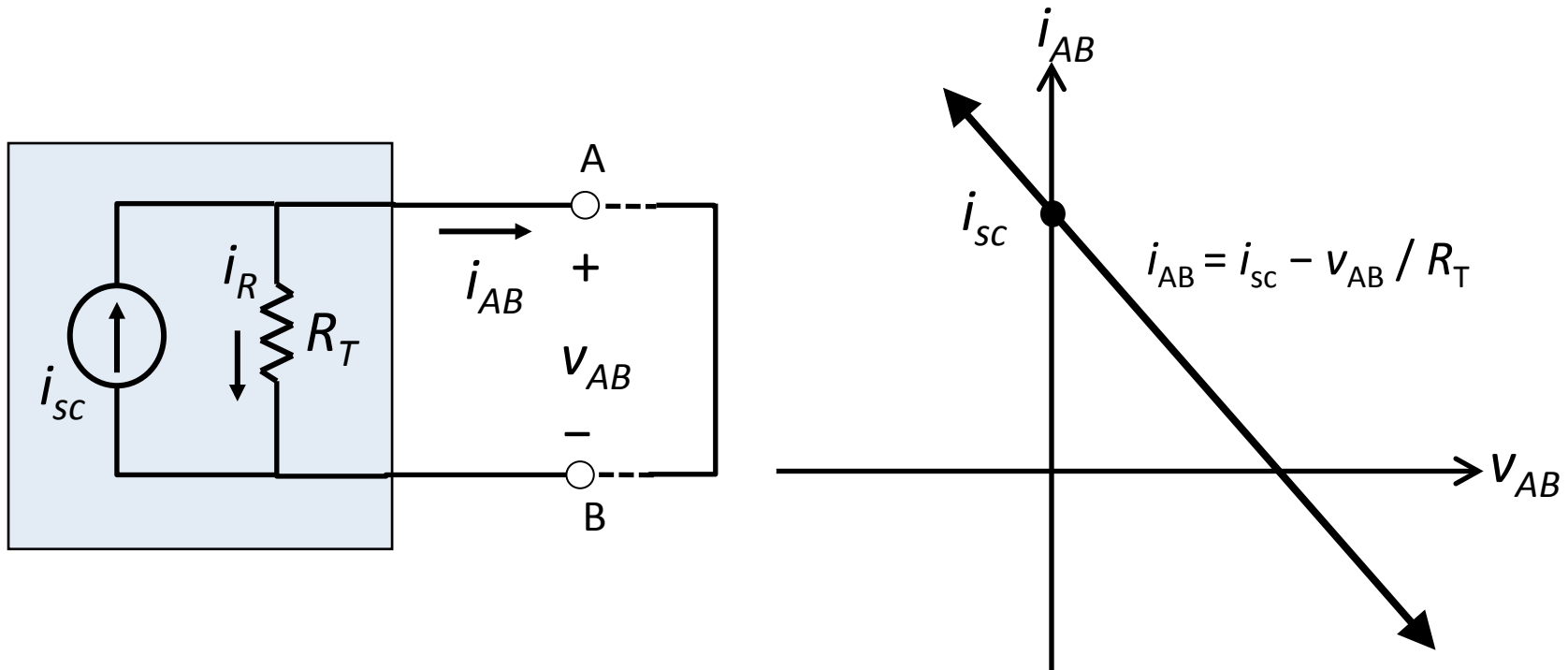


The current i_{sc} is the **short circuit current**, the current that flows through the terminals AB when there is zero terminal voltage $v_{AB}=0V$ (the terminals AB are said to be *shorted*).

Thévenin Resistance

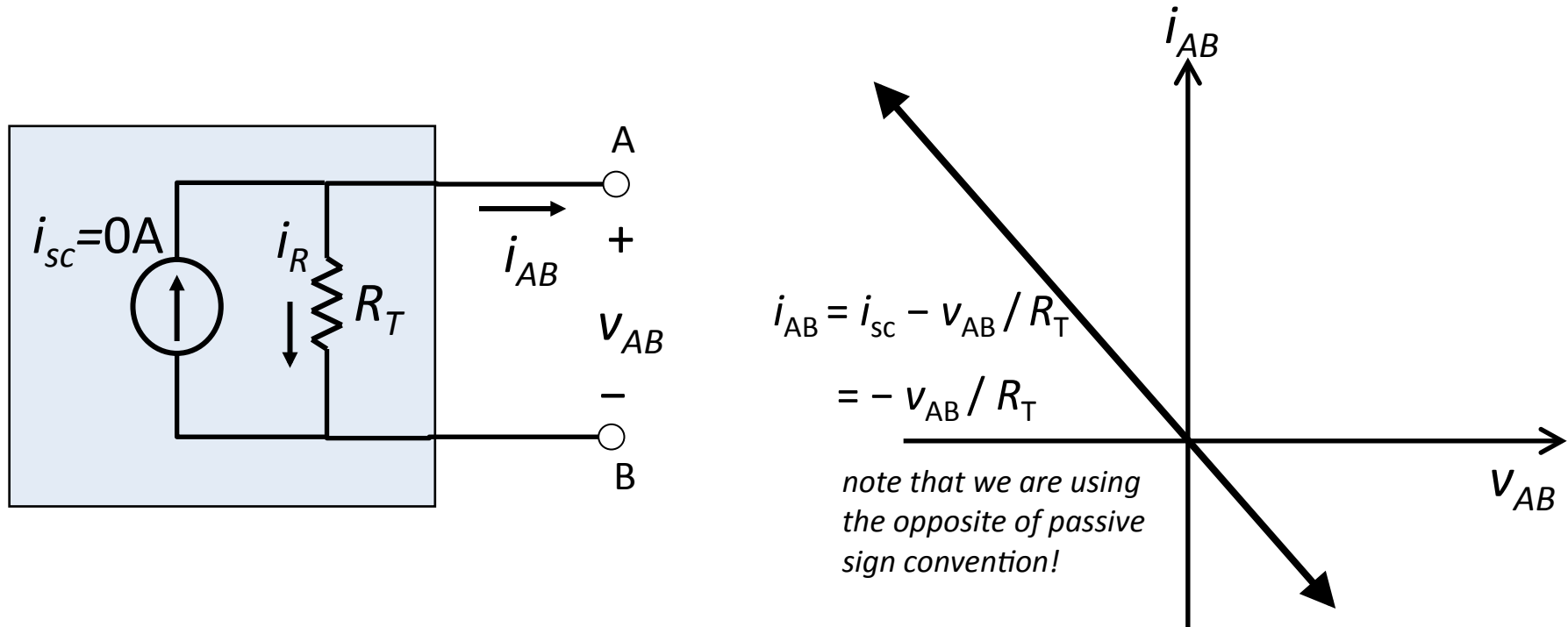

If the current source is *turned off*, $i_{sc} = 0A$, the circuit behaves like an ideal resistor with value equal to the **Thévenin resistance**, R_T .


Finding a Norton Equivalent Circuit

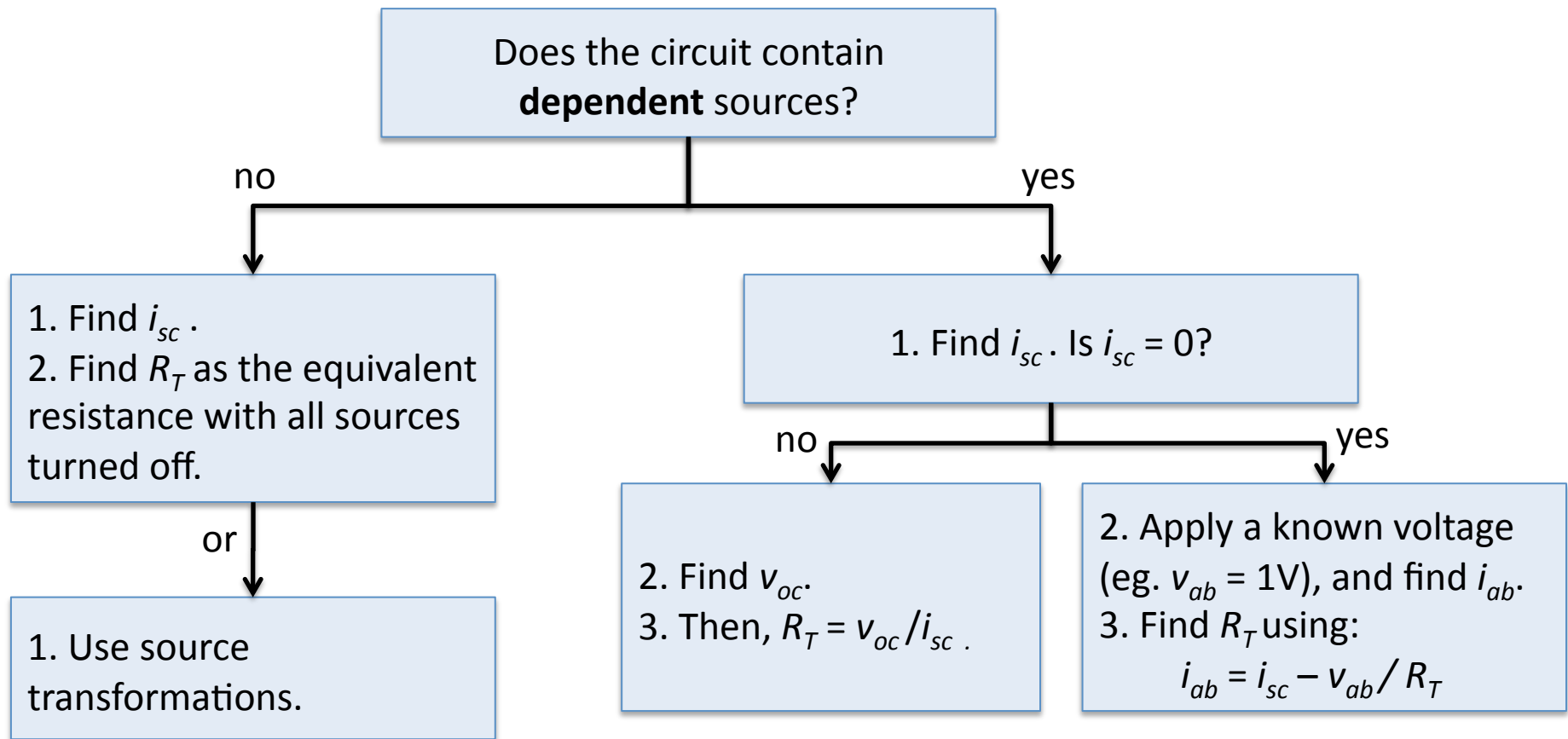

Here, we find i_{sc} first instead of v_{oc} . Alternatively, you can find the Thévenin circuit and apply a source transformation.

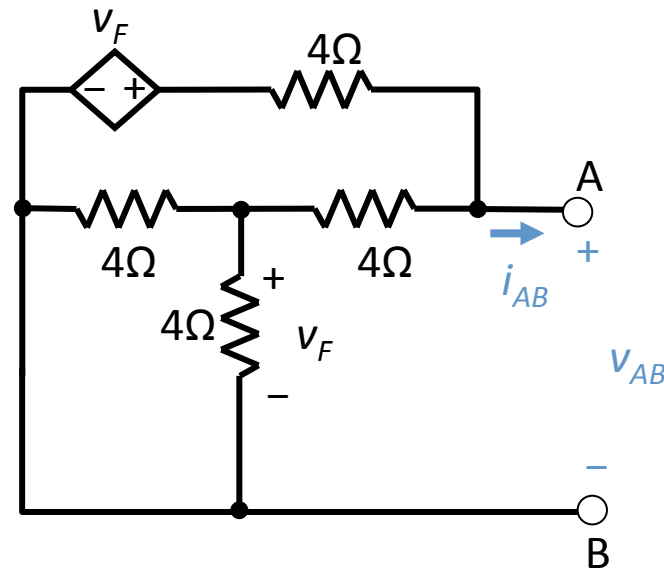Example 1


Find the Norton equivalent of the following circuit with respect to the terminals AB.



Strategy: Find i_{sc} , then v_{oc} , and then $R_T = v_{oc} / i_{sc}$. If this does not work, apply a test source or solve for i_{AB} - v_{AB} directly.

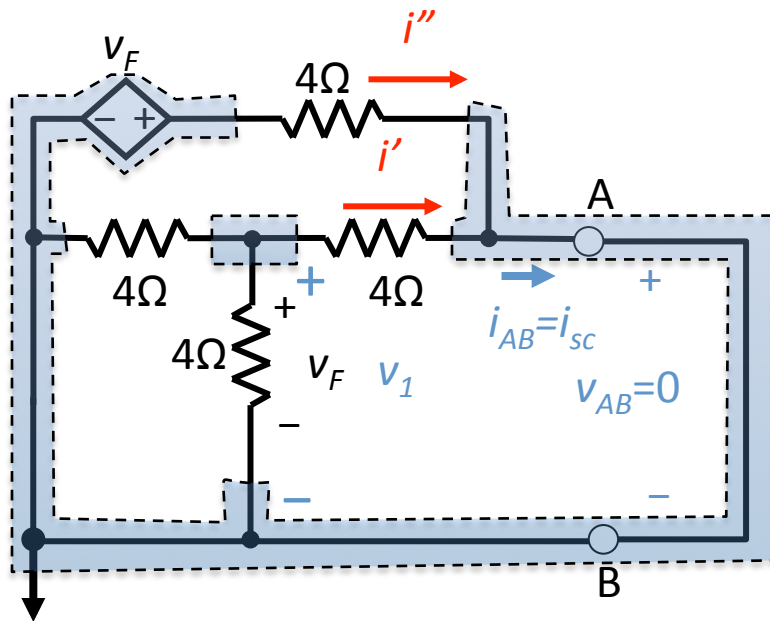Example 1

First, apply a short to AB and find i_{sc} .



We can solve with a single node voltage equation and control variable equation:

$$0 = \frac{v_1}{4\Omega} + \frac{v_1}{4\Omega} + \frac{v_1}{4\Omega}$$


$$v_F = v_1$$

$$\rightarrow v_F = v_1 = 0V$$


$$i_{sc} = i' + i'' = \frac{v_1}{4\Omega} + \frac{v_F}{4\Omega} = 0A$$

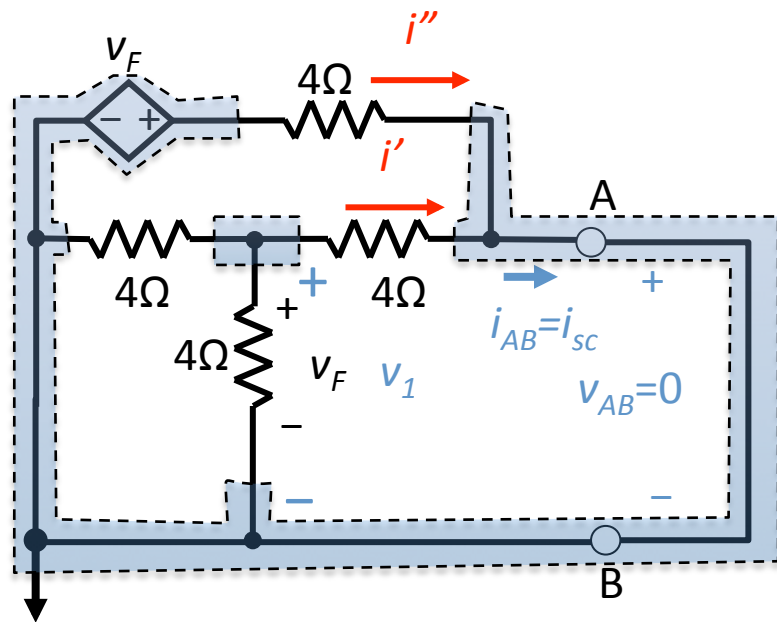Example 1

Since $i_{sc} = 0$, the i_{AB} - v_{AB} line passes through the origin. The two intercepts corresponding to open circuit and short circuit conditions are in fact the same intercept!



$$R_T = v_{oc} / i_{sc} = 0V / 0A =$$

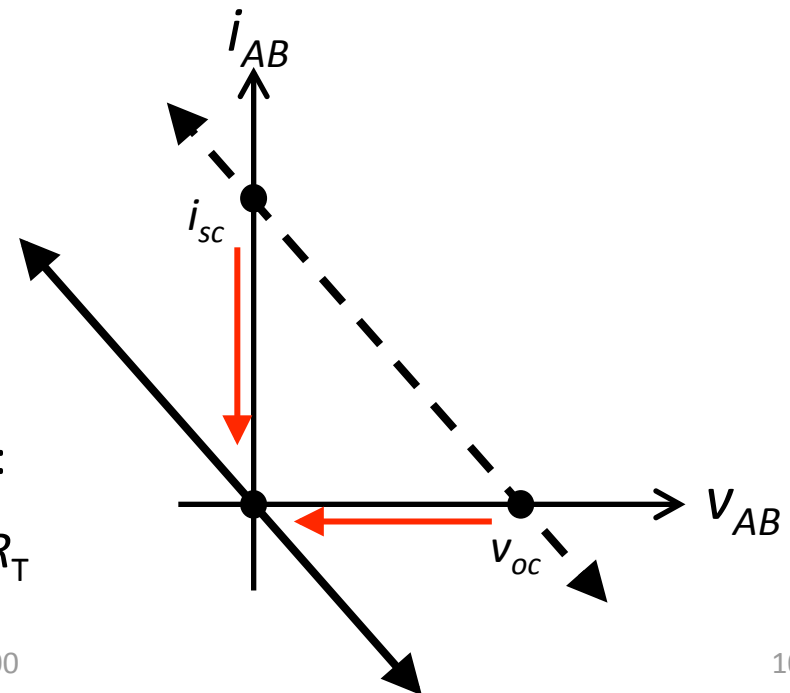


The equation of the line is simplified:

$$i_{AB} = i_{sc} - v_{AB} / R_T = -v_{AB} / R_T$$

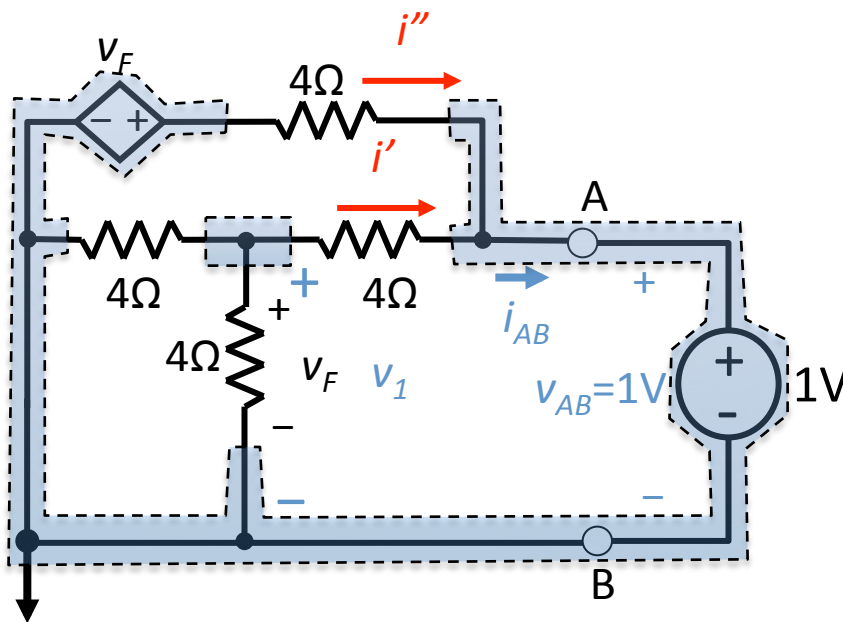Example 1

We need another point on the line. We therefore apply a test voltage of $v_{AB}=1V$ and find the resulting i_{AB} . We could also apply a test current and find the resulting voltage.



We can solve with a single node voltage equation and control variable equation:

$$0 = \frac{v_1}{4\Omega} + \frac{v_1}{4\Omega} + \frac{v_1 - 1V}{4\Omega}$$




$$v_F = v_1$$

$$\rightarrow v_1 = \frac{1/4}{3/4} V = \frac{1}{3} V$$

$$\begin{aligned} i_{AB} = i' + i'' &= \frac{v_1 - 1V}{4\Omega} + \frac{v_F - 1V}{4\Omega} \\ &= \frac{-2/3V}{4\Omega} + \frac{-2/3V}{4\Omega} \\ &= -\frac{1}{3} A \end{aligned}$$

Example 1

We now have another point on the line:

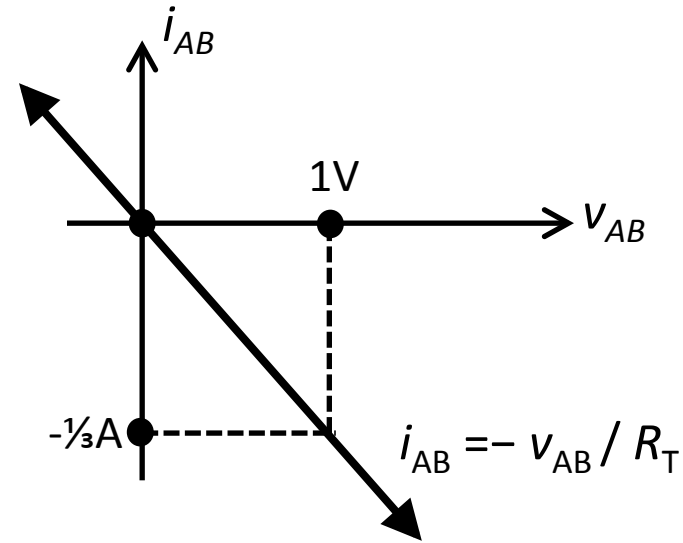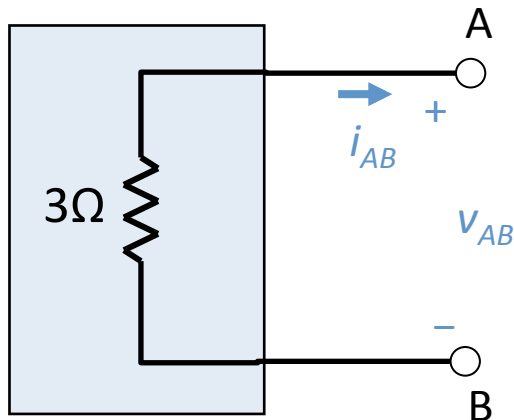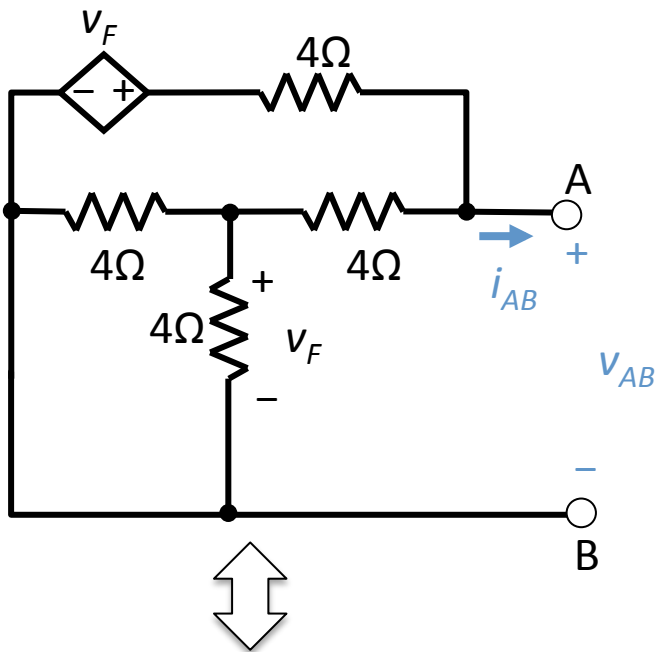


$$\therefore R_T = -\frac{v_{AB}}{i_{AB}} = -\frac{1V}{-\frac{1}{3}A} = 3\Omega$$

Using the fact that a 0A source is an open circuit, the Norton equivalent circuit becomes a Thévenin resistance.

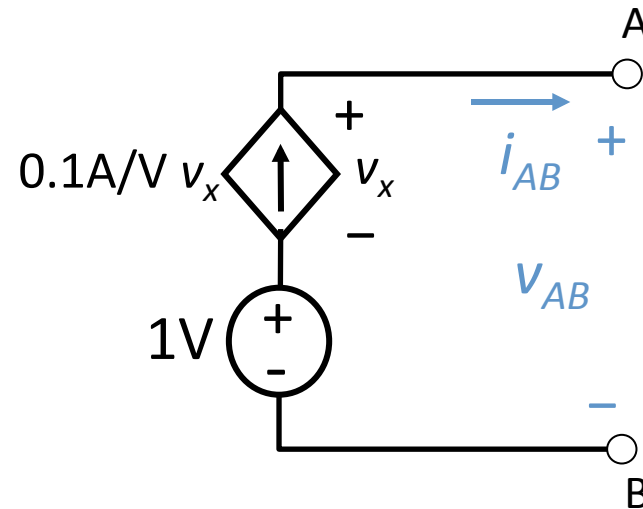Example 2


Find the Norton equivalent of the following circuit with respect to the terminals AB.



Strategy: Find i_{sc} , then v_{oc} , and then $R_T = v_{oc} / i_{sc}$. If this does not work, apply a test source or solve for i_{AB} - v_{AB} directly.

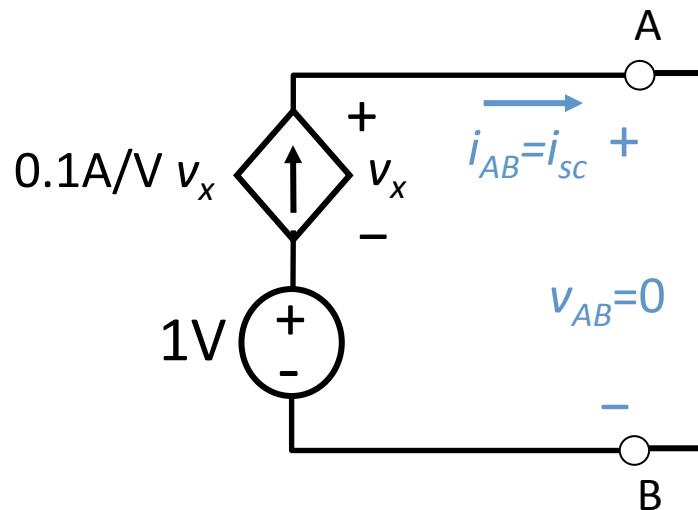Example 2

First, apply a short circuit to AB, and find i_{sc} .




We can solve with a single KVL equation and control variable equation:

$$0 = -1V - v_x \rightarrow v_x = -1V$$

$$i_{sc} = 0.1 \frac{A}{V} \cdot v_x = -100mA$$

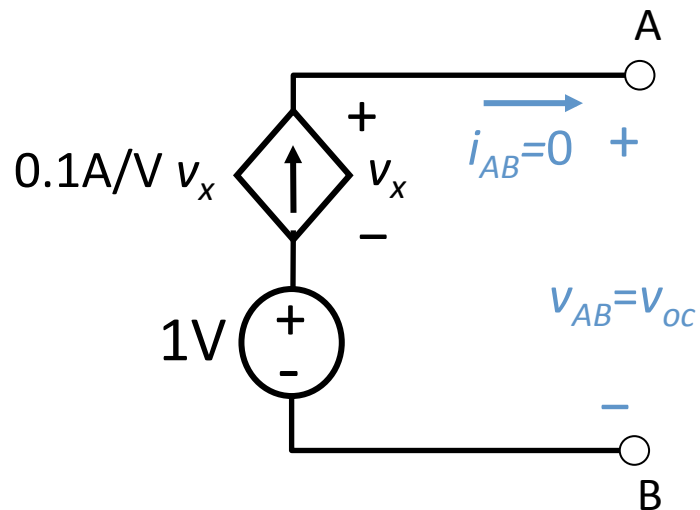Example 2

Second, apply an open circuit to AB, and find v_{oc} .



We can solve with a control variable equation and a single KVL equation:

$$0 = i_{AB} = 0.1 \frac{\text{A}}{\text{V}} \cdot v_x \rightarrow v_x = 0\text{V}$$

$$0 = -1\text{V} - v_x + v_{oc} \rightarrow v_{oc} = 1\text{V} - v_x = 1\text{V}$$

Example 2


The i_{AB} - v_{AB} diagram has an opposite slope to what we usually observe. The Thévenin resistance is negative!

$$R_T = \frac{v_{oc}}{i_{sc}} = \frac{1V}{-100mA} = -10\Omega$$


One consequence is that this circuit model can *deliver* an arbitrarily large amount of power $p_{DEL} = i_{AB} v_{AB}$.

Suggestion: Show that the Thévenin resistance is still negative if you swap the labels A and B.

Question: What happens if a 10Ω load resistance is connected across A and B?

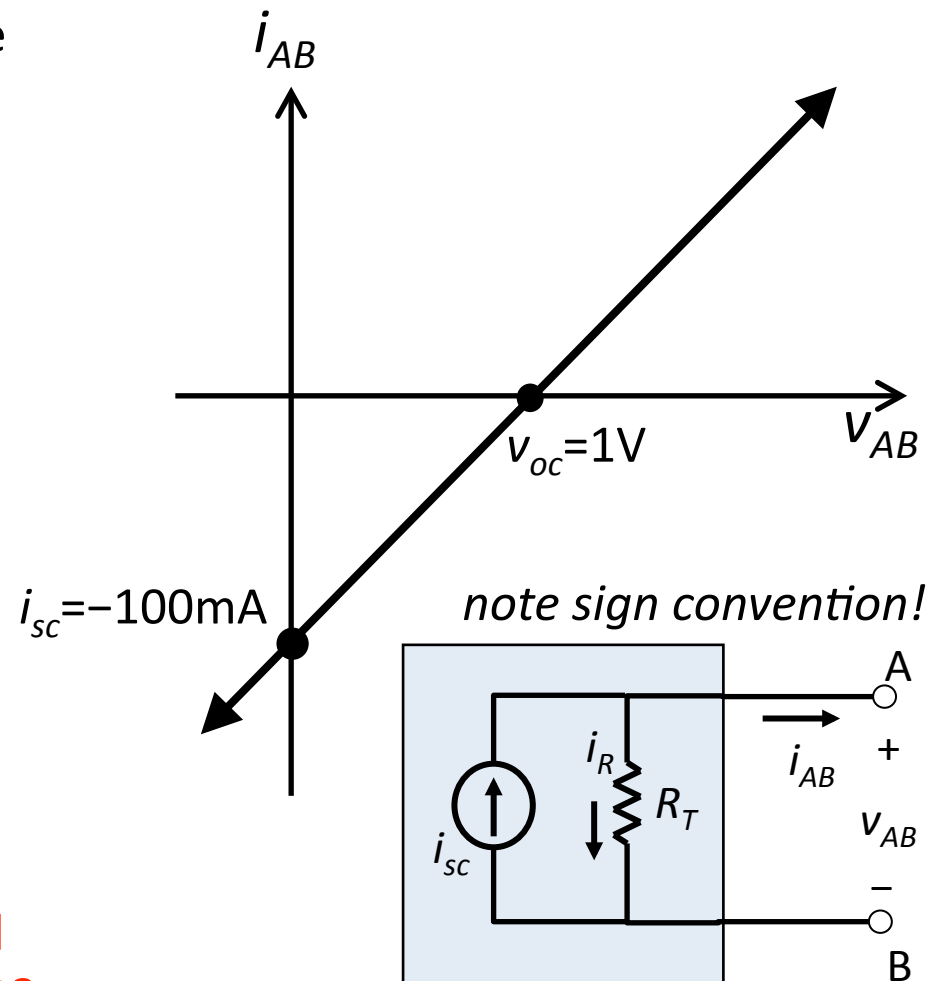

Example 2: Negative Thévenin Resistance

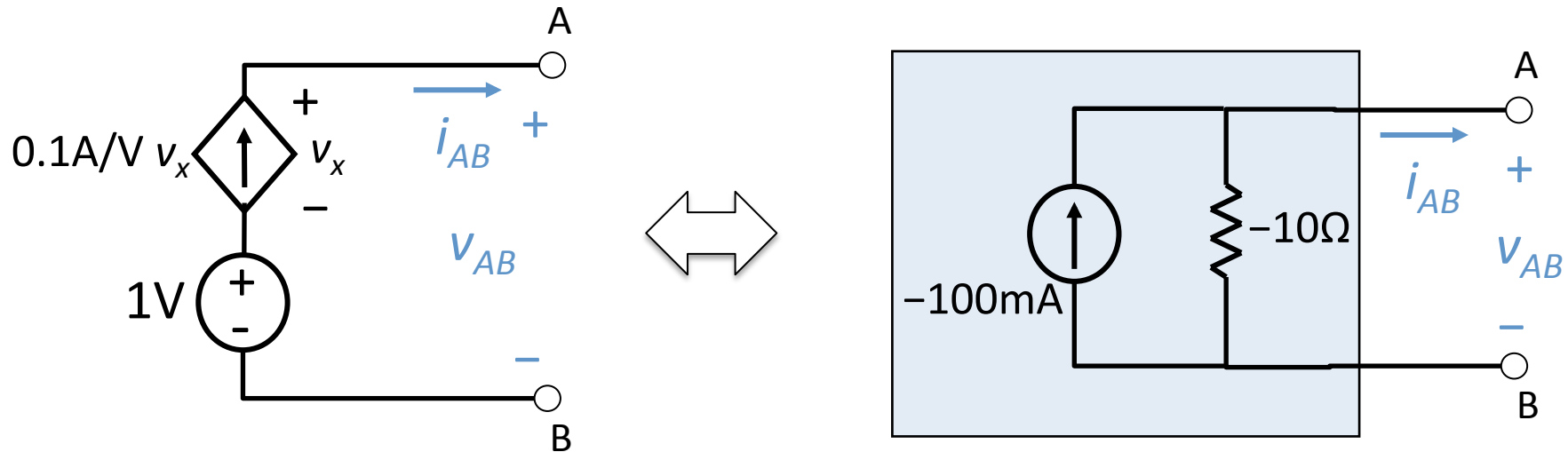

Remember that the Norton and Thévenin equivalent circuits are just compact models to represent linear two-terminal circuits.

Circuits with dependent sources can give rise to negative Thévenin resistance. *Does this mean that nature permits a “negative resistance”?*

