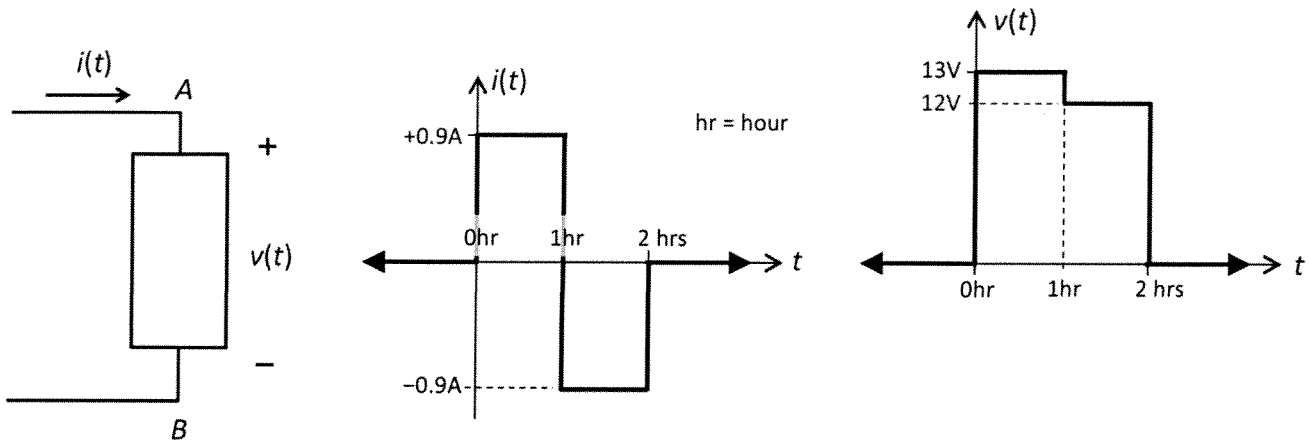


NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

1. Consider the circuit diagram and plots. Answer the questions.



a) Plot the net charge  $q(t)$  that has entered the element through terminal A versus time  $t$ . You may assume that  $q(t) = 0$  for  $t < 0$ . Label the axes of your plot with SI units. [3pts]

b) Plot the net instantaneous power  $p(t)$  absorbed by the element versus time  $t$ . Label the axes of your plot with SI units. [3pts]


c) Plot the net energy  $U(t)$  absorbed by the element versus time  $t$ . You may assume that  $U(t) = 0$  for  $t < 0$ . Label the axes of your plot with SI units. [4pts]

$$\text{a) } q(t) = q(0) + \int_0^t i(t') dt'$$

$$q_{\max} = 0.9\text{A} \cdot 1\text{hr}$$


$$= 0.9\text{A} \cdot 3600\text{s}$$

$$= 3.24\text{ kC}$$

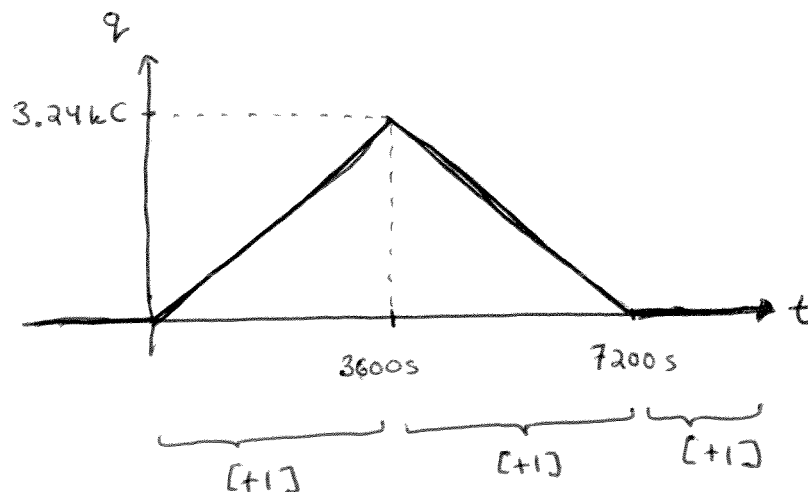

work space

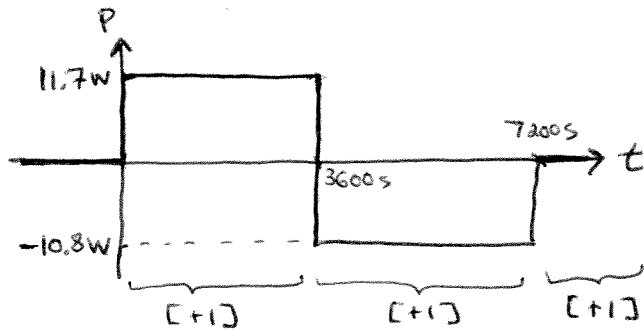
$$b) \quad p(t) = i(t)v(t) = \begin{cases} 13V \cdot 0.9A = 11.7W & 0 < t < 3600s \\ 12V \cdot (-0.9A) = -10.8W & 3600s < t < 7200s \end{cases}$$




$$c) \quad U(t) = U(0) + \int_0^t p(t') dt' \quad [1]$$

$$U_{\max} = 11.7W \cdot 3600s = 42.12kJ$$
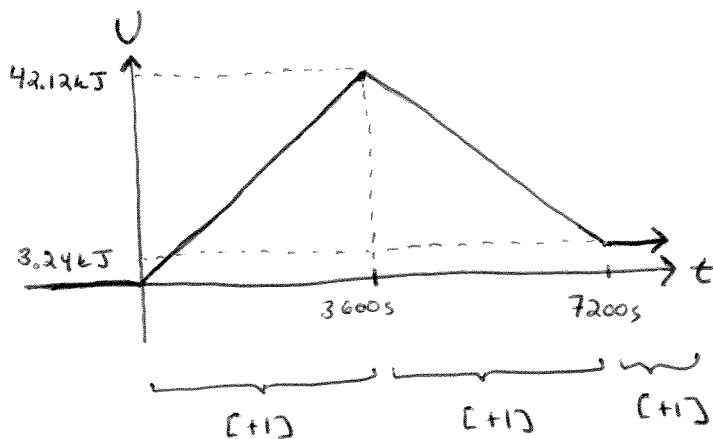
$$U(2hrs) = 11.7W \cdot 3600s + (-10.8W) \cdot 3600s \\ = 3.24kJ$$



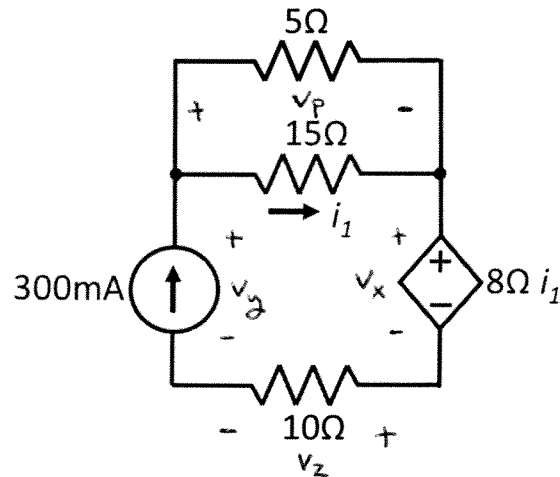2. Consider the circuit diagram. Answer the questions.



- What is the power delivered or absorbed by the dependent source? [3pts]
- What is the power delivered or absorbed by the independent source? [4pts]
- How long must one wait for the 10Ω resistor to dissipate 1kW-hr of energy? Note that the local cost for 1kW-hr is about \$0.05. [3pts]

$$\begin{aligned} a) \quad i_1 &= 300 \text{ mA} \cdot \frac{5\Omega}{5\Omega + 15\Omega} \\ &= 75 \text{ mA} \quad [+1] \end{aligned}$$

$$\begin{aligned} P_{\text{dep}} &= v_X \cdot 300 \text{ mA} \quad [+1] \\ \text{abs} \\ &= (8\Omega \cdot 75 \text{ mA}) \cdot 300 \text{ mA} \\ &= 180 \text{ mW absorbed by dependent source} \quad [+1] \end{aligned}$$

$$\begin{aligned} b) \quad v_P &= 15\Omega \cdot i_1 = 15\Omega \cdot 75 \text{ mA} \quad (0 \text{ hm}) \\ &= 1.125 \text{ V} \quad [+1] \\ v_Z &= 10\Omega \cdot 300 \text{ mA} \quad (0 \text{ hm}) \\ &= 3.0 \text{ V} \quad [+1] \end{aligned}$$

work space

$$\text{KVL: } 0 = -V_y + V_p + V_x + V_z$$

$$V_y = V_p + V_x + V_z$$

$$= 1.125\text{ V} + 8\Omega \cdot 75\text{ mA} + 3.0\text{ V}$$

$$= 4.725\text{ V} \quad [+1]$$

$$P_{\text{ind del}} = 300\text{ mA} \cdot V_y$$

$$= 300\text{ mA} \cdot 4.725\text{ V}$$

$$= 1.4175\text{ W} \quad \text{delivered by independent source } [+1]$$

$$\begin{aligned} \text{c) } P_{\text{diss}} &= (300\text{ mA})^2 \cdot 10\Omega \\ &= 0.9\text{ W} \quad [+1] \end{aligned}$$

$$\frac{\Delta U_{\text{diss}}}{\Delta t} = P_{\text{diss}} \quad [+1]$$

$$\Delta t = \frac{\Delta U_{\text{diss}}}{P_{\text{diss}}} = \frac{1\text{ kW-hr}}{0.9\text{ W}} = 1111.1\text{ hrs}$$

$$= 4\text{ Ms}$$

$$= 4 \times 10^6\text{ s}$$


$$= 46\text{ days } 7\text{ hrs } 6\text{ min } 40\text{ s}$$

[+1] for  
any

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

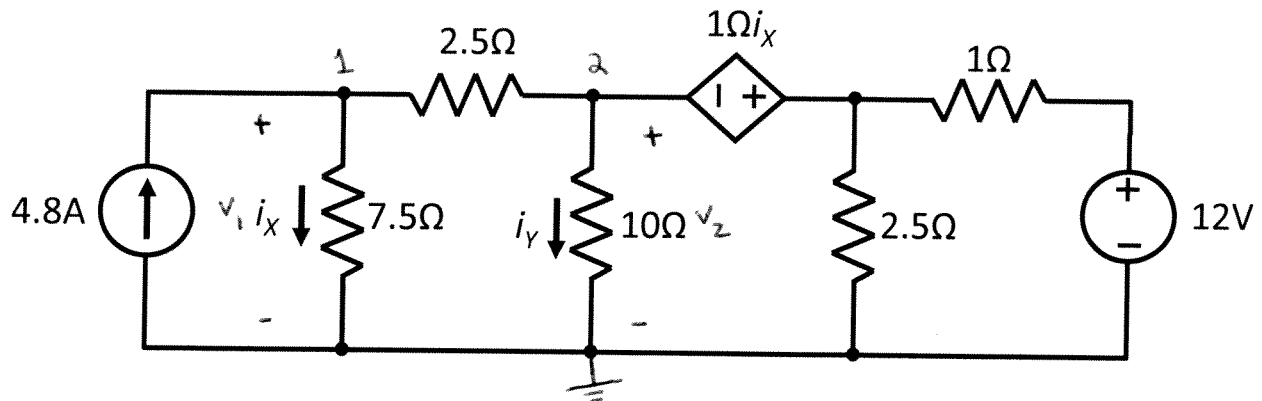1. Consider the circuit diagram. Answer the questions.



- What is the value of the current  $i_x$ ? [6pts]
- What is the value of the current  $i_y$ ? [2pts]
- How much power does the independent current source deliver or absorb? [2pts]

$$a) \quad -4.8 + \frac{v_1}{7.5} + \frac{v_1 - v_2}{2.5} = 0 \quad [+2]$$

$$\frac{v_2 - v_1}{2.5} + \frac{v_2}{10} + \frac{v_2 + i_x}{2.5} + \frac{v_2 + i_x - 12}{1} = 0 \quad [+2]$$

$$i_x = v_1 / 7.5 \quad [+1]$$

$$4.8 = 0.5333 v_1 - 0.4 v_2$$

$$12 = -0.2133 v_1 + 1.9 v_2$$

work space

$$V_1 = \frac{\begin{vmatrix} 4.8 & -0.4 \\ 12 & 1.9 \end{vmatrix}}{\begin{vmatrix} 0.5333 & -0.4 \\ -0.2133 & 1.9 \end{vmatrix}} = \frac{13.92}{0.9279} = 15.00 \text{ V}$$

$$i_x = \frac{15.00 \text{ V}}{7.5 \Omega} = 2.00 \text{ A} \quad [+1]$$


$$b) \quad i_y = \frac{V_2}{10 \Omega} \quad [+1]$$

$$V_2 = \frac{\begin{vmatrix} 0.5333 & 4.8 \\ -0.2133 & 12 \end{vmatrix}}{\begin{vmatrix} 0.5333 & -0.4 \\ -0.2133 & 1.9 \end{vmatrix}} = \frac{7.423}{0.9279} = 8.00 \text{ V}$$

$$i_y = \frac{8.00 \text{ V}}{10 \Omega} = 0.8 \text{ A} \quad [+1]$$

$$\begin{aligned} c) \quad P_{\text{del}} &= 4.8 \text{ A} \cdot V_1 \quad [+1] \\ &= 4.8 \text{ A} \cdot 15.00 \text{ V} \\ &= 72 \text{ W delivered by independent } \underset{\text{current}}{V} \text{ source} \quad [+1] \end{aligned}$$

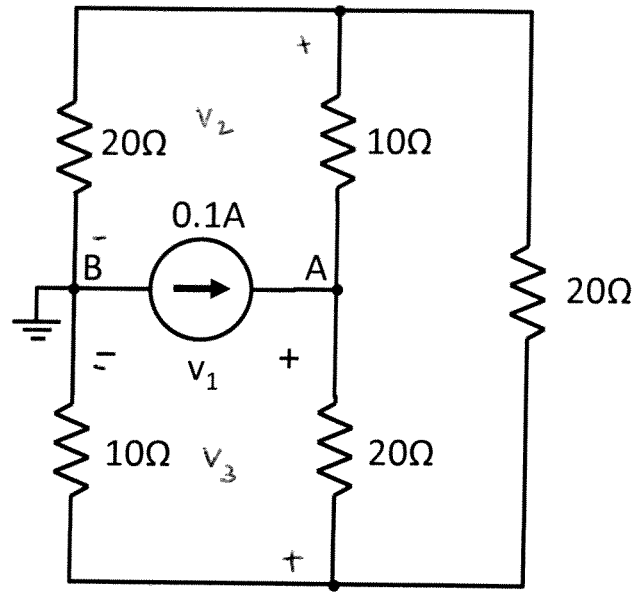2. Consider the circuit diagram. Answer the questions.



a) What is the voltage  $v_1$ ? [5pts]

b) Show by explicit calculation of currents that KCL is satisfied at node B. [2pts]

c) The current source is removed from the circuit, leaving a network of resistors alone. What is the equivalent resistance between nodes A and B? [2pts]

HINT: Consider your work in part a).

$$a) \quad 0 = -0.1 + \frac{v_1 - v_2}{10} + \frac{v_1 - v_3}{20} \quad [+1]$$

$$0 = \frac{v_2}{20} + \frac{v_2 - v_1}{10} + \frac{v_2 - v_3}{20} \quad [+1]$$

$$0 = \frac{v_3}{10} + \frac{v_3 - v_1}{20} + \frac{v_3 - v_2}{20} \quad [+1]$$

$$0.1 = 0.15 v_1 - 0.1 v_2 - 0.05 v_3$$

$$0 = -0.1 v_1 + 0.2 v_2 - 0.05 v_3$$

$$0 = -0.05 v_1 - 0.05 v_2 + 0.2 v_3$$

work space

$$V_1 = \frac{\begin{vmatrix} 0.1 & -0.1 & -0.05 \\ 0 & 0.2 & -0.05 \\ 0 & -0.05 & 0.2 \end{vmatrix}}{\begin{vmatrix} 0.15 & -0.1 & -0.05 \\ -0.1 & 0.2 & -0.05 \\ -0.05 & -0.05 & 0.2 \end{vmatrix}} = \frac{3.75 \times 10^{-3}}{2.625 \times 10^{-3}} = 1.429 \text{ V} \quad [+2]$$

$$b) \quad V_2 = \frac{\begin{vmatrix} 0.15 & 0.1 & -0.05 \\ -0.1 & 0 & -0.05 \\ -0.05 & 0 & 0.2 \end{vmatrix}}{\begin{vmatrix} 0.15 & -0.1 & -0.05 \\ -0.1 & 0.2 & -0.05 \\ -0.05 & -0.05 & 0.2 \end{vmatrix}} = \frac{2.25 \times 10^{-3}}{2.625 \times 10^{-3}} = 0.857 \text{ V}$$

$$V_3 = \frac{\begin{vmatrix} 0.15 & -0.1 & 0.1 \\ -0.1 & 0.2 & 0 \\ -0.05 & -0.05 & 0 \end{vmatrix}}{\begin{vmatrix} 0.15 & -0.1 & -0.05 \\ -0.1 & 0.2 & -0.05 \\ -0.05 & -0.05 & 0.2 \end{vmatrix}} = \frac{1.5 \times 10^{-3}}{2.625 \times 10^{-3}} = 0.571 \text{ V}$$

KCL:  
at B

$$0 = 0.1 \text{ A} - \frac{V_2}{20 \Omega} - \frac{V_3}{10 \Omega} \quad [+1]$$

$$= 0.1 \text{ A} - \frac{0.857 \text{ V}}{20 \Omega} - \frac{0.571 \text{ V}}{10 \Omega}$$

$$= 0.1 \text{ A} - 0.04285 \text{ A} - 0.0571 \text{ A} \quad [+1]$$

$$= 0.000 \text{ A}$$

c) Definition of equivalent resistance gives:

$$R_{eq} = \frac{V_1}{0.1 \text{ A}} \quad [+1]$$


$$= \frac{1.429 \text{ V}}{0.1 \text{ A}} = 14.29 \Omega \quad [+1]$$



NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

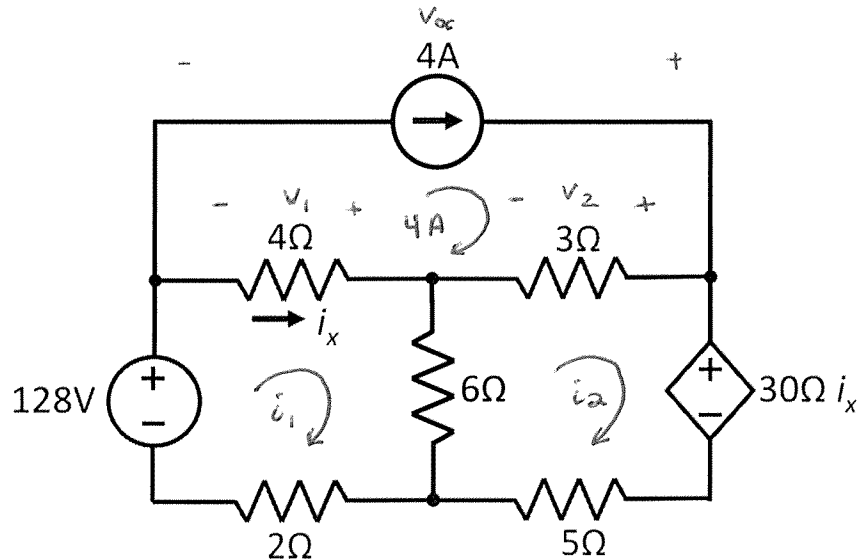1. Consider the circuit diagram. Answer the questions.



a) Which technique, node-voltage analysis or mesh-current analysis, gives a system of equations with fewer variables? [1pt]

b) What is the value of the current  $i_x$ ? [5pts]

c) How much power does the 4A current source deliver or absorb? [2pts] 3pts

d) How much power does the 6Ω resistor absorb? [3pts] 2pts

a) node voltage  $\rightarrow$  3 variables  
 mesh current  $\rightarrow$  2 variables

$$0 = -128 + 4(i_1 - 4) + 6(i_1 - i_2) + 2i_1 \quad [+1]$$

$$0 = 30i_x + 5i_2 + 6(i_2 - i_1) + 3(i_2 - 4) \quad [+1]$$

$$i_x = i_1 - 4A \quad [+1]$$

work space

$$144 = 12i_1 - 6i_2$$

$$132 = 24i_1 + 14i_2$$

$$i_1 = \frac{\begin{vmatrix} 144 & -6 \\ 132 & 14 \end{vmatrix}}{\begin{vmatrix} 12 & -6 \\ 24 & 14 \end{vmatrix}} = 9A \quad [+1]$$

$$i_x = i_1 - 4A$$

$$= 5A \quad [+1]$$

c)

$$V_\alpha = V_1 + V_2$$

$$= 4\Omega(4A - i_1) + 3\Omega(4A - i_2) \quad [+1]$$

$$i_2 = \frac{\begin{vmatrix} 12 & 144 \\ 24 & 132 \end{vmatrix}}{\begin{vmatrix} 12 & -6 \\ 24 & 14 \end{vmatrix}} = -6A \quad [+1]$$

$$P_{del} = 4A \cdot V_\alpha$$

$$= 4A(4\Omega(4A - 9A) + 3\Omega(4A - (-6A)))$$

$$= 40W \quad [+1] \quad \text{delivered by source}$$


d)

$$P_{abs} = 6\Omega \cdot (i_1 - i_2)^2 \quad [+1]$$

$$= 6\Omega(9A - (-6A))^2$$

$$= 1.35 \text{ kW} \quad [+1]$$

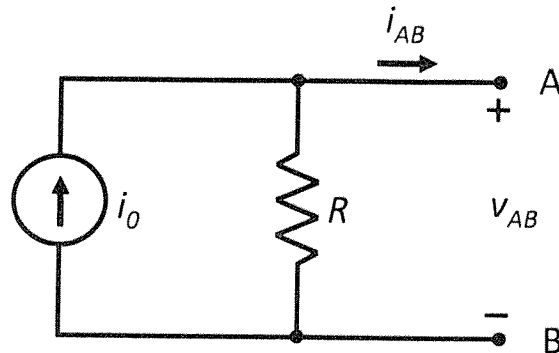
2. Consider the circuit diagram and plot below. If you connect a  $200\text{k}\Omega$  resistor across the terminals A and B, you find that  $v_{AB}=1.24\text{V}$ . If you connect a  $12.5\text{k}\Omega$  resistor across the terminals A and B, you find that  $v_{AB}=0.31\text{V}$ . Answer the questions.



a) Determine the value of  $i_0$  and  $R$ . [4pts]

b) If a resistor with conductance  $G_L = 0\text{ S}$  is connected across the terminals A and B, what is the resulting voltage  $v_{AB}$ ? [2pts]

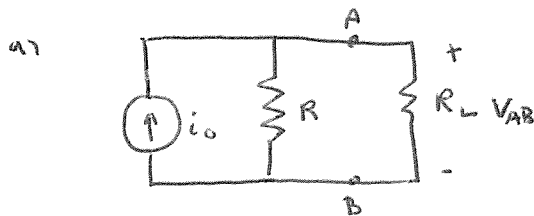c) What resistance should you connect across the terminals A and B in order to give  $v_{AB} = 1.00\text{V}$ ? [2pts]



$$1.24\text{V} = i_0 \cdot R // 200\text{k}\Omega \quad [+1]$$

$$0.31\text{V} = i_0 \cdot R // 12.5\text{k}\Omega \quad [+1]$$

$$1.24\text{V} = i_0 \frac{R \cdot 200\text{k}\Omega}{R + 200\text{k}\Omega}$$

$$0.31\text{V} = i_0 \frac{R \cdot 12.5\text{k}\Omega}{R + 12.5\text{k}\Omega}$$

$$i_0 = 1.24\text{V} \left( \frac{1}{R} + \frac{1}{200\text{k}\Omega} \right)$$

$$i_0 = 0.31\text{V} \left( \frac{1}{R} + \frac{1}{12.5\text{k}\Omega} \right)$$

$$\therefore 1.24\text{V} \left( \frac{1}{R} + \frac{1}{200\text{k}\Omega} \right) = 0.31\text{V} \left( \frac{1}{R} + \frac{1}{12.5\text{k}\Omega} \right)$$


$$\frac{1}{R} = \frac{\frac{0.31}{1.24} \left( \frac{1}{12.5\text{k}\Omega} \right) - \frac{1}{200\text{k}\Omega}}{\left( 1 - \frac{0.31}{1.24} \right)} = 20\text{ }\mu\text{S}$$

$$R = 50 \text{ k}\Omega \quad [+1]$$

$$i_o = 1.24 \text{ V} \left( \frac{1}{50 \text{ k}\Omega} + \frac{1}{200 \text{ k}\Omega} \right)$$

$$= 31 \mu\text{A} \quad [+1]$$

b)

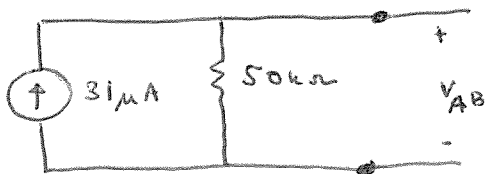

$G_L = 0 \text{ S}$  is equivalent to an open,

$$R_L = 1/G_L \rightarrow \infty$$

$$V_{AB} = i_o R \quad [+1]$$

$$= 31 \mu\text{A} \cdot 50 \text{ k}\Omega$$

$$= 1.55 \text{ V} \quad [+1]$$

c)

$$1.00 \text{ V} = i_o \cdot R // R_L \quad [+1]$$

$$R // R_L = \frac{1.00 \text{ V}}{31 \mu\text{A}} = 32.26 \text{ k}\Omega$$

$$\frac{1}{50 \text{ k}\Omega} + \frac{1}{R_L} = \frac{1}{32.26 \text{ k}\Omega}$$


$$R_L = \frac{1}{\frac{1}{32.26 \text{ k}\Omega} - \frac{1}{50 \text{ k}\Omega}}$$

$$R_L = 90.91 \text{ k}\Omega \quad [+1]$$


NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

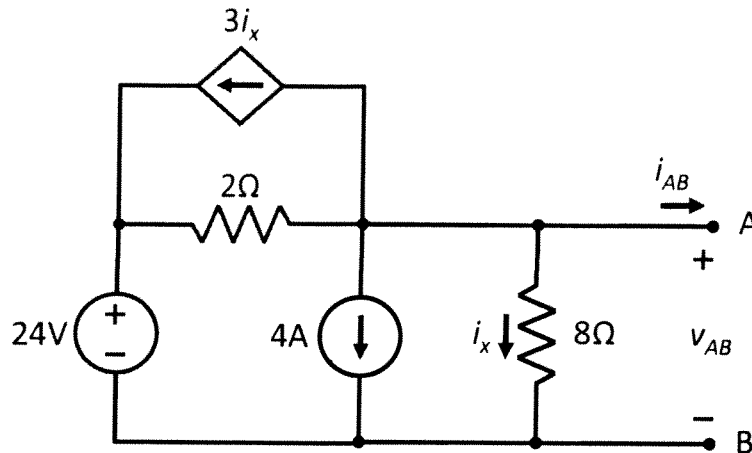1. Consider the circuit diagram. Answer the questions.



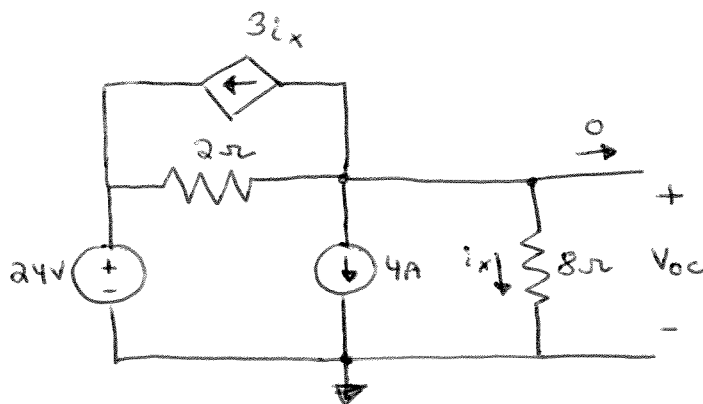- a) What is the Thévenin equivalent of the above circuit with respect to the terminals A and B? [8pts]  
 b) What is the current  $i_{AB}$  if a  $3\Omega$  resistor is connected across the terminals A and B? [2pts]



Use node-voltage method:


$$0 = 3i_x + \frac{V_{OC} - 24V}{2\Omega} + 4A + \frac{V_{OC}}{8\Omega} \quad [1]$$

$$i_x = \frac{V_{OC}}{8\Omega} \quad [1]$$

$$0 = \frac{3V_{OC}}{8\Omega} + \frac{V_{OC} - 24V}{2\Omega} + 4A + \frac{V_{OC}}{8\Omega}$$

$$V_{OC} = \frac{12A - 4A}{\frac{3}{8\Omega} + \frac{1}{2\Omega} + \frac{1}{8\Omega}} = 8V$$

work space

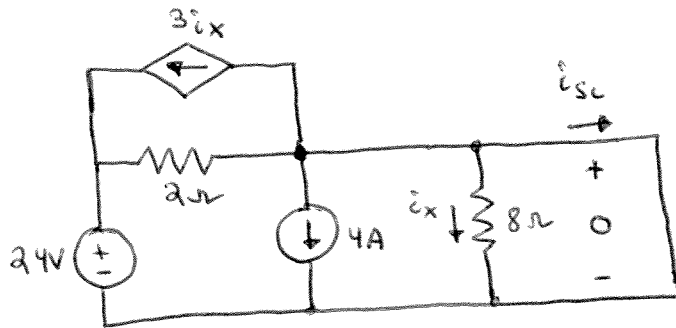

Ohm:

$$i_x = \frac{0V}{8\Omega} = 0A \quad [+1]$$



KCL:

$$\frac{0 - 24V}{2\Omega} + 4A + i_{sc} = 0 \quad [+1]$$

$$i_{sc} = 12A - 4A = 8A \quad [+1]$$

$$R_T = \frac{V_{oc}}{i_{sc}} \quad [+1]$$

$$= \frac{8V}{8A} = 1\Omega$$

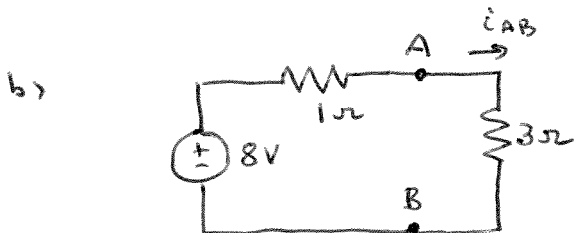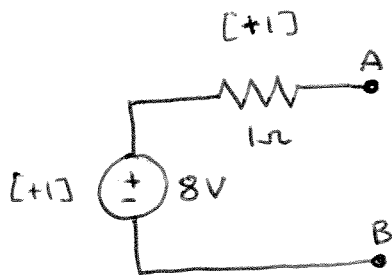


$$i_{AB} = \frac{V_{oc}}{R_T + R} \quad [+1]$$

$$= \frac{8V}{1\Omega + 3\Omega}$$

$$= 2A \quad [+1]$$

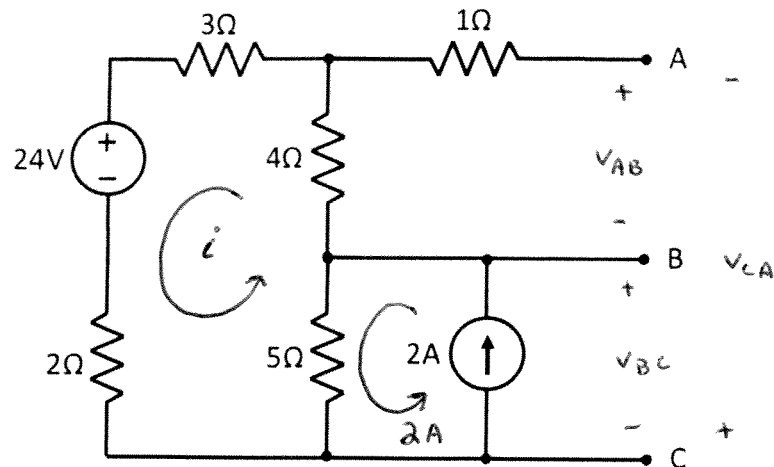2. Consider the circuit below. Answer the questions.




- What is the Thévenin equivalent of the circuit with respect to the terminals A and B. [4pts]
- What is the Thévenin equivalent of the circuit with respect to the terminals B and C. [3pts]
- What is the Thévenin equivalent of the circuit with respect to the terminals C and A. [3pts]

a) Using mesh current with all terminals open:

$$0 = 4\Omega \cdot i + 3\Omega \cdot i + 24V + 2\Omega \cdot i + 5\Omega \cdot (i - 2A) \quad [+1]$$


$$i = \frac{-24V + 10V}{4\Omega + 3\Omega + 2\Omega + 5\Omega} = -1A$$
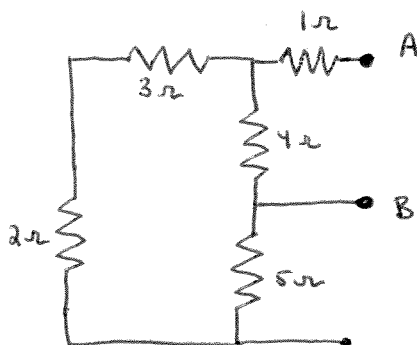
$$V_{AB} = -i \cdot 4\Omega + 0A \cdot 1\Omega = 4V \quad [+1]$$



$$R_T = 1\Omega + 4\Omega // (3\Omega + 2\Omega + 5\Omega) \quad [+1]$$


$$= 3.857\Omega$$

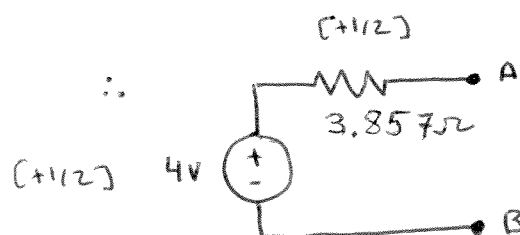


work space

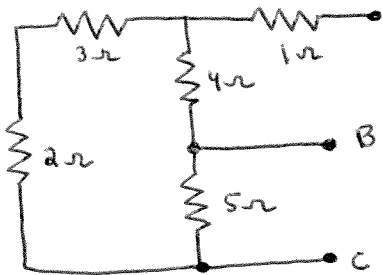b) From analysis with open terminals:

$$V_{BC} = 5\Omega (2A - i) = 15V \text{ [+1]}$$



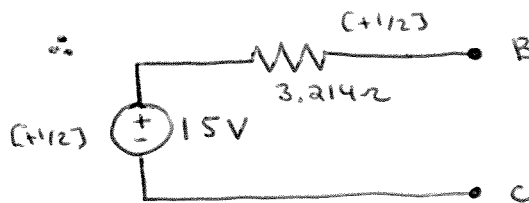
$$R_T = 5\Omega // (4\Omega + 3\Omega + 2\Omega) \text{ [1]}$$
$$= 3.214\Omega$$





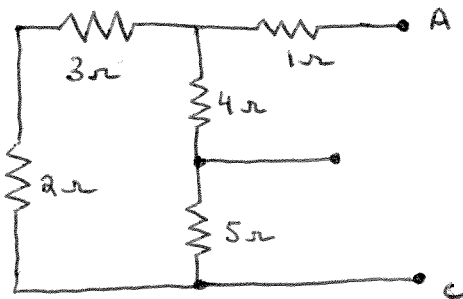c) From analysis with open terminals:

$$V_{CA} = -V_{AB} - V_{BC}$$
$$= -19V \text{ [1]}$$


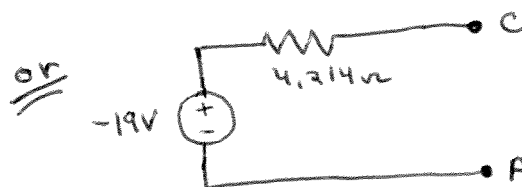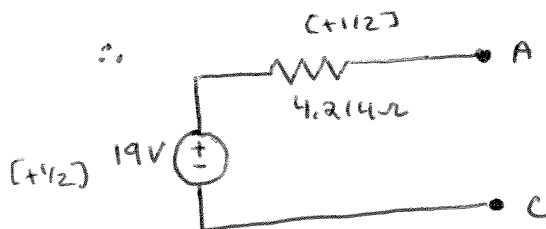
$$R_T = 1\Omega + (3\Omega + 2\Omega) // (4\Omega + 5\Omega) \text{ [1]}$$
$$= 4.214\Omega$$




Take note of polarity of source and terminal labels.




NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

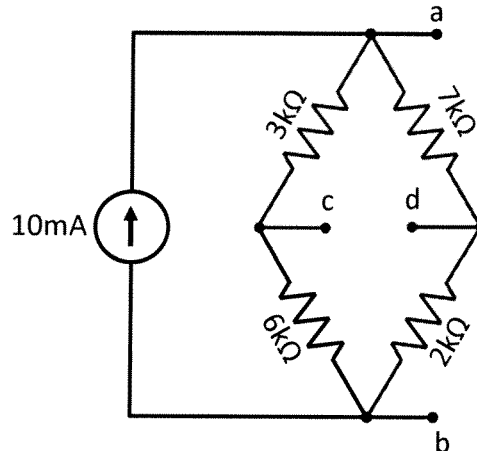1. Consider the circuit diagram. Answer the questions.



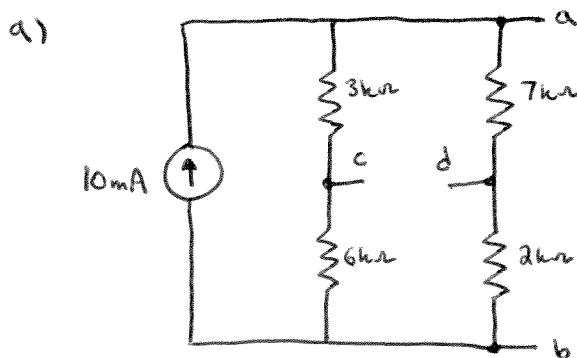- a) What is the maximum power that the network above can deliver to a load resistor connected to the terminals a and b? [3pts]
- b) What is the maximum power that the network above can deliver to a load resistor connected to the terminals c and d? [4pts]
- c) What is the maximum power that the network above can deliver to a load resistor connected to the terminals c and b? [3pts]



$$V_{oc,ab} = 10\text{mA} \cdot (3\text{k}\Omega + 6\text{k}\Omega) \parallel (7\text{k}\Omega + 2\text{k}\Omega) \quad [+1/2]$$


$$= 45\text{V}$$

$$I_{sc,ab} = 10\text{mA} \quad [+1/2]$$

$$P_{max,ab} = \frac{V_{oc,ab}}{2} \cdot \frac{I_{sc,ab}}{2} \quad [+1]$$

$$= \frac{45\text{V}}{2} \cdot \frac{10\text{mA}}{2}$$

$$= 112.5\text{mW} \quad [+1]$$

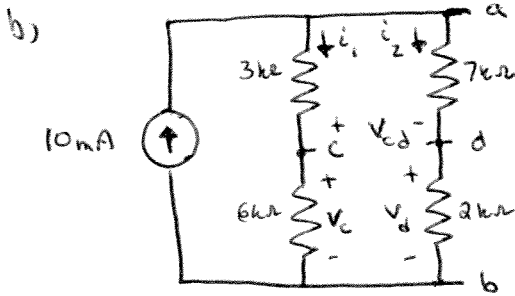

$$P_{max,cd} = \frac{V_{oc,cd}}{2} \cdot \frac{i_{sc,cd}}{2}$$

$$= \frac{V_{oc,cd}^2}{4 R_{T,cd}}$$

$$= 23.61 \text{ mW} \quad [+1]$$

work space

$$\left. \begin{aligned} i_1 &= 10 \text{ mA} \cdot \frac{9 \text{ k}\Omega}{18 \text{ k}\Omega} = 5 \text{ mA} \\ i_2 &= 10 \text{ mA} \cdot \frac{9 \text{ k}\Omega}{18 \text{ k}\Omega} = 5 \text{ mA} \end{aligned} \right\} [+1]$$

$$V_c = 6 \text{ k}\Omega \cdot i_1$$

$$= 6 \text{ k}\Omega \cdot 5 \text{ mA} = 30 \text{ V}$$

$$V_d = 2 \text{ k}\Omega \cdot i_2$$


$$= 2 \text{ k}\Omega \cdot 5 \text{ mA} = 10 \text{ V}$$

$$V_{cd} = V_c - V_d = 20 \text{ V} \quad [+1]$$

$$R_T = (6 \text{ k}\Omega + 2 \text{ k}\Omega) // (3 \text{ k}\Omega + 7 \text{ k}\Omega) \quad [+1]$$

$$= 4.235 \text{ k}\Omega$$

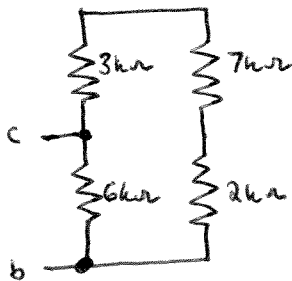c)  $V_{oc,cb} = V_c = 30 \text{ V} \quad [+1]$



$$R_{T,cb} = 6 \text{ k}\Omega // (3 \text{ k}\Omega + 7 \text{ k}\Omega + 2 \text{ k}\Omega) \quad [+1]$$


$$= 4 \text{ k}\Omega$$

$$P_{max,cb} = \frac{V_{oc,cb}}{2} \cdot \frac{i_{sc,cb}}{2}$$

$$= \frac{V_{oc,cb}^2}{4 R_{T,cb}}$$

$$= 56.25 \text{ mW} \quad [+1]$$

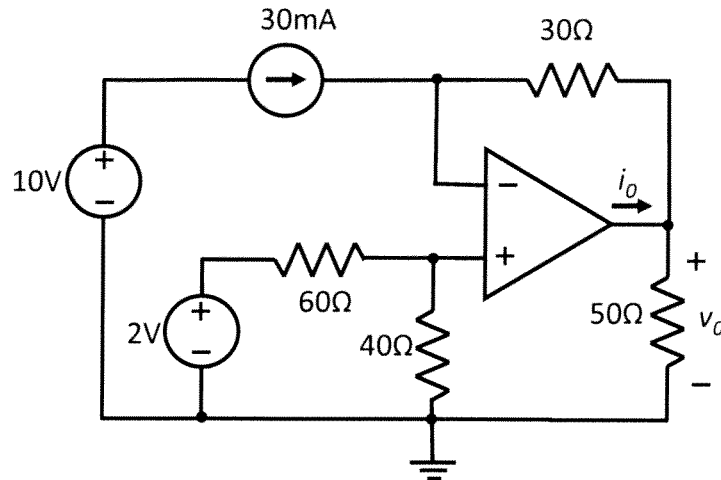
2. Consider the circuit below. Assume ideal op-amp behaviour. Answer the questions.



a) What is the voltage  $v_o$ ? [4pts]

b) How much power does the 30mA current source deliver or absorb? [3pts]

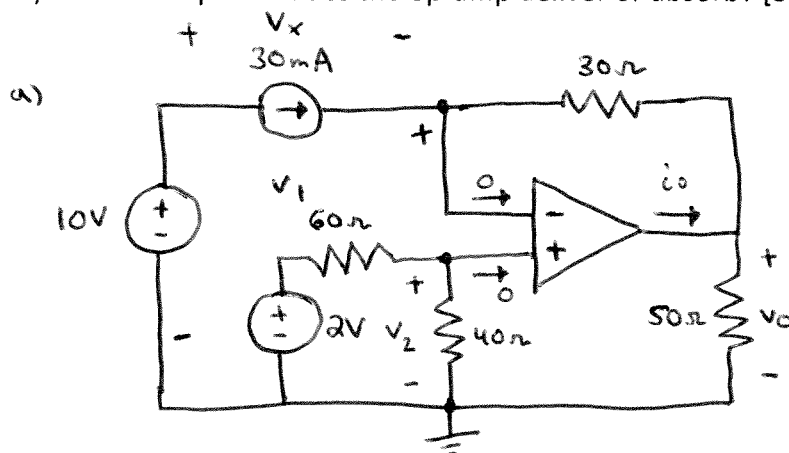c) How much power does the op-amp deliver or absorb? [3pts]



ideal op-amp:

input currents = 0

virtual short  $\rightarrow v_2 = v_1$  [1]

$$v_2 = \frac{40\Omega}{40\Omega + 60\Omega} \cdot 2V \quad [1]$$

$$= 0.8V$$

node voltage equation at inverting input:  $0 = -30mA + \frac{0.8V - v_o}{30\Omega} \quad [1]$

$$v_o = 0.8V - 30mA \cdot 30\Omega$$

$$= -0.1V \quad [1]$$

$$b) \quad KVL: \quad 0 = -10V + v_x + 0.8V \quad (+1)$$

$$v_x = 9.2V$$

$$P_{abs} = 30mA \cdot v_x \quad (+1)$$

$$= 276mW \quad \text{is absorbed by the current source. } (+1)$$

$$c) \quad KCL: \quad 0 = -i_o + \frac{V_o}{50\Omega} + \frac{V_o - V_1}{30\Omega} \quad (+1)$$

$$= -i_o + \frac{(-0.1V)}{50\Omega} + \frac{(-0.1V - 0.8V)}{30\Omega}$$

$$i_o = -32mA$$

$$P_{del} = i_o \cdot V_o \quad (+1)$$


$$= (-32mA) \cdot (-0.1V)$$

$$= 3.2mW \quad \text{is delivered by the op-amp. } (+1)$$

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

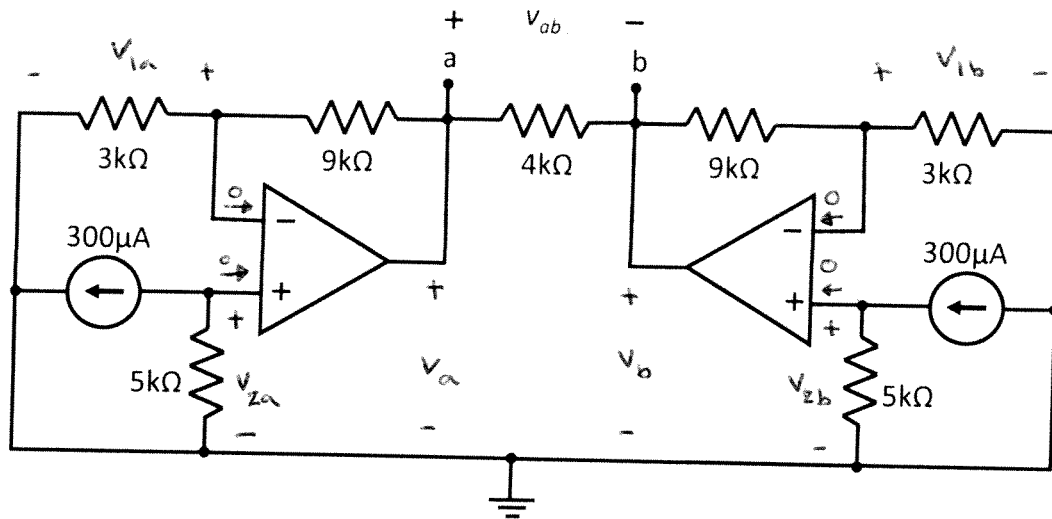1. Consider the circuit diagram. Assume ideal op-amp behaviour. Answer the questions.



- What is the voltage  $v_{ab}$ ? [6pts]
- How much power does the  $4k\Omega$  resistor absorb? [2pts]
- Would your answer to part a) change if a  $5k\Omega$  resistor was connected between the non-inverting input terminals of the two op-amps? [2pts]

$$a) \quad v_{za} = -300\mu A \cdot 5k\Omega = -1.5V \quad [+1]$$

$$v_{1a} = v_{za} \quad [+1/2]$$

$$0 = \frac{-1.5V}{3k\Omega} + \frac{(-1.5V - v_a)}{9k\Omega} \quad [+1]$$

$$v_a = \frac{9k\Omega}{3k\Omega} (-1.5V) + (-1.5V) = -6V$$

$$v_{zb} = +300\mu A \cdot 5k\Omega = +1.5V \quad [+1]$$

work space

$$V_{1b} = V_{2b} \quad [+1/2]$$


$$0 = \frac{1.5V}{3k\Omega} + \frac{(1.5V - V_b)}{9k\Omega} \quad [+1]$$

$$V_b = \frac{9k\Omega}{3k\Omega} (+1.5V) + (1.5V) = +6V$$

$$\begin{aligned} V_{ab} &= V_a - V_b \\ &= -12V \quad [+1] \end{aligned}$$

$$\begin{aligned} b) \quad P_{abs} &= \frac{V_{ab}^2}{4k\Omega} = \frac{(-12V)^2}{4k\Omega} = 36mW \\ &\quad [+1] \end{aligned}$$

c)

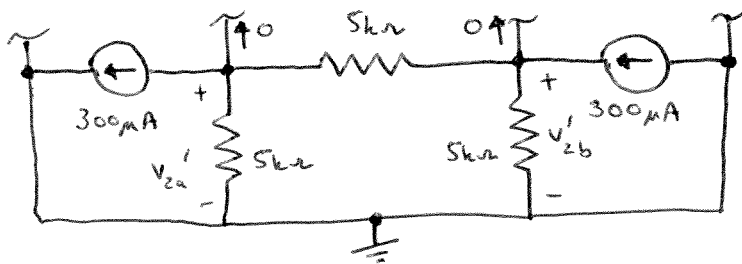

$$0 = 300\mu A + \frac{V'_{2a}}{5k\Omega} + \frac{V'_{2a} - V'_{2b}}{5k\Omega}$$


$$0 = -300\mu A + \frac{V'_{2b}}{5k\Omega} + \frac{V'_{2b} - V'_{2a}}{5k\Omega}$$

$$\begin{aligned} \therefore V'_{2a} &\neq V_{2a} = -1.5V \\ V'_{2b} &\neq V_{2b} = +1.5V \end{aligned} \quad [+1]$$

$\therefore V_a$  and  $V_b$  will be different, as will  $V_{ab}$ .

The answer to part a) will be different. [+1]

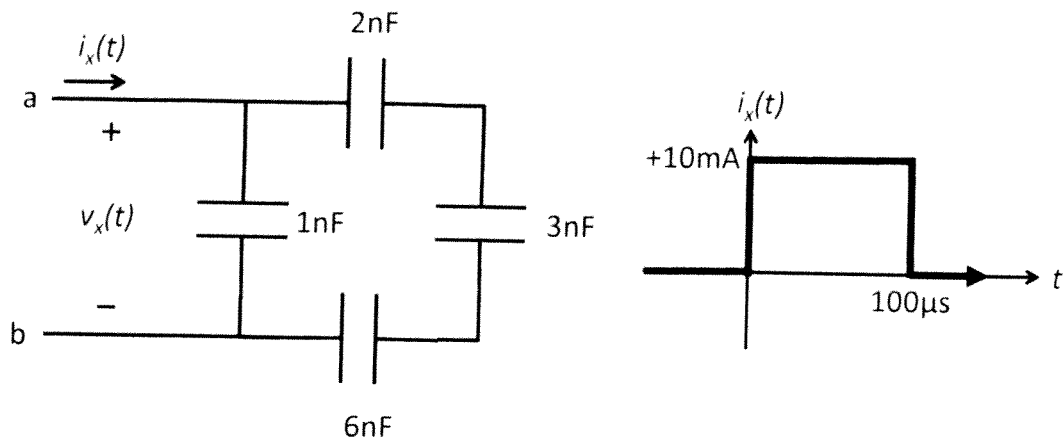2. Consider the circuit and plot below. There is zero charge separation on the capacitors for  $t < 0$ . Answer the questions.



- What is the equivalent capacitance between nodes a and b? [2 pts]
- Plot the voltage  $v_x(t)$  versus  $t$ . [3pts]
- What is the energy stored on the capacitors at time  $t = 200\mu s$ ? [2pts]
- What is the maximum instantaneous power absorbed by the capacitors? [3pts]

$$a) \quad C_{eq} = 1nF + \frac{1}{\frac{1}{2nF} + \frac{1}{3nF} + \frac{1}{6nF}} \quad [+1]$$


$$= 2nF \quad [+1]$$

$$b) \quad i_x(t) = C_{eq} \frac{dv_x(t)}{dt} \quad \therefore \quad v_x(t) = v_x(0) + \frac{1}{C_{eq}} \int_0^t i_x(t') dt'$$

$$v_x(0) = 0 \quad \text{since } q_x(0) = 0$$

$$v_x(100\mu s) = \frac{1}{2nF} \cdot 10mA \cdot 100\mu s$$

$$= 500V$$

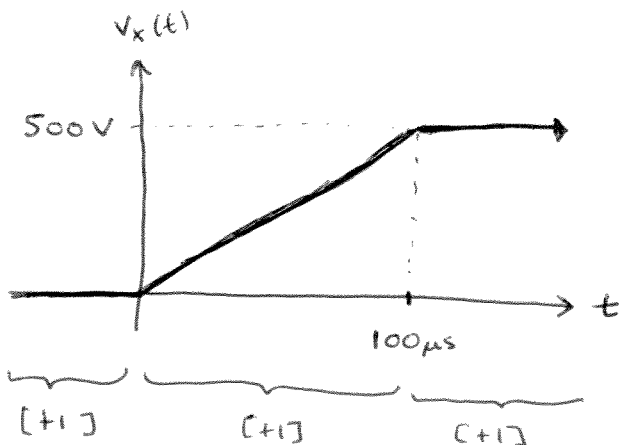

work space

$$\begin{aligned} c) \quad U &= \frac{1}{2} C_{eq} v_x^2 \quad [+1] \\ &= \frac{1}{2} \cdot 2nF \cdot (500V)^2 \\ &= 250 \mu J \quad [+1] \end{aligned}$$

d) Maximum power absorption occurs at time of maximum  $i_x \cdot v_x$ , at the instant before  $t=100\mu s$ . [+2]


$$\begin{aligned} P_{\max_{abs}} &= i_x (100\mu s - \Delta t) \cdot v_x (100\mu s - \Delta t) \quad \text{as } \Delta t \rightarrow 0 \\ &= 10mA \cdot 500V \\ &= 5W \quad [+1] \end{aligned}$$



NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

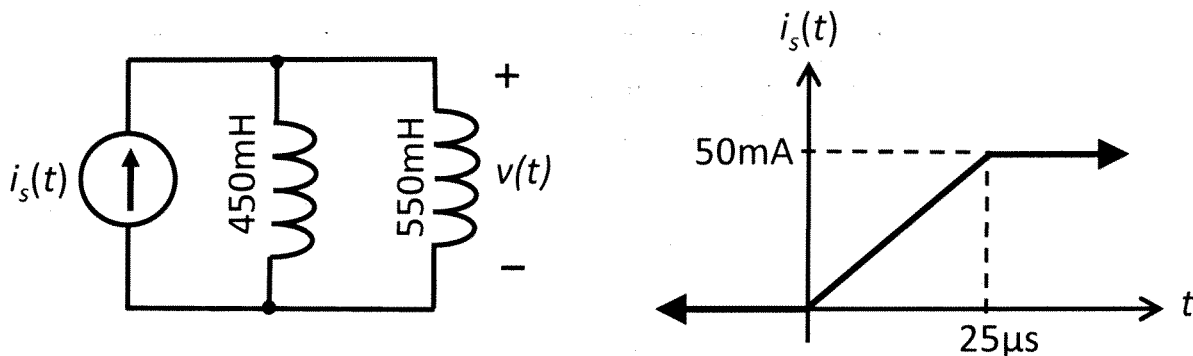1. Consider the circuit diagram and the plot. Assume there is zero stored flux linkage in the inductors for  $t < 0$ . Answer the questions.



- Plot the voltage  $v(t)$ . [5pts]
- How much energy does the current source deliver to the inductors? [2pts]
- What is the current in the  $550\text{mH}$  inductor at  $t = 50\mu\text{s}$ ? [3pts]


HINT: Consider your answer to part a).

$$a) \quad L_{eq} = \left( \frac{1}{450\text{mH}} + \frac{1}{550\text{mH}} \right)^{-1} = 247.5\text{mH} \quad [+1]$$

$$V = L_{eq} \frac{di_s}{dt} \quad [+1]$$

$$0 < t < 25\mu\text{s}$$

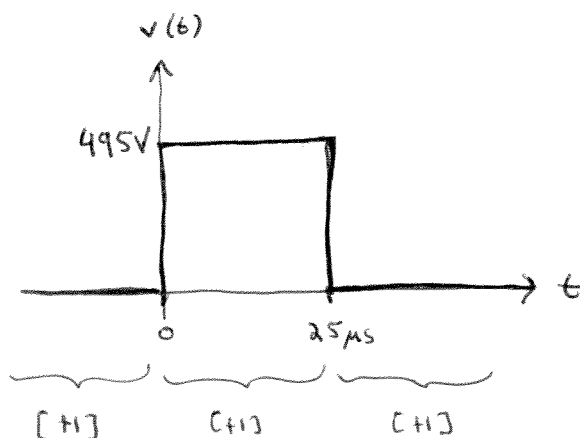
$$V = 247.5\text{mH} \cdot \frac{50\text{mA}}{25\mu\text{s}} = 495\text{V}$$



work space

$$\begin{aligned} b) \quad U &= \frac{1}{2} L_{eq} i_s^2 \quad [+1] \\ &= \frac{1}{2} \cdot 247.5 \text{ mH} \cdot (50 \text{ mA})^2 \\ &= 309.4 \text{ } \mu\text{J} \quad [+1] \end{aligned}$$

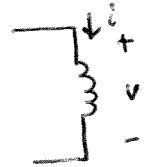
$$c) \quad v = L \frac{di}{dt} \rightarrow i(t) - i(0) = \frac{1}{L} \int_0^t v(t') dt' \quad [+1]$$



$$i(50 \mu\text{s}) - 0 \text{ mA} = \frac{1}{550 \text{ mH}} \cdot 495 \text{ V} \cdot 25 \mu\text{s} \quad [+1]$$

$$i(50 \mu\text{s}) = 22.5 \text{ mA} \quad [+1]$$

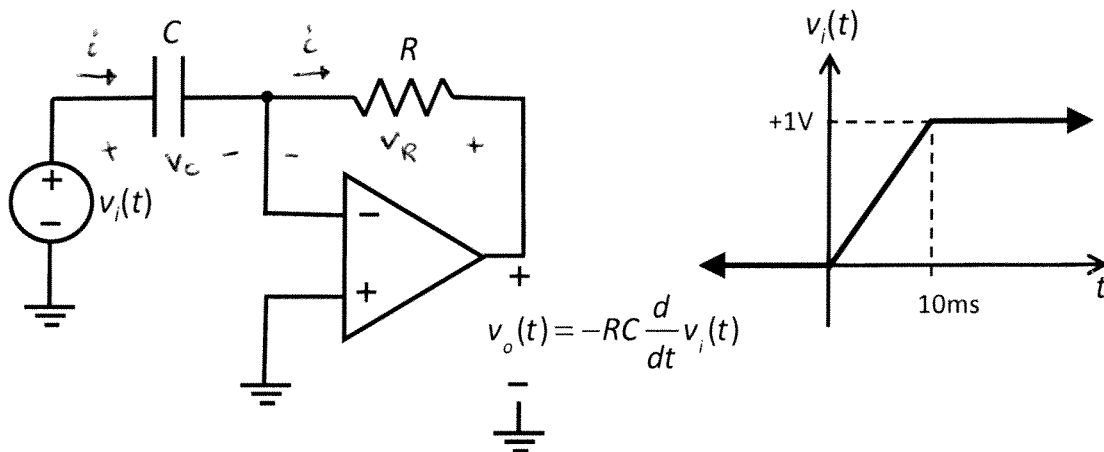2. Consider the circuit and the plot below. Assume that there is zero charge separation on the capacitor for  $t < 0$ . Assume ideal op-amp behavior. Answer the questions.



a) Find the value of  $C$  such that a current of 7mA flows through the independent voltage source  $v_i(t)$  during the time  $0 < t < 10\text{ms}$ ? [3pts]

For the remainder of this question, assume  $C$  is equal to the value that you found in a).

b) How much energy does the capacitor  $C$  store at  $t = 20\text{ms}$ ? [2pts]

c) Find the value of  $R$  such that  $v_o(t) = -3.5\text{V}$  during the time  $0 < t < 10\text{ms}$ ? [2pts]

For the remainder of this question, assume  $R$  is equal to the value that you found in c).

d) What energy does the resistor absorb over the time interval  $0 < t < 10\text{ms}$ ? [3pts]

$$a) \quad i = C \frac{dv_i}{dt} \quad [+1]$$

$$C = \frac{i}{dv_i/dt} = \frac{7\text{mA}}{1\text{V}/10\text{ms}} \quad [+1]$$

$$= 70 \mu\text{F} \quad [+1]$$

$$b) \quad U = \frac{1}{2} C v_i^2 \quad [+1]$$

$$= \frac{1}{2} \cdot 70 \mu\text{F} \cdot 1\text{V}$$

$$= 35 \mu\text{J} \quad [+1]$$

$$c) \quad V_o(t) = -V_R(t) = -i \cdot R \quad [+1]$$

$$R = \frac{-V_o}{i}$$

$$= \frac{-(-3.5V)}{7mA}$$

$$= 500\Omega \quad [+1]$$

$$d) \quad P = i^2 R \quad [+1]$$

$$= (7mA)^2 \cdot 500\Omega$$

$$= 24.5mW$$

$$U = \int P dt' = P \cdot \Delta t \quad [+1]$$


$$= 24.5mW \cdot 10ms$$

$$= 245\mu J \quad [+1]$$

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_


READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

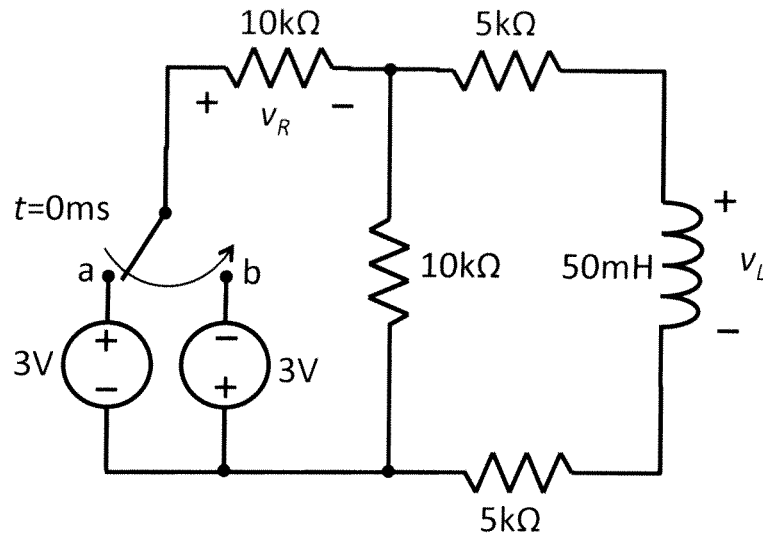1. Consider the circuit diagram. Assume dc steady state for  $t < 0$ . Answer the questions.



a) Find the voltage  $v_L(t)$  for  $t > 0$ . Plot  $v_L(t)$  versus  $t$ , including the dc steady state value for  $t < 0$ . [5pts]

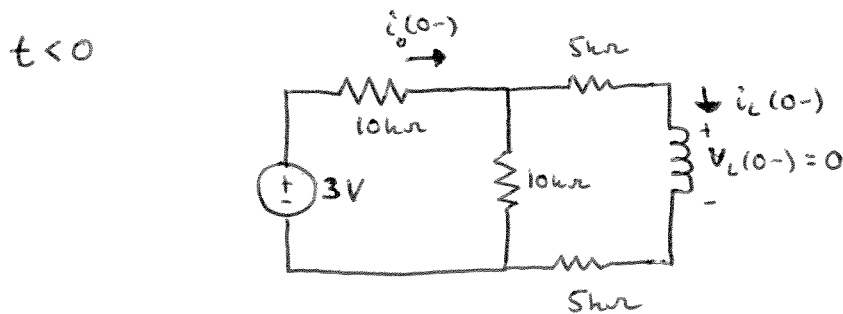b) Find the voltage  $v_R(t)$  for  $t > 0$ . Plot  $v_R(t)$  versus  $t$ , including the dc steady state value for  $t < 0$ . [5pts]



$$i_0(0-) = \frac{3V}{10k\Omega + 10k\Omega \parallel (5k\Omega + 5k\Omega)}$$

$$= 200\mu A$$


$$i_L(0-) = \frac{10k\Omega}{10k\Omega + 10k\Omega} \cdot 200\mu A$$

$$= 100\mu A$$

inductor current is continuous, thus:

$$i_L(0+) = i_L(0-) = 100\mu A \quad [1]$$

$t = 0^+$

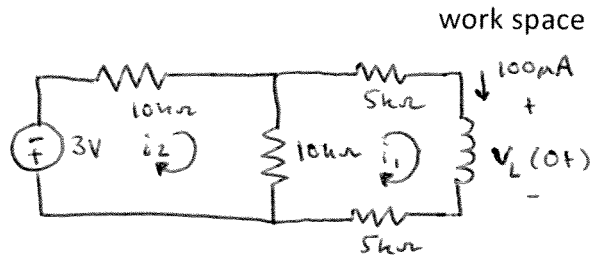

use mesh currents:  $i_1 = 100\mu A$

$$0 = 3V + i_2 \cdot 10k\Omega + (i_2 - 100\mu A) \cdot 10k\Omega$$


$$i_2 = \frac{-3V + 100\mu A \cdot 10k\Omega}{20k\Omega}$$

$$= -100\mu A$$

$$V_R(0^+) = 10k\Omega \cdot i_2 = -1V \text{ [ + ]}$$

$$V_L(0^+) = -5k\Omega \cdot i_1 - 10k\Omega (i_1 - i_2) - 5k\Omega \cdot i_1 = -3V \text{ [ + ]}$$

$t \rightarrow \infty$

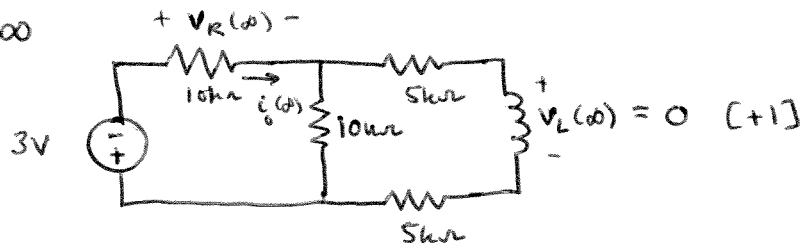

$$i_0(\infty) = \frac{-3V}{10k\Omega + 10k\Omega \parallel (5k\Omega + 5k\Omega)}$$

$$= -200\mu A$$

$$V_R(\infty) = i_0(\infty) \cdot 10k\Omega$$

$$= -2V \text{ [ + ]}$$

$$R_{TH} = 5k\Omega + 10k\Omega \parallel 10k\Omega + 5k\Omega \text{ [ + ]}$$

$$= 15k\Omega$$



$$\tau = \frac{L}{R_{TH}}$$

$$= 3.33ms \text{ [ + ]}$$


$$x(t) = x(\infty) + [x(0^+) - x(\infty)] \exp(-t/\tau)$$

$$V_L(t) = -3V \exp(-t/3.33ms) \text{ [ + ]}$$
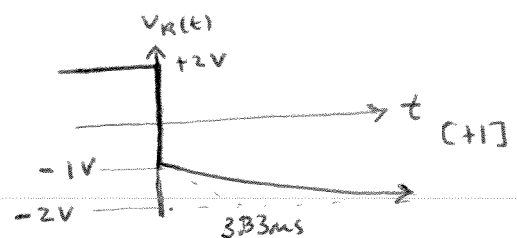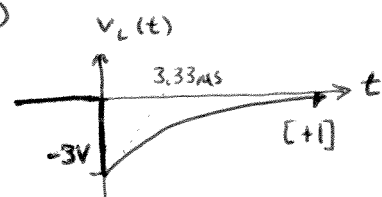
$$V_R(t) = -2V + 1V \exp(-t/3.33ms) \text{ [ + ]}$$




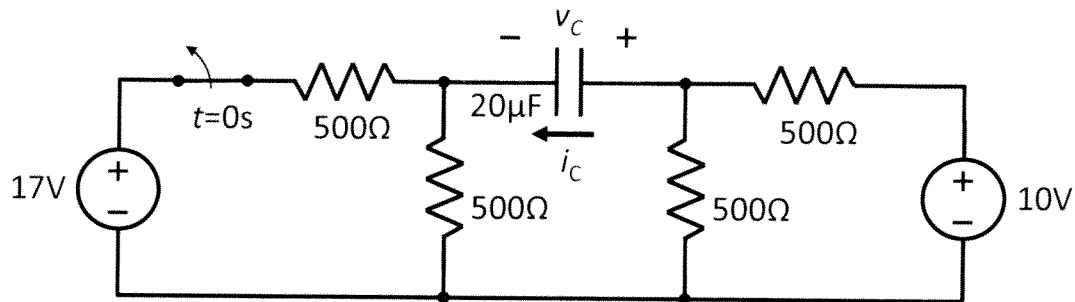2. Consider the circuit below. Assume dc steady state for  $t < 0$ . Answer the questions.




a) Find the voltage  $v_c(t)$  for  $t > 0$ . Plot  $v_c(t)$  versus  $t$ , including the dc steady state value for  $t < 0$ . [5pts]

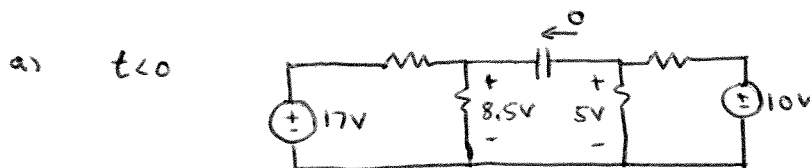b) What is the power delivered by the 10V source at  $t = 0+$ ? [5pts]



$$v_c(0^-) = 5V - 8.5V = -3.5V$$
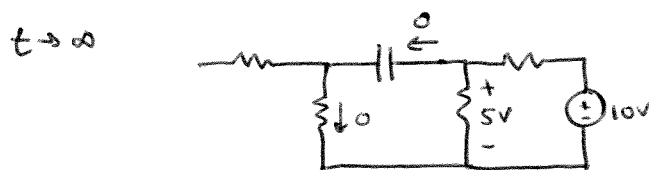
$$v_c(0^+) = v_c(0^-) = -3.5V \quad [+1]$$




$$v_c(\infty) = 5V \quad [+1]$$

$$\begin{aligned} R_{TH} &= 500\Omega // 500\Omega + 500\Omega \\ &= 250\Omega + 500\Omega \\ &= 750\Omega \quad [+1] \end{aligned}$$


$$\tau = R_{TH} \cdot C = 750\Omega \cdot 20\mu F = 15ms \quad [+1]$$
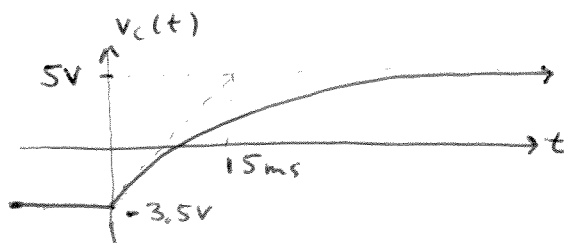
$$\begin{aligned} v_c(t) &= v_c(\infty) + [v_c(0^+) - v_c(\infty)] \exp(-t/\tau) \\ &= 5V - 8.5V \exp(-t/15ms) \quad [+1/2] \end{aligned}$$



work space

b)  $t = 0^+$

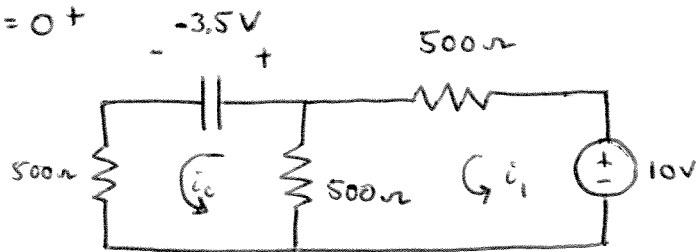

[+1] for circuit diagram

$$i_c(0^+) = C \left. \frac{dv_c}{dt} \right|_{0^+} = 20 \mu\text{F} \cdot \frac{-8.5\text{V}}{-15\text{ms}} \quad [+1]$$

$$= 11.33 \text{ mA}$$

$$\text{KVL: } 0 = -10\text{V} + 500\Omega \cdot i_1 + 500\Omega \cdot (i_1 - i_c) \quad [+1]$$

$$i_1 = \frac{10\text{V} + 500\Omega \cdot 11.33 \text{ mA}}{500\Omega + 500\Omega}$$

$$= 15.67 \text{ mA} \quad [+1]$$

$$P_{\text{del}} = 10\text{V} \cdot i_1$$


$$= 156.7 \text{ mW} \quad [+1]$$



NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

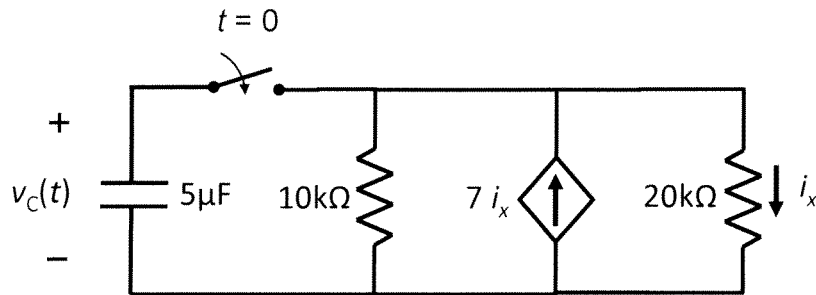1. Consider the circuit diagram. Assume dc steady state for  $t < 0$ , where  $v_C(t) = 1V$  for  $t < 0$ . Answer the questions.



- What is the Thévenin equivalent circuit that the capacitor is connected to at  $t = 0$ ? [3pts]
- What is the voltage  $v_C(t)$  for  $t > 0$ ? Plot  $v_C(t)$  versus  $t$ . [5pts]
- The capacitor is rated to a maximum voltage of 150V. At what time  $t$  will the capacitor voltage exceed its rated value? [2pts]

BONUS: The dependent current source  $7 i_x$  is replaced by a dependent current source  $A i_x$ . What is the range of  $A$  values that results in **stable** circuit response? [2pts]

a)

Apply test source since  $v_{oc} = 0$ . [1]

$$i = \frac{1V}{10k\Omega} + \frac{1V}{20k\Omega} - 7 \cdot \left( \frac{1V}{20k\Omega} \right)$$

$$= -0.2mA$$

$$R_T = \frac{1V}{i} = -5k\Omega$$


[1]

[1]

work space


$$\begin{aligned}
 b) \quad v_c(0+) &= v_c(0-) = 1V \quad [1] \\
 v_c(\infty) &= 0V \quad [1] \\
 \tau &= R_{TH} \cdot C \\
 &= 5k\Omega \cdot 5\mu F \quad [1] \\
 &= 25ms
 \end{aligned}$$
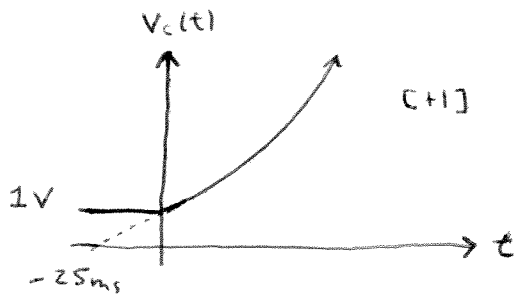
$$\begin{aligned}
 v_c(t) &= v_c(\infty) + [v_c(0+) - v_c(\infty)] \exp(-t/\tau) \\
 &= 1V \exp(t/25ms) \quad [1]
 \end{aligned}$$



$$\begin{aligned}
 c) \quad 150V &= 1V \exp(t/25ms) \quad [1] \\
 t &= 25ms \cdot \ln(150) \\
 &= 125,3 \text{ ms} \quad [1]
 \end{aligned}$$

BONUS

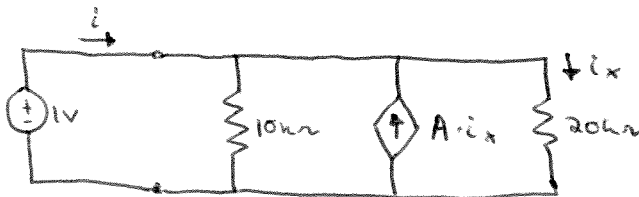



$$\begin{aligned}
 \text{stable response} &\rightarrow \tau > 0 \\
 &\rightarrow R_{TH} > 0 \quad [1] \\
 &\rightarrow i > 0
 \end{aligned}$$

$$i = \frac{1V}{10k\Omega} + \frac{1V}{20k\Omega} - A \cdot \frac{1V}{20k\Omega} > 0$$

$$A < \frac{\frac{1}{10k\Omega} + \frac{1}{20k\Omega}}{\frac{1}{20k\Omega}}$$

$$A < 3 \quad [1]$$

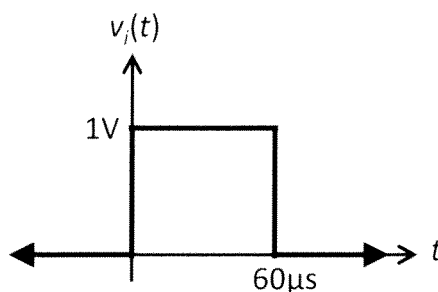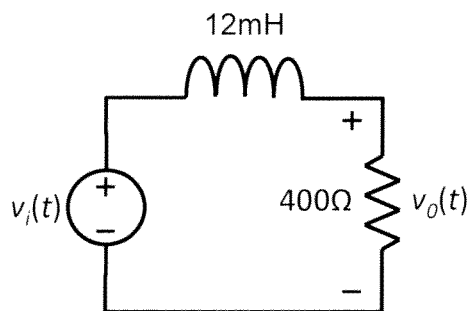2. Consider the circuit below. Assume dc steady state for  $t < 0$ . Answer the questions.



a) Find the voltage  $v_o(t)$  for  $0 < t < 60\mu\text{s}$ . [5pts]

b) Find the voltage  $v_o(t)$  for  $60\mu\text{s} < t$ . [4pts]

c) Plot  $v_o(t)$  versus  $t$ , including the dc steady state value for  $t < 0$ . [1pt]

BONUS: What is the maximum energy that is stored in the inductor? [2pts]

$$a) \quad i_L(0^+) = i_L(0^-) = 0\text{A} \quad [+1]$$

$$v_o(0^+) = i_L(0^+) \cdot 400\Omega = 0\text{V} \quad [+1]$$

$$v_o(\infty) = 1\text{V} \quad [+1]$$

$$\tau = \frac{L}{R_{TH}} = \frac{12\text{mH}}{400\Omega}$$

$$= 30\mu\text{s} \quad [+1]$$

$$v_o(t) = v_o(\infty) + [v_o(0^+) - v_o(\infty)] \exp(-t/\tau)$$

$$= 1\text{V} - 1\text{V} \exp(-t/30\mu\text{s}) \quad [+1]$$

$$b) \quad i_L(60\mu\text{s}^+) = i_L(60\mu\text{s}^-) = \frac{v_o(60\mu\text{s}^-)}{400\Omega} = \frac{1\text{V} - 1\text{V} \exp(-60\mu\text{s}/30\mu\text{s})}{400\Omega} \quad [+1]$$

$$= \frac{0.865\text{V}}{400\Omega}$$

$$v_o(60\mu\text{s}^+) = i_L(60\mu\text{s}^+) \cdot 400\Omega = 0.865\text{V} \quad [+1]$$

$$v_o(\infty) = 0\text{V} \quad [+1]$$


$\tau$  is unchanged

$$v_o(t) = v_o(\infty) + [v_o(60\mu\text{s}^+) - v_o(\infty)] \exp(-(t - 60\mu\text{s})/30\mu\text{s})$$

$$= 0.865\text{V} \exp(-(t - 60\mu\text{s})/30\mu\text{s}) \quad [+1]$$

work space

c)

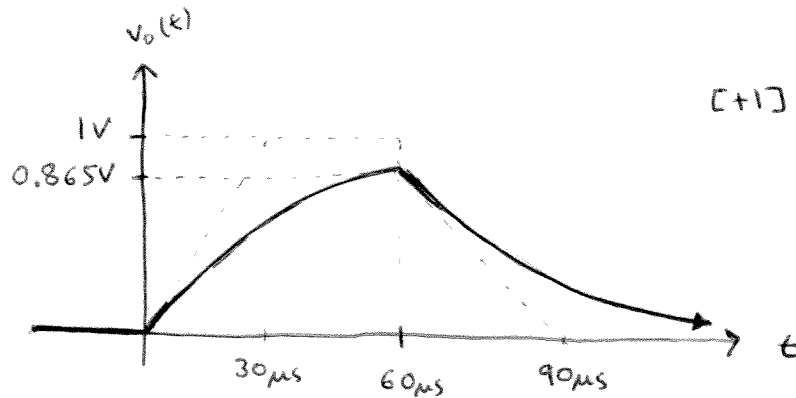

BONUS


$V_o = i_L \cdot 400\Omega$   $\therefore$  maximum inductor current takes place at time of maximum  $V_o$ , [+1]  
which occurs at  $t = 60\mu\text{s}$ .

$$\begin{aligned} U_{\text{max}} &= \frac{1}{2} L i_L^2(60\mu\text{s}) \\ &= \frac{1}{2} \cdot 12\text{mH} \cdot \left( \frac{0.865\text{V}}{400\Omega} \right)^2 \\ &= 28.06\text{ nJ} \quad [+1] \end{aligned}$$

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

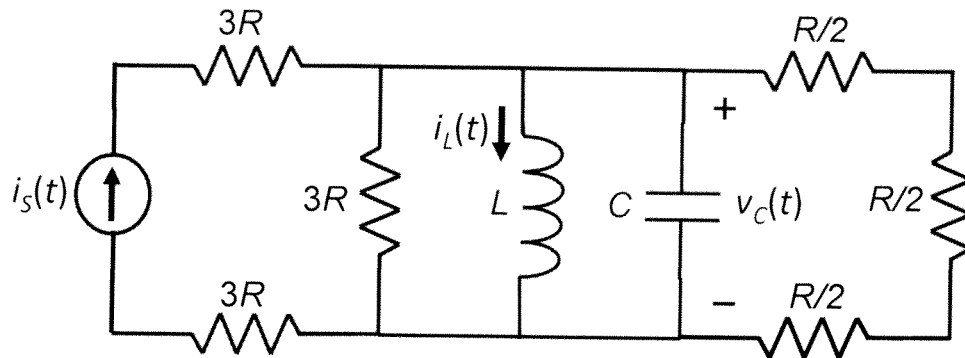1. Consider the circuit diagram. Answer the questions.




a) What is the differential equation satisfied by  $v_C(t)$ ? [6pts]

**HINT:** You may find it useful to simplify the circuit.

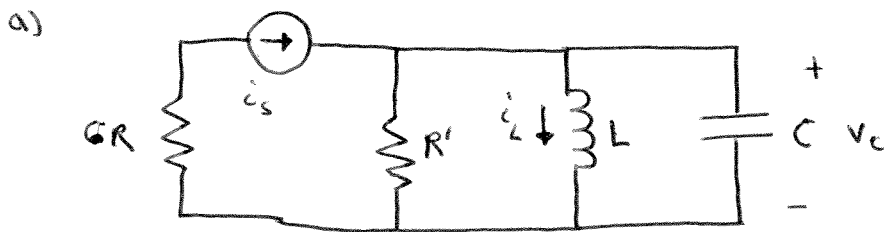b) What is the differential equation satisfied by  $i_L(t)$ ? [4pts]

**BONUS:** Consider a capacitor  $C$  and an inductor  $L$  connected together. The total energy stored in the capacitor and the inductor is  $U = \frac{1}{2}Cv^2 + \frac{1}{2}Li^2$ . Prove that  $dU/dt = 0$ . [2pts]



$$R' = \frac{3R \cdot 3R/2}{3R + 3R/2} = R \quad [+1]$$

KCL:

$$0 = -i_s + \frac{v_C}{R} + \frac{1}{L} \int_0^t v_C(t') dt' + i_L(0) + C \frac{dv_C}{dt}$$

or

$$0 = -i_s + \frac{v_C}{R} + \frac{v_C}{sL} + \frac{v_C}{1/sC} \quad [+1]$$

differentiation  
gives :

$$\frac{di_s}{dt} = \frac{1}{R} \frac{dv_c}{dt} + \frac{1}{L} v_c + C \frac{d^2 v_c}{dt^2}$$

(+1)            (+1)            (+1)            (+1)


b)  $v_c = L \frac{di_L}{dt} \quad (+1)$

Substitute into previous KCL equation:  $(+1)$

$$0 = -i_s + \frac{L}{R} \frac{di_L}{dt} + i_L(t) + LC \frac{d^2 i_L}{dt^2}$$

(+1/2)            (+1/2)            (+1/2)            (+1/2)

c)

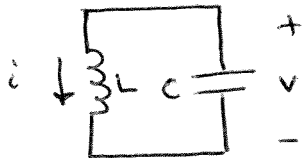

$$U = \frac{1}{2} C v^2 + \frac{1}{2} L i^2$$

$$\frac{dU}{dt} = C v \frac{dv}{dt} + L i \frac{di}{dt} \quad (+1/2)$$


$$v = +L \frac{di}{dt} \quad (+1/2)$$

$$i = -C \frac{dv}{dt} \quad (+1/2)$$

$$\frac{dU}{dt} = CL \frac{di}{dt} \cdot \frac{dv}{dt} + L \left( -\frac{dv}{dt} \right) \frac{di}{dt} \quad (+1/2)$$

$$= 0$$

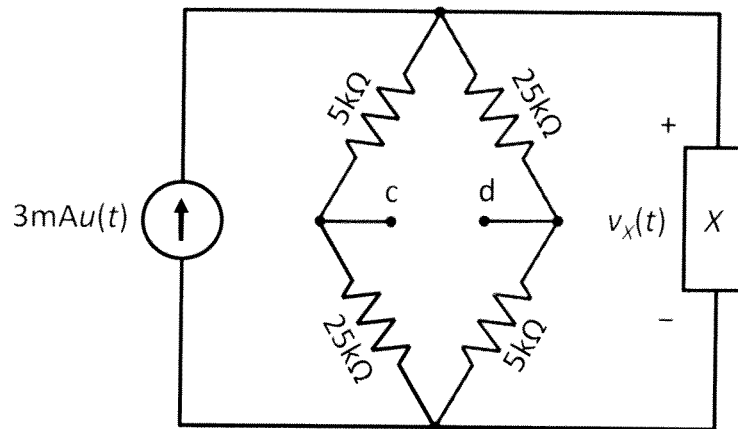2. Consider the circuit below. Assume dc steady state for  $t < 0$ . Answer the questions.



a) Assume that element X is a 10nF capacitor. Find the voltage  $v_x(t)$  for  $0 < t$ . [5pts]

b) Assume that element X is a 10mH inductor. Find the voltage  $v_x(t)$  for  $0 < t$ . [5pts]

BONUS: Assume again that element X is a 10mH inductor. If a 10kΩ resistor is attached across the terminals c and d, will the time constant be lengthened or shortened as compared to that of part b? [2pts]

$$a) \quad v_x(0+) = v_x(0-) = 0 \text{ mA} \cdot R_{TH} = 0 \text{ V} \quad [+1]$$


$$R_{TH} = (5 \text{ k}\Omega + 25 \text{ k}\Omega) \parallel (5 \text{ k}\Omega + 25 \text{ k}\Omega) = 15 \text{ k}\Omega \quad [+1]$$

$$v_x(\infty) = 3 \text{ mA} \cdot 15 \text{ k}\Omega = 45 \text{ V} \quad [+1]$$

$$\tau = R_{TH} \cdot C = 15 \text{ k}\Omega \cdot 10 \text{ nF} = 150 \mu\text{s} \quad [+1]$$

$$v_x(t) = v_x(\infty) + [v_x(0+) - v_x(\infty)] \exp(-t/\tau) \quad t > 0$$
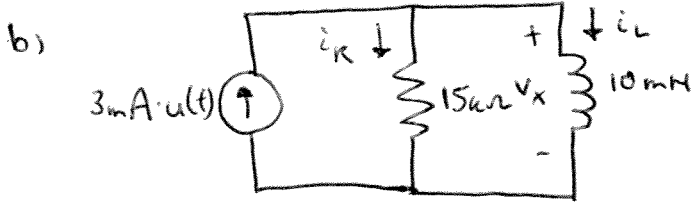
$$= 45 \text{ V} - 45 \text{ V} \exp(-t/150 \mu\text{s}) \quad [+1] \quad t > 0$$



$$i_L(0^+) = i_L(0^-) = 0 \text{ mA} \quad [+1] \quad i_L(\infty) = 3 \text{ mA} \quad [+1]$$



$$\tau = \frac{L}{R_{TH}} = \frac{10 \text{ mH}}{15 \text{ k}\Omega} = 667 \text{ ns} \quad [+1]$$

$$i_L(t) = 3 \text{ mA} - 3 \text{ mA} \exp(-t/667 \text{ ns}) \quad [+1] \quad t > 0$$

$$v_x(t) = 10 \text{ mH} \cdot \frac{di_L}{dt}$$

$$= 45 \text{ V} \exp(-t/667 \text{ ns}) \quad [+1] \quad t > 0$$

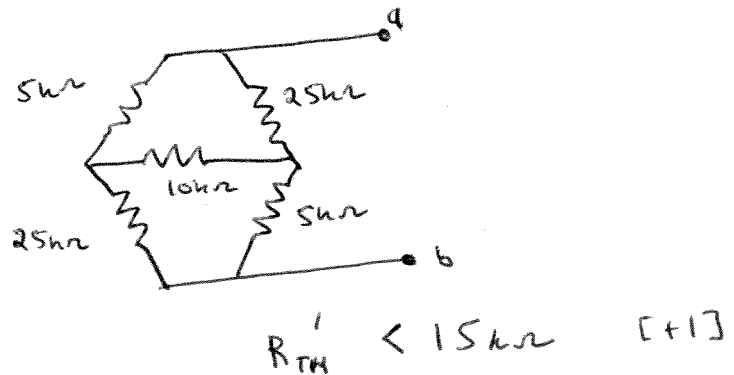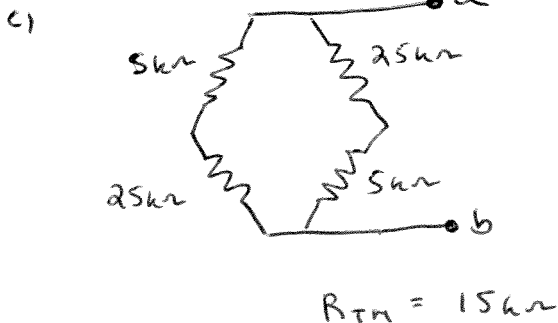\* It is also acceptable to use  $v_x(0^+) = 45 \text{ V}$  and  $v_x(\infty) = 0 \text{ V}$ .



$$\tau = \frac{L}{R_{TH}} \quad \tau' = \frac{L}{R'_{TH}} > \tau \quad [+1]$$

In other words,  $R_{TH}$  is reduced and  $\tau$  is lengthened.