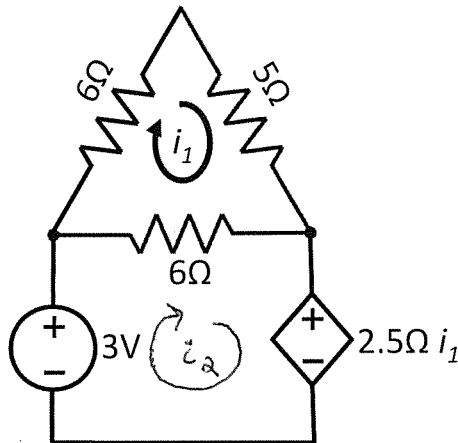


NAME _____ McGill ID# _____

READ each question carefully. Do your work independently. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

Consider the circuit diagram below. Answer the questions.



- 1) How many mesh current variables are required to solve the circuit above? [2pts]
- 2) Write down the mesh current equation(s). [2pts]
- 3) What is the value of i_1 ? [1pt]
- 4) How much power does the 6Ω resistor (located at the bottom edge of the triangle) absorb? [1pt]

1) two mesh currents [2]

$$2) \quad 0 = 5\Omega i_1 + 6\Omega (i_1 - i_2) + 6\Omega i_1 \quad [+1]$$

$$0 = 2.5\Omega i_1 - 3V + 6\Omega (i_2 - i_1) \quad [+1]$$

$$3) \quad \begin{aligned} 0 &= 17i_1 - 6i_2 \\ 3 &= -3.5i_1 + 6i_2 \end{aligned} \quad i_1 = \frac{\begin{vmatrix} 0 & -6 \\ 3 & +6 \end{vmatrix}}{\begin{vmatrix} 17 & -6 \\ -3.5 & +6 \end{vmatrix}} = 0.222A \quad [+1]$$

$$4) \quad i_2 = \frac{\begin{vmatrix} 17 & 0 \\ -3.5 & 3 \end{vmatrix}}{\begin{vmatrix} 17 & -6 \\ -3.5 & +6 \end{vmatrix}} = 0.630 \quad P_{abs} = (i_1 - i_2)^2 6\Omega = 0.996W$$