

# ECSE 200 - Electric Circuits 1


## Problem set 5

ECE Dept., McGill University

## **Part 1: Mesh Current Analysis with Voltage and Current Sources**
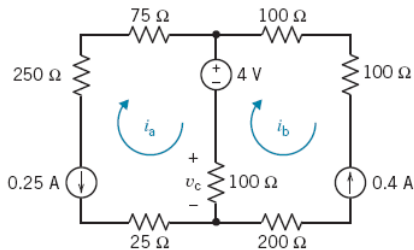
## Problem P 4.6-2


Find  $v_c$  for the circuit shown in the figure below.



## Problem P 4.6-2

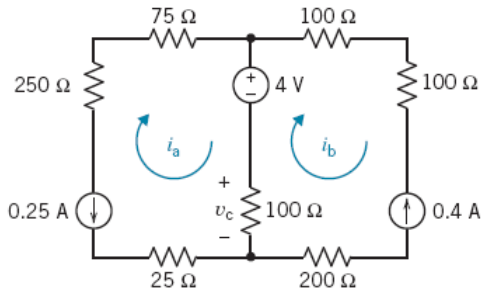
### Solution

- Mesh a:  $i_a = -0.25$  (A).
- Mesh b:  $i_b = -0.4$  (A).
- Apply Ohm's Law:  $v_c = 100(i_a - i_b) = 100 \times 0.15 = 15$  (V).



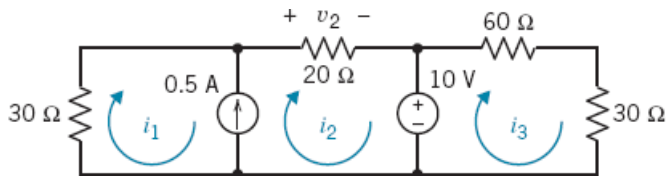
## Problem P 4.6-3

Find  $v_2$  for the circuit shown in the figure below.



## Problem P 4.6-3

### Solution

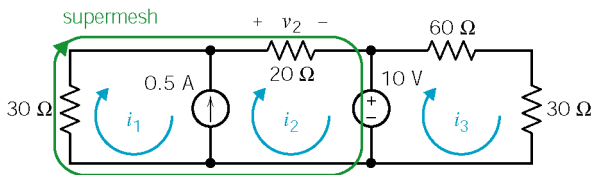

- From mesh 1 and 2 we have  $i_2 = i_1 + 0.5 \text{ (A)}$ .
- Apply KVL to the supermesh:

$$30i_1 + 20i_2 + 10 = 0$$


$$30i_1 + 20(i_1 + 0.5) + 10 = 0$$

$$i_1 = -0.4 \text{ (A)}$$


- $v_2 = 20i_2 = 20(i_1 + 0.5) = 20 \times 0.1 = 2 \text{ (V)}$
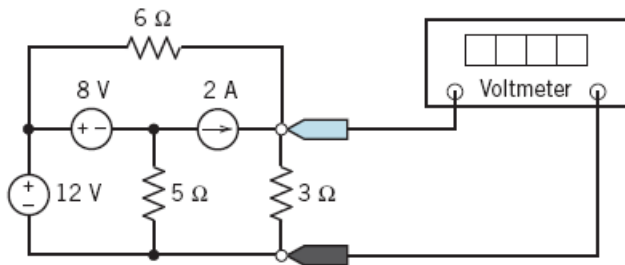
## Problem P 4.6-5

Determine the value of the voltage measured by the voltmeter shown in the figure below. *Answer:* 8 (V).



## Problem P 4.6-5

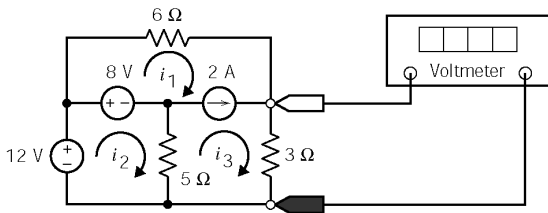

### (Long) solution

- Express the current source current in terms of the mesh currents:

$$i_3 = i_1 + 2 \quad (1)$$

- Supermesh (formed by mesh 1 and mesh 3):


$$6i_1 + 3i_3 - 5(i_2 - i_3) - 8 = 0 \Rightarrow 6i_1 - 5i_2 + 8i_3 = 8 \quad (2)$$

- Mesh 2:  $12 - 8 - 5(i_2 - i_3) = 0 \Rightarrow i_2 - i_3 = 0.2 \quad (3)$

- Solving (1), (2) and (3) results in:  $i_3 = \frac{8}{3} \text{ (A)} \Rightarrow$  the voltage measured by the voltmeter is:  $3i_3 = 8 \text{ (V)}$



## Problem P 4.6-5

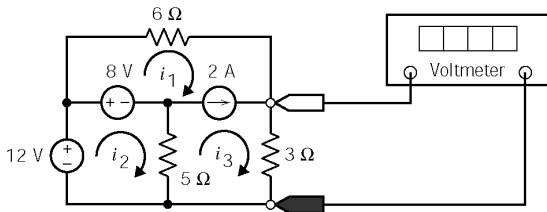

(Short) solution

- Consider only the outer supermesh:

$$12 - 6i_1 - 3i_3 = 0$$


$$12 - 6(i_3 - 2) - 3i_3 = 0$$

$$i_3 = \frac{8}{3} \text{ (A)}$$

- The voltage measured by the voltmeter is:  $3i_3 = 8 \text{ (V)}$ .

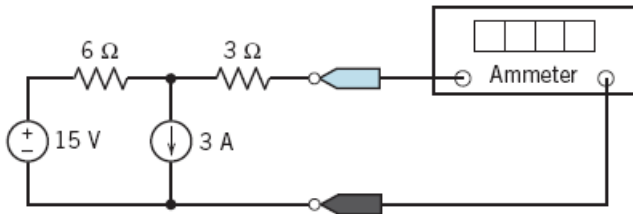
## Problem P 4.6-12

Determine the value of the current measured by the ammeter shown in the figure below.



## Problem P 4.6-12

### Solution

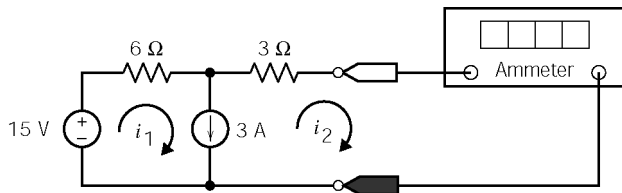

- Express the current source current in terms of the mesh currents:

$$i_2 + 3 = i_1 \quad (1)$$


- Apply KVL for the supermesh (formed by mesh 1 and mesh 2):

$$15 - 6i_1 - 3i_2 = 0 \Rightarrow 5 = 2i_1 + i_2 \quad (2)$$


- Solving (1) and (2) results in  $i_2 = -\frac{1}{3}$  (A), which is the current measured by the ammeter.
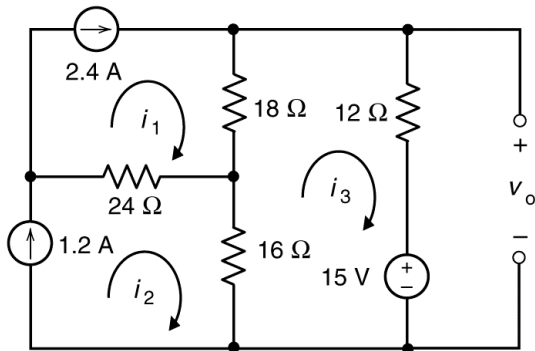
## Problem P 4.6-13

Determine the values of the mesh currents  $i_1$ ,  $i_2$  and  $i_3$  and the output voltage  $v_o$  in the circuit shown in the figure below.



## Problem P 4.6-13

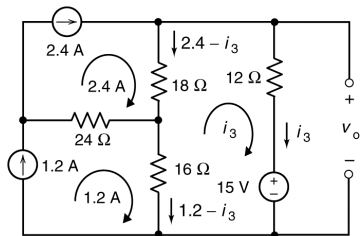

- Express the current source currents as the mesh currents:

$$i_1 = 2.4 \text{ (A)} \quad (1)$$

$$i_2 = 1.2 \text{ (A)} \quad (2)$$

- Apply KVL to mesh 3:


$$12i_3 + 15 - 16(i_2 - i_3) - 18(i_1 - i_3) = 0 \Rightarrow 18i_1 + 16i_2 - 46i_3 = 15 \quad (3)$$

- Solving (1), (2), and (3) results in  $i_1 = 1.369 \text{ (A)}$ ,  $i_2 = 0.169 \text{ (A)}$ , and  $i_3 = 1.0304 \text{ (A)}$ .
- Therefore,  $v_o = 12i_3 + 15 = 27.3648 \text{ (V)}$ .

## Part 2: Mesh Current Analysis with Dependent Sources

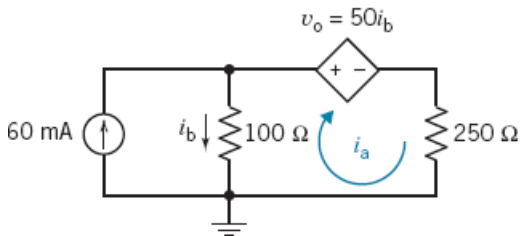
## Problem P 4.7-3

Find  $v_o$  for the circuit shown in the figure below.



## Problem P 4.7-3

### Solution

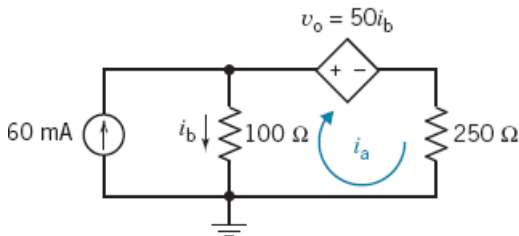

- Express the control current  $i_b$  as a function of the mesh current  $i_a$ :

$$i_b = 0.06 - i_a \quad (1)$$

- Apply KVL to the right mesh:


$$50i_b + 250i_a - 100i_b = 0 \quad (2)$$

- Solving (1) and (2) results in  $i_a = 0.01$  (A) and  $i_b = 0.05$  (A).
- Therefore,  $v_o = 50i_b = 50 \times 0.05 = 2.5$  (V).



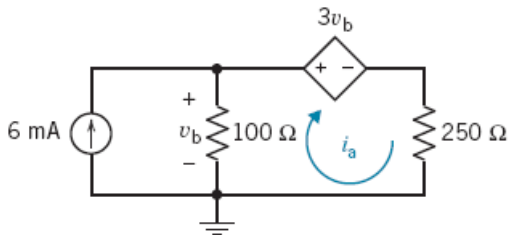
## Problem P 4.7-4

Determine the mesh current  $i_a$  for the circuit shown in the figure below.



## Problem P 4.7-4

### Solution

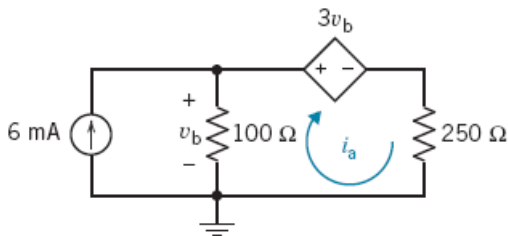

- Express the control voltage  $v_b$  as a function of the mesh current  $i_a$ :

$$\frac{v_b}{100} + i_a = 0.006 \Rightarrow v_b = 0.6 - 100i_a \quad (1)$$


- Apply KVL to the right mesh:

$$v_b - 3v_b - 250i_a = 0 \Rightarrow -2v_b = 250i_a \quad (2)$$

- Solving (1) and (2) results in  $i_a = -0.024$  (A).
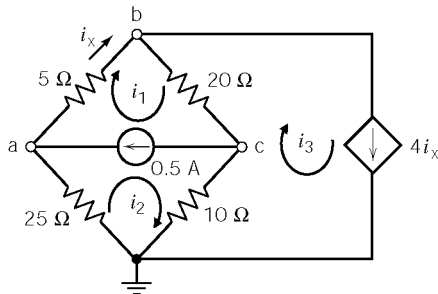
## Problem P 4.7-11

Determine the values of the mesh currents of the circuit shown in the figure below.



## Problem P 4.7-11

### Solution

- Determine the mesh current variables:
  - ▶ Mesh 1:  $i_1 = i_x$
  - ▶ Mesh 2 ( apply KCL to node a):  $i_2 = i_x - 0.5$
  - ▶ Mesh 3:  $i_3 = 4i_x$
- Apply KVL to the supermesh formed by mesh 1 and mesh 2:


$$0 = v_{ab} + v_{bc} + v_{cd} + v_{da}$$

$$0 = 5i_1 + 20(i_1 - i_3) + 10(i_2 - i_3) + 25i_2$$

$$0 = 5i_x + 20(i_x - 4i_x) + 10(i_x - 0.5 - 4i_x) + 25(i_x - 0.5)$$

$$i_x = -0.29167 \text{ (A)}$$

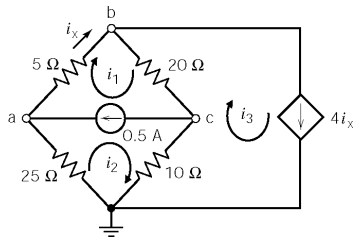
Therefore,  $i_1 = -0.29167 \text{ (A)}$ ,  $i_2 = -0.79167 \text{ (A)}$ , and  $i_3 = -1.16668 \text{ (A)}$ .



## Part 3: Source Transformations

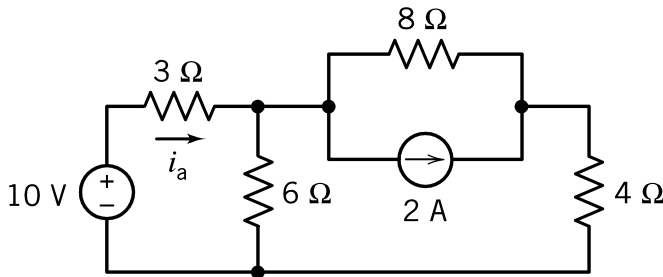
## Problem P 5.2-2

Consider the circuit shown in the figure below. Find  $i_a$  by simplifying the circuit (using source transformations) to a single-loop circuit so that you need to write only one KVL equation to find  $i_a$ .




## Problem P 5.2-2


### Solution

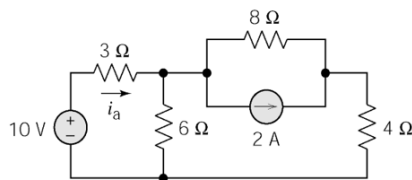


(1)

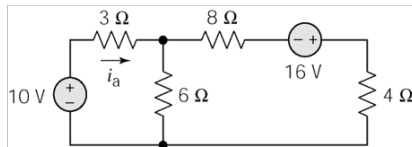

(2)

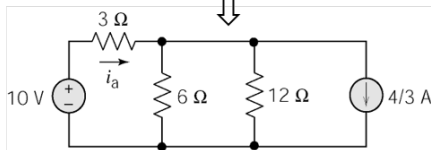

(3)

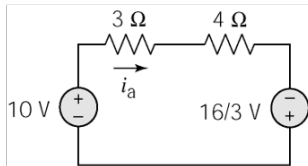


(4)

Apply KVL to the circuit shown in (4):  $7i_a - \frac{16}{3} - 10 = 0 \Rightarrow i_a = 2.19 \text{ (A)}.$
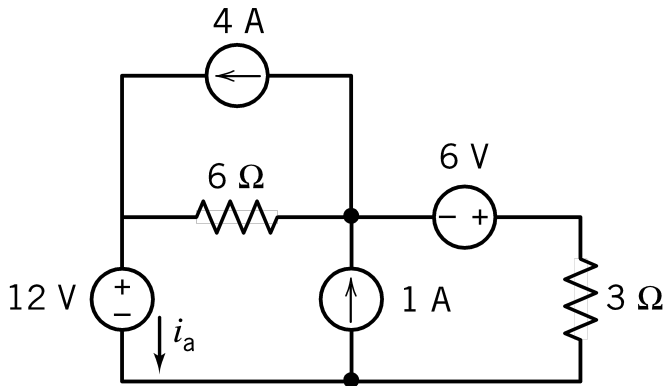
## Problem P 5.2-5




Use source transformations to find the current  $i_a$  in the following circuit.





## Problem P 5.2-5

### Solution

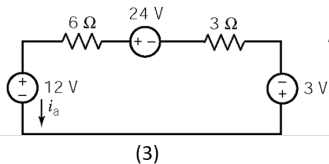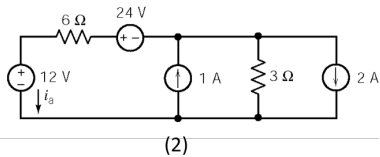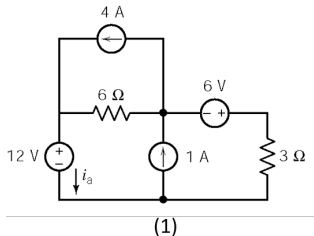


Apply KVL to the final transformed circuit in (3):

$$12 + 3 + 3i_a - 24 + 6i_a = 0 \Rightarrow i_a = 1 \text{ (A)}.$$

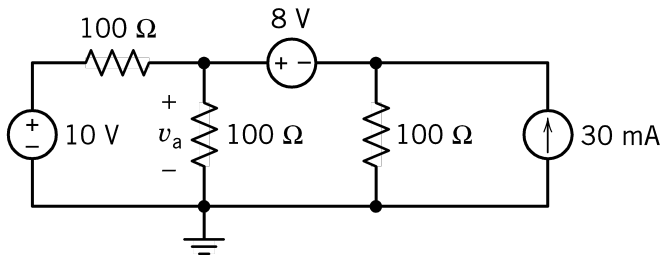
## Problem P 5.2-6

Use source transformations to find  $v_a$  in the following circuit.



## Problem P 5.2-6





### Solution

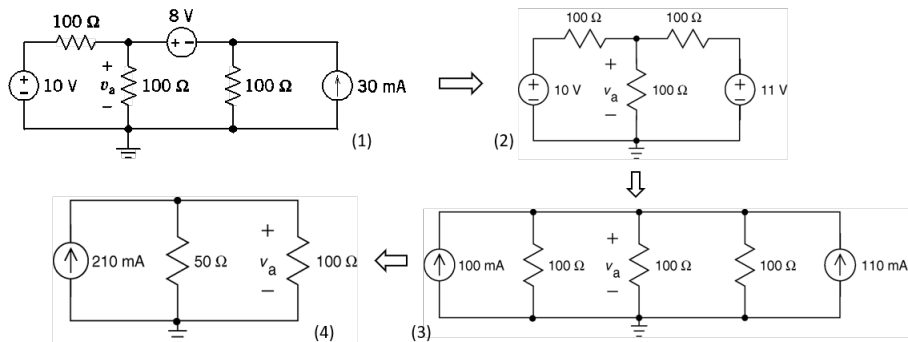

- (1) $\Rightarrow$ (2): A source transformation on the right side of the circuit, followed by replacing serial voltage sources with an equivalent voltage source.

## Problem P 5.2-6


### Solution (cnt.)

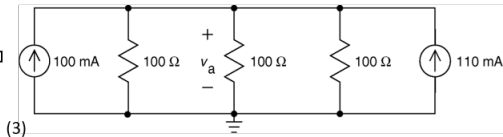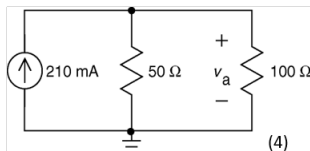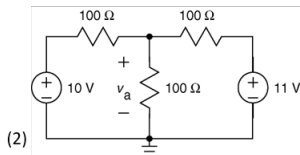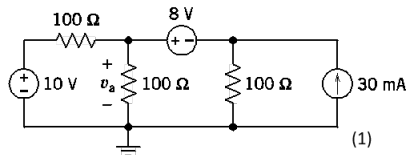

- (2) $\Rightarrow$ (3): Apply source transformations to the voltage sources on both side of the circuit in (2).

## Problem P 5.2-6





### Solution (cnt.)

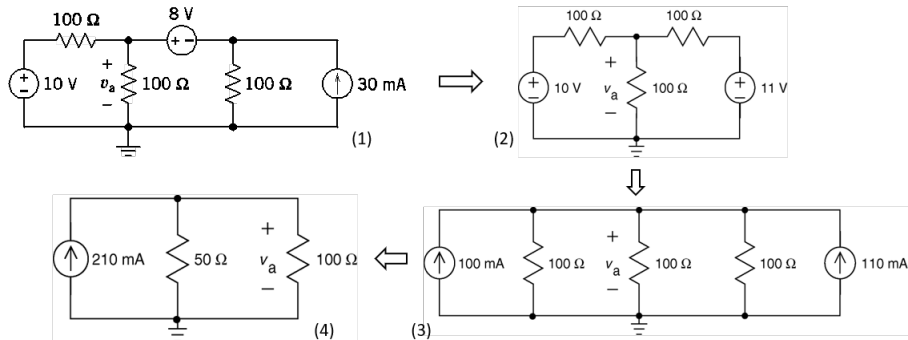

- (3) $\Rightarrow$ (4): Replacing parallel resistors and parallel current sources with an equivalent resistor and an equivalent current source, respectively.

## Problem P 5.2-6

### Solution (cnt.)

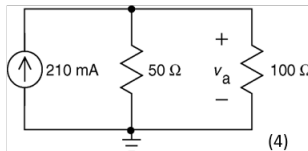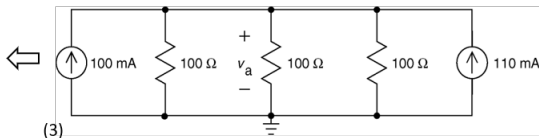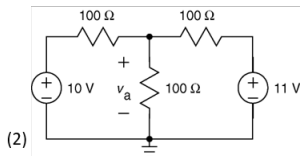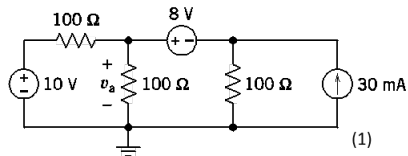

- From the final transformed circuit in (4):  $v_a = 0.21 \times \frac{50 \times 100}{50 + 100} = 7 \text{ (V)}.$

Thank you !