

5. Operational Amplifiers

- Operational Amplifiers
- Negative Feedback
- Ideal Op-Amp Model
- Op-Amp Circuits
- “Practical” Op-Amp Model


Today's Outline

5. Operational Amplifiers


- Operational Amplifiers
- Ideal Op-Amp Model
- Op-Amp Circuits

Operational Amplifier

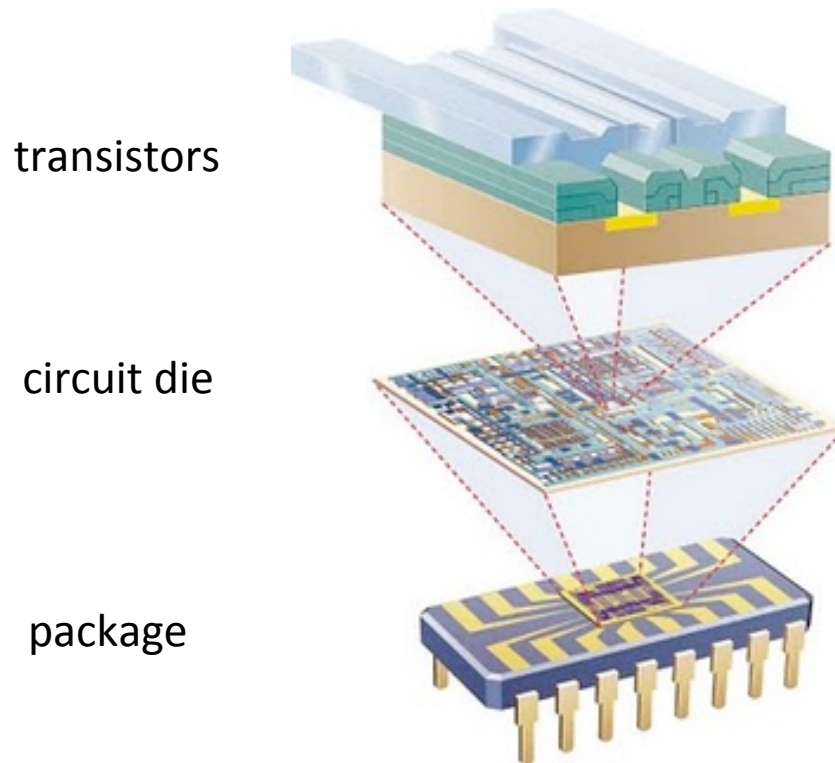The **operational amplifier** (also called an **op-amp** for short) is a very useful, general purpose amplifier circuit. It is composed of transistors, resistors, and capacitors. We will use an ***ideal model*** for the terminal characteristics of the op-amp and study some useful op-amp circuits.



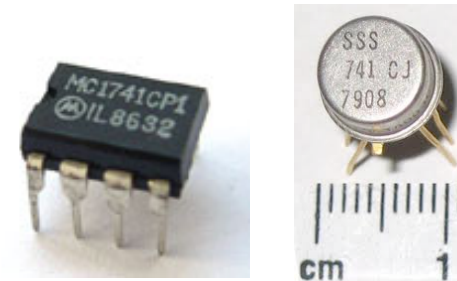
The op-amp is built in to many integrated circuits, and can also be found in discrete packages ready for use on a circuit board:




Operational Amplifier

The Fairchild $\mu A741$ is a classic op-amp design. Designed by David Fullagar, while under the supervision of Gordon Moore (PhD Chemistry, co-founder of Intel, introduced “Moore’s Law”).

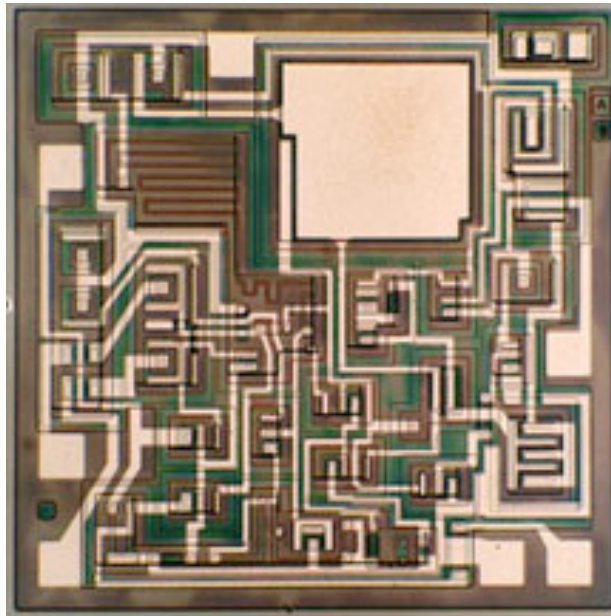You will learn how to design your own op-amp in a future course (ECSE 334)!



photograph of die


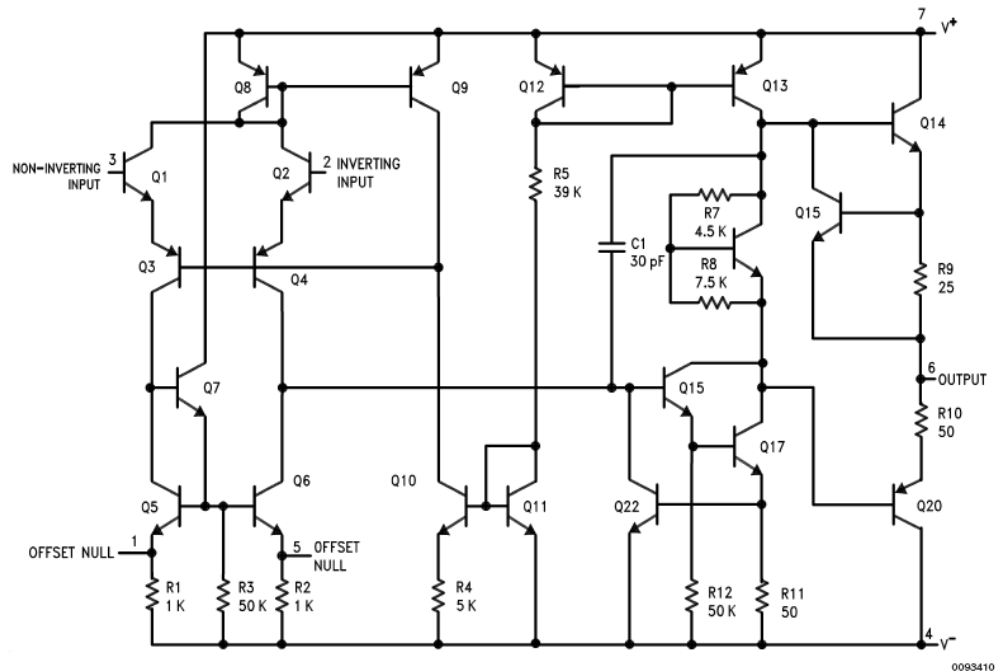


schematic

Operational Amplifier



Op-Amp Circuit Element:

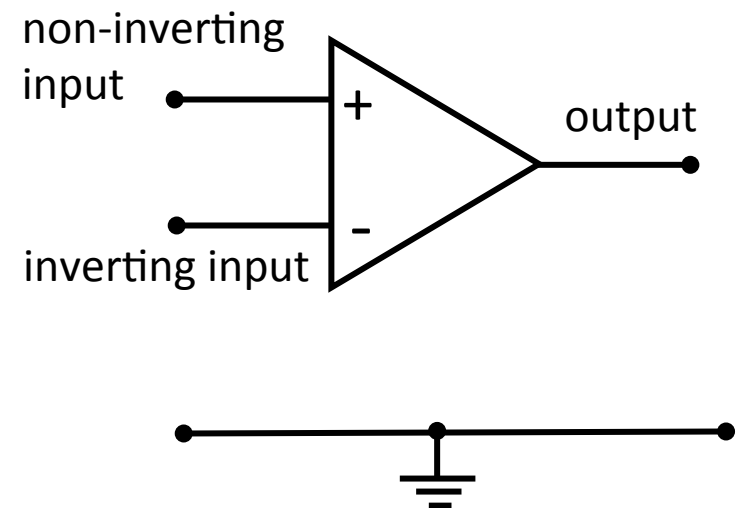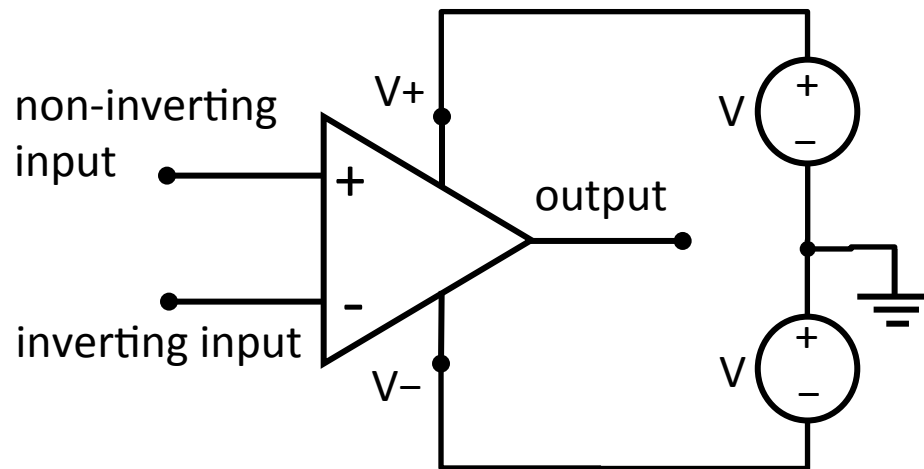- a 6-terminal circuit when power supply terminals are included
- the op-amp can often be modeled as a 4-terminal device
- the “reference terminal” ⏏ is physically connected to the op-amp power supply and is drawn without connection to the rest of the circuit symbol



Operational Amplifier

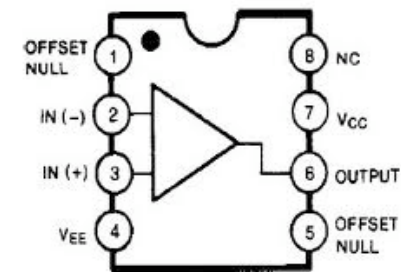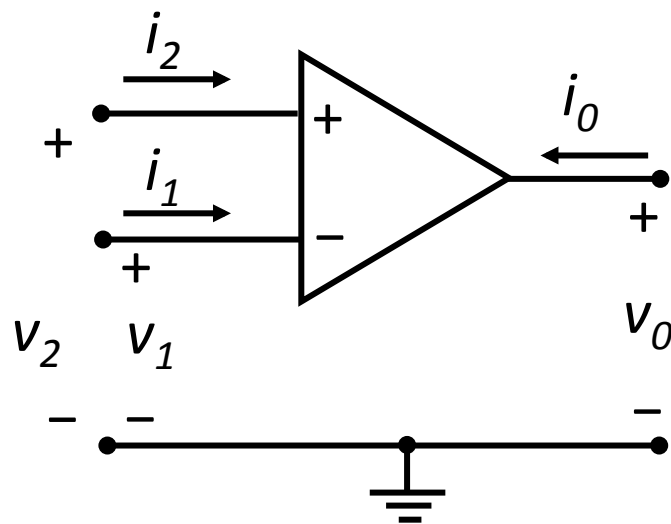
Op-Amp Circuit Variables: By convention, voltage variables are defined with respect to the *reference terminal*. Although drawn as a physically separate entity in a diagram, the reference is physically connected to the op-amp through the power supply.



Negative Feedback

Negative Feedback Loop: The connection of the output terminal back to the inverting input terminal, through a circuit element.

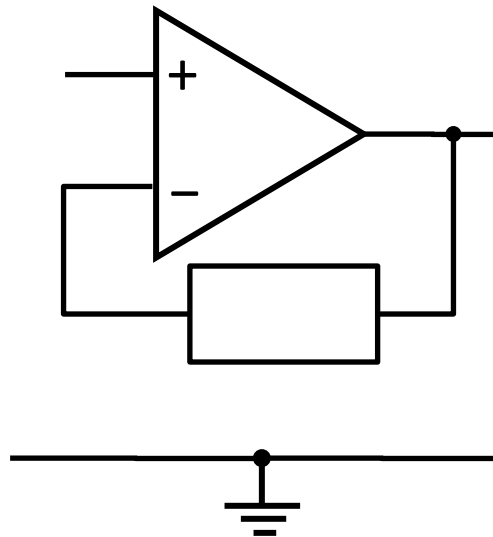
- circuit output is stable, in contrast to positive feedback (*we will return to this point in later lectures*)
- the amplifier becomes **programmable** by using different circuit elements in the negative feedback loop, allowing one to perform different operations on circuit signals



Open Input Approximation

Open input approximation: The currents at the op-amp input terminals are identically zero:


$$i_2 = i_1 = 0$$

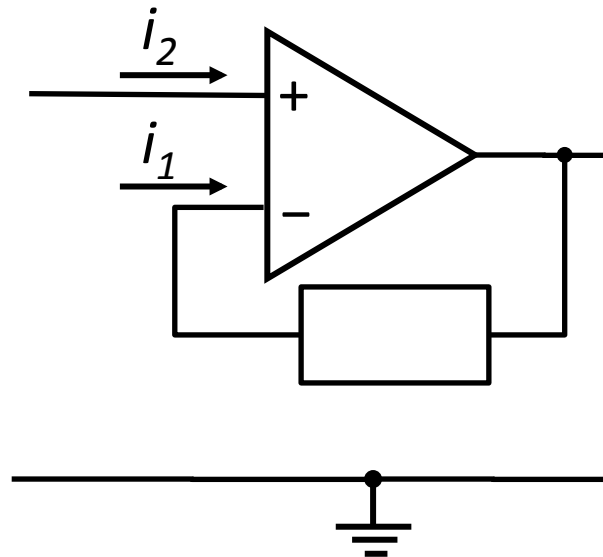

Virtual Short Approximation

Virtual short approximation: The input voltage difference for an op-amp in a negative feedback loop is identically zero:

$$V_2 = V_1$$

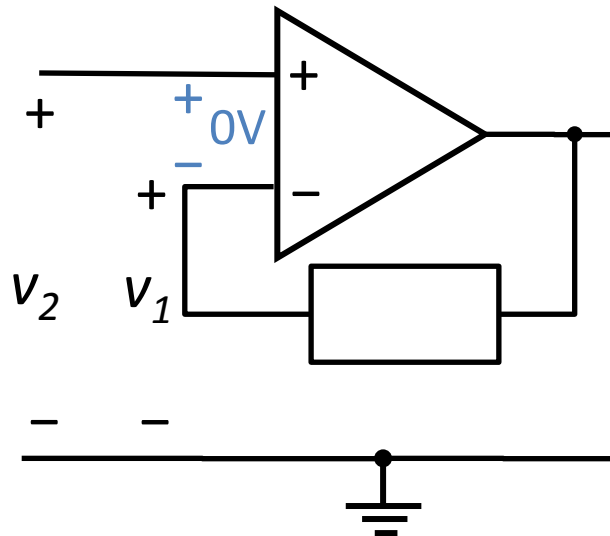

It is the negative feedback loop that enables the op-amp to reach this condition.


Ideal Op-Amp Model

Ideal Op-Amp Model: *Idealized* terminal equations for an op-amp,

$$v_2 = v_1 \quad (\text{virtual short approximation})$$

$$i_2 = i_1 = 0 \quad (\text{open input approximation})$$

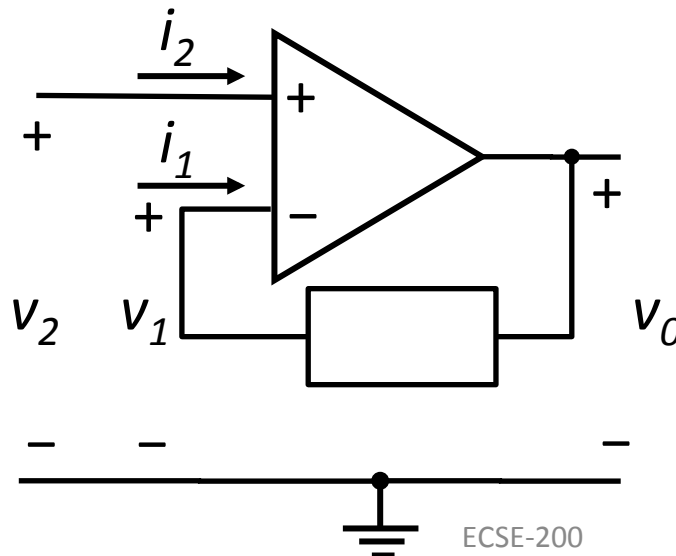
The circuit solution that is found using these terminal equations is useful only for stable circuits, meaning those with ***negative feedback***



output voltage limit


Output voltage cannot exceed power supply voltages: $-V < v_o < +V$

When $v_o = \pm V$, the op-amp output is said to “**saturate**”, and the ***ideal op-amp approximation no longer applies***. Saturation is undesired op-amp behaviour.

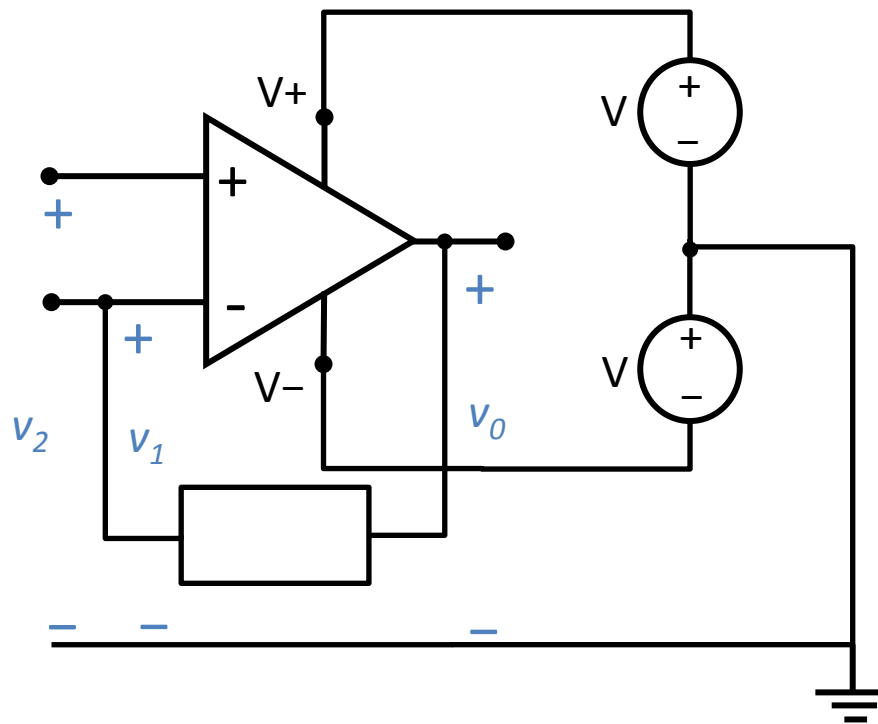

Example 1


Find the ratio v_o / v_{in} , which we call the voltage gain. Assume ideal op-amp behaviour. Calculate the power delivered by the independent voltage source, and the power absorbed by the load resistor.

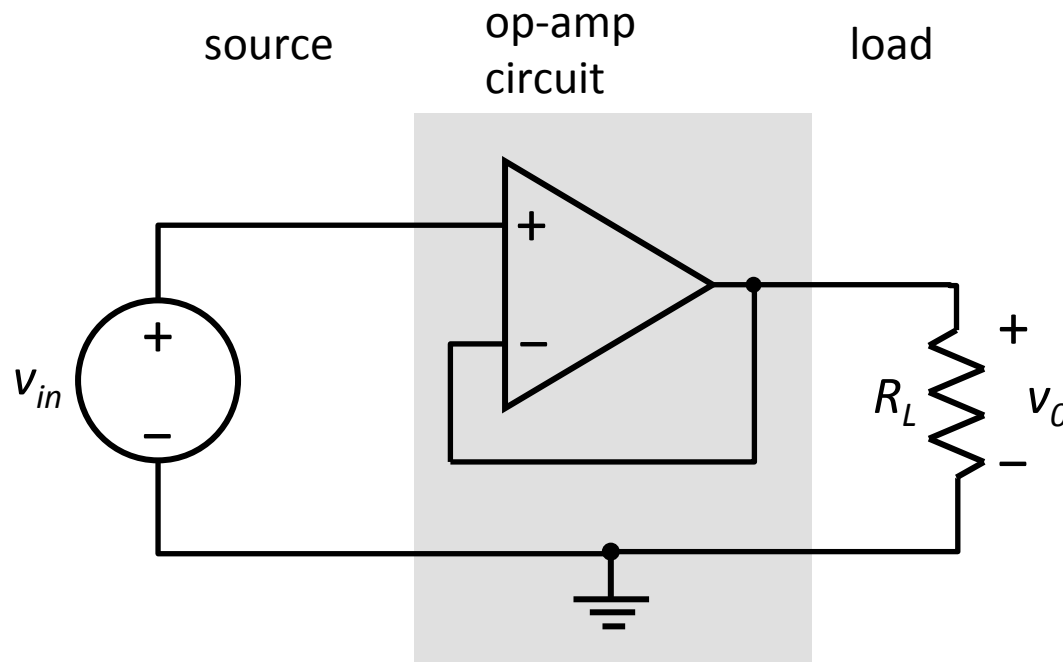

Example 1

Use ideal op-amp equations.


Ideal op-amp: $v_2 = v_1$
 $i_2 = i_1 = 0$

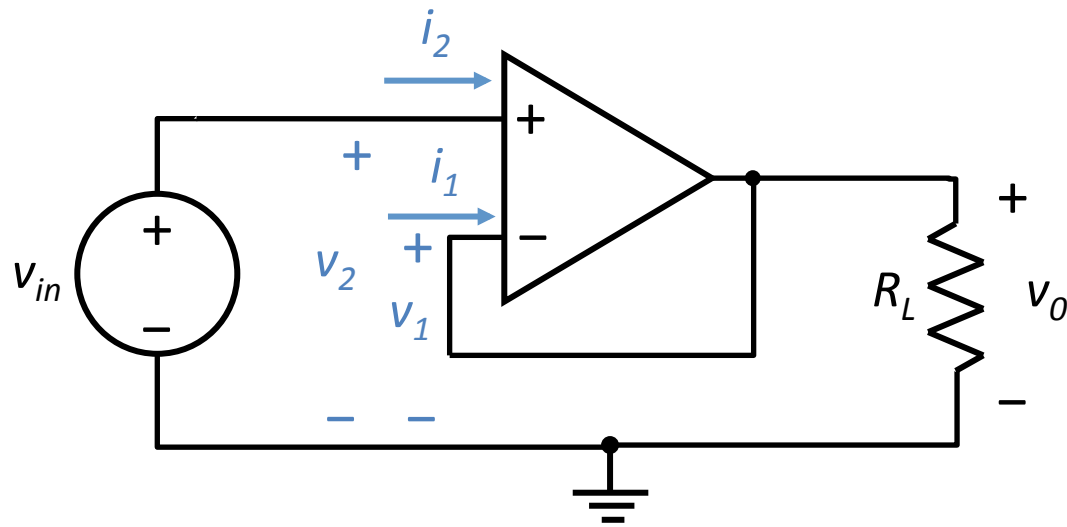

Example 1

Apply KVL.

$$\text{KVL: } 0 = -v_{in} + v_2$$

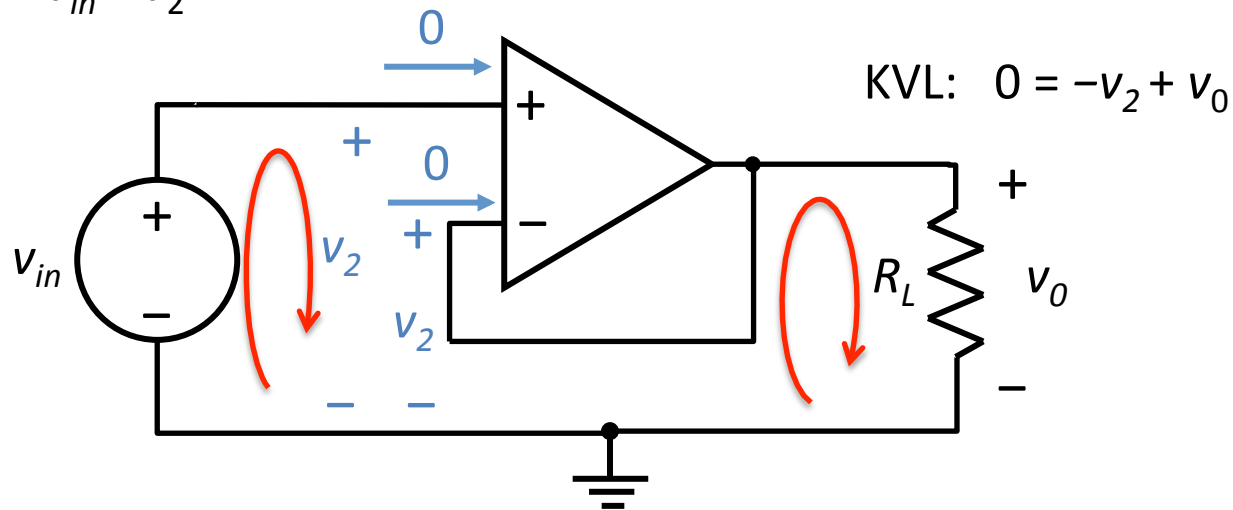

Combining the above: $v_{in} = v_2 = v_o$


$$\frac{v_o}{v_{in}} = 1$$

This op-amp circuit is configured as a **voltage follower**, sometimes also called a **buffer**.

Example 1

Calculate power delivered by source and absorbed by load resistor.

KCL: $i_{in} = i_2 = 0$

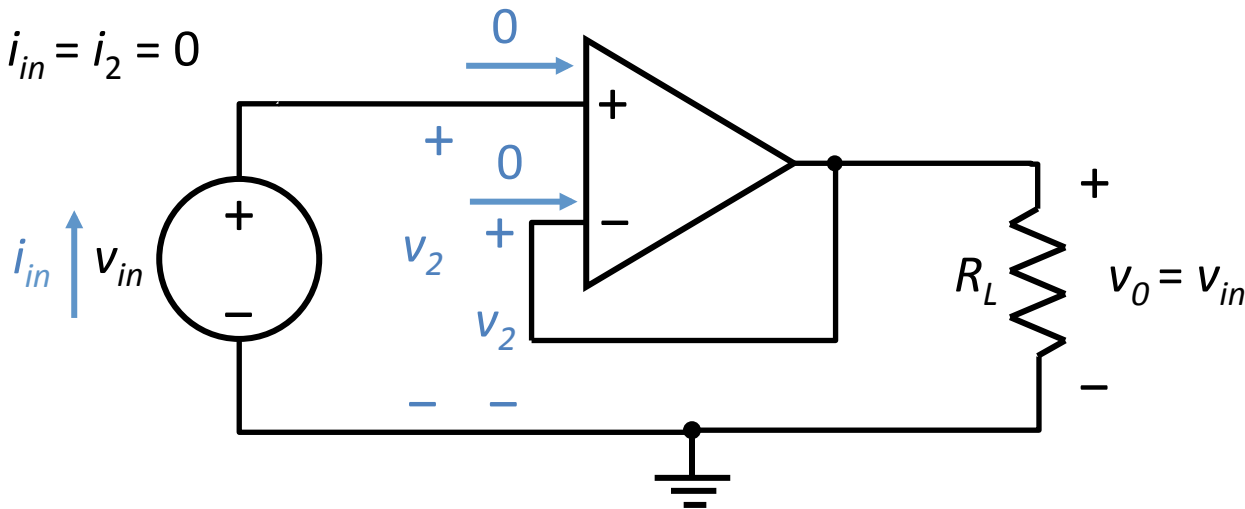

Power delivered by independent source:

$$\begin{aligned} P_{in} &= v_{in} i_{in} \text{ note } i_{in} \text{ reference direction!} \\ &= v_{in} 0 \\ &= 0 \text{ W} \end{aligned}$$


Power absorbed by load resistor:

$$\begin{aligned} P_{abs} &= (v_O)^2 / R_L \\ &= (v_{in})^2 / R_L \end{aligned}$$

The ideal voltage follower draws no power from the source, and delivers power to the load. This is very useful if the source (eg. a computer port) is not capable of delivering sufficient power to the load (eg. a peripheral at the end of a long cable).

Example 1

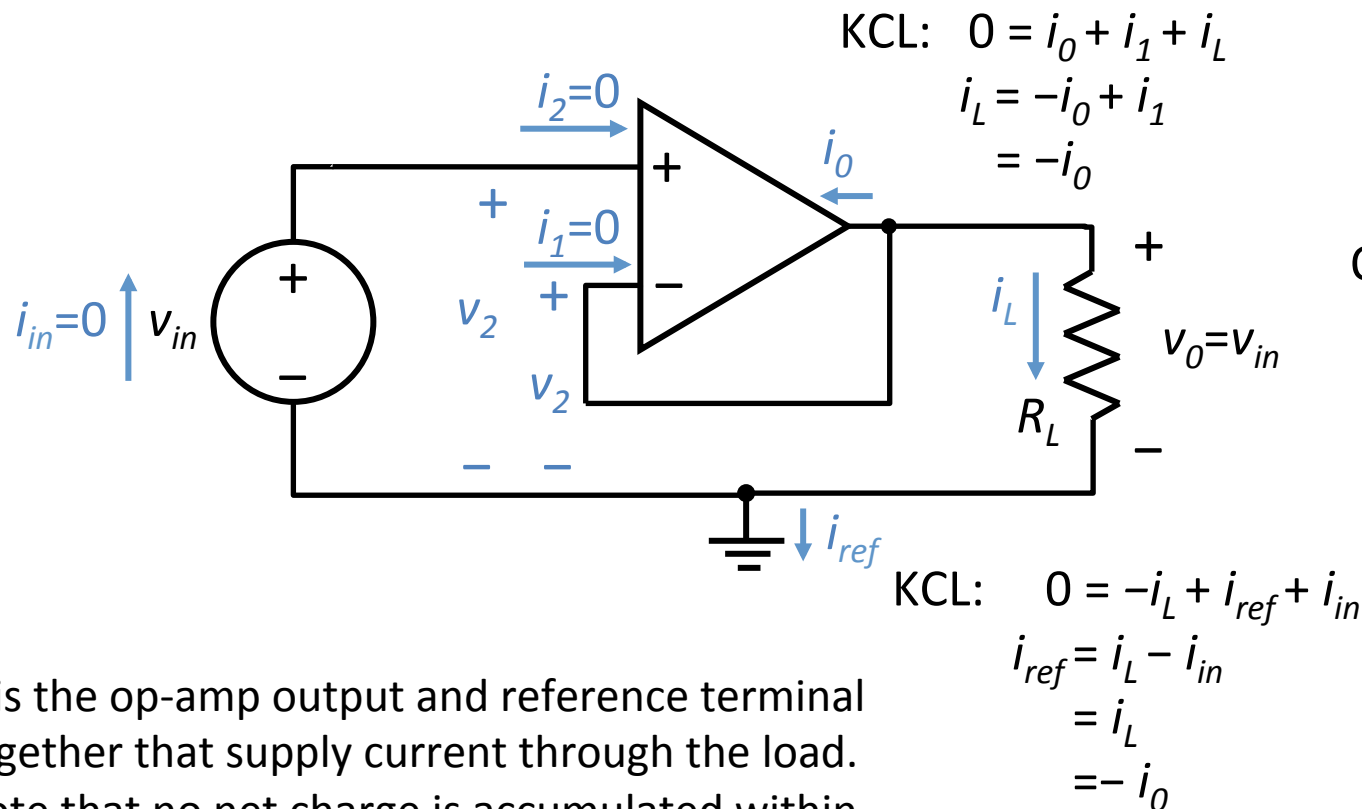
Question: How is the current flowing on the load side?



It is the op-amp output and reference terminal together that supply current through the load. Note that no net charge is accumulated within the op-amp (or its power supplies, not illustrated).


Example 2

Assuming ideal op-amp behaviour, find the voltage gain v_{out}/v_{in} .

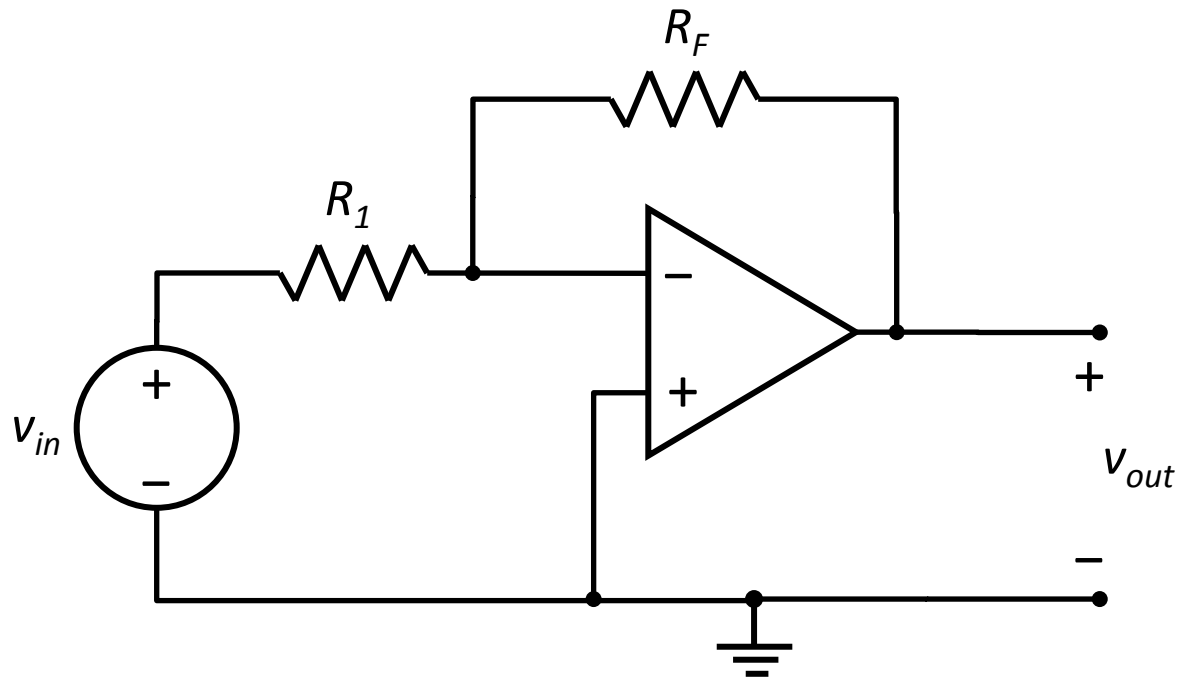


Example 2

Ideal op-amp: $v_2 = v_1$
 $i_2 = i_1 = 0$

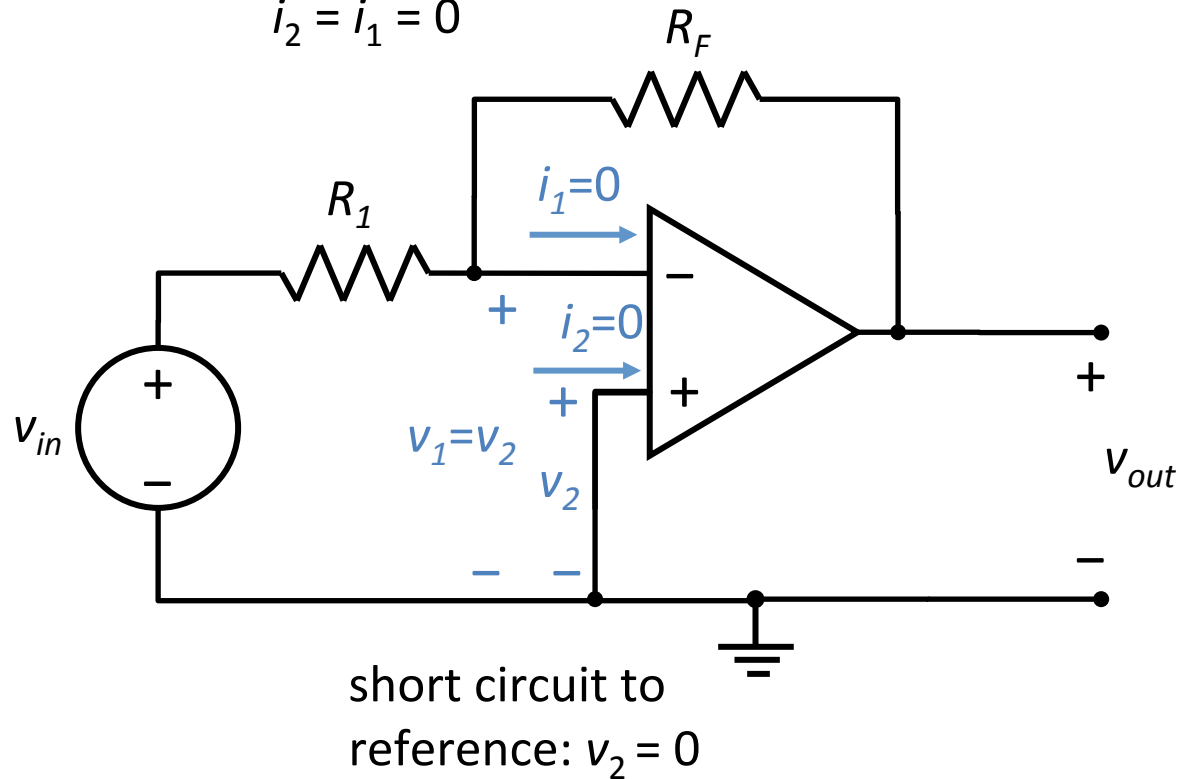

Example 2

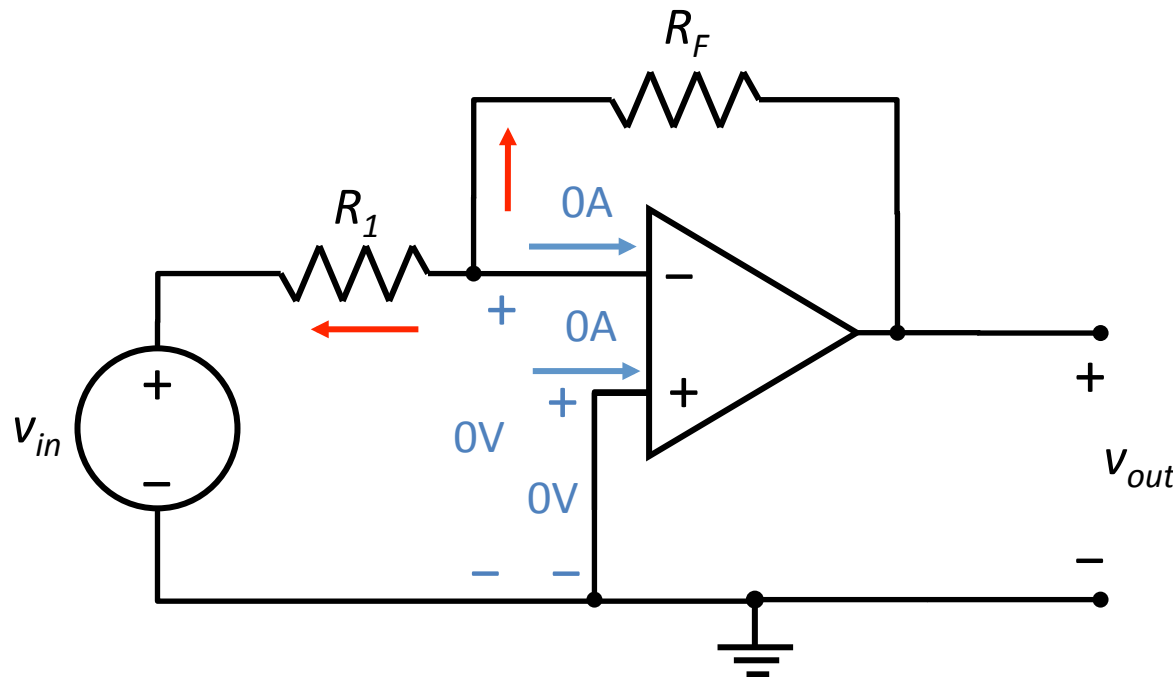

Node voltage equation at inverting input:

$$0 = \frac{0 - v_{in}}{R_1} + \frac{0 - v_{out}}{R_F}$$

$$\frac{v_{out}}{v_{in}} = -\frac{R_F}{R_1}$$


This op-amp circuit is configured as an ***inverting amplifier***. The voltage gain is:

- negative, hence the sign of the v_{out} is inverted from that of v_{in}
- programmed by the ratio of R_F to R_1

This circuit forces the current flowing in R_1 , which is determined by the input voltage, through the feedback resistor R_F .


Example 3

Assuming ideal op-amp behaviour, find the voltage gain v_{out}/v_{in} .

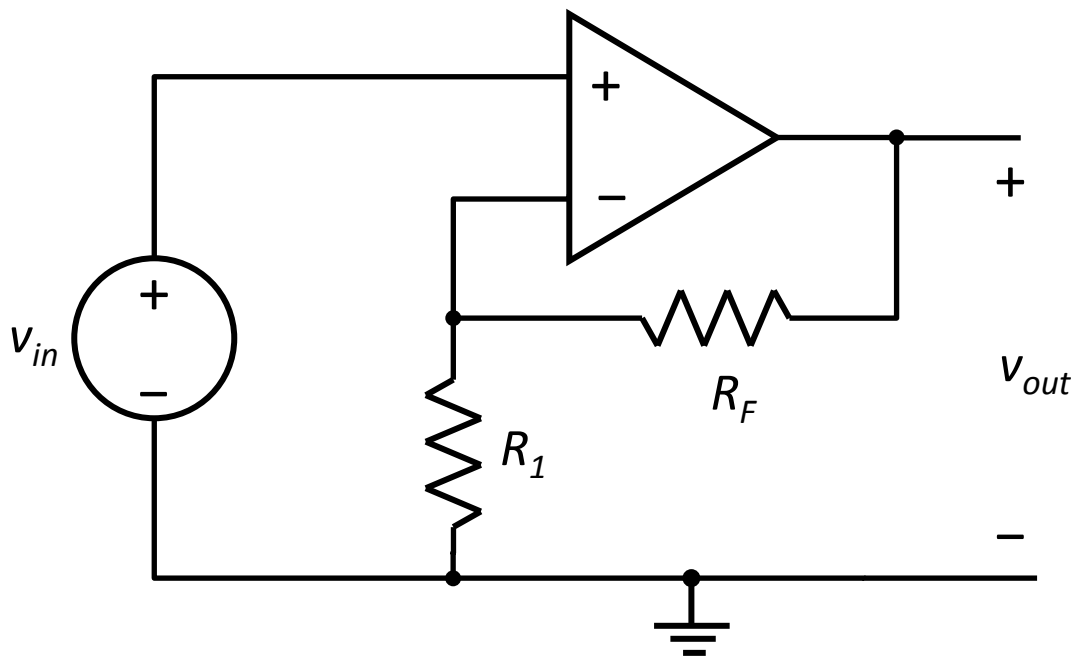

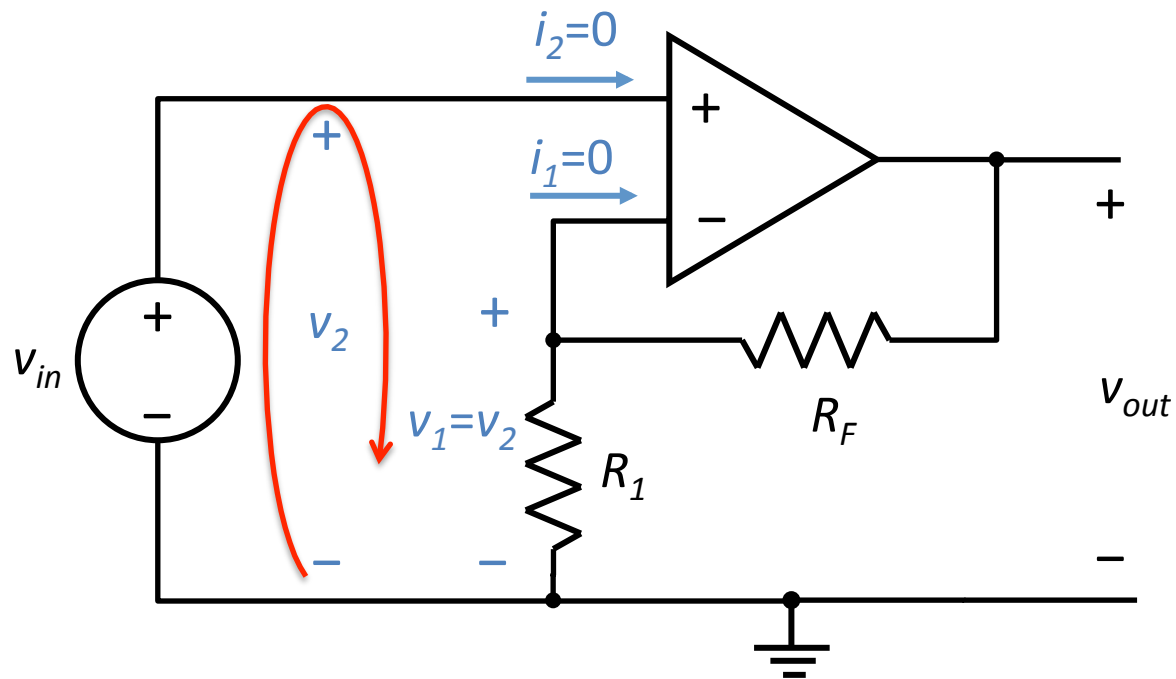
Example 3

Ideal op-amp: $v_2 = v_1$
 $i_2 = i_1 = 0$



KVL: $0 = -v_{in} + v_2$
 $v_2 = v_{in}$

Example 3

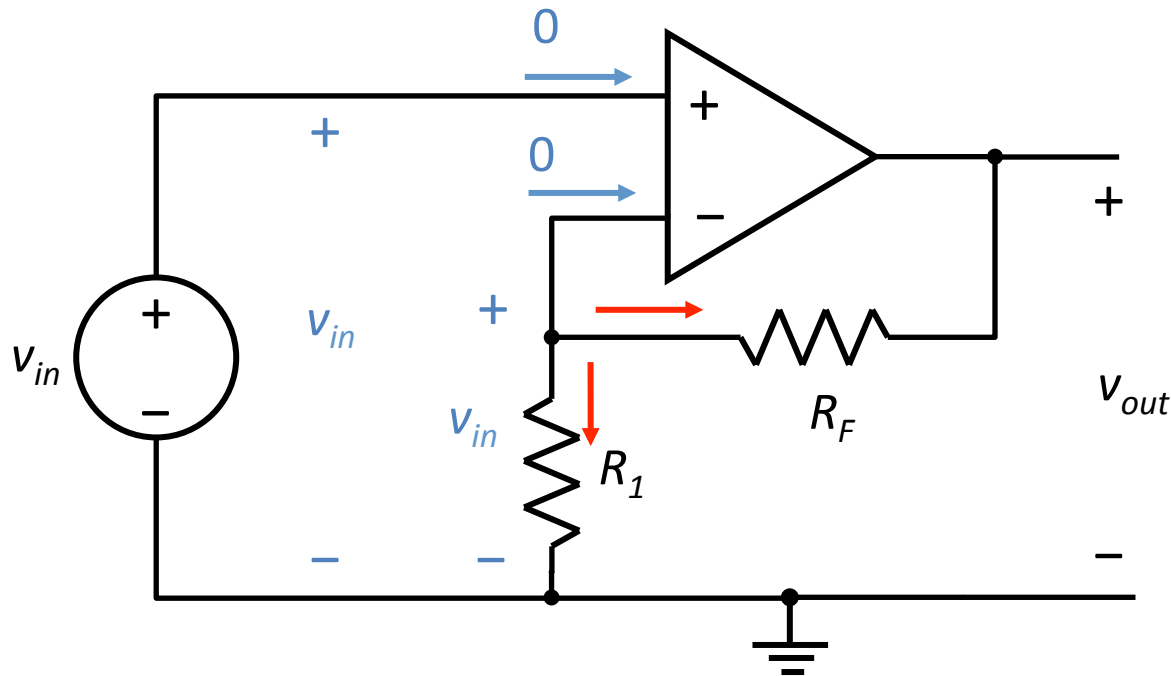

Node voltage equation at inverting input:

$$0 = \frac{v_{in}}{R_1} + \frac{v_{in} - v_{out}}{R_F}$$


$$0 = v_{in} \left(\frac{1}{R_1} + \frac{1}{R_F} \right) - v_{out} \left(\frac{1}{R_F} \right)$$

$$\frac{v_{out}}{v_{in}} = 1 + \frac{R_F}{R_1}$$

This op-amp circuit is configured as a ***non-inverting amplifier***. The voltage gain is:

- positive, hence the sign of the v_{out} is the same as that of v_{in}
- programmed by the ratio of R_F to R_1

a note on analysis

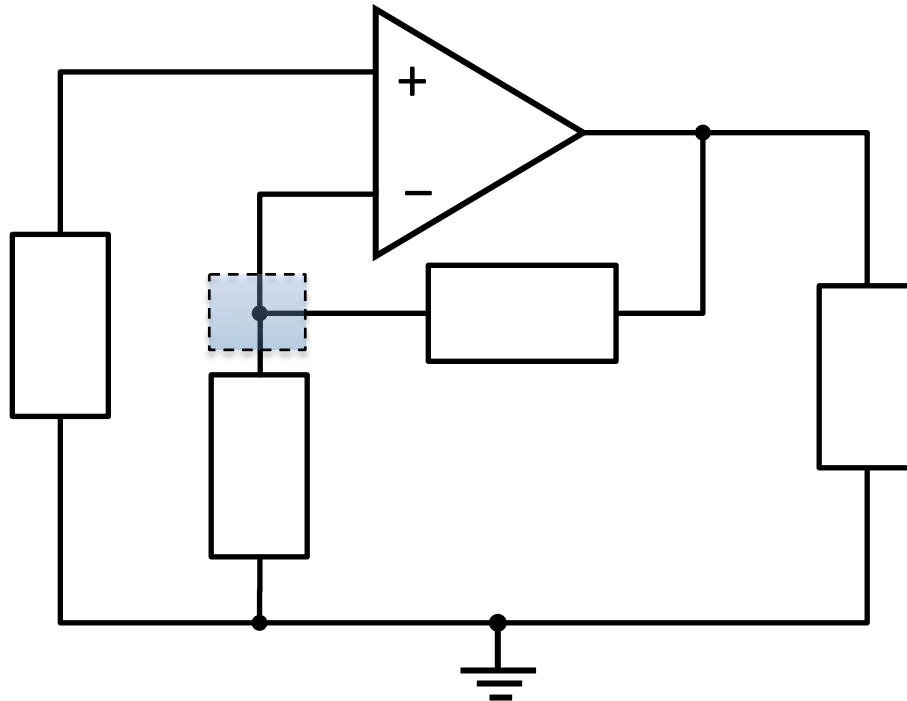

Ideal op-amp circuits in negative feedback can **often** be analyzed by:

- determining what is the non-inverting input voltage
- analyzing current flow at the inverting input terminal

a diversion



the Art of Electronics,
P. Horowitz, W. Hill
1989

Fantastic cook book (reference book with recipes) for a myriad of useful circuits, including op-amp circuits, digital circuits, and transistor circuits.

Includes useful rules of thumb for practical circuit designs.