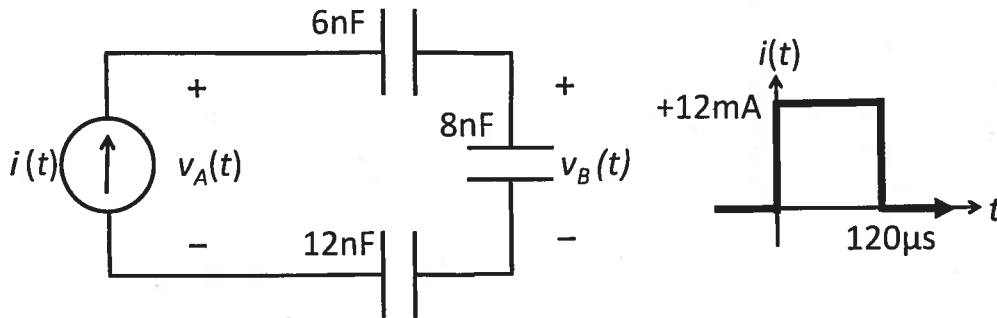


NAME _____ McGill ID# _____

READ each question carefully. Do your work independently. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).



Consider the circuit above. The capacitors store zero energy for time $t < 0$.

- 1) What is $v_A(0+)$? [1pt]
- 2) What is $v_B(0+)$? [1pt]
- 3) What is $v_A(120\mu s)$? [2pts]
- 4) What is $v_B(120\mu s)$? [2pts]
- 5) What is $v_A(t)$ as $t \rightarrow \infty$? [1pt]
- 6) What is $v_B(t)$ as $t \rightarrow \infty$? [1pt]
- 7) What is the maximum power that the current source delivers to the circuit? [1pt]

1) zero energy stored and capacitor voltage continuity implies $v_A(0+) = 0V$ [1]

2) for same reason, $v_B(0+) = 0V$ [1]

$$3) C_{eq} = \left(\frac{1}{6nF} + \frac{1}{8nF} + \frac{1}{12nF} \right)^{-1} = 2\frac{2}{3} nF \text{ [1]}$$

$$v_A(120\mu s) = v_A(0) + \frac{1}{C_{eq}} \int_0^{120\mu s} 12mA \cdot dt = 0V + \frac{12mA \cdot 120\mu s}{2\frac{2}{3} nF} = 540V \text{ [1]}$$

$$4) v_B(120\mu s) = v_B(0) + \frac{1}{8nF} \int_0^{120\mu s} 12mA \cdot dt = 180V \text{ [2]}$$

$$5) i = 0 \text{ for } t > 120\mu s, \text{ thus } v_A(\infty) = 540V \text{ [1]} \quad 6) v_B(\infty) = 180V \text{ [1]}$$

7) Maximum power is delivered at $t = 120\mu s^-$

$$P_{del} = 12mA \cdot 540V = 6.48W \text{ [1]}$$

