

LAST NAME SOLUTIONS

MCGILL ID# _____


FIRST NAME _____

SIGNATURE _____

- Only Faculty standard calculator accepted
- No cellphone allowed
- Show all your work

- Clearly indicate your final answer with the SI unit and multiplier
- You have 45 minutes to complete this quiz

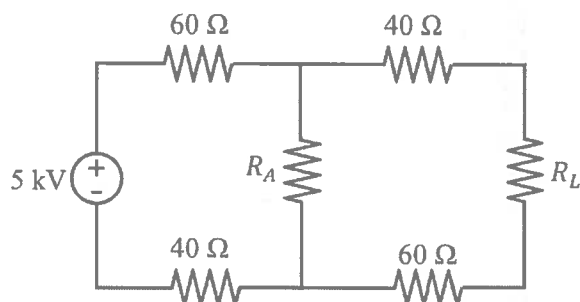Question 1: Consider the circuit shown below. Answer the following questions.



- Under the condition where $R_L = 0 \Omega$, what resistance value should R_A be to maximize the power delivered to R_A and what is the maximum power value that can be delivered to R_A ? [2 pt]
- Under the condition where $1/R_A = 0 \Omega^{-1}$, what resistance value should R_L be to maximize the power delivered to R_L and what is the maximum power value that can be delivered to R_L ? [2 pt]
- Under the same condition where $1/R_A = 0 \Omega^{-1}$, but with the constraint that the current through R_L must be at least 15 A, what resistance value should R_L be to maximize the power delivered to R_L and what is the maximum power value that can be delivered to R_L ? [3 pt]


a) $R_L = 0 \Omega$ (short circuit)

MAX PWR:

$$P_{wr} = \frac{V_{oc}}{2} \cdot \frac{i_{sc}}{2}$$

$$P_{wr} = \frac{2.5kV}{2} \cdot \frac{50A}{2}$$

$$P_{wr} = 31.25 kW$$

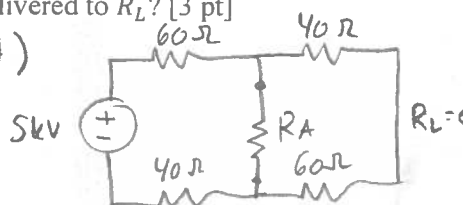


$$V_{oc} = 5kV \cdot \frac{(40\Omega + 60\Omega)}{60\Omega + 40\Omega + 40\Omega + 60\Omega}$$

$$V_{oc} = 5kV \cdot \frac{100\Omega}{200\Omega} = 2.5kV$$

→ MAX PWR TRANSFER THEOREM where $R_A = R_T$

Turning off supply.

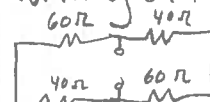

$$R_T = (60 + 40) \parallel (40 + 60)$$

$$R_T = 50\Omega$$

$$\therefore R_A = 50\Omega$$

$$i_{sc} = \frac{V_{oc}}{R_T} = \frac{2.5kV}{50\Omega} = 50A$$

b) $\frac{1}{R_A} = 0 \Omega^{-1} \rightarrow R_A = \infty$ (open circuit)

R_A


$$P_{wr} = \frac{V_{oc}}{2} \cdot \frac{i_{sc}}{2}$$

$$= \frac{5kV}{2} \cdot \frac{25A}{2}$$

$$P_{wr} = 31.25 kW$$

$$V_{oc} = 5kV$$
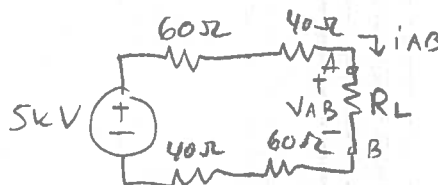
$$i_{sc} = \frac{V_{oc}}{R_T} = \frac{5kV}{200\Omega} = 25A$$




$R_L = R_T$ for max pwr

$$R_T = 200\Omega \quad \therefore R_L = 200\Omega$$

$$\therefore R_L = 133\frac{1}{3}\Omega$$

$$P_{wr} = 30 kW$$

c) $i_{AB} \geq 15A$

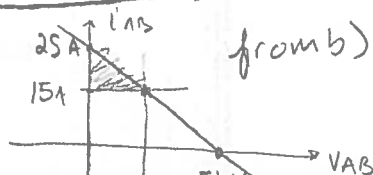


MAX power at $i_{AB} = 15A$

$$V_{AB} = 5kV - 15A \cdot 200\Omega = 2kV$$

$$R_L = \frac{V_{AB}}{i_{AB}} = \frac{2kV}{15A} = 133\frac{1}{3}\Omega$$

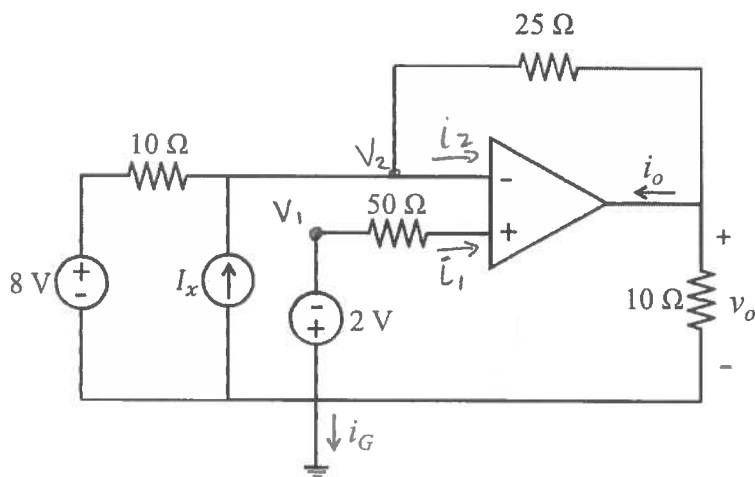Question 2: Consider the circuit shown below. Answer the following questions.



- Under the condition where $I_x = 0$ A, what is the voltage value v_o ? [2 pt]
- Under the condition where $I_x = 1$ A, what is the current value i_o ? [2 pt]
- Under the condition where $I_x = 2$ A, what is the current value i_G ? [2 pt]
- Under the same condition as in part c) where $I_x = 2$ A, what is the power delivered by the current source? [1 pt]

a) $I_x = 0$ A (open-circuit)


from ideal op-amp model $i_1 = i_2 = 0$ $V_1 = V_2$

$$V_1 = -2V = V_2$$

KCL @ inv. node

$$\frac{-2V - 8V}{10\Omega} + \frac{-2V - v_o}{25\Omega} = 0$$
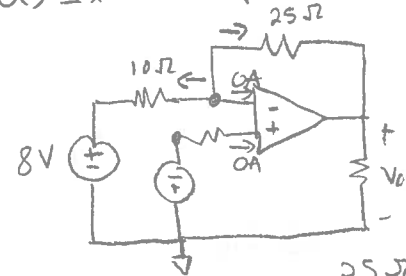
$$-1A - \frac{2V}{25\Omega} = \frac{v_o}{25\Omega} \Rightarrow \boxed{v_o = -27V}$$



b)

ideal model $i_1 = i_2 = 0$ & $V_1 = V_2 = -2V$


$$\text{KCL @ inv. node} \rightarrow \frac{-2V - 8V}{10\Omega} - 1A + \frac{-2V - v_o}{25\Omega}$$

$$-2A - \frac{2V}{25\Omega} = \frac{v_o}{25\Omega} \Rightarrow v_o = -52V$$

KCL @ output node:

$$i_o + \frac{-52 - (-2)}{25\Omega} + \frac{-52}{10\Omega} = 0 \rightarrow i_o = 2A + 5.2A$$

$$\boxed{i_o = 7.2A}$$

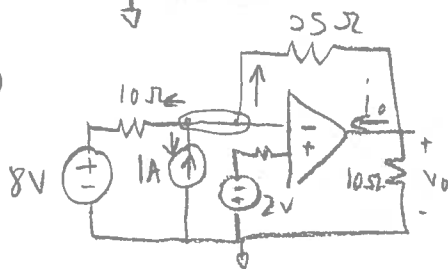

c)

find v_o as in b) KCL @ inv. node:

$$\frac{-2V - 8V}{10\Omega} - 2A + \frac{-2V - v_o}{25\Omega}$$

$$-3A - \frac{2V}{25\Omega} = \frac{v_o}{25\Omega} \Rightarrow v_o = -77V$$


KCL @ ref node

$$\frac{8V - (-2V)}{10\Omega} + 2A + 0A + \frac{-(-77)}{10\Omega} + i_G = 0$$

$$1A + 2A + 7.7A + i_G = 0$$

$$\therefore \boxed{i_G = -10.7A}$$

d)

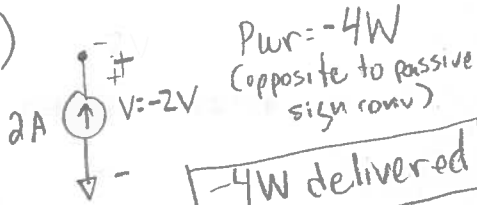

-4W delivered