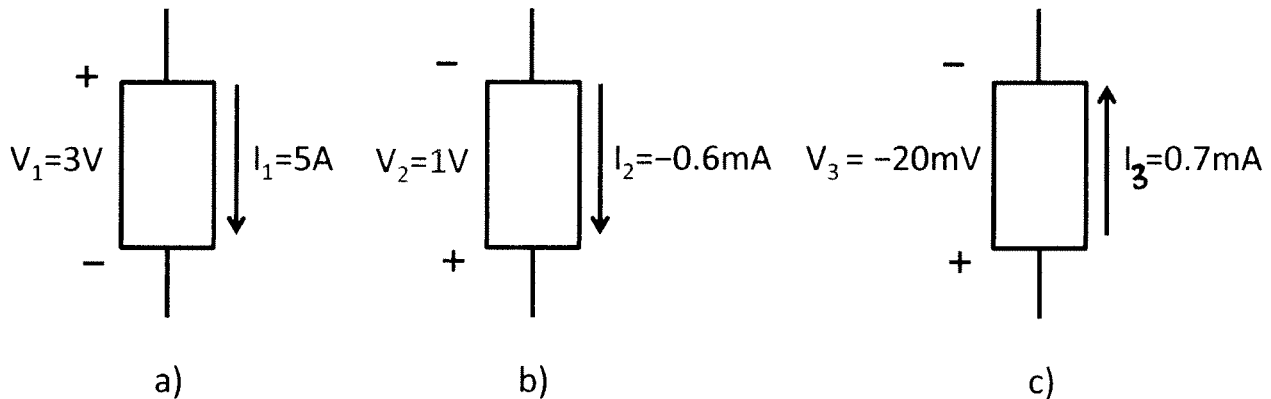


NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

1. For each circuit element below, indicate the power that is being delivered or absorbed by the element. [ 2 pts / element x 3 elements = 6 pts ]




$$\begin{aligned} \text{a) } P_{\text{abs}} &= V_1 \cdot I_1 \quad (\text{passive sign convention}) \quad [+1] \\ &= (3V)(5A) \\ &= 15W \text{ absorbed by element } [+1] \end{aligned}$$

$$\begin{aligned} \text{b) } P_{\text{del}} &= V_2 \cdot I_2 \quad (\text{opposite to passive sign convention}) \quad [+1] \\ &= (1V)(-0.6mA) \\ &= -0.6mW \text{ delivered by element } [+1] \\ &\quad \text{or } 0.6mW \text{ absorbed by element} \end{aligned}$$

$$\begin{aligned} \text{c) } P_{\text{abs}} &= V_3 \cdot I_3 \quad (\text{passive sign convention}) \quad [+1] \\ &= (-20mV)(0.7mA) \\ &= -14\mu W \text{ absorbed by element } [+1] \\ &\quad \text{or } 14\mu W \text{ delivered by element} \end{aligned}$$

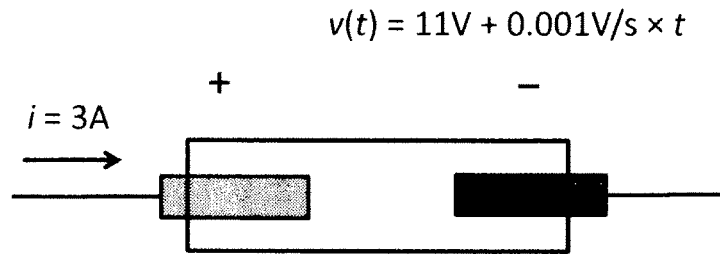2. Consider the electrochemical cell (battery) being recharged below with a constant current.



a) What is the total charge delivered to the cell over the time  $0 < t < 1$  hour, in SI units? [2 pts]

b) What is the power delivered to the cell at the moment  $t = 1200s$ ? [2 pts]

c) What is the total energy delivered to the cell over the time  $0 < t < 1$  hour, in SI units? [3 pts]

$$\begin{aligned} \text{a) } q &= \int_0^{3600s} 3A \, dt = 3A \cdot 3600s \quad [+1] \\ &= 10.8 \, \text{kC} \quad [+1] \end{aligned}$$


$$\begin{aligned} \text{b) } P_{\text{delivered to cell}} &= i \cdot v(1200s) \quad [+1] \\ &= 3A \cdot (11V + 0.001 \frac{V}{s} \times 1200s) \\ &= 36.6 \, \text{W} \quad \text{delivered to cell} \quad [+1] \end{aligned}$$

$$\begin{aligned} \text{c) } \Delta U_{\text{delivered}} &= \int_0^{3600s} P(t) \, dt \quad [+1] \\ &= \int_0^{3600s} 3A \cdot (11V + 0.001 \frac{V}{s} \times t) \, dt \quad [+1] \\ &= 3A \cdot 11V \cdot t \Big|_0^{3600s} + \frac{1}{2} 3A \cdot 0.001 \frac{V}{s} t^2 \Big|_0^{3600s} \\ &= 118.8 \, \text{kJ} + 19.44 \, \text{kJ} \\ &= 138.24 \, \text{kJ} \quad \text{delivered to cell} \quad [+1] \end{aligned}$$

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate). **HINT:** Use KCL, KVL and Ohm's Law. You may find it useful to add clearly defined circuit variables on your circuit diagrams to assist you in your solution.

1. Consider the circuit below.

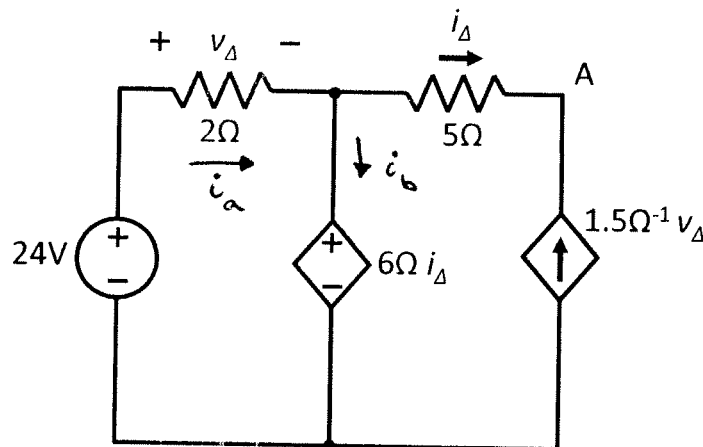

- Write a KVL equation for the left loop in terms of the variables  $v_\Delta$  and  $i_\Delta$ . [1 pt]
- Write a KCL equation for node A in terms of the variables  $v_\Delta$  and  $i_\Delta$ . [1 pt]
- What is the power absorbed by the  $2\Omega$  resistor? [3 pts]
- What is the power absorbed by the  $5\Omega$  resistor? [3 pts]
- What is the power that is delivered or absorbed by the dependent voltage source? [4 pts]

a)  $0 = -24V + v_\Delta + 6\Omega i_\Delta$  [+1]

b)  $0 = -i_\Delta - 1.5\Omega^{-1} v_\Delta$  [+1]

c) Substitution:  $i_\Delta = -1.5\Omega^{-1} v_\Delta$   
 $0 = -24V + v_\Delta + 6\Omega \cdot (-1.5\Omega^{-1}) v_\Delta$   
 $v_\Delta = -3V$  [+1]

$$P_{abs} = \frac{V_{\Delta}^2}{2\Omega} [+1]$$

$$= 4.5 \text{ W } [+1]$$

$$d) \quad i_{\Delta} = -1.5\Omega^{-1} V_{\Delta} = 4.5 \text{ A } [+1]$$

$$P_{abs} = i_{\Delta}^2 \cdot 5\Omega [+1]$$

$$= 101.25 \text{ W } [+1]$$

$$e) \quad \text{Ohm's Law: } V_{\Delta} = i_a \cdot 2\Omega \rightarrow i_a = V_{\Delta} / 2\Omega [+1]$$

$$= -1.5 \text{ A}$$

$$\text{KCL: } 0 = -i_a + i_b + i_{\Delta} [+1]$$

$$i_b = i_a - i_{\Delta}$$

$$= -1.5 \text{ A} - 4.5 \text{ A}$$

$$= -6 \text{ A}$$


$$\text{Power absorbed} = P_{abs} = i_b \cdot 6\Omega i_{\Delta} [+1]$$

$$= (-6 \text{ A}) \cdot (6\Omega \cdot 4.5 \text{ A})$$

$$= -162 \text{ W}$$

or 162 W is delivered by the source [+1]

2. Consider the circuit below.

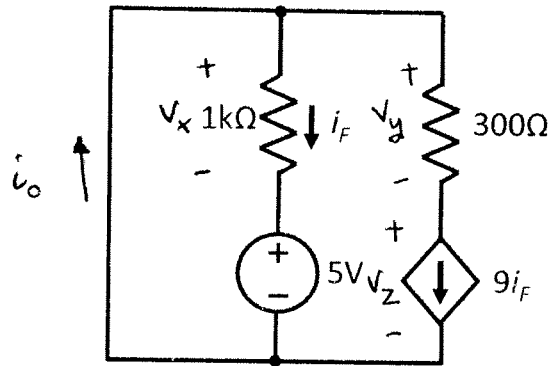

- What is the current  $i_F$ ? Indicate the sign of your answer clearly. [3 pts]
- What is the current flowing through the short circuit in the left-most branch? Indicate clearly both the value and direction of this current. [2 pts]
- What is the power that is delivered or absorbed by the dependent source? [4 pts]

a) KVL on left loop:  $0 = v_x + 5V$  [1]

$$v_x = -5V$$

Ohm's Law:  $i_F = \frac{v_x}{1k\Omega}$  [1]

$$= -5mA$$
 [1]

b) KCL:  $0 = -i_o + i_F + 9i_F$  [1]

$$i_o = 10 i_F$$

$$= -50mA$$
 [1]

work space

c) Ohm's Law and KCL:  $v_y = 9i_F \cdot 300\Omega$  [+1]  
 $= -13.5V$

KVL:  $0 = v_y + v_z$  [+1]  
(exterior loop)  
 $v_z = -v_y$   
 $= 13.5V$


Power absorbed  
by source  $= P_{abs} = 9i_F \cdot v_z$  [+1]  
 $= (9 \cdot -5mA) \cdot 13.5V$   
 $= -607.5mW$

or 607.5mW is delivered by the dependent source. [+1]


NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

1. Consider the circuit below.

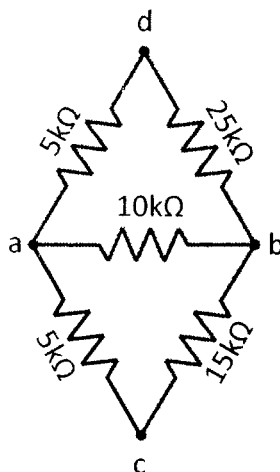


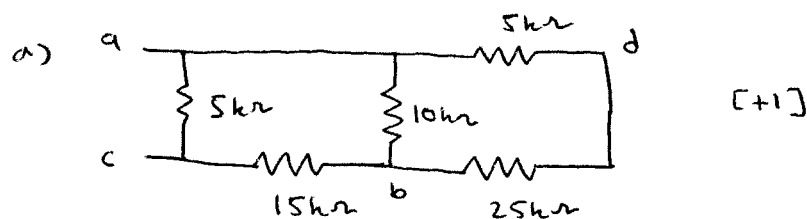- What is the equivalent resistance between nodes a and c? [3 pts]
- What is the equivalent resistance between nodes a and b? [3 pts]
- What is the equivalent resistance between nodes a and d? [3 pts]



$$\begin{aligned}
 R_{ac} &= 5k\Omega // (15k\Omega + 10k\Omega // (5k\Omega + 25k\Omega)) \quad [+1] \\
 &= 5k\Omega // \left(15k\Omega + \frac{10k\Omega \cdot 30k\Omega}{40k\Omega}\right) \\
 &= \frac{5k\Omega \cdot 22.5k\Omega}{27.5k\Omega} \\
 &= 4.091k\Omega \quad [+1]
 \end{aligned}$$

work space

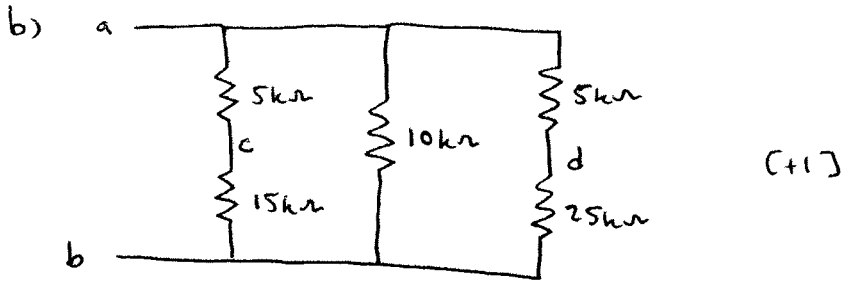


$$R_{ab} = (5+15)k\Omega // 10k\Omega // (5+25)k\Omega \quad (+1)$$

$$= 20k\Omega // 10k\Omega // 30k\Omega$$

$$= \frac{1}{\left(\frac{1}{20k\Omega} + \frac{1}{10k\Omega} + \frac{1}{30k\Omega}\right)}$$

$$= 5.455k\Omega \quad (+1)$$

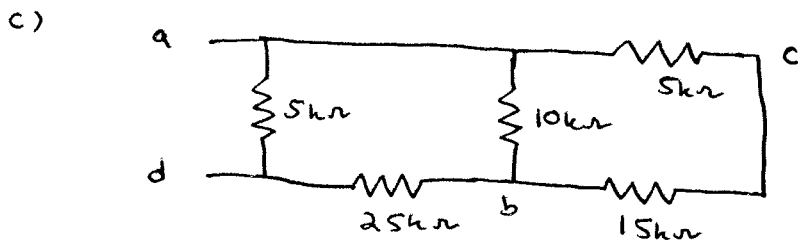

$$R_{ad} = 5k\Omega // (25k\Omega + 10k\Omega // (5k\Omega + 15k\Omega))$$


$$= 5k\Omega // \left(25k\Omega + \frac{10k\Omega \cdot 20k\Omega}{30k\Omega}\right)$$

$$= \frac{5k\Omega \cdot 31.667k\Omega}{36.667k\Omega}$$

$$= 4.318k\Omega$$





2. Consider the following circuit.

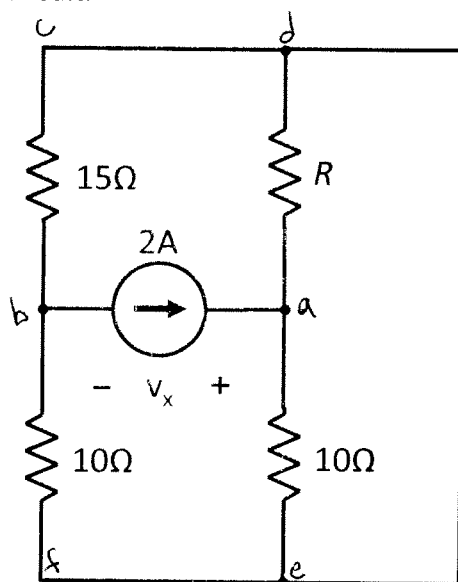

a) If  $R = 15\Omega$ , what is the voltage  $v_x$ ? [4 pts]

**HINT:** You may find it useful to redraw the circuit.

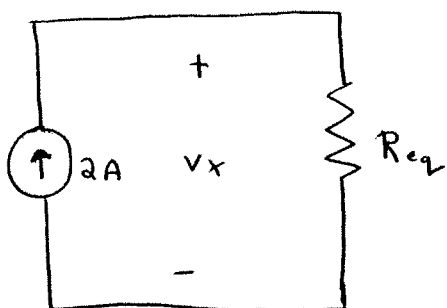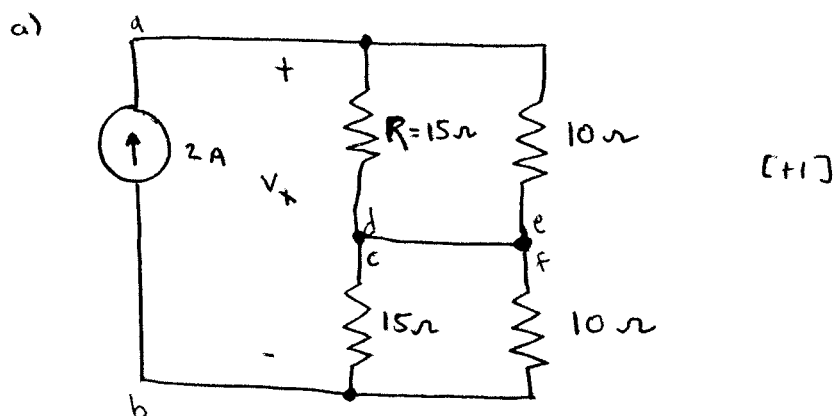b) It is desired that the current source deliver 44W to the circuit. What should the value of  $R$  be in order for this condition to be satisfied? [5 pts]




$$\begin{aligned}
 R_{eq} &= 15\Omega // 10\Omega + 15\Omega // 10\Omega \quad [+1] \\
 &= \frac{15\Omega \cdot 10\Omega}{25\Omega} + \frac{15\Omega \cdot 10\Omega}{25\Omega} \\
 &= 12\Omega
 \end{aligned}$$

$$\begin{aligned}
 v_x &= 2A \cdot R_{eq} \quad [+1] \\
 &= 24V \quad [+1]
 \end{aligned}$$


work space

b)

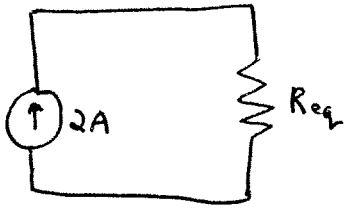

$$P_{del\ source} = P_{abs\ res} = (2A)^2 \cdot R_{eq} \quad [+1]$$
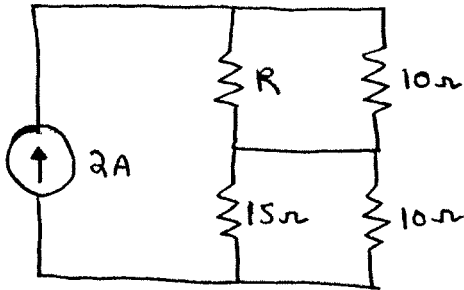
$$R_{eq} = \frac{44W}{(2A)^2} = 11\Omega \quad [+1]$$



$$R_{eq} = R // 10\Omega + 15\Omega // 10\Omega \quad [+1]$$

$$R // 10\Omega = R_{eq} - 15\Omega // 10\Omega$$

$$= 11\Omega - 6\Omega$$

$$= 5\Omega$$

$$\frac{1}{R} + \frac{1}{10\Omega} = \frac{1}{5\Omega} \quad [+1]$$


$$\frac{1}{R} = \frac{1}{5\Omega} - \frac{1}{10\Omega}$$

$$R = 10\Omega \quad [+1]$$

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

1. Consider the circuit below.

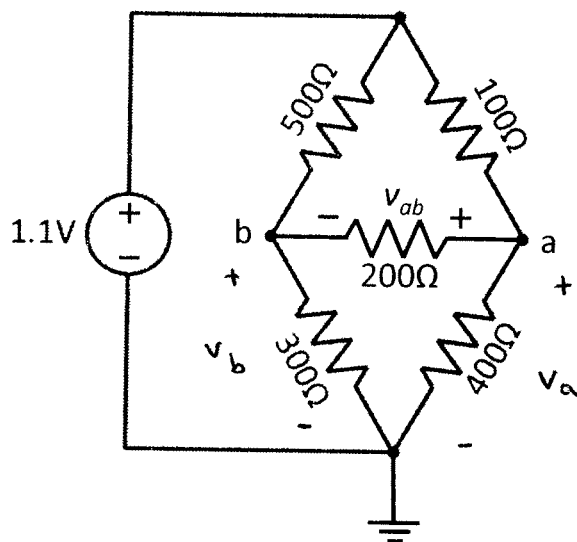

a) What are the node-voltages at the nodes a and b with respect to the identified reference node. [8 pts]

**HINT:** You may find it useful to apply the node-voltage technique.

b) What is the voltage  $v_{ab}$ ? [2 pts]

$$a) \quad 0 = \frac{v_a}{400\Omega} + \frac{v_a - v_b}{200\Omega} + \frac{v_a - 1.1V}{100\Omega}$$

[+1]                      [+1]                      [+1]

$$0 = \frac{v_b}{300\Omega} + \frac{v_b - v_a}{200\Omega} + \frac{v_b - 1.1V}{500\Omega}$$

[+1]                      [+1]                      [+1]

$$\frac{1.1}{100} = v_a \left( \frac{1}{100} + \frac{1}{200} + \frac{1}{400} \right) - v_b \left( \frac{1}{200} \right)$$

$$\frac{1.1}{500} = -v_a \left( \frac{1}{200} \right) + v_b \left( \frac{1}{300} + \frac{1}{200} + \frac{1}{500} \right)$$

work space

$$0.011 = 0.0175 v_a - 0.005 v_b$$

$$0.0022 = -0.005 v_a + 0.0103 v_b$$

$$v_a = \frac{\begin{vmatrix} 0.011 & -0.005 \\ 0.0022 & 0.0103 \end{vmatrix}}{\begin{vmatrix} 0.0175 & -0.005 \\ -0.005 & 0.0103 \end{vmatrix}} = 0.800V \text{ (+)}]$$

$$v_b = \frac{\begin{vmatrix} 0.0175 & 0.011 \\ -0.005 & 0.0022 \end{vmatrix}}{\begin{vmatrix} 0.0175 & -0.005 \\ -0.005 & 0.0103 \end{vmatrix}} = 0.600V \text{ (+)}]$$


b) KVL:  $0 = -v_b - v_{ab} + v_a \text{ (+)}]$

$$v_{ab} = v_a - v_b$$

$$= 0.800V - 0.600V$$

$$= 0.200V \text{ (+)}]$$

2. Consider the following circuit.

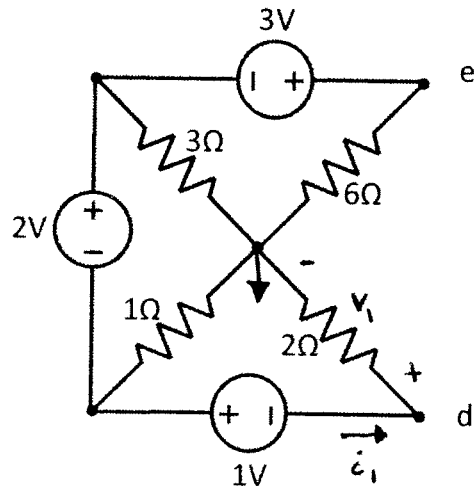

a) What is the voltage across the  $2\Omega$  resistor? Indicate clearly the definition and value of your voltage variable. [5 pts]

**HINT:** You may find it useful to apply the node-voltage technique.

b) How much power does the 1V source deliver or absorb? [3 pts]

c) If a  $12\Omega$  resistor is connected between nodes e and d, how would your answer to part a) change? Justify your answer with an equation or circuit diagram. [1 pt]

a) One supernode equation:

$$0 = \underbrace{\frac{v_1}{2\Omega}}_{[+1]} + \underbrace{\frac{(v_1 + 1V)}{1\Omega}}_{[+1]} + \underbrace{\frac{(v_1 + 1V + 2V)}{3\Omega}}_{[+1]} + \underbrace{\frac{(v_1 + 1V + 2V + 3V)}{6\Omega}}_{[+1]}$$

$$0 = v_1 \left( \frac{1}{2} + 1 + \frac{1}{3} + \frac{1}{6} \right) + \frac{1}{1} + \frac{1+2}{3} + \frac{1+2+3}{6}$$

$$0 = 2v_1 + 3$$

$$v_1 = -1.5V \quad [+1]$$

b)  $i_1 = \frac{v_1}{2\Omega} \quad [+1]$


Power absorbed by source:

$$P_{abs} = 1V \cdot i_1 \quad [+1]$$

$$= 1V \cdot \frac{(-1.5V)}{2\Omega} = -0.75W \quad [+1]$$

or 0.75W is delivered by source.

c)

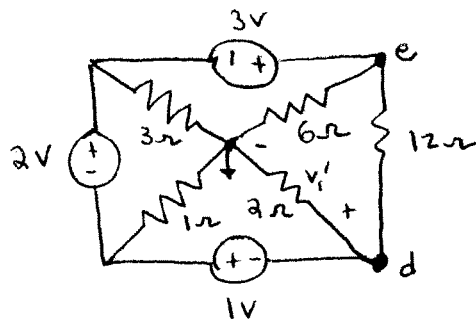


$$\begin{aligned}
 0 = & \frac{v_i'}{2\Omega} + \frac{(v_i' + 1V)}{1\Omega} + \frac{(v_i' + 1V + 2V)}{3\Omega} + \frac{(v_i' + 1V + 2V + 3V)}{6\Omega} \\
 & + \underbrace{\frac{(v_i' - (v_i' + 6V))}{12\Omega}}_{i_{d \rightarrow e}} + \underbrace{\frac{((v_i' + 6V) - v_i')}{12\Omega}}_{i_{e \rightarrow d}}
 \end{aligned}$$

The last two terms cancel, i.e.  $i_{d \rightarrow e} = -i_{e \rightarrow d}$ ,  
 giving the exact same equation for  $v_i'$  as for  $v_i$ .  
 Thus, the voltage across  $2\Omega$  resistor is unchanged. [+1]

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

1. Consider the circuit below.

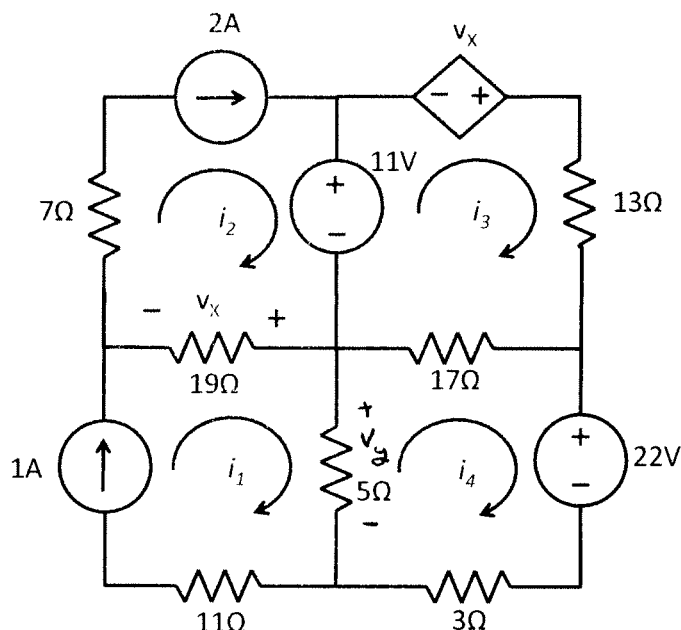

- What is the mesh current  $i_1$ ? [1pt]
- What is the mesh current  $i_2$ ? [1pt]
- What are the mesh currents  $i_3$  and  $i_4$ ? [5pts]
- Would the mesh current  $i_4$  become more positive, more negative, or stay the same if the  $5\Omega$  resistor is replaced with a  $5V$  source having positive terminal pointing towards the top of the page? Justify your answer. [2pts]

a)  $i_1 = 1A$  [1]

b)  $i_2 = 2A$  [1]

c)  $0 = -11V - v_x + 13\Omega i_3 + 17\Omega (i_3 - i_4)$  [1]

$0 = 5\Omega (i_4 - 1A) + 17\Omega (i_4 - i_3) + 22V + 3\Omega i_4$  [1]

$$v_x = \underbrace{19\Omega (i_2 - i_1)}_{= 19V} = 19\Omega (2A - 1A)$$

[1]

work space

Substitution of  $v_x$ :

$$\begin{aligned} 30 &= 30i_3 - 17i_4 \\ -17 &= -17i_3 + 25i_4 \end{aligned}$$



$$i_3 = \frac{\begin{vmatrix} 30 & -17 \\ -17 & 2 \end{vmatrix}}{\begin{vmatrix} 30 & -17 \\ -17 & 25 \end{vmatrix}} = 1A \text{ [+]} \quad i_4 = \frac{\begin{vmatrix} 30 & 30 \\ -17 & -17 \end{vmatrix}}{\begin{vmatrix} 30 & -17 \\ -17 & 25 \end{vmatrix}} = 0A \text{ [+]}$$

$$\begin{aligned} d) \quad v_y &= 5\Omega (i_1 - i_4) \\ &= 5V \text{ [+] } \end{aligned}$$

Replacing the  $5\Omega$  resistor with a  $5V$  source would leave  $i_4$  unchanged, since the voltage drop appearing in the KVL equation for mesh 4 would be unchanged ( $v_y = 5V$ ). [+]



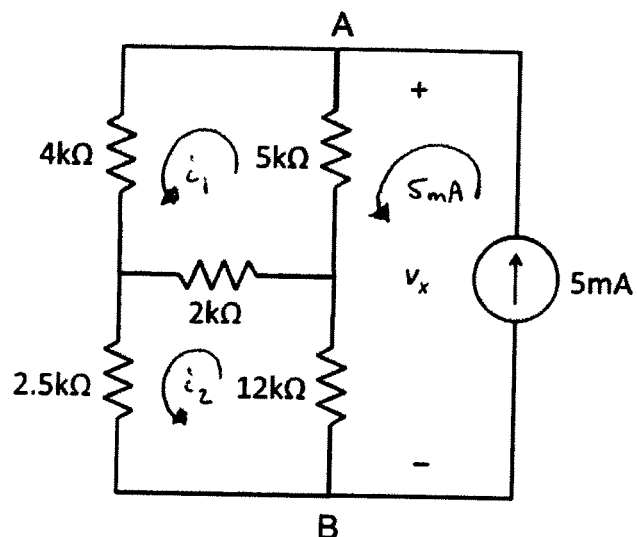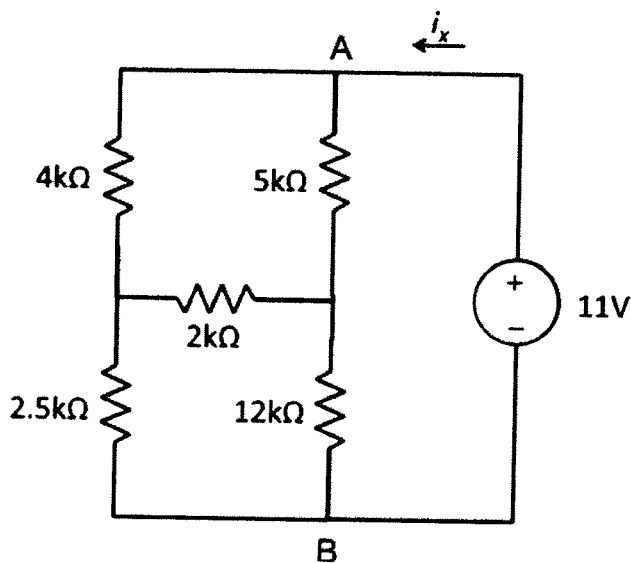2. Consider the following two similar circuits.



- If you are solving for the circuit variables in the **left** circuit, which method requires fewer equations, the node-voltage method or the mesh-current method? [1pt]
- If you are solving for the circuit variables in the **right** circuit, which method requires fewer equations, the node-voltage method or the mesh-current method? [1pt]
- In the **right** circuit, what is the voltage  $v_x$ ? [4pts]
- What is the equivalent resistance of the resistor network between nodes A and B? [2pts]
- What is the current  $i_x$ ? [2 pts]

- 3 mesh variables, 2 node voltage variables  $\rightarrow$  node voltage (+1)
- 2 mesh variables, 3 node voltage variables  $\rightarrow$  mesh current (+1)

$$c) \quad 0 = 5k\Omega(i_1 - 5mA) + 4k\Omega i_1 + 2k\Omega(i_1 - i_2) = 0 \quad (+1)$$

$$0 = 12k\Omega(i_2 - 5mA) + 2k\Omega(i_2 - i_1) + 2.5k\Omega i_2 = 0 \quad (+1)$$

$$25V = 11k\Omega i_1 - 2k\Omega i_2$$

$$60V = -2k\Omega i_1 + 16.5k\Omega i_2$$

$$i_1 = \frac{\begin{vmatrix} 25 & -2000 \\ 60 & 16500 \end{vmatrix}}{\begin{vmatrix} 11000 & -2000 \\ -2000 & 16500 \end{vmatrix}} = 3mA$$


work space

$$i_2 = \frac{\begin{vmatrix} 11000 & 25 \\ -2000 & 60 \end{vmatrix}}{\begin{vmatrix} 11000 & -2000 \\ -2000 & 16500 \end{vmatrix}} = 4 \text{ mA}$$

$$V_x = 5 \text{ k}\Omega (5 \text{ mA} - i_1) + 12 \text{ k}\Omega (5 \text{ mA} - i_2) \quad [+1]$$

$$= 22 \text{ V} \quad [+1]$$


d)

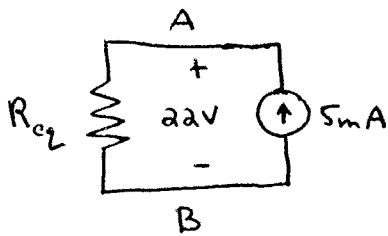

$$R_{eq} = \frac{V_x}{5 \text{ mA}} \quad [+1]$$

$$= \frac{22 \text{ V}}{5 \text{ mA}} = 4.4 \text{ k}\Omega \quad [+1]$$

e)

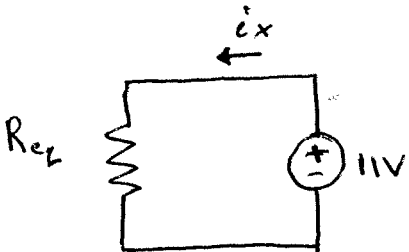


$$i_x = \frac{11 \text{ V}}{R_{eq}} \quad [+1]$$

$$= \frac{11 \text{ V}}{4.4 \text{ k}\Omega} = 2.5 \text{ mA} \quad [+1]$$



NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

1. Consider the circuit below.

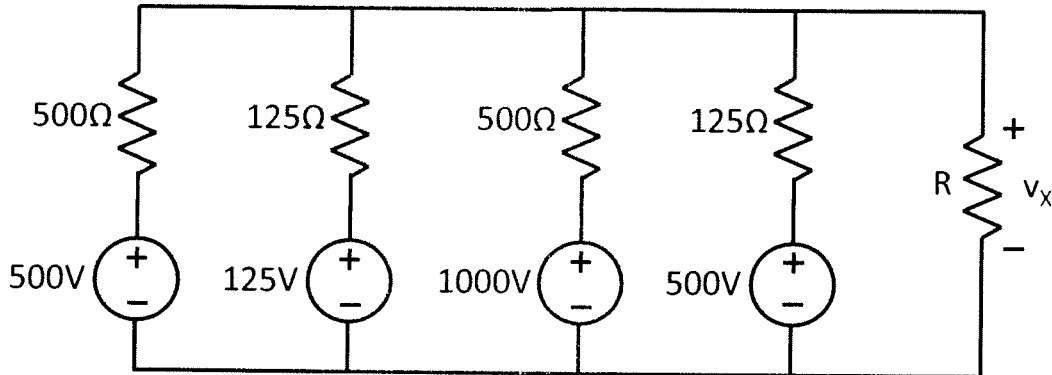

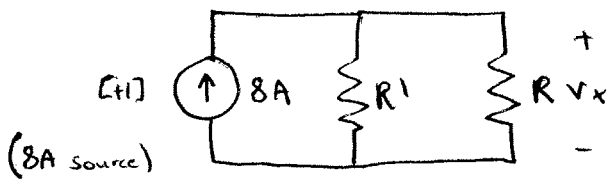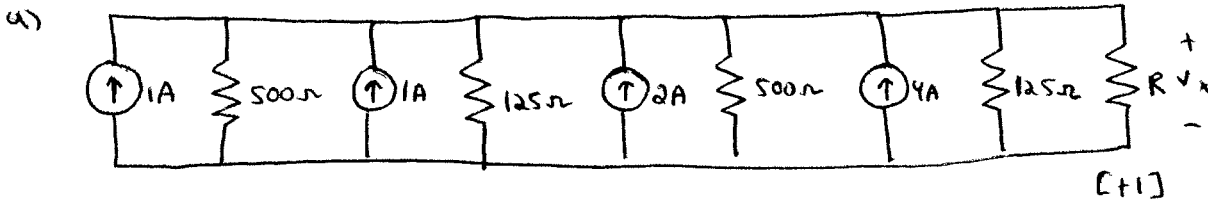
- a) For an arbitrary resistance  $R$ , what is  $v_x$ ? Your answer should include the resistance  $R$ . [4pts]  
 b) What value of  $R$  will give  $v_x = 50V$ ? [2pts]  
 c) For  $1/R = 0\Omega^{-1}$ , what is  $v_x$ ? [2pts]



$$R' = 500\Omega // 125\Omega // 500\Omega // 125\Omega \quad [1]$$

$$\frac{1}{R'} = \frac{1}{500} + \frac{1}{125} + \frac{1}{500} + \frac{1}{125}$$

$$R' = 50\Omega$$

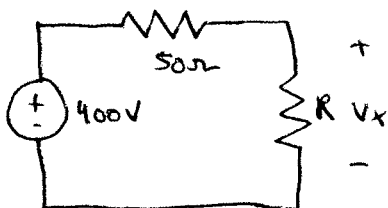

$$v_x = 400V \cdot \frac{R}{R + 50\Omega} \quad [1]$$

$$b) \quad 50V = 400V \frac{R}{R+50\Omega} \quad [+1]$$


$$\frac{1}{8} = \frac{R}{R+50}$$

$$R+50 = 8R$$

$$R = \frac{50}{7} \Omega \quad [+1]$$

$$= 7.143\Omega$$

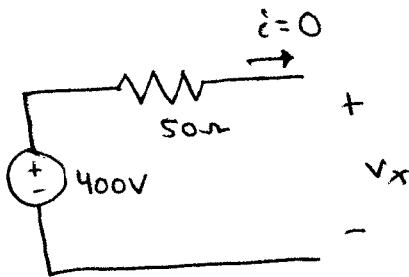c)  $\frac{1}{R} = 0\Omega^{-1}$  is equivalent to an open circuit [+1]




KVL:

$$-400V + 0 \cdot 50\Omega + V_x = 0$$


$$V_x = 400V \quad [+1]$$

2. Consider the following circuit.




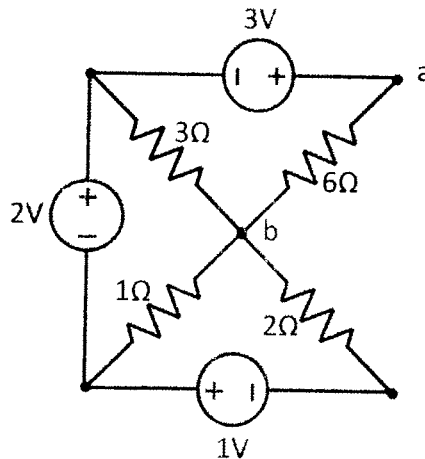


a) Use source transformations and equivalent resistance to find the Thévenin equivalent circuit between the nodes a and b. [8pts]

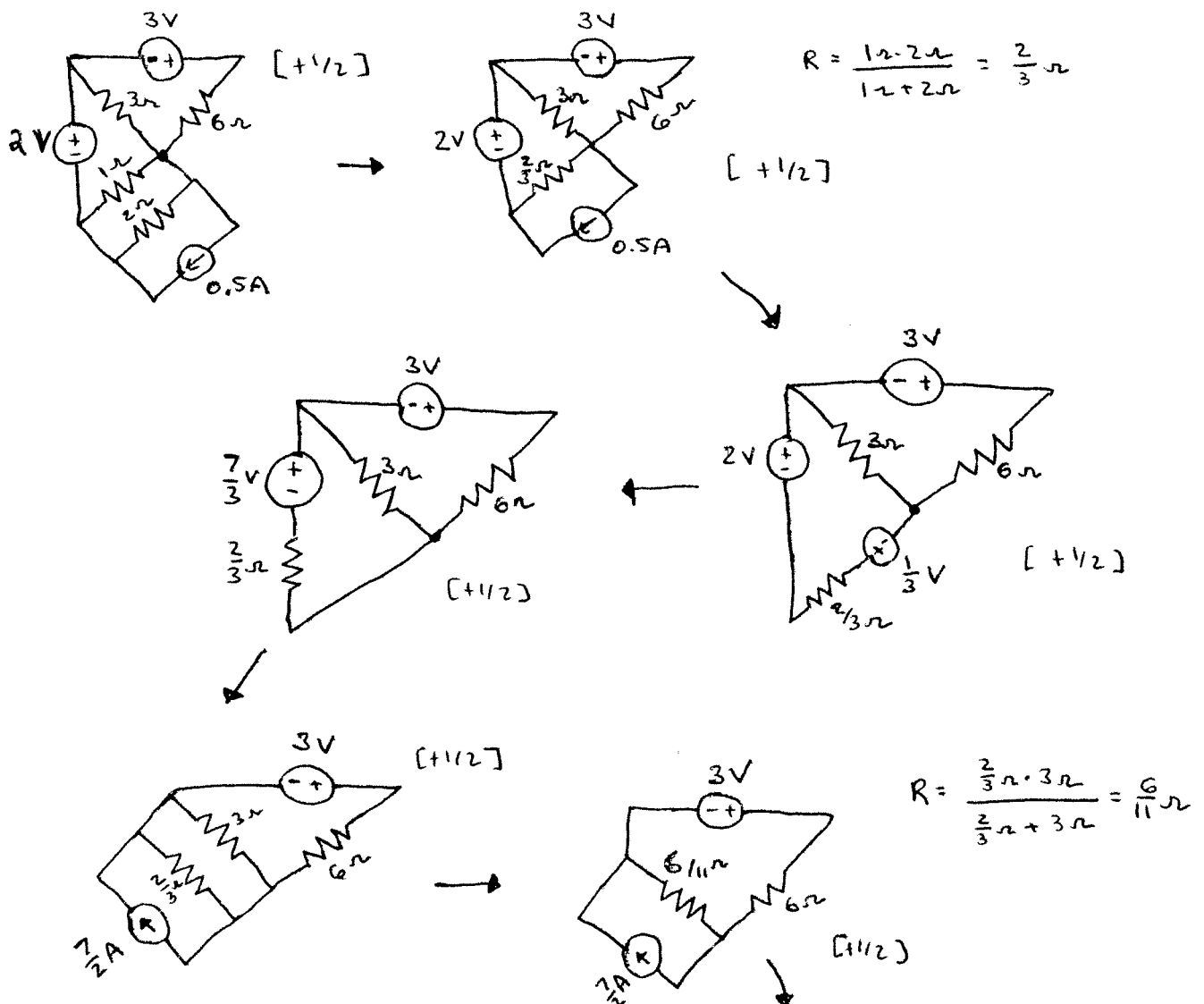b) Consider a short circuit that is applied to nodes a and b; what current will flow through this short circuit? Be sure to indicate the direction of current flow. [2pts]




work space

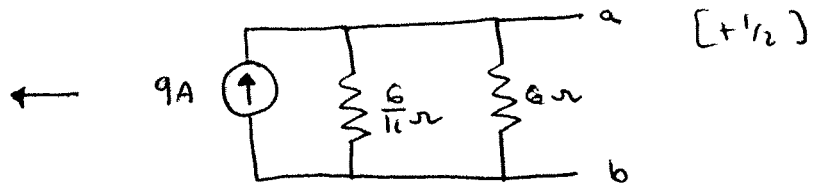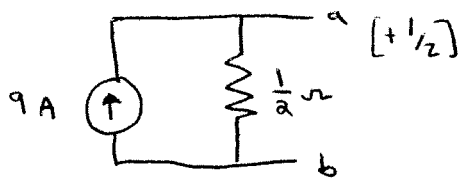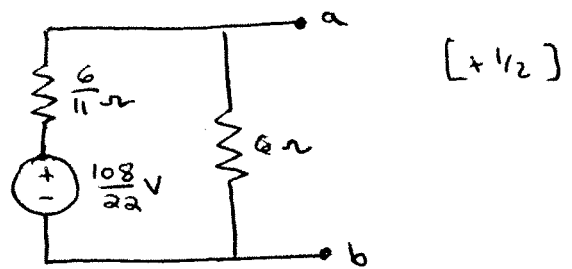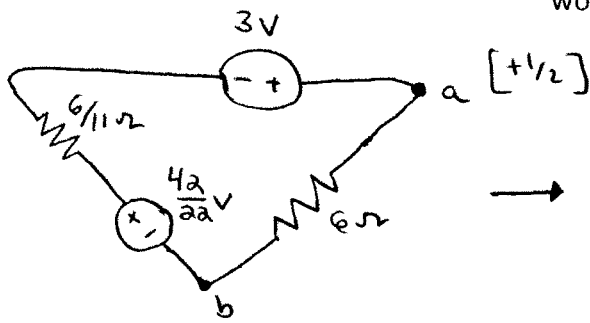


$$R = \frac{6\Omega \cdot \frac{6}{11}\Omega}{6\Omega + \frac{6}{11}\Omega}$$

$$= \frac{36/11}{72/11} \Omega$$

$$= \frac{1}{2} \Omega$$

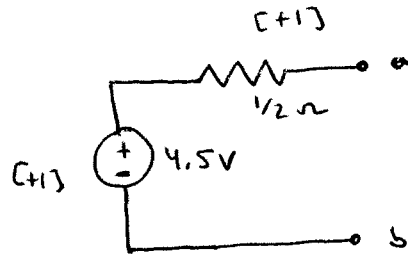

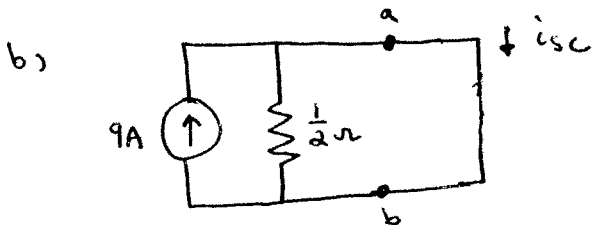[+1] for voltage source and resistor in series]




$$0 = -9A + \frac{0}{1/2\Omega} + i_{sc} \quad [+1]$$

$$i_{sc} = 9A \quad [+1]$$

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_


READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

1. Consider the circuit below.

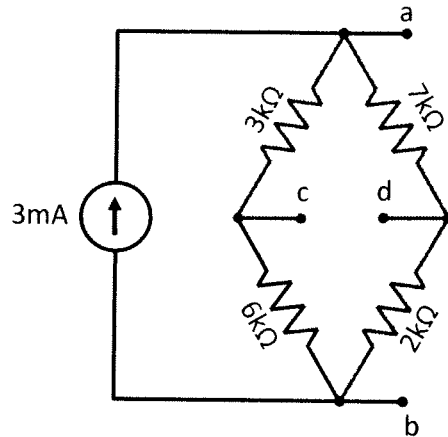


- a) What is the Thévenin equivalent circuit with respect to the terminals a and b? Indicate clearly terminals a and b in your answer. [2pts]  
 b) What is the Thévenin equivalent circuit with respect to the terminals c and d? Indicate clearly terminals c and d in your answer. [5pts]  
 c) If a resistor  $R = 8.888\text{k}\Omega$  is attached between nodes c and d, what voltage will develop across the resistor R? Indicate clearly the polarity of the voltage with respect to terminals c and d. [2 pts]

a)

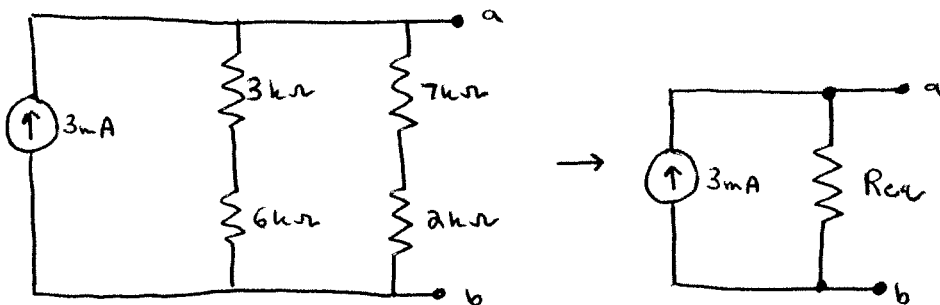


$$R_{th} = (3\text{k}\Omega + 6\text{k}\Omega) \parallel (7\text{k}\Omega + 2\text{k}\Omega) \quad [+1]$$

$$= 4.5\text{k}\Omega$$

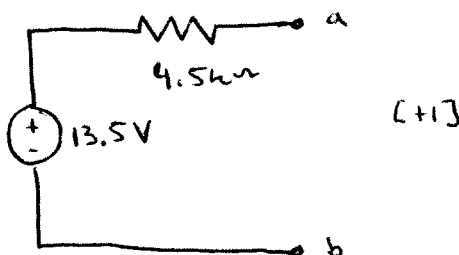

Find  $V_{oc}$ :

b)

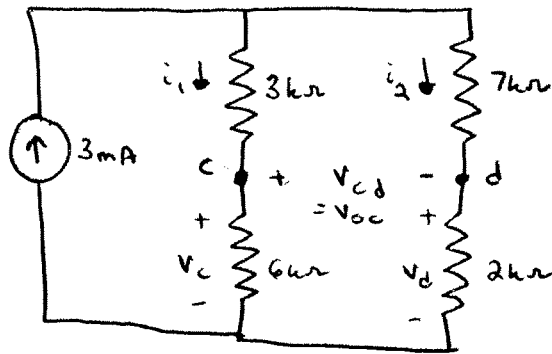

work space


$$i_1 = \frac{3\text{mA} \cdot (7+2)\text{k}\Omega}{((3+6) + (7+2))\text{k}\Omega} = 1.5\text{mA} \quad [+1/2]$$

$$i_2 = \frac{3\text{mA} \cdot (3+6)\text{k}\Omega}{((3+6) + (7+2))\text{k}\Omega} = 1.5\text{mA}$$

$$V_c = i_1 \cdot 6\text{k}\Omega = 9\text{V} \quad [+1/2]$$

$$V_d = i_2 \cdot 2\text{k}\Omega = 3\text{V} \quad [+1/2]$$

Find  $R_T$ :

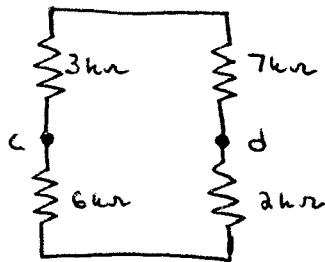


$$\text{KVL: } V_{cd} = V_c - V_d = 6\text{V}$$


$R \quad [+1]$

$$R_T = (3\text{k}\Omega + 7\text{k}\Omega) \parallel (6\text{k}\Omega + 2\text{k}\Omega) \quad [+1]$$
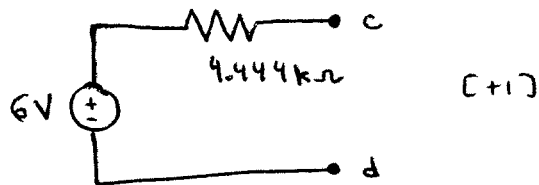
$$= \frac{10\text{k}\Omega \cdot 8\text{k}\Omega}{10\text{k}\Omega + 8\text{k}\Omega} = 4.444\text{k}\Omega$$



c)

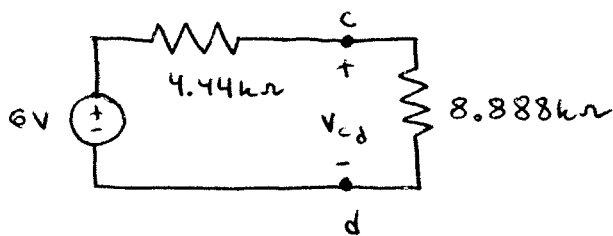


$$V_{cd} = \frac{6\text{V} \cdot 8.888\text{k}\Omega}{4.444\text{k}\Omega + 8.888\text{k}\Omega} \quad [+1]$$

$$= 4\text{V} \quad [+1]$$




2. Consider the following circuit.

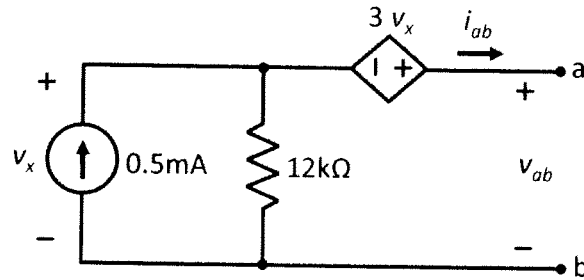

a) Find the Norton equivalent circuit with respect to the terminals a and b. [5pts]

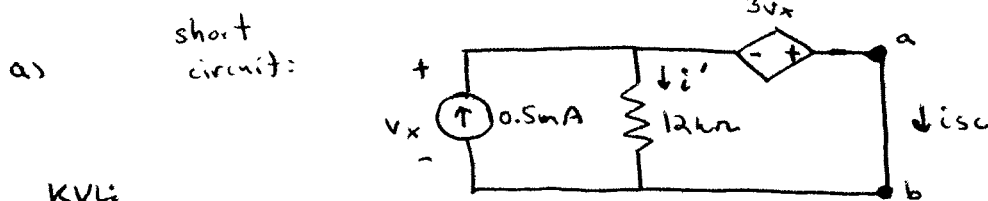b) Find the Norton equivalent circuit with respect to the terminals a and b, if the polarity of the dependent voltage source is reversed (equivalent to a change in the dependent source's controlling equation:  $3v_x \rightarrow -3v_x$ ). [5pts]




KVL:

$$0 = -v_x - 3v_x \quad \text{Ohm: } i' = \frac{v_x}{12k\Omega} = 0mA$$

$$v_x = 0V$$

KCL:  $i_{sc} = 0.5mA$  [+1]

open circuit:

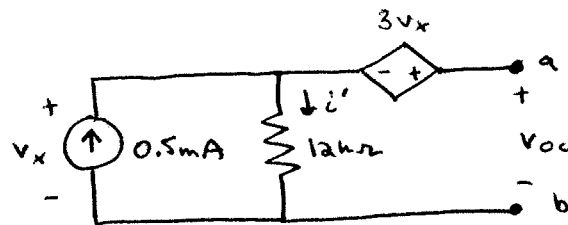


KCL:  $i' = 0.5mA$  [+1]

Ohm:  $v_x = 0.5mA \cdot 12k\Omega = 6V$


KVL:  $0 = -v_x - 3v_x + v_{oc}$

$$v_{oc} = 4v_x = 24V \quad [+1]$$
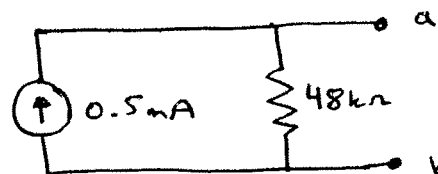
$$R_T = \frac{24V}{0.5mA} = 48k\Omega \quad [+1]$$



b) short circuit:

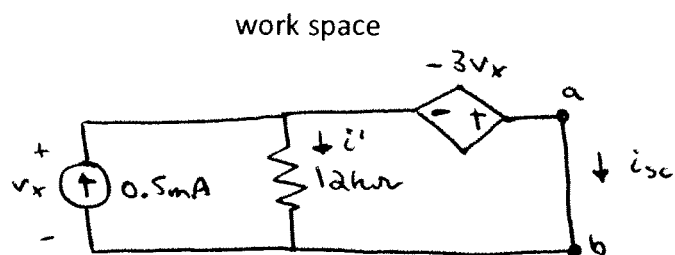

KVL:


$$0 = -v_x - (-3v_x) [+1]$$

$$v_x = 0V$$

Ohm:  $i' = \frac{v_x}{12k\Omega} = 0mA$

KCL:  $i_{sc} = 0.5mA [+1]$

open circuit:

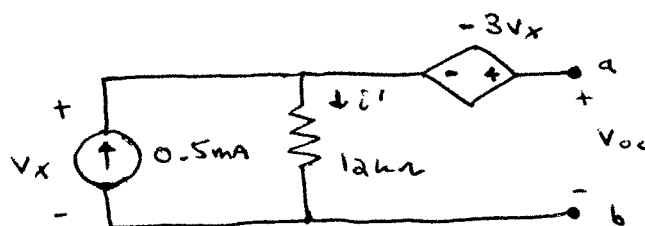

KCL:  $i' = 0.5mA [+1]$


Ohm:  $v_x = 0.5mA \cdot 12k\Omega$   
 $= 6V$

KVL:  $0 = -v_x - (-3v_x) + v_{oc}$

$$v_{oc} = -2v_x$$

$$= -12V [+1]$$

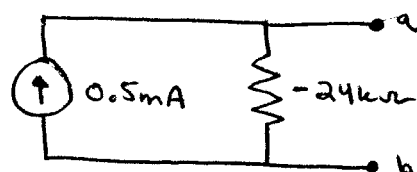
$$R_T = \frac{-12V}{0.5mA} = -24k\Omega [+1]$$



NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_


READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

1. Consider the circuit below.

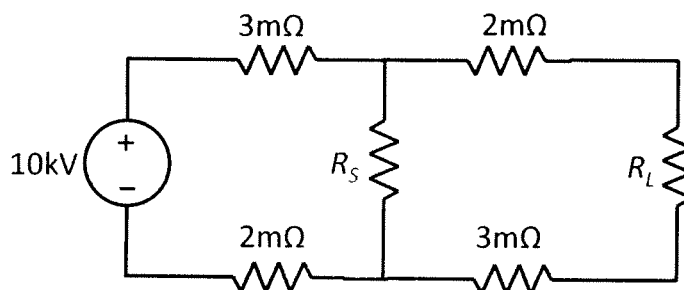


- Under the condition  $R_L = 0\Omega$ , what value should  $R_S$  have in order to maximize the power delivered to  $R_S$  and what is the maximum power that can be delivered to  $R_S$ ? [4pts]
- Under the condition  $1/R_S = 0\Omega^{-1}$ , what value should  $R_L$  have in order to maximize the power delivered to  $R_L$ , and what is the maximum power that can be delivered to  $R_L$ ? [4pts]
- Assume again that  $1/R_S = 0\Omega^{-1}$ . What value should  $R_L$  have in order to maximize the power delivered to  $R_L$ , with the additional constraint that the current through  $R_L$  must be at least 800 kA? [4pts]


a)

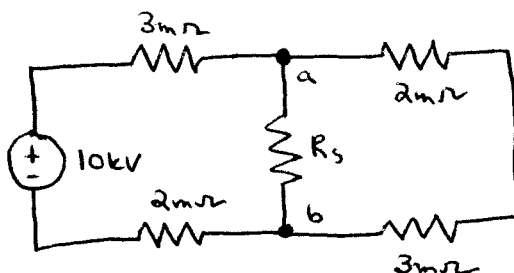

open circuit voltage:

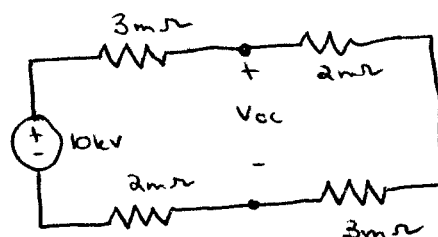

Thévenin resistance

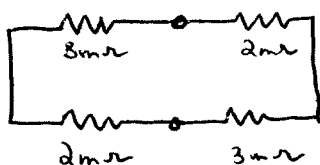

$$V_{OC} = 10kV \cdot \frac{5m\Omega}{5m\Omega + 5m\Omega} \quad [+1]$$

$$= 5kV$$

Maximum power is delivered to  $R_S$  when  $R_S = R_T = 2.5m\Omega$  [+1]


$$R_T = 5m\Omega // 5m\Omega \quad [+1]$$

$$= 2.5m\Omega$$

The maximum power delivered is:

$$P_{max} = \frac{V_{OC}}{2} \cdot \frac{I_{SC}}{2} = \frac{1}{4} V_{OC}^2 / R_T$$

$$= 2.5GW \quad [+1]$$

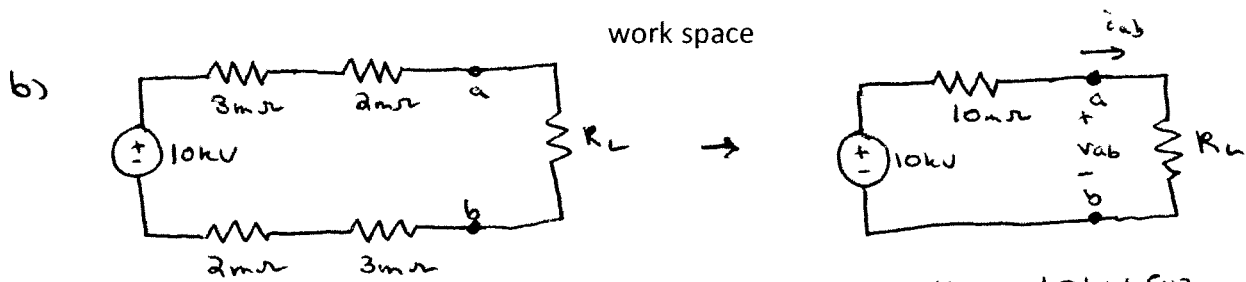

Maximum power is delivered when:


$$R_L = R_T$$

$$= 10m\Omega$$
 [1]

The maximum power delivered is:

$$P = \frac{V_{oc}}{2} \cdot \frac{i_{sc}}{2} = \frac{1}{4} \frac{V_{oc}^2}{R_T} = 2.5 GW$$
 [1]

c)

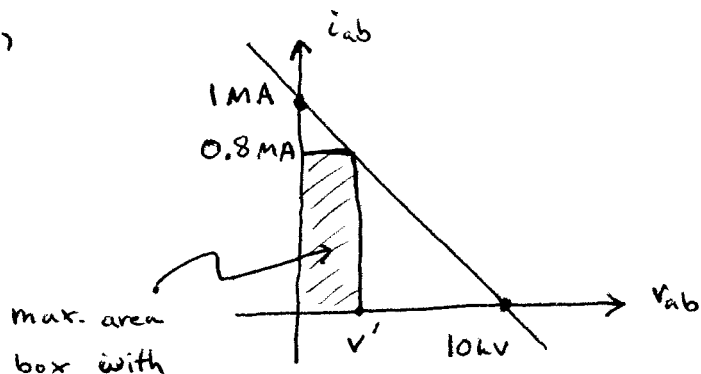

$$i_{sc} = \frac{V_{oc}}{R_T} = \frac{10kV}{10m\Omega} = 1MA$$
 [1]

$$\frac{V'}{10kV} = \frac{1MA - 0.8mA}{1MA}$$

$$V' = 2kV$$
 [1]

$$P_{delivered} = i' \times V'$$

$$= 0.8mA \times 2kV$$


$$= 1.6 GW$$

$$R_L = \frac{V'}{i'}$$

$$= \frac{2kV}{0.8mA}$$

$$= 2.5m\Omega$$
 [1]

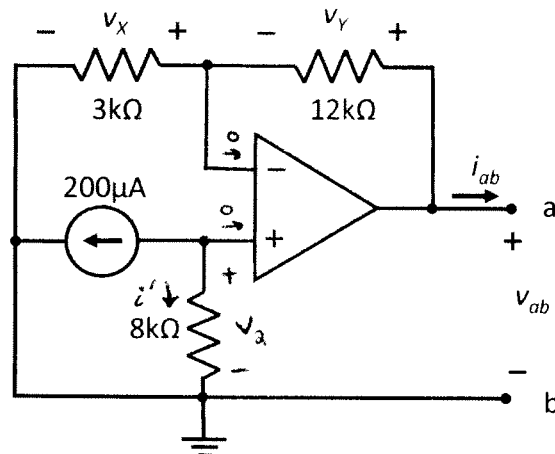2. Consider the following circuit. Assume ideal op-amp behaviour.



- What is the voltage  $v_x$ ? [3pts]
- What is the voltage  $v_y$ ? [2pts]
- What is the voltage  $v_{ab}$ ? [2pts]
- Draw the  $i_{ab}$ - $v_{ab}$  diagram for the above circuit. [2pts]
- With a  $1k\Omega$  resistor connected across the nodes a and b, what is the **total** power that is delivered by the op-amp to the rest of the circuit? [3 pts]

a) ideal op-amp  $\rightarrow$  0A current into input nodes.

$$\text{KCL: } 0 = 200\mu\text{A} + \frac{v_a}{8k\Omega} \quad [+1]$$

$$v_a = -200\mu\text{A} \cdot 8k\Omega = -1.6\text{V}$$

ideal op-amp  $\rightarrow$  input node voltages are equal

$$v_x = v_a \quad [+1]$$

$$v_x = -1.6\text{V} \quad [+1]$$

$$\text{b) KCL: } 0 = \frac{v_x}{3k\Omega} - \frac{v_y}{12k\Omega} \quad [+1]$$


$$v_y = v_x \cdot \frac{12k\Omega}{3k\Omega} = -1.6\text{V} \cdot 4 = -6.4\text{V} \quad [+1]$$

$$\text{c) KVL: } 0 = -v_x - v_y + v_{ab} \quad [+1]$$

$$v_{ab} = v_x + v_y = -8.0\text{V} \quad [+1]$$

work space


d)

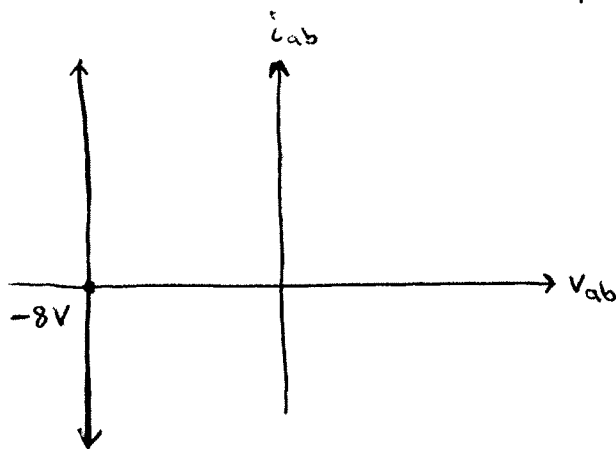

[+1] for vertical line / voltage source behaviour

[+1] for -8V

e/f)

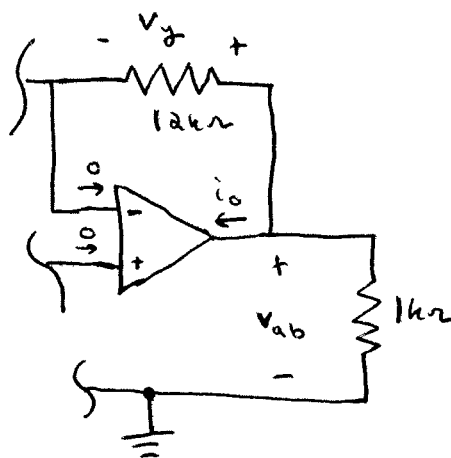

$$\text{KCL: } 0 = i_o + \frac{V_y}{12k\Omega} + \frac{V_{ab}}{1k\Omega} \quad [+1]$$

$$i_o = -\frac{V_y}{12k\Omega} - \frac{V_{ab}}{1k\Omega}$$

$$= -\frac{6.4V}{12k\Omega} - \frac{8V}{1k\Omega}$$

$$= 8.533\text{mA}$$

$$P_{\text{delivered by op-amp}} = -P_{\text{absorbed by op-amp}}$$

$$= - (i_o \cdot V_{ab}) \quad [+1]$$



$$= - (8.533\text{mA} \cdot -8.0V)$$

$$= 68.267\text{mW} \quad [+1]$$

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_


READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

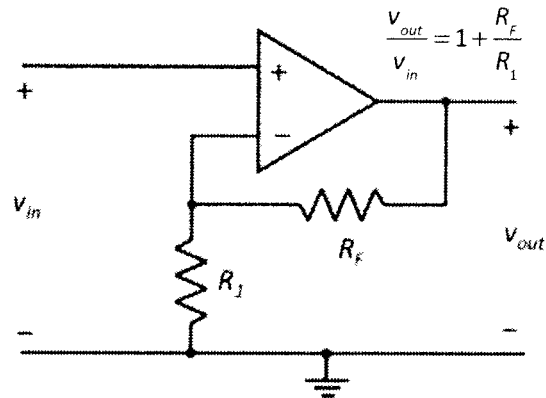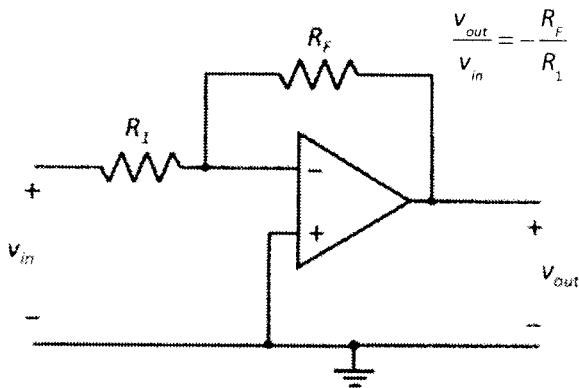1. The circuits below are common operational amplifier circuits. For each design question provide the circuit diagram with resistor values clearly identified. You may assume ideal op-amp behaviour.



- a) Design an op-amp circuit with a voltage gain of  $v_{out}/v_{in} = +5$  and a total power dissipation of 0.5mW when  $v_{out} = +1V$ . [5pts]
- b) Design an op-amp circuit with a voltage gain of  $v_{out}/v_{in} = -5$  and a total power dissipation of 0.5mW when  $v_{out} = +1V$ . [5pts]
- c) Your input signal  $v_{in}$  is produced by a source that has a Thévenin equivalent circuit with  $R_T = 500\Omega$ . If you do not care about the sign of the voltage gain, which of your two op-amp circuits would you select, and why? [BONUS 2pts]

a)

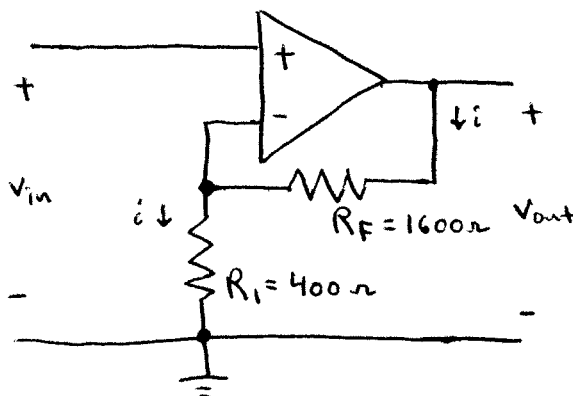

[+2] for configuration

$$\frac{v_{out}}{v_{in}} = 1 + \frac{R_F}{R_1}$$

$$5 = 1 + \frac{R_F}{R_1} \quad [1] \quad \therefore \frac{R_F}{R_1} = 4$$

$$P_{abs} = v_{out} \cdot i$$

$$= \frac{v_{out}^2}{(R_1 + R_F)}$$

$$0.5mW = \frac{1V^2}{R_1 + R_F} \quad [1]$$


$$\therefore R_1 + R_F = \frac{1V^2}{0.5mW} = 2k\Omega$$

$$R_i + R_F = 2k\Omega$$

$$R_F / R_i = 4$$

$$\begin{aligned} 5R_i = 2k\Omega &\rightarrow R_i = 400\Omega \\ R_F = 4R_i &R_F = 1600\Omega \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} [+1]$$

b)

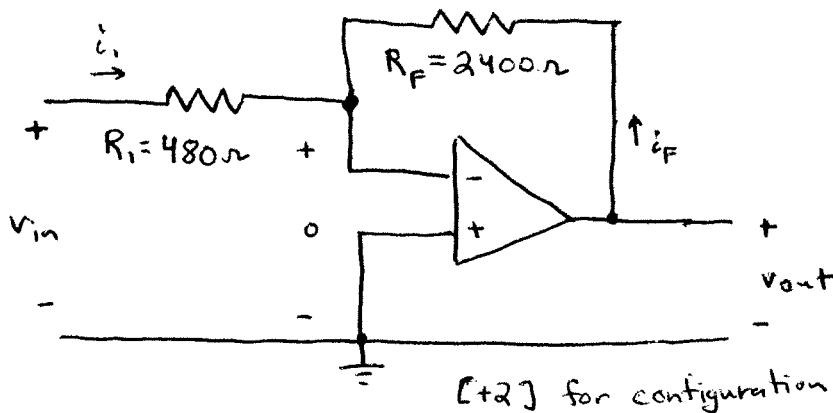

$$\begin{aligned} \frac{v_{out}}{v_{in}} &= -\frac{R_F}{R_i} \\ -S &= -\frac{R_F}{R_i} \quad [+1] \end{aligned}$$

$$P_{abs} = v_{out} \cdot i_F + v_{in} \cdot i_i$$

$$= \frac{v_{out}^2}{R_F} + \frac{v_{in}^2}{R_i}$$

$$0.5mW = \frac{(1V)^2}{R_F} + \frac{(1V/-5)^2}{R_i} \quad [+1]$$

$$\frac{0.5mW}{1V^2} = \frac{1}{R_F} + \frac{1}{25R_i}$$

$$\frac{1}{2k\Omega} = \frac{1}{5R_i} + \frac{1}{25R_i}$$

$$R_i = 2k\Omega \left( \frac{1}{5} + \frac{1}{25} \right)$$


$$R_i = 480\Omega$$

$$R_F = 5R_i = 2400\Omega \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} [+1]$$

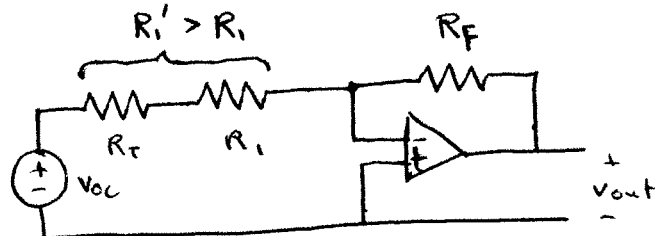c) The non-inverting amplifier is preferable. [+1]

The inverting amplifier gain is effectively reduced by the presence of  $R_T$ . [+1]



$$\frac{v_{out}}{v_{in}} = -\frac{R_F}{R_i + R_T}$$





work space

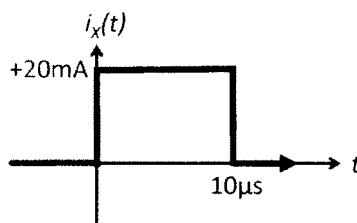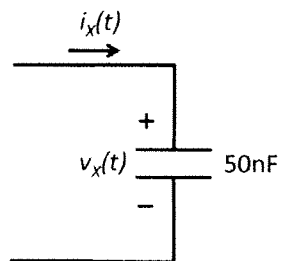2. Consider the following capacitor and specified current pulse. The capacitor is uncharged for  $t < 0$ .




- What is the voltage  $v_x$  for  $t < 0$ ? [1pt]
- What is the voltage  $v_x$  for  $t > 10\text{ }\mu\text{s}$ ? [4pts]
- Plot  $v_x(t)$  versus  $t$ . [3pts]
- How much energy is stored in the capacitor at  $t = 10\text{ }\mu\text{s}$ ? [2pts]
- How much power is delivered to the capacitor at  $t = 5\text{ }\mu\text{s}$ ? [BONUS 2pts]

a)  $v_x = 0\text{ V}$  [1]   
 for  $t < 0$

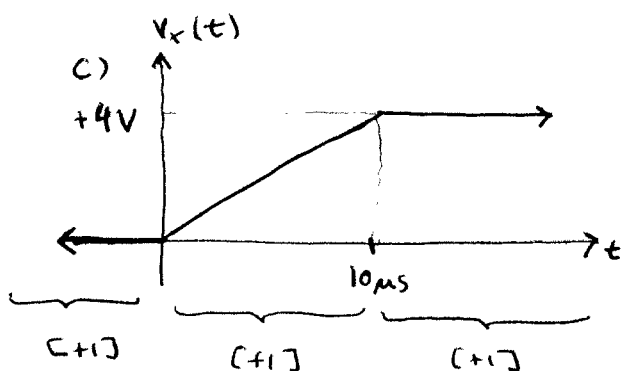b)  $q_{0 \rightarrow 10\text{ }\mu\text{s}} = \int_0^{10\text{ }\mu\text{s}} i_x(t) dt$  [1]   
  $= 20\text{ mA} \cdot 10\text{ }\mu\text{s}$    
  $= 200\text{ nC}$  [1]

$q_{0 \rightarrow 10\text{ }\mu\text{s}} = C \cdot v_x$  [1]

$v_x = \frac{200\text{ nC}}{50\text{ nF}} = 4\text{ V}$  [1]



d)  $U = \frac{1}{2} C v_x^2$  [1]   
  $= \frac{1}{2} \cdot 50\text{ nF} \cdot (4\text{ V})^2 = 400\text{ nJ}$  [1]



e)  $P_{\text{del. to cap.}} = v_x \cdot i_x \big|_{t=5\text{ }\mu\text{s}}$  [1]   
  $= 2\text{ V} \cdot 20\text{ mA}$    
  $= 40\text{ mW}$  [1]

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

1. Consider the circuits below. You may assume ideal op-amp behaviour.

$$v_o(t) = -RC \frac{d}{dt} v_i(t)$$

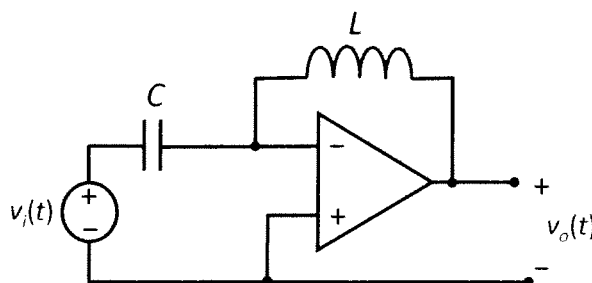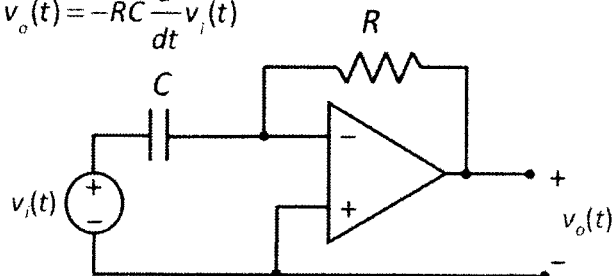

a) An ac input voltage  $v_i(t) = A_i \cos(2\pi ft)$  is applied to the input of the left circuit, where the amplitude  $A_i = 1V$ . At what frequency  $f$  is the amplitude of the resulting ac output voltage  $v_o(t)$  also equal to 1V? [3pts]

b) Design the op-amp circuit on the left, giving the value of  $R$  and  $C$ , according to the following specifications. When the input voltage increases at 400mV/ms, the current drawn from the input voltage source should be 100μA and the output voltage should be  $v_o = -1V$ . [4pts]

c) For the circuit on the right, express the output voltage  $v_o(t)$  in terms of the input voltage  $v_i(t)$ . [3pts]

d) Design the op-amp circuit on the right, giving the value of  $L$  and  $C$ , according to the following specifications. The current drawn from the input voltage source should be 100μA when the input voltage increases at 1V/ms. With an ac input voltage  $v_i(t) = A_i \cos(2\pi ft)$ , the amplitude of the ac output voltage should be equal to the input amplitude  $A_i$  at a frequency  $f = 10\text{kHz} = 10^4\text{s}^{-1}$ . [BONUS 4pts]


$$a) \quad v_o = -RC \frac{d}{dt} (A_i \cos(2\pi ft)) \quad [+1]$$

$$= -RC A_i 2\pi f \cdot \sin(2\pi ft)$$

$$\underbrace{\quad}_{A_o = R C A_i \cdot 2\pi f} \quad [+1]$$

$$f = \frac{1}{2\pi RC} \quad [+1]$$

b)

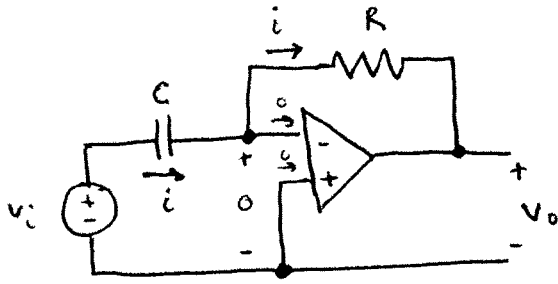

work space


$$i = C \frac{dv_i}{dt}$$

$$C = \frac{i}{dv_i/dt} = \frac{100 \mu A}{400 mV/ms} = 250 nF \quad [+1]$$

$$v_o = -RC \frac{dv_i}{dt} = -Ri$$

$$R = \frac{-v_o}{i} = \frac{-(-1V)}{100 \mu A} = 10 k\Omega \quad [+1]$$

c)

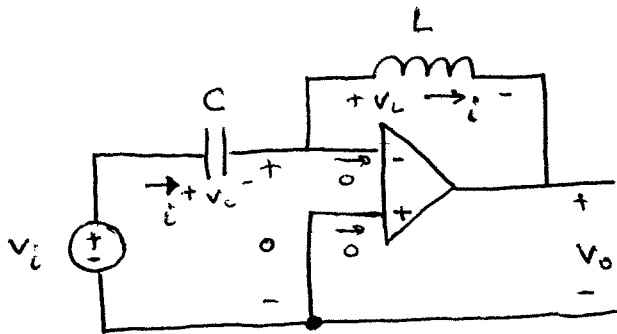

$$\text{KVL: } v_c = v_i \quad v_L = -v_o$$

$$i = C \frac{dv_i}{dt} \quad [+1]$$

$$v_L = L \frac{di}{dt} \quad [+1]$$

$$\therefore v_o = -v_L = -L \frac{di}{dt}$$

$$= -L \frac{d}{dt} \left( C \frac{dv_i}{dt} \right)$$

$$= -LC \frac{d^2 v_i}{dt^2} \quad [+1]$$

$$d) \quad i = C \frac{dv_i}{dt}$$

$$C = \frac{i}{dv_i/dt} = \frac{100 \mu A}{1V/ms} = 100 \text{ nF}$$

[+1]

$$v_i = A_i \cos(2\pi f t)$$

$$v_o = -LC \frac{d^2}{dt^2} (A_i \cos(2\pi f t))$$

$$= -LC - A_i \cdot (2\pi f)^2 (-\cos(2\pi f t))$$

$$= LC A_i (2\pi f)^2 \cos(2\pi f t) \quad [+1]$$

$$\underbrace{\hspace{10em}}_{A_o}$$


$$\frac{A_o}{A_i} = LC (2\pi f)^2 = 1$$

$$L = \frac{1}{C \cdot (2\pi f)^2}$$

$$= \frac{1}{100 \text{ nF} \cdot (2\pi \cdot 10^4 \text{ s}^{-1})^2}$$

$$= 2.533 \text{ mH} \quad [+1]$$

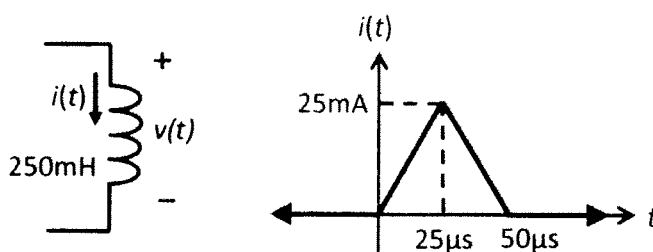
2. Consider the following inductor and specified current pulse.



- What is the voltage  $v$  at  $t=10\mu s$ ? [2pts]
- What is the voltage  $v$  at  $t=40\mu s$ ? [2pts]
- Plot  $v(t)$  versus  $t$ . [4pts]
- What is the energy stored by the inductor at  $t=40\mu s$ ? [2pts]

$$a) \quad v = L \frac{di}{dt} = 250 \text{ mH} \cdot \frac{25 \text{ mA}}{25 \mu s} = +250 \text{ V} \quad [1]$$
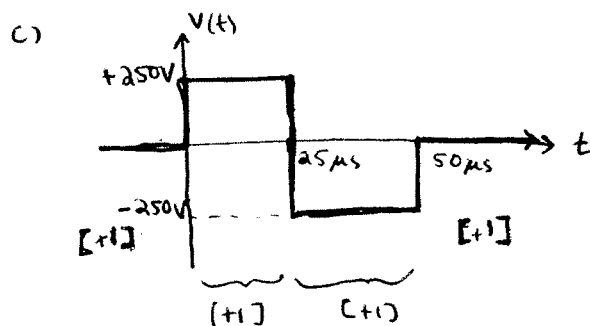
$$b) \quad v = L \frac{di}{dt} = 250 \text{ mH} \cdot \frac{-25 \text{ mA}}{25 \mu s} = -250 \text{ V} \quad [1]$$




$$d) \quad i = \frac{10 \mu s}{25 \mu s} \times 25 \text{ mA} = 10 \text{ mA}$$

$$U = \frac{1}{2} L i^2 = \frac{1}{2} \cdot 250 \text{ mH} \cdot (10 \text{ mA})^2 = 12.5 \mu \text{ J} \quad [1]$$

NAME \_\_\_\_\_ McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

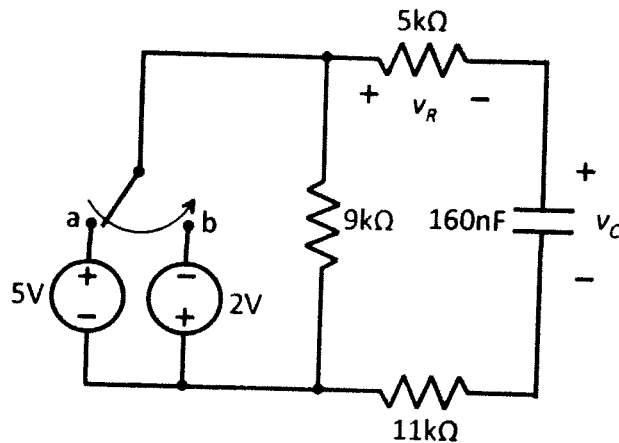
1. Consider the circuit below. The switch moves from position a to position b instantaneously at  $t=0$ . The circuit is in dc steady state for  $t < 0$ .



- a) What is the voltage  $v_C(t)$  for  $t > 0$ ? [6pts]  
 b) What is the voltage  $v_R(t)$  for  $t > 0$ ? [4pts]  
 c) At what time  $t$  is the energy stored by the capacitor a minimum? [BONUS 4pts]


a)  $t < 0$ ,

$$V_C(0^-) = V_C(0^+) = 5V \quad [+1]$$

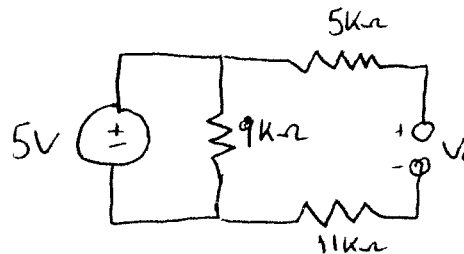

$t > 0$ ,

$$V_C(\infty) = -2V \quad [+1]$$

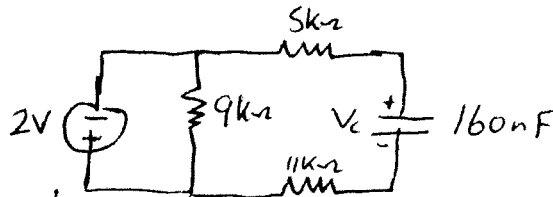

$$V_C(t) = V_C(\infty) + [V_C(0^+) - V_C(\infty)]e^{-t/\tau} \quad [+1]$$

$$\tau = R_{eq}C$$

$$R_{eq} = 5k\Omega + 11k\Omega = 16k\Omega \quad [+1]$$

$$\Rightarrow \tau = 2.56 \text{ ms} \quad [+1]$$

$$\Rightarrow V_C(t) = -2 + 7e^{-\frac{t}{2.56 \text{ ms}}} \text{ V}, \quad t > 0 \quad [+1]$$


work space

$$\begin{aligned}
 b) \quad i(t) &= C \frac{dV_C(t)}{dt} \quad [+1] \\
 &= (160 \text{ nF}) \left[ -\frac{1}{2.56 \times 10^{-3}} \cdot 7 \cdot e^{-\frac{t}{2.56 \times 10^{-3}}} \right] \\
 &= -437.5 e^{-\frac{t}{2.56 \times 10^{-3}}} \mu\text{A} \quad [+1]
 \end{aligned}$$

$$\begin{aligned}
 V_R(t) &= i(t) R_{\text{skz.}} \quad [+1] \\
 &= \boxed{-2.1875 e^{-\frac{t}{2.56 \times 10^{-3}}} \text{ V}, t > 0} \quad [+1]
 \end{aligned}$$

$$c) \quad U = \frac{1}{2} C V_C^2 \quad [+1]$$

minimum energy occurs at minimum  $|V_C|$

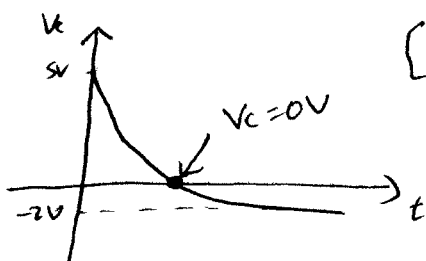

[+1]

$$-2 + 7e^{-\frac{t}{2.56 \text{ ms}}} = 0$$


$$e^{-\frac{t}{2.56 \text{ ms}}} = \frac{2}{7} \quad [+1]$$

$$\frac{-t}{2.56 \text{ ms}} = \ln\left[\frac{2}{7}\right]$$

$$\Rightarrow \boxed{t = 3.207 \text{ ms}} \quad [+1]$$



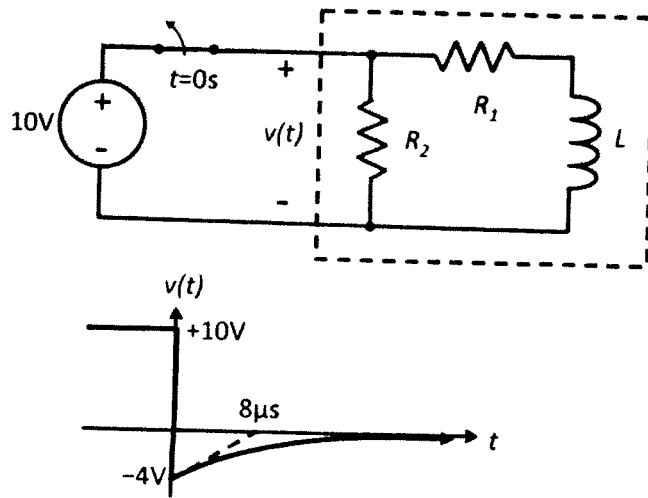2. Consider the following circuit and voltage  $v(t)$ . The switch opens instantaneously at  $t=0$ . The circuit is in dc steady state for  $t<0$ . It is also known that 3.5mA is delivered by the independent source for  $t<0$ .




What are the values of  $R_1$ ,  $R_2$  and  $L$ ? [10 pts]

$t < 0,$   
 $R_{eq} = \frac{10V}{3.5mA}$


$$= R_1 // R_2 = 2857 \Omega$$
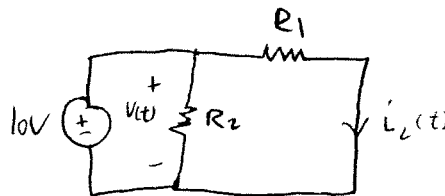
$$i_L(0^-) = i_L(0^+) = \frac{10}{R_1} \quad [+2]$$



$t > 0,$
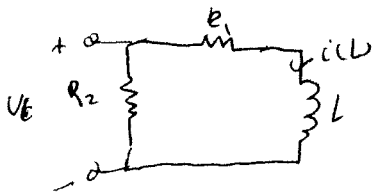
$$v(0^+) = -4V \quad (\text{from } v(t) \text{ vs. } t \text{ plot})$$



$$\frac{-4}{R_2} + i_L = 0 \quad [+2]$$

$$\Rightarrow i_L(0^+) = \frac{4}{R_2}$$


$$\Rightarrow \frac{10}{R_1} = \frac{4}{R_2} \Rightarrow R_2 = 0.4 R_1 \quad [+1]$$

Using  $R_1 // R_2 = 2857 \Omega$  and  $R_2 = 0.4 R_1$

$$\Rightarrow R_1 = 10k\Omega, R_2 = 4k\Omega \quad [+1]$$

work space

$$\tau = \frac{L}{R_t} \quad [+1]$$

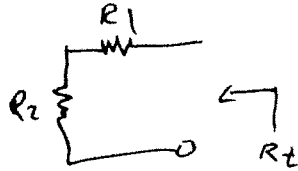

$$\Rightarrow R_t = R_1 + R_2 \quad [+1]$$
$$= 14 \text{ k}\Omega$$

$$\Rightarrow L = R_t \tau$$


$$= (14 \text{ k}\Omega) (8 \mu\text{s}) \quad \rightarrow \text{(from } v(t) \text{ vs. } t \text{ plot)}$$

$$= 0.112 \text{ H} \quad [+1]$$

NAME Answer Key McGill ID# \_\_\_\_\_

READ each question and its parts carefully before starting. SHOW ALL YOUR WORK. Give units on your answers (where appropriate).

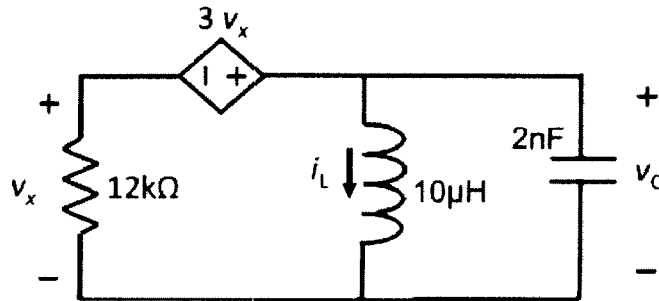1. Consider the circuit below. Recall that  $\omega_0 = (LC)^{-1/2}$  and  $\alpha = 1/(2RC)$  for a parallel RLC circuit.



a) Simplify the above circuit to a parallel RLC circuit. [3 pts]

b) Find the characteristic equation for the above circuit. [3 pts]


**HINT:** You may find it useful to apply the operator method.

c) What are the roots  $s_1$  and  $s_2$  of the characteristic equation? [2pts]

d) Is the above circuit over-damped, critically damped, or under-damped? [2 pts]

e) If it is known that  $i_L(0) = 1\text{mA}$  and  $v_c(0) = 0\text{V}$ , what is the natural response  $i_L(t)$  for  $t > 0$ .


[ BONUS 4pts ]

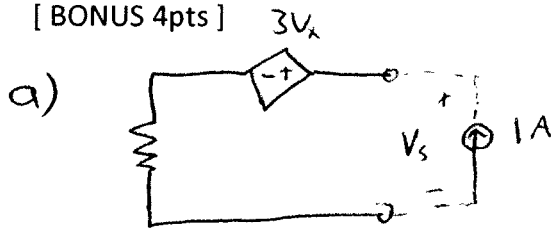

$$V_x = 12\text{KV}$$

$$V_s = 3V_x + V_x = 4V_x = 48\text{KV}$$
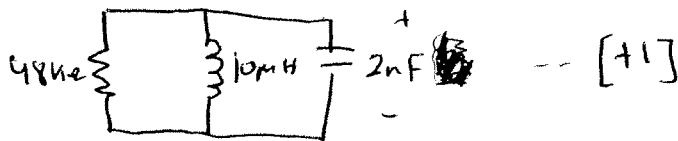
$$\Rightarrow R_t = 48\text{K}\Omega \quad 48\text{K}\Omega \quad \dots [+2]$$



b)

$$\frac{V_c}{48\text{K}\Omega} + i_L + C \frac{dv_c}{dt} = 0$$

$$V_c = L \frac{di_L}{dt} = 10\mu\text{H} \frac{di_L}{dt}$$

$$\frac{10\mu\text{H}}{48\text{K}\Omega} \frac{di_L}{dt} + i_L + 2\text{nF} \cdot 10\mu\text{H} \frac{d^2 i_L}{dt^2} = 0 \quad [+1]$$

$$s^2 + 10.42 \cdot 10^3 s + 50 \cdot 10^{12} = 0 \quad [+2]$$

$$c) s_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$\Rightarrow s_{1,2} = -5.21 \cdot 10^3 \pm j 7.07 \cdot 10^6 \quad [+2]$$

d)  $s_{1,2}$  are imaginary  $\Rightarrow$  circuit is under-damped  $[+2]$

$$e) i_L(t > 0) = e^{-\alpha t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)]$$

$$\alpha = \frac{1}{2RC} = 5.21 \cdot 10^3 \quad [+1/2]$$

$$\omega_d = 7.07 \cdot 10^6 \quad [+1/2]$$


$$i_L(0) = I_m A = A_1 \quad [+1/2]$$

$$V_L(0) = 0 = L \frac{di_L(0)}{dt}$$

$$\Leftrightarrow \frac{di_L(0)}{dt} = 0 = -\alpha A_1 + \omega_d A_2 \Leftrightarrow A_2 = \frac{\alpha A_1}{\omega_d} = 737_n A \quad [+1/2]$$

$$\Rightarrow i_L(t > 0) = e^{-5.21 \cdot 10^3 t} [I_m A \cdot \cos(7.07 \cdot 10^6 t) + 737_n A \cdot \sin(7.07 \cdot 10^6 t)] \quad [+2]$$

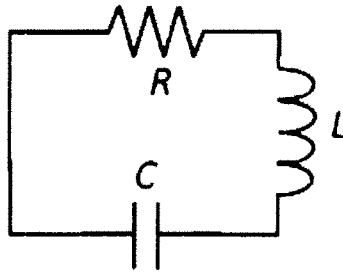2. Consider the following circuit. and voltage  $v(t)$ . Recall that  $\omega_0 = (LC)^{-1/2}$  and  $\alpha = R/(2L)$  for a series RLC circuit.



- a) Specify the value of  $R$  and  $L$  in the circuit above such that critically damped response with  $s_1 = s_2 = -10^4 \text{ rad/s}$  is obtained using a  $C = 250 \text{ nF}$  capacitor. [4 pts]  
 b) Specify the value of  $R$  and  $C$  in the circuit above such that under-damped response is obtained with: undamped resonant frequency  $\omega_0 = 10^6 \text{ rad/s}$ , damping coefficient  $\alpha = 10^3 \text{ rad/s}$ , and an inductance  $L = 600 \text{ nH}$ . [4 pts]  
 c) What is the damped resonant frequency  $\omega_d$  for the circuit specified in part b)? Give your answer in rad/s. [2pts]

a) For a critically damped response,

$$s_1 = s_2 = -\alpha \quad [+1]$$

$$\Rightarrow s_1 = s_2 = -\frac{R}{2L}$$

$$\Rightarrow -10^4 = -\frac{R}{2L} \quad \Rightarrow \frac{R}{L} = 2 \times 10^4 \quad [+1]$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

We use  $s^2 + 2\alpha s + \omega_0^2 = 0$  to find  $\omega_0$

$$\Rightarrow s^2 + 2\alpha s + \omega_0^2 = 0$$

$$(-10^4)^2 + 2(10^4)(-10^4) + \omega_0^2 = 0$$

$$\Rightarrow \omega_0^2 = 10^8$$

$$\Rightarrow \omega_0 = 10^4 \text{ rad/s} \quad [+1]$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \Rightarrow 10^8 = \frac{1}{LC}$$

$$\Rightarrow L = 0.04 \text{ H} \quad [+1] \Rightarrow R = 800 \Omega \quad [+1]$$

work space

$$b) \omega_0 = \frac{1}{\sqrt{LC}}$$

$$10^6 = \frac{1}{\sqrt{LC}} \Rightarrow \frac{1}{LC} = 10^{12}$$

$$\Rightarrow C = 1.6 \mu F \quad [+2]$$

$$\alpha = \frac{R}{2L}$$

$$\Rightarrow 10^3 = \frac{R}{(2)(600nH)}$$

$$\Rightarrow R = 1.2 \times 10^{-3} \Omega \quad [+2]$$

c)  $\omega_d$  for under-damped response

$$\omega_d = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad [+1]$$

$$= \sqrt{10^6 - 10^{12}}$$

$$\approx 10^6 j \text{ rad/s} \quad [+1]$$