

PS #4 PRACTICAL AMMETER PROBLEM


①

- 1) D'ARSONVAL GALVANOMETER
 Full-scale current (i_{fs}) of 1mA
 Internal resistance (R_m) of 50 Ω
 Measured current (i_m)

Ratio of measured current i_m
 to current i_A (using current division)

$$i_A = i_m \frac{R_p}{R_m + R_p}$$
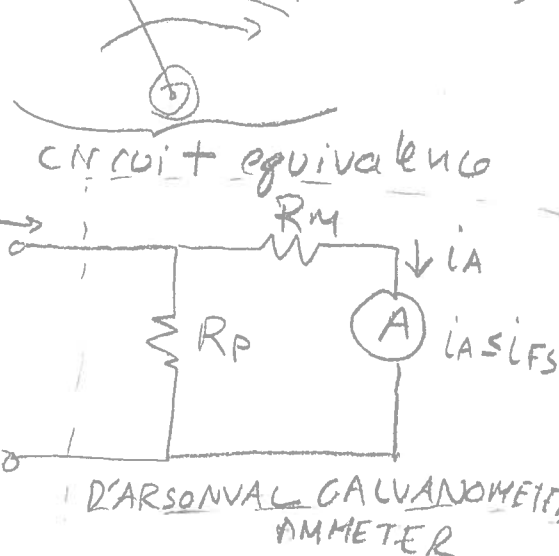
$$i_m = i_A \left(\frac{R_m + R_p}{R_p} \right) = i_A \left(1 + \frac{R_m}{R_p} \right)$$



- a) We want to measure up to 1mA. Since the full-scale is 1mA, we can measure the current directly without R_p .
 An open circuit is the same as $R_p \rightarrow \infty$
 $i_m = i_A \left(1 + \frac{R_m}{\infty} \right)$
 $i_m = i_A$
 $R_p = \infty$

- b) We want to measure up to 10.0mA ($i_m = 10.0mA$).
 At that i_m , we will reach full-scale $\rightarrow i_A = i_{fs} = 1mA$
 therefore $i_m = i_A \left(1 + \frac{R_m}{R_p} \right) \Rightarrow 10.0mA = 1mA \left(1 + \frac{50\Omega}{R_p} \right)$
 $R_p = 5.556\Omega$

- c) We want to measure up to 100.0mA ($i_m = 100mA$)
 At that i_m , we will reach full-scale $\rightarrow i_A = i_{fs} = 1mA$

$$i_m = i_A \left(1 + \frac{R_m}{R_p} \right) \Rightarrow 100mA = 1mA \left(1 + \frac{50\Omega}{R_p} \right)$$

In this problem:

Note that as more current need to be measured, R_p gets smaller to allow to "diverse" more current away


$R_p = 0.505\Omega$

2) The practical voltmeter uses a d'Arsonval

Galvanometer with a series resistance.

A large series resistance (R_s) allows to keep the current within the full-scale limit (i_{fs}).

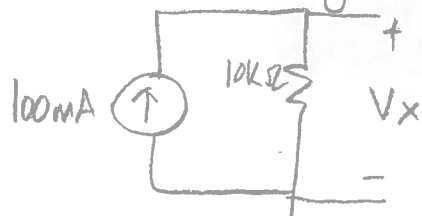
Recall that an ideal voltmeter doesn't draw any current. In practice, there is some current, leading to some errors in the measurement.



$$V_x = 10k\Omega \cdot 100mA = 1000V = 1KV$$

Ideally, we would find that $V_x = 1KV$. In practice, we don't measure exactly that value. Let's see what we get depending on the voltmeter we use.

Practical voltmeter

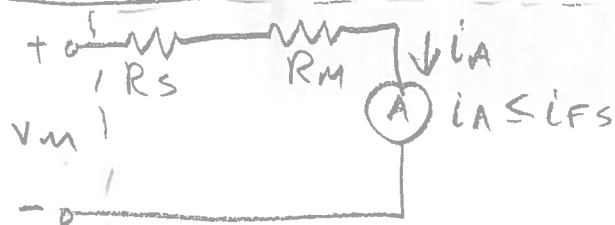

The relationship between i_A and V_m we use

$$V_m = i_A (R_s + R_m)$$

a) $R_m = 100\Omega$ and $i_{fs} = 50\mu A$ ($i_A = i_{fs}$ when $V_m = 100V$)
 $100V = 50\mu A (R_s + 100\Omega) \rightarrow R_s = 2M\Omega - 100\Omega \approx 2M\Omega$

$$R_s \approx 2M\Omega$$

When using that voltmeter

$$V_x = i_x \cdot 10k\Omega \quad i_x = 100mA \times \frac{2M\Omega}{2M\Omega + 10k\Omega}$$

$$i_x = 99.5mA$$

$$V_x = 995V$$

note: 5V lower than actual value

b) $R_m = 50\Omega$ ($i_{fs} = 1mA$) ($i_A = i_{fs}$ when $V_m = 100V$)

$$100V = 1mA (R_s + 50\Omega) \rightarrow R_s = 100k\Omega - 50\Omega \approx 100k\Omega = R_s$$

$$100k\Omega + 50\Omega \approx 100k\Omega$$

$$V_x = i_x \cdot 10k\Omega \quad i_x = 100mA \times \frac{100k\Omega}{100k\Omega + 10k\Omega}$$

$$i_x = 90.9mA$$

$$V_x = 909V$$

91V below ideal value!

