



Electric Circuits 1

ECSE 200A - 001

Monday, December 18, 2017, at 2:00 PM

EXAMINER: Prof. Odile Liboiron-Ladouceur

ASSOC. EXAMINER: Prof. Sharmistha Bhadra

STUDENT NAME:	SOLUTIONS	McGILL ID:											
---------------	-----------	------------	--	--	--	--	--	--	--	--	--	--	--

INSTRUCTIONS:



EXAM:	CLOSED BOOK <input checked="" type="checkbox"/> OPEN BOOK <input type="checkbox"/>	
	SINGLE-SIDED <input type="checkbox"/> PRINTED ON BOTH SIDES OF THE PAGE <input type="checkbox"/>	
	MULTIPLE CHOICE ANSWER SHEETS <input type="checkbox"/>	
	ANSWER IN BOOKLET <input checked="" type="checkbox"/> EXTRA BOOKLETS PERMITTED: YES <input checked="" type="checkbox"/> NO <input type="checkbox"/>	
	ANSWER ON EXAM <input type="checkbox"/>	
SHOULD THE EXAM BE: RETURNED <input checked="" type="checkbox"/> KEPT BY STUDENT <input type="checkbox"/>		
CRIB SHEETS:	NOT PERMITTED <input checked="" type="checkbox"/> PERMITTED <input type="checkbox"/> e.g. one 8 1/2X11 handwritten double-sided sheet <u>Specifications:</u>	
DICTIONARIES:	TRANSLATION ONLY <input type="checkbox"/> REGULAR <input type="checkbox"/> NONE <input checked="" type="checkbox"/>	
CALCULATORS:	NOT PERMITTED <input type="checkbox"/> PERMITTED (Faculty Standard Only) <input checked="" type="checkbox"/>	
ANY SPECIAL INSTRUCTIONS: e.g. molecular models		

Carefully read each question. There is a total of five questions. Write your answers in the exam booklet. Write your name on the exam booklet. Each question has multiple parts (a, b, c, d ...) to answer. Show the steps you take to find your answer and clearly indicate your answer. Write your answers using SI units and SI multipliers. Each question is worth 20 points for a total of 100 points.

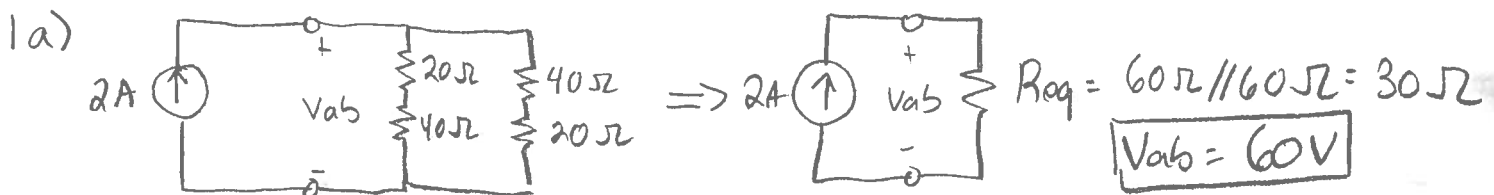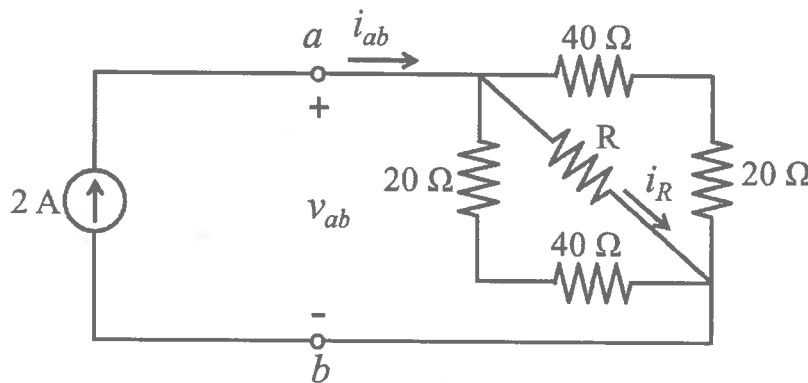Question 1



Consider the circuit shown below. Answer the following questions.

- What is the voltage v_{ab} if the resistance R is infinite ($R \rightarrow \infty$)?
- What is the current i_R through the resistor R if its resistance is zero ($R = 0 \Omega$)?
- What is the power delivered by the current supply if the resistance R is 60Ω ($R = 60 \Omega$)?
- Illustrate the relationship between the current i_{ab} and the voltage v_{ab} by plotting the i_{ab} - v_{ab} diagram of the circuit on the right side of the a-b terminals (i.e., disconnect the current supply). Clearly label your diagram. Assume the resistor R has a resistance R of 30Ω ($R = 30 \Omega$).



Extra Working Space

1 c)

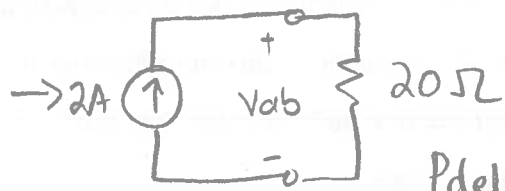
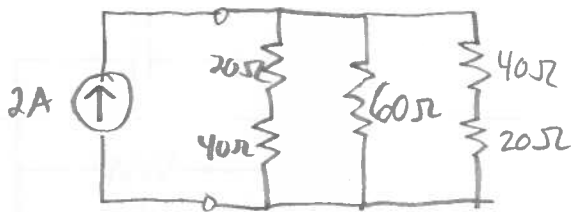


$$P_{del} = 2A \cdot V_{ab}$$


$$= 2A \cdot 2A \cdot 20\Omega$$

$$P_{del} = 80W$$

1 d)

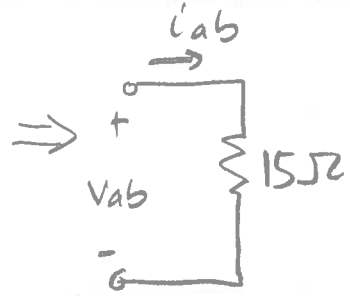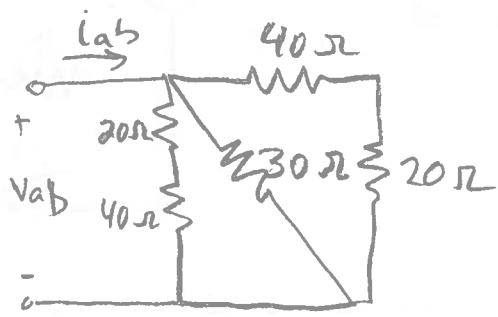



$$i_{ab} = \frac{V_{ab}}{15\Omega}$$

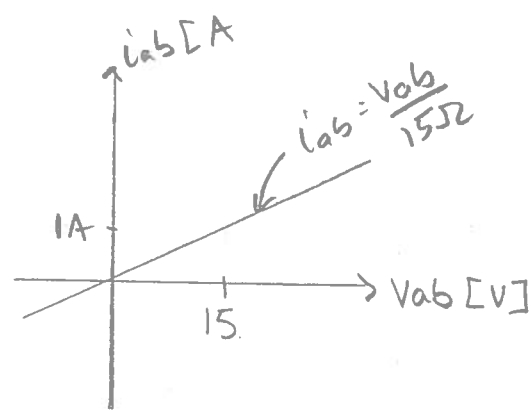

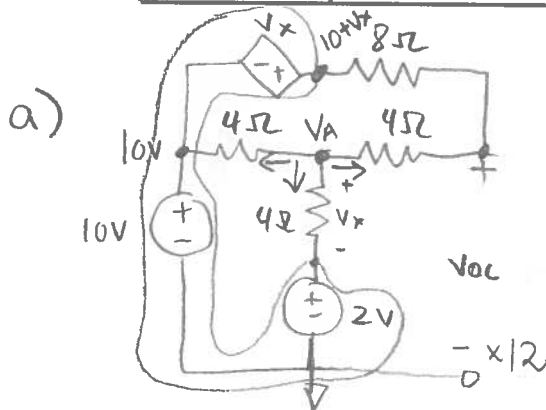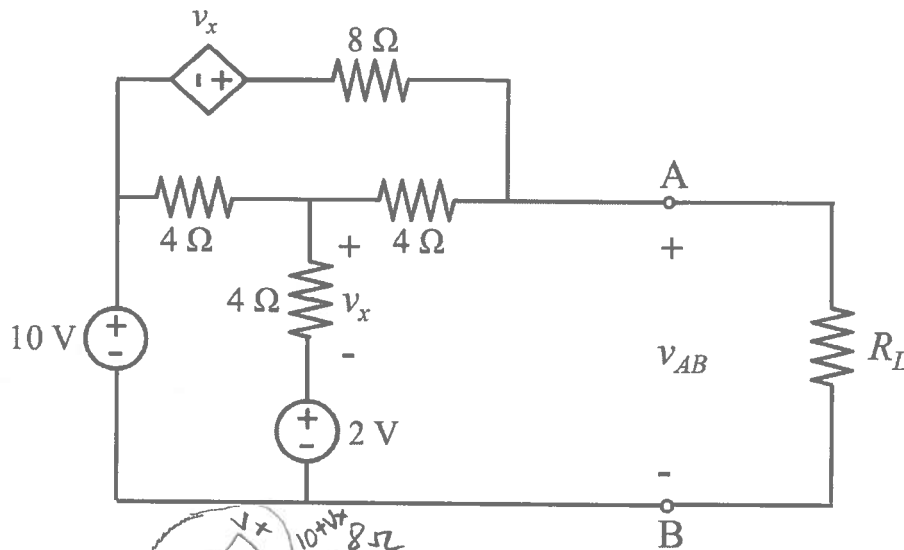Question 2

Consider the circuit shown below. Answer the following questions.

- What is the value of v_x when an open circuit is applied to terminals A and B ($R_L \rightarrow \infty$)?
- What is the value of v_x when a short circuit is applied to terminals A and B ($R_L \rightarrow 0$)?
- What is the Norton equivalent circuit with respect to the terminals A and B?
- What is the maximum power that the circuit can deliver to an optimally chosen load resistor R_L ?
- What should R_L be for maximum power transfer if the current i_{AB} is 1 A?



using nodal analysis
KCL to find node voltage V_A

Control variable
 $V_x = V_A - 2V$


$$\frac{V_A - 2V}{4\Omega} + \frac{V_A - 10V}{4\Omega} + \frac{V_A - (10 + V_x)}{4\Omega + 8\Omega} = 0$$

$$3V_A - 6V + 3V_A - 30V + V_A - 10 - V_A + 2V = 0$$

$$6V_A - 44V = 0 \quad V_A = \frac{22}{3}V$$

$$V_x = \frac{22}{3} - \frac{6}{3} = \frac{16}{3}V$$

b) $R_L = 0$

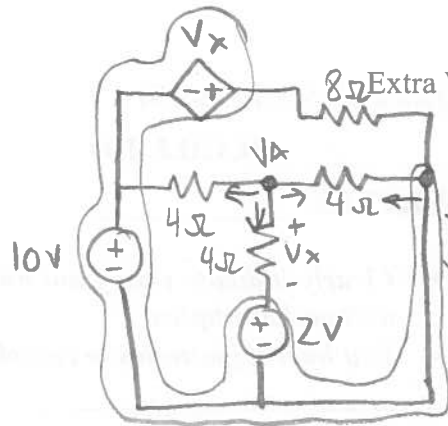

KCL to find V_A


$$\frac{V_A - 10V}{4\Omega} + \frac{V_A - 2V}{4\Omega} + \frac{V_A}{4\Omega} = 0$$

$$V_A - 10V + V_A - 2V + V_A = 0$$

$$3V_A = 12V \quad V_A = 4V$$

$$V_x = V_A - 2V = 2V$$

c) Norton equiv circuit:

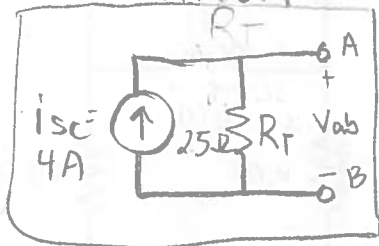


from conf. in b), find i_{sc}

$$\text{KCL at terminal A: } \frac{0V - 4V}{4\Omega} + i_{sc} + \frac{0 - 12V}{4\Omega} = 0$$

$$i_{sc} = \frac{16V}{4\Omega} = 4A$$

for R_T , find V_{oc} from part a)

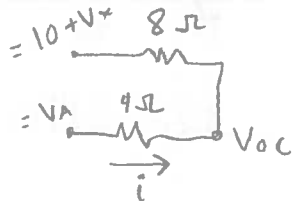

$$i = \frac{V_A - (10 + V_x)}{4\Omega + 8\Omega} = \frac{V_A - (10 + V_A - 2)}{12} = \frac{-10 + 2}{12} = -\frac{8}{12}A$$

$$i = -\frac{2}{3}A$$

$$\frac{V_A - V_{oc}}{4\Omega} = i \rightarrow V_A - 4i = V_{oc}$$

$$R_T = \frac{V_{oc}}{i_{sc}} = \frac{10V}{4A} = \frac{5}{2}\Omega = 2.5\Omega$$

$$\frac{22}{3} + 4 \cdot \frac{2}{3} = V_{oc}$$


$$V_{oc} = \frac{30V}{3} = 10V$$

~~Extra Working Space~~

d) $R_L = R_T = 2.5\Omega$
 \uparrow from part c)

$$P_{W_{max}} = \frac{V_{oc}}{2} \cdot \frac{i_{sc}}{2} = \frac{i_{sc} \cdot R_T \cdot i_{sc}}{4} = \frac{i_{sc}^2 \cdot R_T}{4} = \frac{4^2 \cdot 2.5}{4}$$

$$P_{W_{max}} = 10W$$

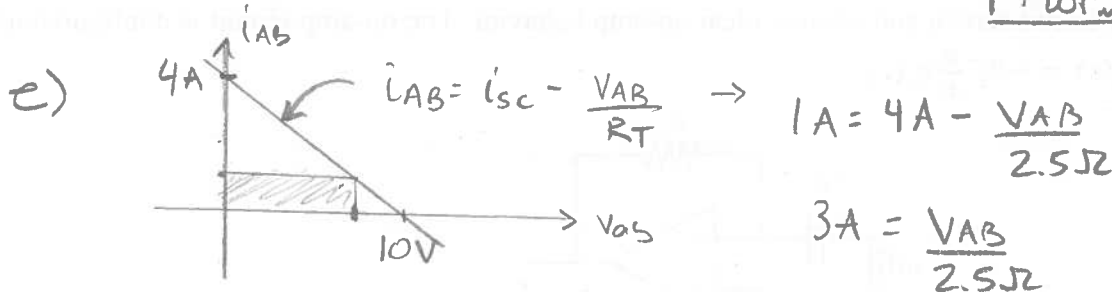


$$V_{AB} = 7.5V$$

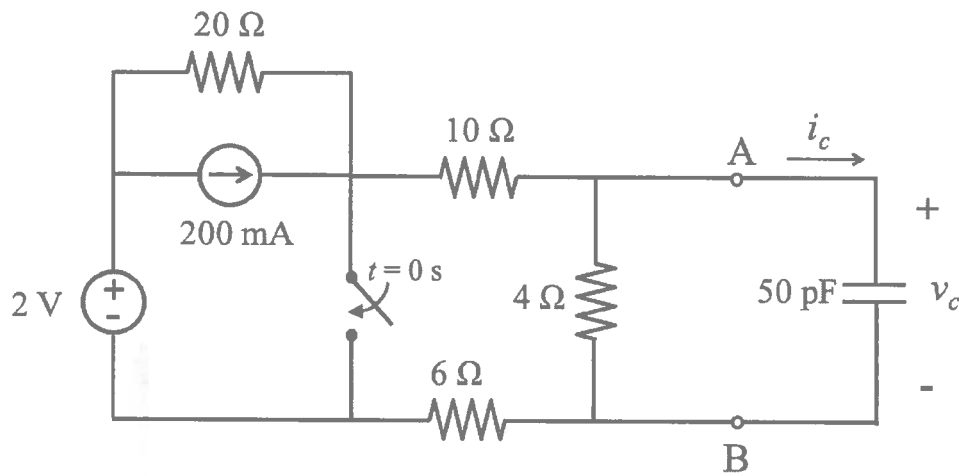
Question 3

Consider the circuit shown below. The circuit is in dc steady state for $t < 0$ s. The switch closes at $t = 0$ s. Answer the following questions.

- Draw the Thevenin equivalent circuit connected to the capacitor for $t < 0$ s.
- Draw the Thevenin equivalent circuit connected to the capacitor for $t > 0$ s.
- What is $v_c(t)$ for $t > 0$?
- What is $i_c(t)$ for $t > 0$?



3a) $t < 0$ s steady state

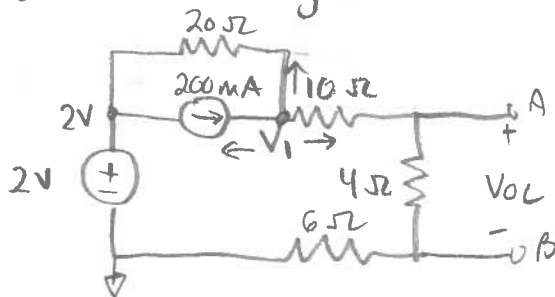

$$V_{oc} = 3V \cdot \frac{4\Omega}{20\Omega} = \frac{3}{5} V$$

only ind. src, so find V_{oc} , then R_T

$$V_{oc} = V_1 \cdot \frac{4\Omega}{6\Omega + 4\Omega + 10\Omega}$$

find V_1 with nodal analysis


$$-0.2A + \frac{V_1 - 2V}{20\Omega} + \frac{V_1}{20\Omega} = 0$$

$$\times 20 \rightarrow -4V + V_1 - 2V + V_1 = 0$$


$$2V_1 = 6V \rightarrow V_1 = 3V$$

Find R_T by shutting off supplies.

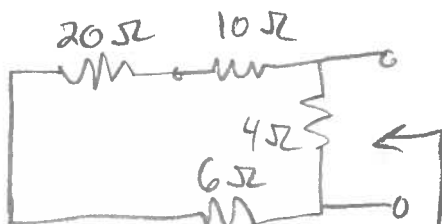
200mA \rightarrow 0A \rightarrow open
2V \rightarrow 0V \rightarrow short


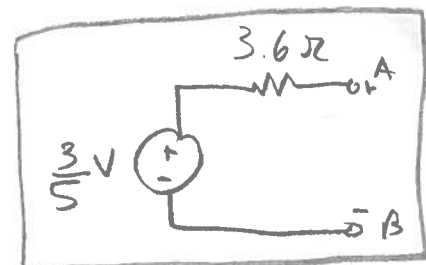
$$R_T = 4\Omega \parallel (20\Omega + 10\Omega + 6\Omega) = 3.6\Omega$$



b) $t > 0s$

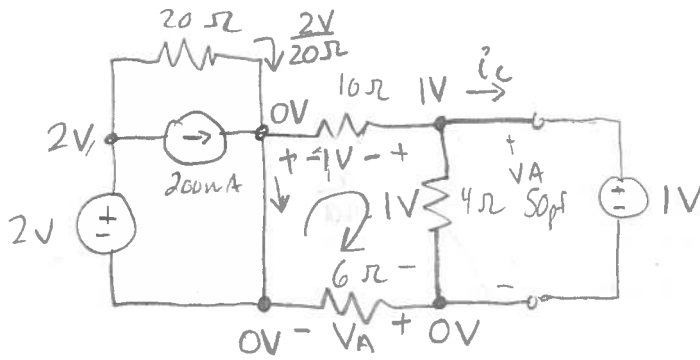


$$V_{oc} = 0V$$

$$i_{sc} = 0A$$


for a src of 1V.

$$KVL: -1V + 1V + V_A = 0 \rightarrow V_A = 0V$$
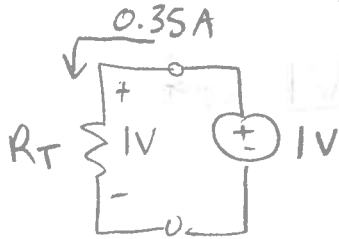
$$KCL: \frac{1V}{10\Omega} + \frac{1V}{4\Omega} + i_c = 0 \quad i_c = -0.1 + 0.25 = -0.35A$$




$$R_T = \frac{1V}{0.35A} = 2.857\Omega$$

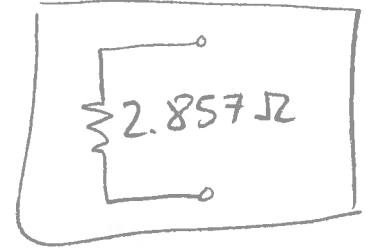

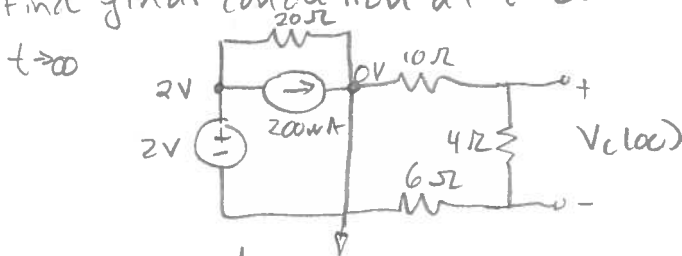c) Find initial condition using voltage continuity $V_c(0^-) = V_c(0^+)$

$$\text{from part a) } V_c(0^-) = V_c(0^+) = \frac{3}{5}V$$

Find final condition at $t \rightarrow \infty$



No current thru $4\Omega \rightarrow V_c(\infty) = 0V$

time constant

$$\tau = R_T C: \frac{100}{357} \cdot 50 \times 10^{-12} = \frac{1000}{7} \times 10^{-12} = \frac{1}{7} ns = 142.86 ps.$$

$$v_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-t/\tau} V, t > 0$$

$$V_c(t) = \frac{3}{5} e^{-\frac{7t}{ns}} V, t > 0$$

$$d) i = C \frac{dv}{dt}$$

$$i_c(t) = 50 \times 10^{-12} F \frac{d}{dt} \left[\frac{3}{5} e^{-\frac{7t}{ns}} \right]$$


$$= 30 \times 10^{-12} \cdot \left(-\frac{7}{10^{-9}} \right) e^{-\frac{7t}{ns}} = 210 \times 10^{-3} e^{-\frac{7t}{ns}}$$

$$i_c(t) = 0.21 e^{-\frac{7t}{ns}} A \quad t > 0$$

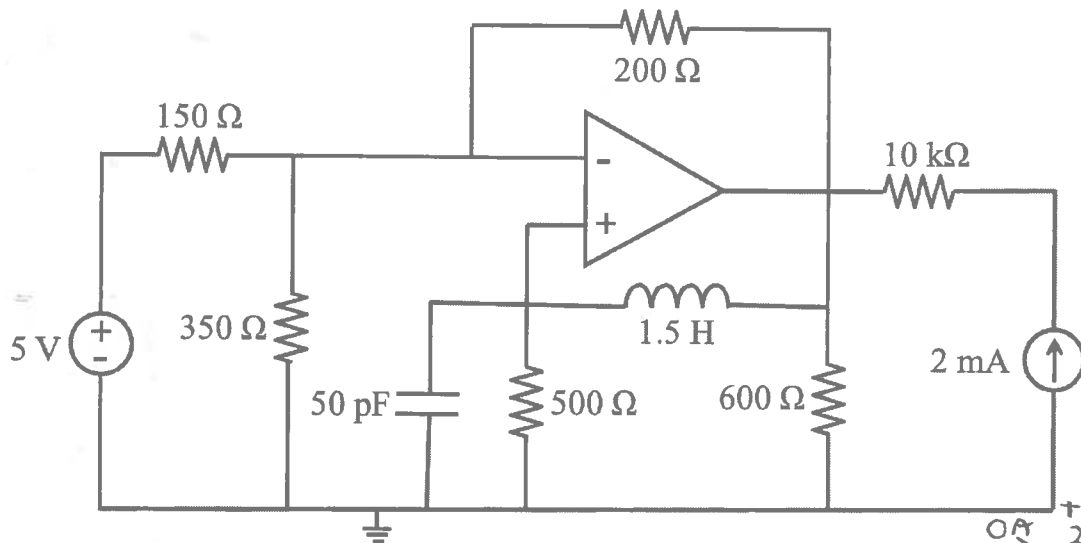Question 4

Consider the circuit shown below. Assume that the operational amplifier is ideal and that the circuit is in dc steady state. Answer the following questions.

- What is the power supplied by the current source and the voltage source?
- What is the resistor that dissipates the most power?
- What is the electrical energy absorbed by the $500\ \Omega$ in one second?
- What is the energy stored by the capacitor and by the inductor?



a) Redraw for steady state


$$i = \frac{5V}{(150+350)\Omega} = 10\text{ mA}$$

Power supplied
by 5V
supply: 50 mW

$$V_A = 10\text{ mA} \cdot 350\Omega = 3.5\text{ V}$$

$$V_O - V_A = 2\text{ mA} \cdot 10\text{ k}\Omega = 20\text{ V} \rightarrow V_O = 23.5\text{ V}$$

Power supplied by current source: 47 mW

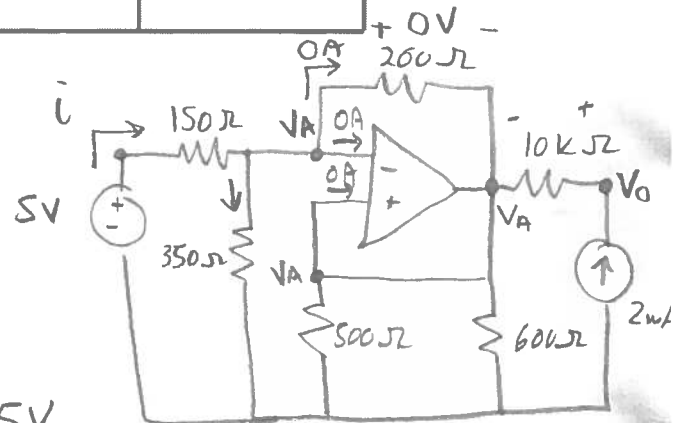

b) Pwr: $V \cdot I = I^2 R$ or $\frac{V^2}{R}$

$$150\Omega: (10\text{ mA})^2 \cdot 150\Omega = 15\text{ mW}$$

$$350\Omega: (10\text{ mA})^2 \cdot 350\Omega = 35\text{ mW}$$

$$500\Omega: \frac{(3.5\text{ V})^2}{500\Omega} = 24.5\text{ mW}$$

$$600\Omega: \frac{(3.5\text{ V})^2}{600\Omega} = 20.42\text{ mW}$$

$$10\text{ k}\Omega: \frac{(20\text{ V})^2}{10\text{ k}\Omega} = 40\text{ mW}$$

10 kΩ


Extra Working Space

c) $\frac{dU}{dt} = \text{power} \rightarrow U(t) = \int_0^{1s} p(t) dt = \int_0^1 24.5 \text{ mW} dt$

↑
constant
in steady
state

$U = 24.5 \text{ mJ}$

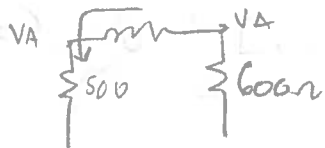d) $U = \frac{1}{2} C V^2 = \frac{1}{2} 50 \times 10^{-12} (3.5 \text{ V})^2 = \boxed{306.25 \text{ pJ}}^{\text{cap}}$



$U = \frac{1}{2} L i^2 = \frac{1}{2} 1.5 \text{ H} \left(\frac{3.5 \text{ V}}{500 \Omega} \right)^2 = \boxed{36.75 \mu\text{J}}^{\text{inductor}}$