

ECSE-200 Electric Circuits 1  
Quiz #6 (Feb. 22, 2019)



LAST NAME \_\_\_\_\_ MCGILL ID# \_\_\_\_\_

FIRST NAME \_\_\_\_\_ SIGNATURE \_\_\_\_\_


- Only Faculty standard calculator accepted
- No cellphone allowed
- Show all your work
- Clearly indicate your final answer with the SI unit and multiplier
- You have 45 minutes to complete this quiz

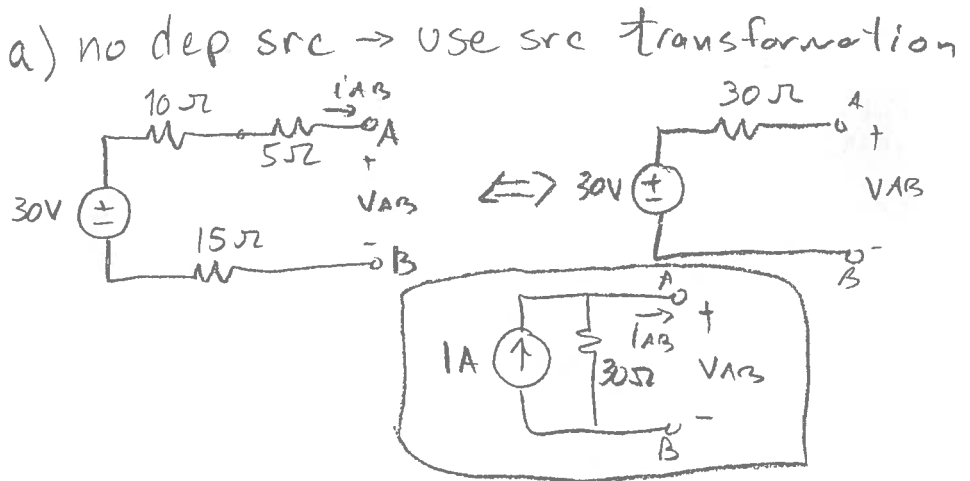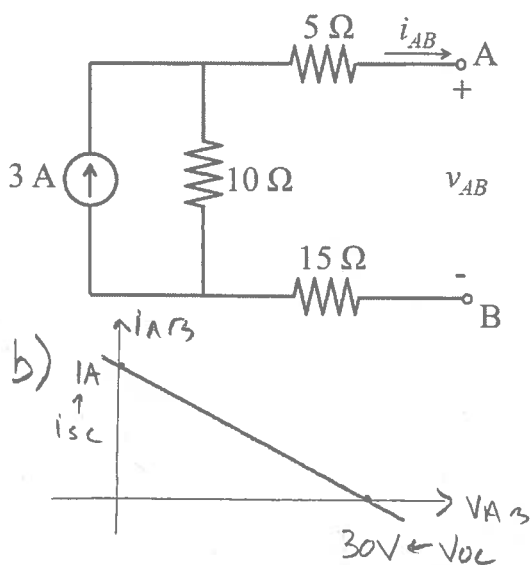**Question 1:** Consider the circuit shown. Answer the following questions.

- Find and draw the Norton equivalent circuit of the circuit. [2 pt]
- Draw the  $i_{AB} - v_{AB}$  diagram indicating the open-circuit voltage ( $v_{OC}$ ) and the short-circuit current ( $i_{SC}$ ). [2 pt]
- What is the value of the power delivered by the independent current supply of the circuit shown (i.e., the 3 A supply) if a short-circuit connects terminals A and B? [1 pt]
- What is the current value  $i_{AB}$  at the terminals A and B if a load resistance equal to the Thévenin resistance is connected across terminals A and B? [1 pt]



c)  $R_L = 0$

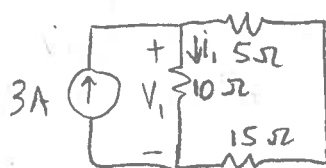

$$P_{wr} = 3A \times V_1 \quad V_1 = 10\Omega i_1 = 10\Omega \left( \frac{3A(5\Omega + 15\Omega)}{(10\Omega + 5\Omega + 15\Omega)} \right)$$

$$V_1 = 20V$$



**Pwr delivered 60W**

d)  $R_L = R_T = 30\Omega$

$$i_{AB} = 0.5A$$

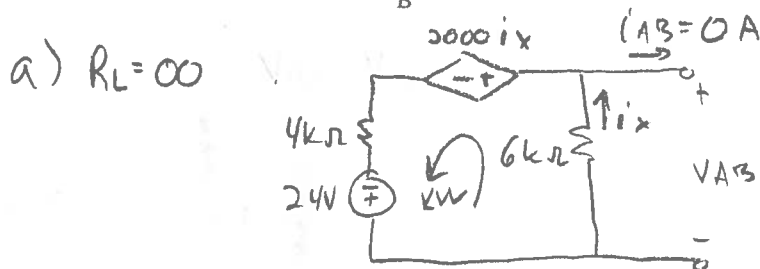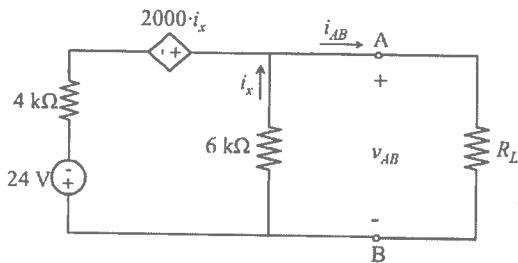**Question 2:** Consider the circuit shown below. Answer the following questions.


- As shown, a load resistance  $R_L$  is connected across the terminals A and B. What is the voltage value  $v_{AB}$  if the load resistance  $R_L$  is replaced with an open-circuit (i.e.,  $R_L \rightarrow \infty$ )? [2 pt]
- What is the current value  $i_{AB}$  if the load resistance  $R_L$  is replaced by a short-circuit (i.e.,  $R_L = 0 \Omega$ )? [2 pt]
- Replace and redraw the part of the circuit to the left of terminals A and B by its Thévenin equivalent circuit. Clearly indicate the open-circuit voltage ( $v_{OC}$ ) value and the Thévenin resistance value ( $R_T$ ). [2 pt]
- What should the resistance value  $R_L$  be for the current at the terminal be  $-2 \text{ mA}$  ( $i_{AB} = -2 \text{ mA}$ )? [2 pt]



$$\begin{aligned} \text{KVL} \quad 6000 i_x + 2000 i_x + 4000 i_x - 24 \text{ V} &= 0 \\ 12,000 i_x &= 24 \text{ V} \\ i_x &= 2 \text{ mA} \end{aligned}$$

$$V_{AB} = -i_x \cdot 6 \text{ k}\Omega = -12 \text{ V}$$

$$\boxed{V_{AB} = -12 \text{ V}}$$

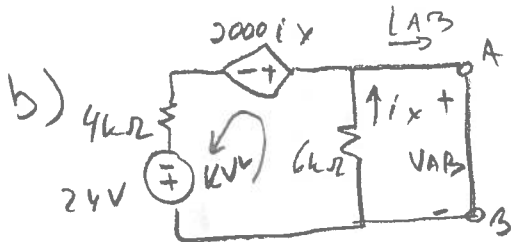


$$i_x = 0 \text{ A b/c of } V_{AB} = 0 \text{ V}$$

$$\begin{aligned} \text{KVL:} \quad 2000(0) + 4000(-i_{AB}) - 24 \text{ V} + 6000(0) &= 0 \\ 4000 i_{AB} &= -24 \text{ V} \end{aligned}$$

$$\boxed{i_{AB} = -6 \text{ mA}}$$

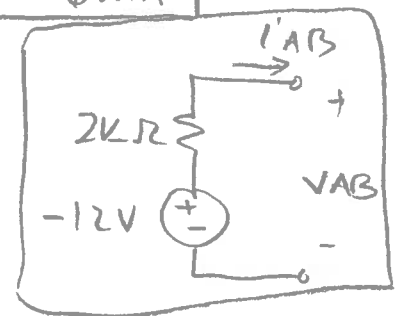c) from a) & b)  $R_T = \frac{V_{OC}}{i_{SC}} = \frac{-12 \text{ V}}{-6 \text{ mA}} = 2 \text{ k}\Omega$



d)  $V_{AB} = V_{OC} - i_{AB} R_T$

$$V_{AB} = -12 \text{ V} - (-2 \text{ mA})(2 \text{ k}\Omega) = -12 \text{ V} + 4 \text{ V} = -8 \text{ V}$$

$$R_L = \frac{+V_{AB}}{i_{AB}} = \frac{+(-8 \text{ V})}{-2 \text{ mA}} = 4 \text{ k}\Omega$$

$$\boxed{R_L = 4 \text{ k}\Omega}$$