



ECSE-200 Electric Circuit 1
Quiz #1 (Jan. 18, 2019)

LAST NAME SOLUTIONS MCGILL ID# _____

FIRST NAME _____ SIGNATURE _____

- Carefully read the questions
- Show all your work
- Clearly indicate your final answer
- Plagiarism will have important consequences
- Answer must provide the appropriate symbol for the multiplier and SI unit where applicable
- Only Faculty standard calculators are accepted
- You have 45 minutes to complete this quiz

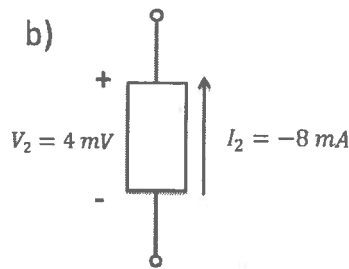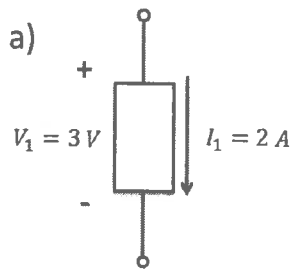Question 1. Consider the four circuit elements below. For each circuit element, indicate the power that is being delivered or absorbed by the element. [2 pts / element \times 3 elements = 6 pts].





a) (passive sign convention) $P_1 = V_1 \cdot I_1 = 3V \cdot 2A = 6W$ $[+]$
power is absorbed $[+]$

b) $P_2 = V_2 \cdot I_2 = 4 \times 10^{-3}V \cdot (-8 \times 10^{-3}A)$
 $= -32 \times 10^{-6}W$
 $= -32 \mu W$ $[+]$

(not following passive sign convention)

$32 \mu W$ power absorbed $[+]$

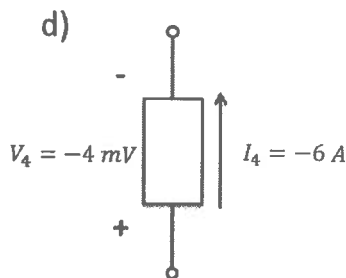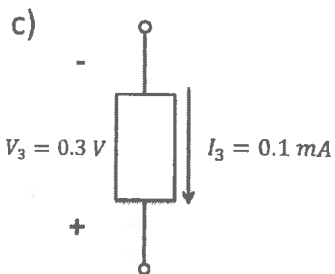

c) (not following passive sign conv.)

$P_3 = V_3 \cdot I_3 = 0.3V \cdot 0.1 \times 10^{-3}A$
 $= 0.03 \times 10^{-3}W$
 $= 30 \mu W$


power is delivered $[+]$

d) (passive sign conv.)

$P_4 = (-4 \times 10^{-3}V) \cdot (-6A)$
 $= 24 \times 10^{-3}W$

$24mW$ power is absorbed $[+]$

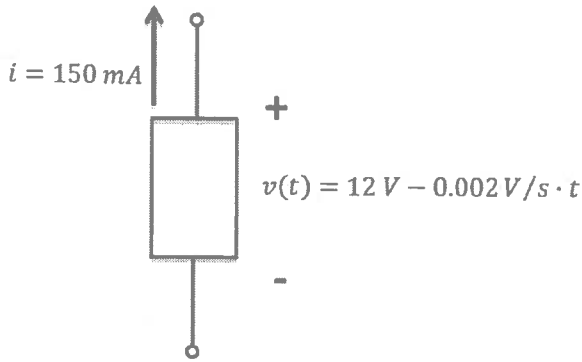Question 2. Consider the circuit element below which represents a battery. Answer the questions.



- (a) What is the instantaneous power $p(t)$ delivered by the battery at time $t = 500$ s? [2 pts]
- (b) What is the energy delivered by the battery over the time interval $0 \text{ s} \leq t \leq 500 \text{ s}$? [3 pts]
- (c) How much charges will exit the battery from the + terminal at the end of the time interval over the time interval $0 \text{ s} \leq t \leq 500 \text{ s}$? [2 pts]

$$a) p(t) = i \cdot v(t) = 150 \times 10^{-3} \text{ A} (12 \text{ V} - 0.002 \text{ V/s} \cdot t) \quad [+1]$$

$$= 1800 \times 10^{-3} \text{ W} - 0.3 \times 10^{-3} \frac{\text{W}}{\text{s}} \cdot t$$

$$p(t=500 \text{ s}) = 1.8 \text{ W} - 0.3 \frac{\text{mW}}{\text{s}} \cdot 500 \text{ s}$$

$$= 1.8 \text{ W} - 150 \text{ mW} = \boxed{1.65 \text{ W}} \quad [+1]$$

$$b) U(t_2) - U(t_1) = \int_{t_1}^{t_2} p(t) dt = \int_{0 \text{ s}}^{500 \text{ s}} (1.8 \text{ W} - 0.3 \frac{\text{mW}}{\text{s}} \cdot t) dt \quad [+1]$$


$$U(500 \text{ s}) - U(0 \text{ s}) = \left(1.8 \text{ W} t - \frac{1}{2} 0.3 \frac{\text{mW}}{\text{s}} \cdot t^2 \right) \Big|_0^{500 \text{ s}} \quad [+1]$$

$$= 900 \text{ J} - 37.5 \text{ J} = \boxed{862.5 \text{ J}} \quad [+1]$$

$$c) I = \frac{dQ}{dt} \quad [+1] \quad I = 150 \text{ mA} \quad \Delta t = 500 \text{ s}$$

$$Q = 150 \times 10^{-3} \text{ A} \cdot 500 \text{ s} = \boxed{75 \text{ C}} \quad [+1]$$

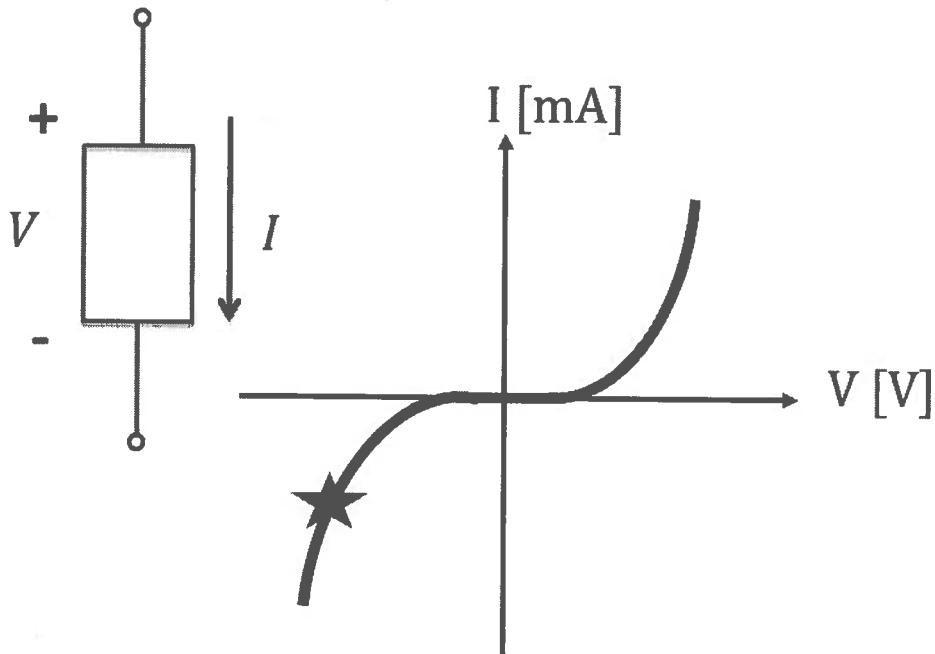Question 3. Consider the I-V diagram for the circuit element shown. Write if the statement is true or false.



- a) The circuit element is not a linear circuit element [1 pt]. TRUE
- b) The circuit element is a passive element. [1 pt] TRUE
- c) The element delivers energy at the star, which indicates a measurement made. [1 pt] FALSE